

ELECTRICAL

Engineering

KAIZEN
TEAM

Fundamentals of Electrical Engineering Circuits

2.1 Charge, current, Kirchoff's current law

The fundamental electric quantity is charge, the smallest amount of charge that exists is the charge carried by an electron

$$q_e = -1.602 \times 10^{-19} \text{ C} \quad q_p = +1.602 \times 10^{-19} \text{ C}$$

Electric current: the time rate of change of charge passing through a predetermined area (usually a cross section of a metal wire)

$$i = \frac{\Delta q}{\Delta t}$$

$\Delta q \Rightarrow$ units of charge through cross-sectional Area
 $\Delta t \Rightarrow$ units of time ; $i \Rightarrow$ current

Ampere: unit of current = 1 ampere = 1 coulomb / second

* the positive direction of current flow is that of positive charges. theoretical ↘

Kirchoff's current law: because charge can't be created or destroyed must be conserved "the sum of the current at a node must equal zero" [node: junction of two or more conductors]

Voltage (potential difference): the total work per unit charge associated with the motion of charge btw 2 points $V = \text{joule / coulomb}$


Source: elements that provide Energy


Load: elements that dissipate Energy

⊕ source

⊖ load

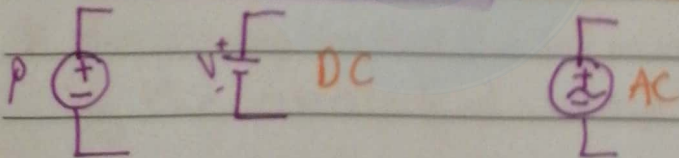
ideal voltage source: provide a prescribed voltage across its terminals irrespective of the current flowing through it. The amount of current supplied by the source is determined by the circuit connected to it "active element"



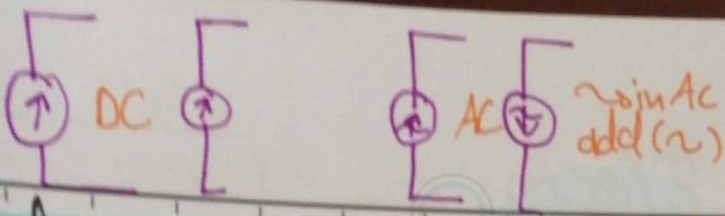

ideal current source: provides a prescribed current to any circuit connected to it, the voltage generated by the source is determined by the circuit connected to it

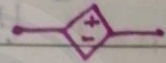dependent or controlled sources: whose output (current or voltage) is a function of some other voltage or current



power the rate at which energy is expended $P = I V$

Electric circuit has 3 components

- 1- source of power ex: battery \Rightarrow voltage or current source
- 2- load (appliance) ex: light bulb \Rightarrow Resistance, inductor capacitor.
- 3- inter connection ex: wires & cables

units desired to find in electric currents.

- 1- Voltage ^{derived} 2- current ^{Basic} 3- Power ^{derived}


SI Prefixes


- | | | | |
|-----------------------|---------------------------|----------------------|-------------------|
| T - Tera - 10^{12} | G - Giga - 10^9 | M - mega - 10^6 | k - kilo - 10^3 |
| m - milli - 10^{-3} | μ - micro - 10^{-6} | n - nano - 10^{-9} | |

Coulomb = $A \times sec$

2 ways to show a current ^{\rightarrow + voltage} 1- quantity & direction

There are 2 types of current sources

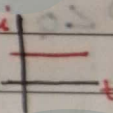1) Direct current (DC) \Rightarrow remains constant with time 

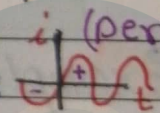2) Alternating current (AC) \Rightarrow varies sinusoidally with time ^(periodic) 

* Also in voltage you have 2 types DC [Battery] & AC

$V_{ab} = V_a - V_b = (-V_{ba}) = V_b - V_a$

* my referce is the +ve sign and that's where i begin.

* the assumption that the terminal + polarity is higher than - polarity by the amount of voltage drop; if -ve don't change your assumption

V → Volt
 I → Amp
 P → W

Vid #2
 week 1

Third Quantity: Power

Power: The rate of change of energy per unit time (Watts)


$$P = \frac{dw}{dt} = I V \Rightarrow \text{derived from voltage}$$

Classification of circuit components

- 1) Passive components: absorb power, resistor, inductor, capacitor
- 2) Active components: deliver power, battery, source of power

Passive Sign Convention

$$P = \pm V_{ab} \times I_{ab}$$

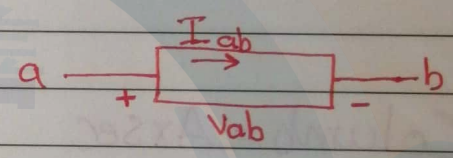

(+) → if current enters positive (-) → if current enters negative

if $P \geq 0 \Rightarrow$ passive \Rightarrow absorbs power


if $P < 0 \Rightarrow$ Active \Rightarrow delivers power (absorbing negative power)

Example: find the power (Generated or absorbed)

$$P = \pm VI$$

enters negative $\Rightarrow -$	enters negative (-)	enters positive (+)	enters positive (+)
$P = (-)4 \times 3 = -12W$	$P = (-)4 \times 3 = -12W$	$P = (+)4 \times 3 = 12W$	$P = (+)4 \times 3 = 12W$
supplies 12W	supplies 12W	absorbs 12W	absorbs 12W

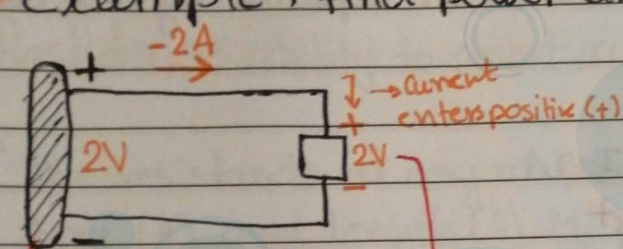Example: find power and determine (supply/absorb)




current enters negative (-)

$$P = (-) 2 \times (-2) = 4W$$

absorb power

$$\Sigma P = 0; \text{ element 2} = -4W$$
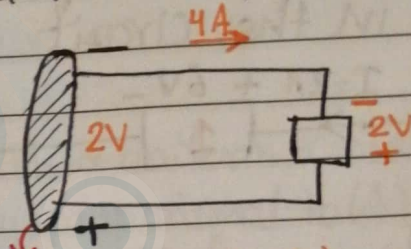
$$P = (+) (-2) \times (2) = -4W \checkmark$$



enters positive (+)


$$P = (+) (2) \times (4) = 8W$$

absorb power

$$\text{element 2 must be } -8W$$

$$P = (-) (2) \times (4) = -8W \checkmark$$

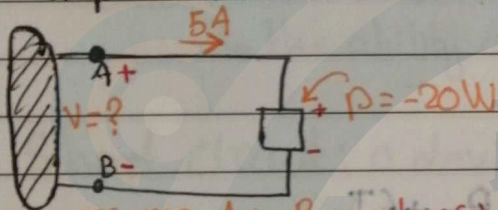Example: determine unknown voltage or current.



assume A+, B-; enters (+)


$$P = (+) V_{AB} \times 5 = -20$$

$$V_{AB} = -4V$$

voltage in B is higher

you can assume whatever

(+/-) you want; but stick to it.

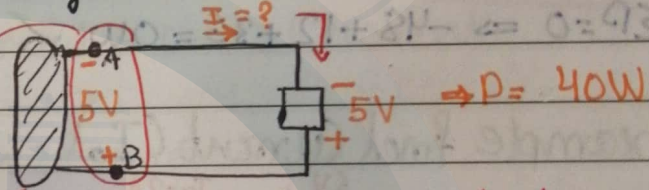

in here polarity is ready; don't assume

current enters negative

$$P = (-) 5 \times I = 40W$$

$$I = -8A$$


$$V_{BA} \Rightarrow V_B - V_A = 5V$$

Instantaneous power $P(t) = v(t) i(t)$

Energy absorbed or supplied by an element from t_0 to t


$$W = W(t_0 - t) = \int_{t_0}^t p(\tau) d\tau = \int_{t_0}^t v(\tau) i(\tau) d\tau$$

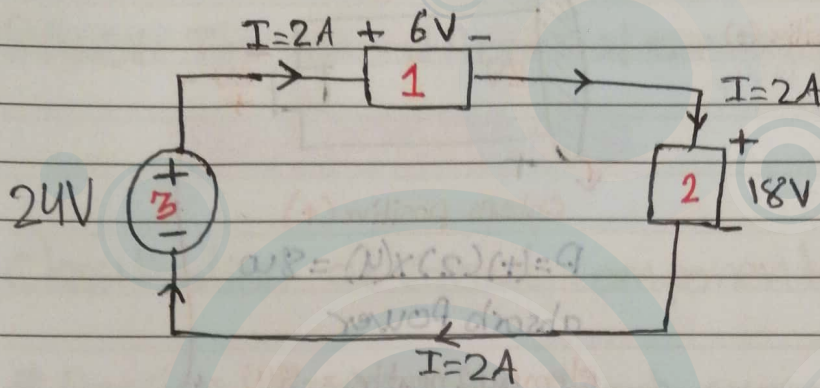Example: determine power absorbed or supplied by each element in the circuit



Element 3 \Rightarrow current enters negative (-) $P = (-)(24)(2) = -48W$ supply
 Element 1 \Rightarrow current enters (+) $P = (+)(6)(2) = +12W \Rightarrow$ absorb
 Element 2 \Rightarrow current enters (+) $P = (+)(18)(2) = +36W \Rightarrow$ absorb
 $\therefore \Sigma P = 0 \Rightarrow -48 + 12 + 36 = 0W \checkmark$

Example find current (I_0)

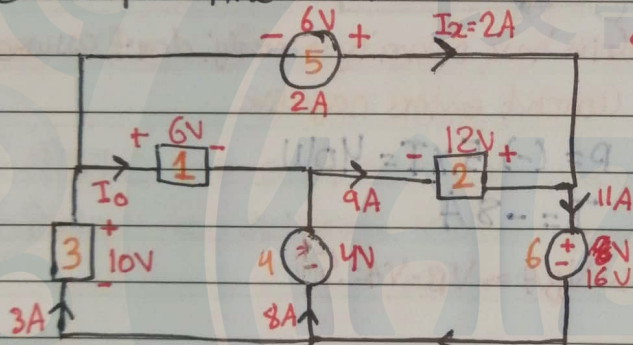

Element 1 $\Rightarrow P_1 = +6I_0$

$$P_2 = -12 \times 9 = -108W$$

$$P_3 = -3 \times 10 = -30W$$



$$P_4 = -4 \times 8 = -32W$$

$$P_5 = -2 \times 6 = -12W$$

$$P_6 = 11 \times 16 = 176W$$

$$\Sigma P = 0 \Rightarrow 6I_0 - 108 - 30 - 32 - 12 + 176 = 0 \Rightarrow 6I_0 - 6 = 0, I_0 = -1A$$

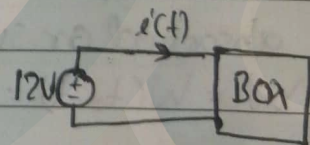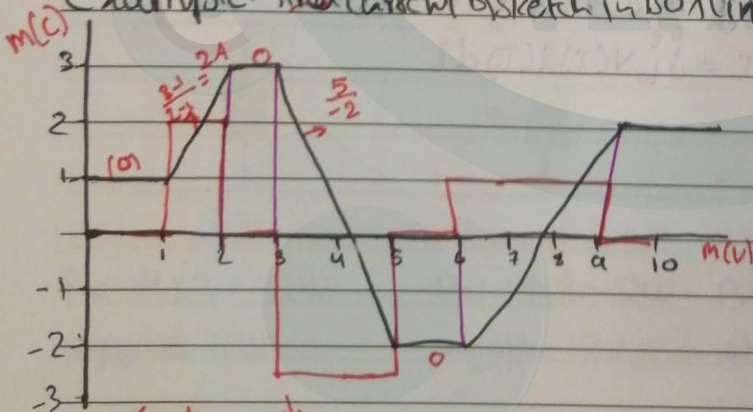Example: find current sketch in Box (inst)




Final slope in each point and that's P/V

Resistance

vid #1
week 2.

Resistance: ability to resist current. Ω OHM

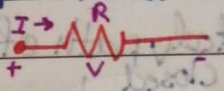"The resistance of any material with a uniform cross-section (Area (A) and length (l)) is inversely proportional to (A) and directly proportional to (l)" $R \propto l/A$ $R = \rho \frac{l}{A}$



Resistance always has absorbed power that turns to heat energy

OHM's Law: $V = IR$ $P = V^2/R$ always positive


Conductivity $G = 1/R$ Siemens (S) or mho (Υ)
↳ the ability of an element to conduct current

$$P = I^2 R$$

Short circuit: a device with zero resistance


Open circuit: a device with zero conductance (∞ resistance)

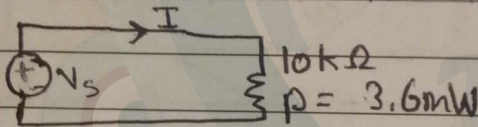Example: the power absorbed by the $1k\Omega$ resistor in the following circuit is $3.6mW$, Determine voltage & current in the circuit.




$$P = I^2 R; 3.6m = I^2 \cdot 10k; I = 0.6mA$$
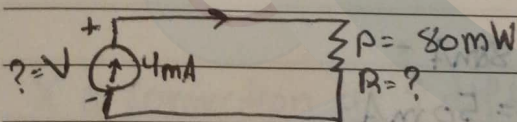
$$V = IR; 6 \times 10^{-4} \times 10 \times 10^3 = 6V$$



$$P = I^2 R; 80m = (4mA)^2 \cdot R$$

$$V_s = IR$$

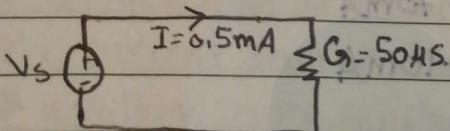

$$G = 1/R \Rightarrow R = 1/50m = 20\Omega$$

$$P = I^2 R, V = IR$$

Nodes

Node (true node) is the point of connection of three or more circuit elements

binary node (b-node) has only 2 components connected to it

Branch: part of the circuit - collection of elements

loop: repeatedly path of the current that does not cross any closed true nodes but once

- that means that it starts and ends at the same point

Mesh: a path that does not include a smaller path in it

Series & Parallel connections

Series: when two or more elements are connected and they belong to the same branch $\frac{+}{-}$ Same I , different V


Parallel: when two or more elements are connected btw the same 2 true nodes \parallel Same V , different I

Kirchhoff's Current Law (KCL): The Algebraic sum of the currents entering a node (or a closed boundary) is zero

$$\sum I_{in} = \sum I_{out}$$

$$I_1 + I_2 = I_3 + I_4$$

Example: find the unknown currents

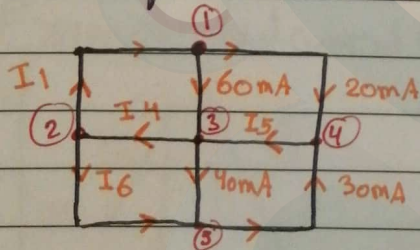

node 1 $\Rightarrow I_1 = 60 + 20 = 80 \text{ mA}$

node 4 $\Rightarrow 30 + 20 = I_5 = 50 \text{ mA}$

node 3 $\Rightarrow 50 + 60 = 40 + I_4 = 70 \text{ mA}$

node 2 $\Rightarrow 70 = 80 + I_6 = -10 \text{ mA}$


loop direction
clockwise

Kirchhoff's Voltage Law (KVL) the algebraic sum of the voltage in any closed path or loop is zero

sum of voltage drops = sum of voltage rises

* i choose a point and go clockwise, if enters from (negative) the voltage is negative and vice versa; the same applies to $(I \times R)$

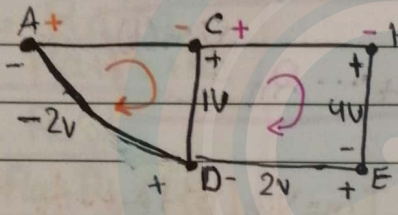
Example: Find V_{AC} & V_{CH} in the following circuit



$$+V_{AC} + 1 + 2 \Rightarrow V_{AC} = -3V$$

$$+V_{CH} + 4 + 2 - 1 = 0 \Rightarrow V_{CH} = -5V$$

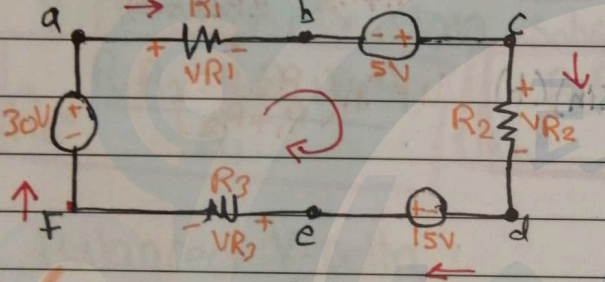
Example: $V_{R1} = 26V$, $V_{R2} = 14V$; Find V_{R3}



$$-30 + 26 - 5 + 14 - 15 + V_{R3} = 0$$

$$V_{R3} = -10V$$

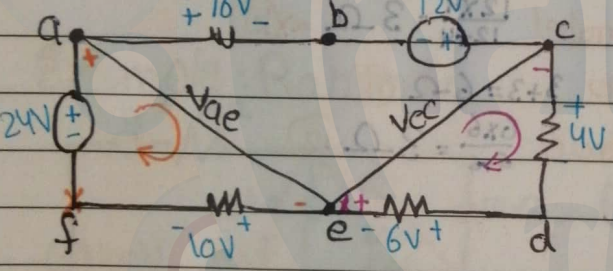Example: Find V_{ae} & V_{ec} ; $V_{ae} = V_a - V_e$



$$-24 + V_{ae} + 10 = 0$$

$$V_{ae} = 14V$$

$$V_{ec} + 4 + 6 = 0$$

$$V_{ec} = -10V$$

- * a connection of 2 different current sources in series is impossible
- * a connection of 2 different voltage sources in parallel is impossible
- * a current source supplying zero current is equivalent to an open circuit
- * a voltage source supplying zero Volt is equivalent to a short circuit

Voltage, Current Division

Series Resistors

"The sum of resistors in series is the sum of resistors"

same current

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

Voltage Division \rightarrow must be series

"In a series combination of n resistors, the voltage drop across the resistor $R_j, j=1, 2, \dots, n$ is

$$V_j(t) = \frac{R_j}{R_1 + R_2 + \dots + R_n} V_{in}(t)$$

Parallel Resistors

same voltage

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$I_{in} = V_{in} \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2} \quad \leftarrow 2 \text{ Res only}$$


Current Division

must be parallel

$$i_j(t) = \frac{G_j}{G_1 + G_2 + \dots + G_n} i_{in}(t)$$

$$i_1 = i_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$

Example:

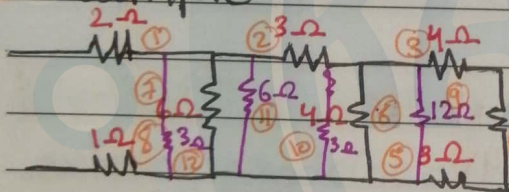

(3) + (4) + (5) series $4 + 5 + 3 = 12 \Omega \Rightarrow (7)$

(9) + (6) \Rightarrow parallel $\frac{12 \times 4}{12 + 4} = 3 \Omega = (10)$

(2) + (10) \Rightarrow series $3 + 3 = 6 \Omega (11)$

(11) + (7) \Rightarrow parallel $\frac{6 \times 6}{6 + 6} = 3 \Omega (12)$

(1) + (12) + (8) \Rightarrow series $2 + 3 + 1 = 6 \Omega = R_{eq}$

$\pi \rightarrow Y$

$\Delta \rightarrow \pi$


Y & Delta Networks

↳ a three terminal connection

Delta-Y Conversion

Solving for R_1, R_2, R_3

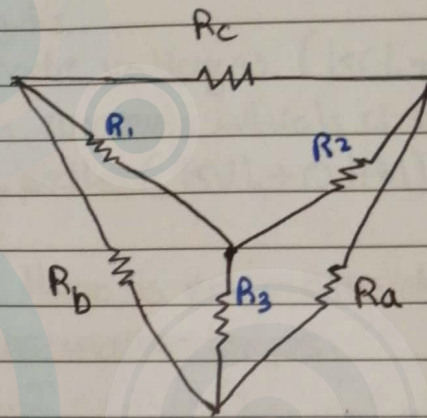$\Delta \rightarrow Y$
 $\pi \rightarrow Y$



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Y-Delta Conversion, solving for R_a, R_b, R_c

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Balanced Y-Delta

when $R_1 = R_2 = R_3 = R_Y$ & $R_a = R_b = R_c = R_\Delta$ then $R_Y = \frac{R_\Delta}{3}$ or $R_\Delta = 3R_Y$

Example: Rabandi

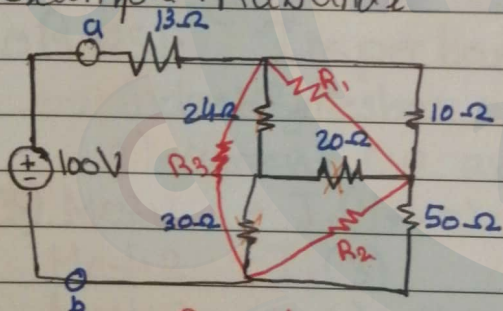

*changing $\Delta \rightarrow Y$ won't do me any good.

* $Y \rightarrow \Delta$ will simplify to series & parallel

$$R_1 = \frac{(24 \times 20) + (20 \times 30) + (30 \times 24)}{30} = 60 \Omega \rightarrow \frac{1800}{30}$$

$$R_2 = \frac{1800}{24} = 75 \Omega$$

$$R_3 = 1800/20 = 90 \Omega$$

now R_1 and 10Ω parallel $\Rightarrow \frac{60 \times 10}{70} = 8.571 \Omega$

R_2 and 50Ω parallel $\Rightarrow \frac{75 \times 50}{75 + 50} = 30 \Omega$

$30 + 8.571 = 38.571 \Omega$ // with R_3

$$\frac{90 \times 38.57}{90 + 38.57} = 26.99 \Omega \text{ series with } 13 = \boxed{39.99 \Omega}$$

$$i = \frac{V}{R} = \frac{100V}{39.99 \Omega} = 2.5 A$$

ch3 Mesh Analysis

Week 3 p. 11

2) Methods for circuit analysis

- 1) Nodal analysis to find all node voltages (KCL + OHM)
- 2) Mesh analysis: to find mesh currents which circulate around closed path (KVL + OHM)

* Mesh is a mesh if & only if there is no loop inside it

* a loop is a loop even if it contains smaller loops.

Mesh analysis procedure


- 1) identify the meshes j different.
- 2) suppose each mesh contains a current "CW"
- 3) apply KVL to each mesh $V_1 + V_2 + RI + \dots$
 * keep in mind that i will have an element with 2 mesh currents $(I_1 - I_2) \Rightarrow I_1$ my current mesh current $I_2 \Rightarrow$ the other mesh current moving in the opposite direction
- 4) you will then have j number of equations with j no. of meshes and j no. of unknowns (currents)
- 5) use simultaneous equations to solve or matrices

OR USE Inspection Method must all be voltage sources or at least no shared current source between meshes.

- 1) identify meshes
- 2) current CW and you move CW
- 3) Mesh 1 $+ I_1(4+3+2) - I_2(3+2) - I_3(0) - 7V = 0$
 Mesh 2 $- I_1(3) + I_2(3+2+2) - I_3(2+2) - 3V = 0$
 Mesh 3 $- I_1(0) - I_2(2+2) + I_3(6+2+2) + 0V = 0$


4) solve 3 eq 3 unknowns

ex) find $i \Rightarrow i = (I_2 - I_3)$

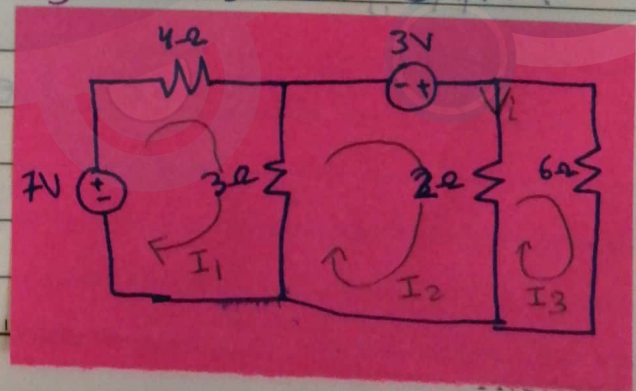

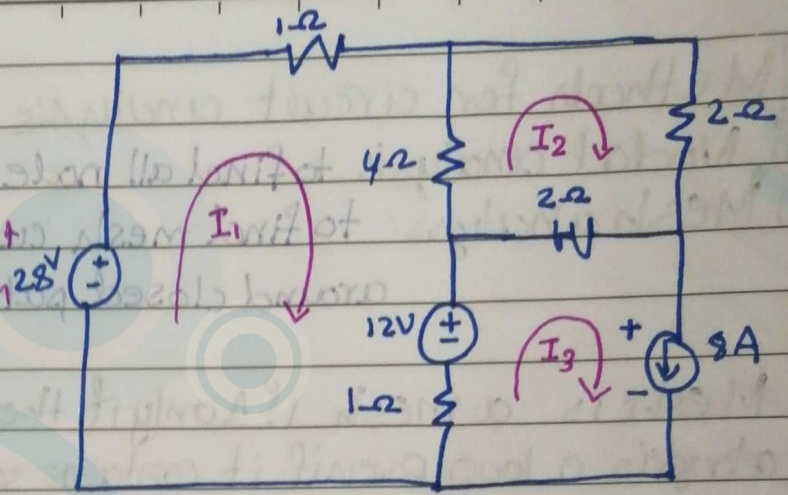Example

* Study note: the 8A current source is (already I_3 (mesh current)) no need to get it because it's ^{not} shared current and has (+) on it



$$\text{mesh 1} \rightarrow +I_1(1+4+1\Omega) - I_2(4\Omega) - I_3(1\Omega) + 12V - 28V = 0$$

$$6I_1 - 4I_2 - 8 + 12 - 28 = 0 \Rightarrow 6I_1 - 4I_2 = 24$$

$$\text{mesh 2} \rightarrow -I_1(4\Omega) + I_2(4+2+2\Omega) - I_3(8) + 0 = 0$$

$$-I_1(4) + 8I_2 - 8I_3 = 16$$

Find value of v in current source (8A)

$$\text{use KVL} \Rightarrow +V_s + 1(8 - I_1) - 12 + 2(8 - I_2) = 0$$


Mesh Analysis when current sources are shared between two meshes

- 1) Assign Mesh currents to every mesh in the circuit
- 2) Define the supermeshes (when 2+ shared current source)
- 3) Write KVL for each regular mesh
- 4) Apply KVL & KCL to supermeshes
- 5) Solve the system of equations

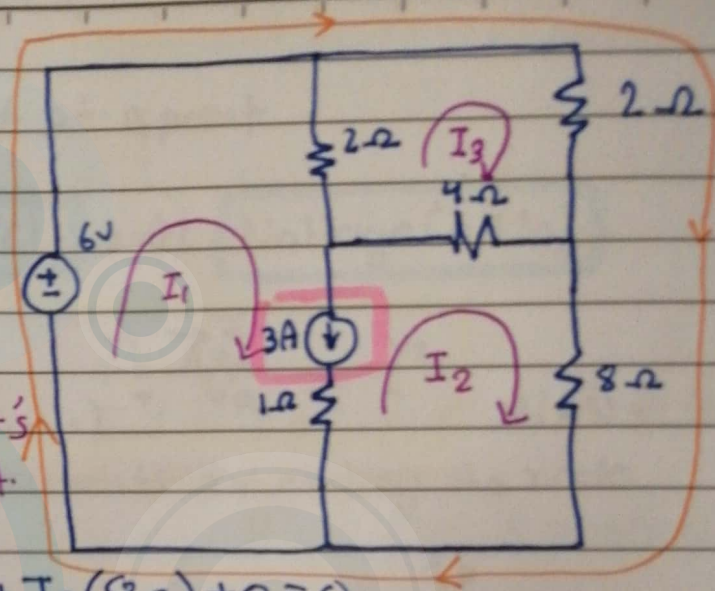Example

in here the (3A) source is a shared current source so i need to use super mesh analysis

- start with mesh 3 because it's not part of the shared current.



$$\text{mesh 3} \Rightarrow -I_1(2\Omega) - I_2(4\Omega) + I_3(8\Omega) + 0 = 0$$

now use supermesh (this huge orange mesh) [must NOT include the shared current source]

$$+I_3(2\Omega) + I_2(8\Omega) - 6V = 0 \rightarrow \text{i choose } \pm I \text{ depending on direction with/against}$$

my third equation will come from the current source itself

$$3A = I_1 - I_2$$

* solve

Example

$I_1 = 2mA \Rightarrow$ ready from current source


$$4mA = I_2 - I_3$$

super mesh

$$-6V + 1k\Omega I_3 + 2k\Omega I_2 + 2k\Omega (I_2) + 1k\Omega (I_3 - 2mA) = 0$$

* solve.

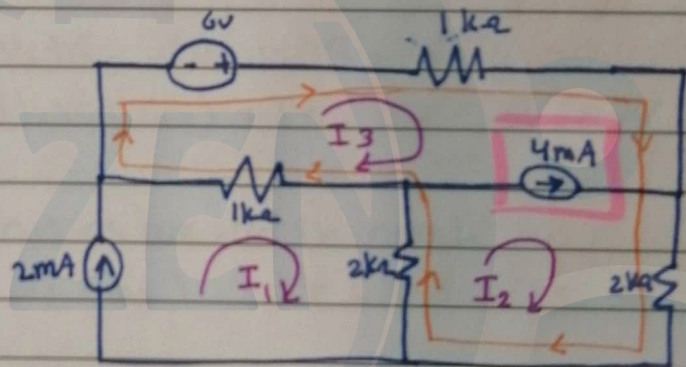study note: i tried to choose whichever loop/mesh that will avoid the shared current source.




Nodal Analysis

Nodes: when 2+ elements meet at a point

Nodal Analysis \Rightarrow using **KCL** and **Voltage CoHM**

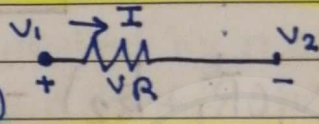
$$I = \frac{V_1 - V_2}{R} \text{ or } I = G(V_1 - V_2)$$



$V_1 - V_2$

in node analysis i assume all currents are exiting the node unless it states otherwise.

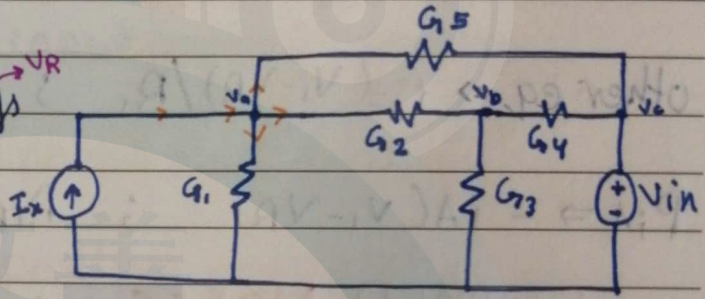in node analysis i must always assume a reference where the $V = 0$, usually is the common one and is usually grounded \equiv



at node A $\Rightarrow (V_a - V_b)G_1 + (V_a - V_c)G_2 + (V_a - V_e)G_5 = I_s$
 $V_a(G_1 + G_2 + G_5) - V_b(G_2) - V_c(G_5) = I_s$

OR i could do it by inspection as we did in mesh

Node A $\Rightarrow +V_a(G_1 + G_2 + G_5) - V_b(G_2) - V_c(G_5) = I_s$

- name the nodes


- put (-)(+) based on the node you are working on

- put all the elements on that node that are btwn your node & other.

node B $\Rightarrow -V_a(G_2) + V_b(G_2 + G_3 + G_4) - V_c(G_4) = 0$ no current source

node c \Rightarrow i have a voltage source then $= V_c = V_{in} - V_a \Rightarrow V_{in} = V_c$
 and the voltage source isn't shared.

Example: Write the nodal equations

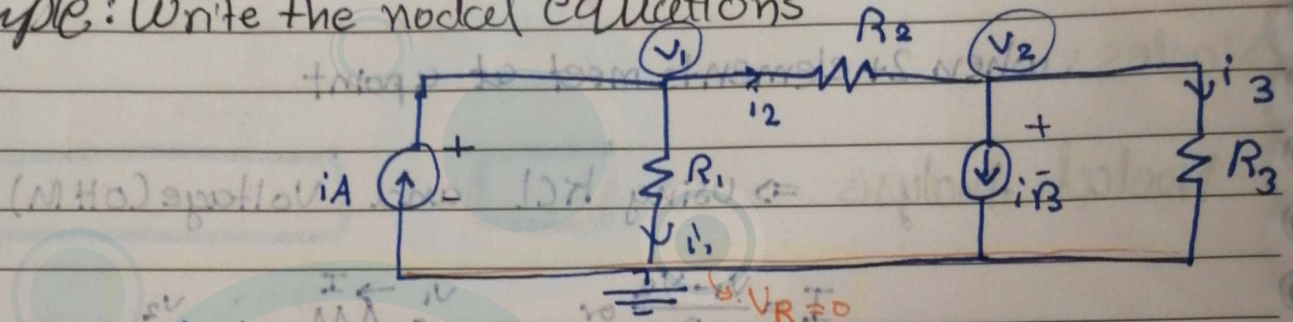

at node 1 $+V_1(\frac{1}{R_1} + \frac{1}{R_2}) - V_2(\frac{1}{R_2}) = iA$ \rightarrow cuz it's entering


at node 2 $-V_1(\frac{1}{R_2}) + V_2(\frac{1}{R_2} + \frac{1}{R_3}) = -iB$ \rightarrow cuz it's exiting

other eq $\Rightarrow i_1 = (V_1 - V_R)/R_1$; $i_2 = (V_1 - V_2)/R_2$; $i_3 = \frac{V_2 - V_R}{R_3}$


$P_{iA} \Rightarrow -iA(V_1 - V_R)$; $P_{iB} \Rightarrow +iB(V_2 - V_R)$

SUPPER NODES (when i have a shared voltage source btwn two node i use super nodes

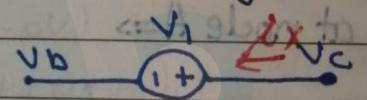$V_1 = (V_c - V_b)$; then i assume there is



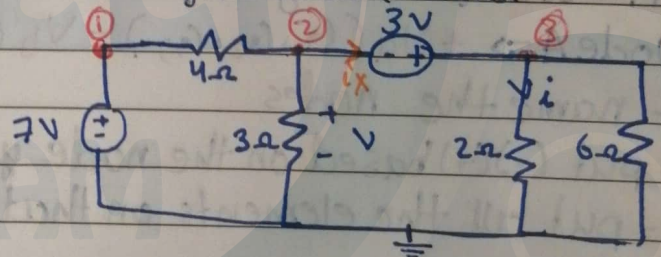a current (pick any direction you like) then continue solving on the nodes as if the voltage doesn't exist with respect to ix



example

$V_1 - 0 = 7$; $V_3 - V_2 = 3$

at node 2 $-V_1(\frac{1}{4}) + V_2(\frac{1}{4} + \frac{1}{3}) + ix = 0$

$ix = +V_3(\frac{1}{2} + \frac{1}{6})$

$V = V_2 - V_R = 0$

$i = (V_3 - 0)/2$

Superposition

Superposition:

Linearity: a system is linear if and only if it

- 1) If the input of the system is multiplied by a constant then the output is also multiplied by a same constant.
- 2) the output of the system to a sum of inputs is the sum of the outputs to each input applied separately.

Example $\rightarrow V = IR$ not linear $\Rightarrow P = I^2 R$

Steps for applying superposition principle

- 1) Kill all sources but one. find the desired current/voltage due to that source.

How to kill voltage source (replace with short circuit [line]) —


How to kill current source (replace with open circuit [cutted line]) —

keep in mind to keep the (+) (-) of V and direction of i


- 2) Repeat steps for each sources

- 3) find total desired voltage or current by algebraically adding the contribution due to each source.


Example: using superposition to find I

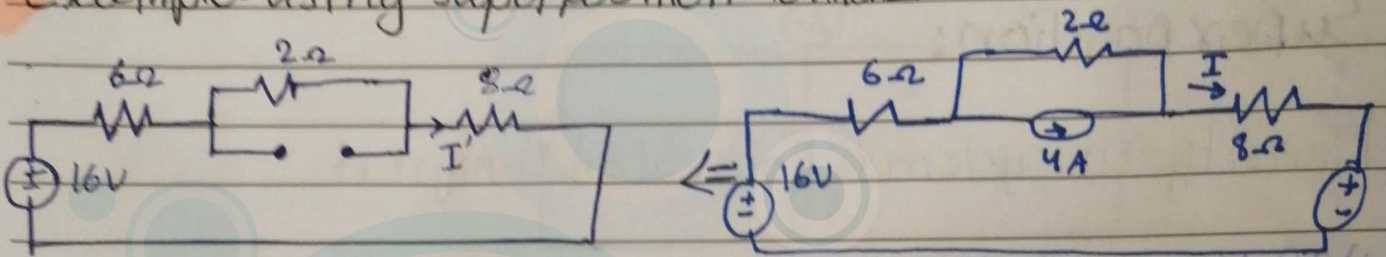

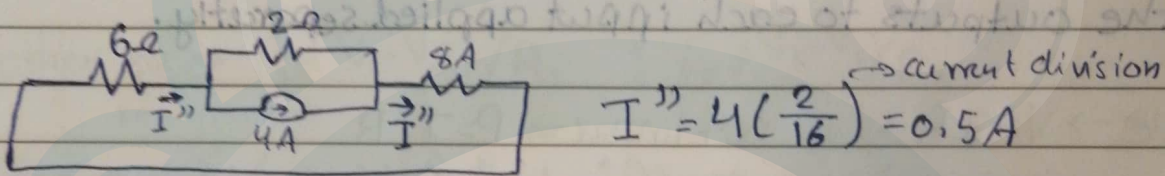↳ in this way i replaced the current source with open circuit and voltage source with short circuit creating one simple circuit with $(8+2+6\Omega)=16\Omega$ and 16V in this way $I' = 1A$


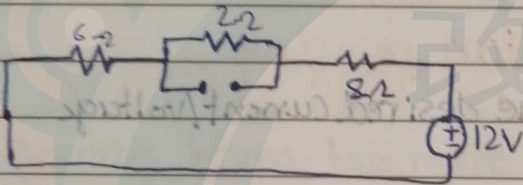
$$I'' = 4 \left(\frac{2}{16} \right) = 0.5A$$




$$I''' = -12/16 = -3/4 A$$

$$I = I' + I'' + I''' \Rightarrow 1 + 0.5 - 0.75 = 0.75A$$

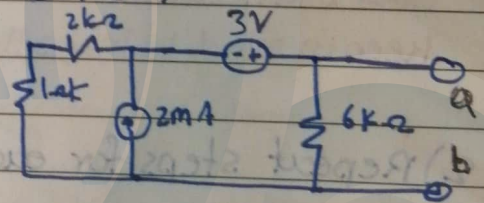Example
deleting the current source

$$\frac{3}{9} = \frac{1}{3} = \frac{6 \times 1/3}{6} = v_0' = 0.5V$$




deleting the voltage source.

$$2mA \left(\frac{3}{9} \right) = \frac{6m}{9} \times 6k = 4V = v_0''$$

$$V = v_0' + v_0'' = 0.5 + 4V = 4.5V$$


Source Transformation Week 4 Pt 1

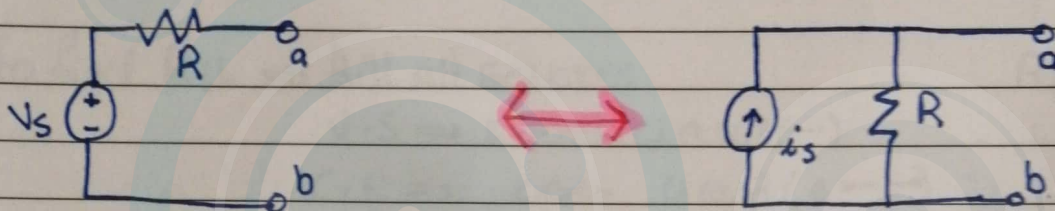Source transformation: process of replacing a voltage source in series with a resistor R with a current source in parallel with a resistor (with the same resistance value as R) and vice versa $i_s = \frac{V_s}{R}$ $V_s = i_s R$





direction of current is important.

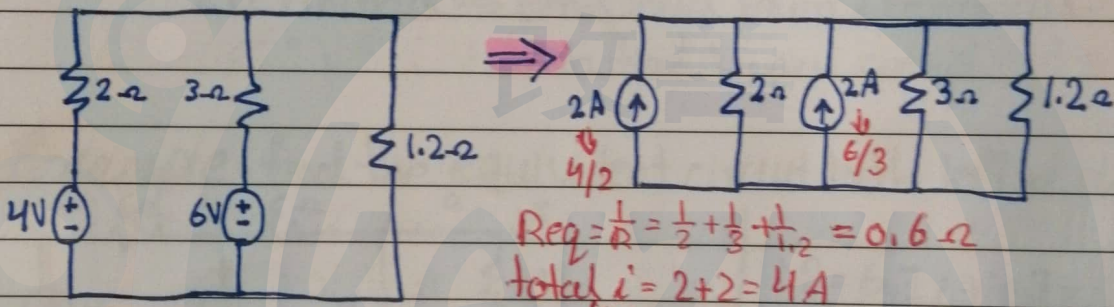Example: find the current in the $1.2\text{-}\Omega$ resistor



using current division $\Rightarrow \left(\frac{1/1.2}{1/1.2 + 1/2 + 1/3}\right) \times 4 = 2\text{A}$

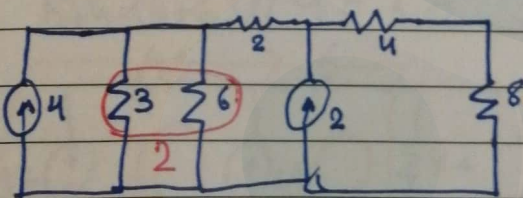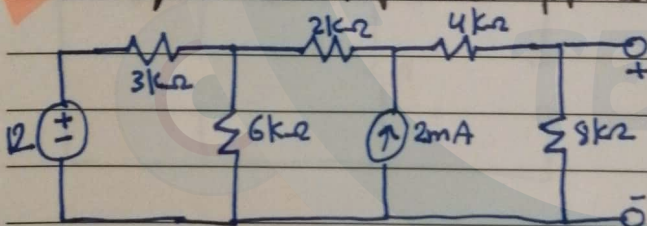Example: use repeated application of ST to find V_o



* keep repeating till you get one voltage source and all the rest R are in series then use voltage division.

$V_o = 8$


Thevenin and Norton equivalent circuits.

Thevenin theorem: any linear circuit containing several voltages and Resistances can be replaced by just one single voltage in series with a single resistance connected across the load voltage (V_{th}) & Resistance (R_{th})

to find $R_{th} \Rightarrow$ kill all sources
 $V.S \Rightarrow$ short circuit (\dashv)
 $C.S \Rightarrow$ open circuit ($\bullet \dashv$)
 btwn 2 terminals $\Rightarrow R_{eq} \Rightarrow R_{th}$


to find $V_{th} \Rightarrow V$ open circuit
 2 terminals \Rightarrow omit load btwn 2 terminals
 then find V open circuit

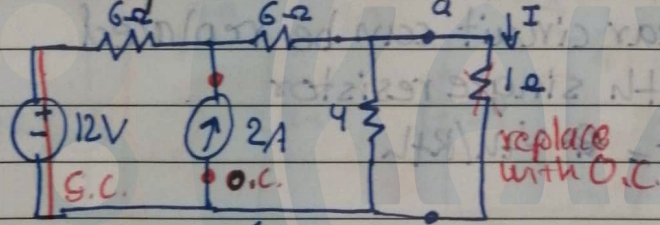Example: find the equivalent circuit to the left at a, b then I



$$12 = 6I_1 + 10I_2$$


$$2 = -I_1 + I_2$$

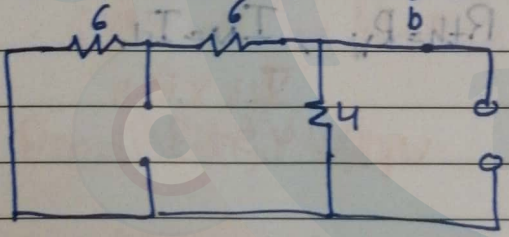


$$I_2 = 1.5A$$

$$V_{OC} = V_{th} = 1.5 \times 4 = 6V$$

$$R_{th} = (6+6) // 4 = 3\Omega$$

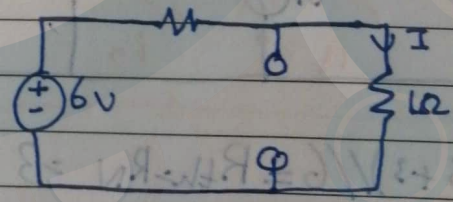


$$I = 6/4 = 1.5A$$

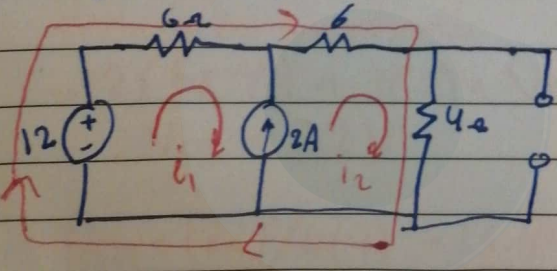


Solve using mesh

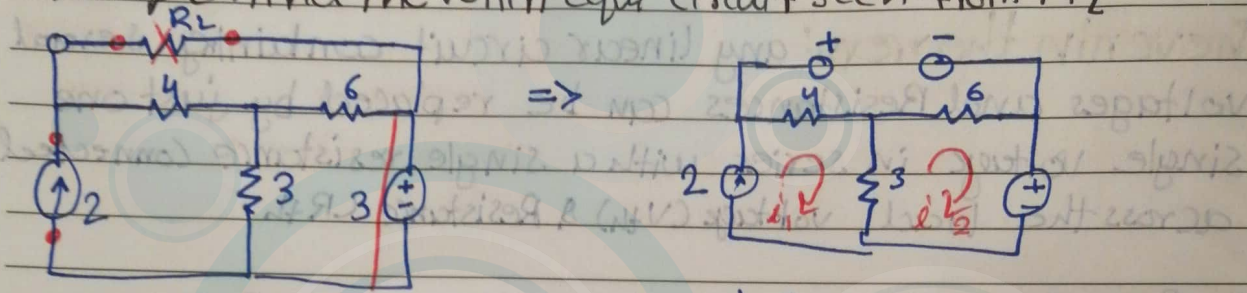
Example: find the venin equi circuit seen from R_L



$i_1 = 2$; $i_2 =$

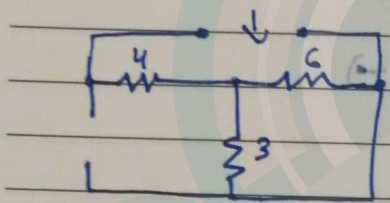

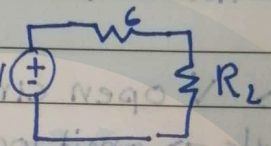$V_{OC} = 6k \left(\frac{1}{3} m - 1 \right) (2m) = 0$
 $V_{OC} = 10V$




$6 // 3 = 2$
 $2 + 4 = 6 = R_{th}$
 $I = \frac{10}{R_L + 6}$; $P = I^2 R_L$

Norton theorem: any linear circuit can be replaced by a single current I_N // with single resistor

$I_{norton} = I_{short\ circuit} = \frac{V_{th}}{R_{th}}$

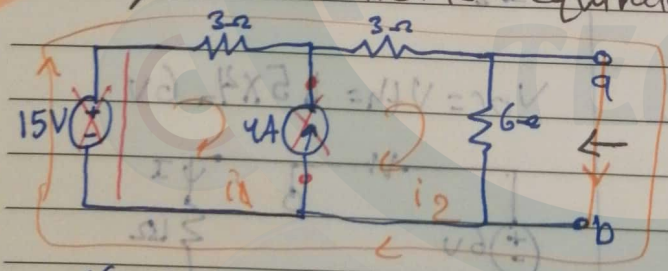Example find the Norton equivalent $R_{th} = R_N$, $I_N = I_{sh}$




$V_{th} = 4.5 \times 3$

$3 // (3 + 3) // 6 = R_{th} = R_N = 3$

$15 = 3A + 3 \times 2A \Rightarrow I_2 = 4.5 = I_{th}$
 $4 = -i_1 + I_2$

Max Power transfer.

W4P4

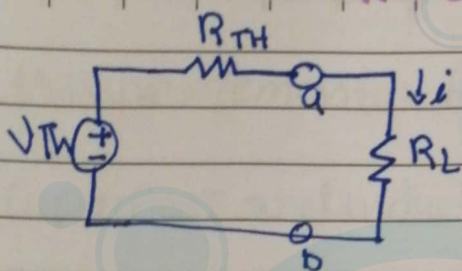

$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

maximum power to the load.


$$P_L = (V_{th})^2 / (4R_{th})$$

$$\text{Efficiency} = (P_{out}) / P_{in} = P_L / P_{source}$$

$$P_{source} = (V_{th}^2) / 2R_{sth}$$

Efficiency = 0.5 Always.

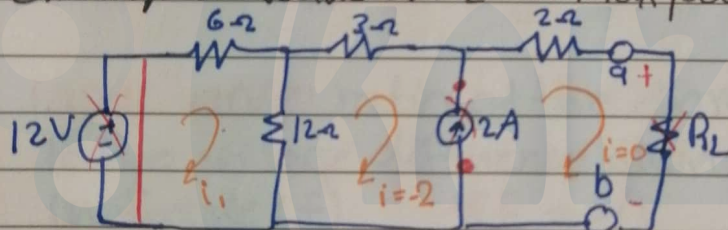Example: value of R_L for max power transfer; max power



$$R_L = R_{th}$$

$$V_{oc} = V_{th}$$

$$6 // 12 = 4 \Rightarrow 4 + 3 + 2 = 9 \Omega = R_L = R_{th}$$

$$P_m = (V_{th})^2 / 4R_{th}$$

$$i_1 = 18I_1, -12(-2) = 12 \Rightarrow i_1 = -2/3 A$$

then take supermesh.

$$-12(6x - 2/3) + 3(-2) + V_{oc} = 0$$

$$V_{oc} = 22V$$

$$P_{max} = (22)^2 / 4(9) = 13.44 W$$

Capacitors

Passive elements: Resistors, capacitors, inductors


Capacitors and inductors can store energy **storage elements**

DC \Rightarrow **has** Resistor, capacitor, inductor

Capacitor: consists of 2 conducting plates separated by an insulator or dielectric

$$C = \frac{\epsilon A}{d}$$

capacitor with applied voltage

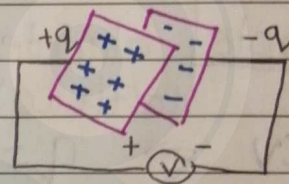


factors affecting the value of capacitance

- 1) Area: larger Area \Rightarrow larger capacitance (A)
- 2) spacing btwn the plates: smaller space \Rightarrow greater C (d)
- 3) material permittivity: higher permittivity \Rightarrow greater C (ϵ)

Capacitance: ratio of the charge on one plate of a capacitor to the voltage difference btwn the two plates measured in Farade (F)

$$F = C/V$$

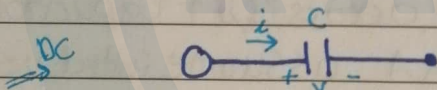

$$i = C \frac{dv}{dt}$$

* a constant voltage across a capacitor creates no current through the capacitor, = **open circuit**.

* i can change arbitrary but voltage won't (it take time to change)

* A capacitor has **memory** $V = \frac{1}{C} \int i dt + v(t_0)$

* capacitor voltage depends on the past history ($-\infty \rightarrow t_0$) of the capacitor current

Energy storage in capacitance

$$P = vi = CV \frac{dV}{dt}$$

$$W = \frac{1}{2} CV^2$$

$$W = \frac{q^2}{2C}$$

under DC and steady state condition \Rightarrow cap open circuit

Example Calculate charge stored on a 3 pF capacitor with 20V across it. Find energy stored in capacitor

$$q = CV \Rightarrow q = 3 \times 10^{-12} \times 20 = 60 \text{ pC}$$

$$W = \frac{1}{2} CV^2 = \frac{1}{2} \times 3 \times 10^{-12} \times 400 = 600 \text{ pJ}$$

example the voltage across 5 μ F capacitor is $v(t) = 10 \cos 6000t$ V, find current through it

$$i = C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt} (10 \cos 6000t) \\ = -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t = -0.3 \sin 6000t \text{ A}$$

example determine the voltage across 2 μ F capacitor if the current is $i(t) = 6e^{-3000t}$ mA assume initial $v=0$

$$v = \frac{1}{C} \int_0^t i dt + v(0) \text{ and } v(0) = 0$$


$$v = \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000t} dt \cdot 10^{-3} = \frac{3 \times 10^3 - 3000t}{-3000} e^{-3000t} \Big|_0^t$$

$$= (1 - e^{-3000t}) \text{ V}$$

Capacitors pt2

(week 5 pt 2)

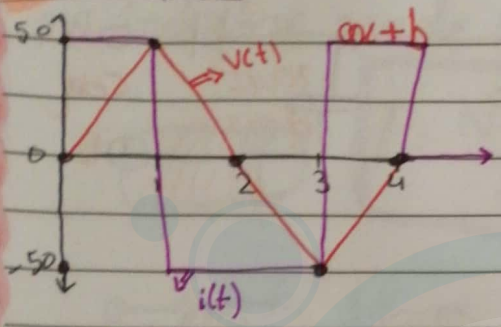
example Determine current through a $200\mu\text{F}$ when V is



$$v(t) = \begin{cases} 50t\text{V} & 0 < t < 1 \\ 100 - 50t\text{V} & 1 < t < 3 \\ -200 + 50t\text{V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

$$i(t) = 200\mu\text{A} \times \begin{cases} 50 \\ -50 \\ 50 \\ 0 \end{cases}$$

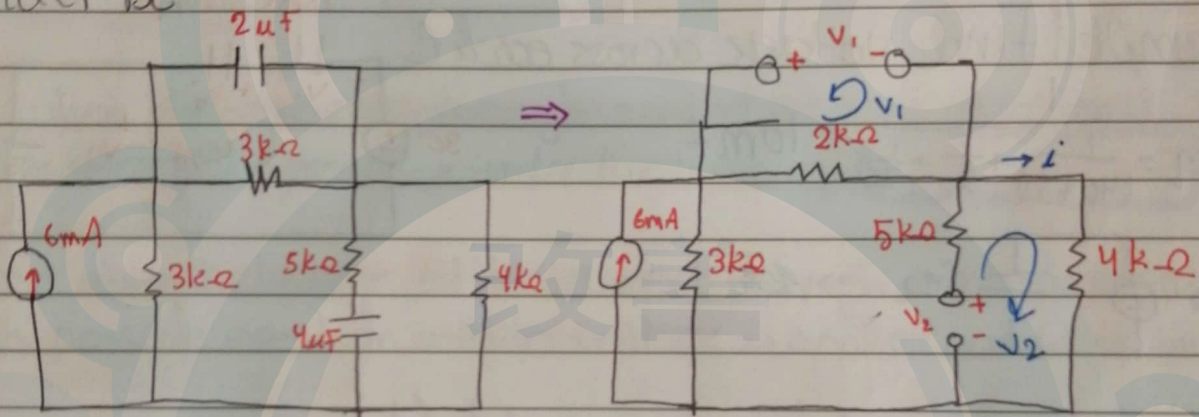example Find Energy in each capacitor under DC



under DC conditions, replace each by OC (no I, but has V)

$$v_1 = 2000i = 4\text{V}$$

$$i = \frac{3}{3+2+4} (6\text{mA}) = 2\text{mA}$$

$$w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} (2 \times 10^{-3}) (4)^2 = 16\text{mJ}$$

$$v_2 = 4000i = 8\text{V}$$

$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} (4 \times 10^{-3}) (8)^2 = 128\text{mJ}$$

* i can treat capacitors ~~like~~ ^{opposite} resistor eqn in series & parallel

parallel $C_{eq} = C_1 + C_2 + C_3 + \dots + C_n$

$$i = i_1 + i_2 + i_3$$


series $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$

$$V = V_1 + V_2 + V_3$$

Can also use π - Δ but in opposite

$$Y_C = R$$

example Find eq C btun a,b

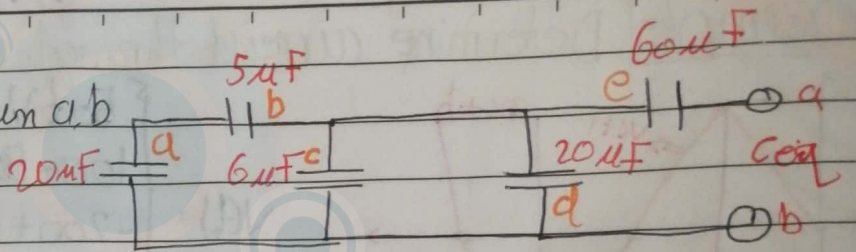

$$a, b \text{ series } \frac{1}{a} + \frac{1}{b} = \frac{5 \times 20}{5+20} = 4$$



$$\text{parallel with } c \Rightarrow 4+6 = 10 \mu$$

$$10+20 = 30 \mu$$

$$\frac{30 \times 60}{90} = 20 \mu = eq$$

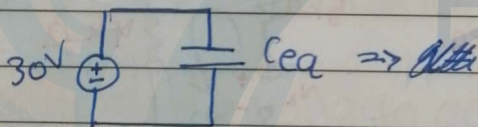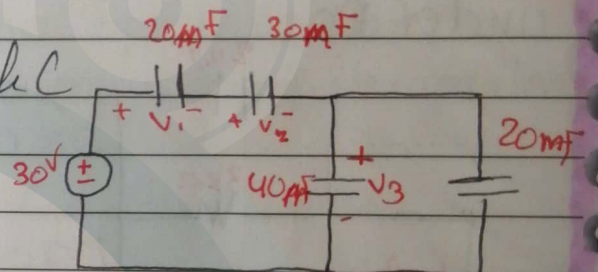example Find voltage across each C

$$C_{eq} = \frac{1}{\frac{1}{40+20} + \frac{1}{30} + \frac{1}{20}} = 10mF$$



Using Voltage division $V_1 = 30 \left(\frac{\frac{1}{20}}{\frac{1}{20} + \frac{1}{10}} \right) = 15V$


$$V_3 = 30 \left(\frac{\frac{1}{60}}{\frac{1}{10}} \right) = 5$$

$$V_2 = 30 \left(\frac{\frac{1}{30}}{\frac{1}{10}} \right) = 10V$$

Inductors

Week 5 pt 3

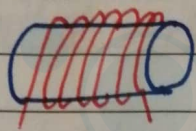an inductor made of a coil of conducting wire




$$L = \frac{N^2 \mu A}{l}$$

N: # of turns

l: length

A: cross sectional Area


μ : permeability of the core

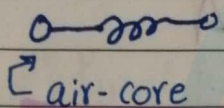

air-core

Stores Energy in seconds & restores in seconds

$$V = L \frac{di}{dt}$$

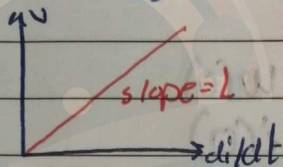

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

* When the current through an inductor is constant, the voltage across the inductor is zero. **short circuit** "DC"

* no abrupt change of the current through an inductor is possible except an infinite voltage is applied across the inductor.

* Can be used to generate a high voltage "igniting element"

* the current through an inductor **can't change abruptly**

* ideal inductor **doesn't** dissipate energy

* Energy stored in inductor $w = \frac{1}{2} L i^2$ $i(-\infty) = 0$

Ex | $i = 10t e^{-5t}$ $L = 0.1 \text{ H}$ $v = ?$ $w = ?$

$$v = L \frac{di}{dt}$$

$$v = 0.1 \frac{d}{dt} (10t e^{-5t}) = e^{-5t} + t(-5) e^{-5t} = e^{-5t} (1 - 5t) \text{ V}$$

$$w = \frac{1}{2} L i^2 \Rightarrow \frac{1}{2} (0.1) (100t^2) e^{-10t} = 5t^2 e^{-10t} \text{ J}$$

ex | find current through 5-H if v is

$$v(t) = \begin{cases} 30t^2 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

find energy $0 < t < 5$
assume $i(0) = 0$

$$i = \frac{1}{L} \int_0^t v(t) dt + i(t_0)$$

$$i = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A}$$

Energy $0 < t < 5 \Rightarrow w(5) - w(0)$


$$= \frac{1}{2} L i(5)^2 - \frac{1}{2} L i(0)^2$$

$$= \frac{1}{2} 5 (2 \times 5^3)^2 - 0 = 156.25 \text{ kJ}$$

ex | under DC conditions find


(a) i , v_C , i_L

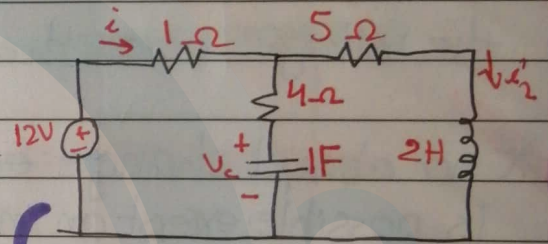(b) Energy stored in capacitor & inductor



on DC, change Cap \Rightarrow ∞ , ind \Rightarrow SC.

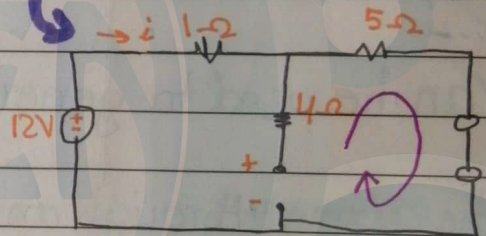in that way there's no current through the 4- Ω Resistor so the circuit is of one loop $i = i_L$



$$i_L = i = \frac{V}{R} = \frac{12}{5+1} = 2 \text{ A}$$

$$-v_C + 5i = 0 \quad -v_C + 5(2) = 0 \quad , v_C = 10 \text{ V}$$

$$w_C = \frac{1}{2} C V^2 = \frac{1}{2} (1) (10)^2 = 50 \text{ J}$$

$$w_L = \frac{1}{2} L i^2 = \frac{1}{2} (2) (2)^2 = 4 \text{ J}$$

Series inductors


$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$

parallel inductors

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}$$

* just like a resistor, can use Δ $L_y = \frac{1}{3} L_0$

ex) Find L_{eq}

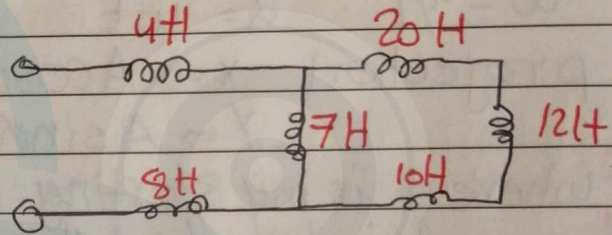


$$20 + 12 + 10 = 42H$$

$$\frac{42 \times 7}{42 + 7} = 6H$$

$$6H + 4H + 8H = 18H = L_{eq}$$

ex) Find L_{eq}

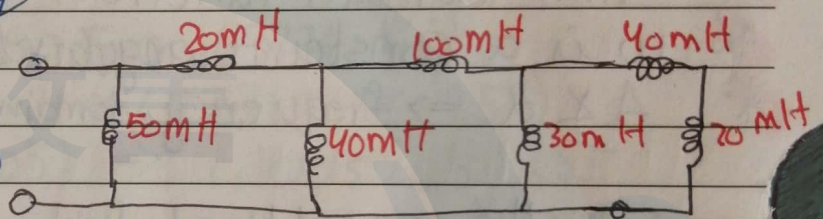

$$40 + 20 = 60$$

$$\frac{60 \times 30}{60 + 30} = 20$$

$$20 + 100 = 120$$

$$\frac{120 \times 40}{120 + 40} = 30$$

$$30 + 20 = 50$$

$$\frac{50 \times 50}{50 + 50} = 25mH = L_{eq}$$

ex) $i(t) = 4(2 - e^{-10t})$ mA if $i_2(0) = -1$ mA

find $i_1(t)$; $v(t)$, $v_1(t)$, $v_2(t)$; $i_1(t)$, $i_2(t)$

• $i'(0) = i_1'(0) + i_2'(0)$ 1 V @ (A)


$$4(2 - e^{-10 \times 0}) = i_1'(0) - 1$$

$$1 + 4 = i_1'(0) = 5 \text{ mA}$$

• $v_1 = L \frac{di}{dt} \Rightarrow v_1 = 2 \frac{d}{dt} 4(2 - e^{-10t}) = -80e^{-10t}$

• $L_{eq} = \frac{12 \times 4}{12 + 4} + 2 = 5H$, $v(t) = 5 \frac{d}{dt} (4(2 - e^{-10t})) = 5/40e^{10t} \text{ m}$

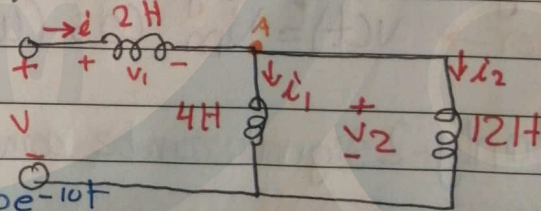• $v_2 = v - v_1 \Rightarrow 5/40(e^{10t}) - (-80e^{-10t})$



$$i_1 = \frac{1}{4} \int_0^t v_2 dt + i_1(0)$$

$$i_2 = \frac{1}{12} \int_0^t v_2 dt + i_2(0)$$

$$\Rightarrow \text{OR} \Rightarrow i_2(t) = i(t) - i_1(t)$$

AC analysis

WG pt 1

A sinusoidal voltage/current source produces a voltage that varies with time like a sinusoidal function (periodic), also cosine function


Phaser: $\alpha \Rightarrow$ angle, $\omega =$ angular velocity (ccw)

$$\omega = \alpha/t \quad \alpha = \omega t$$

projection $x \Rightarrow A \cos \alpha = A \cos(\omega t) = A \cos(\omega t + \theta)$

$y \Rightarrow A \sin \alpha = A \sin(\omega t) = A \sin(\omega t + \theta)$

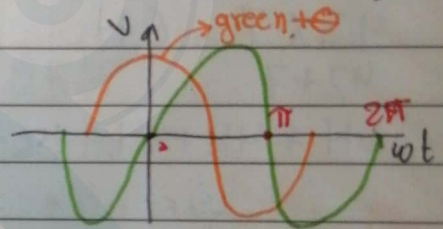- * where θ is my starting angle
- * A is length of the vector
- * time domain function
- * ω is a constant angular velocity
- * A & $\alpha \Rightarrow$ frequency domain function



period: is the required time to finish one cycle T (seconds)


V_{in} : peak, highest value of wave

frequency: # of cycles in 1 second

$$f = 1/T \text{ (Hertz or cycles per second)}$$

Angular frequency: $\omega = 2\pi f = 2\pi/T$ radians per seconds

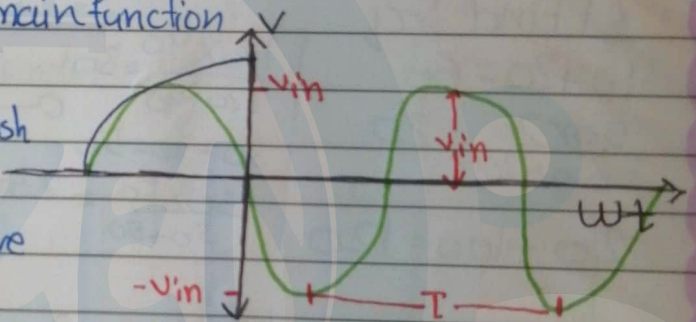phaser $\rightarrow v(t) = V_m \cos(\omega t + \phi)$ phase shift $\leftarrow \pm \Rightarrow$



* only 2 signals can be compared if and only if they have same frequency

orange leads green by ϕ ; green lags orange by ϕ

* cosine leads sin by 90° ; sin lags cosine by 90°

\rightarrow out of phase

$$\phi = \frac{\text{Phase shift (no. of div)} \times 360}{T \text{ (no. of div)}}$$

Peak $0 \rightarrow \max$
 Amplitude avg $\rightarrow \max$
 if $0 = \text{avg} \Rightarrow \text{peak} = \text{amplitude}$

change sinusoidal to phaser $v = V_m \cos(\omega t - 90 + \phi)$

ex | given a sinusoid $5 \sin(4\pi t - 60^\circ)$ calculate amplitude, phase, angular frequency, period & frequency
 amplitude = 5 angular frequency = $4\pi \text{ rad/s}$ period $1/f = 0.5 \text{ sec}$
 phase = -60° $\omega = 4\pi = 2\pi f \Rightarrow f = 2 \text{ Hz}$

* if we add 10 then the only thing that's gonna change is the peak which is $(5+10) = 15 = \text{DC} \Rightarrow \text{average}$

ex | find the phase angle btwn $i_1 = -4 \sin(377t + 25^\circ)$ and $i_2 = 5 \cos(377t - 40^\circ)$, Does i_1 lead or lag i_2 ?

$\sin(\omega t + 90^\circ) = \cos \omega t$
 $i_2 = 5 \cos(377t - 40^\circ + 90^\circ) = 5 \sin(377t + 50^\circ)$
 $i_1 = -4 \sin(377t + 25^\circ) = 4 \sin(377t + 180^\circ + 25^\circ)$
 $= 4 \sin(377t + 205^\circ) \Rightarrow i_1 \text{ leads } i_2 \text{ by } 155^\circ$

$\cos(\omega t - 90^\circ) = \sin \omega t$ $\sin(\omega t + 180^\circ) = -\sin \omega t$

phasor Rectangular $\Rightarrow Z = x + jy = r(\cos \phi + j \sin \phi)$
 Polar $\Rightarrow Z = r \angle \phi$ $r = \sqrt{x^2 + y^2}$ $\phi = \tan^{-1} y/x$
 Exponential $\Rightarrow Z = re^{j\phi}$

ex | $(5 + j2)(-1 + j4) = 5 \angle 60^\circ$

using symbols change polar to cartesian calculus $(x + jy)$ then go to complex numbers Pre-calc and enter the equation:

$e^{j\phi} = \overset{\text{Real}}{\cos \phi} + j \overset{\text{Imaginary}}{\sin \phi}$ Euler's identity

timedomain $V_m \cos(\omega t + \phi) \Leftrightarrow V = V_m \angle \phi$ phasor domain
 must be cosine

AC Analysis pt. 2 w6 pt 2.

ex) Transform the following sinusoids to phasors

a) $6 \cos(50t - 40^\circ) = 6 \angle -40^\circ$

b) $4 \sin(30t + 50^\circ)$ change to \cos "+90"
 $= 4 \cos(30t + 50 + 90) = 4 \cos(30t + 140) = 4 \angle 140^\circ$

b leads a by $(140 - 40) = 100^\circ$

a lags b by $(140 - 40) = 100^\circ$

ex) Transform the phasors to sinusoids

a) $V = -10 \angle 30^\circ = 10 \angle 30 + 180 = 10 \angle 210 = 10 \cos(\omega t + 210)$

b) $j(5 - j12) = j5 - (-1)(12) = 12 + j5, r = \sqrt{12^2 + 5^2} = 13$

$\phi = \tan^{-1}(5/12) = 22.62^\circ \Rightarrow 13 \cos(\omega t + 22.62^\circ)$

on calculator \Rightarrow mode \rightarrow Cmplx \Rightarrow "write equ" \Rightarrow shif[2] \Rightarrow [3] \Rightarrow [=]

ex) $5 \cos(10t + 30^\circ) + 10 \sin(10t + 90^\circ) + 4$

i can add things up only if $\omega = \omega$

the 4 @ the end represents the DC AKA average of signal $f=0$


so i treat it like a real number.

$10 \sin(10t + 90) = 10 \cos(10t)$

$= 5 \angle 0 + 10 \angle 0 = 15 \angle 0 + 4$

$= 15 \cos(10t) + 4$ Amp = 15 peak = $15 + 4 = 19$

min = $15 - 4 \Rightarrow 11$

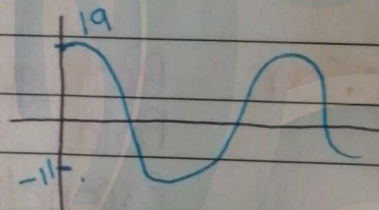

Diff btwn $v(t)$ & V

- $v(t)$ is instantaneous or time domain representation

- V is the frequency or phasor domain representation

- $v(t)$ is time-dependant v is not.

- $v(t)$ is always real with no complex term. V is generally complex

$$\omega = 2\pi f$$

Time Domain

$$v(t) = V_m \cos(\omega t + \phi)$$

$$v(t) = V_m \sin(\omega t + \phi)$$

$$\int \frac{dv}{dt}$$

$$\int v dt$$

 \Leftrightarrow
 \Leftrightarrow
 \Leftrightarrow
 \Leftrightarrow

Phasor domain

$$V = V_m \angle \phi$$

$$V = V_m \angle \phi - 90$$

$$J \omega V$$

$$V / J \omega$$

ex Use phasor approach, determine the current $i(t)$ in a circuit described by the integro-differential eqn.

$$4i + 8 \int i dt - 3 di/dt = 50 \cos(2t + 75^\circ)$$

$$4i + 8i/J\omega - 3J\omega = 50 \angle 75$$

$$i(4 + 8/J\omega) = 50 \angle 75 + 3J\omega$$

$$i(4 + 8/J2) = 50 \angle 75 + 3J2$$

$$i(4 + 4/J) = 50 \angle 75 + 6J$$

$$i(t) = 4.642 \cos(2t + 143.2)$$

$$I(4 - 10j) = 50 \angle 75$$

$$I = \frac{50 \angle 75}{4 - 10j}$$

$$4 - 10j$$

impedance = $Z(\omega)$

$$R \Rightarrow Z = R$$

$$L \Rightarrow Z = j\omega L$$

$$C \Rightarrow Z = -j/(\omega C) = 1/(j\omega C)$$

$$V = IR \Rightarrow V = IZ \text{ (all in vectors)}$$


$$V \angle \phi = (I \angle \phi)(Z \angle \theta)$$

Real + j Imag

Resistance

Reactant (-2)

ex

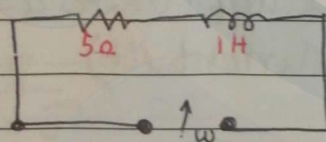


$$5\Omega \Rightarrow 5\Omega ; 1H \Rightarrow j\omega L$$

$$5 + j10$$

$$\omega = 10$$


inductive load.

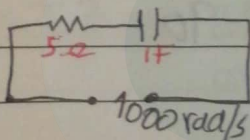

$$5\Omega \Rightarrow 5\Omega \quad 1F$$

$$Z = 5 - j1000$$

capacitive load

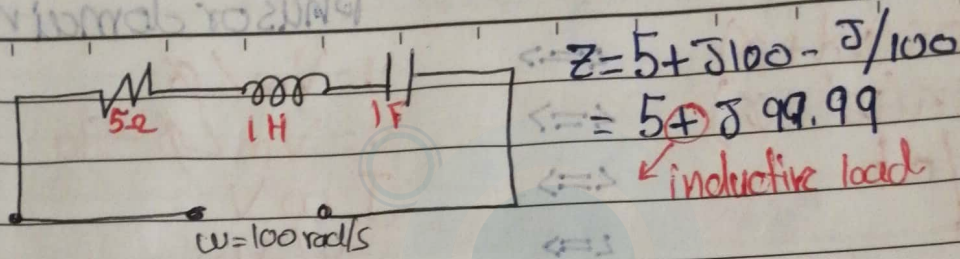


Cases:

- $Z \Rightarrow$ Resistive Pure (only real) $\text{Re} + j0$ $|| \neq 0$
- inductive load $\text{real} + jX$ $|| \neq +ve$
- capacitive load $R - jX$ $|| \neq -ve$

$1/Z \Rightarrow$ admittance $\Rightarrow Y = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$

$Y = G + jB$
 Conductance Susceptance

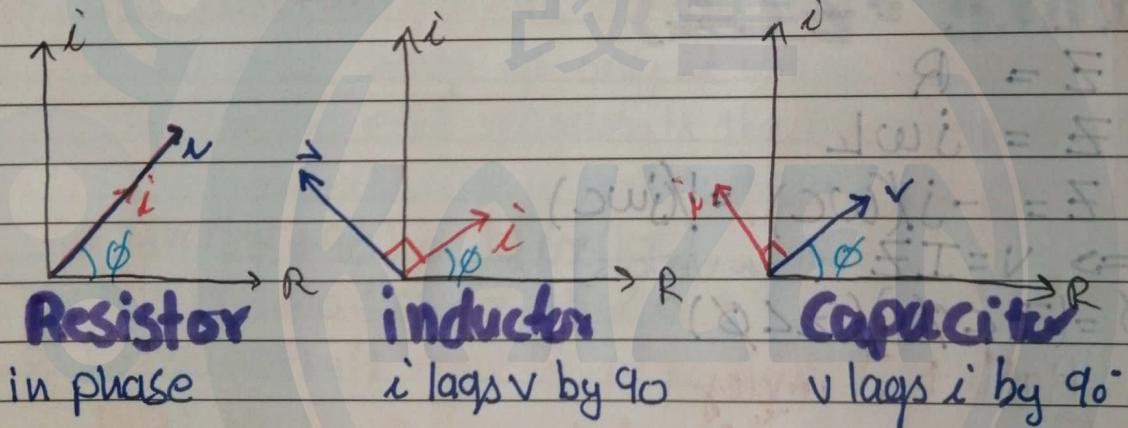$V = IZ \Rightarrow V = I/Y \Rightarrow I = VY$



ex if voltage $v(t) = 6 \cos(10t - 30^\circ)$ is applied to a $50 \mu F$ capacitor, calculate the current $i(t)$ through the capacitor

$6 \cos(10t - 30^\circ) \Rightarrow 6 \angle -30$

$50 \mu F = Z_c = 1/j(100) \times 50 \times 10^{-6} \Omega = 200 \angle -90$

$I = V/Z = \frac{6 \angle -30}{200 \angle -90} = 30000 \angle -60$
 $= 30 \cos(10t + 60) \text{ mA}$

1. AC FW element

impedance calculation

R $Z = R$ $Y = 1/R$


~~impedance~~
L $Z = j\omega L$ $Y = 1/j\omega L$

C $Z = 1/j\omega C$ $Y = j\omega C$ $1/\omega = Z$

$Z = j\omega L$
 DC \Rightarrow short $\rightarrow \text{---} \text{---}$ $\omega = 0, Z = 0$
 \uparrow frequency \Rightarrow open $\rightarrow \text{---} \text{---}$ $\omega \rightarrow \infty, Z \rightarrow \infty$

$Z = 1/j\omega C$
 DC \Rightarrow open $\rightarrow \text{---} \text{---}$ $\omega = 0, Z \rightarrow \infty$
 high frequency \Rightarrow short $\rightarrow \text{---} \text{---}$ $\omega \rightarrow \infty, Z = 0$

ex) find $v(t)$ and $i(t)$

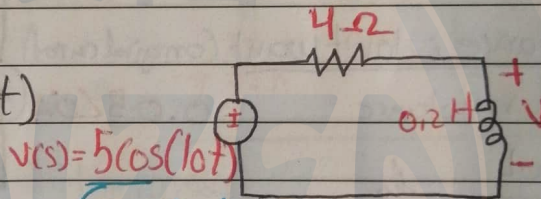

change everything to phase (must always be cos)

$5 \cos(10t) = 5 \angle 0$ $4 \Omega = 4i$ $0.2 \text{H} = j10 \times 0.2 = j2 \Omega$

KVL = $-5 \angle 0 + 4i + j2i = 0$

$\frac{5}{4 + j2} =$ on calc \Rightarrow then shift 2 $r \angle \theta = 1.118 \angle (10t - 26.56^\circ) \text{A}$

$v = IZ \Rightarrow j2 \times 1.118 \angle -26.56$
 on calc \Rightarrow shift $|Z|$ $r \angle \theta$

$Z_{in} \Rightarrow$ find eq like resistors.

AC Analysis Pt 3

Summary:- Source $\Rightarrow A \cos(\omega t + \phi)$ phasor $A \angle \phi$

impedance $Z =$ (Ω)	$\left\{ \begin{array}{l} R \Rightarrow R \\ L \Rightarrow j\omega L \\ C \Rightarrow 1/j\omega C = -j\omega C \end{array} \right.$	$\left. \begin{array}{l} \text{ } \times \ominus Z \\ R \pm jX \end{array} \right\}$		

$V = IZ \Leftrightarrow V = I/Y$


- if Resistive load $\Rightarrow V$ & I in phase "same angle"
- if inductive load $\Rightarrow i$ lags V $\angle V - \angle i = \angle Z$
- if capacitive load $\Rightarrow i$ leads V $\ominus \angle V - \ominus \angle i = \ominus \angle Z$

example: application of current Division for phasors

find I_1

$i = \frac{\text{resistance i don't want (original current)}}{\text{total resistance}}$

$0.05 \angle 0^\circ \text{ A}$

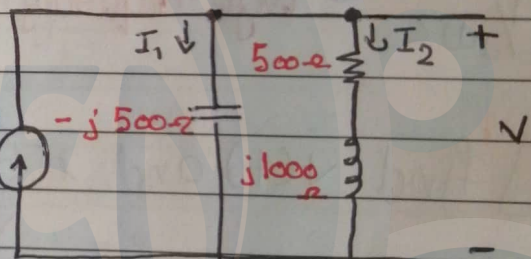

$$i_1 = \frac{R + j\omega L}{R + j\omega L + 1/j\omega C} i_0$$

$$= \frac{(500 + j1000)}{500 + j1000 - j500} (0.05 \angle 0^\circ) = i_1 = 0.079 \angle 68.4^\circ \text{ A}$$


$$i_2 = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} (i) = \frac{-j500}{500 + j1000 - j500} (0.05 \angle 0^\circ) \Rightarrow i_2 = 0.03535 \angle -45^\circ \text{ A}$$

Example! - Calculate $v_o(t)$

Change voltage $\Rightarrow 10 \angle 75^\circ$

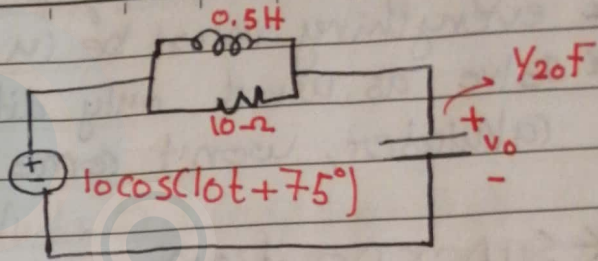0.5 H inductor $\Rightarrow j\omega L = j10 \times 0.5 = j5$

$1/20F \Rightarrow 1/j\omega C = 1/j10(1/20) = -j2$



let $Z_1 =$ impedance of inductor // resistor

$$Z_1 = 10 // j5 = (10 \times j5) / (10 + j5) = 2 + 4j$$

$Z_2 =$ impedance of capacitor $= -j2$

$V_o = \frac{\text{Voltage i want (original voltage)}}{\text{total voltage}}$


$$V_o = \frac{Z_2}{Z_1 + Z_2} (V) = \frac{-j2}{-j2 + 2 + 4j} \times 10 \angle 75^\circ = 7.07 \angle -60^\circ = 7.07 \cos(10t - 60^\circ)$$

Example: find Z_{in} , $\omega = 10 \text{ rad/s}$

$Z_1 \Rightarrow$ Series $\Rightarrow 50 + j\omega L = 50 + j20$

$Z_1 // Z_2 \Rightarrow Z_2 \Rightarrow 1/j\omega C = 1/j(10)(4 \times 10^{-3}) = -25j$
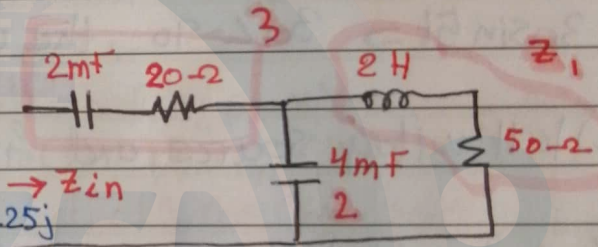
$$\frac{(50 + j20) \times (-25j)}{50 + j20 - 25j} = 10.891 + 1.089j$$



$$Z_3 \Rightarrow 20 + 1/j\omega C = 20 + 1/j(10)(2 \times 10^{-3}) = 20 - 50j \quad Z_{total} = 32.37 - 73.76j$$

Driving point impedance \Rightarrow total Z

Driving Point admittance $\Rightarrow 1/\text{total } Z$

phasor current = phasor voltage / total Z

particular response (steady state-response) = current in sinusoidal form.

current leads voltage & vice versa by ϕ

To find which is which on graph find point that they both move together (up or down) and see who hits point first (down \Rightarrow point ϕ)

* Using Nodal Analysis and Mesh

* everything must be in phasor form


* solve as usual only difference can't solve using calculator, won't come complicated in test.

* Superposition

- used when i have different frequencies.

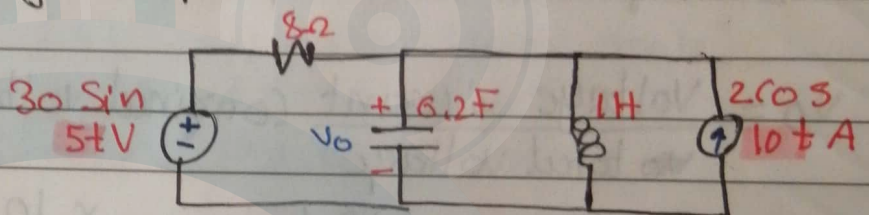Example: find V_0 using superposition

Since voltage & current source have different ω



1) Kill current then solve

$30 \sin 5t \Rightarrow 30 \angle -90^\circ$, the $\omega = 5$ then use voltage division

2) Kill voltage source and find impedance when $\omega = 10$

* can't add both because i have different frequencies
write in time domain (frequency in $A \cos \omega t + \theta$)

* using source transformation & Thevenin & Norton

Max power $Z_L = Z_{th}$ ~~*~~ \rightarrow pure resistive

AC Power Calc Pt 1

instantaneous Power

$$P(t) = v(t) i(t) = V_m I_m (\cos(\omega t + \theta_v) \cos(\omega t + \theta_i))$$

$$P(t) = \frac{1}{2} V_m I_m (\cos(\theta_v - \theta_i)) + \frac{1}{2} V_m I_m (\cos(2\omega t + \theta_v + \theta_i))$$

constant Power
Average Power

sinusoidal Power
dependant on 2ω

Average Power: $\theta_v = \theta_i \Rightarrow$ resistive load case

$\theta_v - \theta_i = \pm 90$ reactive load case $P = 0 \Rightarrow \cos 90 = 0$

$P = 0 \Rightarrow$ absorbs no average power

Example:- find inst & Avg Power absorbed by passive

$$v(t) = 80 \cos(\omega t + 20^\circ) \quad i(t) = 15 \sin(\omega t + 60^\circ) = 15 \cos(\omega t - 30^\circ)$$

$$\text{Average} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \cdot 80 \cdot 15 \cdot (\cos(20 - (-30))) = 385.67 \text{ W}$$

$$\text{inst} = \text{Average} + \frac{1}{2} V_m I_m (\cos(2\omega t + \theta_v + \theta_i)) = 385.6 + 600 \cos(2\omega t - 10^\circ)$$

Example: current $I = 10 \angle 30^\circ$ flows through impedance find Average P

$$\text{if } Z = 20 \angle -22^\circ \Omega$$


$$P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \theta_v - \theta_i = \theta_Z \quad v = IZ = 20 \times 10 = 200$$

$$= \frac{1}{2} 200 \times 10 \cos(-22) = 927.18 \text{ W}$$

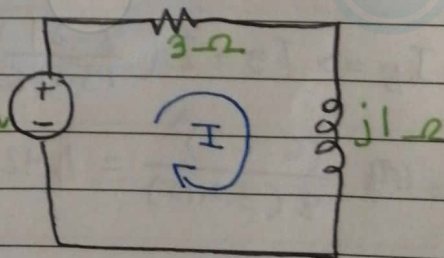Example: Avg Power Absorbed by Resistor & inductor, P supplied by the source

$$\text{total } Z = 3 + j2$$

$$I = \frac{8 \angle 45}{3 + j} = 2.53 \angle 26.56^\circ \quad 8 \angle 45^\circ \text{ V}$$



Avg Power in Resistor $\Rightarrow V_R = IR = 7.589 \angle 26.56$

$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (2.53) (7.589) \cos(0) = 9.6 \text{ W}$

Avg Power in inductor $V_L = IL = 2.53 \angle 116.57$

$P = \frac{1}{2} V_m I_m \cos(90) = 0 \text{ W}$

Avg Power Applied $= \frac{1}{2} (8) (2.53) \cos(45 - 26.57) = 9.6 \text{ W}$

* watch out for the signs and where the current enters the voltage.

Max Power transfer

if $X_L = -X_{th}$ and $R_L = R_{th}$

$P_{max} = \frac{|V_{TH}|^2}{8R_{TH}}$

if the load is purely real

$R_L = \sqrt{R_{th}^2 + X_{th}^2} = |Z_{th}|$

$Z_L = R_{th} - jX_{th} = Z_{th}^*$

\Rightarrow at max power transfer.


Example: find Z_L that absorbs max Avg Power, max Avg Power

$Z_1 = 8 \parallel j4 \Rightarrow 8 + j4 + j10 = 8 + 6j$

$= 8 + j14$

$Z_1 \parallel Z_2 = \frac{(8 + 6j) \times 5}{8 + 6j + 5} = 3.415 + j0.73 \Omega$

$Z_{th}^p = 3.415 - j0.73 \Omega = Z_L$

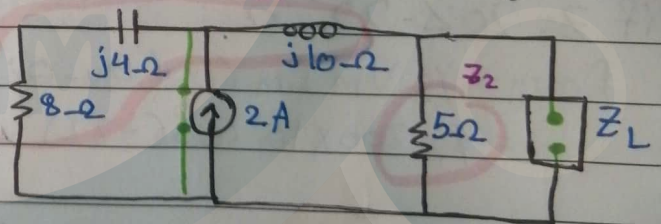

$V_{oc} = 5 I_5 \Rightarrow I_5 = 2 \left(\frac{8 - j4}{13 + j6} \right) = 0.25 \angle -57.34^\circ = V_{th}$

$P_{max} = \frac{(0.25)^2}{8(3.415)} = 1.429 \text{ W}$


Maximum Average Power for Resistive load

When load is purely resistive $R_L = \sqrt{R_{th}^2 + X_{th}^2} = |Z_{th}|$

* first find Z_{th} and V_{th} across R_L

$$80\Omega + j60\Omega = 80 + j60$$
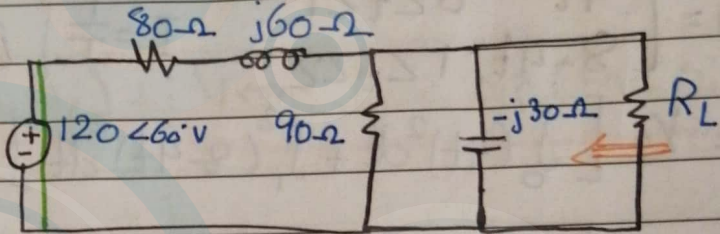
$$90 \parallel -j30 = \frac{90 \times -j30}{90 - j30}$$



$$= 9 - 27j \parallel 80 + j60 \Rightarrow 17.181 - j24.57\Omega = Z_{th}$$

$$R_L = |Z_{th}| = \sqrt{17.181^2 + 24.57^2} = 29.99\Omega \approx 30\Omega$$

$$V_{th} = 120\angle 60^\circ \left(\frac{9 - 27j}{(9 - 27j) + 80 + j60} \right) = 35.98\angle -31.91^\circ$$

$$\text{Current through load } I = \frac{V_{th}}{Z_{th} + R_L} = \frac{35.98\angle -31.91^\circ}{30 + (17.181 - j24.57)} = 0.67\angle -4.4^\circ$$

Max Avg Power absorbed by R_L is

$$P_{max} = \frac{1}{2} |I|^2 R_L = \frac{1}{2} \times (0.67)^2 \times 30 = 6.863 \text{ W}$$

Effective or RMS value

if AC $\Rightarrow P = \frac{1}{2} I_m^2 R$ if DC $\Rightarrow P = I_{eff}^2 R$

$$I_{eff} = I_m / \sqrt{2}$$

the effective value or root mean square (RMS) value of a periodic current is the DC value that delivers the same P/A-s per cycle current

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$P_R = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

Example

find RMS value of the current waveform, calculate Avg Power if the current is applied to a 9Ω resistor

$$i(t) = \begin{cases} 4t & 0 < t < 1 \\ 8-4t & 1 < t < 2 \end{cases} \quad I^2 = \frac{1}{T} \int_0^T i^2 dt$$

$$I^2 = \frac{1}{2} \left[\int_0^1 (4t)^2 dt + \int_1^2 (8-4t)^2 dt \right] = 16/3$$

$$I_{rms} = \sqrt{16/3} = 2.309A$$

$$P = I_{rms}^2 R = (16/3)(9) = 48W$$

Ex2) $T = \pi$, $v(t) = 8\sin(ct)$, $0 < t < \pi$, find RMS, Avg P, if $R = 6$

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{\pi} \int_0^{\pi} (8\sin(ct))^2 dt = 32$$

$$V_{rms} = \sqrt{32} = 5.65V \quad P = \frac{V_{rms}^2}{R} = \frac{32}{6} = 5.333W$$

Apparent Power = $V_{rms} \times I_{rms} = S$ (VA)

Power factor = $\cos(\theta_v - \theta_i) = \cos(\theta_2)$ (0 to 1) (unitless)

$P = S \times \text{Power factor}$

Example:- calculate PF seen by the source and the Avg power supplied by the source.

$$\text{total } Z \Rightarrow 10 + j4 \parallel (8 - j6) = 12.69 \angle 20.62^\circ$$

$$= 12.69 \angle 20.62^\circ$$


$$PF = \cos(\theta_2) = \cos(20.62) = 0.936 \text{ lagging}$$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{40 \angle 0^\circ}{12.69 \angle 20.62^\circ} = 3.152 \angle -20.62^\circ$$

Avg P supplied = Avg P absorbed

$$P = I_{rms}^2 R = (3.152)^2 (11.88) = 118W \text{ OR}$$
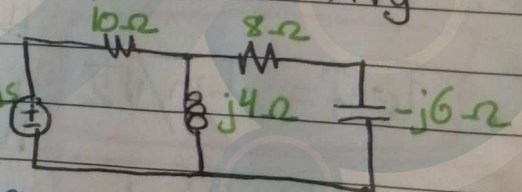
$$P = V_{rms} I_{rms} PF = (40)(3.152)(0.936) = 118W$$



Complex Power

$$V = V_m \angle \theta_v \quad I = I_m \angle \theta_i$$

$$S = \frac{1}{2} V I^* = |V_{rms}| |I_{rms}| \angle \theta_v - \theta_i$$

$$S = \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_P + j \underbrace{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_Q$$

P : is the average power in Watts (Active) delivered to a load and it's the only useful power (W)

Q : is the reactive power exchange btwn the source and the reactive part of the load (VAR)


$Q = 0$	resistive loads	unity pf	$X = 0$
$Q < 0$	capacitive loads	leading pf	$-jX + R$
$Q > 0$	inductive loads	lagging pf	$R + jX$

$$P = I_{rms}^2 R$$

$$Q = I_{rms}^2 X$$

$$S = \sqrt{P^2 + Q^2}$$

Power triangle

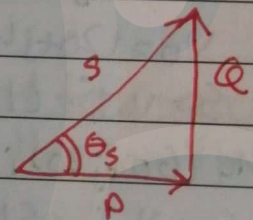

AC Power Calc


Example: The $60\ \Omega$ resistor absorbs 240W Avg Power, Calc V & Complex Power of each branch, total complex power?

$$P = I_2^2 R \Rightarrow I_2 = \sqrt{\frac{P}{R}} = \sqrt{\frac{240}{60}} = 2\text{ rms.}$$

$$V_0 = I_2 (60 + j20) = 120 + j40$$

$$I_1 = \frac{V_0}{30 - j30} = 3.2 + j2.4$$

$$I = I_1 + I_2 = 5.2 + j2.4$$

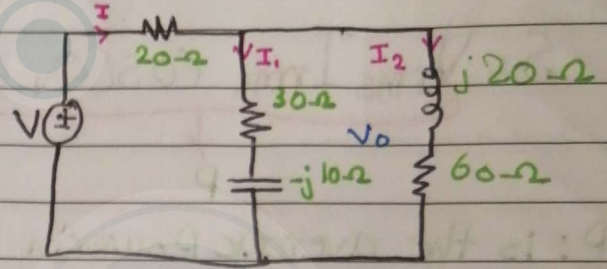

$$V = 20I + V_0 = (104 + j48) + (120 + j40)$$

$$V = 224 + j88 = 240.67 \angle 21.45^\circ \text{ rms}$$

for the $20\text{-}\Omega$ resistor

$$V = 20I = 204 + j48 = 114.54 \angle 24.8^\circ, I = 5.2 + j2.4 = 5.727 \angle 24.8^\circ$$

$$S = VI^* = (114.54 \angle 24.8^\circ)(5.727 \angle -24.8^\circ) \Rightarrow S = 656\text{ VA}$$

for the $(30 - j10)$ impedances

$$V_0 = 120 + j40 = 126.5 \angle 18.43^\circ, I_1 = 3.2 + j2.4 = 4 \angle 36.87^\circ$$

$$S_1 = V_0 I_1^* = (126.5 \angle 18.43^\circ)(4 \angle -36.87^\circ), S_1 = 506 \angle -18.44^\circ = 480 - j160\text{ VA}$$

for the $(60 + j20)$ impedance $I_2 = 2 \angle 0^\circ$

$$S_2 = V_0 I_2 = (126.5 \angle 18.43^\circ)(2 \angle 0^\circ) S_2 = 253 \angle 18.43^\circ = 240 + j80\text{ VA}$$

overall complex power supplied by the source

$$S_T = VI^* = (240.67 \angle 21.45^\circ)(5.727 \angle -24.8^\circ) = 1378 \angle -3.35^\circ = 1376 - j80\text{ VA}$$

Example: loads parallel, load 1 has 2kW , $\text{pf} = 0.75$ leading, load 2, 4kW $\text{PF} = 0.95$ lagging, find PF at 2 loads, complex power supplied by source

$$\text{load 1} \Rightarrow \text{leading} \Rightarrow -\cos(0.75) = \theta = -41.4$$

$$P_1 = S_1 \cos \theta, \Rightarrow S_1 = P_1 / \cos \theta = \frac{2000}{0.75} = \frac{2000}{\cos(-41.4)} = 2666.667$$

$$Q_1 = S_1 \sin \theta = -176.85, S_1 = P_1 + jQ_1 = 2000 - j176.85 \text{ (leading)}$$

$$\text{load 2} \Rightarrow P_2 = 4000, \text{PF} = 0.95 = \cos \theta_2 \Rightarrow \theta_2 = 18.19, S_2 = P_2 / \cos \theta_2 = 4210.53$$

$$Q_2 = S_2 \sin \theta_2 = 1314.4, S_2 = P_2 + jQ_2 = 4000 + j1314.4 \text{ lagging}$$

$$\text{Total complex power} \Rightarrow S = S_1 + S_2 = 6 - j0.4495\text{ kVA}$$

$$\text{PF} = P/|S| = 6000/6016.18 = 0.9972 \text{ leading}$$

* Complex real, reactive powers at the sources equal the respective sums of the complex, real, reactive powers at the individual loads

* For parallel circuits connection.

$$S = V_1 I_1^* + V_2 I_2^* + \dots + V_N I_N^*$$

$$S = S_1 + S_2 + \dots + S_N$$

Power Factor correction:

W8P2.

is the process of increasing the power factor without altering the voltage or current to the original load

preferable to have high value, necessary for economic reason.

put capacitance in parallel with inductive load, vice versa

$$Q_c = Q_1 - Q_2 = P(\tan \theta_1 - \tan \theta_2) = \omega C V_{rms}^2$$

$$Q_1 = S \sin \theta_1 = P(\tan \theta_1)$$

$$C = Q_c / \omega V_{rms}^2 = P(\tan \theta_1 - \tan \theta_2) / \omega V_{rms}^2$$

$$P = S_1 \cos \theta_1 \quad , \quad Q_2 = P \tan \theta_2$$

$$L = V_{rms}^2 / \omega Q_L$$

Example: find the value of the capacitance needed to correct a load at 140k VAR at 0.85 lagging pf to unity Pf. the load is supplied by a 110 volt(rms), 60Hz line.

$$pf = 0.85 = \cos \theta \quad , \quad \theta = 31.79^\circ$$

$$Q = S \sin \theta = S = Q / \sin \theta = 140 / \sin(31.79^\circ) = 265.8 \text{ KVA}$$

$$P = S \cos \theta = 225.93 \text{ kW}$$

for $Pf = 1 = \cos \theta \Rightarrow \theta_1 = 0$, since P remains same

$$P = P_1 = S_1 \cos \theta_1 \Rightarrow S_1 = P_1 / \cos \theta_1 = 225.93$$


$$Q_1 = S_1 \sin \theta_1 = 0 \Rightarrow Q_n = 0$$

difference btwn the new Q_1 and the old Q is Q_c

$$Q_c = 140 \text{ KVAR} = \omega C V_{rms}^2$$

$$C = \frac{140 \times 10^3}{(2\pi)(60)(110^2)} = 30.69 \text{ mF.}$$

Example: find V_s for the circuit

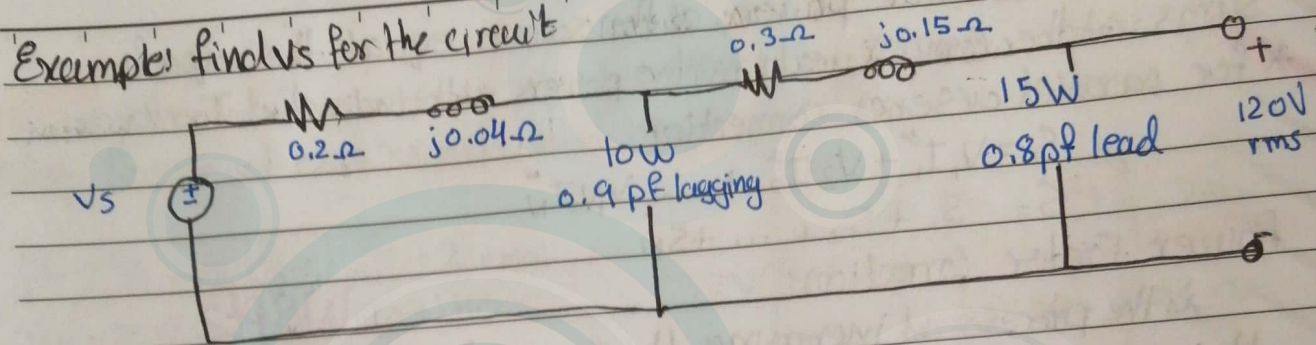

$$S_2 = 15 - j \frac{15}{0.8} \sin(\cos^{-1}(0.8)) = 15 - j11.25$$

$$S_2 = V_2 I_2^*, \quad I_2^* = S_2 / V_2 = 15 - j11.25 / 120 = 0.125 + j0.09375$$

$$V_1 = V_2 + I_2(0.3 + j0.15)$$

$$V_1 = 120 + (0.125 + j0.09375)(0.3 + j0.15), \quad V_1 = 120.02 + j0.0469$$

$$S_1 = 10 + j \frac{10}{0.9} \sin(\cos^{-1}(0.9)) = 10 + j4.843$$

$$S_1 = V_1 I_1^*, \quad I_1^* = S_1 / V_1 = \frac{11.111 \angle 25.84^\circ}{120.02 \angle 0.22^\circ} = I_1 = 0.093 \angle -25.82^\circ$$

$$I_1 = 0.0837 - j0.0405, \quad I = I_1 + I_2 = 0.2087 + j0.053$$

$$V_s = V_1 + I(0.2 + j0.04)$$

$$V_s = (120.02 + j0.0469) + (0.2087 + j0.053)(0.2 + j0.04)$$

$$V_s = 120.06 + j0.0658 \quad V_s = 120.66 \angle 0.03^\circ \text{ V}$$

Example: A 120-V rms, 60-Hz source, find pf, C

$$\theta_1 = \cos^{-1}(0.8) = 36.87^\circ, \quad S_1 = P_1 / \cos \theta_1 = \frac{24}{0.8} = 30 \text{ kVA}$$

$$Q_1 = S_1 \sin \theta_1 = 30 (\sin 36.87^\circ) = 18 \text{ kVAR}, \quad S_1 = 24 + j18 \text{ kVA}$$

$$\theta_2 = \cos^{-1}(0.95) = 18.19^\circ, \quad S_2 = P_2 / \cos \theta_2 = \frac{40}{0.95} = 42.105 \text{ kVA}$$


$$Q_2 = S_2 \sin \theta_2 = 13.144 \text{ kVAR}, \quad S_2 = 40 + j13.144 \text{ kVA}$$

$$S = S_1 + S_2 = 64 + j31.144 \text{ kVA}$$

$$\theta = \tan^{-1}(31.144/64) = 25.95^\circ \quad \text{pf} = \cos \theta = 0.8992 \text{ (lagging)}$$

$$\theta_2 = 25.95^\circ, \theta_1 = 0^\circ, \quad Q_c = P(\tan \theta_2 - \tan \theta_1) = 64 \tan(25.95^\circ) = 31.144 \text{ kVAR}$$




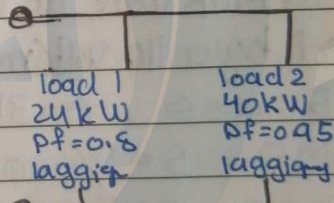
$$C = \frac{Q_c}{\omega V_{\text{rms}}^2} = \frac{31.144}{2\pi(60)(120)^2} = 5.74 \text{ mF}$$





Three-Phase-System pt!

wq pt!

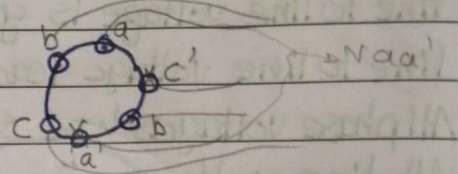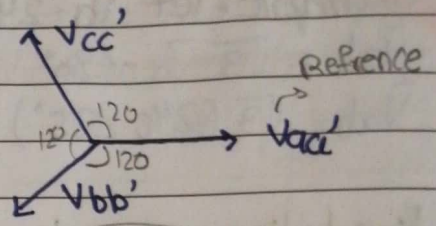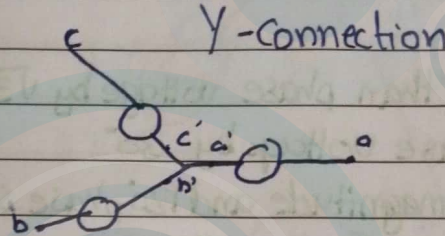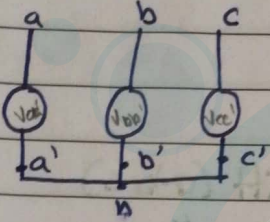3 phase \Rightarrow produces constant power
 \Rightarrow has 6 terminal wires
 connected as Y or Delta.




Delta connected

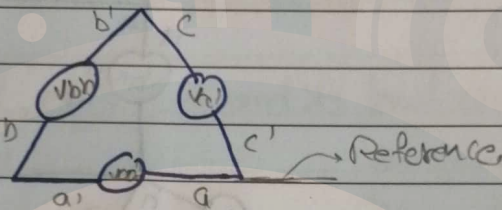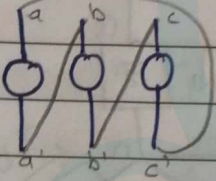

phase voltage \Rightarrow Phase to ground voltage
 line voltage \Rightarrow line to line voltage

$$\begin{aligned} \bar{V}_{an} &= \bar{V}_a = V \angle 0^\circ \\ \bar{V}_{bn} &= \bar{V}_b = V \angle -120^\circ \\ \bar{V}_{cn} &= \bar{V}_c = V \angle 120^\circ \end{aligned}$$

positive sequence

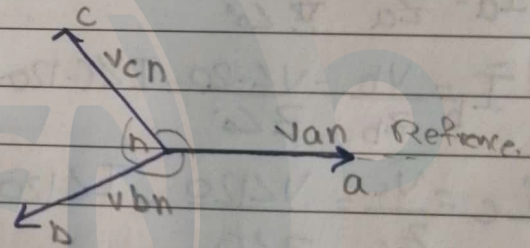

$$\begin{aligned} \bar{V}_{ab} &= \bar{V}_{an} - \bar{V}_{bn} = (V \angle 0^\circ) - (V \angle -120^\circ) = \sqrt{3} V \angle 30^\circ \\ \bar{V}_{bc} &= \sqrt{3} V \angle -90^\circ \\ \bar{V}_{ca} &= \sqrt{3} V \angle 150^\circ \end{aligned}$$

unless stated otherwise:

- all voltages are line-line
- all powers are for 3 phase
- positive sequence
- voltage sources are all balanced.

Example: let $V_a = 240 \angle 25^\circ$, calculate line-line voltages

$$\bar{V}_{ab} = \sqrt{3} \bar{V}_a \angle 30^\circ$$

$$\bar{V}_{ab} = \sqrt{3} (240 \angle 25^\circ) \angle 30^\circ = 415.7 \angle 55^\circ$$

line to line voltage is greater than phase voltage by $\sqrt{3}$

line to line voltage leads phase voltage by 30°

All phase voltages have same magnitude and 120° phase shift (a-b-c)

All line voltages " " " " " "

$$\bar{Z}_a = \bar{Z}_b = \bar{Z}_c = \bar{Z}$$

$$\bar{V}_{an} = \bar{V}_a = V \angle 0^\circ$$

$$\bar{V}_{bn} = \bar{V}_b = V \angle -120^\circ$$


$$\bar{V}_{cn} = \bar{V}_c = V \angle 120^\circ$$

$$\bar{I}_a = \frac{\bar{V}_a}{\bar{Z}_a} = \frac{V \angle 0^\circ}{Z \angle \theta} = I \angle -\theta$$

$$\bar{I}_b = \frac{\bar{V}_b}{\bar{Z}_b} = \frac{V \angle -120^\circ}{Z \angle \theta} = I \angle (-120^\circ - \theta)$$

$$\bar{I}_c = \frac{\bar{V}_c}{\bar{Z}_c} = \frac{V \angle 120^\circ}{Z \angle \theta} = I \angle (120^\circ - \theta)$$
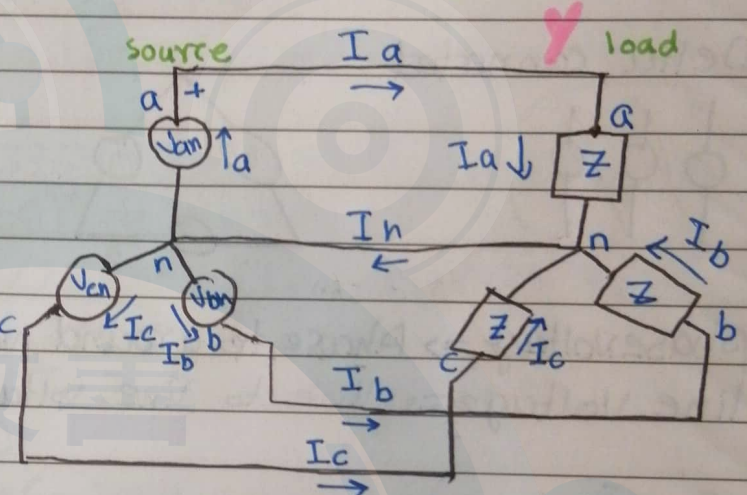
$$\bar{I}_n = \bar{I}_a + \bar{I}_b + \bar{I}_c = 0$$



load voltage is equal to line-line voltage

line current is greater than load current $\bar{I}_a = \sqrt{3} \bar{I}_{ab} \angle -(\theta + 30^\circ)$

line current lags load current by 30°

\bar{I}_a = line current

\bar{I}_{ab} = generator current


$$\bar{I}_{ab} = \bar{I}_a + \bar{I}_{ca}$$

$$\bar{I}_{ab} = \frac{\bar{I}_a}{\sqrt{3}} \angle 30^\circ$$

$$\bar{I}_{bc} = \bar{I}_{ab} \angle \theta_{bc} - 120^\circ$$

$$\bar{I}_{ca} = \bar{I}_{ab} \angle \theta_{bc} + 120^\circ$$
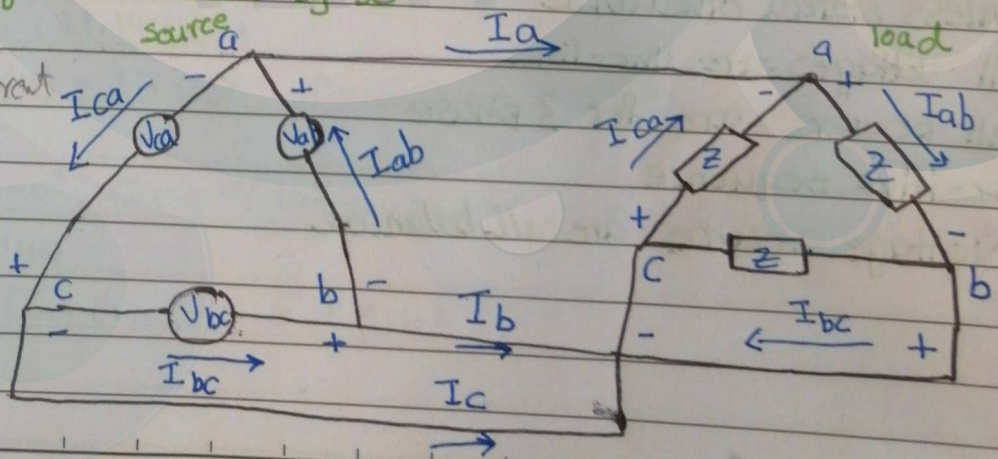
$$\bar{I}_{ac} = \bar{I}_{ca} \angle \theta_{ca} - 180^\circ$$




Mixed Connections

in this case, transform one

Y- Δ Transformation

$$Z_Y = \frac{1}{3} Z_{\Delta}$$

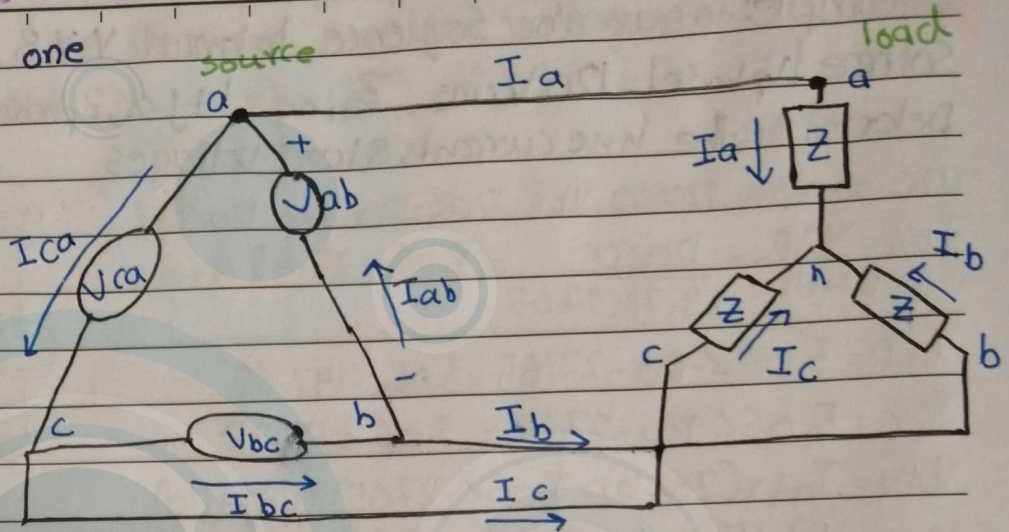

Example! Current at load, eq Y load and its load current

$V_{an} \Rightarrow$ phase voltage = 120V


$$\text{Current at load } \bar{I}_{ab} = \frac{V_{ab}}{Z} = \frac{\sqrt{3} \times 120 \angle 30^\circ}{5 \angle 37^\circ} = 41.57 \angle -7^\circ \text{ A}$$

$$\text{Part 2} \Rightarrow Z_Y = \frac{Z_{\Delta}}{3} = \frac{5 \angle 37^\circ}{3} = 1.67 \angle 37^\circ$$

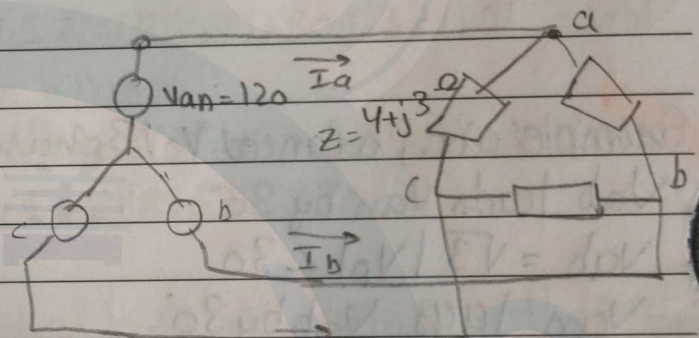Part 3 \Rightarrow load current in Δ load =

$$\bar{I}_a = \sqrt{3} I_{ab} \angle -30^\circ = \sqrt{3} (41.57 \angle -7^\circ) \angle -30^\circ = 72 \angle -37^\circ \text{ A}$$

$$I_c = 72 \angle -37^\circ + 120, I_{ac} \Rightarrow I_{ca} = 41.57 \angle -7^\circ + 120 \quad I_{bc} = I_{ca} \angle \theta - 180^\circ$$




Example! calculate line current

2 loads in parallel, transform 1

$$Z_{2Y} = \frac{1}{3} Z_2 = \frac{12 - j9}{3} = 4 - j3 \Omega$$

$$Z_{1Y} \parallel Z_{2Y} = 25/8 \Omega$$
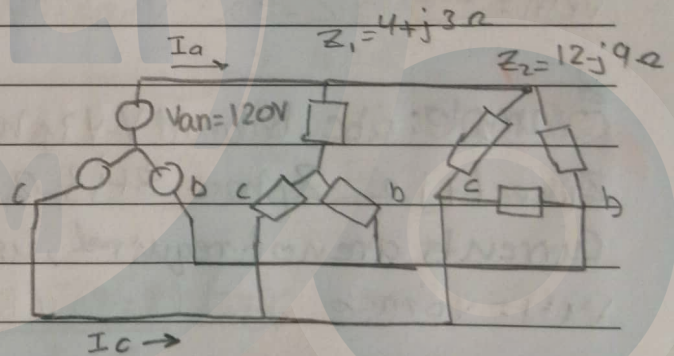
$$I_a = \frac{120 \angle 0^\circ}{25/8} = 38.4 \text{ A}$$



Example: for an abc sequence, balanced Y-Y 3 phase circuit
 Source $V_{\text{phase}} = 120 \text{ V}_{\text{rms}}$, $Z_{\text{line}} = 1 + j2$, $Z_{\text{phase}} = 20 + j10$
 Determine the line currents & load voltages

abc $\Rightarrow V_{\text{an}} = 120 \angle 0^\circ$, $V_{\text{bn}} = 120 \angle -120^\circ$, $V_{\text{cn}} = 120 \angle 120^\circ$

$I_{\text{aA}} = \frac{V_{\text{an}}}{21 + j11} = \frac{120 \angle 0^\circ}{23.71 \angle 27.65^\circ} = 5.06 \angle -27.65^\circ \text{ A}_{\text{rms}}$


$I_{\text{bB}} = 5.06 \angle -120 - 27.65 = 5.06 \angle -147.65^\circ$

$I_{\text{cC}} = 5.06 \angle 120 - 27.65 = 5.06 \angle 92.35^\circ$

$V_{\text{AN}} = I_{\text{aA}} \times (20 + j10) = (5.06 \angle -27.65^\circ) \times (20 + j10)$
 $= 113.15 \angle -1.08^\circ \text{ V}_{\text{rms}}$

$V_{\text{BN}} = 113.15 \angle -1.08 - 120 = 113.15 \angle -121.08^\circ \text{ V}_{\text{rms}}$

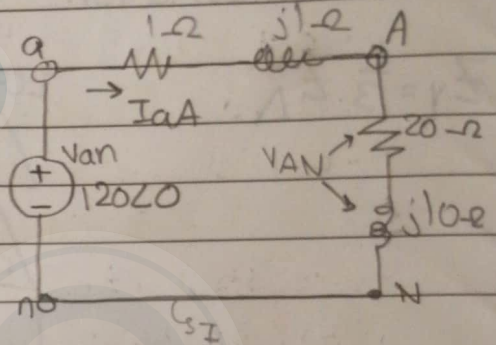$V_{\text{CN}} = 113.15 \angle -1.08 + 120 = 113.15 \angle 118.92^\circ \text{ V}_{\text{rms}}$



Example: abc, balanced Y-Y 3 phase $V_{\text{an}} = 120 \angle 90^\circ \text{ V}_{\text{rms}}$ find line voltage

V_{ab} leads V_{an} by 30°

$V_{\text{ab}} = \sqrt{3} |V_{\text{p}}| \angle 30^\circ$

V_{an} lags V_{ab} by 30°

$V_{\text{ab}} = \sqrt{3} \times 120 \angle 120^\circ$, $V_{\text{bc}} = \sqrt{3} \times 120 \angle 0^\circ$, $V_{\text{ca}} = \sqrt{3} \times 120 \angle 240^\circ$

$V_{\text{ab}} = 208 \angle 0^\circ$, find phase voltage

$V_{\text{an}} = \frac{208}{\sqrt{3}} \angle -30^\circ$, $V_{\text{bn}} = \frac{208}{\sqrt{3}} \angle 150^\circ$, $V_{\text{cn}} = \frac{208}{\sqrt{3}} \angle 90^\circ$

Example: abc, balanced Y-Y 3 phase $V_{\text{phase}} = 104.02 \angle 26^\circ$

$Z_{\text{line}} = 1 + j2$, $Z_{\text{phase}} = 8 + j3$ determine source phase voltage

Currents are not required, use inverse voltage divider


$V_{\text{AN}} = V_{\text{phase}} \quad V_{\text{an}} = \frac{(8 + j3)}{(8 + j3) + (1 + j2)} V_{\text{AN}}$

$V_{\text{AN}} = 1.15 \angle 3.41^\circ$

$V_{\text{an}} = 120 \angle 30^\circ$

$V_{\text{bn}} = 120 \angle -90^\circ$

$V_{\text{cn}} = 120 \angle 150^\circ$

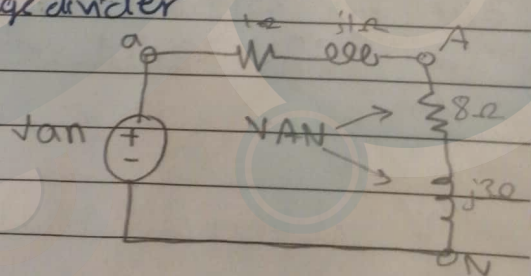

Example: Determine line currents and line voltages at the loads

Source is Delta connected

Convert to Y

$V_{ab} = V_L \angle 0^\circ$

$V_{bc} = V_L \angle -120^\circ$

$V_{ca} = V_L \angle 120^\circ$

$V_{an} = V_L / \sqrt{3} \angle -30^\circ$

$V_{bn} = V_L / \sqrt{3} \angle -150^\circ$

$V_{cn} = V_L / \sqrt{3} \angle 90^\circ$

Analyse one phase $I_{aA} = \frac{208 / \sqrt{3} \angle -30^\circ}{12.1 + j4.2} = 9.38 \angle -49.14^\circ$

$V_{AN} = (12 + j4) \times 9.38 \angle -49.14^\circ = 118.65 \angle -30.71^\circ$

$V_{ab} = \sqrt{3} |V_p| \angle 30^\circ$ $V_{AB} = \sqrt{3} \times 118.65 \angle 0.71^\circ$


Determine the other phases using the balance.

$I_{bB} = 9.38 \angle -169.14^\circ$

$V_{BC} = \sqrt{3} \times 118.65 \angle -119.29^\circ$

$I_{cC} = 9.38 \angle -71.86^\circ$

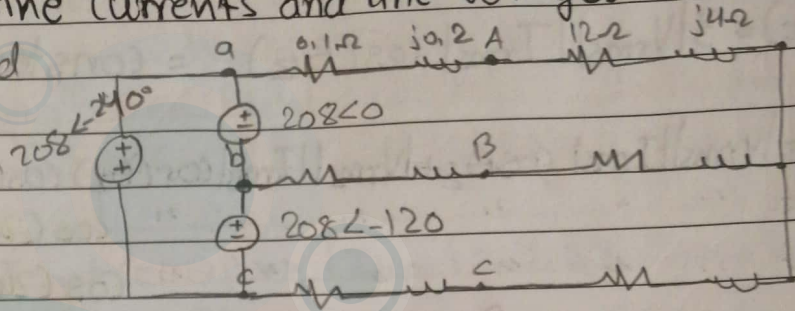$V_{CA} = \sqrt{3} \times 118.65 \angle 120.71^\circ$



Example: Delta connected load consists of $10\text{-}\Omega$ series with 20mH inductance
source is Y connected, abc, $120\text{-V}_{\text{rms}}$, 60Hz , find all line and phase currents

no need to convert, i have V_{an}

$V_{an} = 120 \angle 30^\circ$, $V_{AB} = 120\sqrt{3} \angle 60^\circ$

$Z_{\text{inductance}} = 2\pi \times 60 \times 0.02 = 7.54\text{-}\Omega$

$Z_{\Delta} = 10 + j7.54\text{-}\Omega = 12.52 \angle 37.02^\circ$, $Z_Y = 4.17 \angle 37.02^\circ$

$I_{AB} = V_{AB} / Z_{\Delta} = 120\sqrt{3} \angle 60^\circ / 12.52 \angle 37.02^\circ = 16.6 \angle 22.98^\circ$

$I_{BC} = 16.6 \angle -97.02^\circ$ $I_{CA} = 16.6 \angle 142.98^\circ$

$I_{aA} = 28.75 \angle -7.02^\circ$, $I_{bB} = 28.75 \angle -127.02^\circ$, $I_{cC} = 28.75 \angle 112.98^\circ$


$|V_L| = \sqrt{3} |V_{\text{phase}}|$, $\theta_L = \theta_{\text{phase}} + 30^\circ$

line-phase voltage relationship

$|I_{\text{line}}| = \sqrt{3} |I_{\Delta}|$

$\theta_{\text{line}} = \theta_{\Delta} - 30^\circ$

line-phase current relationship.

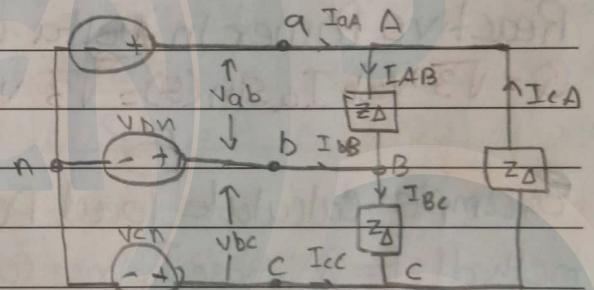

3 Phase Power

wloptl.

$$P(t) = 3 |V_{rms}| |I_{rms}| \cos(\theta_z) = \text{constant}$$

$$P_a(t) = |V_{rms}| |I_{rms}| \cos \theta_z + |V_{rms}| |I_{rms}| \cos(\theta_z) \cos(2\omega t + 2\theta_v - \theta_z)$$

$$P_b(t) = \dots \dots \dots \cos(2\omega t + 2\theta_v - 120^\circ - \theta_z)$$

$$P_c(t) = \dots \dots \dots \cos(2\omega t + 2(\theta_v + 120^\circ) - \theta_z)$$

$$P = V_{\text{phase}} I_{\text{phase}} \cos(\theta) \quad \theta = \theta_v - \theta_i = \text{pf}$$

for single phase $\rightarrow Q = V_{\text{phase}} I_{\text{phase}} \sin(\theta)$ θ is the angle b/w phase voltage & phase current.

for 3-phase $\rightarrow P = 3 V_{\text{phase}} I_{\text{phase}} \cos(\theta)$
 $\rightarrow Q = 3 V_{\text{phase}} I_{\text{phase}} \sin(\theta)$

Real Power in Y circuit

$$P = \sqrt{3} V_{ab} I_a \cos(\theta) = \sqrt{3} V_{\text{line}} I_{\text{line}} \cos(\theta) \quad \theta_z$$

Reactive Power in Y circuit

$$Q = \sqrt{3} V_{ab} I_a \sin(\theta) = \sqrt{3} V_{\text{line}} I_{\text{line}} \sin(\theta)$$

Real Power in Delta circuit $\rightarrow \sqrt{3} V_{ab} I_a \cos(\theta) = \sqrt{3} V_{\text{line}} I_{\text{line}} \cos(\theta)$

$$P = 3 V_{\text{phase}} I_{\text{phase}} \cos(\theta) = 3 V_{ab} I_{ab} \cos(\theta)$$


Reactive Power in Delta circuit

$$Q = \sqrt{3} V_{ab} I_a \sin(\theta) = \sqrt{3} V_{\text{line}} I_{\text{line}} \sin(\theta)$$

Example: calculate load Power

method 1: $P = 3 V_{\text{phase}} I_{\text{phase}} \cos \theta$


$$P = 3 V_{ab} I_{ab} \cos \theta = 3 \times (\sqrt{3} \times 120) \times \frac{\sqrt{3} \times 120 \angle 30}{4 - (j \times 3)} \times \cos(\tan^{-1}(-3/4)) = 20.736 \text{ kW}$$

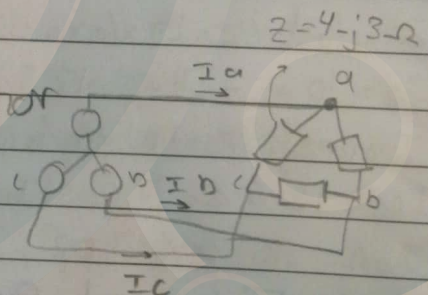

method 2: $P = \sqrt{3} V_{\text{line}} I_{\text{line}} \cos \theta$

$$P = \sqrt{3} V_{ab} I_a \cos \theta = \sqrt{3} \times 208 \times 72 \times \cos(\tan^{-1}(-3/4)) = 20.736 \text{ kW}$$

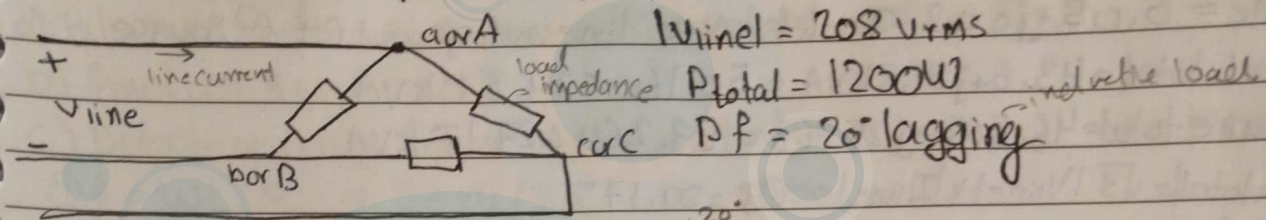Example: determine the magnitude of the line currents and the value of load impedance per phase in the delta.



$$P_{total} = \sqrt{3} |V_{line}| |I_{line}| \cos \theta_f \Rightarrow |I_{line}| = 3.54 \text{ Arms}$$

$$Q_{total} = \sqrt{3} |V_{line}| |I_{line}| \sin \theta_f$$

$$|I_{line}| = \sqrt{3} |I_{\Delta}| \Rightarrow |I_{\Delta}| = 2.05 \text{ Arms}, \theta_{line} = \theta_{\Delta} - 30^\circ$$

$$|Z_{\Delta}| = |V_{line}| / |I_{\Delta}| = 101.46 \angle +20^\circ$$

Example: abc, balanced Y-Y 3 phase, source $V_{phase} = 120V_{rms}$

$Z_{line} = 1 + j2$, $Z_{phase} = 20 + j10 - 2$, determine real & reactive

power per phase at the load, and total real, reactive and complex power @ the source

balanced circuit \Rightarrow data on any phase is sufficient

$$V_{an} = 120 \angle 0^\circ, V_{bn} = 120 \angle -120^\circ, V_{cn} = 120 \angle 120^\circ$$

$$I_{aA} = V_{an} / (2 + j11) = 120 \angle 0^\circ / 23.7 \angle 27.65^\circ = 5.06 \angle -27.65^\circ$$

$$V_{AN} = I_{aA} \times (20 + j10) = 5.06 \angle -27.65^\circ \times 22.36 \angle 26.57^\circ = 113.15 \angle -1.08^\circ$$

$$S_{phase} = V_{AN} I_{aA}^* = 113.15 \angle -1.08^\circ \times 5.06 \angle 27.65^\circ = 572.54 \angle 26.57^\circ = 512 + j256.09$$

$$S_{source\ phase} = V_{an} I_{aA}^* = 120 \angle 0^\circ \times 5.06 \angle 27.65^\circ = 607.2 \angle 27.65^\circ = 537.86 + j281.78 \text{ VA}$$

$$P_{total\ source} = 3 \times 537.86 \text{ W}, Q_{total\ source} = 3 \times 281.78 \text{ VA}, S_{total\ source} = P_{ts} + jQ_{ts} = 1582.6 \text{ VA}$$

Example: total S, combined pf

load 1: 24 kW @ pf = 0.6 lagging

load 2: 10 kW @ pf = 1, load 3: 12 kVA @ pf = 0.8 leading

$$P_1 = 24 \text{ kW}, pf = 0.6 \text{ lag} \Rightarrow |S_1| = 40 \text{ kVA}, Q_1 = \sqrt{|S_1|^2 - P_1^2} = 32 \text{ kVA}$$

$$\text{lagging} \Rightarrow \text{inductive } S_1 = 24 + j32 \text{ VA} \times 10^3$$

$$P_2 = 10 \text{ kW}, pf = 1 \Rightarrow S_2 = 10 + j0 \text{ kVA}$$

$$P_3 = 9.6 \text{ kW}, |Q_3| = 7.2 \text{ kVA leading pf} \Rightarrow \text{capacitive } S_3 = 9.6 - j7.2 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 43.6 + j24.8 \text{ kVA} = 50.16 \angle 29.63^\circ \text{ pf} = 0.869 \text{ lagging}$$

Continued:

If line current = 139.23 Arms and if the line impedance $Z_{line} = 0.05 + j0.02 \Omega$ determine line voltage and pf @ source

$$S_{load\ total} = 43.6 + j24.8 \text{ kVA} = 50.16 \angle 29.63^\circ \text{ kVA}$$

$$S_{source\ total} = 46.508 + j25.963 = 53.264 \angle 29.17^\circ \text{ kVA}$$

$$|S_{total}| = \sqrt{3} |V_{line}| |I_{line}| \quad \theta_f = 29.17^\circ$$

$$|I_{line}| = 139.23 \text{ Arms}$$

$$S_{line} = 3 \times Z_{line} I_{line} I_{line}^* = 3 \times Z_{line} |I_{line}|^2$$

$$S_{line} = 2908 + j1163 \text{ (VA)}$$

$$V_{line} = 53.264 / \sqrt{3} \times 139.13 = 220.87 \text{ V rms}$$

$$\text{pf} = \cos \theta_f = \cos (29.17^\circ) = 0.873 \text{ lagging}$$

Resonance

will ptl.

must be pure resistive

$$\omega_0 = 1/\sqrt{LC} \text{ rad/s or } f_0 = 1/2\pi\sqrt{LC} \text{ Hz}$$

$$Z = R + j(\omega L - 1/\omega C)$$

$$Z = R \text{ @ Resonance } I = V_s/R \quad P = R I_{rms}^2$$

$$V_L = V_s \quad |V_L| = |V_C|$$

$$V_L = I(\omega L) = (V_s/R)(\omega L) = V_s(\omega L/R)$$

$$\text{if } \omega L/R > 1 \Rightarrow V_L > V_s$$

$$V_C = (V_s/R) / \omega C = V_s / R(\omega C)$$

$$\text{Quality factor} = V_L = V_s = \omega L/R = 1/\omega C R$$

$$1/(\omega C R) = QF, \quad QF = \text{Reactive Power} / \text{Real Power} = \text{Stored } \epsilon / \text{dissipated}$$

Frequency response at resonance circuit current

$$I = |I| = V_m / \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$\omega_2 - \omega_1 = BW$$

$$\text{Average Power } P(\omega) = \frac{1}{2} I^2 R$$

$$\text{Highest Power } P(\omega_0) = \frac{1}{2} V_m^2 / R$$

$$\text{Half Power} = P(\omega_1) = P(\omega_2) = \frac{1}{2} \frac{(V_m/\sqrt{2})^2}{R} = \frac{V_m^2}{4R}$$

$$\omega_1 = R/2L + \sqrt{(R/2L)^2 + 1/LC} = \omega_2 \quad \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\text{Bandwidth } B = \omega_2 - \omega_1$$

Example: a series connected circuit has $R=4\Omega$, $L=25\text{mH}$

- a) Calculate value of C that will produce a Q of 50.
- b) find ω_1 & ω_2 and B
- c) Determine avg Power dissipated at $\omega = \omega_0, \omega_1, \omega_2$ $V_m = 100\text{V}$

$$Q = \frac{\omega L}{R} \Rightarrow 50 \times 4 / 25 = \omega_0 = 8000 \text{ rad/sec}$$

$$= (\frac{1}{LC})^{0.5} = C$$

d) $B = \omega_0 / Q \Rightarrow 8000 / 50 = 160 \text{ rad/s}$

$$\omega_1 = \omega_0 - B\omega/2, \quad \omega_2 = \omega_0 + B\omega/2$$

c) $P_{\omega_0} = (100^2 / 4(2 \times 4))$ $P(\omega_1) = 0.5 P(\omega_0) = P(\omega_2)$

Parallel Resonance.

$$Y = 1/R + j(\omega C - 1/\omega L) \rightarrow \text{when } Y=0$$


Resonance frequency $\omega_0 = 1/\sqrt{LC}$ rad/s or $f_0 = 1/2\pi\sqrt{LC}$ Hz

@ Resonance $Y = G = 1/R$

$$B\omega = \omega_0 / Q$$

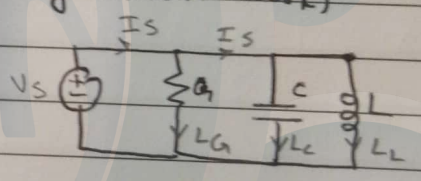Example: if the source operates @ resonant frequency of the network, compute all branch currents

$V_s = 120 \angle 0^\circ$, $G = 0.01 \text{ S}$, $C = 600 \mu\text{F}$, $L = 120 \text{ mH}$



$$I_G = 0.01 \times 120 \angle 0^\circ = 1.2 \angle 0^\circ = I_s$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{0.12 \times (6 \times 10^{-4})} = 117.85 \text{ rad/s}$$

$$I_C = (1 \angle 90^\circ) \times (117.85) \times 600 \times 10^{-6} \times 120 \angle 0^\circ = 8.49 \angle 90^\circ$$

$$I_L = 8.49 \angle -90^\circ$$

$$I_G = G V_s$$

$$I_C = j\omega C V_s = \frac{j\omega C}{Y} I_s$$

$$I_L = 1/j\omega L V_s = \frac{1/j\omega L}{Y} I_s$$

Example: resonant frequency

$$Z = 10 \angle 0^\circ + j\omega L$$

$$C = 1/(\omega_0 \cdot 2) + j\omega L$$

$$\omega = \frac{\sqrt{19}}{2} = 2.179 \text{ rad/s}$$

tab/2 imag = 0

End of Electrical
2020/2021 Fall