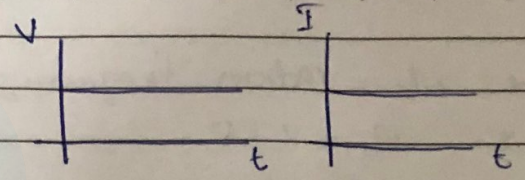




20/7/2020

Time dependent signal sources

DC sources → fixed value



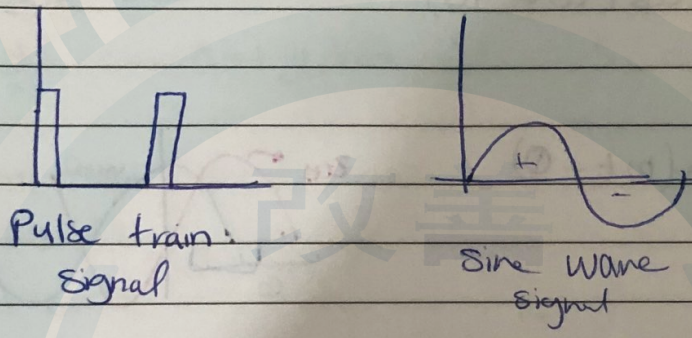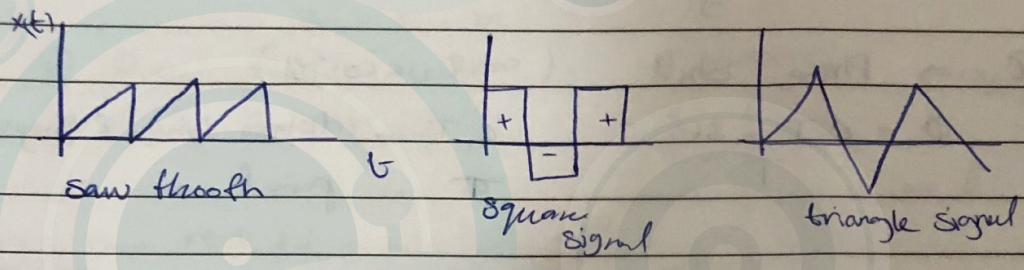
AC sources → generates voltages & currents varying with time



* Periodic signal: its a signal which repeats itself after one periode (T)

* Sinusoidal signals

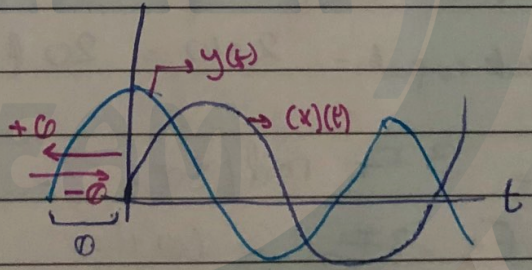
$X(t) = A \cos(\omega t + \theta)$
 $y(t) = B \cos \omega(t)$



cos 180 = sin 0

Peak to peak

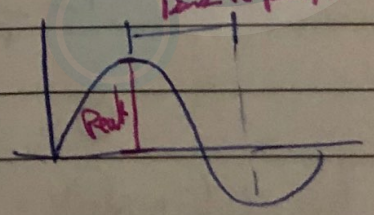Amplitude of signal, peak value
 Peak → P
 Peak to peak → 2P



* ω = radian frequency \Rightarrow unit: rad/sec

$$\omega = 2\pi f$$

* f : Natural frequency \rightarrow unit: Hz


* Period $\Rightarrow T = \frac{1}{f}$ sec

* $\phi \Rightarrow$ Phase shift ($\cos 0$ vs $\cos 180^\circ$)

* $\phi = \Delta T \times \frac{360}{T}$ $\Delta T \rightarrow$ distance btw 2 signals in second
 $T \rightarrow$ period

$$\sin \omega t = \cos(\omega t - 90^\circ)$$

$$z(t) = \cos(\omega t + \phi)$$

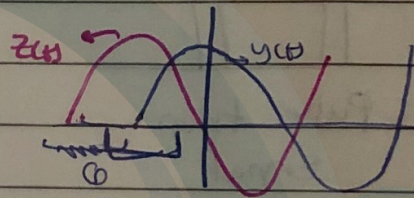

$$\text{ex } i(t) = 10 \cos(377t + 30^\circ)$$

$$I_{\text{peak}} = 10 \text{ A}$$

$$I_{\text{Peak to peak}} = 2 \times 10 = 20 \text{ A}$$

$$\omega = 377 \text{ rad/sec} = 2\pi f$$

$$f = \frac{377}{2\pi} = 60 \text{ Hz}$$

$$T = \frac{1}{f} = .016 \text{ sec}$$

$$\phi = 30^\circ$$

$$i(.1 \text{ sec}) = 10 \cos(377 \times .1 + 30) = 7.8 \text{ A}$$

* moved to left +30

Complex number

$$i / j = \sqrt{-1}$$

$$j^2 = -1$$


Complex number has 2 form

① rectangular form

$$Z = x + jy$$

② Polar form


$$Z = r / \theta$$

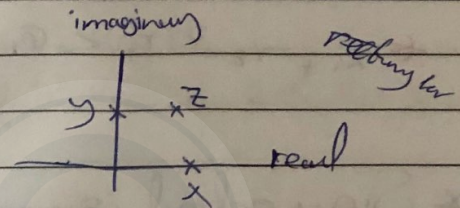

* conversion from rect to polar

$$r = \sqrt{x^2 + y^2}$$
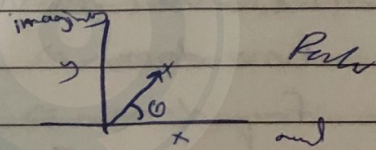
$$\theta = \tan^{-1} \frac{y}{x} \rightarrow z = r / \theta$$




* conversion from polar to rect


$$x = r \cos \theta$$

$$y = r \sin \theta$$


EX $Z_1 = 4 + 3j$

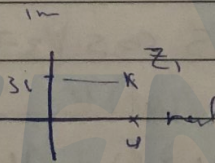

$$Z_2 = 16$$

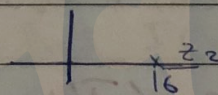

$$Z_3 = -3j$$

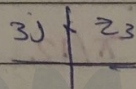

* Mathematical op.

1 addition

$$X_1 = a + jb \quad X_2 = c + jd$$

$$X_1 + X_2 = a + c + j(b + d)$$

2 subtraction

$$X_1 - X_2 = a - c + j(b - d)$$

3 Multiplication

$$X_1 \cdot X_2 = (a + jb) \cdot (c + jd) = ac + jad + jcb - bd$$

4 division

$$\frac{X_1}{X_2} = \frac{a + jb}{c + jd} \cdot \frac{(c - jd)}{(c - jd)} = \frac{ac + bd}{c^2 - d^2} + j \frac{bc - ad}{c^2 - d^2}$$

* Polar

$$X_1 = r_1 \angle \theta_1$$

$$X_2 = r_2 \angle \theta_2$$

$$\star X_1 + X_2 = r_1 \angle \theta_1 + r_2 \angle \theta_2 = r_1 r_2 \angle \theta_1 + \theta_2$$

$$\star \frac{X_1}{X_2} = \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle \theta_1 - \theta_2$$

$$\star X_1 - X_2 = r_1 \angle \theta_1 - r_2 \angle \theta_2 \rightarrow \text{use calculator}$$

* Sinusoidal signals in freq domain

time domain $\Rightarrow X(t) = A \cos(\omega t + \theta)$

freq domain $\Rightarrow X(j\omega) = A \angle \theta \rightarrow$ phase shift returned to cosine signal

cos الزاوية لا يتم تحويلها

↳ peak value

ex) $V_1(t) = 15 \cos(377t + \frac{\pi}{4})$ V

$$V_2(t) = 15 \cos(377t + \frac{\pi}{2})$$
 V

find $V_s(t) = V_1(t) + V_2(t)$

Solu:

$$V_1(j\omega) = 15 \angle \frac{\pi}{4} = 10.61 + j 10.61$$
 V

$$V_2(j\omega) = 15 \angle \frac{\pi}{2} = 14.49 + j 3.88$$
 V


$$V(s)(j\omega) = V_1(j\omega) + V_2(j\omega)$$

$$= 25.1 + j 14.49$$

$$= 28.98 \angle \frac{\pi}{6}$$

$$V_s(t) = 28.98 \cos(377t + \frac{\pi}{6})$$

* الزاوية 377 غير

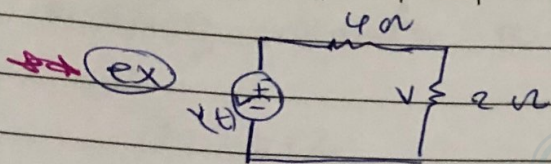

$$V(t) = 12 \cos(377t + 40^\circ)$$

find $i(t) + V_2(t)$

$$\bar{V}_{j\omega} = 12 \angle 40$$

$$V_2(\bar{I}\omega) = \frac{(12 \angle 40) * 2}{2 + 4} = 4 \angle 40$$

$$V_2(t) = 4 \cos(377t + 40) \text{ V}$$


$$\bar{I}(j\omega) = \frac{V_2(j\omega)}{2} = \frac{4 \angle 40}{2} = 2 \angle 40 \text{ A}$$

$$i(t) = 2 \cos(377t + 40) \text{ A}$$

* Impedance:

→ we will describe the circuit elements RLC in AC circuit → they will have impedance

(1) Resistor

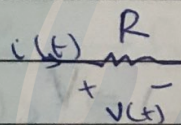

if $V(t) = V_{amp} \cos(\omega t + \theta)$

$$\bar{V}(j\omega) = V_m \angle \theta$$

$$V = IR$$

to find $\bar{I}(j\omega) = \frac{\bar{V}(j\omega)}{R} = \frac{V_m \angle \theta}{R} = \frac{V_m}{R} \angle \theta$

$$i(t) = \frac{V_m}{R} \cos(\omega t + \theta)$$

$$Z(j\omega) = \frac{V(j\omega)}{\bar{I}(j\omega)} = \frac{V_m \angle \theta}{\frac{V_m}{R} \angle \theta} = R \angle 0$$

$$\boxed{Z_R(j\omega) = R} \checkmark$$

↓
no
Phase
shift

* inductor

$$v(t) = L \frac{di(t)}{dt}$$

if $i_L(t) = I_m \cos(\omega t + \theta)$

$$I_L(j\omega) = I_m \angle \theta$$

$$V(t) = I_m (\omega L) (-\sin(\omega t + \theta))$$

$$= I_m (\omega L) \cos(\omega t + \theta + 90^\circ)$$


$$V(j\omega) = I_m (\omega L) \angle (\theta + 90^\circ)$$

$$Z_L(j\omega) = \frac{V(j\omega)}{I_L(j\omega)} = \frac{I_m (\omega L) \angle (\theta + 90^\circ)}{I_m \angle \theta}$$

$$Z_L(j\omega) = \omega L \angle (\theta + 90^\circ - \theta)$$

$$Z_L(j\omega) = (\omega L \angle 90^\circ) = (j\omega L) \Omega$$

* capacitor

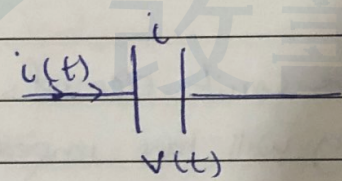

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

if $v_c(t) = V_m \cos(\omega t + \theta) \Rightarrow V_c(j\omega) = V_m \angle \theta$

so

$$i_c(t) = V_m (\omega C) (-\sin(\omega t + \theta))$$

$$= (\omega C) V_m \cos(\omega t + \theta + 90^\circ)$$

$$I_c(j\omega) = \omega C V_m \angle (\theta + 90^\circ)$$


$$Z_c(j\omega) = \frac{V_c(j\omega)}{I_c(j\omega)} = \frac{V_m \angle \theta}{\omega C (V_m) \angle (\theta + 90^\circ)}$$

$$\frac{1}{\omega C} \angle (\theta - \theta - 90^\circ)$$

$$Z_c(j\omega) = \frac{1}{\omega C} \angle -90^\circ = \frac{-j}{\omega C} \Omega$$

21/7/2020

* Using calculator to solve complex num.

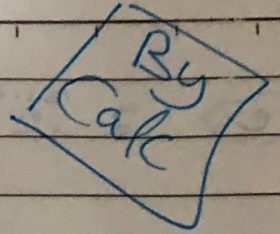

$$x = 3 + 2j$$

$$y = 5 + j$$

$$\Rightarrow x \cdot y = (3 + 2j)(5 + j) \Rightarrow \text{mode} \rightarrow 2 \rightarrow \\ = (13 + 13j) \rightarrow \text{rec}$$

$$= 18.38 \angle 45 \quad \text{mode} \rightarrow 2 \rightarrow \text{shift} \rightarrow 3$$

$$\Rightarrow x \div y = \frac{17}{26} + \frac{7}{26}j$$

$$= .707 \angle 22.4$$

rec ← Polar (وضوح)
 shift → 4

$$\Rightarrow 3 \angle 20 + 4 \angle -15 = 6.682 - 9.21 \times 10^3 j$$

[* Review


$$= 6.68 \angle -0.08^\circ$$

$$Z_R(j\omega) = R \rightarrow \text{fixed with freq variation}$$


$$Z_L(j\omega) = j\omega L = \omega L \angle 90$$


$$Z_C(j\omega) = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90$$

* series

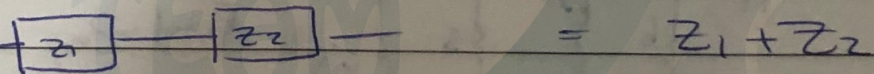

* Parallel

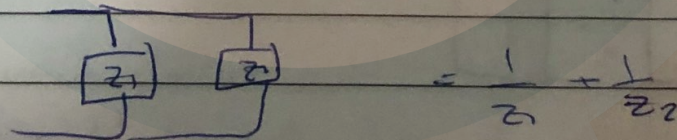

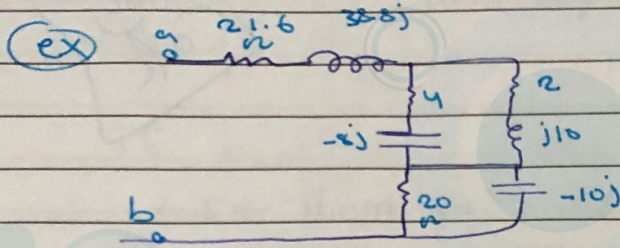

find Z_{eq} btw a & b


$2 \parallel j10 \rightarrow$ series $Z_1 = 2 + j10$

$4 \parallel -j8 \rightarrow$ series $Z_2 = 4 - j8$



$-j10 \parallel 20 \rightarrow$ parallel $Z_3 = \frac{1}{\frac{1}{20} + \frac{1}{-j10}} = 4 - j8$

$21.6 \parallel (38.8j) \rightarrow$ series $Z_4 = 21.6 + 38.8j$

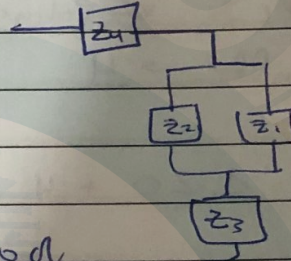$Z_5 = \frac{1}{\frac{1}{Z_2} + \frac{1}{Z_1}} \Rightarrow$ parallel
 $Z_5 = 14.4 - j8j$



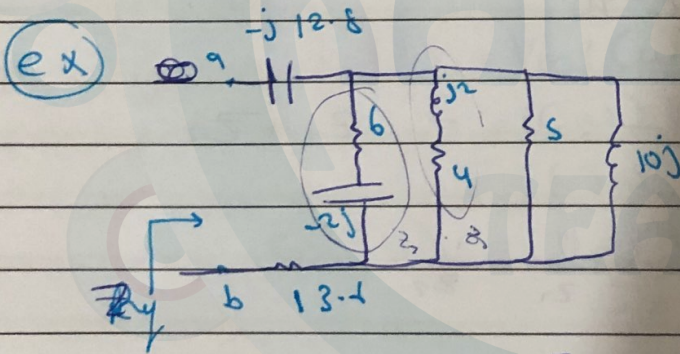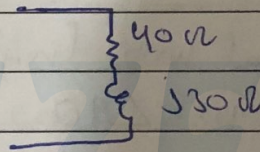$Z_{eq} = Z_4 + Z_5 + Z_3 = 40 + j30 \Omega$




find Z_{eq}

$Z_1 = 4 + 2j$ $Z_2 = 6 - 2j$

$\frac{1}{Z_y} = \frac{1}{4 + 2j} + \frac{1}{6 - 2j} + \frac{1}{5} + \frac{1}{j10} \rightarrow Z_y = \frac{22}{13} + \frac{6}{13}j$

الجواب $\rightarrow 15.3 - 12.34j -$

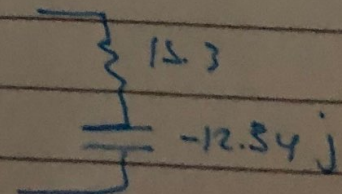


AC - analysis steps

- 1 note the frequency of the sinusoidal excitation
- 2 convert all source to phasor form (freq domain)
- 3 convert each circuit elements to impedance form

$$Z_R = R \quad Z_L = \omega L j \quad Z_C = \frac{-j}{\omega C}$$

- 4 solve the resulting phasor circuit using any method (mesh, nodal, superposition, S.T, SP, Norton, theorem, KCL, KVL, ohm, divider)

- 5 convert to time domain

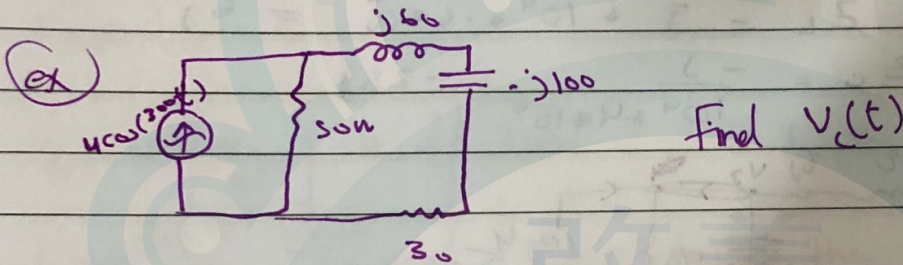

Solu (1) $\omega = 300 \text{ rad/sec}$

(2) $j60 \quad \checkmark$
 $-j100 \quad \checkmark$

(3) $4 \cos(300t) = 4 \angle 0^\circ \text{ A} = \bar{I}$


(3) $Z_1 = 30 + 60j - 100j$

$Z_1 = 30 - 40j \text{ ohm}$

using current division


$$I = 4 \angle 0^\circ \frac{1}{\frac{1}{Z_1} + \frac{1}{50}} = 2 + j$$

$$\frac{1}{Z_1} + \frac{1}{50}$$

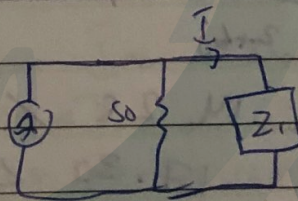

$V_C = I * -j100 = 223.6 \angle -63.4^\circ \text{ volt}$

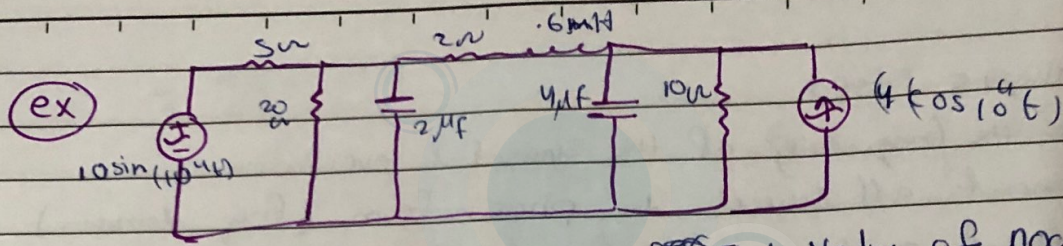$V_C(t) = 223.6 \cos(300t - 63.4^\circ) \text{ volt}$



Find value of nodal voltages

① $\omega = 10^4 = \omega$


② $10 \sin(10^4 t) = 10 \cos(10^4 t - 90^\circ) = 10 \angle -90^\circ$

$4 \cos 10^4 t = 4 \angle 0^\circ$

③ $2 \mu F \rightarrow \frac{-j}{\omega C} \rightarrow \frac{-j}{2 \times 10^4 \times 10^{-6}} = -50j = Z_C$

$0.6 \text{ mH} \Rightarrow Z_L = j \times 10^4 \times 0.6 \times 10^{-3} = 6j$

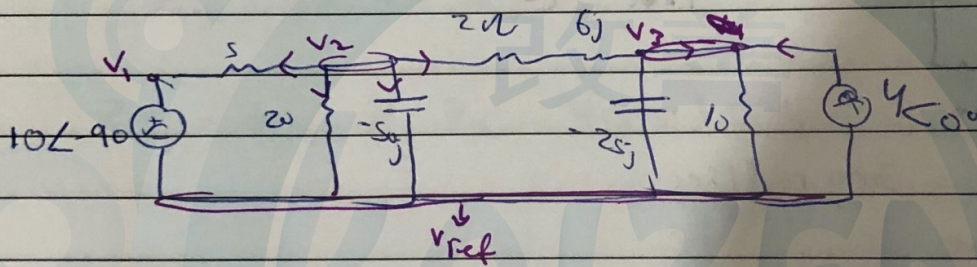$4 \mu F = Z_C = \frac{-j}{10^4 \times 4 \times 10^{-6}} = -25j$



@ V_1 $V_1 = 10 \angle -90^\circ$

@ V_2 $\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{V_2}{-50j} + \frac{V_2 - V_3}{2 + 6j} = 0$

@ V_3 $\frac{V_2 - V_3}{2 + 6j} + 4 \angle 0^\circ - \frac{V_3}{-25j} + \frac{V_3}{10} = 0$


$V_1 = 14.28 \angle -54.8^\circ \text{ volt}$

$V_2 = 17.33 \angle 1.99^\circ \text{ volt}$

$V_1 = 14.28 \cos(10^4 t - 54.8^\circ)$ ①

$V_2 = 17.33 \cos(10^4 t + 1.99^\circ)$ ②

ex

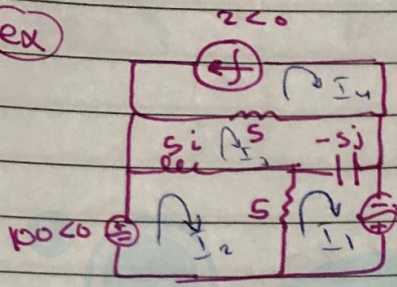

Write mesh eqns


Solve $I_4 = -2 \angle 0 \text{ A}$

@ $I_1 \rightarrow -50 \angle 0 + 5I_1 - 5jI_1 - 5I_2 - 5jI_3 = 0$

@ $I_2 \rightarrow 5I_1 + 5I_2 - 100 \angle 0 - 5I_1 - 5jI_3 = 0$


@ $I_3 \rightarrow 5I_3 + 5jI_3 - 5jI_1 - 5jI_2 + 5I_1 - 5I_4 = 0$

ex

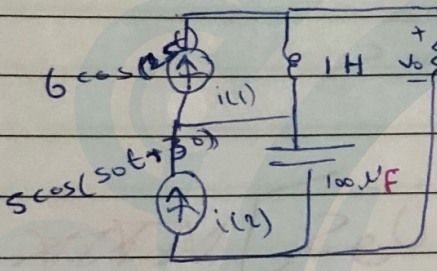

Note if the sources didn't have same radian freq (ω) \rightarrow use only s. position

leave i_1

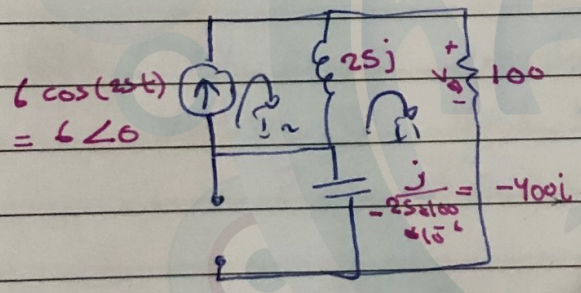

$I_2 = 6 \angle 0$

@ $I_1 \rightarrow 100I_1 - 400jI_1 + 25jI_1 - 25jI_2 = 0$


$\omega = 25$

$V_0' = 100 \angle I_1 = 38.75 \angle 165 \text{ volt}$

leave i_2

$I_1 = 5 \angle 30$

$(50j + 100 - 200j)I_1 + 200jI_2 = 0$

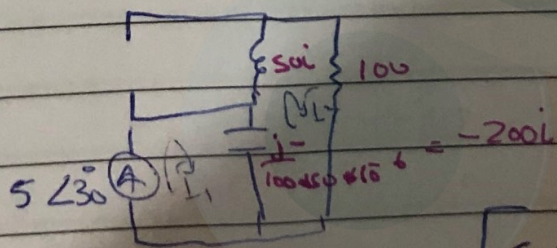

$V_0'' = I_2 * 100 = 554.7 \angle -3.7^\circ$

$\omega = 50$


$\sum V_0 \neq V_0' + V_0'' \rightarrow$ due to diff ω .

$V_0 = 36.55 \cos(25t + 165^\circ) + 554.7 \cos(50t - 3.7^\circ)$

Ex Given:

$$V(t) = 12 \sin(500t + 30)$$

$$i(t) = .2 \cos(500t)$$

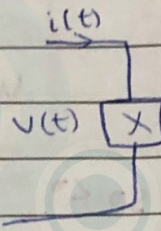

Soln $\rightarrow V(t) = 12 \cos(500t - 60) = 12 \angle -60$

$$I(t) = .2 \angle 0$$

$$X = \frac{V}{I} = \frac{12 \angle -60}{.2 \angle 0} = 60 \angle -60 \Omega$$

$$X = \underbrace{30}_{30 \Omega} - \underbrace{51.9 j}_{51.9 \Omega} \Omega$$


$$X_C = \frac{1}{\omega C} \rightarrow 51.9 = \frac{1}{500 C}$$

$$C = 38.5 \mu F$$


[a + b - 51.9 j] ~~XXXX~~

Y-Δ circuit

$$[Z \rightarrow j / -j]$$

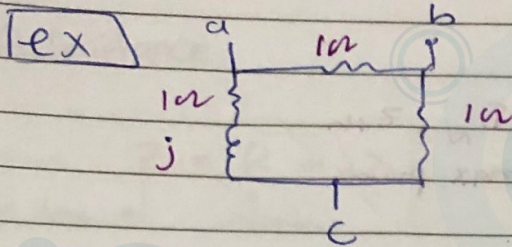


convert from Δ to Y

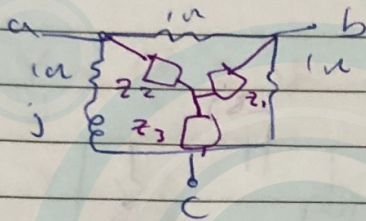

$$Z_1 = \frac{1 \times 1}{1 + 1 + (1+j)} = \frac{1}{3+j} = .3 - .1j \Omega$$

$$Z_2 = \frac{1(1+j)}{3+j} = .39 + j.2 \Omega$$
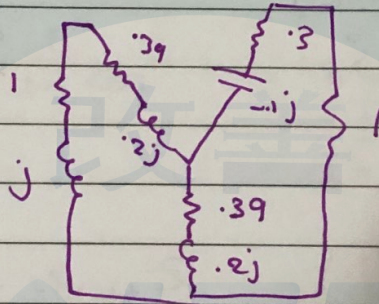
$$Z_3 = \frac{1 * (1+j)}{3+j} = .39 + .2j \Omega$$



~~max~~ max power transfer in AC circuit.

value of load to get max power transfer

$$Z_L = Z_{th}^* \rightarrow \text{conjugate}$$

ex: $Z_1 = 3 + 2j$


$$Z_1^* = 3 - 2j$$

* only change the sign of imaginary part

ex: $12 \angle 60^\circ = Z_1$


$$12 \angle 60^\circ = Z_1^*$$

ex

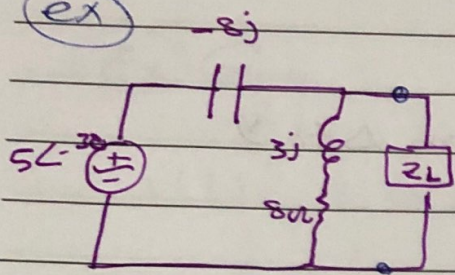

Find V_{th} , I_N , Z_{th}
 Z_L for max power


Solu →

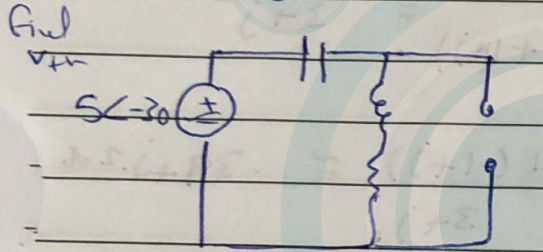

$$V_{th} = \frac{(5\angle-30^\circ)(8+j8)}{8+8j-8j}$$

$$V_{th} = 7.07 \angle 15^\circ$$


Find I_N →

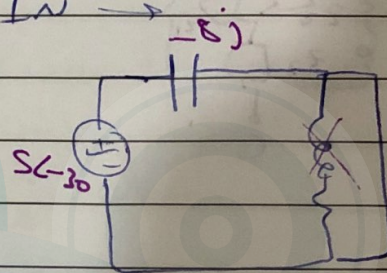

$$I_N = \frac{5\angle-30^\circ}{-8j}$$

$$I_N = 0.625 \angle 60^\circ \text{ A}$$

* find Z_{th}

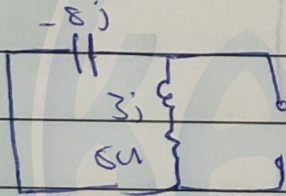

$$Z_{th} = 8 - j8 \ \Omega$$

* the value of $Z_{load} \Rightarrow P_{max}$

$$Z_{load} = Z_{th}^* = 8 + j8 \ \Omega$$

Admittance

$$Z = R + jX \rightarrow \text{reactance (} X_L \text{ or } X_C)$$

imag. part \leftarrow \downarrow resistors


$$Y = G + jB \rightarrow \text{susceptance}$$

admittance \downarrow \downarrow conductance

$$Y = \frac{1}{Z} \quad G = \frac{1}{R} \quad \frac{1}{X} = B$$

ex $Z = 100 \angle 53^\circ$ Find Y
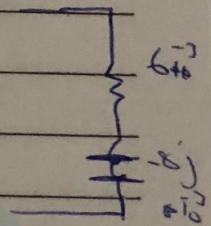
$$Y = \frac{1}{Z} = \frac{1}{100 \angle 53^\circ} = \frac{6 \times 10^{-3}}{\downarrow G} - \frac{j8 \times 10^{-3}}{\downarrow BL}$$



$$Z = 60.2 + j80$$

$$\frac{1}{60.2} = 16.6 \neq 6 \times 10^{-3}$$

$$\frac{1}{80j} = 12.5 \neq 8 \times 10^{-3}$$


Notes

1 $Z_L(j\omega) = j\omega L = \omega L \angle 90$

$X_L = \omega L \rightarrow$ reactance

$\omega = 2\pi F$

$X_L = 2\pi F \cdot L$

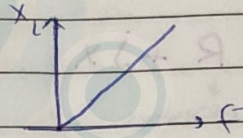


@ $F=0 \rightarrow DC=0$

$X_L = 0 \Omega \rightarrow$ inductor acts as short circuit

@ $F=\infty \rightarrow X_L = \infty \Omega \rightarrow$ open circuit

2 $Z_C(j\omega) = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90$

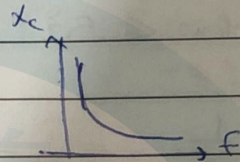
$X_C = \frac{1}{\omega C} \rightarrow$ reactance



@ $F=0$ (DC) $\rightarrow X_C = \infty$ open circuit

@ $F=\infty$ (DC) $\rightarrow X_C = 0$ short circuit

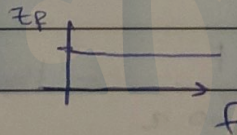3 $Z_R(j\omega) = R \rightarrow$ independent of freq



4 $Z = R + jX$

@ F $Z = R$

assume

$V = V_m \angle 0$

Same angle

So $I = \frac{V_m \angle 0}{R} = \frac{V_m}{R} \angle 0$

So no phase shift btw
voltage & current across the
resistor

Phase shift btw V & $I = 0$


* if $Z = -jX_C \rightarrow$ pure capacitive

assume $V = V_m \angle 0$

$$I = \frac{V_m \angle 0}{X_C \angle -90} = \frac{V_m}{X_C} \angle 0 + 90$$

أول تارة ز تنويفها والعزى $i(t)$

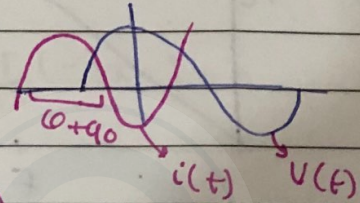\therefore Current I leads voltage V lag by 90° + voltage V lag the current by 90°




* if $Z = jX_L \rightarrow$ pure inductive

assume $V = V_m \angle 0$

$$I = \frac{V_m \angle 0}{X_L \angle 90} = \frac{V_m}{X_L} \angle 0 - 90$$

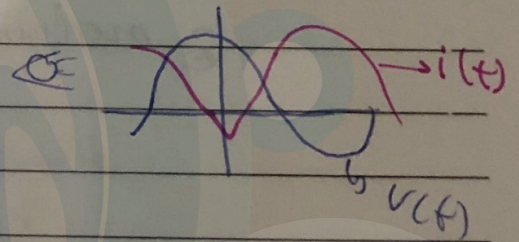\therefore voltage V leads current I lag by 90° + current I lag the voltage.




* if $Z = R + jX_L \rightarrow$ behaves like inductive $0 < \phi < 90$


* if $Z = R - jX_C \rightarrow$ behaves like conductive $0 > \phi > -90$

Series RLC-circuits

26/7/2020

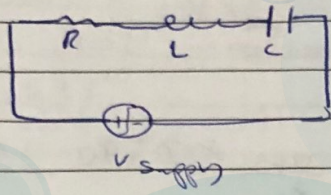


$$Z_{eq} = R + j(X_L - X_C)$$

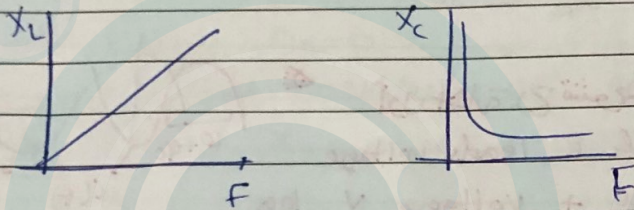

@ low freq $X_C > X_L \Rightarrow$ assume circuit acts like capacitor (L & C) (I leads)

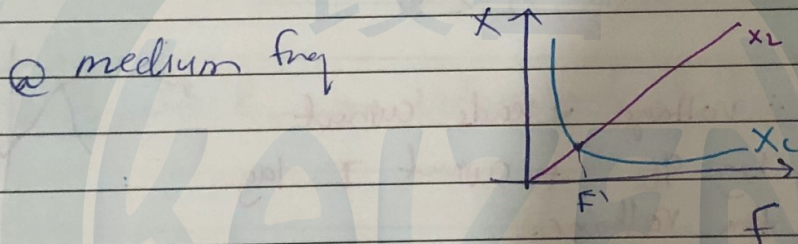@ high freq $X_C < X_L \Rightarrow$ assume circuit acts like inductor



@ F' $X_L = X_C \rightarrow$ resonance frequency

@ resonant freq

$$\frac{1}{\omega C} = \omega L \rightarrow \omega^2 = \frac{1}{LC} \rightarrow \omega = \frac{1}{\sqrt{LC}}$$


resonant omega
(resonant radian freq)

$$\omega_r = \frac{1}{\sqrt{LC}} = 2\pi F_r$$

$$F_r = \frac{1}{\sqrt{LC} * 2\pi} \Rightarrow Z_{eq} = R \text{ (Pure resistor)}$$

$X_L = X_C \rightarrow$ capacitor & inductor cancel each other
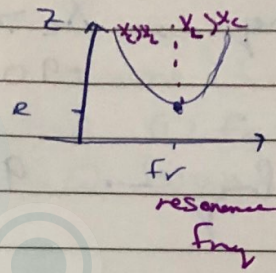
$$Z_{eq} = R \quad \text{bec } X_L = X_C$$



@ f_r by KVL

$$-V_{supply} + IR + IjX_L + I(-jX_C) = 0$$


@ $f_r \quad X_L = X_C$

$$-V_{supply} + IR + 0 = 0$$

$$I_{max} = V_{supply} / R \quad \text{Resonant current}$$

$$\vec{V}_C = -\vec{V}_L \rightarrow \text{out of phase}$$

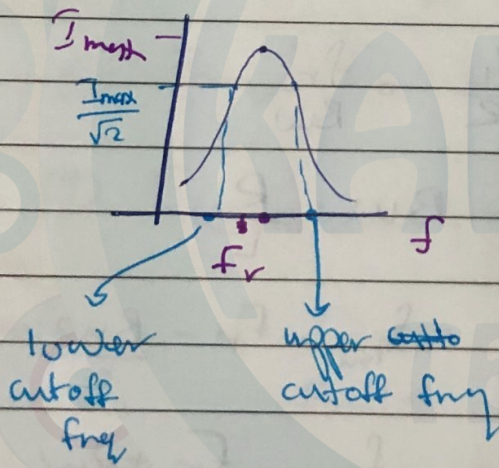(R) is the only part of the circuit which dissipates power




Power dissipation is given by

$$I = I_{max} / \sqrt{2}$$

$$P = I^2 R$$

$$P/2 = \frac{1}{2} I^2 R$$

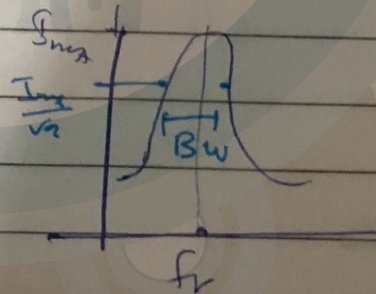


$$\text{Band width} = f_H - f_L \quad \text{Hz}$$

$$\frac{(1+i)^n - 1}{(1+i)^n i}$$

@ low freq $\rightarrow X_C > X_L \rightarrow -90 < \phi < 0$ @ pure C

@ high freq $\rightarrow X_L > X_C \rightarrow 90 > \phi > 0$ @ pure L

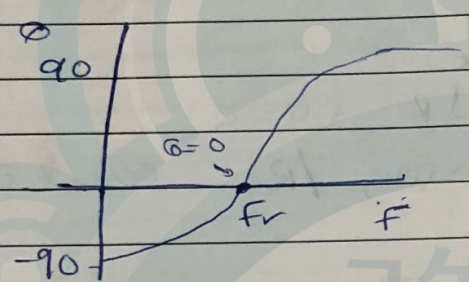@ $f_r \rightarrow X_L = X_C$
 $Z_{eq} = R$ $\phi = 0$



* variation of ϕ @ Z_{eq} with freq

* Quality factor: relation btw max energy stored to the energy dissipated

$$Q = \frac{dX/d}{dR} = \frac{X_C}{R} = \frac{X_L}{R} = \frac{f_r}{BW}$$

* special case: if $Q > 10$ $BW = \frac{R}{L}$


$$f_{low} = f_r - \frac{BW}{2}$$

$$f_{high} = f_r + \frac{BW}{2}$$

$$I_{max} = \frac{V_{supply}}{R}$$

$$P_{max} = I_{max}^2 * R$$

ex 8

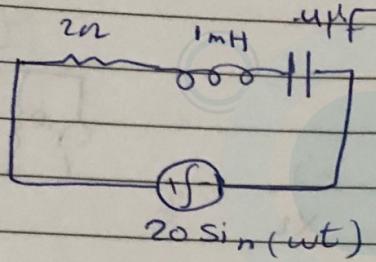

assume $Q > 10$

Find (1) f_r (2) ω_r (3) BW

(4) Q (5) ω_L

Solu


$$20 \sin(\omega t) \rightarrow 20 \cos(\omega t - 90)$$

$$(1) f_r = \frac{1}{\sqrt{2\pi LC}} = 7.9 \text{ kHz}$$

$$(2) \omega_r = 2\pi f_r = 50 \text{ k rad/sec}$$

$$(3) BW = \frac{R}{L} \quad (Q > 10 \text{ is valid}) \rightarrow 2000 \text{ rad/sec}$$

$$(4) Q = \frac{\omega_r}{BW} = 25$$

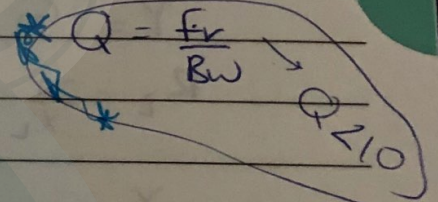

$$(5) \omega_L = \omega_r + \frac{BW}{2} = 2\pi f_L$$

$$(6) \omega_{High} = \omega_r - \frac{BW}{2} = 2\pi f_H$$

$$(7) I_{max} = \frac{V_{supply}}{R} = \frac{20 \angle -90}{2} = 10 \angle -90 \text{ A}$$

$$(8) Z_{max} = R = 2 \Omega$$

$$(9) I (@\omega_L \& \omega_H) = \frac{I_{max}}{\sqrt{2}}$$

Note: if $Q < 10$

$$BW = f_H - f_L = \text{Hz}$$


$$Q = \frac{f_r}{BW}$$

* Parallel RLC circuits

$$Y_R = \frac{1}{Z_R} = \frac{1}{R}$$

$$Y_L = \frac{1}{Z_L} = \frac{1}{j\omega L} = -\frac{j}{X_L}$$
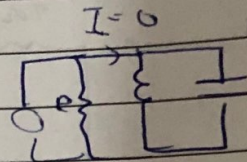
$$Y_C = \frac{1}{Z_C} = \frac{1}{-j/\omega C} = j\omega C = \frac{j}{X_C}$$



Y total =




$$\frac{1}{R} + \frac{-j}{X_L} + \frac{j}{X_C}$$

$$Y = G + jB$$

$$B_L = \frac{-j}{X_L}$$

$$B_C = j\omega C$$
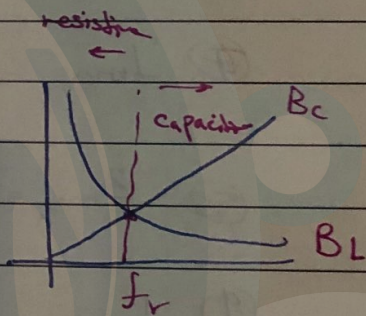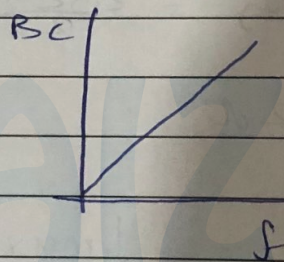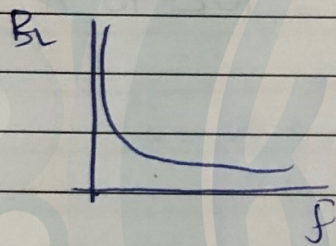
$$Y_{total} = \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$$



@ resonance freq

$$B_L = B_C$$


$$\frac{1}{\omega L} = \omega C$$

$$\omega_r = \frac{1}{\sqrt{LC}}$$


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

* @ resonance $|I_L| = |I_C|$ Because $B_L = B_C$ (same V on them)
 But out of phase • circulating currents btw L & C

$$Y = \frac{1}{R} = G$$

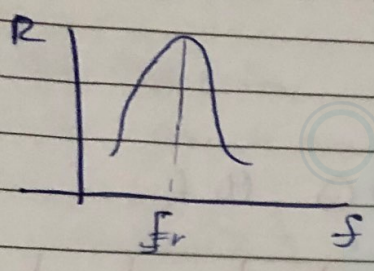

$I_{min} = \frac{V_{sup}}{R}$

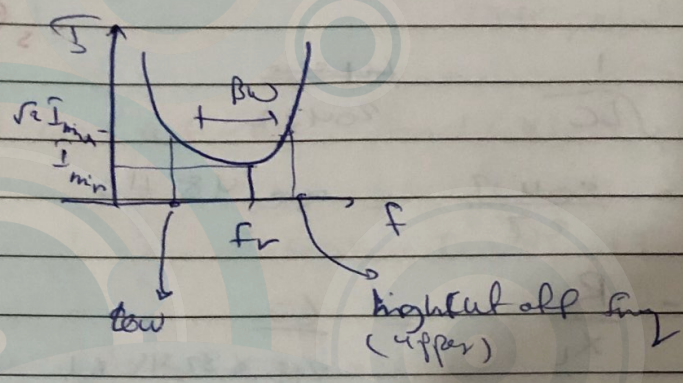

$BW = f_H - f_L \text{ (Hz)}$

$Q = \frac{\text{max energy stored}}{\text{max energy lost}}$

$Q = \frac{P}{\omega L} = \omega RC = R \sqrt{\frac{C}{L}} = \frac{R}{X_L} = \frac{R}{X_C}$

$Q = \frac{\omega r}{BW} = \frac{f_r}{BW} \text{ (Power factor)}$

$f_L = f_r - \frac{BW}{2}$


$f_H = f_r + \frac{BW}{2}$

\sqrt{I} انجازه بين resonance lines = 0

$(1+i)^n i$

ex:

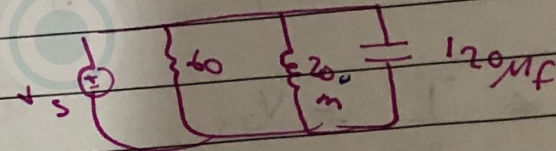$v_s = 100 \cos(\omega t)$
 find (1) f_r (2) BW (3) (1) (4) f_L
 (5) f_H (6) I_{min}



$$\omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{204.12}$$

$$(1) f_r = \frac{204.12}{2\pi} = 32.48 \text{ Hz}$$

$$(2) Q = \frac{R}{X_L} = \frac{60}{2\pi \times 32.48 \times 1} = \frac{60}{40.8} = 1.47$$

$$(3) BW = \frac{f_r}{Q} = \frac{32.5}{1.47} = 22 \text{ Hz}$$

$$(4) f_H = f_r + \frac{1}{2} BW = 43.5 \text{ Hz}$$

$$f_L = f_r - \frac{1}{2} BW = 21.5 \text{ Hz}$$

$$(5) I_{min} = \frac{V}{R} = \frac{100 \cos(204.12)t}{60} = \frac{100}{60} = 1.67 \text{ A}$$

$$Y \text{ at } f_r = \frac{1}{R} = \frac{1}{60} \text{ S}$$

$$Z \text{ at } f_r = R = 60 \Omega$$

* the avg value: measuring the mean of the voltage or current over a period time.


$$\langle x(t) \rangle = \frac{1}{T} \int_0^T x(\tau) d\tau \rightarrow \text{integral of the signal over period of time}$$

ex $x(t) = A \cos(\omega t - \phi)$ find $\langle x(t) \rangle$

$$\langle x(t) \rangle = \frac{1}{T} \int_0^T A \cos(\omega \tau + \phi) d\tau$$

$$\sin \tau = 0 \quad \left[\frac{\omega}{T} + A \right] \sin(\omega \tau + \phi) \Big|_0^T =$$

$$\boxed{= 0 \text{ zero}}$$

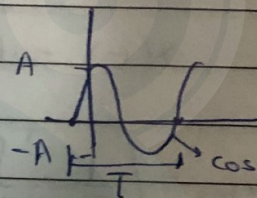


* Note: the avg of sinusoidal signal is zero independent of amplitude or frequency

(ex) find $\langle x(t) \rangle$

$$\langle x(t) \rangle = \frac{1}{T} \int_0^T x(\tau) d\tau$$

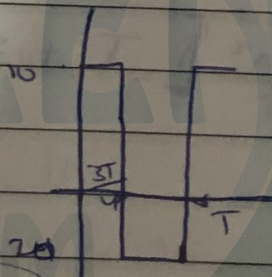
$$= \frac{1}{T} \left[\int_0^{3T/4} 10 d\tau + \int_{3T/4}^T -20 d\tau \right]$$



$$\frac{1}{T} \left[\frac{30}{4} T - \frac{20}{4} T \right] = \frac{10}{4} = \langle x(t) \rangle$$

$$\frac{1}{(1+i)^N i}$$

* Root mean square (RMS)

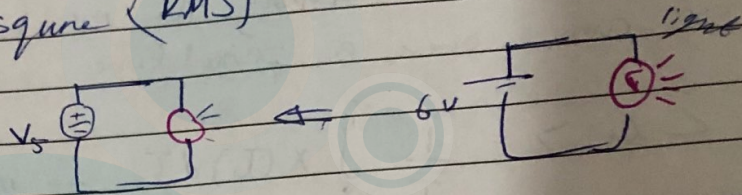

RMS = effective value of varying voltage or current

$$x_{rms} = \sqrt{\frac{1}{T} \int_0^T (x^2)(t) dt} = x_{effective}$$

ex $x(t) = A \cos(\omega t)$

$$x_{rms} = \sqrt{\frac{1}{T} \int_0^T A^2 \cos^2(\omega t) dt}$$

$$\cos^2 x = \frac{1}{2} (1 + \cos 2x)$$

$$\sqrt{\frac{1}{T} \int_0^T A^2 \left(\frac{1}{2} (1 + \cos 2\omega t) \right) dt}$$


$$\sqrt{\frac{2A^2}{2T} \int_0^T T + \sin 2\omega t dt} = \sqrt{\frac{(T+0) 2A^2}{2T}}$$

$$= \frac{A}{\sqrt{2}}$$

* for sinusoidal signal

$$* x_{rms} = \frac{\text{Peak value}}{\sqrt{2}}$$

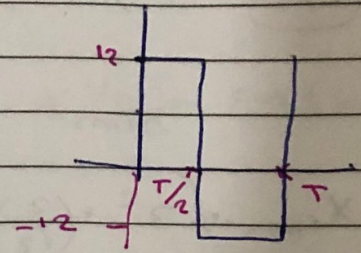ex $x(t) = \begin{cases} 12 & 0 \leq t \leq \frac{T}{2} \\ -12 & \frac{T}{2} \leq t \leq T \end{cases}$



$$x_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \left[\int_0^{T/2} 12^2 dt + \int_{T/2}^T (-12)^2 dt \right]}$$

$$\sqrt{\frac{1}{T} \left[\frac{144}{2} T + \frac{144}{2} T \right]} = \sqrt{144} = 12$$

Note: For square wave signal

① $x_{rms} = A \rightarrow$ max value

② for triangular signal

$$x_{rms} = \frac{A}{\sqrt{3}}$$

③ for DC - signal

$$x_{rms} = \text{DC value}$$

ex: $V_{rms} = 220$ volt

$V_{peak} = ?$

$$V_{peak} = V_{rms} * \sqrt{2}$$

$$= 220 * \sqrt{2} = 311 \text{ volt}$$

* Note: $V(t) = V_1 \cos(\omega t) + V_2 \sin(\omega t) + \dots + V_0$

$V_{rms} = ?$

$$V_{rms} = \sqrt{(V_{DC})^2 + \sum_{i=1}^n \frac{V_i^2}{2}}$$

$$RMS \text{ total} = \sqrt{(RMS_1)^2 + (RMS_2)^2 + \dots + (RMS_n)^2}$$

ex: $x(t) = 3 + 2 \cos(\omega t)$

$x_{rms} =$

$$x_{rms} = \sqrt{3^2 + \left(\frac{2}{\sqrt{2}}\right)^2}$$

$$= \sqrt{9 + 2} = \sqrt{11}$$

$$RMS_1 = 3$$

$$RMS_2 = \frac{Peak}{\sqrt{2}} = \frac{2}{\sqrt{2}}$$

ex:

$$v(t) = 4 \cos(100t) + 12 \sin(100t) - 6 \cos(300t) + 5$$


$$V_{rms} = \sqrt{\left(\frac{4}{\sqrt{2}}\right)^2 + \left(\frac{12}{\sqrt{2}}\right)^2 + \left(\frac{-6}{\sqrt{2}}\right)^2 + 5^2} = \sqrt{123} = 11.1$$

27/7/2020

* Power in AC-circuit

- (1) instantaneous power
- (2) complex power
- (3) avg power

(1) instantaneous power:

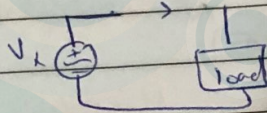


if $v(t) = V_m \cos(\omega t + \theta_v)$
 Peak \downarrow Phase \downarrow

$i(t) = I_m \cos(\omega t + \theta_i)$

$P(t) = v(t) i(t)$

$= V_m \cos(\omega t + \theta_v) * I_m \cos(\omega t + \theta_i)$

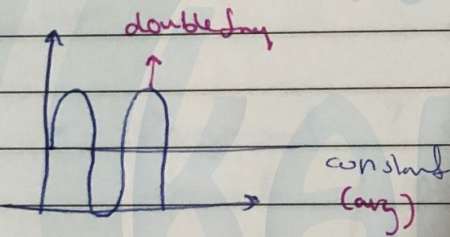$= \frac{V_m I_m}{2} \cos(2\omega t + \theta_i + \theta_v) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$
 oscillating signal with double freq \downarrow constant value (avg power) (DC component)



(2) Avg power

$P_{avg} = \frac{1}{T} \int_0^T P(t) dt$

$P_{avg} = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) dt$

$= \frac{V_m I_m}{2} \left[\int_0^T \cos(2\omega t + \theta_v + \theta_i) dt + \int_0^T \cos(\theta_v - \theta_i) dt \right]$

$$= \frac{V_m I_m}{2T} \times T \cos(\theta_v - \theta_i)$$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

ex:

$$I = I_m \angle \theta_i$$

$$V = V_m \angle \theta_v$$

$$Z = \frac{V}{I} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i} = \frac{V_m}{I_m} \angle (\theta_v - \theta_i)$$

$$|Z| = \frac{V_m}{I_m}, \theta_z = \theta_v - \theta_i$$

$$P_{avg} = \frac{1}{2} I_m^2 |Z| \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \frac{V_m^2}{|Z|} \cos(\theta_v - \theta_i)$$

دالة القدرة
|Z|

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$= I_{rms}^2 |Z| \cos(\theta_v - \theta_i)$$

$$= \frac{V_{rms}^2}{|Z|} \cos(\theta_v - \theta_i)$$

arms v

دالة القدرة

ex: $V(t) = 14.14 \sin(377t)$


find (1) P_{avg} for load RL
(2) $P(t)$

Soln:

$$V(t) = 14.14 \cos(377t - 90)$$

$$V(t) = 14.14 \angle -90$$

$$\omega = 377 \text{ rad/sec}$$

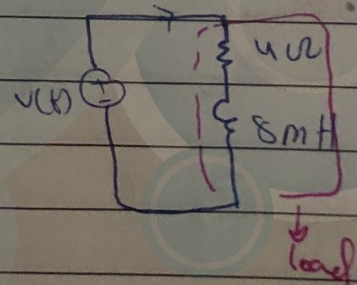

$$X_L = 377 \times 8 \times 10^{-3} = 3 \Omega$$

$$Z_{\text{load}} = R + jX_L = 4 + j3 = 5 \angle 36.9^\circ \Omega$$

$$|Z_{\text{load}}| = 5 \quad \theta_{\text{load}} = 36.9^\circ = \theta_v - \theta_i$$

$$I = \frac{V}{Z} = \frac{14.14 \angle -90^\circ}{5 \angle 36.9^\circ} = 2.83 \angle -126.9^\circ \text{ A}$$

$$I_{\text{max}} = 2.83$$

$$\theta_i = -126.9^\circ$$

$$* P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= 0.5 \times 14.14 \times 2.83 \cos 36.9^\circ$$

$$P_{\text{avg}} = 16 \text{ W}$$

$$\text{or } P_{\text{avg}} = \frac{1}{2} I_m^2 |Z| \cos(\theta_v - \theta_i) \Rightarrow$$

$$\text{or } P_{\text{avg}} = \frac{1}{2} \frac{V_m^2}{|Z|} \cos(\theta_v - \theta_i) \Rightarrow$$

$$(2) P(t)_{\text{inst}} = v(t) \times i(t)$$

$$= 14.14 \cos(377t - 90^\circ) \times 2.83 \cos(377t - 126.9^\circ)$$


$$= 40 \cos(377t - 90^\circ) \cos(377t - 126.9^\circ) \text{ W}$$

ex 2

$$V = 110 \angle 0^\circ \text{ volt}$$

$$\omega = 377 \text{ rad/sec}$$

find P_{avg} for the load

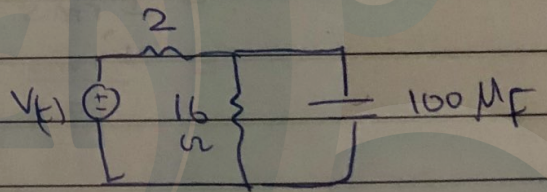

Solu:


$$Z_C = \frac{-j}{\omega C} = \frac{-j}{377 \times 100 \times 10^{-6}} = -26.5j \Omega$$

$$Z_{\text{load}} = \frac{16 \times (-26.5j)}{16 - 26.5j} = 13.7 \angle -31.2^\circ \Omega$$

$$|Z|_{\text{load}} = 13.7$$

$$\theta_{\text{load}} = -31.2^\circ$$

$$P_{avg} = \frac{1}{2} \frac{V_m}{|Z|_{load}} \cos(\theta_v - \theta_i)$$

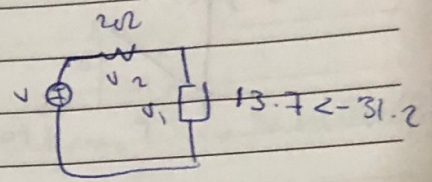

$$V_1 = \frac{110 \angle 0^\circ (13.7 \angle -31.2^\circ)}{2 + 13.7 \angle -31.2^\circ}$$

$$V_1 = 97.5 \angle -38.5^\circ \text{ V}$$

$$V_m = 97.5$$

$$\theta = -38.5$$

$$P_{avg} = \frac{1}{2} \frac{(97.5)^2}{13.7} \cos(-31.2^\circ) = 296.8 \text{ W}$$

$$\text{or } P_{avg} = \frac{1}{2} \frac{I_m^2 |Z| \cos(\theta_v - \theta_i)}{\text{constant @ load}}$$

$$I = \frac{V_1}{Z_{load}} = \frac{97.5 \angle -38.5^\circ}{13.7 \angle -31.2^\circ} = 7.116 \angle -27.3^\circ \text{ A}$$

$$P_{avg} = \frac{1}{2} (7.116)^2 (13.7) \cos(-31.2^\circ) = \cancel{966} 296.8 \text{ W}$$

* Complex Power: product of rms voltage & the complex conjugate of the rms current

if voltage = $V_{rms} \angle \theta_v$

current $I_{rms} \angle \theta_i$

$$P_s = V_{rms} \angle \theta_v * (I_{rms})^*$$

$$= (V_{rms} \angle \theta_v) (I_{rms} \angle -\theta_i)$$

$$= V_{rms} I_{rms} \angle \theta_v - \theta_i \quad \text{Polar form}$$


$$S = \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_{\text{Real Power}} + j \underbrace{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_{\text{Reactive Power (VAR)}}$$

apparent Power (VA)

real power

avg Power

(W) dissipated power

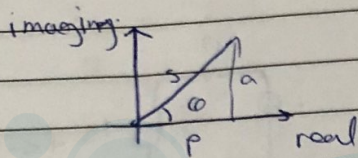

$$\theta = \omega_v - \omega_i$$

$$S = V_{rms} I_{rms}^*$$


$$= P + jQ$$

$$P = V_{rms} I_{rms} \cos(\omega_v - \omega_i) \omega$$

$$Q = V_{rms} I_{rms} \sin(\omega_v - \omega_i) \text{ VAR}$$

$$* Z = R + jX$$

$$Z = \frac{V_{rms}}{I_{rms}}$$

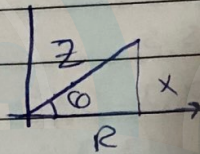

$$V_{rms} = I_{rms} * Z$$

$$S = (I_{rms} * Z) I_{rms}^*$$

$$S = |I_{rms}|^2 Z$$

$$S = |I_{rms}|^2 (R + jX)$$

$$= \underbrace{|I_{rms}|^2 R}_P + j \underbrace{|I_{rms}|^2 X}_Q$$

measure the energy exchanged between the source & the reactive impedance

* Summary :

$$PS' = V_{rms} I_{rms}^*$$

$$= V_{rms} I_{rms} \cos(\omega_v - \omega_i) + j V_{rms} I_{rms} \sin(\omega_v - \omega_i)$$

$$= |I_{rms}|^2 R + j |I_{rms}|^2 X$$

$$|I_{rms}| = I_{rms} \angle \theta$$

PF

* Power factor

PF = cos(θv - θi)

0 < PF < 1

S = Vrms Irms cos(θv - θi) + j (Vrms) Irms sin(θv - θi)

P = Vrms Irms cos(θv - θi) PF

PF = P / (Vrms Irms) = P / |S|

|S| = sqrt(P^2 + Q^2)

Cases for PF

(1) when PF = 1 -> pure resistive load

θv = θi cos(θv - θi) = cos 0 = 1

sin(θv - θi) = 0

Q = 0

(2) when PF = 0 -> pure inductive load

Q > 0 PF = lag

PF = 0 cos(θv - θi) = cos 90 = 0

L, special case for pure inductive

-> pure capacitive load

Q < 0

PF = cos(θv - θi) = cos(90) = 0

③ inductive load PF \rightarrow lag
capacitive load PF \rightarrow leading

(ex) PF = .8 lag \rightarrow inductive load
 $|S| = 1000$ VA $Q > 0$

$$S = |S| \angle + \cos^{-1}(\text{PF})$$

$$\text{PF} = \cos(\omega v - \omega i)$$

$$\cos^{-1}(\text{PF}) = (\omega v - \omega i)$$

lagging $\Rightarrow \omega_s$ is +ve

$$S = |S| \angle (\omega v - \omega i)$$

(ex) PF = .8 lead

$$|S| = 1000 \text{ VA}$$

\rightarrow capacitive
 $Q < 0$

$$\text{PF} = \cos(\omega v - \omega i)$$

$$\Rightarrow \omega v - \omega i = \cos^{-1}(\text{PF})$$


$$S = |S| \angle - \cos^{-1}(\text{PF})$$

leading $\Rightarrow \omega_s = -ve$

ex

$$V = 110 \angle 0$$

$$\omega = 377 \text{ rad/sec}$$

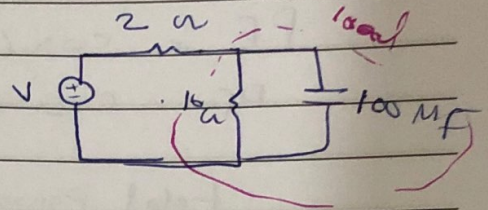

find S P Q PF

Solu:

$$Z_c = \frac{-j}{\omega C} = -j 26.5 \Omega$$

$$Z_1 = 16 \parallel -j 26.5 \Omega = \frac{16 \cdot -j 26.5}{16 - j 26.5} = 13.7 \angle -31.2$$

$$I = \frac{V}{2 + Z_1} = \frac{110 \angle 0}{2 + 13.7 \angle -31.2}$$

$$I = \underline{7.116 \angle -27.35 \text{ A}}$$

$$S = V_{rms} I_{rms}^*$$


$$= \left(\frac{110}{\sqrt{2}} \angle 0 \right) \left(\frac{7.116}{\sqrt{2}} \angle -27.35 \right) = 391.4 \angle -27.35 \text{ VA}$$

$$= 347.6 - j 179.8 \rightarrow \text{complex Power}$$

total power reactive power

$$P = 347.6 \text{ W} \quad Q = -179.8 \text{ VAR}$$
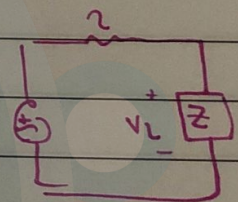
$$V_L = \frac{V_{supply} \cdot Z}{2 + Z} = 97.5 \angle -3.8 \text{ V}$$



$$Q = \frac{|V_L|^2}{X_c} = \frac{\left(\frac{97.5}{\sqrt{2}} \right)^2}{26.5} = 179.4 \text{ VAR}$$

$$P_{total} = P(2\Omega) + P_{load}$$

$$P(2\Omega) = I_{rms}^2 \cdot 2$$

$$= \left(\frac{7.116}{\sqrt{2}} \right)^2 \cdot 2 = 50.64$$

$$P_{load} = \frac{(V_{rms})^2}{16} = \frac{\left(\frac{97.5}{\sqrt{2}} \right)^2}{16} = 297.1 \text{ W}$$

$$P_{total} = 297.1 + 50.64 = 347.7 \text{ W}$$

$$PF = \cos(\theta_v - \theta_i)$$

$$PF = \cos(0 - 27.35) = .89 \text{ leading}$$

↓
capacitive

Total Power Factor

Disipl insv - $\cos \theta$ \rightarrow $\cos \theta$
 \rightarrow capacitive load

改善

KAIZEN

TEAM

Chp 11 [Power

Power inst: $I(t) * v(t)$
 $= \frac{V_m I_m}{2} \cos(2\omega t + \phi_v + \phi_i) + \frac{V_m I_m}{2} \cos(\phi_v - \phi_i)$

Power avg: $\frac{V_m I_m}{2} \cos(\phi_v - \phi_i)$

Power complex: $\frac{V_{rms} I_{rms}}{\angle(\phi_v - \phi_i)} = V_{rms} I_{rms}^*$
 $V_{rms} I_{rms} \cos(\phi_v - \phi_i) + j V_{rms} I_{rms} \sin(\phi_v - \phi_i)$
 $= \frac{V_m I_m}{2} \cos(\phi_v - \phi_i) + j V_{rms} I_{rms} \sin(\phi_v - \phi_i)$
avg power (dissipated power) Reactive power

$$= |I_{rms}|^2 (R + jX)$$


• $\phi_v - \phi_i$

28/7/2020

complex power ex:

(ex) ass rms values:

Find S P Q PF

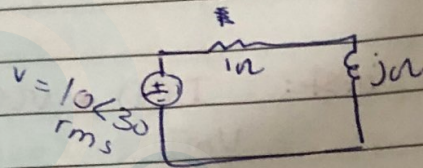

Solu:

$$Z = 1 + j1 \Omega = 1.41 \angle 45$$

$$I_{rms} = \frac{V}{Z} = \frac{10 \angle 30}{1.41 \angle 45} = 7.07 \angle -15 \text{ A}$$

$$S = I_{rms}^* \times V_{rms}^* = (10 \angle 30) (7.07 \angle 15)$$

$$= S_0 + 50j$$

$$P = S_0 \text{ W}$$

$$Q = +50 \text{ VAR}$$

$$P = |I_{rms}|^2 R = 7.07^2 \times 1 = 50 \text{ W}$$

$$Q = |I_{rms}|^2 |X| = (7.07)^2 \times 1 = 50 \text{ var}$$


$$PF = \cos(\theta_v - \theta_i)$$

$$= \cos 30 - 15 = \cos 45 = .707 \quad \boxed{\text{lag}}$$

load is inductive

(ex) $v(t) = 14.14 \sin(377t)$

find S, P, Q, PF

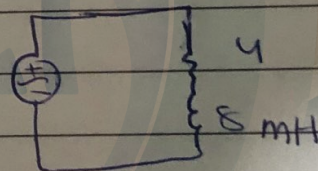

Solu $\rightarrow v(t) = 14.14 \cos(377t - 90)$

$$\omega = 377 \text{ rad/sec} \quad 8 \times 10^{-3} \times 377j = 3j$$

$$Z = 8 \times 10^{-3} + 377j + 4 = 4 + 3j$$

$$S = I_{rms}^* \times V_{rms}$$

$$\frac{V}{Z} = \frac{14.14 \angle -90}{4 + 3j} = \frac{14.14 \angle -90}{4 + 3j}$$

من (المطلوب)

$$\rightarrow I = 2.828 \angle -127^\circ \text{ A}$$

$$\frac{I}{\sqrt{2}} = I_{\text{rms}} =$$

$$S = \frac{2.828 \angle -127^\circ}{\sqrt{2}} \times \frac{14.14 \angle -90^\circ}{\sqrt{2}} = 20 \angle 37^\circ \text{ VA}$$

$$S = 16 + j12$$

$$P = 16 \text{ W}$$

$$Q = 12 \text{ VAR}$$

inductive load (lag)

$$P = I_{\text{rms}}^2 * R = \left(\frac{2.828}{\sqrt{2}}\right)^2 * 4 = 16 \text{ W}$$

$$Q = |I_{\text{rms}}|^2 |X| = \left(\frac{2.828}{\sqrt{2}}\right)^2 * 3 = 12 \text{ VAR}$$

$$\text{PF} = \cos(\theta_v - \theta_i) = \cos(-90^\circ - (-127^\circ)) = \cos 37^\circ$$

$$\text{PF} = .8 \text{ lag}$$

ex

assume RMS values

1) dissipated power


2) total reactive value

3) complex power

4) PF

$$\text{Soln} \rightarrow C \rightarrow \frac{-j}{470 * 10^{-6} * 377} = -5.6 \mu$$

$$L \rightarrow j * .05 * 377 = 18.85$$

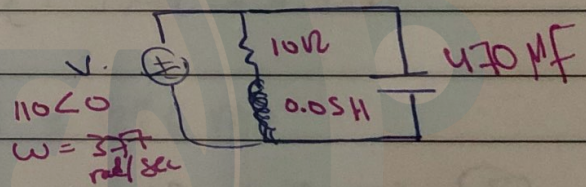

(1) dissipated power $\rightarrow R$ $\frac{P}{W}$

$$P = |I_{rms}|^2 R = \frac{|V_{rms}|^2}{2}$$

$$V_1 = \frac{(110 \angle 0)(10)}{10 + j18.85} = 51.55 \angle -62.05^\circ$$

$$P_R = \frac{|V_1|^2}{R} = \frac{(51.55)^2}{10} = 265.7 \text{ W}$$

$$(2) Q_L = \frac{|V_L|^2}{X_L} = |I_L|^2 X_L$$

$$V_L = \frac{(110 \angle 0)(18.85 \angle 90^\circ)}{10 + j18.85j} = 97.2 \angle 27.95^\circ (V)$$

$$Q_L = \frac{(97.2)^2}{18.85} = 501.2 \text{ VAR}$$

$$Q_C = \frac{(110)^2}{5.6} = 2160.7 \text{ VAR}$$

$$Q_{total} = jQ_L + jQ_C = 501.2j - 2160.7j = -j1659 \text{ volt AR}$$

$$(3) \text{ complex power} = P_{total} + Q_{total}$$

$$S = 265.7 - j1659 \text{ VA}$$

(Complex Power)

$$S = V_{rms} I_{rms}^*$$

$$I_{rms} = 110 \angle 0$$

$$Z_{total} = (10 + j18.85 - 5.6j)$$


S → بتکون کجی

والت

$$S = 110 \angle 0 + 15.3 \angle -80$$

$$= 265.4 - j 1659 \text{ VA}$$

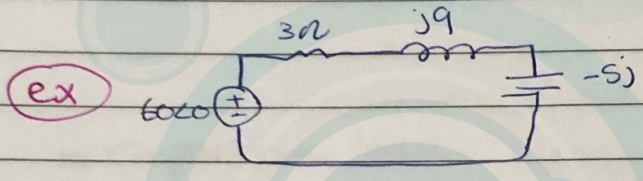(4) $Pf = \cos(\phi_v - \phi_i) = \cos(0 - 80) = .173$ leading
capacitive



assume RMS values
find S for the load

Solu:

$Z_{total} = 3 + j4 = 5 \angle 53.13^\circ \Omega$

Q1) $I_{rms} = \frac{60 \angle 0}{5 \angle 53.13} = 12 \angle -53.13 \text{ A}$

$S = V_{rms} I_{rms}^* = 60 \angle 0 (12 \angle 53.13) = 720 \angle 53.13$
 $\hat{S} = (432 + j576) \text{ VA}$

Q2)


$P = |I_{rms}|^2 R = 12^2 * 3 = 432 \text{ W}$

$Q_L = |I_{rms}|^2 X_L = 12^2 * 9 = 1296 \text{ VAR}$

$Q_C = |I_{rms}|^2 X_C = 12^2 * 5 = 720 \text{ VAR}$

$S = P + jQ = 432 + j1296 - 720j$
 $\hat{S} = 432 + j576 \text{ VA}$

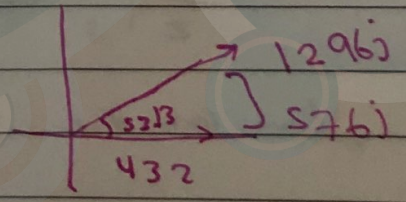$Pf = \cos(\phi_v - \phi_i)$
 $Pf = \cos(0 - 53.13)$
 $Pf = .6$ lagging



important facts related to Complex Power.


⊙ Impedance triangle

$$Z = R + jX$$

$$P = |Z| \cos \theta$$

$$jX = |Z| \sin \theta$$
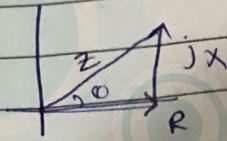
$$\theta = \tan^{-1} \left(\frac{X}{R} \right)$$



$$|Z| = \sqrt{R^2 + X^2}$$

⊙ Power triangle


$$S = P + jQ$$

$$P = |S| \cos \theta$$

$$Q = |S| \sin \theta$$


$$\theta = \tan^{-1} \left(\frac{Q}{P} \right)$$

$$|S| = \sqrt{P^2 + Q^2}$$

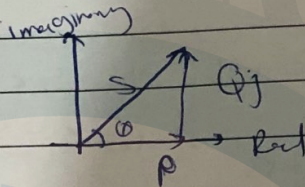

$$S = P + jQ$$


$$S = P - jQ$$

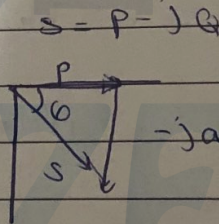

⊕ Resistive load


$$Z = R$$

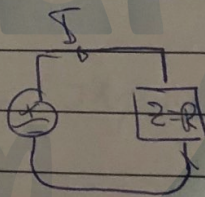assume $V_s = 1 \angle 0^\circ \text{ V}$



$$\bar{I} = \frac{V_s}{Z} = \frac{1 \angle 0^\circ \text{ V}}{R} \rightarrow \frac{1}{R} \angle 0^\circ \text{ V}$$

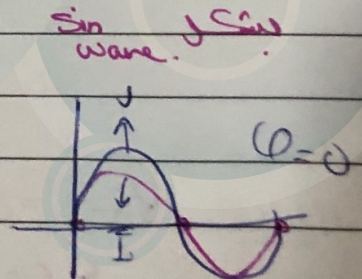You can see $\theta_v = \theta_i$
 $\theta_v - \theta_i = 0$



∴ the voltage & the current across R are in phase


$$PF = \cos(\theta_s - \theta_i)$$

$$PF = 1$$

$$Q = |S| \sin(\theta_v - \theta_i) = 0$$


$$P = |S| \cos(\theta_v - \theta_i) = |S|$$

سنگر متوازن

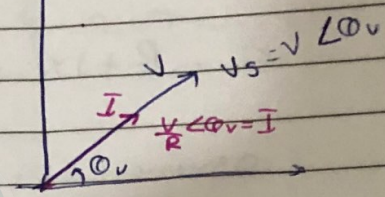

* Capacitive load

$$Z = R - jX = |Z| \angle -\tan^{-1}\left(\frac{X}{R}\right)$$

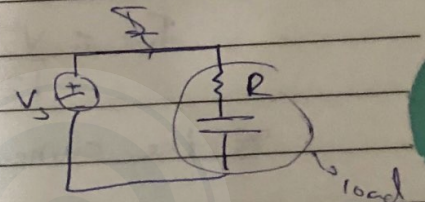


assume $V_s = V \angle \theta_v$

$$I = \frac{V_s}{Z} = \frac{V \angle \theta_v}{|Z| \angle -\tan^{-1}\left(\frac{X}{R}\right)}$$

$$I = \frac{V}{|Z|} \angle \theta_v + \tan^{-1}\left(\frac{X}{R}\right) \rightarrow \text{positive value}$$

* the current leads the voltage

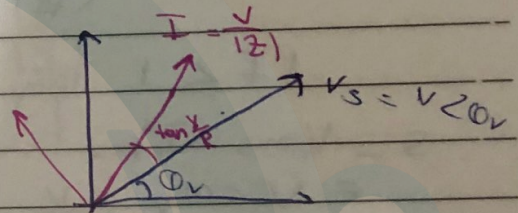


$$PF = \cos(\theta_v - \theta_i)$$

$$\cos(\theta_v - (\theta_v + \tan^{-1}\left(\frac{X}{R}\right)))$$

$$\cos(-\tan^{-1}\left(\frac{X}{R}\right))$$

PH < 1 → leading

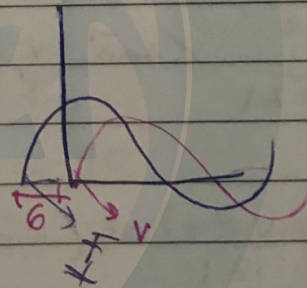

$$S = V_{rms} I_{rms}$$


$$= V \angle \theta_v \left(\frac{V}{|Z|} \angle -\theta_v + \tan^{-1}\left(\frac{X}{R}\right) \right)$$

$$\frac{V^2}{|Z|} \angle -\tan^{-1}\left(\frac{X}{R}\right)$$

$$= \frac{V^2}{|Z|} \cos\left(-\tan^{-1}\left(\frac{X}{R}\right)\right) + j \frac{V^2}{|Z|} \sin\left(-\tan^{-1}\left(\frac{X}{R}\right)\right)$$

Q < 1 → negative

* Inductive loads

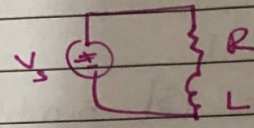


$$Z = R + jX = |Z| \angle \tan^{-1}\left(\frac{X}{R}\right)$$

assume $V_s = V \angle \omega t$

$$I = \frac{V_s}{Z} = \frac{V \angle \omega t}{|Z| \angle \tan^{-1}\left(\frac{X}{R}\right)}$$

$$I = \frac{V}{|Z|} \angle \omega t - \tan^{-1}\left(\frac{X}{R}\right)$$

* the current lag voltage

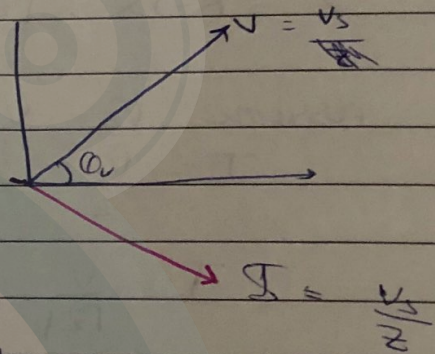

$$PF = \cos(\omega_v - \omega_i)$$

$$= \cos(\omega_v - \omega_v - \tan^{-1}\left(\frac{X}{R}\right))$$

$$= \cos \tan^{-1}\left(\frac{X}{R}\right)$$

PF < 1 lag



$$S = V_{rms} I_{rms}^*$$

$$= V \angle \omega t \left(\frac{V}{|Z|} \angle -\omega t + \tan^{-1}\left(\frac{X}{R}\right) \right)$$


$$= \frac{V^2}{|Z|} \angle \tan^{-1}\left(\frac{X}{R}\right) \rightarrow \text{angle } i +$$

$$= \frac{V^2}{|Z|} \cos\left(\tan^{-1}\left(\frac{X}{R}\right)\right) +$$


$$j \frac{V^2}{|Z|} \sin\left(\tan^{-1}\left(\frac{X}{R}\right)\right)$$

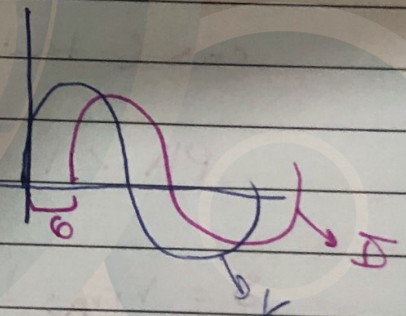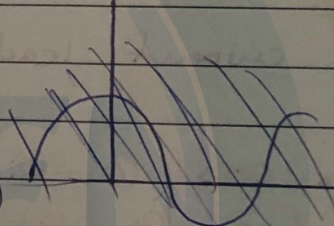

(ex)


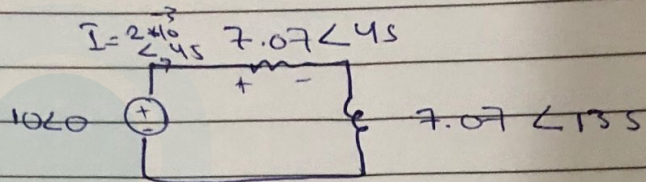


Draw phasor diagram:

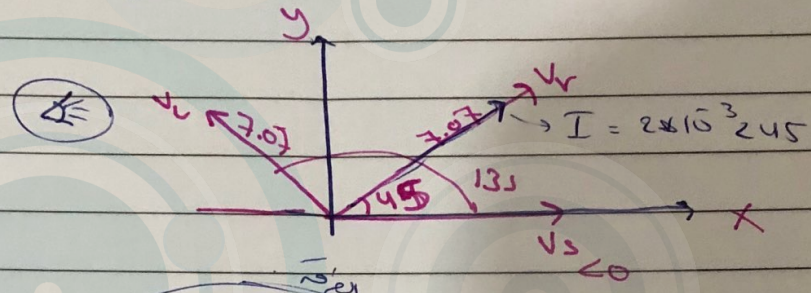

I lags V_r
 V_r leads V_s
 $135 - 45$

(ex)

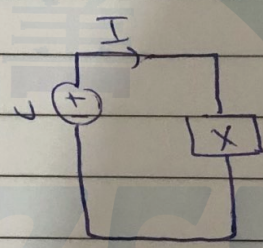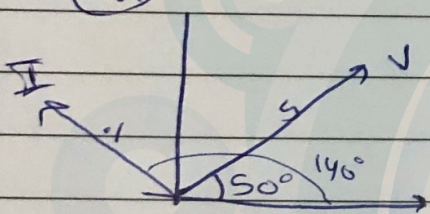

$V = 5 \angle 50$
 $I = 0.1 \angle 140$

$X = \frac{V}{I} = \frac{5 \angle 50}{0.1 \angle 140}$

$X = 50 \angle -90$

$X = -j50 \rightarrow$ Pure capacitive

