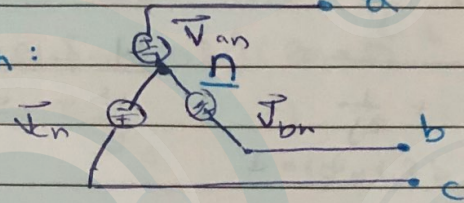


Three phase system: we have 3 sinusoidal voltages with equal amplitudes & freq but 120° phase shift between them.

Y or Δ configuration

① Y configuration:





* $V_{line} = \sqrt{3} V_{ph}$

n: neutral node

$\vec{V}_{an} = V \angle 0^\circ$ $V: rms$

$\vec{V}_{bn} = V \angle -120^\circ$

$\vec{V}_{cn} = V \angle -240^\circ$

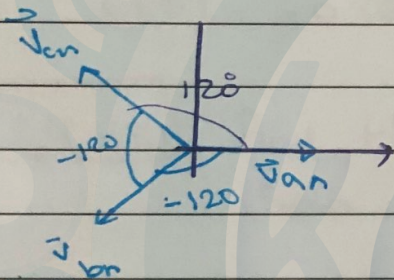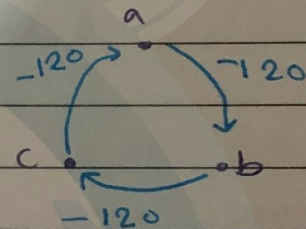


$\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = ??$

Note: $V \angle 0^\circ + V \angle -120^\circ + V \angle -240^\circ = 0$


$\vec{V}_{an} / \vec{V}_{bn} / \vec{V}_{cn} \rightarrow$ phase voltages

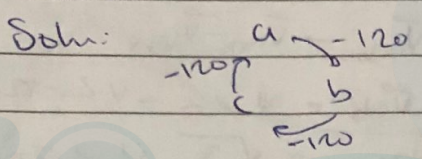ex: if $\vec{V}_{an} = 120 \angle 60$ volt
find \vec{V}_{bn} & \vec{V}_{cn}




$$\vec{V}_{bn} = 120 \angle -60$$

-120 V

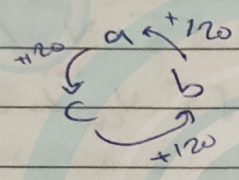


$$\vec{V}_{cn} = 120 \angle 180 \rightarrow 60 + 120 = 180$$

b to c $\rightarrow -60 - 120 = -180$

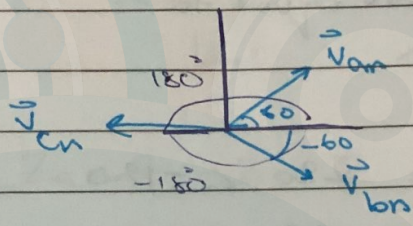

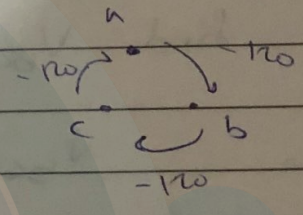
ex $V_{Bn} = 240 \cos(\omega t + 10)$
find $V_{An}(t)$ & $V_{Cn}(t)$




Solu $V_{Bn} = 240 \angle 10$


$$V_{An} = 240 \angle 130 = 240 \cos(\omega t + 130)$$

$$V_{Cn} = 240 \cos(\omega t - 110)$$

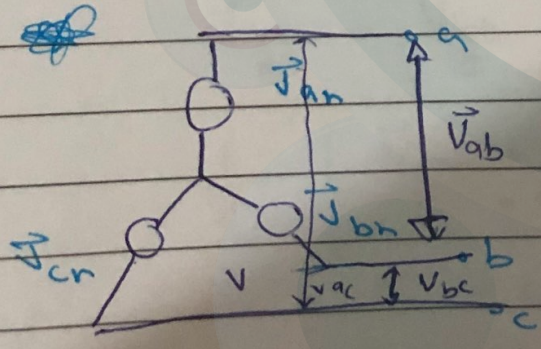

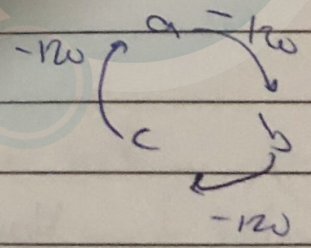$\vec{V}_{ab} / \vec{V}_{bc} / \vec{V}_{ca} \rightarrow$ line voltages



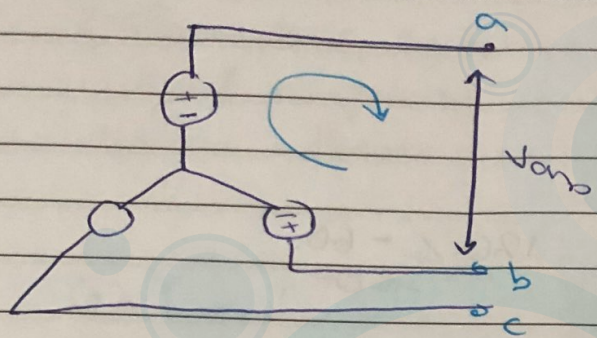

By KVL: $\vec{V}_{bn} - \vec{V}_{an} + \vec{V}_{ab} = 0$

$$\vec{V}_{ab} = \vec{V}_{an} - \vec{V}_{bn}$$

$$\vec{V}_{ab} = V \angle 0^\circ - V \angle -120^\circ$$

supply

$$\vec{V}_{ab} = \sqrt{3} V_{an} \angle 30^\circ$$

$$\vec{V}_{bc} = \sqrt{3} V_{bn} \angle 30^\circ$$

$$\vec{V}_{ca} = \sqrt{3} V_{cn} \angle 30^\circ$$


the line voltages are equal to $\sqrt{3} * V_n \angle 30^\circ$

(ex) if $V_{bn} = 220 \angle -120^\circ$
 $V_{an} = 220 \angle 0^\circ$ phase voltages
 find $V_{bc} \rightarrow V_{ca}$

Soln $V_{bc} = \sqrt{3} V_{bn} \angle 30^\circ$
 $= \sqrt{3} (220 \angle -120^\circ) \angle 30^\circ = 381.1 \angle -90^\circ \text{ (V)}$


$$\vec{V}_{ca} = \sqrt{3} \vec{V}_{cn} \angle 30^\circ = \sqrt{3} \vec{V}_{cn} \angle 30^\circ$$
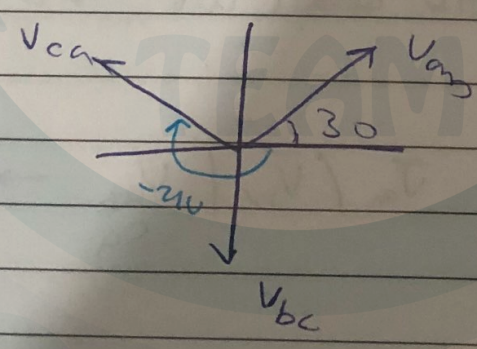
$$= \sqrt{3} \angle 220 \angle -240 \angle 30^\circ = 381.1 \angle -210^\circ \text{ (V)}$$



$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ = \sqrt{3} (220 \angle 0^\circ) \angle 30^\circ$$

$$= 381.1 \angle 30^\circ$$

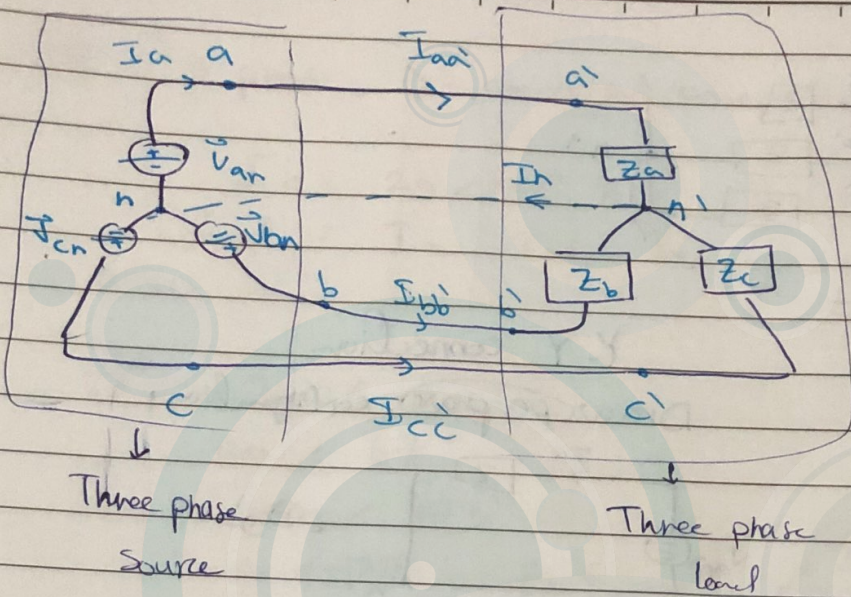


assume Balanced Load $\rightarrow Z_a = Z_b = Z_c = Z$

$I_a \rightarrow$ phase current

$I_{aa'} \rightarrow$ line current
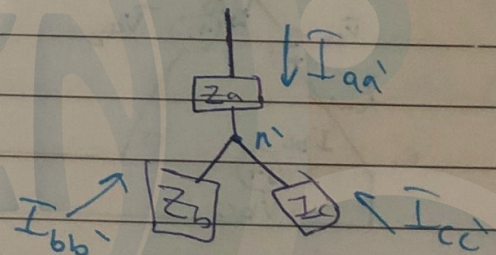
$$I_{\text{phase}} = I_{\text{line}} \rightarrow \text{a/c/s/s/c}$$




$$I_a + I_b + I_c = 0$$

$$\frac{\vec{V}_{an}}{Z} + \frac{\vec{V}_{bn}}{Z} + \frac{\vec{V}_{cn}}{Z} = 0 = I_n$$

$$\frac{1}{Z} (\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn}) = I_n$$

$I_n = 0 \rightarrow$ current in the wire between $(n-n') = 0$

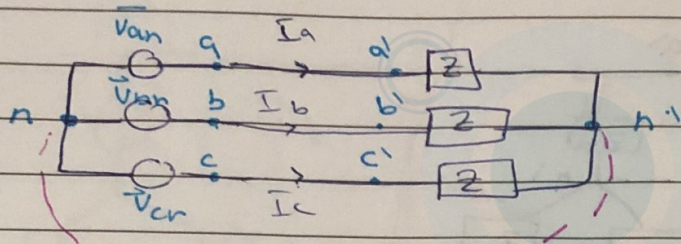$V_{nn'} = 0 \rightarrow$ any element between n & n' is not used in calculation




$$I_n = 0$$

$$V_{nn'} = 0$$


Y-Y connection

Draw per phase configuration

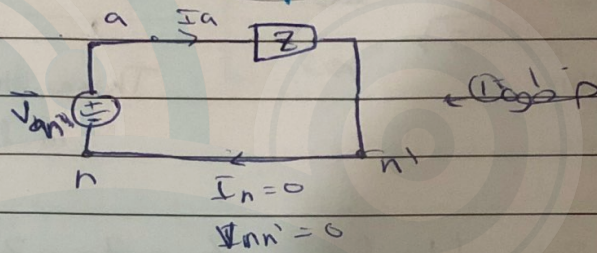

C g i b i o i S a s

* تسمى دائرة

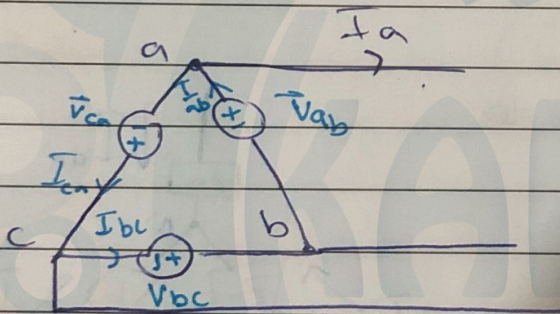

* note → Δ connection is rarely used

$$I_{ab} \neq I_a$$

ساده لكل

$$I_{ab} = I_a + I_{ca}$$

$$I_a = I_{ab} - I_{ca}$$

$$\Rightarrow I_a = \sqrt{3} I_{ab} \angle -30^\circ$$

$$I_b = \sqrt{3} I_{bc} \angle -30^\circ$$

$$I_c = \sqrt{3} I_{ca} \angle -30^\circ$$

$I_a / I_b / I_c \rightarrow$ line current

$I_{ab} \circ I_{bc} \circ I_{ca} \rightarrow$ phase current

$$V_{\text{phase}} = V_{\text{line}}$$

⊗ 3 phase, Δ-connected power supply

$$I_c = 20 \angle 53^\circ \text{ A}$$

Find: $I_a, I_{ab}, I_{bc}, I_b, I_{ca}$



Soln:

$$\vec{I}_a = \vec{I}_c \angle -120$$

$$20 \angle -67^\circ$$

$$\vec{I}_b = 20 \angle 173^\circ$$

$$= 20 \angle -187^\circ$$

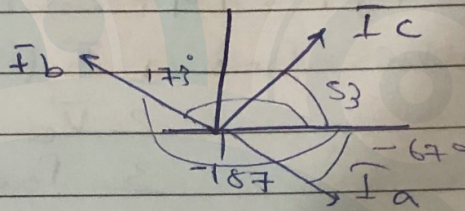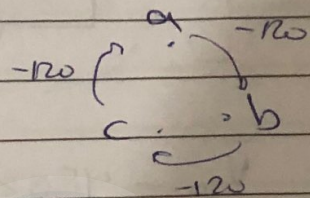



$$\rightarrow \vec{I}_a = \sqrt{3} I_{ab} \angle -30$$

$$\rightarrow \vec{I}_{ab} = \frac{20 \angle -67}{\sqrt{3} \angle -30} = 11.55 \angle -37 \text{ A}$$

$$\rightarrow \vec{I}_b = \sqrt{3} I_{bc} \angle -30 \Rightarrow I_{bc} = 11.55 \angle -157^\circ$$
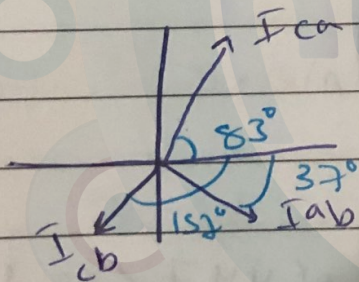
$$\rightarrow \vec{I}_c = \sqrt{3} I_{ca} \angle -30 \rightarrow \vec{I}_{ca} = 11.55 \angle 83 = 11.55 \angle -27$$



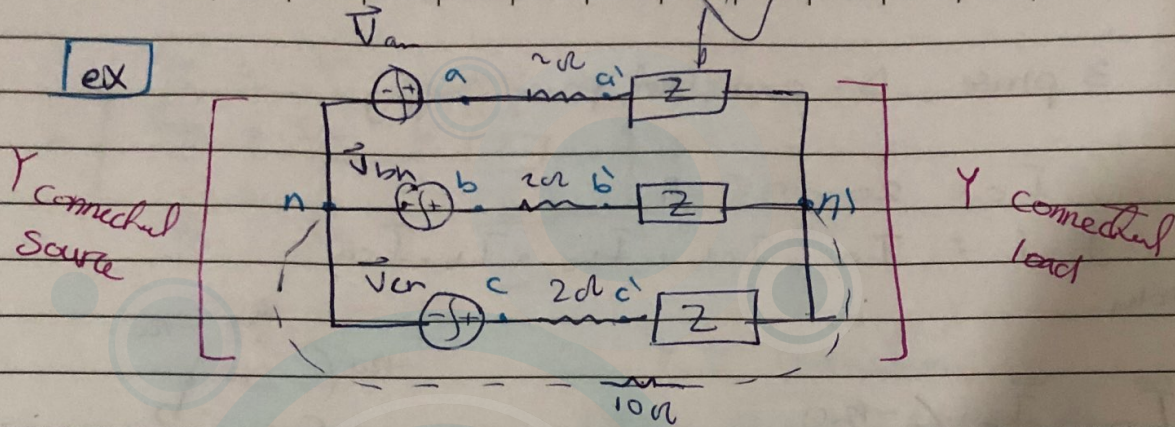

$V_{an} = 480 \angle 0$


$Z = 2 + j4 = 4.47 \angle 63.4^\circ \Omega$

assume rms values find: $\pm \vec{S}$ @ the load

- 1 \vec{V}_{cn}
- 2 Power losses in wires
- 3 PF @ load
- 4 A @ source
- 5 \vec{S} @ source.

Solu ->

1 Draw per phase system

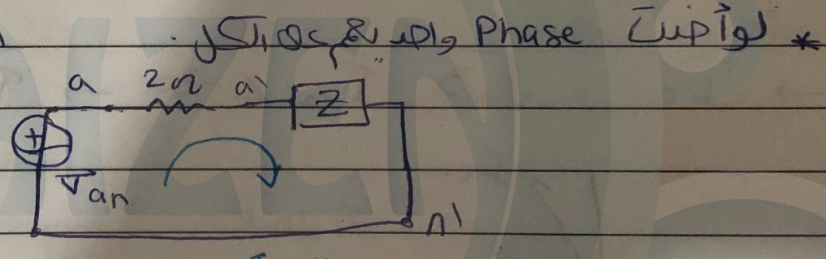

By KVL

$V_{an} + 2I_a + ZI_a = 0$

$I_a = 84.85 \angle -45^\circ \text{ A}$

$V_z = V_{an'} = I_a * Z = (84.85 \angle -45^\circ) * (4.47 \angle 63.4^\circ) = 379.5 \angle 18.4 \text{ volt}$

$\vec{S}_{load} = V_{an'} I_a^* = (379.5 \angle 18.4^\circ) (84.85 \angle 45^\circ)$
 Phase A = $32.2 \times 10^3 \angle 63.4 \text{ VA}$

$S_{load} (\text{total}) = 3 * 32.2 \times 10^3 \angle 63.4$

Phases * $\sqrt{3} = 96.6 \times 10^3 \angle 63.4 \text{ VA}$


(2) $\vec{V}_{ca} = \sqrt{3} \vec{V}_{ca} \angle 30$

given $\vec{V}_{an} = 480 \angle 0$

$\vec{V}_{cn} = \vec{V}_{an} \angle 120$

$\vec{V}_{cn} = 480 \angle 120$

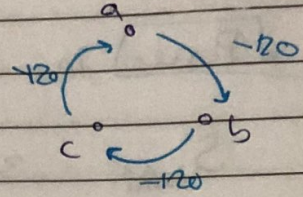$\vec{V}_{ca} = \sqrt{3} * 480 \angle 120 * \angle 30 = 831.4 \angle 150^\circ$ (V)



المطلوب $\vec{V}_{c'a'} = \sqrt{3} \vec{V}_{c'n'} \angle 30$

$\vec{V}_{an} = 379.5 \angle 18.4$ من فرق الجهد

$\vec{V}_{cn} = \vec{V}_{an} = 379.5 \angle 18.4 \angle 120 = 379.5 \angle 138.5$

$\vec{V}_{c'a'} = \sqrt{3} * 379.5 \angle 138.5 \angle 30 = 657.3 \angle 168.4^\circ$

(3) Power losses in wires

Power loss in Phase a = $|I_a|^2 * R = 84.8^2 * 2 = 14.4 \text{ kW}$

Power losses total = $3 * 14.4 = 43.2 \text{ kW}$

(4) PF @ load = $\cos(\theta_v - \theta_i) = \cos(18.4 - -45)$

@load = 0.45 lag

(5) PF @ source = $\cos(\theta_v - \theta_i) = \cos(0 - -45) = 0.75 \text{ lag}$

(6) $\vec{S}_{\text{source}} = \vec{V}_{an} * \vec{I}_a^* = 480 \angle 0 * 848 \angle 45$

= $40.73 * 10^3 \angle 45 \text{ VA}$

$\vec{S}_{\text{total}} = 3 * 40.73 * 10^3 \angle 45 = 122.2 * 10^3 \angle 45 \text{ VA}$

$S_{\text{source}} = S_{\text{load total}} + S_{\text{losses total}}$

Power in 3 phase system

$$\begin{aligned} \vec{S}_{\text{total}} &= 3 V_{\text{phase}} \vec{I}_{\text{phase}}^* \\ &= \sqrt{3} \vec{V}_{\text{line}} \vec{I}_{\text{line}}^* \\ &= P_{\text{total}} + jQ_{\text{total}} \end{aligned}$$


$$\begin{aligned} P_{\text{total}} &= 3 V_{\text{phase}} I_{\text{phase}} \cos(\theta_v - \theta_i) \\ &= \sqrt{3} V_{\text{line}} I_{\text{line}} \cos(\theta_v - \theta_i) \end{aligned}$$

$$Q = 3 V_{\text{phase}} I_{\text{phase}} \sin(\theta_v - \theta_i)$$

$$= \sqrt{3} V_{\text{line}} I_{\text{line}} \sin(\theta_v - \theta_i)$$

$$\text{PF} = \cos(\theta_v - \theta_i) \begin{matrix} \rightarrow \text{lead} \\ \downarrow \text{lag} \end{matrix}$$

Y-D connection

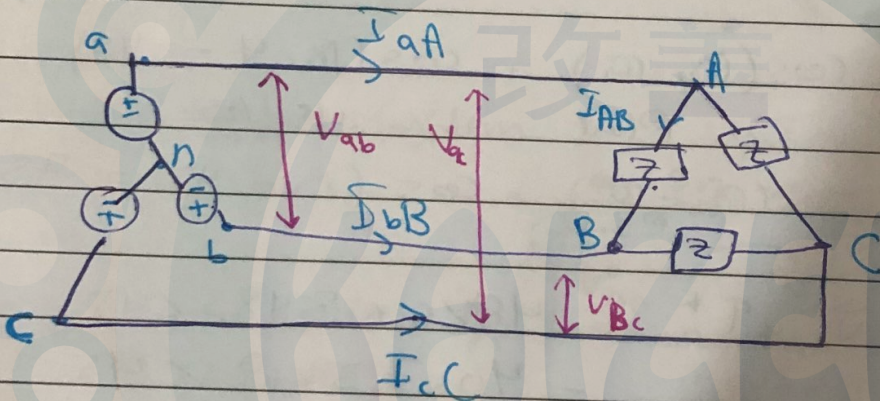

$Z_{\text{load}} = \text{balanced}$

$$V_{AB} = V_{ab}$$

$$\vec{I}_{AB} = \frac{\vec{V}_{ab}}{Z} = \frac{\sqrt{3} \vec{V}_{an}}{Z} \angle 30^\circ$$

$$\vec{I}_{BC} = \frac{\vec{V}_{bc}}{Z} = \frac{\sqrt{3} \vec{V}_{bn}}{Z} \angle 30^\circ$$


$$\vec{I}_{CA} = \frac{\vec{V}_{ac}}{Z} = \frac{\sqrt{3} \vec{V}_{cn}}{Z} \angle 30^\circ$$

$$\text{or } I_{aA} = \sqrt{3} I_{AB} \angle -30^\circ$$

Example

7/8/2020

(ex)

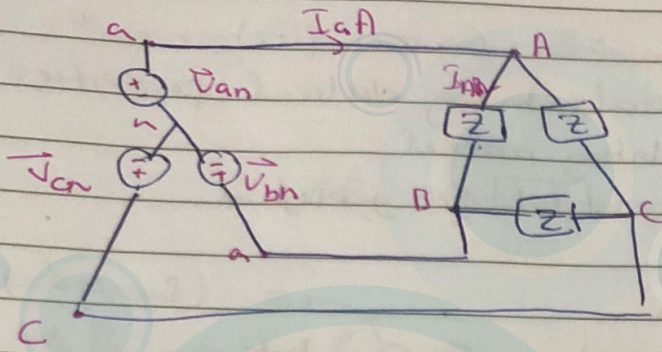

given: $Z = 8 + 4j \Omega$
 find ① \vec{I}_{AB}

$\vec{V}_{an} = 100 \angle 10^\circ$ volt
 ② S_{total} (same)

Solu \rightarrow

method ①

$$\vec{I}_{AB} = \frac{\vec{V}_{ab}}{Z} = \frac{\sqrt{3} \vec{V}_{an} \angle 30^\circ}{Z}$$

$$= \frac{\sqrt{3} (100 \angle 10^\circ) \angle 30^\circ}{8 + 4j}$$

$$\vec{I}_{AB} = 19.36 \angle 13.4^\circ \text{ A}$$


method ②

conversion from Δ to Y

$$Z_1 = \frac{Z \times Z}{3Z} = \frac{Z}{3} = 2.67 + j1.33$$

connection is $y \rightarrow y$

* Draw per phase

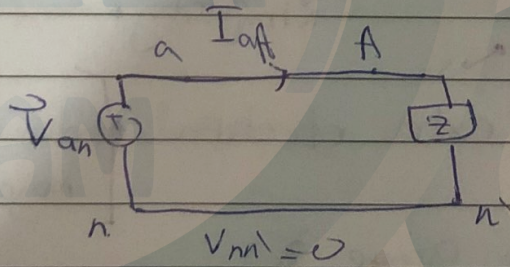

نکات *

آمزینا
 صلا

$$I_{aA} = \frac{\vec{V}_{an}}{Z} = 33.53 \angle -16.6^\circ \text{ A}$$

$$I_{aA} = \sqrt{3} \vec{I}_{AB} \angle -30^\circ$$

$$\vec{I}_{AB} = 19.36 \angle 13.4^\circ \text{ A}$$

* $S_{total} = 3 V_{phase} \times I_{phase}$


$$= 3 \angle 100 \angle 10^\circ (33.53 \angle +16.6^\circ) = 10.06 \text{ kW} \angle 26.6^\circ \text{ VA}$$

Five Apple

* Semiconductor - Devices : Si, Germanium (Ge)

semiconductors are materials having electrical properties between conducting & insulating material

المواد التي لها خواص بين موصل و عازل

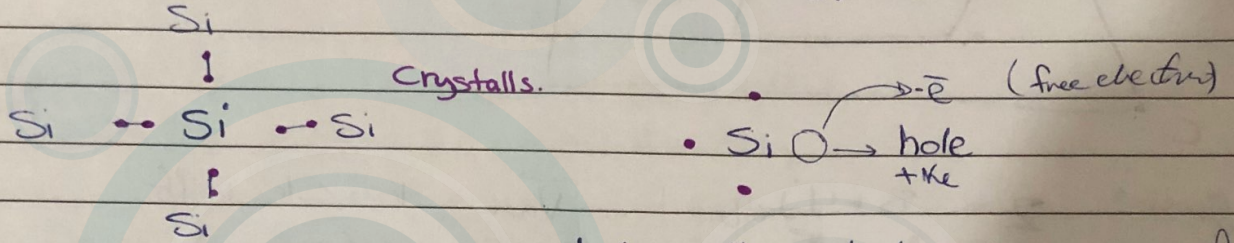


hole: When electron leaves the atom it creates a hole with + sign

* Two types of charge carrier

- ① free electron → -ve sign
 - ② hole → +ve sign
- they both travel in opposite direction


* Doping: a way to control of # of charges by adding impurities to the structure of semi conductor

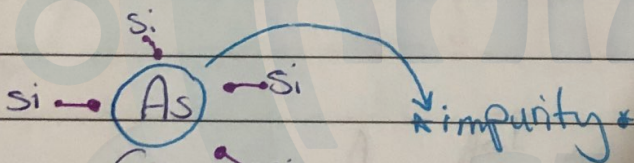- impurities could be from group 5 of periodic table (5 e in the last level




donor → n-type semiconductor
majority carrier is e (-ve sign)

* Group 3

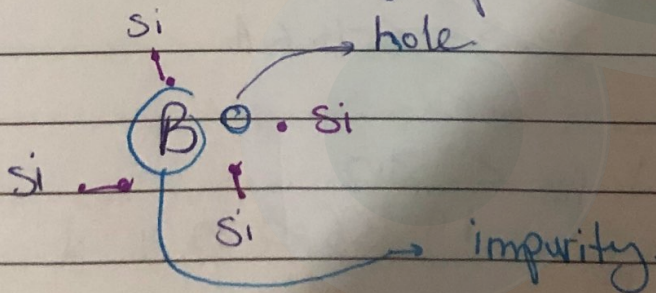


acceptor → p type semiconductor
majority carrier is hole (+ve sign)

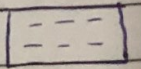Summary: So n-type semiconductor: majority is electron (-ve) sign




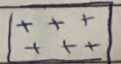P-type semiconductor: majority is hole (+ve) sign




* Pn junction & semiconductor Diode

P-type → majority is holes +ve sign

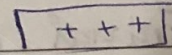


n-type → majority is electrons

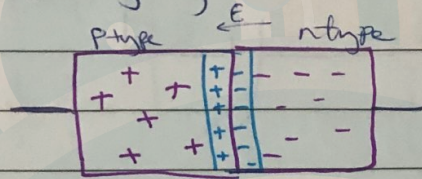


depletion region

depletion region: region where free electron recombine with hole. (no charge carrier)

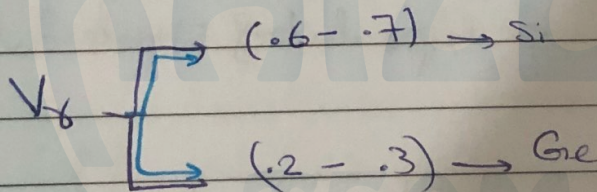
→ Charge separation causes potential to exist @ pn junction & called gamma $V = V_g$



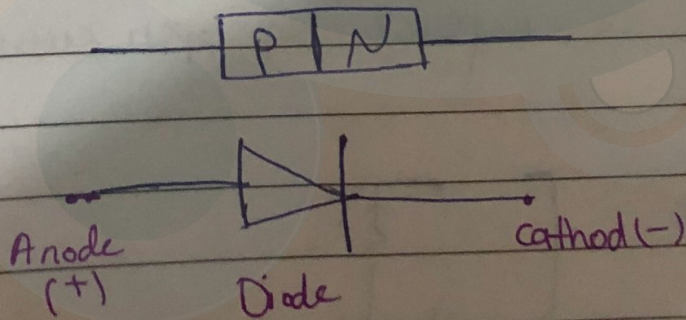
* connecting Pn Junction to external source




① Reverse Biase

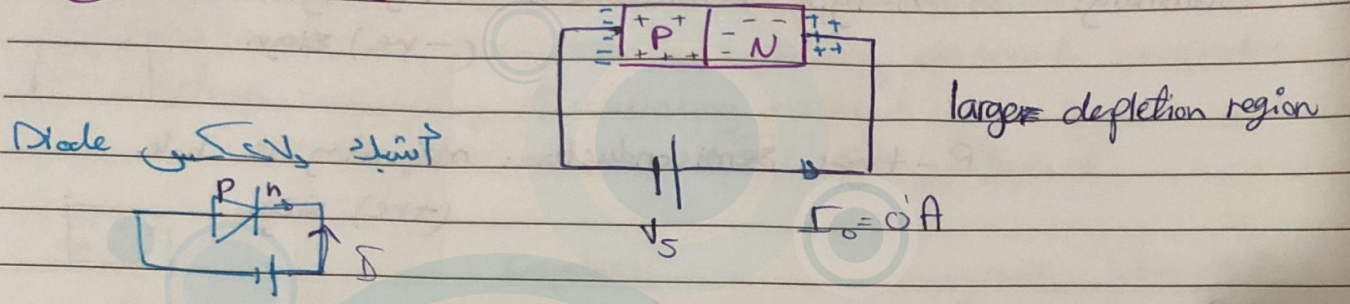


② Forward Biase

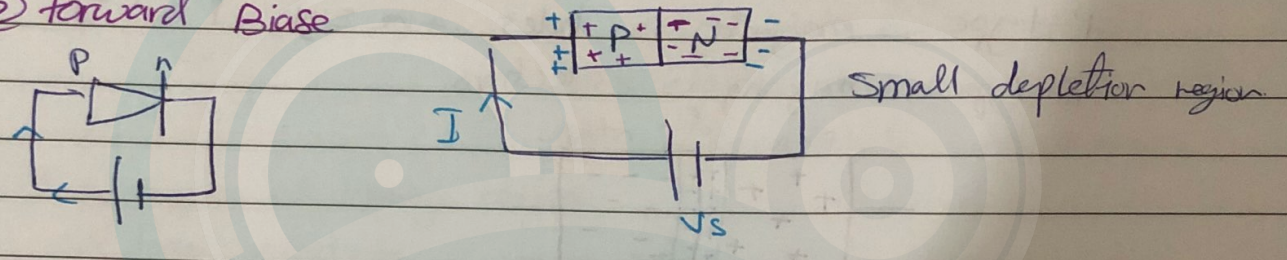


* Ideal Diode

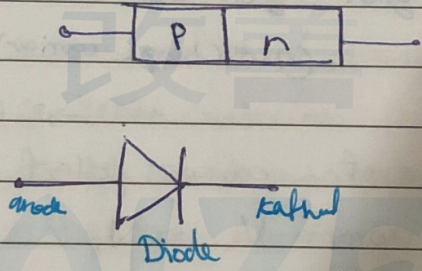


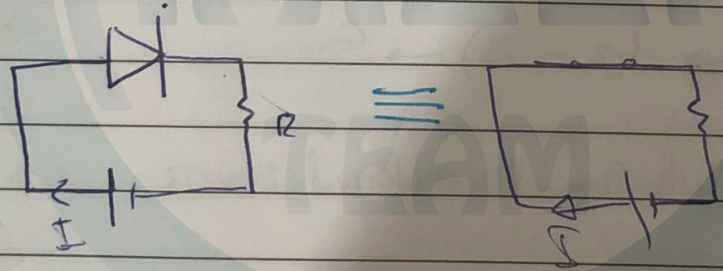① Forward bias: Diode is replaced by short circuit



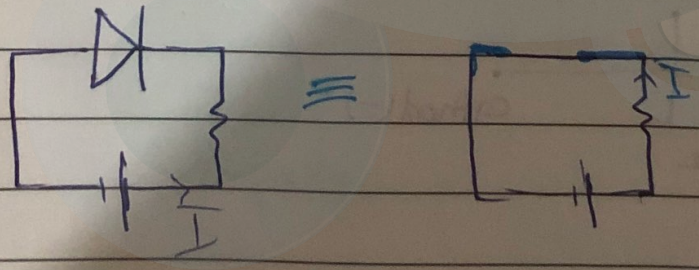② Reverse bias: Diode is replaced by open circuit






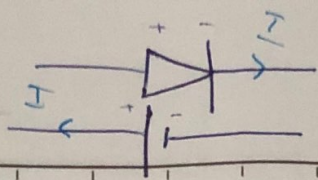

Polarity

⊛ Practical Diode

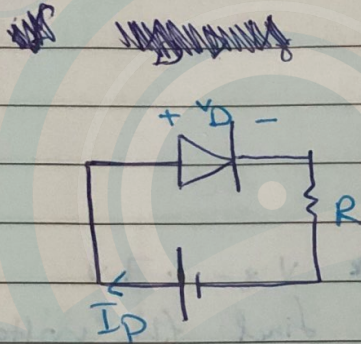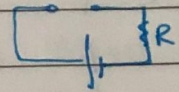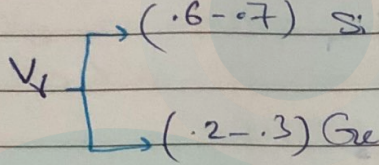① Forward Biase: Diode is replaced by supply with value of:



Forward

① forward off if $V_D < V_g$

② forward on if $V_D > V_g$

$$I_D = (I_0 (e^{qV_D/kt} - 1)) \text{ A}$$


$$I_D = I_0 (e^{qV_D/kt} - 1)$$

q : electron charge = $1.6 \times 10^{-19} \text{ C}$

T : temperature Kelvin



k : Boltzman constant $1.381 \times 10^{-23} \text{ J/K}$

I_0 : saturation current (μA)


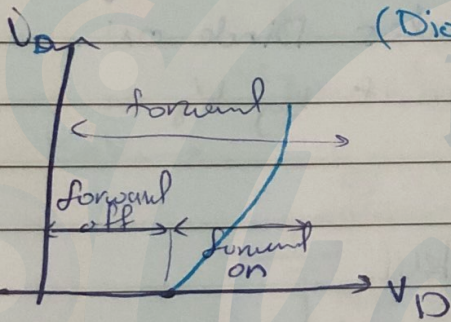


(Diode eqn)

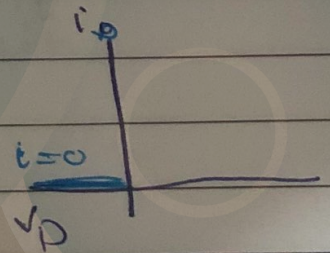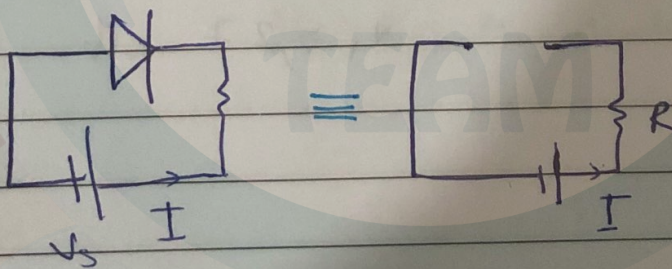
② Reverse Biase: Diode is replaced by open circuit



I-V characteristic for diode

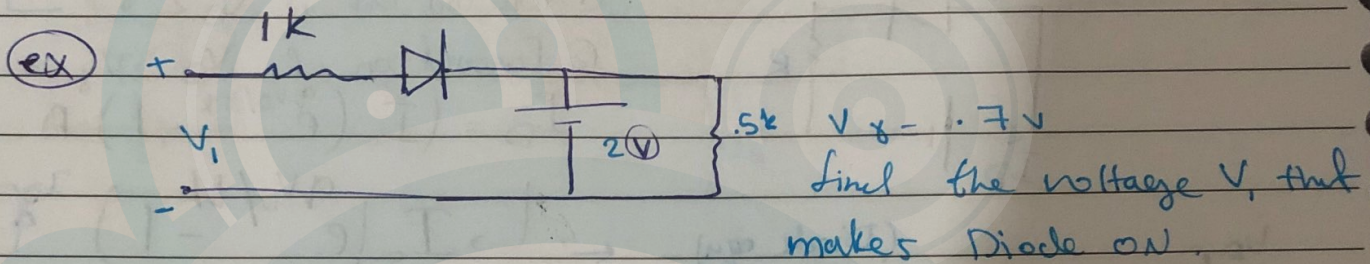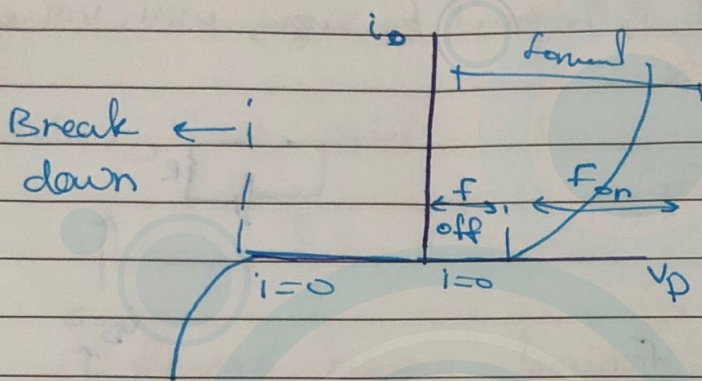

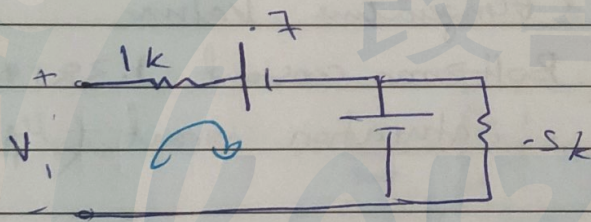Solu \rightarrow Since Diode is ON \rightarrow replace it by V_f



By KVL

$$-V_i + 0 + 1k + 0.7 + 2 = 0$$

$$V_i = 2.7 \text{ volt}$$

on standard Test junction

to make diode ON

$$V_i > 2.7 \text{ volt}$$

10/8/2020


* Steps to solve to know if Diode is on

1 replace diode by open circuit

2 find V_D on diode

3 if $V_D > V_g \Rightarrow$ diode is on

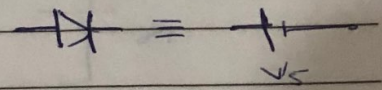
\Rightarrow replace it by voltage source have value of V_g



4 if $V_D < V_g \Rightarrow$ diode is off


\Rightarrow replace it by open circuit.

ex

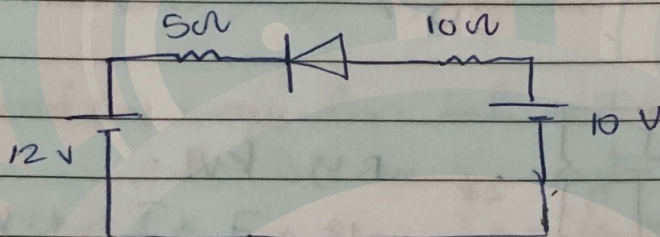

$V_g = .7V \rightarrow$ find if diode on or off

Solu \rightarrow

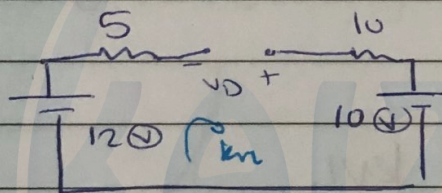


By KVL $\Rightarrow 12 + 5 \times 0 - V_D + 5 \times 0 + 10 = 0$

open circuit $\Rightarrow I = 0$

$V_D = -2$ volt


$V_g > V_D \Rightarrow$ diode is off

ex 2

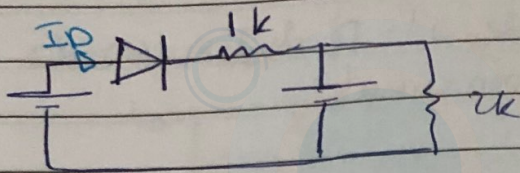

$V_f = .7$ find I_D

Solu:

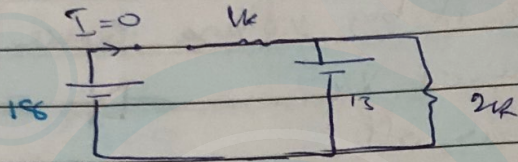


By KVL =

$$-18 + V_D + 0 + 13 = 0$$

$$V_D = 5$$

$V_D > V_f \therefore$ Diode is on

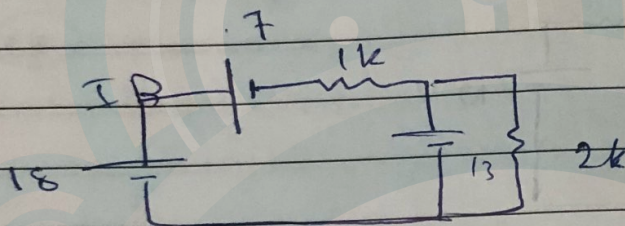


By KVL:

$$-18 + .7 + I_D(1k) + 13 = 0$$

$$I_D = 4.3 \text{ mA}$$

* load line

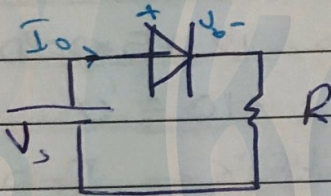

using KVL

$$-V_s + V_D + I_D R = 0$$

$$I_D = \frac{V_s - V_D}{R} \quad \rightarrow (1)$$

$$I_D = I_0 \left(e^{\frac{qV_D}{kT}} - 1 \right) \quad \rightarrow (2)$$

I_0 & V_0
are unknowns


* موارد ليتي بصحولين

* ماينفع باستخدام الالاد \rightarrow \leftarrow \rightarrow \leftarrow من حيث الالاد graphs

Load line

10/8/2020

Chag detesh lab

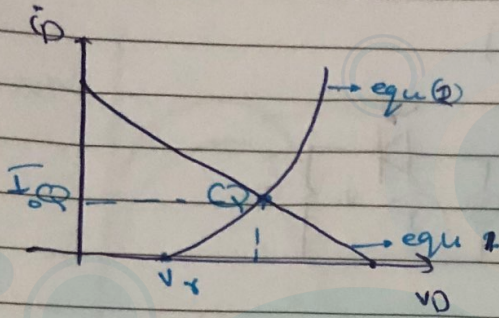

Q : Quiescent point (J Stobis)



Solution graphically $\rightarrow V_{DQ}$ & I_{DQ}

Load line: equation between I_D & V_D

for this ex \rightarrow load line eq:

$$I_D = \frac{V_s}{R} - \frac{V_D}{R}$$

(ex) Find I_D & V_D using the graph

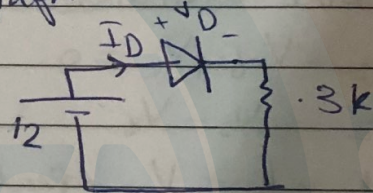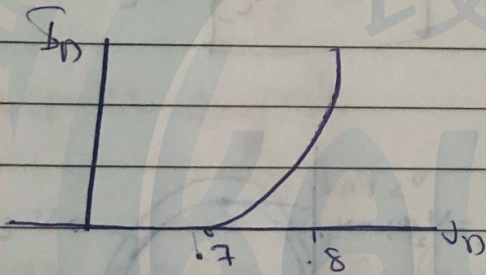


Soln \rightarrow to find load line use KVL

$$-12 + V_D + .3k \cdot I_D = 0$$

$$I_D = \frac{12}{.3k} - \frac{V_D}{.3k} \rightarrow \text{if } I_D = 0 \quad V_D = 12 \text{ V}$$
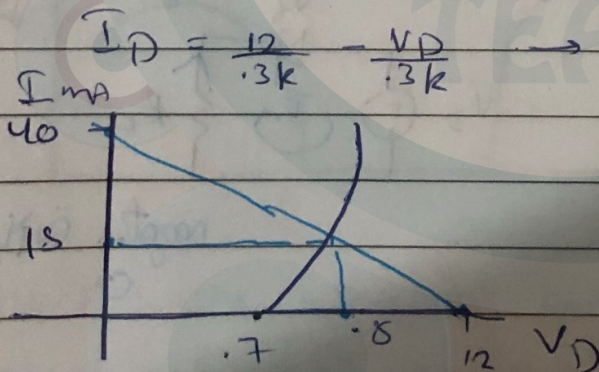
$$\text{if } V_D = 0 \quad I_D = \frac{12}{.3} = 40 \text{ mA}$$





From graph \rightarrow

$$V_{DQ} = 7.9 \text{ volt}$$

$$I_{DQ} = 15 \text{ mA}$$

(@ Q point)

* 1 Half wave rectifier (HWR)

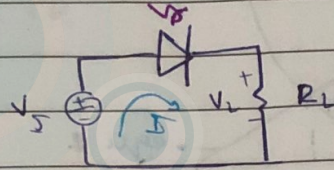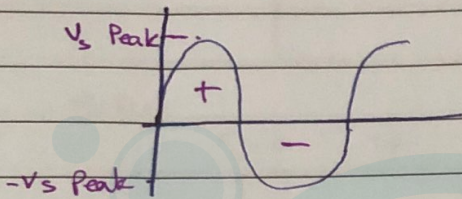

(A) During the +ve cycle

By KVL \rightarrow to test if diode


is on or off \rightarrow

$$-v_s + V_D + 0 = 0$$

$$V_D = v_s$$

to make diode on $\rightarrow V_D > V_\gamma$

$v_s > V_\gamma \rightarrow$ should be


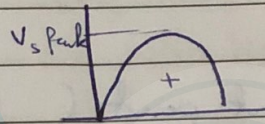


By KVL when diode is on

$$-v_s + V_\gamma + V_L = 0$$

$$V_L = v_s - V_\gamma$$
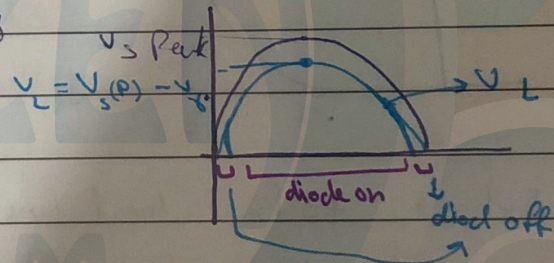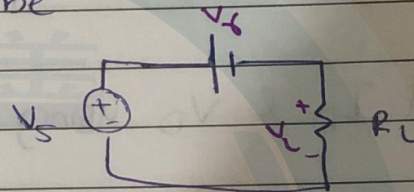
$$V_{L \text{ peak}} = V_s (\text{Peak}) - V_\gamma$$




(B) During the negative cycle


Diode is reverse biased

\Rightarrow off \Rightarrow open circuit


$$I = 0 \quad V_L = 0$$

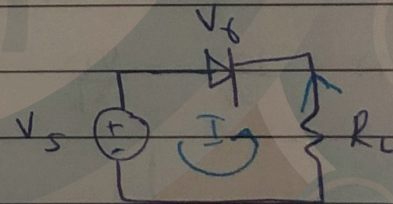

negative cycle

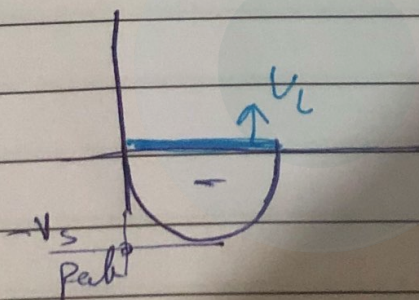

Q. 10

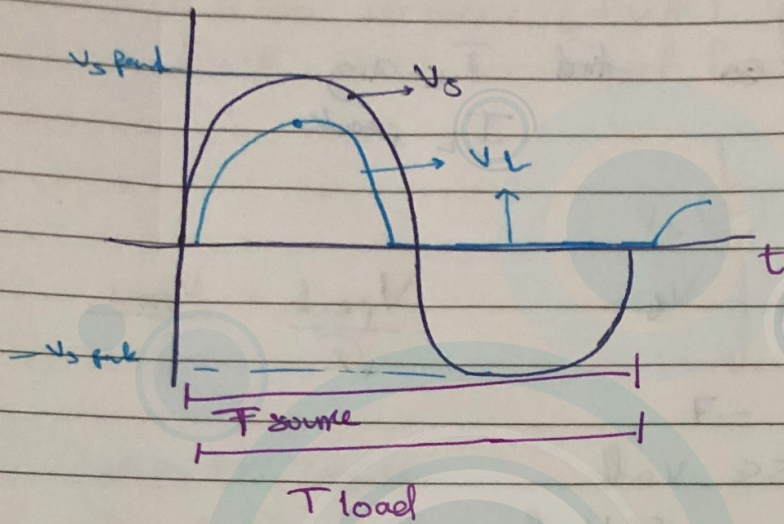

$$\rightarrow \therefore T_{\text{source}} = T_{\text{load}}$$



$$\rightarrow f_{\text{source}} = f_{\text{load}}$$

$$\rightarrow V_L \text{ avg} = \frac{1}{T} \int_0^T V_L(t) dt = V_{L \text{ avg}} = \frac{V_L \text{ peak}}{\pi}$$

$$\rightarrow I_L (\text{avg}) = \frac{V_L \text{ avg}}{R}$$


$$\rightarrow I_L (\text{peak}) = \frac{V_L \text{ peak}}{R}$$

* adding capacitor effects:

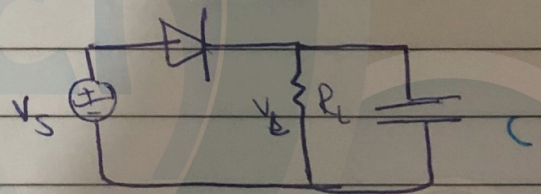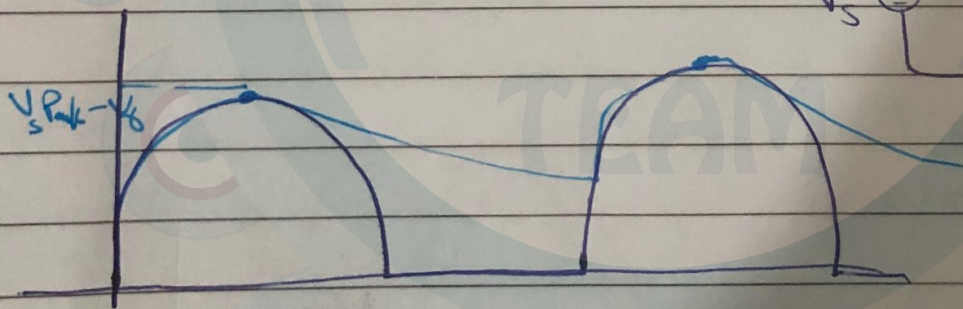

HW R: one way to convert from AC to DC but this method is inefficient

ex

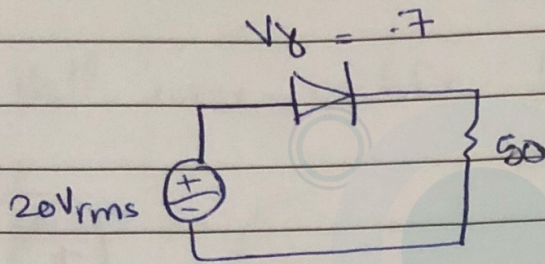

find I_L avg
 I_L peak

Solu: HWR

$$V_{L \text{ peak}} = V_{s \text{ peak}} - V_d$$

$$\frac{V_{\text{peak}}}{\sqrt{2}} = \frac{V_{\text{rms}}}{\sqrt{2}}$$

$$\textcircled{1} \quad V_{L \text{ peak}} = 20\sqrt{2} - 0.7 \\ = 27.58 \text{ Volt}$$


$$\textcircled{2} \quad I_{L \text{ peak}} = \frac{V_{L \text{ peak}}}{50} = 0.5516 \text{ A}$$

$$\textcircled{3} \quad V_L \text{ avg} = \frac{V_{L \text{ peak}}}{\pi} = \frac{27.58}{\pi} = 8.78 \text{ V}$$

$$I_L \text{ avg} = \frac{V_L \text{ (avg)}}{50} = 0.175 \text{ A}$$

② Full wave rectifier (FWR) using bridge

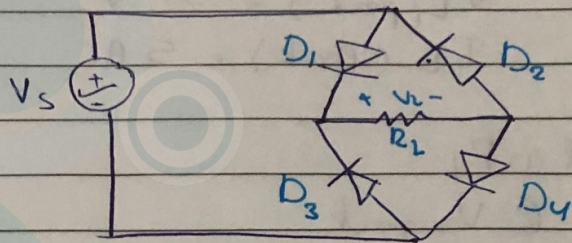FWR: used to convert from AC to DC with efficient way



Ⓐ During +ve cycle

D_1 & D_4 on


D_2 & D_3 off

By KVL

$$-V_s + V_d + V_L + V_d = 0$$

$$V_L = V_s - 2V_d$$
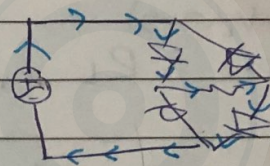
$$V_{L \text{ peak}} = V_{s \text{ (peak)}} - 2V_d$$





Ⓑ During (-ve) cycle

$$V_{L \text{ peak}} = V_{s \text{ peak}} - 2V_d$$

D_3 & $D_2 \rightarrow$ on

D_1 & $D_4 \rightarrow$ off

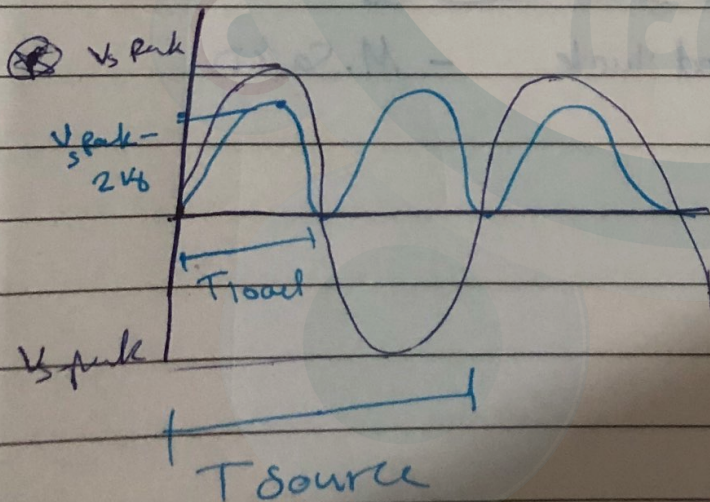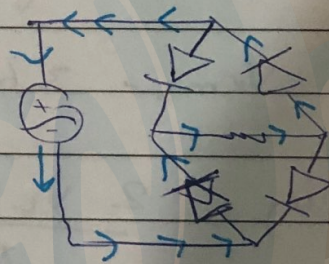

$$T(\text{source}) = 2T(\text{load})$$

$$1/T_{\text{source}} = 1/2 T_{\text{load}}$$

$$2I_{\text{source}} = I_{\text{load}}$$

$$V_{L \text{ peak}} = V_{s \text{ peak}} - 2V_d$$

$$V_{L \text{ avg}} = 2V_{L \text{ peak}} / \pi$$

$$I_{L \text{ avg}} = V_{L \text{ avg}} / R_L$$

Ex FWR, Bridge, V_s (all bridges) = 6V

$$V_L(\text{peak}) = 50 \text{ V}$$

$$I_L(\text{Peak}) = 5 \text{ A}$$

find (1) R_L

(2) $V_s(\text{peak})$

(3) $V_s(\text{rms})$

(4) $V_L(\text{avg})$

Solu: $R_L = \frac{V_L(\text{peak})}{I_L(\text{peak})} = \frac{50}{5} = 10 \Omega$

$$V_L(\text{peak}) = V_s(\text{peak}) - I V_s$$

$$50 = V_s(\text{peak}) - 2 \times 6$$

$$V_s(\text{peak}) = 51.2 \text{ volt}$$

$$V_s(\text{rms}) = \frac{V_s(\text{Peak})}{\sqrt{2}}$$

$$V_{\text{rms}} = 36.2 \text{ volt}$$

$$V_L(\text{avg}) = \frac{2 V_L(\text{peak})}{\pi} = 31.83 \text{ volt}$$



Allah mashaAllah

Good luck - M. SAKO