

Question #	Q1 (8)	Q2 (3)	Q3 (5)	Q4 (8)	Q5 (6)	Q6 (8)	Q7 (5)	Q8 (7)
Grade:	6	7	5	8	2	8	5	5


Show Your Calculations




Question # 1 (8 points)

For the circuit shown below, use voltage and current dividers to calculate

a.	the voltage v_1 .	$v_1 =$	24 v	V
b.	the voltage v_2 .	$v_2 =$	6 v	V
c.	the voltage v_3 .	$v_3 =$	6 v	V
d.	the current i_1 .	$i_1 =$	3 A	A
e.	the current i_2 .	$i_2 =$	2 A	A
f.	the current i_3 .	$i_3 =$	1 A	A

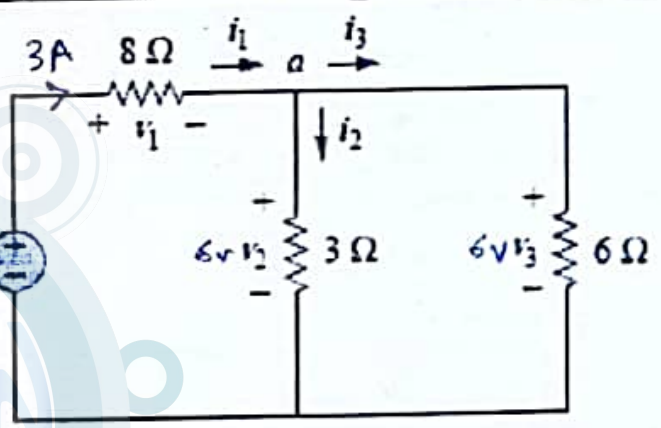

$V = IR$

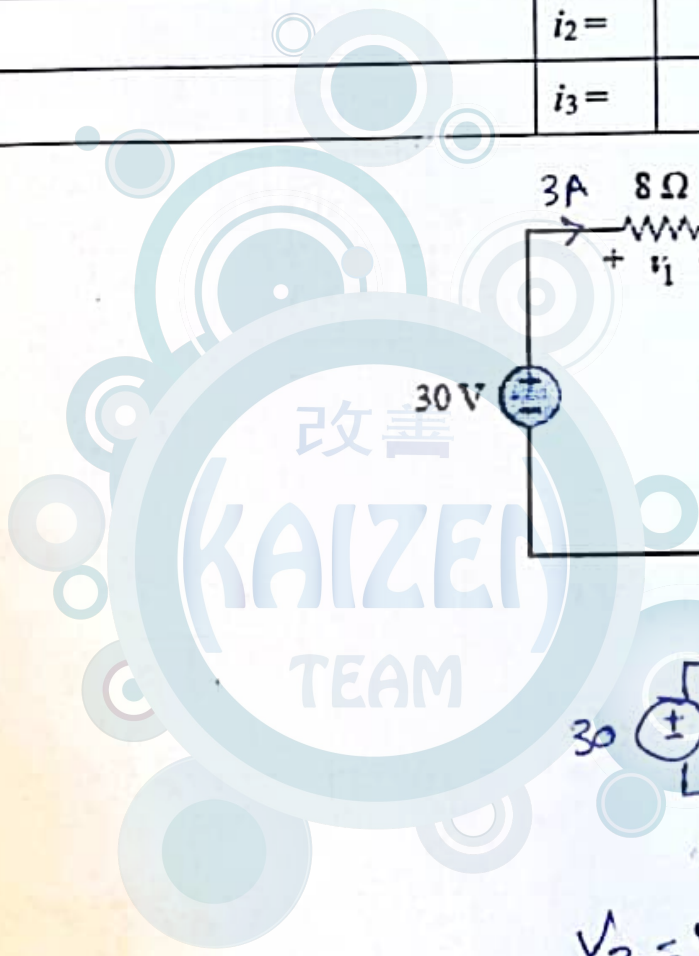


30 V \square 10Ω $I_{\text{total}} = 3 \text{ A}$
 $v_1 = 24 \text{ V}$
 $v_3 = v_2 = 6 \text{ V}$
 $i_2 = 2 \text{ A}, i_3 = 1 \text{ A}$

Question 2 (3 points)

Find R_{eq} for the circuit shown below.

$R_{eq} = 5 \text{ k}\Omega$

Show Your Calculations

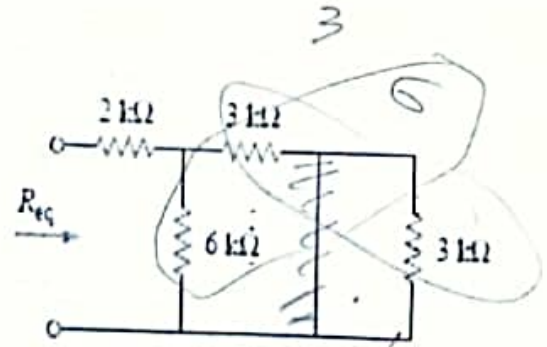

Series $3 + 3 = 6 \text{ k}\Omega$
 Parallel $\frac{1}{6} + \frac{1}{6} = \frac{2}{6} = \frac{1}{3} \text{ k}\Omega$
 Series $3 + 2 = 5 \text{ k}\Omega$

Question 3 (5 points)

For the circuit shown below, find

Show Your Calculations

a.	the current I .	$I =$	-0.2 A	A
b.	the power absorbed by the $4\text{-}\Omega$ resistor.	$P_{4\Omega} =$	0.16 absorbed	W
c.	the power absorbed by the $6\text{-}\Omega$ resistor.	$P_{6\Omega} =$	0.24 absorbed	W
d.	the power generated or absorbed by the 3-V voltage source.	$P_{3V} =$	0.6 absorbed	generated W
e.	the power generated or absorbed by the 5-V voltage source.	$P_{5V} =$	-1 absorbed	generated W

(a) $-3 + 4I + 5V + 6I = 0$


$I = -0.2 \text{ A}$

(b) $P_{4\Omega} = IV = I^2 R = (-0.2)^2 4 = 0.16 \text{ watt}$

(c) $P_{6\Omega} = I^2 R = (-0.2)^2 (6) = 0.24 \text{ watt}$

(d) $P_{3V} = IV = -(-0.2) 3 = 0.6 \text{ watt}$

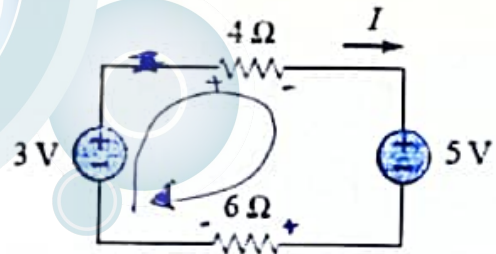
(e) $P_{5V} = IV = -0.2 \times 5 = -1 \text{ watt}$



Question 4 (8 points)**Show Your Calculations**

For the circuit shown below, the voltage across the resistance R is $V_o = 4V$, find

a.	the current I_1 supplied by the 20-V voltage source,	$I_1 =$	1 A ✓	A
b.	the current I_2 flowing through the 6- Ω resistor,	$I_2 =$	0.667 A ✓	
c.	the resistance R .	$R =$	12 Ω ✓	Ω
d.	the equivalent resistance seen by the voltage source.	$R_{eq} =$	20 Ω ✓	Ω

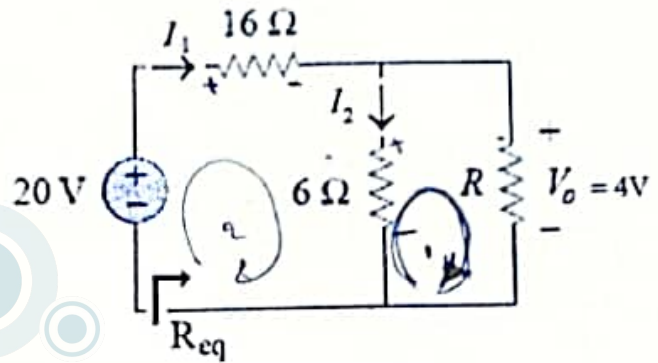

Loop (1)

$$-I_2 \times 6 + 4 = 0$$

$$+I_2 \times \frac{6}{6} = \frac{+4}{6}$$

$$I_2 = 0.667$$

Loop (2)

$$-20 + I_1 \times 16 + 4 = 0$$

$$I_1 = 1A$$

$$R = \frac{V}{I} = \frac{4}{0.333} \approx 12 \Omega$$

$$\text{Parallel } R_{eq} = \frac{1}{12} + \frac{1}{6} = \frac{1}{4} = 4 \Omega$$

$$\text{Series } 4 + 16 = 20 \Omega$$

Question # 5 (6 points)




Show Your Calculations

For the circuit shown below, use the principle of superposition to find the current i . Draw the corresponding circuit diagrams



a.	Find the current i_1 due to the 6-V voltage source.	$i_1 =$	8	A
b.	Find the current i_2 due to the 2-A current source.	$i_2 =$	∞	A
c.	Find the total current i due to both sources.	$i =$	$8 + \infty = \infty$	A


① Leave 6V

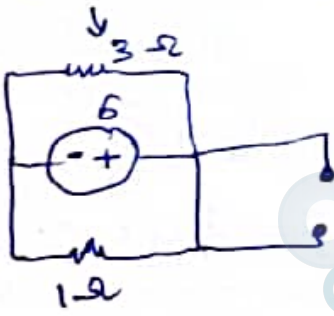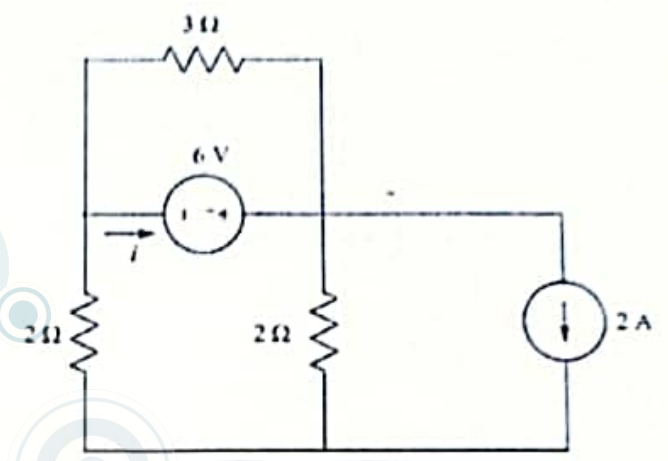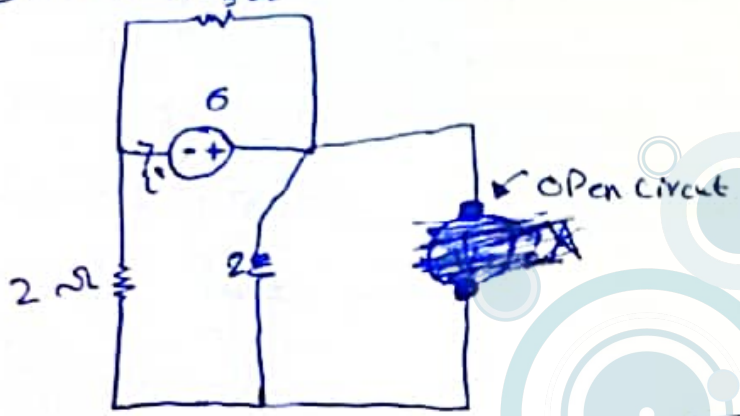

$R_{eq} = 0.75 \Omega$

$I' = \frac{V}{R} = \frac{6}{0.75} = 8A$

② Leave 2A

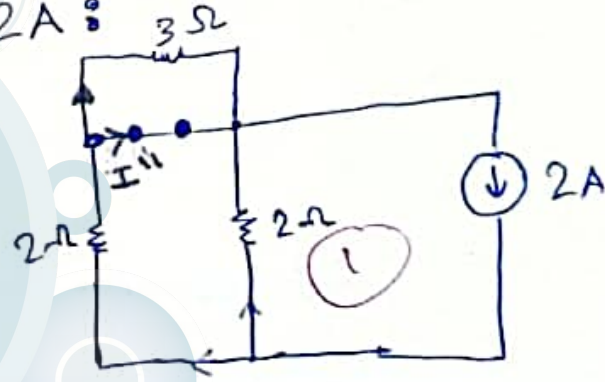


$I'' = \infty, R = 0$



Question # 6 (8 points)

For the circuit shown below use mesh current analysis to find the mesh currents I_1 , I_2 and I_3 .

a.	$I_1 =$	6	A
b.	$I_2 =$	6	A
c.	$I_3 =$	8 A	A

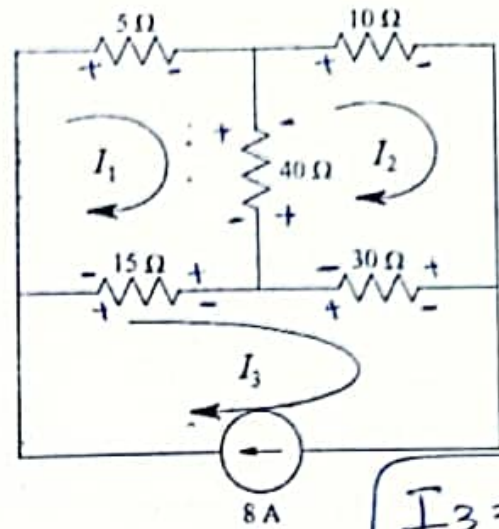

$I_3 = 8A$

I_1 :

$$5I_1 + 40(I_1 - I_2) + 15(I_1 - I_2) = 0$$

$$5I_1 + 40I_1 - 40I_2 + 15I_1 - 15I_2 = 0$$

$$60I_1 - 40I_2 = 0 \quad \text{--- ①}$$

I_2 :


$$+10I_2 + 30I_2 - 30I_3 + 40I_2 - 40I_1 = 0$$

$$80I_2 - 40I_1 = 240 \quad \text{--- ②}$$

Question # 7 (5 points)

For the circuit shown below, use node voltage analysis to find the node voltages V_A and V_B .

a.	$V_A =$	12	V
b.	$V_B =$	18	V

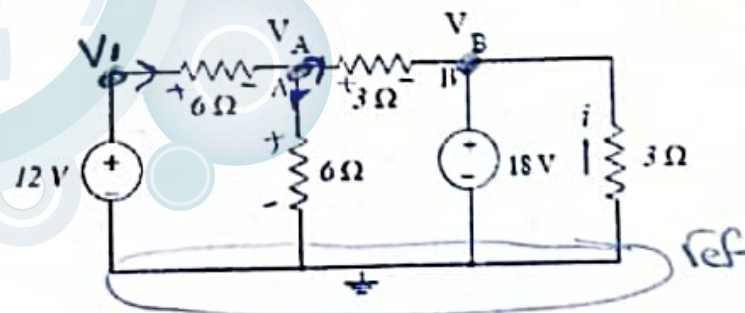

$\sum I_{in} = \sum I_{out}$

$$\frac{12 - V_A}{6} = \frac{V_A - 18}{3} + \frac{V_A}{6}$$



$V_B - 0 = 12$

~~2-VA~~

Question # 8 (7 points)



For the circuit shown below, find

a.	the load resistance R_L for maximum power transfer	$R_L =$	6 <input checked="" type="checkbox"/>	Ω
b.	the Thevenin equivalent voltage	$V_{th} =$	+36 <input checked="" type="checkbox"/>	V
c.	the maximum power absorbed by the load R_L .	$P_{max} =$	216 <input checked="" type="checkbox"/>	W

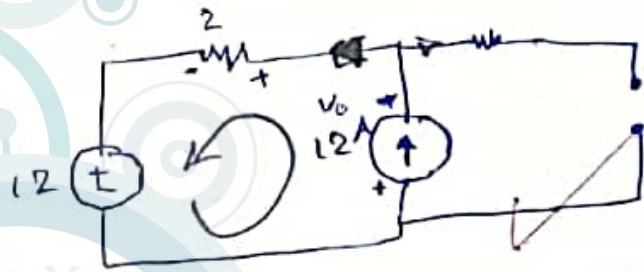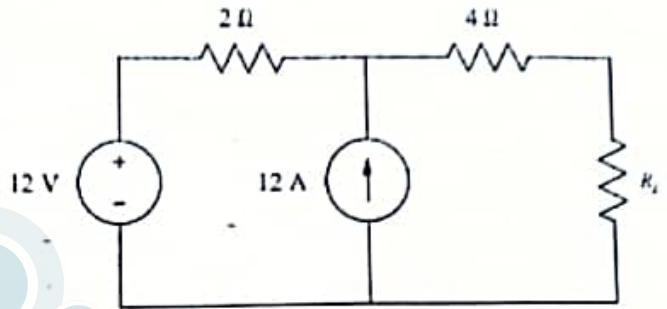

Loop: $V_{th} + 24 + 12 = 0$

$V_{th} = +36$

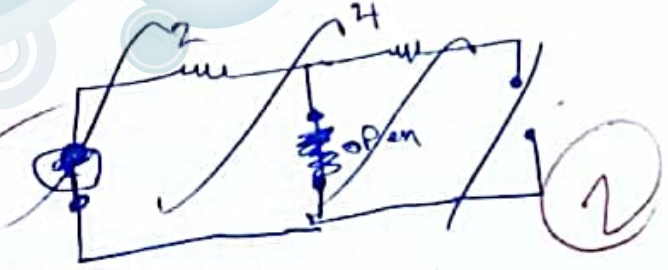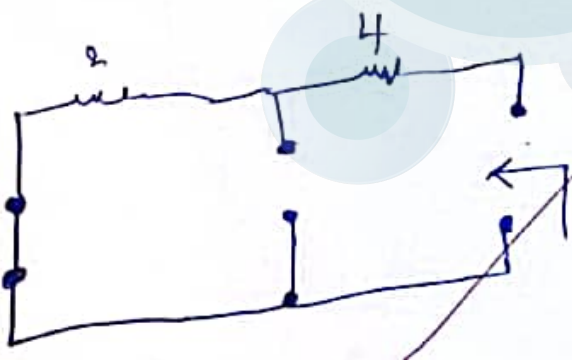

$R_{th} = 6 \Omega$

3

2