

Question # 6 (8 points)

For the circuit shown below use mesh current analysis to find the mesh currents I_1 , I_2 and I_3 .

a.	$I_1 =$	6	A
b.	$I_2 =$	6	A
c.	$I_3 =$	8 A	A


$$\text{I}_1 : 5\bar{\Gamma}_1 + 40(\bar{\Gamma}_1 - \bar{\Gamma}_2) + 15(\bar{\Gamma}_1 - \bar{\Gamma}_3) = 0$$

$$5\bar{\Gamma}_1 + 40\bar{\Gamma}_1 - 40\bar{\Gamma}_2 + 15\bar{\Gamma}_1 - 15\bar{\Gamma}_3 = 0$$

$$60\bar{\Gamma}_1 - 40\bar{\Gamma}_2 - 15\bar{\Gamma}_3 = 0 \quad \textcircled{1}$$

$$\text{I}_2 : +10\bar{\Gamma}_2 + 30\bar{\Gamma}_2 - 30\bar{\Gamma}_3 + 40\bar{\Gamma}_2 - 40\bar{\Gamma}_1 = 0$$

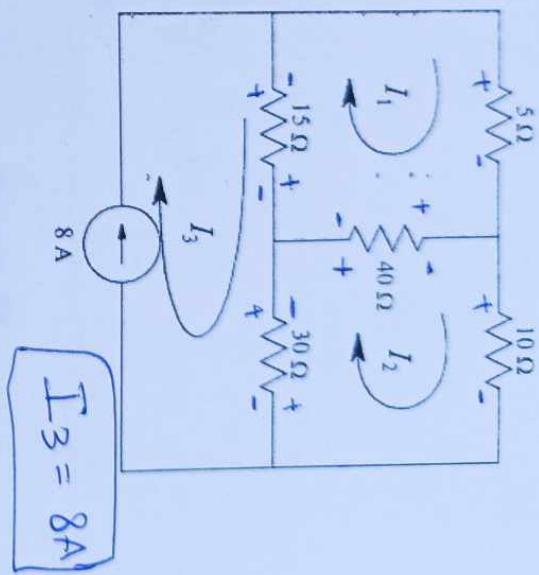
$$80\bar{\Gamma}_2 - 40\bar{\Gamma}_1 = 240 \quad \textcircled{2}$$



Question # 7 (5 points)

For the circuit shown below, use node voltage analysis to find the node voltages V_A and V_B .

a.	$V_A =$	12	V
b.	$V_B =$	18	V

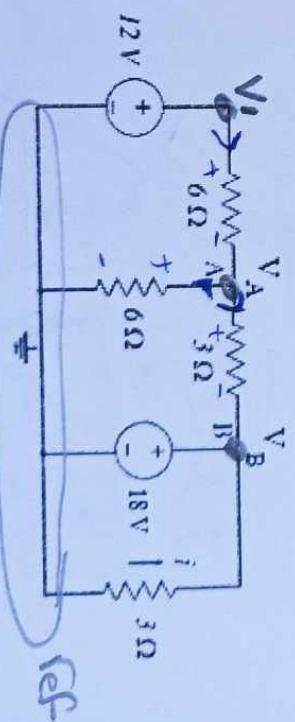

$$\sum I_{in} = \sum I_{out}$$

$$\frac{12 - V_A}{6} = \frac{V_A - 18}{3} + \frac{V_A}{6}$$

$$V_B - 0 = 12$$


~~2nd~~

Question 4 (8 points)

Show Your Calculations

For the circuit shown below, the voltage across the resistance R is $V_o = 4V$, find

- | | | | | |
|----|---|------------|-------------|----------|
| a. | the current I_1 supplied by the 20-V voltage source, | $I_1 =$ | 1 A ✓ | A |
| b. | the current I_2 flowing through the 6Ω resistor, | $I_2 =$ | 0.667 A | |
| c. | the resistance R , | $R =$ | 12Ω | Ω |
| d. | the equivalent resistance seen by the voltage source. | $R_{eq} =$ | 20 Ω | Ω |

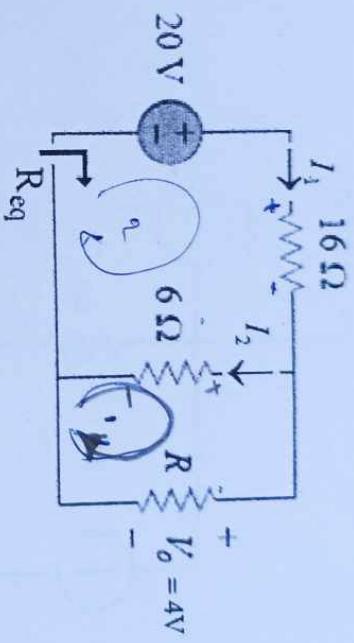

loop 1

$$-I_2 \times 6 + 4 = 0$$

$$+ I_2 \times 6 = 4$$

$$I_2 = 0.667 A$$

loop 2

$$-20 + I_1 \times 6 + 4 = 0$$

$$I_1 = 1 A$$

$$R = \frac{V}{I} = \frac{4}{0.333} \approx 12 \Omega$$


$$R_{parallel} = \frac{1}{12} + \frac{1}{6} = \frac{1}{4} = 4 \Omega$$

$$Series 4 + 16 = 20 \Omega$$

Question # 8 (7 points)

For the circuit shown below, find


a.	the load resistance R_L for maximum power transfer	$R_L =$	6	✓
b.	the Thevenin equivalent voltage	$V_{th} =$	36	✗
c.	the maximum power absorbed by the load R_L .	$P_{max} =$	216	✗

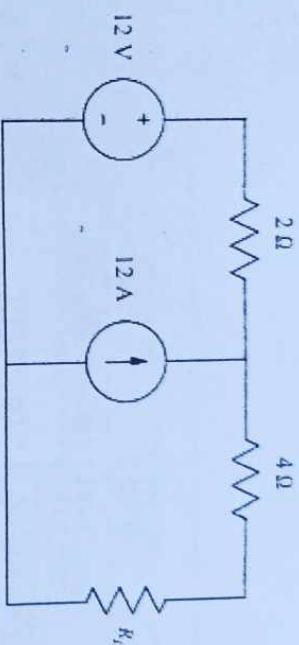


Loop: $V_{th} + 24 + 12 = 0$

$V_{th} = -36$

Part b:

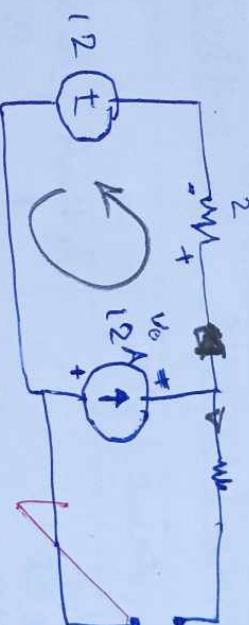

(3)

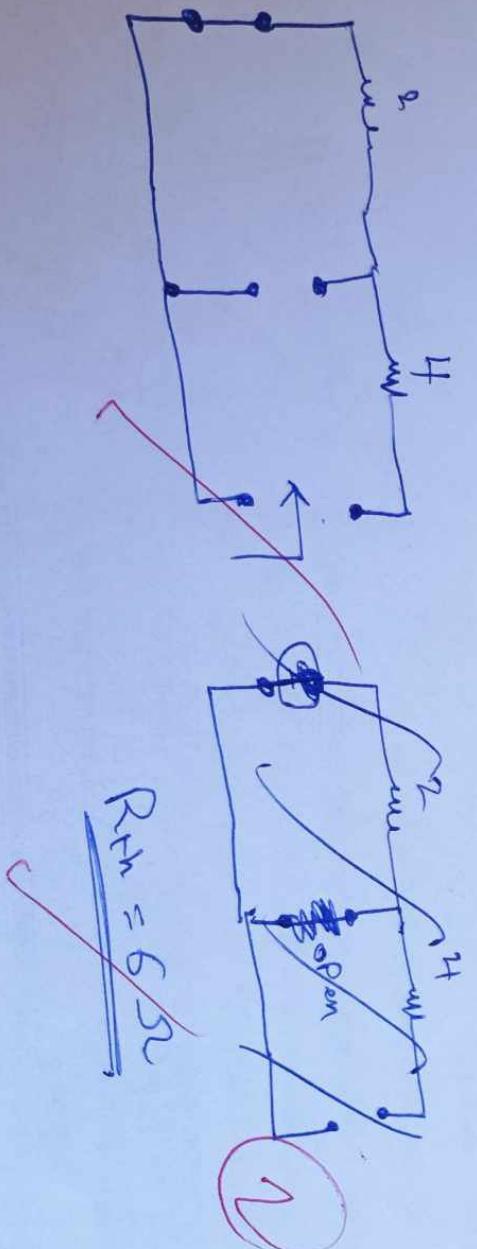

$R_{th} = 6\Omega$



Question #5 (6 points)

For the circuit shown below, use the principle of superposition to find the current i . Draw the corresponding circuit diagrams


Show Your Calculations

a.	Find the current i_1 due to the 6-V voltage source.	$i_1 =$	8 ✓ A
b.	Find the current i_2 due to the 2-A current source.	$i_2 =$	∞ ✓ A
c.	Find the total current i due to both sources.	$i =$	$8 + \infty = \infty$ ✓ A

① Leave 6V

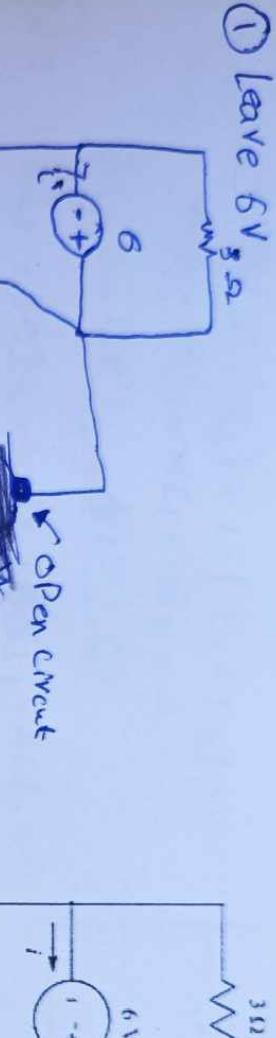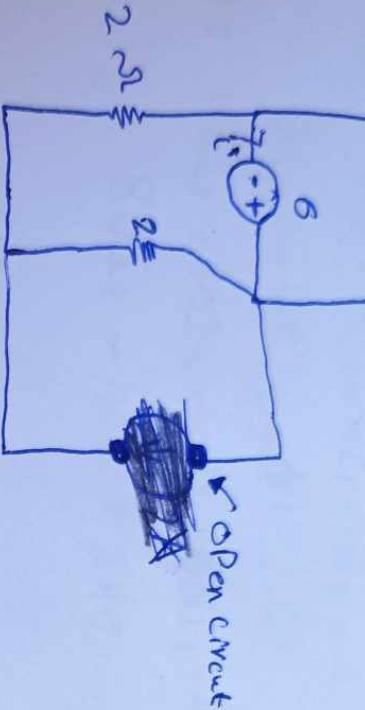

② Leave 2A

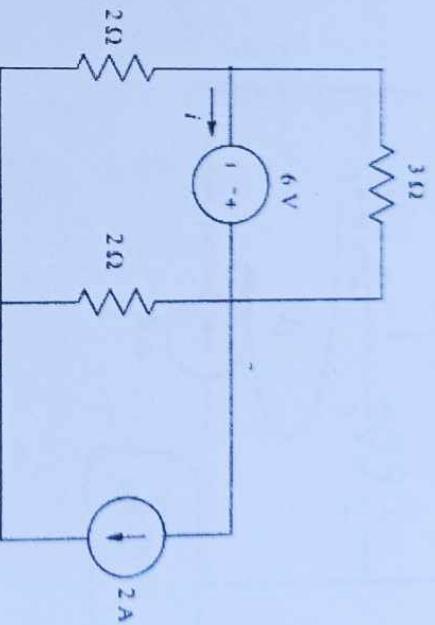

Req = 0.75 Ω

$$I' = \frac{V}{R} = \frac{6}{0.75} = 8 \text{ A}$$


$$I'' = \infty, R = 0$$

Question #	Q1 (8)	Q2 (3)	Q3 (5)	Q4 (8)	Q5 (6)	Q6 (8)	Q7 (5)	Q8 (7)
Grade:	6	9	5	8	2	8	5	5

Show Your CalculationsQuestion # 1 (8 points)

For the circuit shown below, use voltage and current dividers to calculate

a.	the voltage v_1 .	$v_1 =$	24 v	V
b.	the voltage v_2 .	$v_2 =$	6 v	V
c.	the voltage v_3 .	$v_3 =$	6 v	V
d.	the current i_1 .	$i_1 =$	3 A	A
e.	the current i_2 .	$i_2 =$	2 A	A
f.	the current i_3 .	$i_3 =$	1 A	A

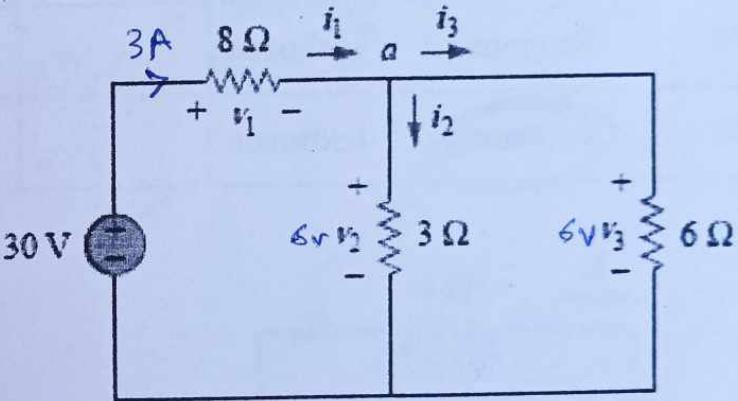

$$V = IR$$

$$30 \text{ V} \parallel 10 \Omega \quad I_{\text{total}} = 3 \text{ A}$$

$$V_1 = 24 \text{ V}$$

$$V_3 = V_2 = 6 \text{ V}$$

$$i_2 = 2 \text{ A}, i_3 = 1 \text{ A}$$

Question 2 (3 points)

Find R_{eq} for the circuit shown below.

$$R_{eq} = \boxed{5} \text{ k}\Omega$$

Show Your Calculations



(S)

$$\begin{aligned} &\text{Series } 3 + 3 = 6 \cancel{\text{k}\Omega} \\ &\text{Parallel } \frac{1}{6} + \frac{1}{6} = 3 \cancel{\text{k}\Omega} \\ &\text{Series } 3 + 2 = 5 \text{k}\Omega \end{aligned}$$



Question 3 (5 points)

For the circuit shown below, find

a. the current I .	$I =$	-0.2 A	A
b. the power absorbed by the 4-Ω resistor.	$P_{4\Omega} =$	0.16 absorbed	W
c. the power absorbed by the 6-Ω resistor.	$P_{6\Omega} =$	0.24 absorbed	W
d. the power generated or absorbed by the 3-V voltage source.	$P_{3V} =$	0.6 absorbed	generated W
e. the power generated or absorbed by the 5-V voltage source.	$P_{5V} =$	-1 absorbed	generated W

$$(a) -3 + 4I + 5V + 6I = 0$$

$$I = -0.2 \text{ A}$$

$$(b) P_{6\Omega} = IV = I^2 R = (-0.2)^2 4$$

$$= 0.16 \text{ watt}$$

$$(c) P_{6\Omega} = I^2 R = (-0.2)^2 (6) = 0.24 \text{ watt}$$

$$(d) P_{3V} = IV = -(-0.2) 3 = 0.6 \text{ watt}$$

$$(e) P_{5V} = IV = -0.2 \times 5 = -1 \text{ watt}$$