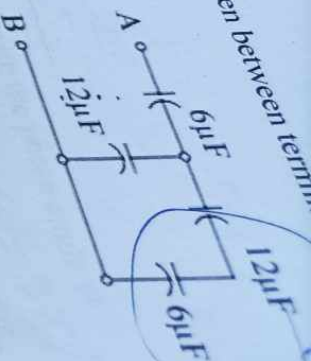


Question # 2 (10 points)

a. For the circuit shown below, find the equivalent capacitance C_{eq} seen between terminals



Series: $\frac{1}{6\mu F} + \frac{1}{12\mu F} \rightarrow 4\mu F$

Parallel: $(12 + 4)\mu F = 16\mu F$

Series: $(\frac{1}{18\mu F} + \frac{1}{6\mu F}) \rightarrow$

$4.36\mu F$

$C_{eq} = 20\mu F$


b. For the circuit shown below, determine C_x if the equivalent capacitance is $20\mu F$.

Series: $(10 + 40)\mu F = 50\mu F$

~~$\frac{1}{50\mu F} + \frac{1}{C_x} = \frac{1}{20\mu F}$~~

Series: $\frac{1}{40} + \frac{1}{10} \rightarrow 8$

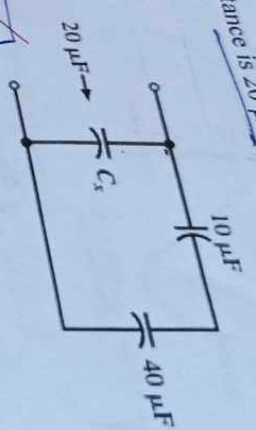
Parallel: $C_x + 8 \div 20 \rightarrow C_x = 12\mu F$





Parallel: $(\frac{1}{20} + \frac{1}{8})^{-1} \rightarrow 6H$

Series: $L_T = 6 + 14 = 20H$

✓ 2

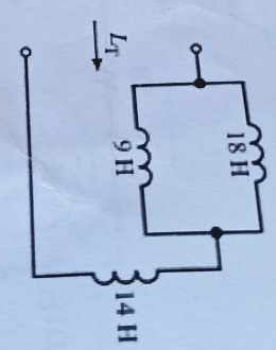

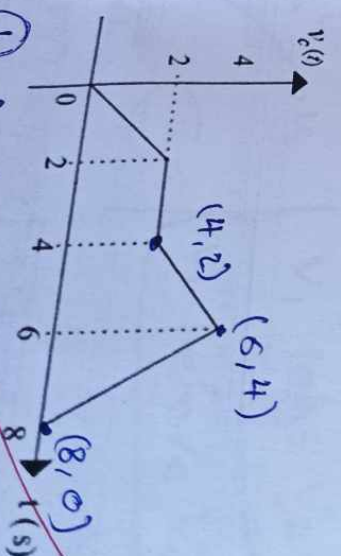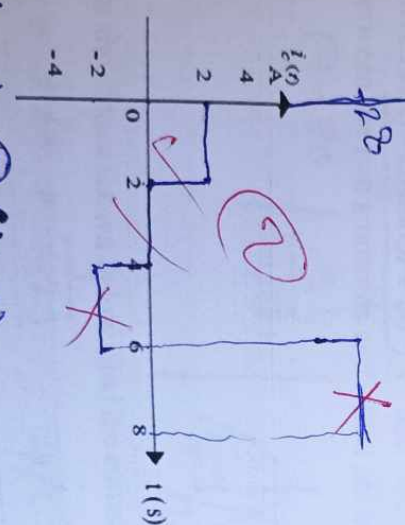d. If the voltage across a $2F$ capacitor is shown below, draw the waveform for the capacitor current $i_c(t)$.



(6-8)
 $m = \frac{0-4}{8-6} = \frac{-4}{2} = -2$
 $y = -2(x-8)$
 $y = -2x + 16$
 $y = -2 + 16 = 14$
 $i_c(t) = 2 \times 14 = 28$

(4-6)s
 $m = \frac{4-2}{6-4} = \frac{2}{2} = 1$
 $y - 2 = 1(x-4)$
 $y = x - 4 + 2 = x - 2$
 $y' = -1$
 $i_c(t) = 2 \times -1 = -2A$


(2) For (2-4)s
 $i_c(t) = 2 \times 1 = 2A$
 $m = 0$
 $y = 2 \rightarrow y' = 0$
 $i_c(t) = 0A$

$\frac{2-0}{2-0}$


Question # 5 (8 points)

For the circuit shown below, find

b.	the voltage phasor of the voltage source.	$V_s =$	50∠0	V
a.	the impedance of the inductor and capacitor,	$Z_L =$	12j	Ω
		$Z_C =$	-j/16	Ω
b.	the current phasor and current sinusoid flowing through the 1/12-F capacitor in polar.	$I =$		A
		$i(t) =$		A
b.	the voltage phasor and voltage sinusoid across the 3-H inductor.	$V =$		V
		$v(t) =$		V

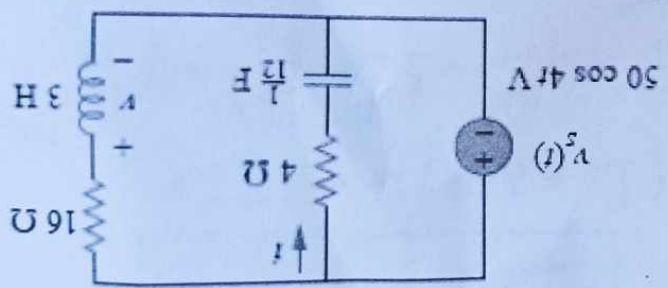


$Z_L = 12j$
 $Z_C = -j/16$
 $Z_{C||R} = -j/16 = 0.33$

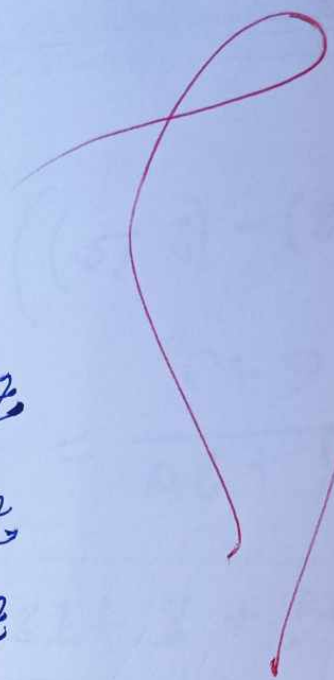

Question # 6 (5 points)

For the circuit shown below, use mesh current analysis to find:

a.	the mesh currents I_1 and I_2 .	$I_1 =$	$3.35 + 0.12j$ A
		$I_2 =$	$2 \angle 0$ A
b.	the voltage V_o across the $4\text{-}\Omega$ resistor.	$V_o =$	5.88 V

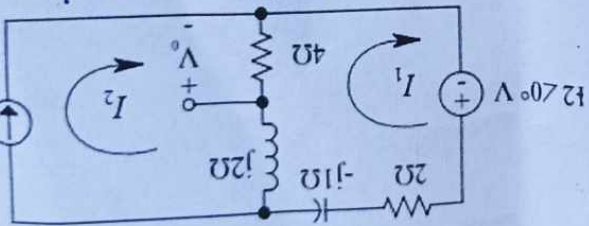

$$I_1: 2I_1 - 1jI_1 + (I_1 - 2\angle 0)2j + (I_1 - 2\angle 0)4 = 12\angle 0$$

$$2I_1 - 1jI_1 + 2jI_1 + 2\angle 0 + 4I_1 - 4\angle 0 - 0.7\angle 0 \times 4 - 12\angle 0 = 0$$

$$6 + jI_1 = 4j + 8 + 12$$

$$I_1 = \frac{6 + j}{4j + 20} = 3.35 + 0.12j$$

$$\left[(3.35 + 0.12j) \times 4 - 12\angle 0 \right] \times 4 = 5.88 = V_o$$

4.5


Question # 3 (15 points)

a. In a linear circuit, if the voltage source is $v_s(t) = 12 \sin(314t + 30^\circ)$ V, find the frequency f and the period T of the voltage waveform.

~~$\omega = 314 \text{ rad/s} \approx 2\pi f$~~
 $f = 49.97 \approx 50 \text{ Hz}$
 $T = \frac{1}{f} = \frac{1}{50}$

$v_s(t) = 12 \cos(314t + 30 - 90)$
 $\omega = 314 \text{ rad/s}$
 $f = 50 \text{ Hz}$
 $T = 0.02 \text{ s}$

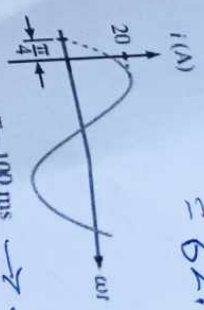b. Write the equation of the sinusoidal current waveform shown below with the phase angle θ expressed in degrees.



$20 \cos(62.836t + 45^\circ)$


$\omega = 2\pi f$
 $= 62.83$

$f = \frac{1}{T} = \frac{1}{100 \times 10^{-3}} = 10 \text{ Hz}$

c. Obtain the sinusoidal waveforms corresponding to each of the following phasors:


- i. $\bar{V}_1 = 60 \angle 15^\circ \text{ V}, \omega = 10 \text{ rad/s} \rightarrow v_1 = 60 \cos(10t + 15^\circ)$
- ii. $\bar{V}_2 = 6 + j8 \text{ V}, \omega = 40 \text{ rad/sec} \rightarrow v_2 = 10 \cos(40t + 53.13^\circ)$

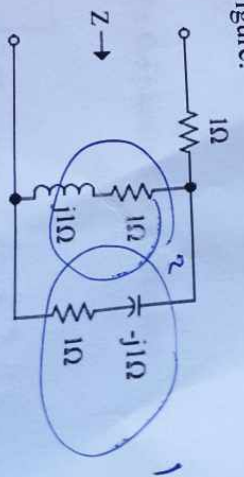d. Find the frequency domain impedance Z shown in the following figure.




Series $Z = 1 + j\omega L$
 Parallel $Z = \frac{1}{\frac{1}{2} + \frac{1}{1+j}} = Z = 1 \angle 90^\circ$
 $Z_{eq} = 1 + 1 = 2 \angle 90^\circ$

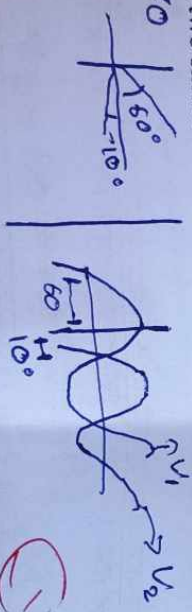e. Given $v_1(t) = 20 \sin(\omega t + 60^\circ)$ V and $v_2(t) = 60 \cos(\omega t - 10^\circ)$, determine the phase angle θ between the two sinusoids and which one lags the other.



v_1 lags v_2 by 90°
 v_1 before v_2

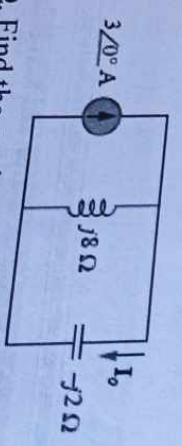f. For the circuit shown below, find the current phasor I_o .



$I = \frac{30 \angle 0 \times \frac{1}{-2j}}{\frac{1}{-2j} + \frac{1}{8j}} = 4 \text{ A}$

g. A series RLC circuit has $R = 30 \Omega$, $X_C = 50 \Omega$, and $X_L = 90 \Omega$. Find the equivalent impedance Z_{eq} of the circuit.


$Z_{eq} = 30 + j90 - j50 = 30 + 40j \Omega$

Question # 4 (7 points)

I. For the circuit shown below, if the voltage source voltage $E = 100 \angle 0^\circ$ V, find


a.	the impedance seen by the source in rectangular and polar form.	$Z =$	$3 + 4j$	Ω
b.	the current phasor supplied by the source.	$I =$	$20 \angle -53.13$	A
c.	the voltage across the 3- Ω resistor R and V_R across the 4- Ω reactor X_L .	$V_R =$	$60 \angle -53.13$	V
		$V_L =$	$80 \angle 36.87$	V

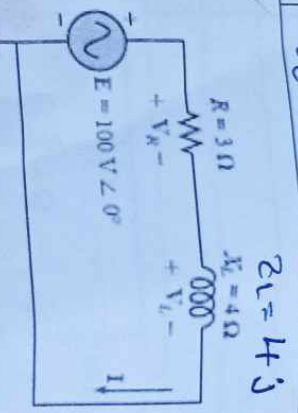$Z_{eq} = 3 + 4j$
 $I = \frac{100 \angle 0^\circ}{3 + 4j} = \frac{100 \angle 0^\circ}{5 \angle 53.13}$
 $= 20 \angle -53.13$ A




$V_R = I R = 20 \angle -53.13 \times 3 = 60 \angle -53.13$ V
 $V_L = I X_L = 20 \angle -53.13 \times 4j = 80 \angle 36.87$ V

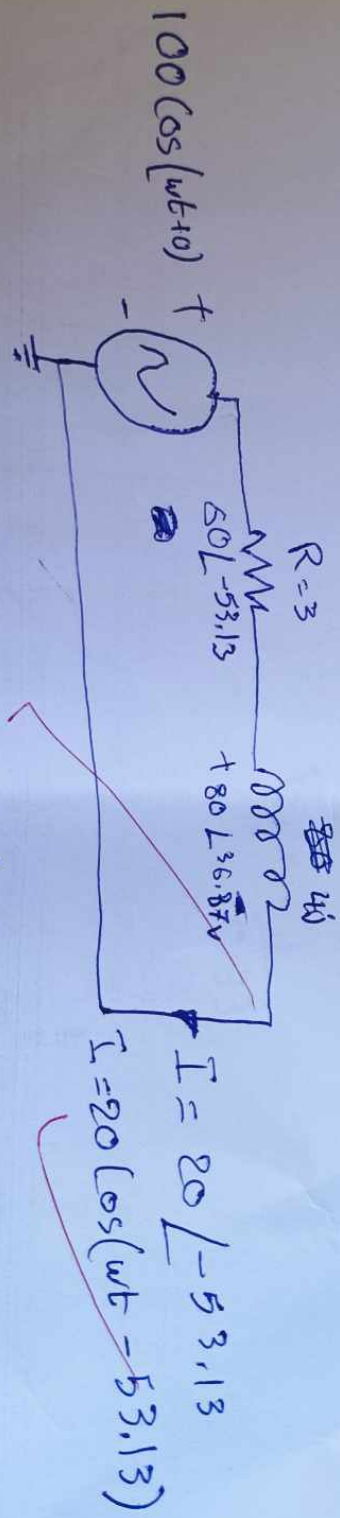II. Draw the phasor diagram showing the phasors E , I , V_R and V_L . Take the phasor E as a reference.



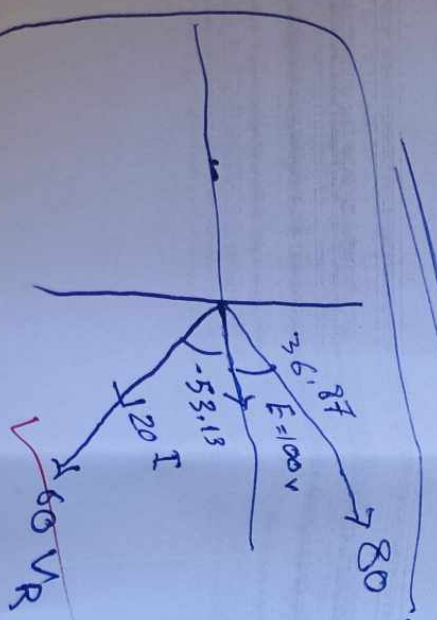$V_R = 60 \cos(\omega t - 53.13)$
 $V_L = 80 \cos(\omega t + 36.87)$




Question #	Q1 (5)	Q2 (10)	Q3 (15)	Q4 (7)	Q5 (8)	Q6 (5)	Grade
Grade:	0	8	13	7	2	4.5	34.5/50

Question # 1 (5 points)

Find the energy stored in each capacitor and inductor, under steady-state conditions, in the circuit shown below.

$$E = \frac{1}{2} C V^2$$
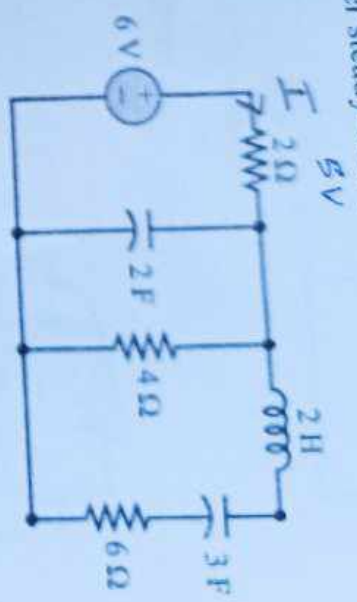
$$2F \rightarrow \frac{1}{2} \times 2 \times (1)^2 = 1 \text{ Joule}$$



~~$$V = \frac{6 \times 2}{2 + 4} = 5V$$~~

