



* **Experiment 1** Measurement Devices

Bread board are usually limited to low frequencies (less than 10 MHz)


Fine → knob that is used for more accurate values with smaller steps

⊕ high voltage terminal ⊖ low voltage terminal

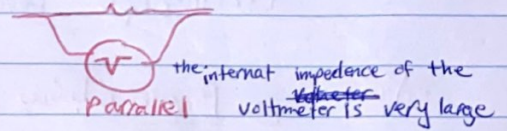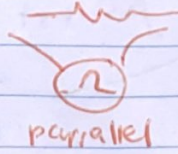DC → Average value measurement
AC → rms value measurement



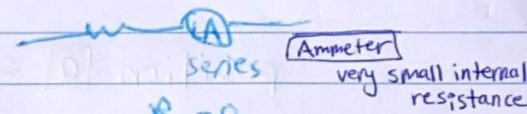$R \rightarrow \infty$
so $I = 0$ going through the voltmeter



$R = 0$
so $V = 0$

* **Experiment 3** Network Theorems

Voltage source → short circuit (Kill)
current source → open circuit (Kill)

$\sum P = 0$

power consumed = power generated


Power (P)

$$P = IV$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

consumed ⊕
generated ⊖

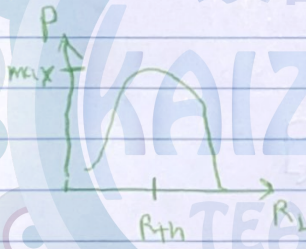

power is not linear
Superposition لا يجزأ
position.

Mesh/nodal → are usually for individual solutions
However superposition → is used to deal with linear circuits that have multiple independent sources

Sinusoidal signals

* **Function Generator** (Experiment 4)

Shape → sin shape
Rectangular
triangular (sawtooth)

output
coaxial cable → (twist)
BC connector
crocodile ← Red ⊕
Black ⊖

Amplitude (Ampl) → V_{pp} (نظر)
peak to peak
Knob غير متحركة

في Function Generator
بقدر اعبر
Amplitude
Frequency

* الكسارة بتعطيني الخطوات من frequency
1 Hz

1M 100K 10K 1K 100 10 1

5M Knop يتحرك خيس دركات من كل شغلة


maximum

Inductor \rightarrow

Capacitor \rightarrow

Oscilloscope Device
AC part
can measure the instantaneous values of a sinusoidal signal as well as its peak, rms, and peak to peak values
it displays ~~single~~ signals (waveforms) that are functions of time
كل زوج اسول Division

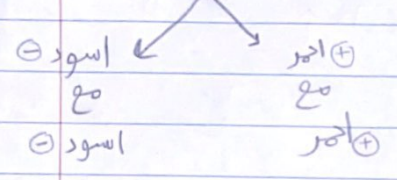كل الكبيسات
مجرد توضيح للإشارة
Scale zoom
* لازم ينشيك Parallel مع اي إشارة



Ch1 Ch2

Horizontal 10
vertical 8

• $\rightarrow 0.2$

position 0 zero

frequency \propto number of cycles
فردى

* نقصر ال Amplitude للزيادة
بطول الهمزة لفرق

بعد عدد الكريجات من Peak to peak

amplitude knob \uparrow $V_p \uparrow$
فردى

period
(الوقت اللازم لتمام دورة)

4 كريجات مثلا
Scale 0.5
 $v = 4 \times 0.5 = 2V$

改善 V_{PP}

DC coupling

Capacitor (PF) يكون بوحدة (PF)

it have two frequencies
120
1K
Measure RLC meter component meter

1st Digit
2nd Digit
Multiplier
Tolerance
Voltage

Digital multimeter
AC يكس
I RMS

inductor } M F
+ has a small internal resistance

اذا كست DC بار AC يكون بي
Average
DC \rightarrow I average

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

لما ازيد ال Amplitude تزيد الإشارة ولها نقص ال Amplitude
بقل الإشارة (الهدنة)

لما ازيد ال Frequency تزيد عدد ال cycles

Resistance impedance variation
ماليها


Experiment (1)

$V = IR$ Ohm's Law

$R_{series} = R_1 + R_2 + R_3 \dots$

For two resistors $\rightarrow R_{parallel} = \frac{R_1 \times R_2}{R_1 + R_2}$

Voltage Division

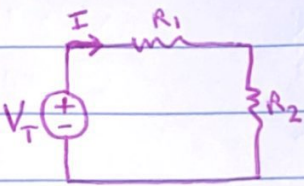


$I = \frac{V_T}{R_1 + R_2}$

$V_1 = V_T \times \frac{R_1}{R_1 + R_2}$


$V_2 = V_T \times \frac{R_2}{R_1 + R_2}$

Current Divider

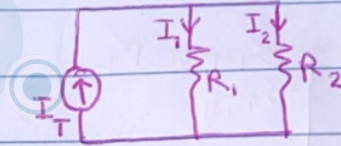

$I_1 = \frac{I_T \times R_2}{R_1 + R_2}$

$I_2 = \frac{I_T \times R_1}{R_1 + R_2}$

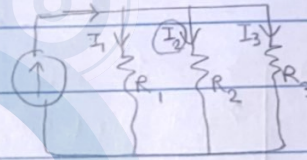

$I_2 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \times I_{Total}$

Experiment (2)

in DC \rightarrow capacitor \rightarrow (open circuit)

in DC \rightarrow inductor \rightarrow (short circuit)


Nodal Analysis $\sum I_{in} = \sum I_{out}$

Number of equations = Number of Nodes


- (1) خطوات الحل
- (2) active node و reference node
- (3) إيجاد التيار في كل مقاومة
- (4) KCL

Mesh Analysis

$\sum V = 0$ for each loop

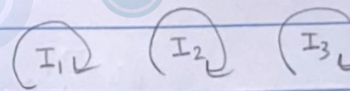

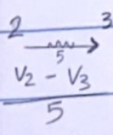بفرض التيار تبع ال mesh
ياي يشتغل فيها هو الأكبر
و بطرفه من الثاني



Experiment (3)

superposition Kill all sources except one
Kill one source and keep the other

$$I = \tilde{I} + \overset{\hat{~}}{I}$$


$$V = \tilde{V} + \overset{\hat{~}}{V}$$

$P \neq \tilde{P} + \overset{\hat{~}}{P}$ → because it is not linear

$V_{th} = V_{oc}$

V_{th} thevenin

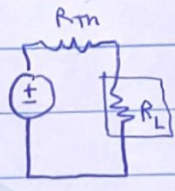- remove R_L
- Leave it open
- Find V_{th}



$P = IV$

$P = I^2 R$

$P = \frac{V^2}{R}$

⊕ Consumed
⊖ generated

$R_{th} = R_{ab}$

R_{th} thevenin

- remove R_L
- Kill all sources
- Find R_{th}

$I_N = I_{sc}$


I_N Norton

- remove R_L
- Put short circuit
- Find I_N




for maximum power

$R_L = R_{th}$

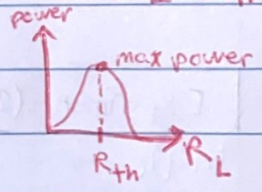

Experiment (4)


Capacitor

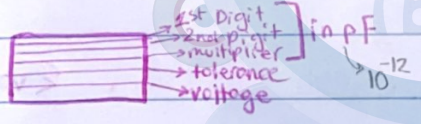

$\omega = 2\pi f = \frac{2\pi}{T}$

Scale (Time per Division) → Horizontal controls
position

Inductor

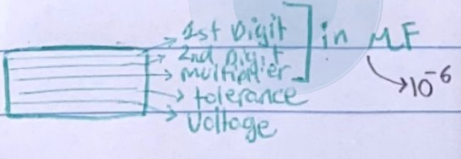

Scale (Volt per Division) → Vertical controls
position

Coil choke resists changes in electric current (it have a small internal resistance)

* $V_{peak\ to\ peak} = 2V_p$

* Root mean Squared → $V_{rms} = \frac{V_p}{\sqrt{2}}$

* Frequency → $f = \frac{1}{T}$ Hz

frequency f (Hz)
 عتمة التردد

Experiment (5)

Capacitive Reactance

(R-C) circuits $\begin{cases} \text{series} \\ \text{parallel} \end{cases}$


PF Lead

in (R-C) I_s leads V_s by θ

$V_s = V_p$
 source peak

RC circuit


Series

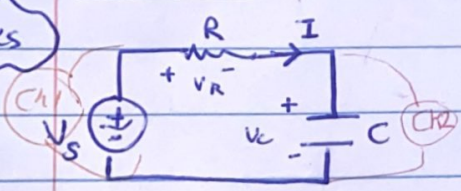


نقط
 Ch ① supply
 Ch ② output on Capacitor

تفتقرن ال
 supply هو ال reference

phasor diagram

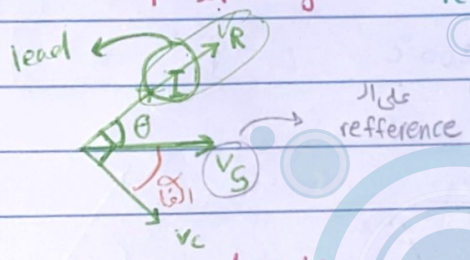

Time domain

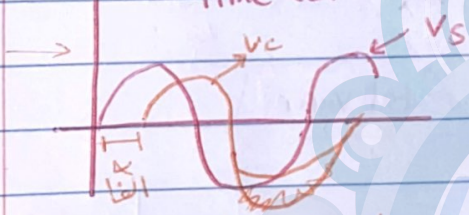

V_s lead V_C by α
 V_C lag V_s

Ch 1 lead supply
 Ch 2 Capacitor

Ohms law
 $V = IR$

Equations


Total current $I = \frac{V_R}{R} = |I| \angle I$

Capacitor impedance $X_C = \frac{|V_C|}{|I|}$


Total impedance magnitude $|Z| = \frac{|V_S|}{|I|}$

Total impedance phase $\angle Z = \angle V_S - \angle I$



Parallel

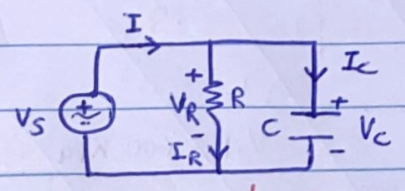

phasor diagram

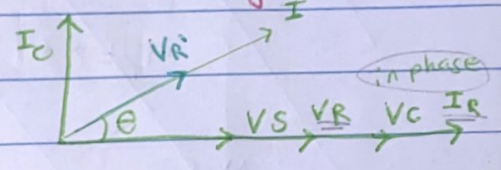

Time domain

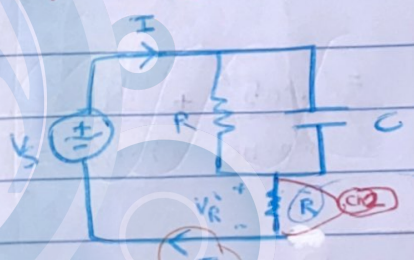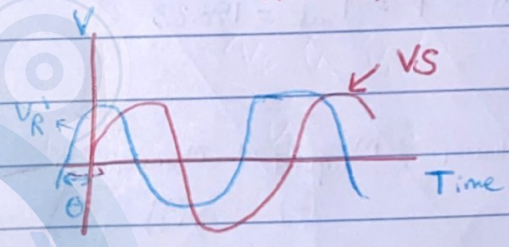

مكان اتوصف التيار
 كلوا اوسilloscope
 بخص R وبتحليل
 عالتيوار
 10-ohm
 very small Resistor

Equations

$I = \frac{V_R}{R}$

$V_R = V_S - V_C = V_C$

$I_R = \frac{V_R}{R}$

$I_C = I - I_R$

I and $V_R \rightarrow$ in phase

لكن هو نفس ال
 Amplitude

$B_C = \frac{|I_C|}{|V_C|}$

$|Y| = \frac{|I|}{|V_S|}$

$\angle Y = \angle I - \angle V_S$

Power and Power factor

$S \rightarrow$ average complex power (VA)

$P \rightarrow$ average real power (W)

$Q \rightarrow$ average reactive power (VAR)

Average complex power (V.A) \rightarrow

$$S = P + jQ = V_{rms} I_{rms} \angle(\angle V - \angle I) = \frac{1}{2} V_p I_p \angle(\angle V - \angle I)$$

Average Real Power (W) \rightarrow

$$P = V_{rms} I_{rms} \cos(\angle V - \angle I) = \frac{1}{2} V_p I_p \cos(\angle V - \angle I)$$

Average Reactive Power (VAR) \rightarrow

$$Q = V_{rms} I_{rms} \sin(\angle V - \angle I) = \frac{1}{2} V_p I_p \sin(\angle V - \angle I)$$

Apparent Power \rightarrow

$$|S| = V_{rms} I_{rms} = \frac{1}{2} V_p I_p$$

$$PF = \cos(\angle V - \angle I)$$

\rightarrow which is (Lead) for capacitive Loads

$X_L \propto \text{Frequency}$
 فري

*Experiment (6) Inductive Reactance





in (R-L) V_s lead I_s always

(R-L) circuit \rightarrow series
 \rightarrow parallel



\rightarrow P.F \rightarrow Lag

Series

Parallel

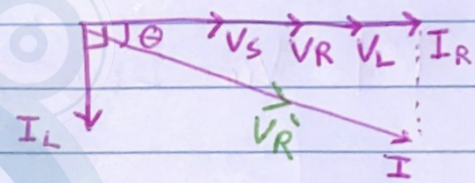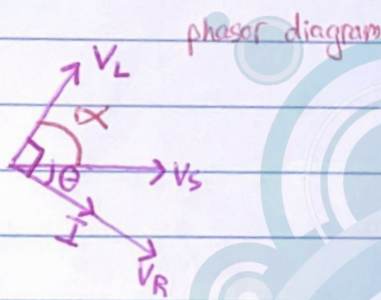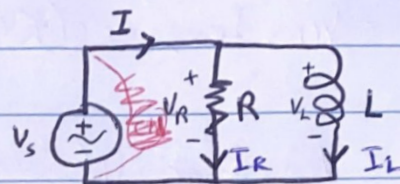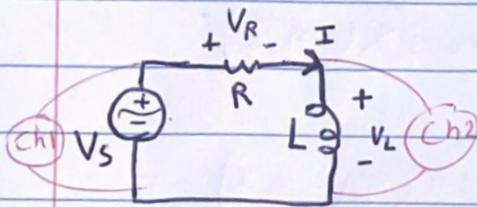

time domain

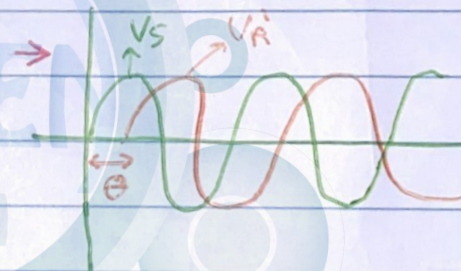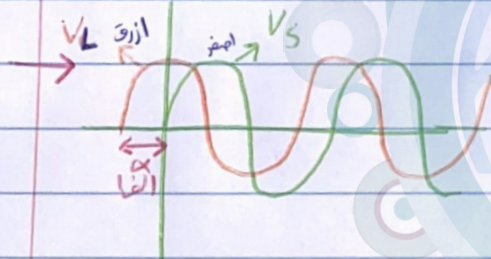

V_s lead V_R
 V_R lag V_s

Equations

$$I = \frac{V_R}{R} = |I| \angle I$$

$$X_L = \frac{|V_L|}{|I|}$$

$$Z = \frac{|V_s|}{|I|}$$

$$\angle Z = \angle V_s - \angle I$$

Equations

$$I = \frac{V_R}{R} = |I| \angle I$$

$$V_R = V_s - V_L = V_L \angle \theta \angle V_R$$

$$I_R = \frac{V_R}{R} = |I_R| \angle I_R$$

$$I_L = I - I_R = |I_L| \angle I_L$$


$$B_L = \frac{|I_L|}{|V_L|}$$

$$Y = \frac{|I|}{|V_s|}$$

$$\angle Y = \angle I - \angle V_s$$

oscilloscope shows voltage related to time

y \rightarrow voltage

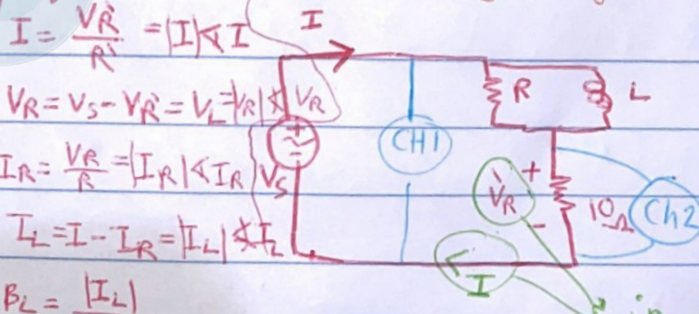

$$I = \frac{V_R}{10 \Omega}$$

in phase

$R = 10 \Omega$ phase shift
 very small Resistor
 اینس بہی کم ال

عنوان اختیار بالجهاز

Power and Power Factor

Average complex power (V.A) ← $S = P + jQ = V_{rms} I_{rms} \angle (\phi_V - \phi_I) = \frac{1}{2} V_p I_p \angle (\phi_V - \phi_I)$

Real power (W) ← $P = V_{rms} I_{rms} \cos(\phi_V - \phi_I) = \frac{1}{2} V_p I_p \cos(\phi_V - \phi_I)$

Reactive power (VAR) ← $Q = V_{rms} I_{rms} \sin(\phi_V - \phi_I) = \frac{1}{2} V_p I_p \sin(\phi_V - \phi_I)$



Power Factor ← $PF = \cos(\phi_V - \phi_I)$ it is lagging in inductive loads

Apparent Power ← $|S| = V_{rms} I_{rms} = \frac{1}{2} V_p I_p$

Experiment (7) Diode Applications



\oplus موجب اهر
 \ominus سلكة اسود

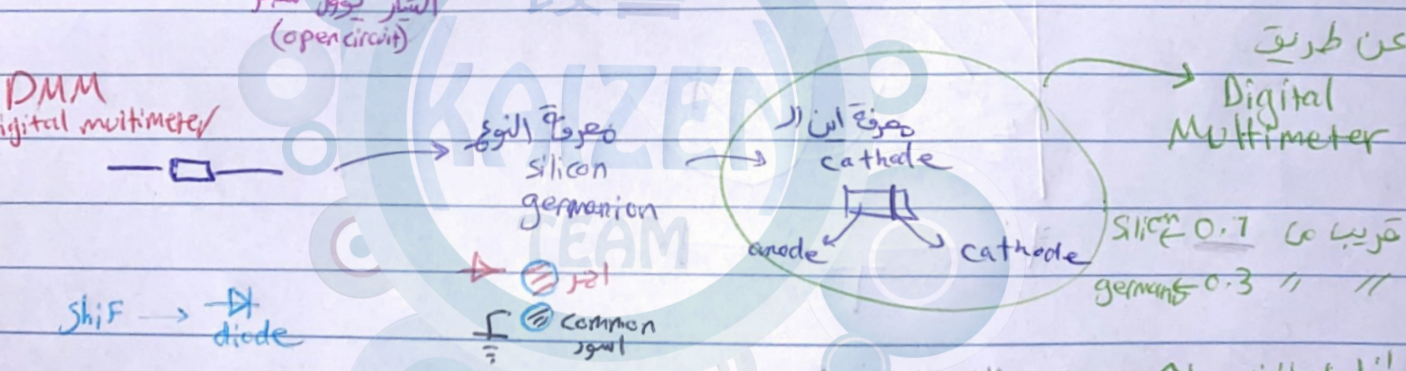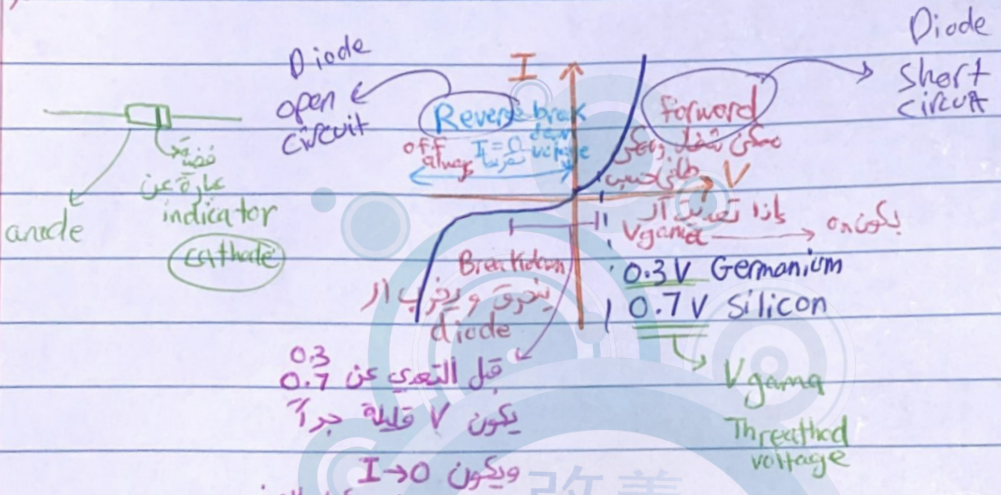


اذا اسطاني -OL- مثلا طلعت 0.5
 يكون overload يعني Reversed biased circuit
 اذا تعدينا فابنكن forward

in Reversed
 $V_{diode} \rightarrow (-)$ minuse

diode off
 open circuit

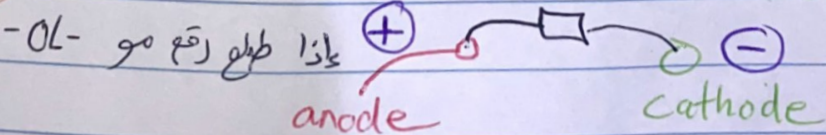$V_{diode} = V_{Supply}$
 forward \rightarrow on
 off




8

$$V_{dc} = \frac{V_{peak}}{\pi}$$

time constant $\tau = R \times C$

$$T = \frac{1}{f}$$

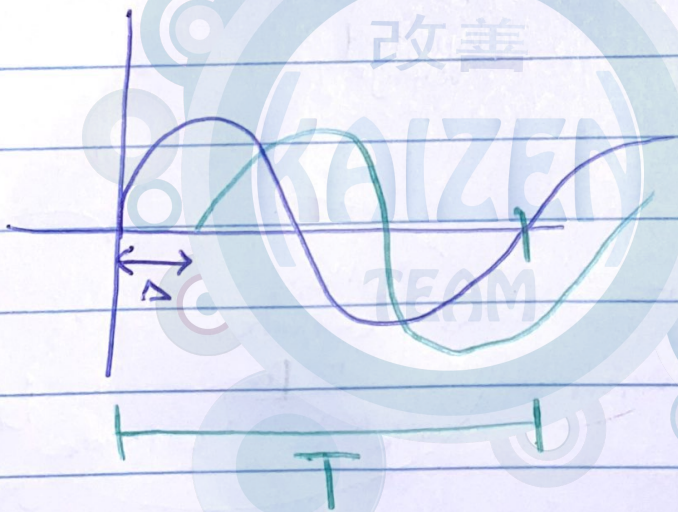

$$\theta = \frac{\Delta(\text{Div}) \times 360^\circ}{T(\text{Div})}$$