

Experiment 1:

Breadboards have low frequencies less than 10 MHz.

DC power supply (constant voltage)
direct-current

(+) High voltage terminal

(-) Low voltage terminal.

* Series and parallel resistors :- (theoretical).

$$\textcircled{A} R_{\text{series}} = R_1 + R_2 + R_n \dots, \quad R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_n} \dots}$$

$$\textcircled{B} V = V_1 + V_2 + \dots, \quad V = V_1 = V_2 = V_n$$

$$\textcircled{C} I = I_1 = I_2 \dots, \quad I = I_1 + I_2 + I_3$$

$$\textcircled{D} R = \frac{V}{I}$$

$$\textcircled{E} \text{Voltage division rule: (series)} \quad V_{R_k} = \frac{V_s \times R_k}{R_{\text{tot}} \text{ (series)}}$$

$$\textcircled{F} \text{Current division rule: (parallel)} \quad I_{R_k} = \frac{V_s \text{ (parallel)}}{R_k}$$


Experiment 2

Perim

inductors are considered "short circuits" in DC circuits


capacitors are considered "open circuits" in DC circuits.

Nodal analysis: KCL. current source

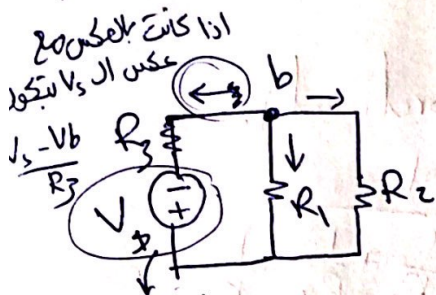

$$\frac{V_b + V_s}{R_3} + \frac{V_b}{R_1} + \frac{V_b}{R_2} = 0.$$

Mesh analysis: KVL. voltage source

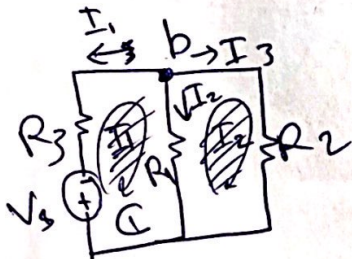

$$-V_s - I_2 R_1 + I_1 R_1 + I_1 R_3 = 0.$$

deviation means: error

$$\frac{\text{theory} - \text{measured}}{\text{theory}} \times 100\%$$

Experiment 3:

Superposition:

If a circuit has more than one voltage / current source, we can calculate what each voltage / current source gives from I , V summing them up for each resistance.

alone

$$I_1 = I_s + I_D$$

$$V_1 = V_s + V_D$$

However, power (p) does not abide by this.



Thevenin-Norton:

V_{Th} is measured by putting a voltmeter in an open circuit (instead of R_{load}).

I_N is measured by putting a jumper in an ~~open~~ circuit to make it short and putting an ammeter in this short circuit.

R_{Th} we kill all sources and put jumpers instead and we measure R_{tot} using ohmmeter from same spot as before.

R_{Th} is also $\frac{V_{Th}}{I_N}$

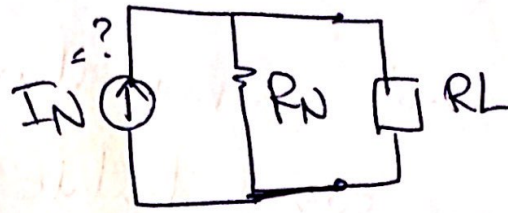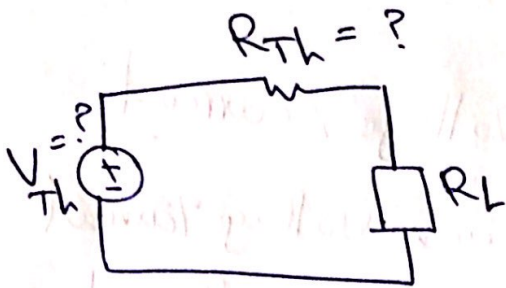


Max Power transfer: $P = \frac{V^2}{R}$

max power is at R_{Th}

(a wiper and outer terminal)

Use a potentiometer as a rheostat for changing the resistance and testing at what resistance is max power at R_L (the same spot), measure

voltage for this rheostat at a certain resistance and see power, it will be at R_{Th} .

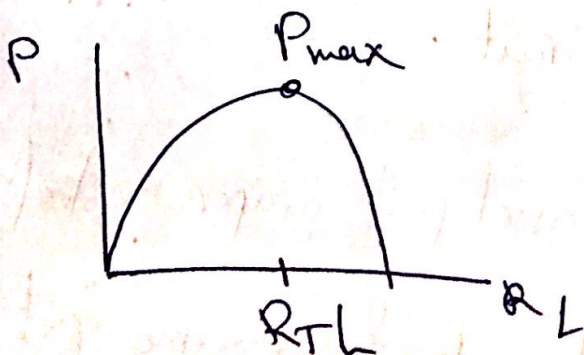

Experiment 4: Sinusoidal signals.

Amplitude: Peak V_p , maximum value in sinusoidal waveform.
voltage level.

② Oscilloscope و Functiongen. الى اليمين ، الى اليسار
من اليمين الى اليسار

From upper peak to lower (max to min)
(من القمة الى القاع)

③ V_{p-p} (peak to peak) voltage.

and we read voltage depending on that (taking into consideration scaling) on oscilloscope.

④ to read frequency we read period on oscilloscope,

by $\frac{\text{division}}{\text{zoom}} \times \text{delay}$,
(sec, Ms, ms)
time/div

then $f = \frac{1}{T}$

⑤ $V_{p-p} = 2V_p$

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

⑥ cycles are periods.


$$V_s(t) = V_p \sin(\omega t)$$
$$= V_p \sin(2\pi f t)$$

impedance of any component is in Ohm.

ω is angular velocity.
if $V_p = 5$ then $V_{pp} = 10$.

Experiment 5: Capacitive reactance.

① V_c with V_s lag
negative ϕ

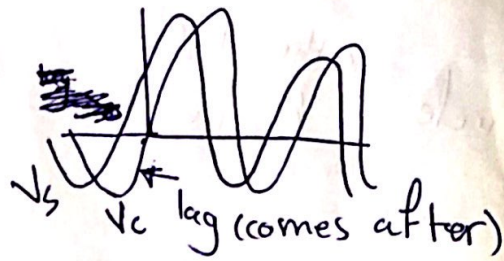


ϕ V_c with $V_s = \frac{\Delta(\text{div}) \times 360}{T(\text{div})}$ (negative)

$\Delta(\text{div})$: 2 waves (phase shift)
(او اللفظان)

$T(\text{div})$: Period (الفترة)

② To change $V_c \rightarrow V_R$ we change R and C places.

ϕ V_R with $V_s =$ same thing

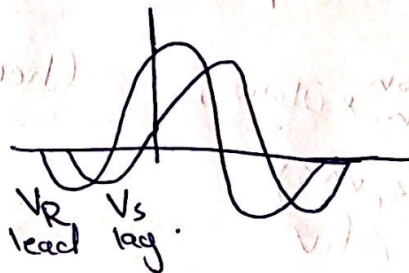

or $I = \frac{V_R}{R}$

③ X_c reactance (like resistance) = $\frac{|V_c|}{|I|}$
B Lms susceptance.

Parallel Part B is a different circuit, but you are going to do this all over again, remember that AC circuits are SO much like DC and we used a small 'R' to figure out $\frac{I}{V} = \frac{V}{R}$ because we can't do that on V_s


total impedance $Z = \frac{|V_s|}{|I|}$
Y Lms admittance.

or $Z = R - \frac{j}{\omega C}$

$\phi Z = \phi V_s - \phi I$ (deg°)

Experiment 6: Inductive reactance.

① V_L with V_{RS} lead positive. ϕ

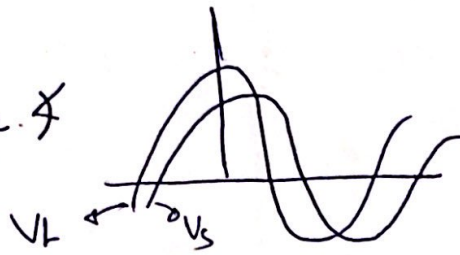

ϕ V_L with V_S = same thing.

② $V_L \rightarrow V_R$



* remember that $V_{pp} = 2V_p$

$$I = \frac{V_R}{R}$$

$$\textcircled{3} X_L = \frac{|V_L|}{|I|}$$

$$Z = \frac{(V_S)}{|I|} \text{ or } Z = R + j\omega L$$

$$\phi Z = \phi V_S - \phi I$$

complex power $S = \frac{1}{2} V_p I_p \phi (V - I)$

real power $P = \frac{1}{2} V_p I_p \cos (V - I)$

reactive power $Q = \frac{1}{2} V_p I_p \sin (V - I)$

power factor $PF = \cos (V - I)$

Bonuses:

* For a series RC circuit I leads V_s .

" " " RL = I lags V_s .


* admittance $Y = \frac{1}{Z}$ * $Y = \phi I - \phi V_s$.

* $\omega = \frac{2\pi}{T}$ or $2\pi f$

* Phasor diagrams:


RC

Series

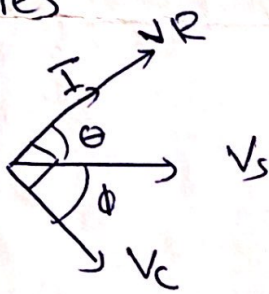


~~RL~~

Parallel

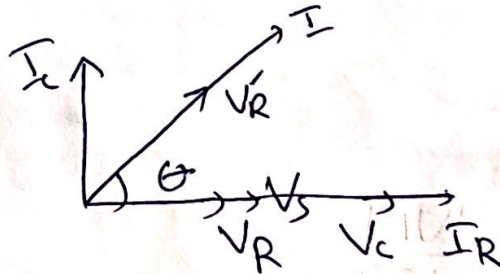

RL

Series

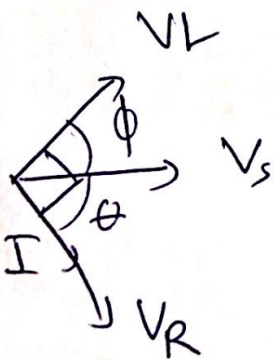

Parallel

