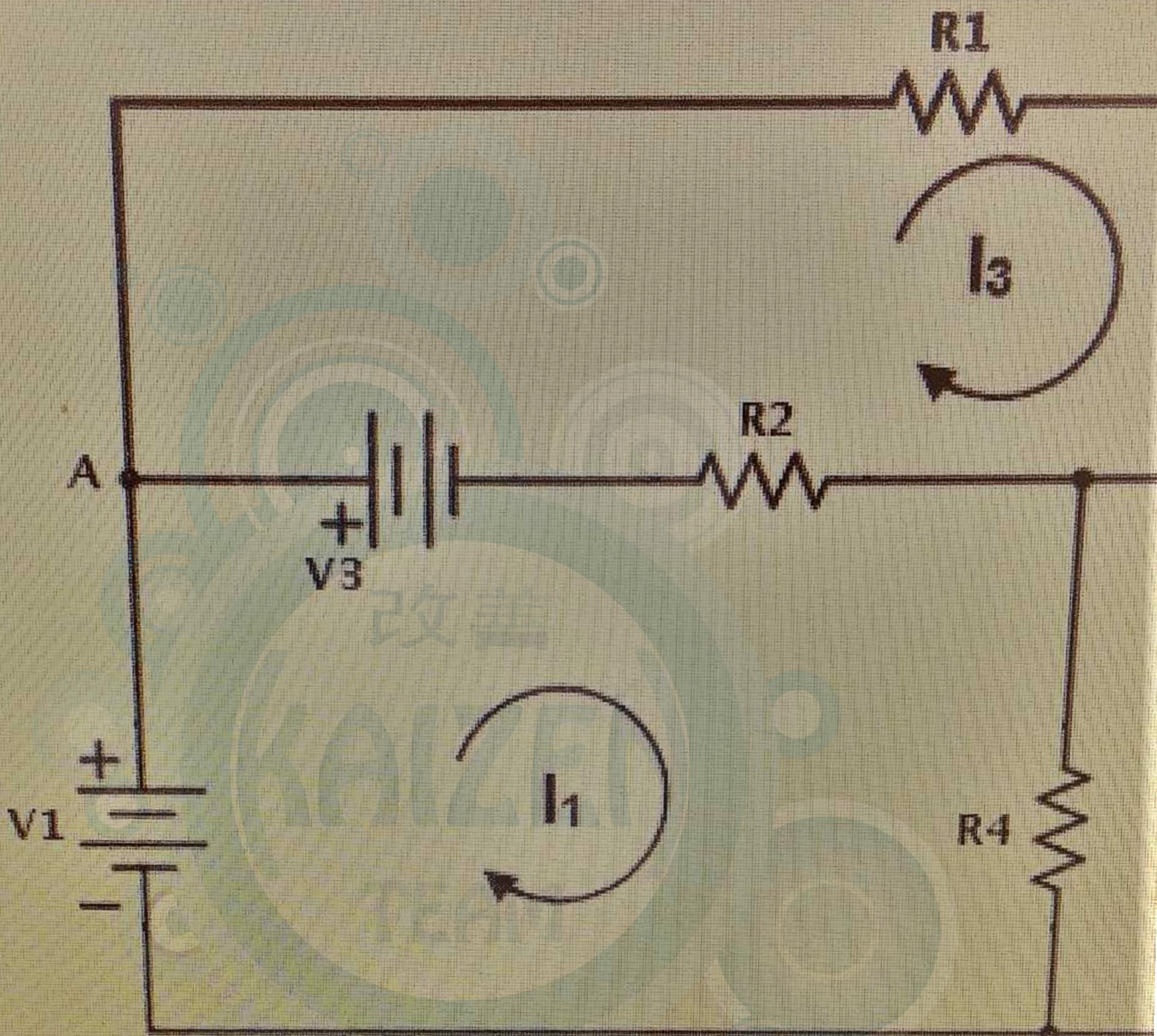


The correct mesh equation for current I₂ is: Eq

(1.5 Points)



$$-V_2 = I_2(R_3 + R_4) - (I_3)(R_3) - (I_1)(R_4)$$



$$V_1 - V_3 = I_1(R_2 + R_4) - (I_2)(R_4) - (I_3)(R_2)$$



$$V_3 = I_3(R_2 + R_3 + R_1) - (I_1)(R_2) - (I_2)(R_3)$$



$$V_2 = I_2(R_3 + R_4) - (I_3)(R_3) - (I_1)(R_4)$$

The peak to peak voltage (Vpp) for CH1 is approximately:
(1.5 Points)

- 1.6 volt
- 2.8 volt
- 7.6 volt
- 5.6 volt

19

The frequency for CH2 signal is:
(1.0 Points)


- 950 Hz
- 125 Hz
- 800 Hz
- 1250 Hz

13

In the oscilloscope, the volt/div knob controls:
(1.5 Points)

- The number of time for each vertical division on the screen.
- The number of time for each horizontal division on the screen.
- The number of volts for each vertical division on the screen.
- The number of volts for each horizontal division on the screen.

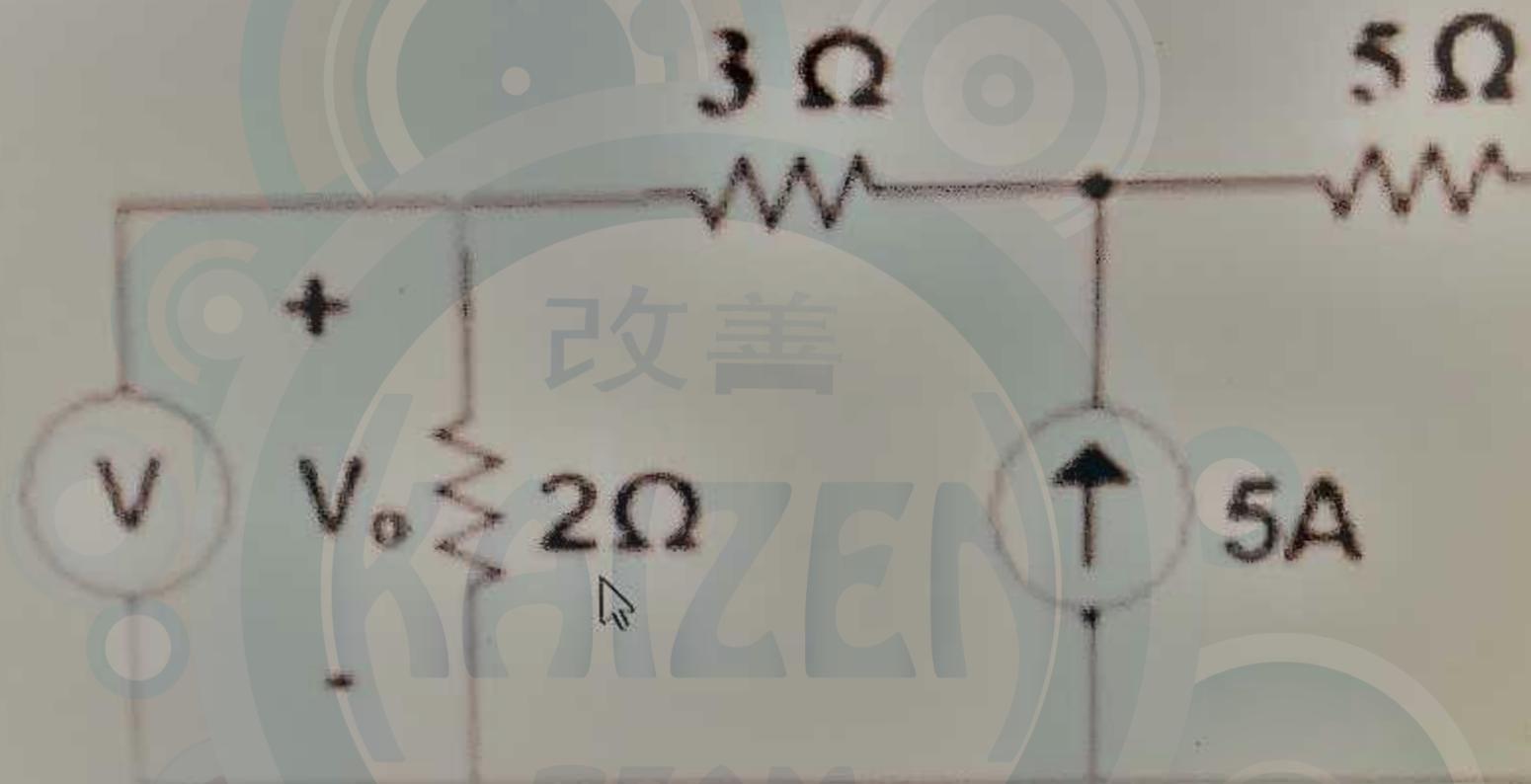For the circuit shown below, if a superposition theorem has been carried voltage V_o , then the effect of the current source on the voltage (V_o) can (1.5 Points)



Connecting a wire in parallel with the voltage source

Disconnecting the voltage source and replacing it by a short circuit

Disconnecting the current source

Disconnecting both the voltage source and the current source

The expected reading for the Ammeter A2 is approximately; 

(1.5 Points)

- 267.6 mA
- None of the above
- 26.7 mA
- 2.67 mA

16


The value of the voltage source Vs is approximately:


(1.5 Points)

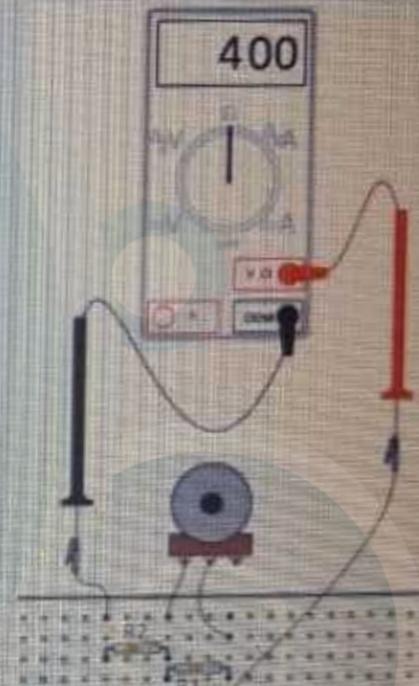- 22.7 volt
- None of the above
- 2.27 volt
- 227.6 volt

10


If $R_1 = R_2 = 250 \text{ ohm}$, then the potentiometer value will be: (1.5 Points)



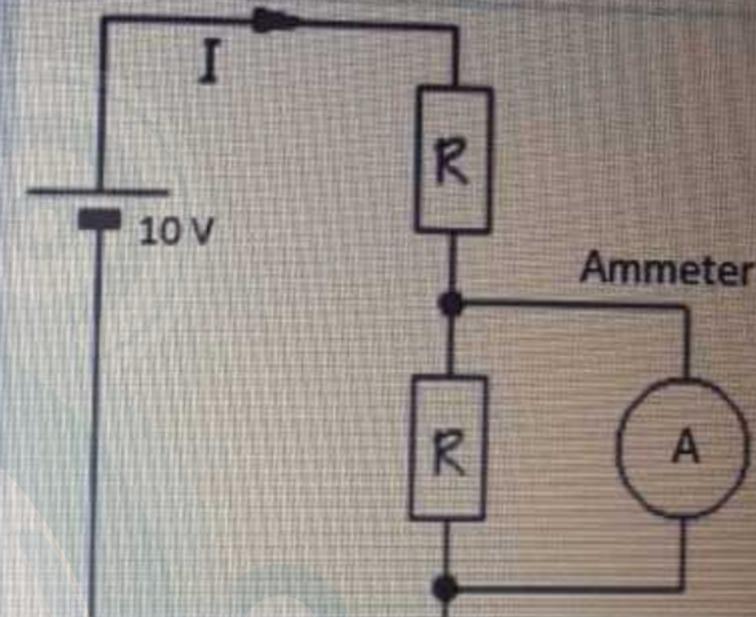


If $R=180$ ohm, then the Ammeter reading (in Ampere) is:
(1.5 Points)

0.055

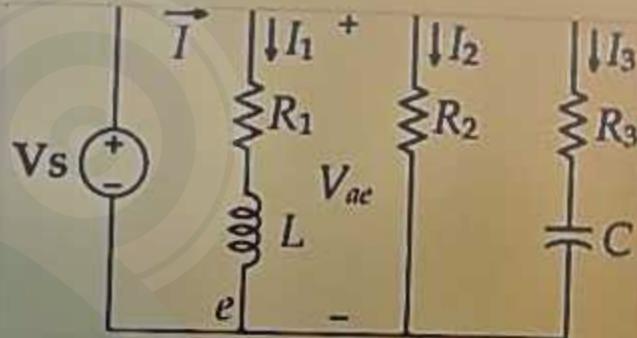

Replacing the capacitor (C) by an inductor in the following circuit, this will: □
 (1.5 Points)

- increase the value of the total current |
- make no changes to the current values |
- increase the value of the current I_2 |
- make the current I_3 equal to zero |
- decrease the value of the total current |

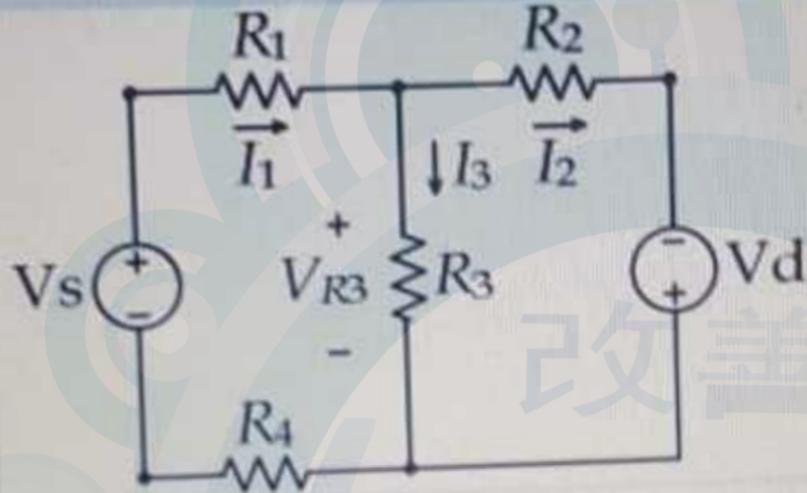


	Due to V_s only	Due to V_d only
I_1	8.19	4.49
I_2	2.62	-4.01
I_3	5.57	8.5

12

If $R_2 = 220$ ohm, then the value of the total absorbed power by it (in Watt) is:

425.063

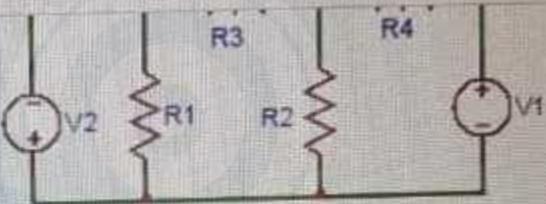

$$\frac{V_b}{R2} + \frac{V_b - V_1}{R4} + \boxed{} = 0$$


One of the student wrote the nodal equation at node b for the circuit shown, the missing term in the box is: (1.5 Points)

- $(V_b + V1) / R4$
- None of the above
- $V_b / R1$
- $(V_b - V2) / R3$
- $(V_b + V2) / R3$

(1.5 Points)

Black	0	Blue	6
Brown	1	Violet	7
Red	2	Grey	8
Orange	3	White	9
Yellow	4	Gold	$\pm 5\%$
Green	5	Silver	$\pm 10\%$

505.09

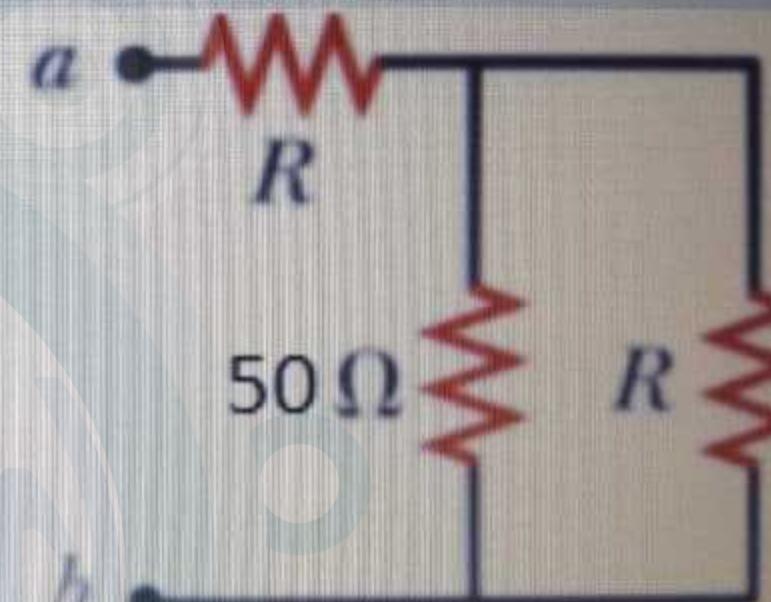

Back

Next

Page 2 of 2

15

IF the total absorbed power by the resistor R3 is 150 W, this mean than the power absorbed by R3 due to Vs only is 112 W and the power absorbed by R3 due to Vd only is 38 W.
(1.5 Points)

- True
- False

Back

Next

Page 6 of 9

14

IF $R_2 = 20 \text{ ohm}$, $R_3 = 20 \text{ ohm}$ and $R_4 = 10 \text{ ohm}$, then the value of the resistor R_1 for maximum power transfer is:
(2 Points)

160.8

15

IF the total absorbed power by the resistor R_3 is 150 W , this mean than the power absorbed by R_3 due to V_s only is 112 W and the power absorbed by R_3 due to V_d only is 38 W .
(1.5 Points)

• (2 Points)

425.062

13

If $R_3 = 60 \text{ ohm}$, then the voltage drop on it (in volt) is:
(1.5 Points)

844.2

14

IF $R_2 = 20 \text{ ohm}$, $R_3 = 20 \text{ ohm}$ and $R_4 = 10 \text{ ohm}$, then the value of the resistor R_1 for maximum power transfer is:
(2 Points)

To find the Norton resistor of a circuit, we had to open all the current sources and short all the voltage sources.

(1.5 Points)

True

False

[Back](#)

[Next](#)

16

Applying Thevenin's theorems to a circuit yields to:
(1.5 Points)

- equivalent current source and a resistor in series
- equivalent voltage source and a resistor in parallel
- equivalent voltage source and a resistor in series
- equivalent current source and a resistor in parallel


17

To find the Norton resistor of a circuit, we had to open all the current sources and short all the voltage sources. []
(1.5 Points)

Red
Red
Red
Silver

Black	0	Blue	6
Brown	1	Violet	7
Red	2	Grey	8
Orange	3	White	9
Yellow	4	Gold	±5%
Green	5	Silver	±10%

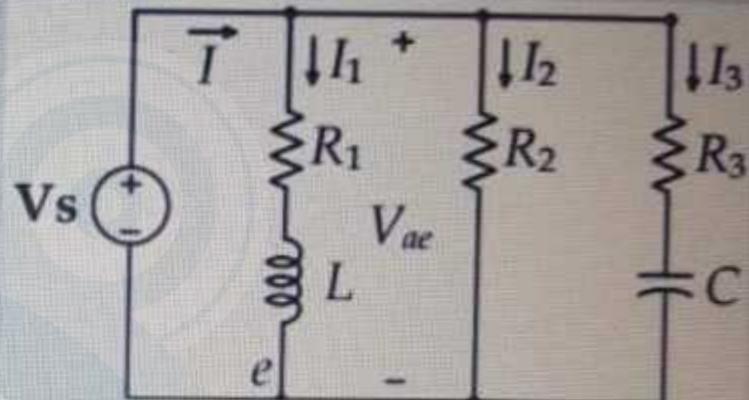
- 1.98 nF - 2.42 nF
- 198 nF - 242 nF
- 19.8 nF - 24.2 nF
- 19.8 mF - 24.2 mF
- 19.8 F - 24.2 F



Replacing the capacitor (C) by an inductor in the following circuit, this will: (1.5 Points)

- increase the value of the total current |
- make no changes to the current values
- increase the value of the current I_2
- make the current I_3 equal to zero
- decrease the value of the total current |

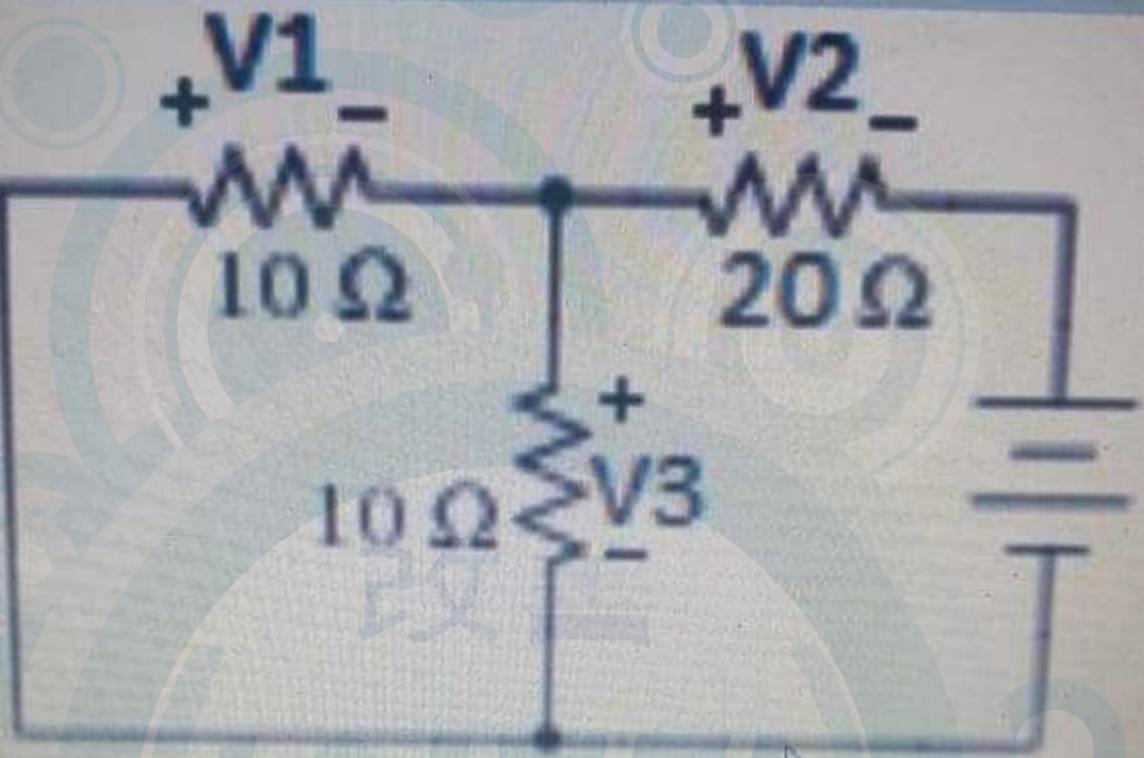
A student connected the circuit shown and he measured the resistor voltages and record them in the shown table but, accidentally, he wrote one of the readings wrong. The wrong voltage (V_1 or V_2 or V_3) is: (2 Points)



V_1	V_2	V_3
2.4	-9.6	2.4

V_1 is the wrong voltage. It have to be a negative value.

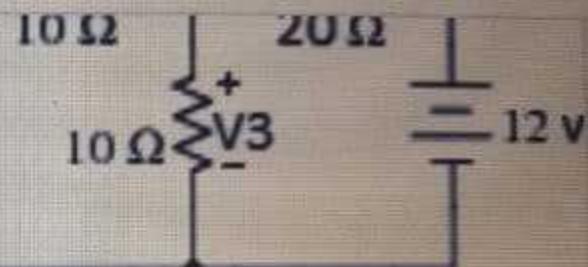EE204_Midterm.. (Electrical Engineering LAb 204)



V1	V2	V3
2.4	-9.6	2.4

A student connected the circuit shown and he measured the resistor voltages and record them in the shown table but, accidentally, he wrote one of the reading wrong. The wrong voltage (V1 or V2 or V3) is:
(2 Points)

v1

Next

Refer to the signals shown on the scope screen. If both signals have a frequency of 4 kHz and the CH2 scale = 0.85 volt/Div. answer the following questions:




19

The time/Div scale will be:
(2 Points)

Enter your answer

ical Engineering LAb 204)

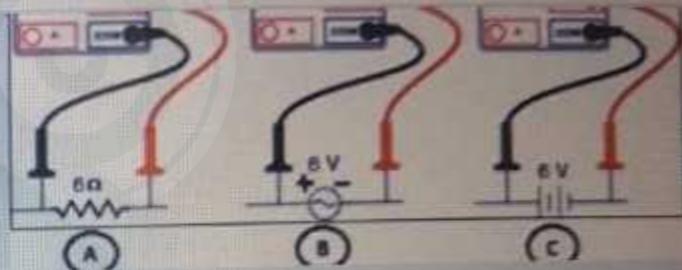


The correct connection and reading in the following Figure is: **B**
(1.5 Points)

- A
- B
- C
- None is correct

(1.5 Points)

Black	0	Blue	6
Brown	1	Violet	7
Red	2	Grey	8
Orange	3	White	9
Yellow	4	Gold	$\pm 5\%$
Green	5	Silver	$\pm 10\%$


505.09

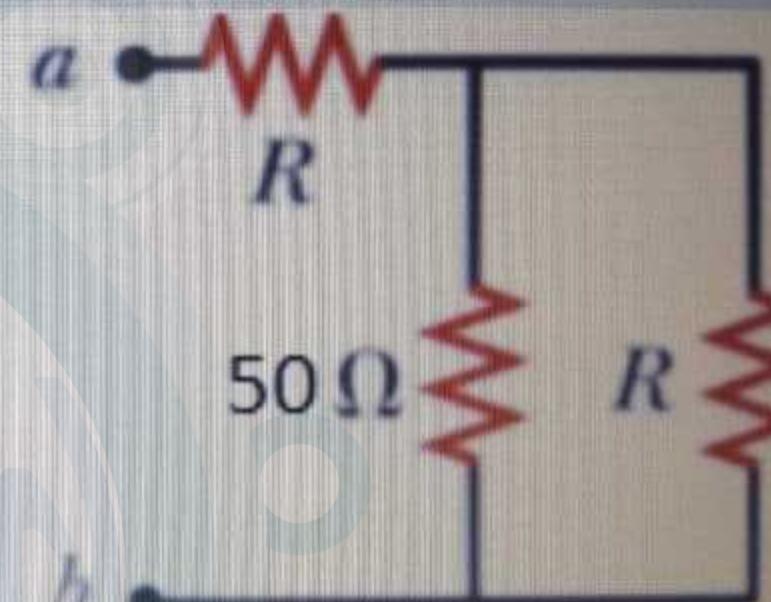

Back


Next

Page 2 of 2

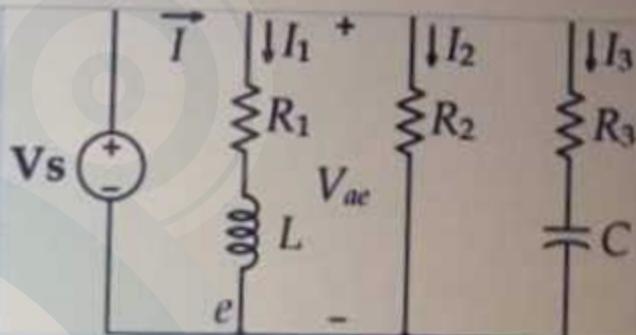

Replacing the capacitor (C) by an inductor in the following circuit, this will: (1.5 Points)

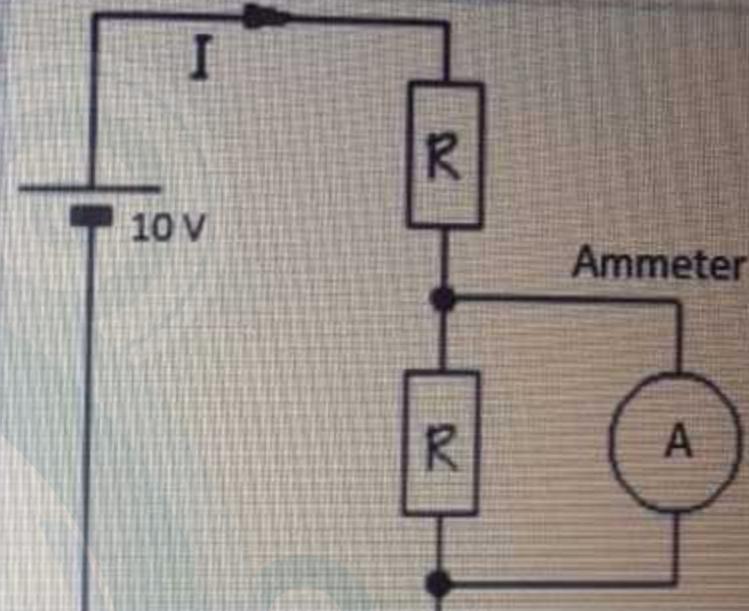
- increase the value of the total current I .
- make no changes to the current values.
- increase the value of the current I_2 .
- make the current I_3 equal to zero.
- decrease the value of the total current I .



If $R=180$ ohm, then the Ammeter reading (in Ampere) is:
(1.5 Points)

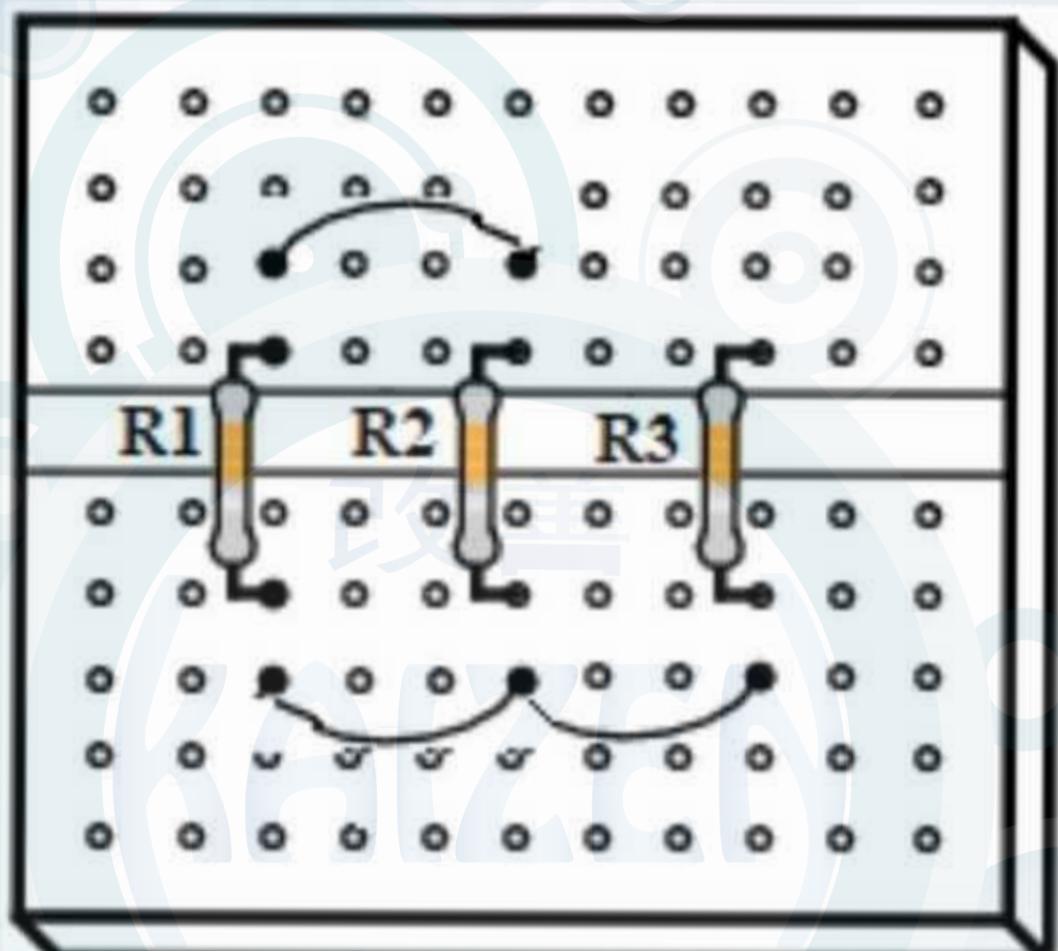0.055


Three resistors are connected on a breadboard as shown in the figure. How can you describe this connection?
(1.5 Points)



- all resistors are connected in parallel
- all resistors are connected in series
- R2 in series with the parallel resistors (R1 and R3)
- R3 in series with the parallel resistors (R1 and R2)

25

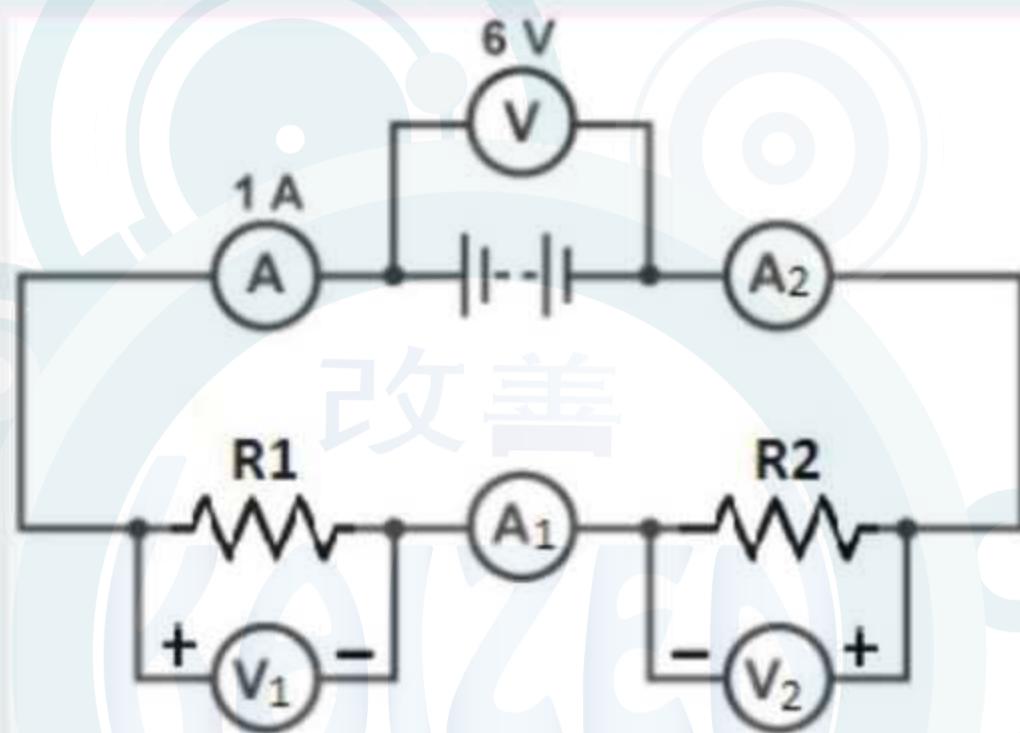IF $R_1 = R_2$, then the correct reading of the voltmeter V_2 (in volt) is:
(1.5 Points)




-3

26

Three resistors are connected on a breadboard as shown in the figure. How can you describe this connection?
(1.5 Points)

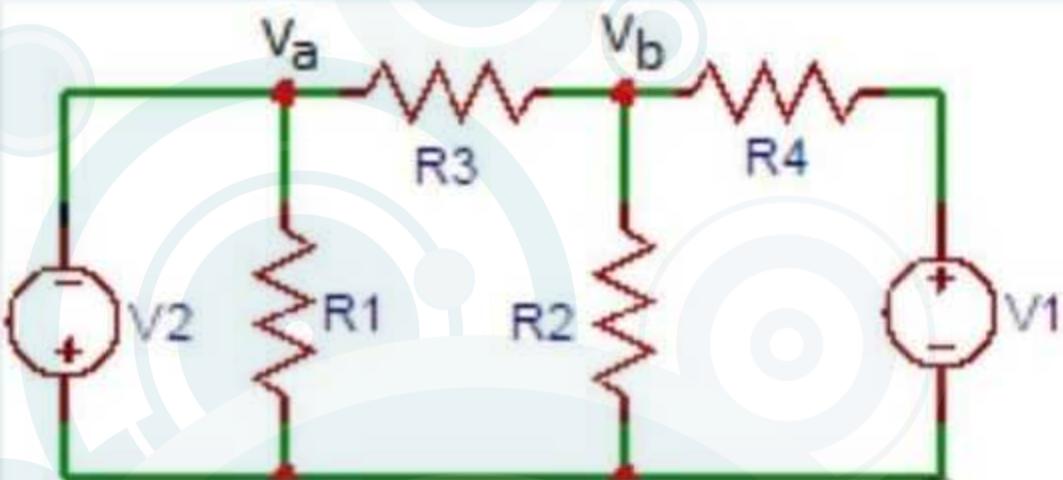equation at node b for the circuit shown,
the missing term in the box is:
(1.5 Points)



$$\frac{V_b}{R2} + \frac{V_b - V_1}{R4} + \boxed{} = 0$$

(Vb - V2) / R3

Vb / R1

(Vb + V2) / R3


None of the above

(Vb + V1) / R4


Full wave rectifier

23

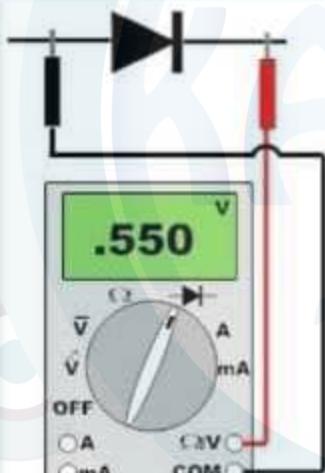
- If the diode is working well, which of the following is the correct reading.
- (A or B or C)
(1.5 Points)



(A)

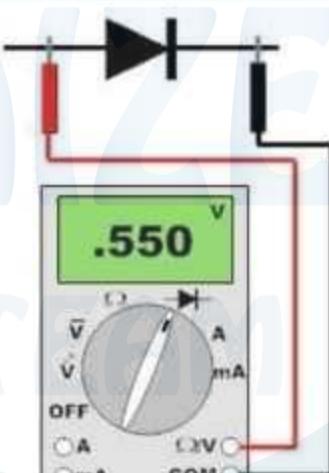

(B)

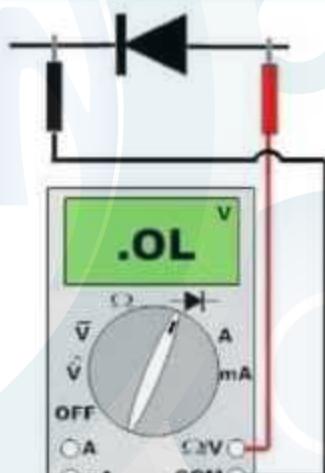


(C)

B

9

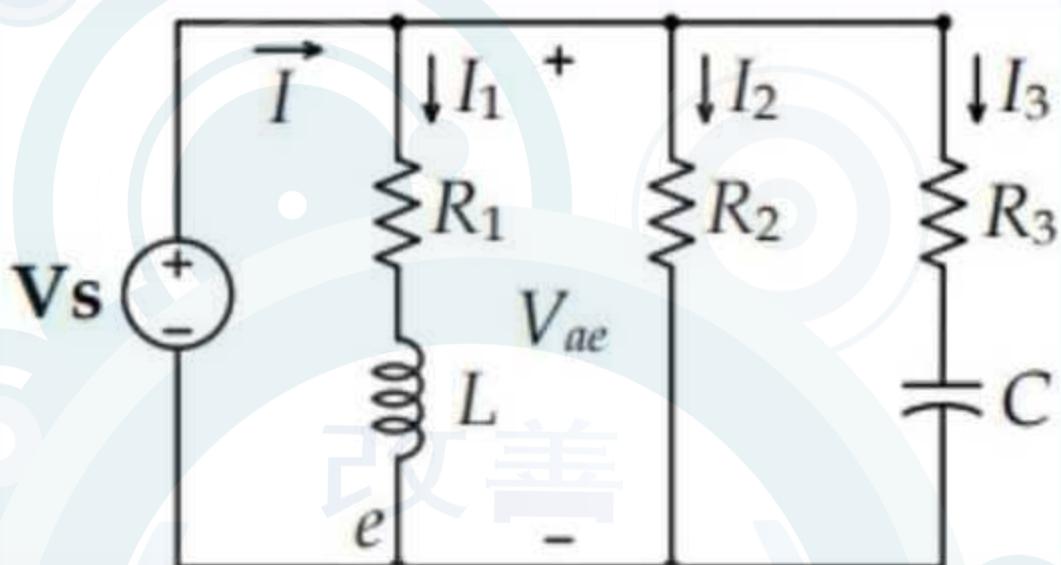Replacing the capacitor (C) by an inductor in the following circuit, this will:
(1.5 Points)



- make no changes to the current values

- decrease the value of the total current I

- increase the value of the current I_2
- make the current I_3 equal to zero
- increase the value of the total current I


24

We can control the amplitude of the signal displayed on the oscilloscope screen by adjusting:
(1.5 Points)

- The Vertical position knob on oscilloscope.
- the Volt/div knob on oscilloscope.
- the Time/div knob on oscilloscope.
- the amplitude knob at the Function Generator.

8

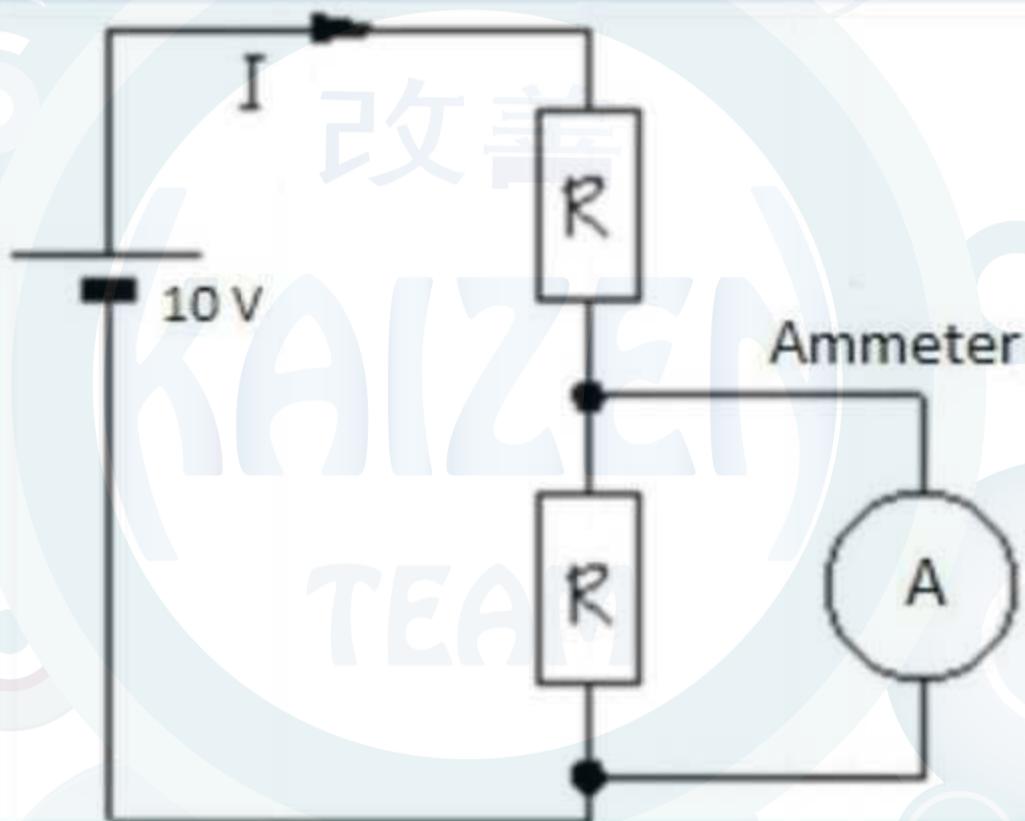If $R=180 \text{ ohm}$, then the Ammeter reading (in Ampere) is:
(1.5 Points)




0.05

7

A student connected the circuit shown and he measured the resistor voltages and record them in the shown table but, accidentally, he wrote one of the reading wrong. The wrong voltage (V_1 or V_2 or V_3) is:

(2 Points)

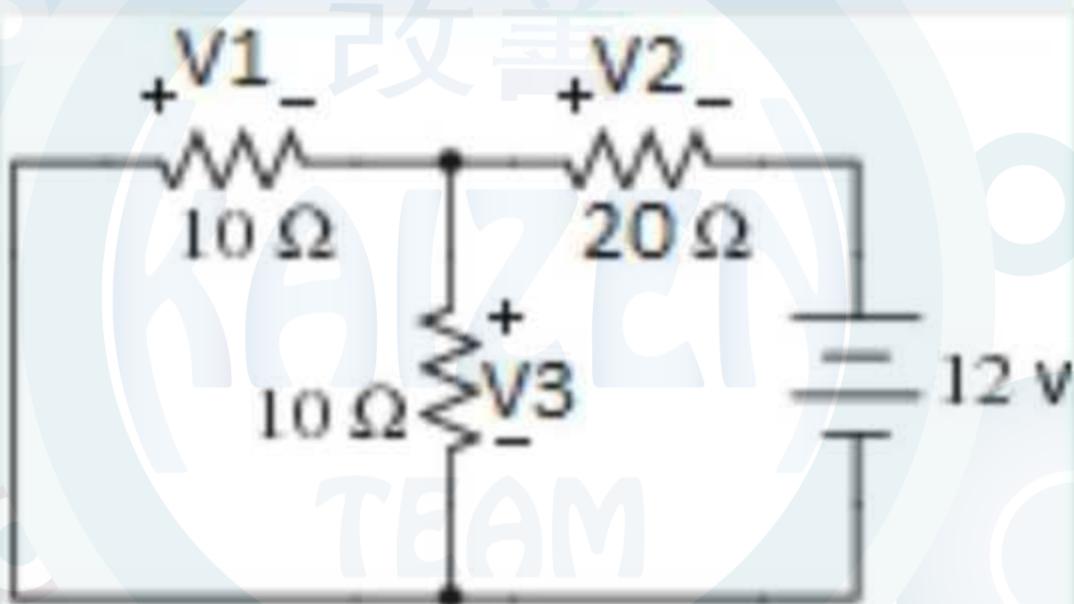

V_1	V_2	V_3
2.4	-9.6	2.4

V1

改善

measuring
method

The correct connection and reading in the following Figure is:
(1.5 Points)



Q. A

Q. C

Q. E


None is correct

8. For a series RL circuit, if the resistance value is halved, then the total impedance magnitude will:
(1.5 Points)

- decrease
- be hard to know
- remain constant
- increase

For the circuit shown, if the resistor R =
(Yellow, Blue, Brown), then the
equivalent resistance (in ohm) between
the terminals a and b is:
(1.5 Points)

Black	0	Blue	6
Brown	1	Violet	7
Red	2	Grey	8
Orange	3	White	9
Yellow	4	Gold	$\pm 5\%$
Green	5	Silver	$\pm 10\%$

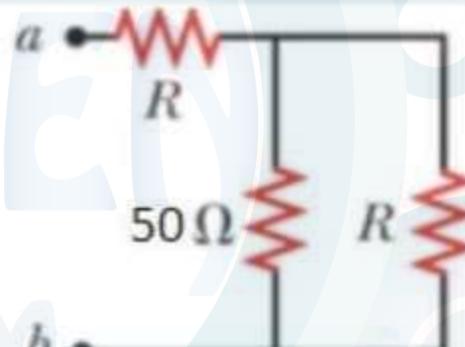

7. An RLC circuit consists of $R = 24 \Omega$, $|XL| = 120 \Omega$ and $|XC|$, are in series across a 60 V source. If the resonance frequency is 2kHz, then the value of capacitor is:
(1.5 Points)

- 9.55 nF
- 663.1 nF
- 9.55 microF
- 663.1 microF

7. An RLC circuit consists of $R = 24 \Omega$, $|XL| = 120 \Omega$ and $|XC|$, are in series across a 60 V source. If the resonance frequency is 2kHz, then the value of capacitor is: (1.5 Points)

- 663.1 nF
- 663.1 microF
- 9.55 nF
- 9.55 microF

8. For a series RL circuit, if the resistance value is halved, then the total impedance magnitude will:
(1.5 Points)

- decrease
- be hard to know
- remain constant
- increase

6. A 47Ω resistor and a capacitor with 150Ω of capacitive reactance are in series across an 4 Vp ac source. The total current expressed in rectangular form, is approximately:

(1.5 Points)

- $I = (24.3 - j 7.61) \text{ mA}$
- $I = (7.61 - j 24.3) \text{ mA}$
- $I = (24.3 + j 7.61) \text{ mA}$
- $I = (7.61 + j 24.3) \text{ mA}$

21

Number of the horizontal divisions on the whole scope screen is:
(1.5 Points)

- 8 division
- 5 division
- 4 division
- 10 division


If you adjust the digital multimeter as a voltmeter, then choosing between (VAC) or (VDC) is according to:
(1.5 Points)

- number of resistors in the circuit
- polarity of the supply



the type of the supply

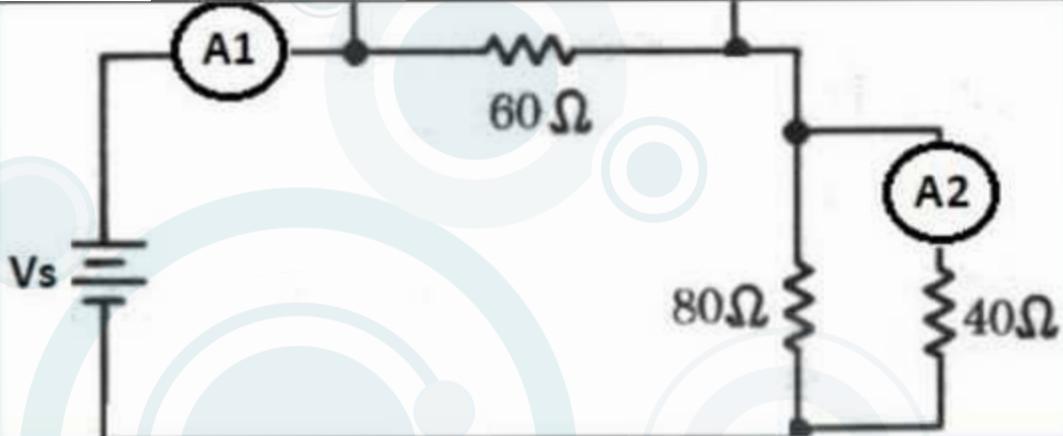- the way of voltmeter connection in the circuit



15

The expected reading for the Ammeter A2 is approximately;
(1.5 Points)

None of the above

267.6 mA

26.7 mA

2.67 mA

3. For an RL circuit, when the supply frequency increases, then:

(2 Points)


- both series and parallel RL impedances will decrease
- both series and parallel RL impedances will increase
- the series RL impedance will increase and parallel RL impedance will decrease
- the series RL impedance will decrease and the parallel RL impedance will increase

For the circuit shown below, if a superposition theorem has been carried out to measure the voltage V_o , then the effect of the current source on the voltage (V_o) can be found by:
(1.5 Points)



- Disconnecting the voltage source and replacing it by a short circuit
- Connecting both the voltage source and the current source
- Connecting a wire in parallel with the voltage source
- Disconnecting the current source

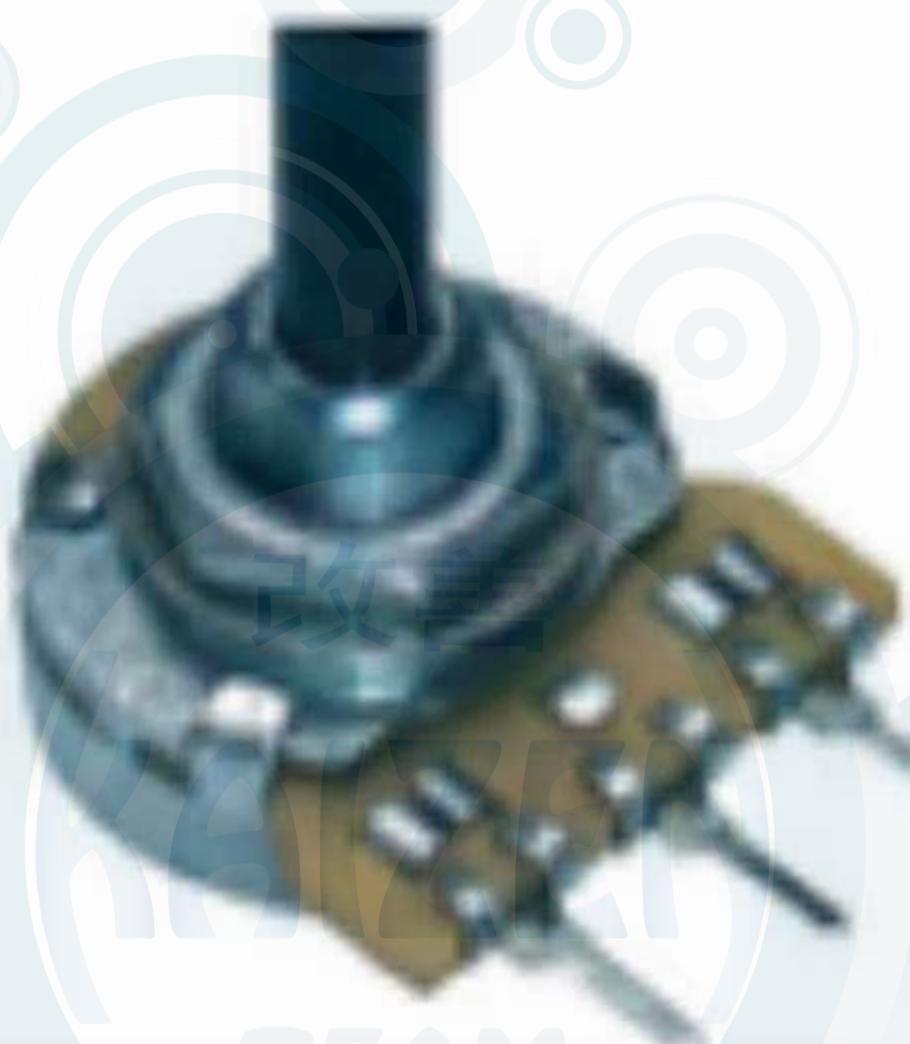The following component is a:
(1.5 Points)



Variable inductor

Potentiometer.

Variable capacitor

Bridge