

Exp 1 :- Resistors and DC circuits.

⊛ Resistors :-


Symbol R 

→ the value of a Resistor can be known :

① From the Color Code on the Resistor


② By measuring the value of it using an ohmmeter.

Ex: ① 4-color Codes

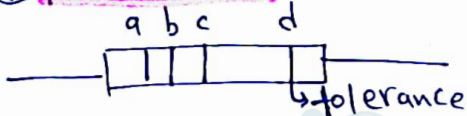

$$R = a b \times 10^c \pm d$$

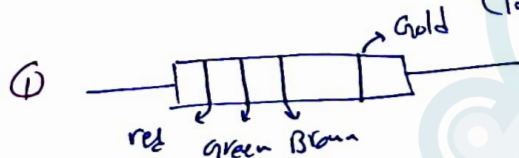
$\downarrow$
 $(\frac{d}{100}) \times (ab \times 10^c)$



$$R = 250 \pm 5\% \Omega$$


$\rightarrow (\frac{5}{100}) \times 250 = 12.5$
 $250 + 12.5, 250 - 12.5$
 237.5

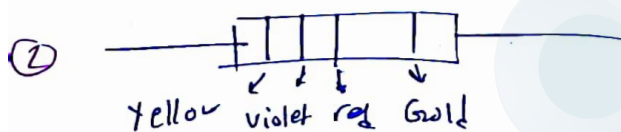when reading the Resistor let the tolerance to the right and the other colors to the left. (start reading from the left to the right)



$$R = 4700 \pm 0.05 \Omega$$


⊛ 5-color Codes.

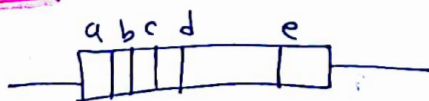

$$R = a b c \times 10^d \pm e$$


Black → 0	Blue → 6
Brown → 1	Violet → 7
red → 2	gray → 8
orange → 3	white → 9
Yellow → 4	Tolerance:
Green → 5	Gold → 5%
	silver → 10%

Ex:



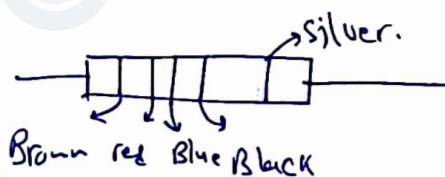


$$R = 126 \pm 0.1 \Omega$$

* Bread Board:

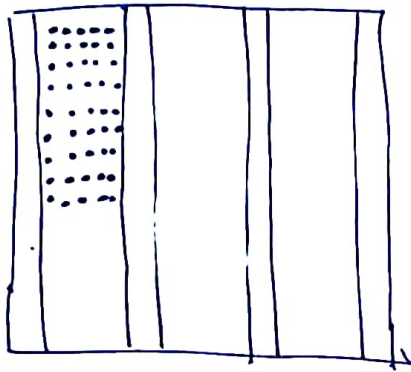

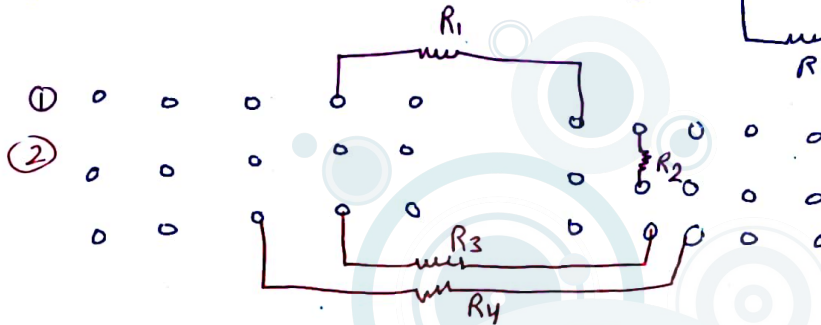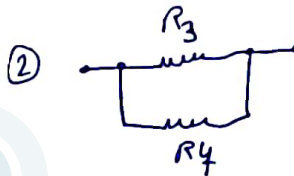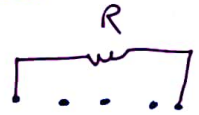
each 5 Series dots represents a node
 *if the resistor is connected on the same node, it creates a short circuit.



① R_1 one end is connected to node ① and the other end at node ②

R_2 is connected where R_1 ended (at node ②) and the other end is same node ③

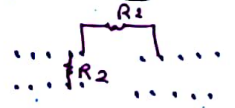④ node ③ can be the vertical node or the horizontal node
 Both are correct.



② R_3, R_4 start at the same node and end at the same node.

* DC Supply



→ Power device: DC Power Supply

it provides a steady direct current (DC) voltage to power electronic circuits.

→ Measuring device:

- digital multimeter → measures: diode, ohm, Volt, capacitor, Current

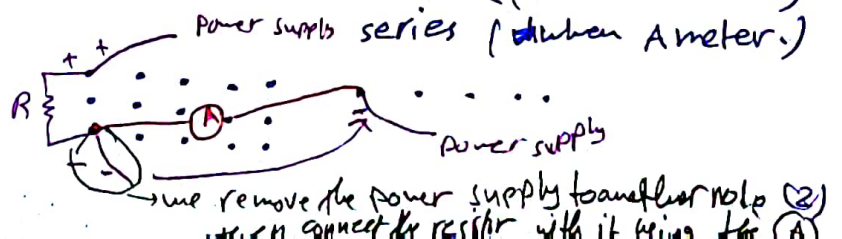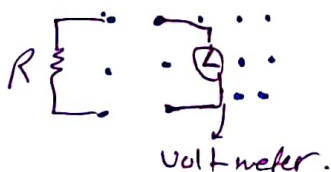↳ digital multimeter is always connected parallel (when Volt meter)



⇒ when measuring the resistance (Ω)

remove all supplies in the circuit

لا تترك أي مصدر طاقة في الدارة أثناء قياس المقاومة
 thevinin R

EP2: Resistors and D.C. circuits.

Ex: Find the color code for each resistor (4 Band resistors)

① $R = 160\Omega$
 Brown Blue red


② $R = 120\Omega$
 Brown red red

③ $R = 1000\Omega$
 Brown Black orange

$R = ab \times 10^c \pm d$

* ohmmeter.

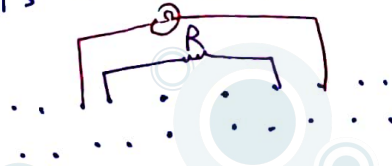→ using the digital multimeter as (ohmmeter) to find the resistance.
 (the ohmmeter is connected parallel with the resistors).



* connecting Resistors in parallel and series and finding the resistance.

⇒ series:

$\Sigma R = R_{\text{series}} = R_1 + R_2 + R_3$




ohmmeter.

The ohmmeter is connected in parallel with the circuit.

(positive wire on the beginning of it and the negative wire on the end of it)

⇒ parallel:

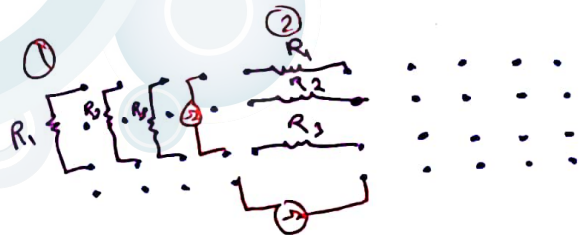$\Sigma R_{\text{parallel}} = \frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$



* voltage and current division.

⇒ voltage division.

* in Series: the total voltage is divided among the resistors

$V_{\text{tot}} = V_1 + V_2 + V_3 + \dots + V_n$

⇒ if you have n resistors $R_1, R_2, \dots, R_n$ in series with a total voltage V_{tot} , the voltage across resistor R_i is:

$V_i = \frac{R_i}{R_{\text{total}}} \times V_{\text{tot}}$

⊕ in parallel : the voltage across all Resistors is the same.

$$V_{\text{parallel}} = V_{\text{tot}}$$

⇒ this is because all the Branches in a parallel circuit share the same two nodes.

⇒ Current division.

⊕ in series : the current is the same through all components because there is only one path for the current to flow.

$$I_{\text{series}} = I_{\text{total}}$$

⇒ this means the current does not divide, it remains constant throughout the circuit.

⊕ in parallel : the current divides between the branches in inverse proportion to their resistances. (Branches with lower resistance will carry more current, while those with higher resistance will carry less)

⇒ For two resistors R_1, R_2 connected in parallel, and total current I_{tot} :

$$I_1 = \frac{R_2}{R_1 + R_2} \times I_{\text{tot}}$$

$$I_2 = \frac{R_1}{R_1 + R_2} \times I_{\text{tot}}$$

⇒ For n resistors $R_1, R_2, \dots, R_n$ the current through any branch is:

$$I_i = \frac{R_{\text{eq}}}{R_i} \times I_{\text{tot}}$$

$$R_{\text{eq}} \rightarrow \frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

* Capacitors and inductors

* Capacitor

$$I = 0$$

$$C = \frac{Q}{V}$$

C: Capacitance (Farad)

Q: charge (in Coulombs)

V: voltage (in Volts)

- A capacitor blocks direct current (DC) once it is fully charged.
- initially, current flows as the capacitor charges.
- over time, the current decreases and eventually stops when the capacitor is fully charged.
- The branch behaves like an open circuit after charging.

* inductor

- The branch behaves like an short circuit, allowing the DC current to flow freely.


$$L = \tau R$$

L: inductance (in Henries)

τ : time constant (in Sec)

R: Resistance in series with the inductor (in ohms)

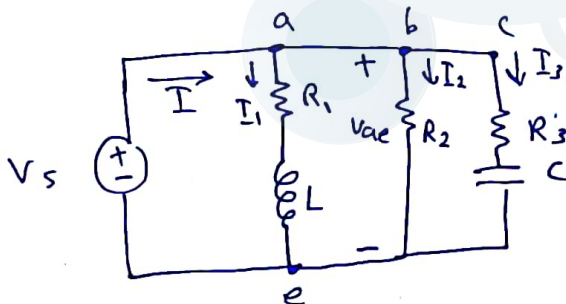⇒ the current might decrease just a little due to the inner resistance of the inductor




$$I_3 = 0$$

$I_1 \rightarrow$ stays the same value

when finding the current in any Branch just connect the ammeter in parallel from the end where the I is flowing,  Connect from here

* Nodal and mesh analysis

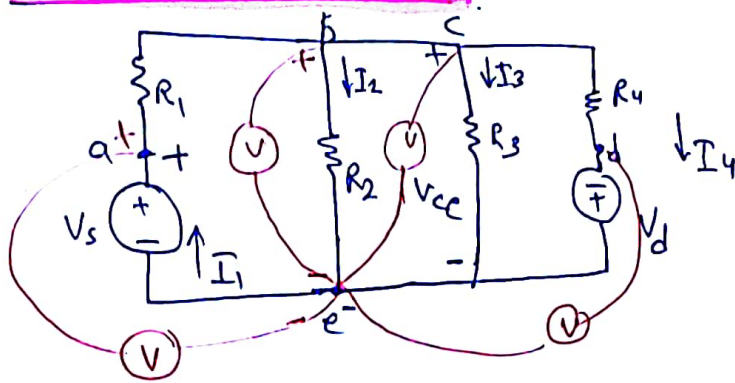

* Note! when connecting an A always connect it from the end with the current flow

* Nodal Analysis

Steps for nodal:

- 1- identify all nodes in the circuit
- 2- choose a reference node
- 3- for each node apply Kirchhoff's Current law (KCL)

$$\sum I_{in} = \sum I_{out}$$

- 4- express the currents in terms of node voltages using ohm's law
- 5- solve the system of equations for the unknown node voltages.

$$I = \frac{V}{R}$$

* Mesh analysis

- 1- Identify all meshes in the circuit (a mesh is a loop that does not contain any other loops inside it)



3-meshes.

- 2- define a mesh current for each mesh (generally, clockwise or counterclockwise)
- 3- for each mesh, apply Kirchhoff's voltage law (KVL).

$$\sum V = 0$$


- 4- express each voltage in terms of the mesh currents using ohm's law

$$V = IR$$

- 5- solve the system of equations for the unknown mesh currents.

EXP 3: Network Theorem

* Superposition Theorem

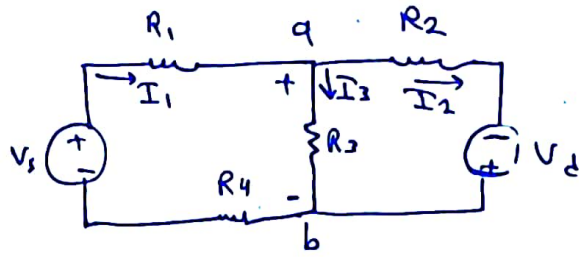

Steps For Applying Superposition:

1- identify all independent sources in the circuit. These can be voltage source or current source

2- turn off all but one independent source:

- For voltage source: Replace it with a short circuit (wire),
- For current source: Replace it with an open circuit (a break in the circuit)

3- Solve the circuit with the remaining active source using any of the usual circuit analysis methods (e.g.: Ohm's law, Kirchhoff's laws, mesh or nodal analysis)

4- Repeat steps 2 and 3 for each independent source in the circuit.

5- Sum the individual contributions from each active source to find the total voltage or current at each point in the circuit.

* Thevenin and Norton

⇒ Thevenin: states that any linear two-terminal circuit can be replaced with an equivalent circuit consisting of:

- 1- a single voltage source V_{th} 2- in series with a single resistor R_{th}

Steps to find thevenin equivalent:

1- remove the load resistor (if present)

2- find V_{th} : Determine the open-circuit voltage across the terminals (where the load resistor was connected).

3- find R_{th} : • Turn off any sources (replace voltage source with short circuits and current sources with open circuits) • Find the equivalent resistance ^{seen} across the terminals.

4- Replace the original circuit with the Thevenin equivalent circuit. (7)

⇒ **Norton**: States that any linear 2-terminal circuit can be replaced with an equivalent circuit consisting of:

- 1- A single current source I_N
- 2- in parallel with a single resistor R_N

steps to find Norton equivalent:

- 1- Remove the load resistor (if present)
- 2- Find I_N : Determine the short circuit current across the terminals
- 3- Find R_N :
 - R_N is the same as R_{th} in Thevenin's equivalent circuit.
 - Turn off all ~~independent~~ independent sources and find the equivalent resistance seen across the terminals.
- 4- Replace the original circuit with the Norton equivalent circuit.

* $R_{th} = R_N$

* $I_N = \frac{V_{th}}{R_{th}}$

* $V_{th} = I_N R_N$

* V_{th} can be found by using any circuit analysis (Ohm's law, Voltage Division, Nodal Analysis, mesh Analysis)

$$V_{th} = V_{ab}$$

↳ the potential difference between 2 terminals (a, b)

Imp Note:

- Use open circuit voltage to find V_{th} .
- For R_{th} :
 - combine resistors based on their series or parallel configuration after deactivating sources.
 - if the resistor is on an open circuit branch take it.

* Maximum Power Transfer Theorem

A load resistor (R_L) will receive the maximum power from a circuit when its resistance is equal to the Thevenin resistance (R_{th}) of the circuit as seen from the load's terminals. $R_L = R_{th}$.

Key points:

- 1- the source circuit must first be simplified to its Thevenin equivalent, which consists of:
 - Thevenin voltage (V_{th})
 - " Resistance (R_{th})
- 2- once R_{th} is known, the load resistance (R_L) should be set to match R_{th} for Max power transfer.

$$\textcircled{*} P_{max} = \frac{V_{th}^2}{4R_{th}}$$

For exp4:

$\textcircled{*}$ lead / lag

EXP 4: Sinusoidal signals.

AC

Function Generator Device

Key features:

- wave form Type: Sine wave, Square wave, Triangular wave, Sawtooth wave
- Frequency Range: Adjustable from a few Hz to several MHz
- Amplitude control: Allows adjustment to the output signal's voltage.

Oscilloscope Device

Key features:

- Axes: ~~Y~~ Y-axis → Voltage / X-axis → Time.
- Triggering: Allows stable display of repetitive wave form.
- Probes: used to connect the oscilloscope to the circuit.
- Measurements: voltage, frequency, phase, rise time.

measures took from a sinusoidal signal.

- 1- U_{peak} :- Count the number of vertical divisions of the signal to the highest point
- Find the vertical scale (2V/div)
 - Multiply # of div. by the # of squares.

$$U_p = \# \text{ of squares} \times \text{Volt/div.}$$

2- $V_{pp} = 2 U_p$

3- $U_{RMS} = \frac{U_p}{\sqrt{2}}$ or $V_{RMS} = \frac{V_{pp}}{2\sqrt{2}}$

4- Frequency $f = \frac{1}{T}$ T → period

5- Period $T = \# \text{ of horizontal squares} \times \text{time/div.}$

6- phase shift ϕ or $\phi = \frac{\Delta t}{T} \times 360$

7- Amplitude (A) $A = V_p$

* Time / div
Horizontal


* Volt / div
vertical

$\Delta t = \overset{\text{time}}{\text{difference between the two signals.}}$

Exp 5: Capacitive reactance

* RC circuit: (phasor diagram)

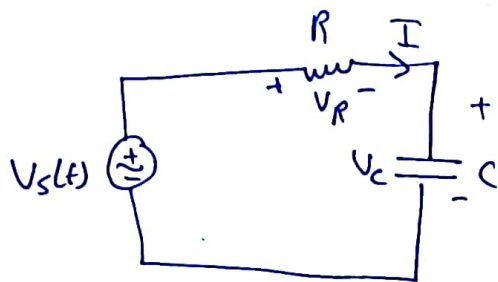* in series: Resistor in series with capacitor




* always assume that the supply is the reference.

$$\Rightarrow \phi_{V_s} = \text{Zero}$$

* the current passes in the circuit before the V_C is on the capacitor

I leads V_C with $\phi = 90^\circ$

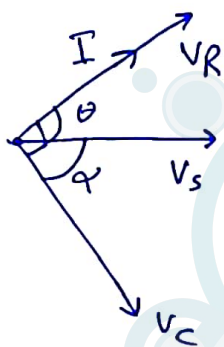


* On a resistor the current passing through the resistor is in phase with the V on the resistor

I, V_R in phase


* The current and voltage at the capacitor I leads V_C $\phi = 90^\circ$
because the current goes through the capacitor first to charge it then voltage occurs.

$\Rightarrow$ therefore

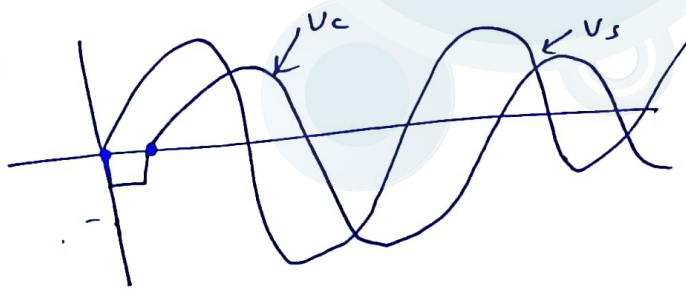


V_s leads V_C


* In parallel

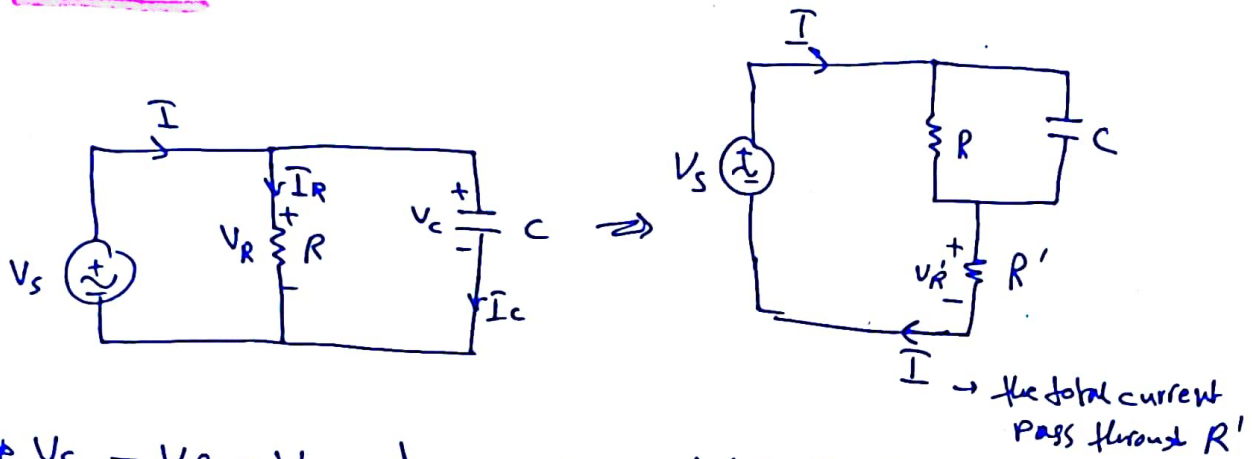

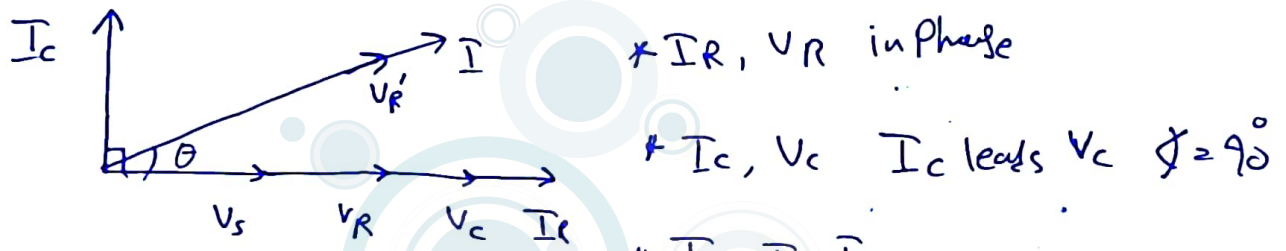* $V_s = V_R = V_C$ because connected in parallel



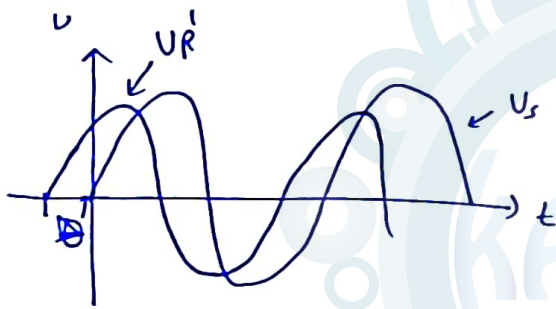* $\underline{I} = \underline{I_C} + \underline{I_R}$
 ↓
 Resultant of I_C and I_R




* I, V_R' in phase $\phi = 0$

$\Rightarrow V_R'$ lead V_s

Exp 6: Inductive reactance

* Phasor diagram



* in series

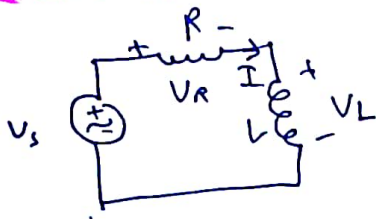

* $I \text{ lag } V_s \quad \phi = \theta$


* $I, V_R \text{ in phase } \phi = 0$

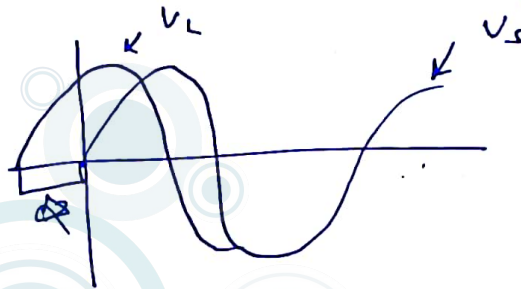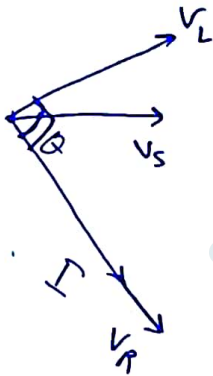* $I, V_L \quad V_L \text{ lead } I \quad \phi = 90^\circ$



$V_L \text{ lead } V_s$

* in parallel


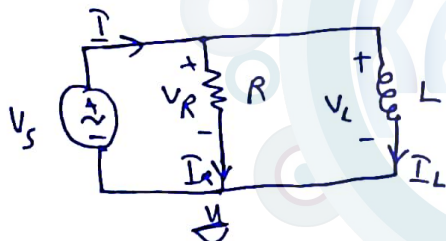


* $V_s = V_R = V_L \rightarrow \text{in phase}$


* $I_R, V_R \text{ in phase}$

* $I_L, V_L \quad I_L \text{ lag } V_L \quad \phi = 90^\circ$

* $I = I_L + I_R \rightarrow \phi = \theta$

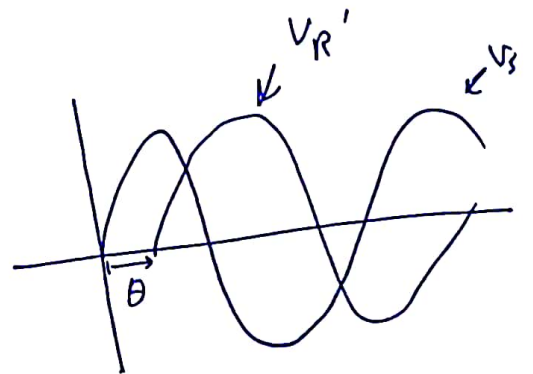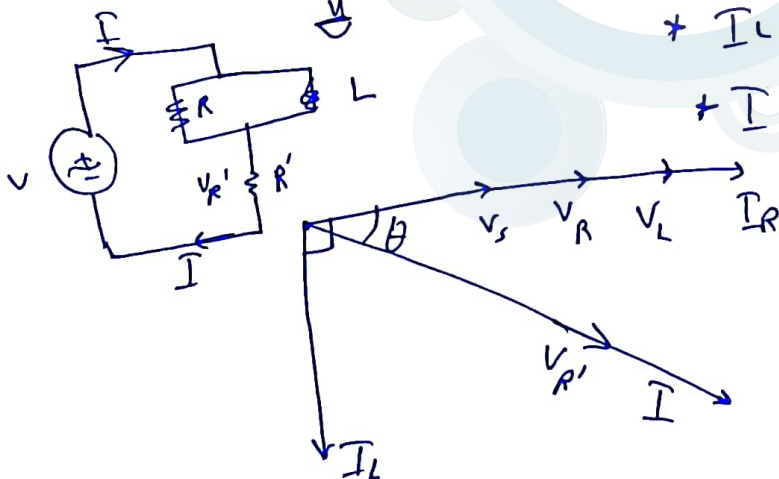

Exp 7: Diode characteristics.

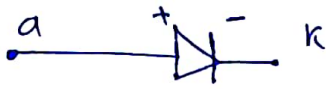

a: Anode, k: Cathode

* the Diode starts working at specific V


Germanium $\rightarrow V \approx 0.3V$
Silicon $\rightarrow V = 0.7V$

if it didn't reach or exceed the V , then it's an open circuit

* if the diode was connected in opposite direction $I=0$, Reverse Breakdown Voltage
called the off ~~region~~ region.

3 regions:

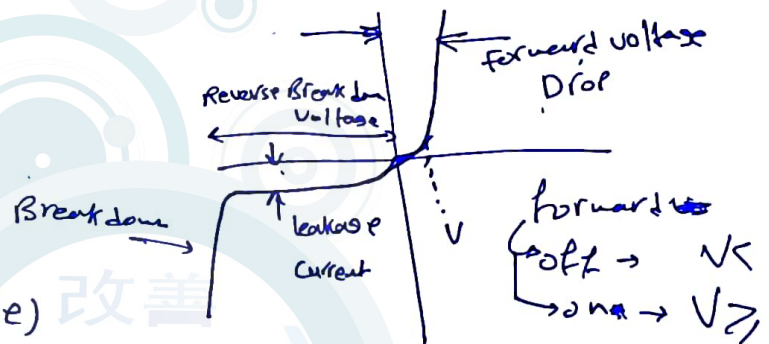- 1- Forward region
- 2- off region (Reverse)
- 3- Breakdown



diode is connected parallel with digital multimeter.

Exp 8: Diode applications