

Don't do it

ecosystem is very

1967

HeV

2.4

hardback

100%

Q)

میں

1. Max


(Exp 1)

Resistor

4-colors

$$a b \times 10^c \quad (\text{Tolerance}) \quad \pm d$$

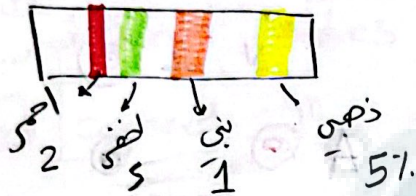5-colors $a b c \times 10^d \quad (\text{Tolerance}) \quad \pm e$




$$25 \times 10^1 \pm 0.05$$

$$250 \pm (0.05 \times 250)$$

4-color-code


$$250 \pm 12.5$$

Range (237.5 - 262.5)

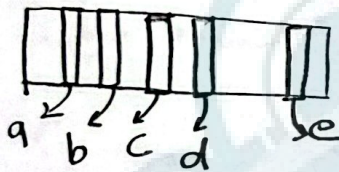

5-color-code
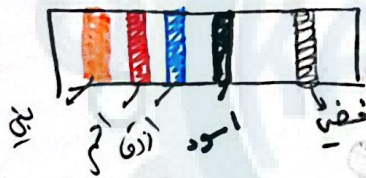
$$a b c \times 10^d \pm \frac{e}{\text{tolerance}}$$



$$126 \times 10^1 \pm 10\%$$

$$126 \pm 12.6 \rightarrow \text{Range}$$

bread board

one node




$$V_1 = V_2$$

short circuit


$$\Delta V = \text{zero}$$




$$\sum I = \text{zero}$$

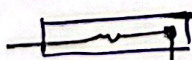

series

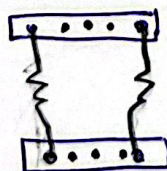

Parallel

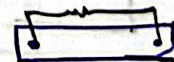

$$\Delta V = \text{zero}$$

$$I = \text{zero}$$

no Resistance

short circuit

1 [2] supply:-

(DC) constant with time

① digital multimeter


ACV \rightarrow V_{rms} (effective) voltage




DCV \rightarrow Direct voltage

Ω \rightarrow Resistance

DCA \rightarrow direct current

ACA \rightarrow effective current (I_{rms})

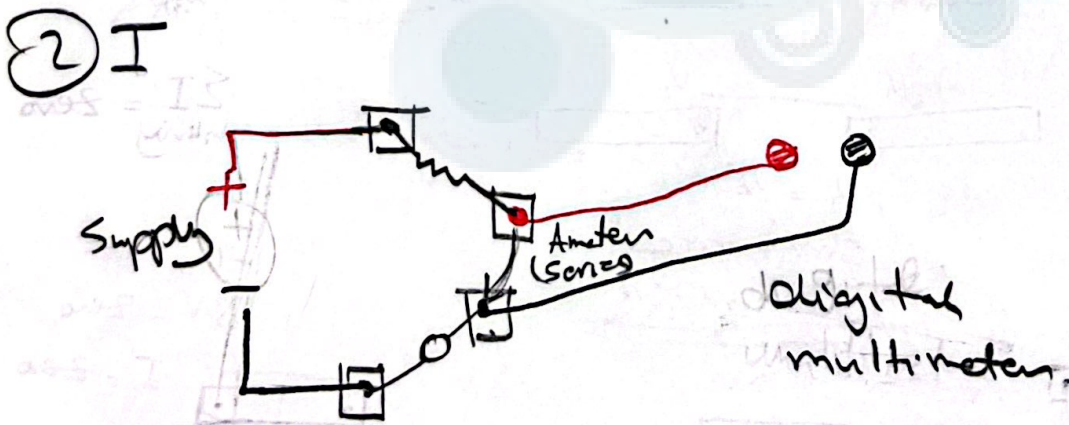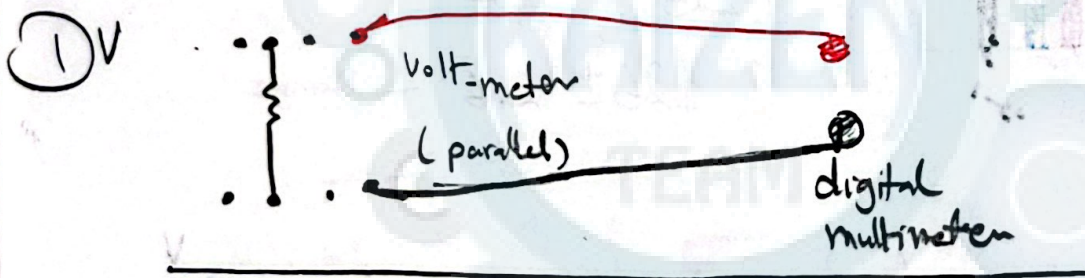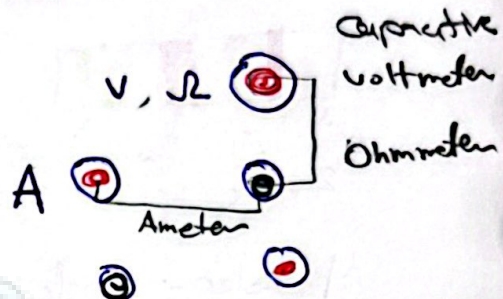 dial \rightarrow ① shift ② check \Rightarrow choose



③ Resistance (R)



Can't be measured while it's connected to the circuit

- ① you must remove all of the supplies
- ② put the (resistance of resistor) at any two different nodes, but alone (not connected to any supply)
- ③ connect the ohmmeter in parallel




- ④ you can find its value by the color code -- (nominal value)

Exp2

4 - color - code

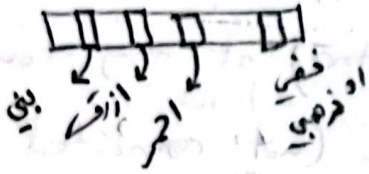[1] $1600 \Omega \rightarrow 16 \times 10^2$



way

1

by the

color

code


[2] $1200 \Omega \rightarrow 12 \times 10^2$

أصفر أحمر أسود


[3] $1000 \rightarrow 10 \times 10^2$

أصفر أسود

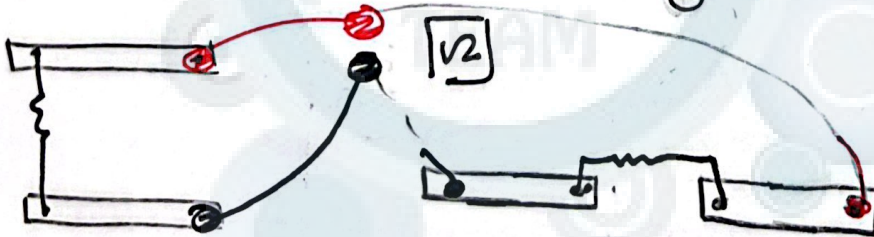Second way \rightarrow by The ohmeter digital multimeter




① Form the circuit

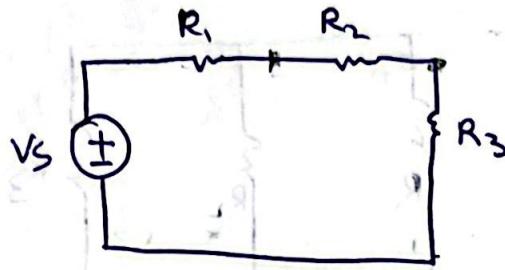

② Set V_s on the DC-power supply

don't turn the power supply on unless your circuit is connected


Voltmeter
 $V = V_{on} R_2$

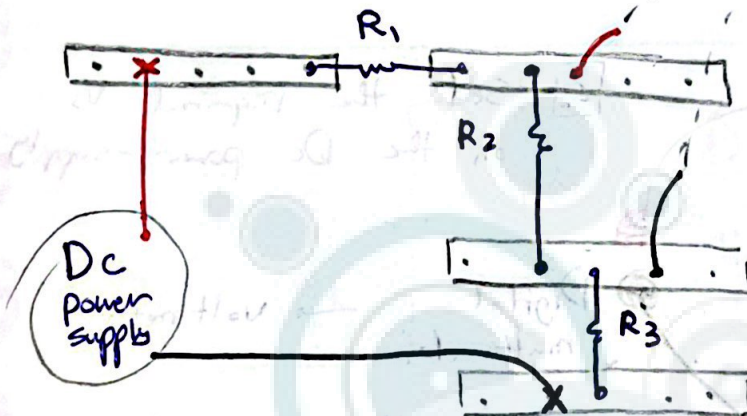


① First step


② to measure the voltages... connect the voltmeter parallel to the resistor...

to find the currents

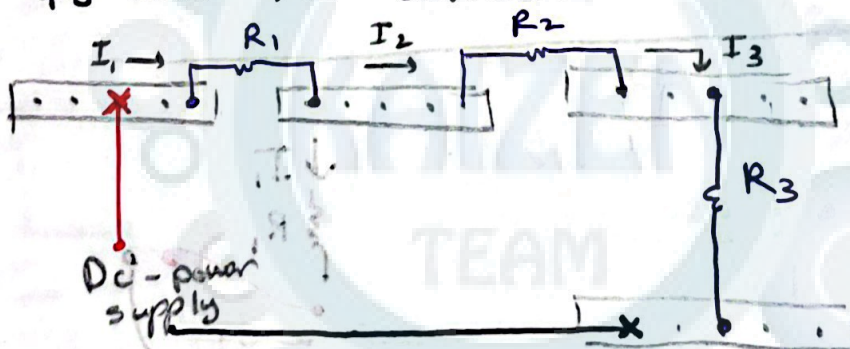


②

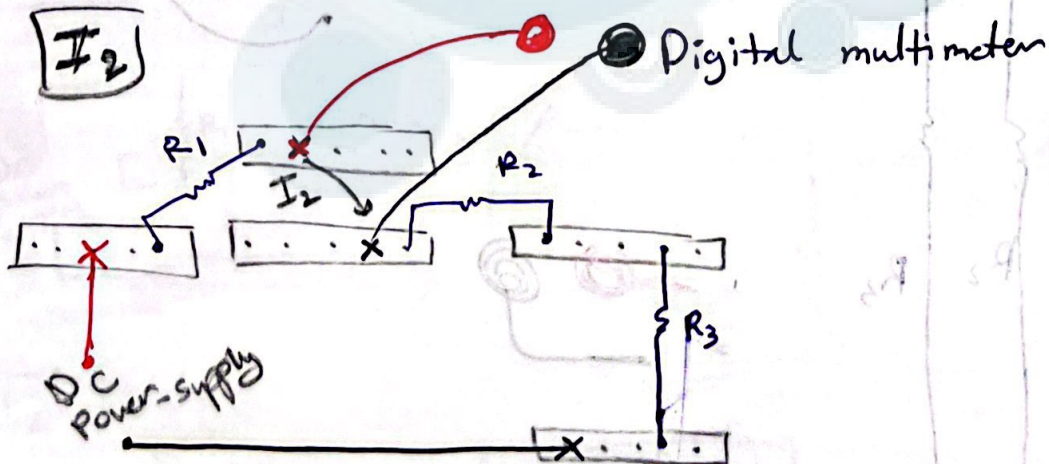

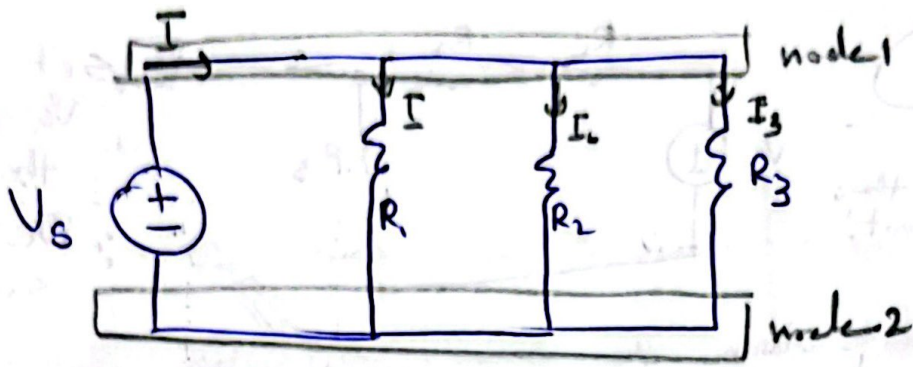

① Form the circuit

① V :

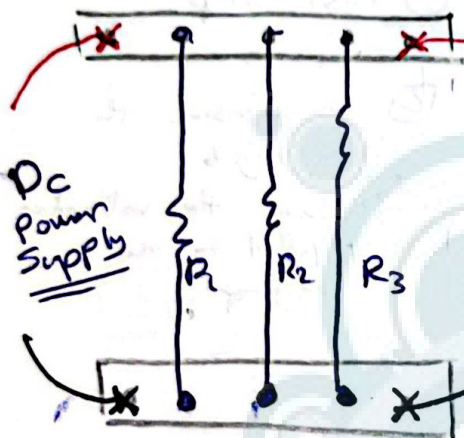


② Set the required V_s on the DC-power-supply

Digital multi-meter \rightarrow Volt meter




$$V = V_1 = V_2 = V_3 = V_s$$

② I :

I_1

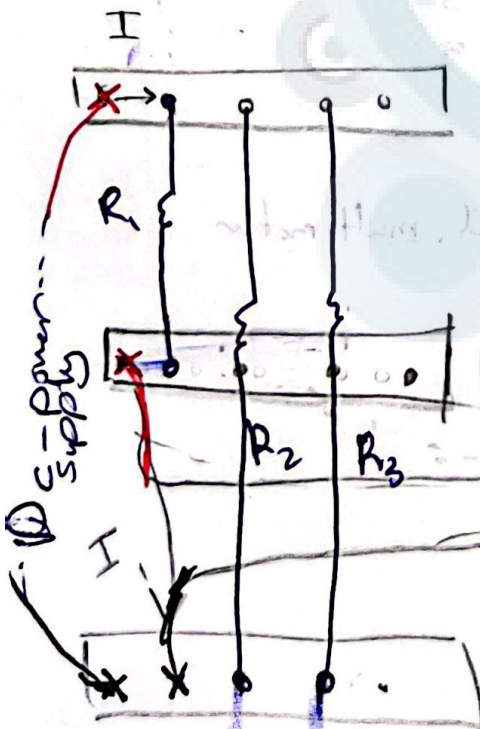

Ammeter

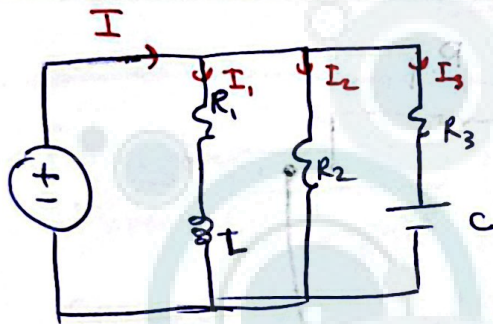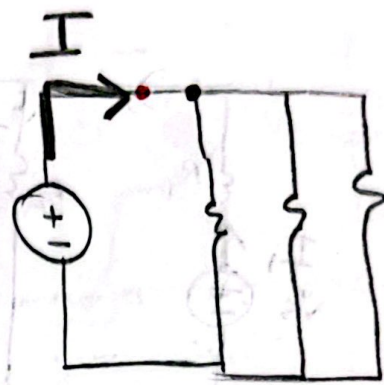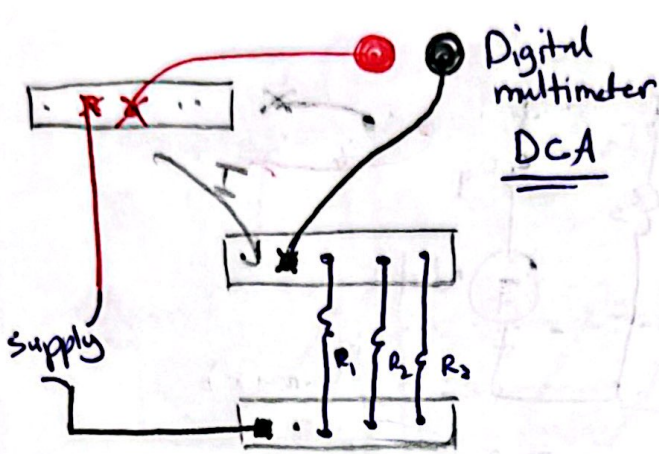


DC - circuit

$$I_3^* = (Zero)$$


$$I_1 = (I_1 \text{ without } L)$$

In
DC-circuit :-

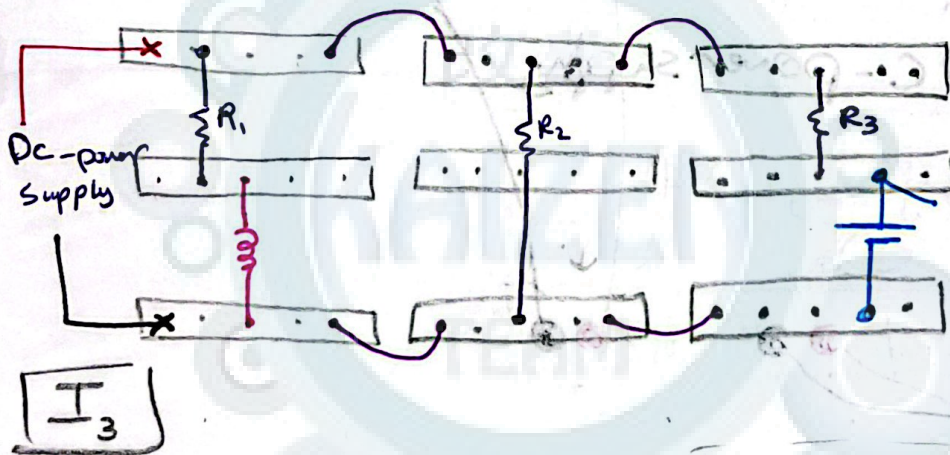

① Inductor
↓
short circuit

② capacitor
↓
open circuit

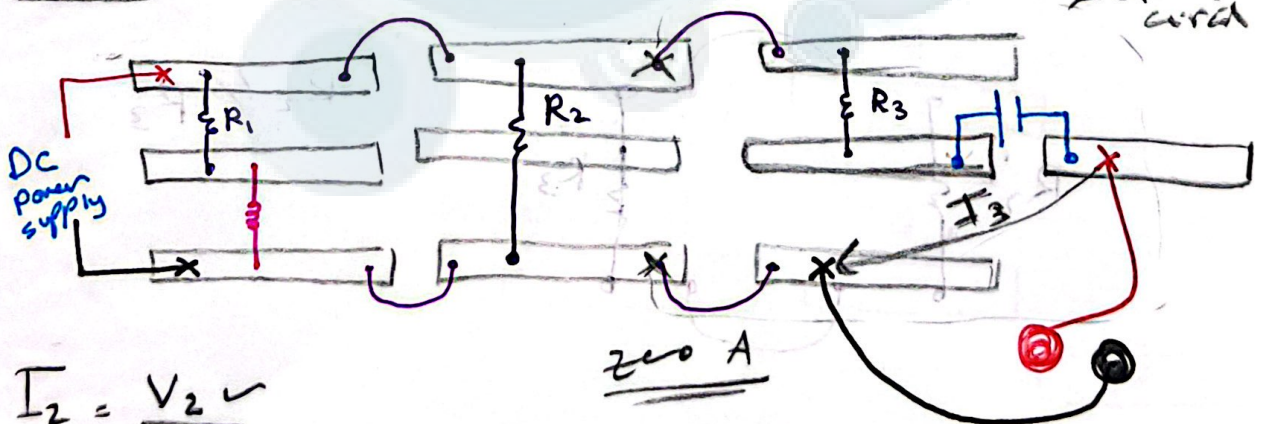




$$I_2 = \frac{V_2}{R_2 L}$$

constant



zero

Digital multimeter

DCA

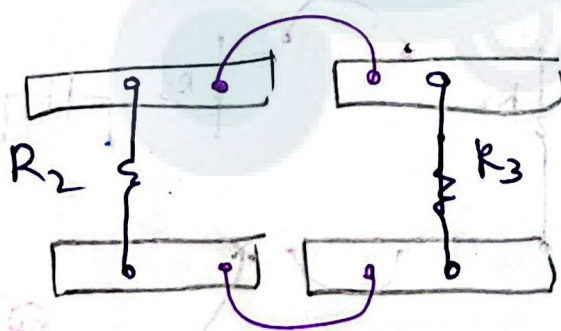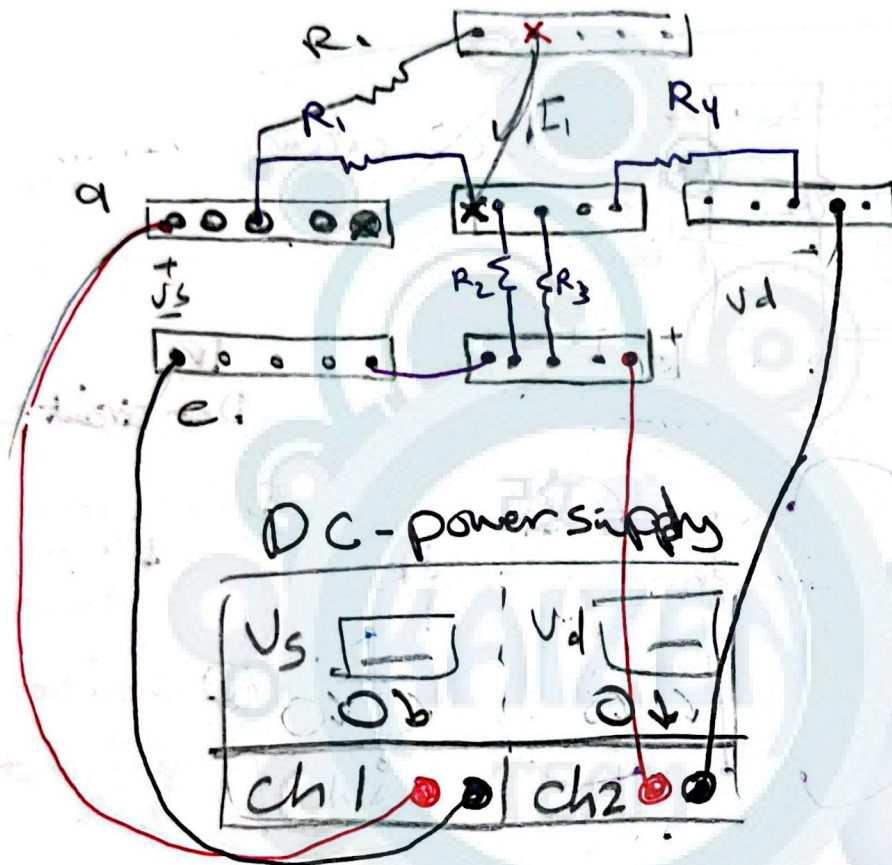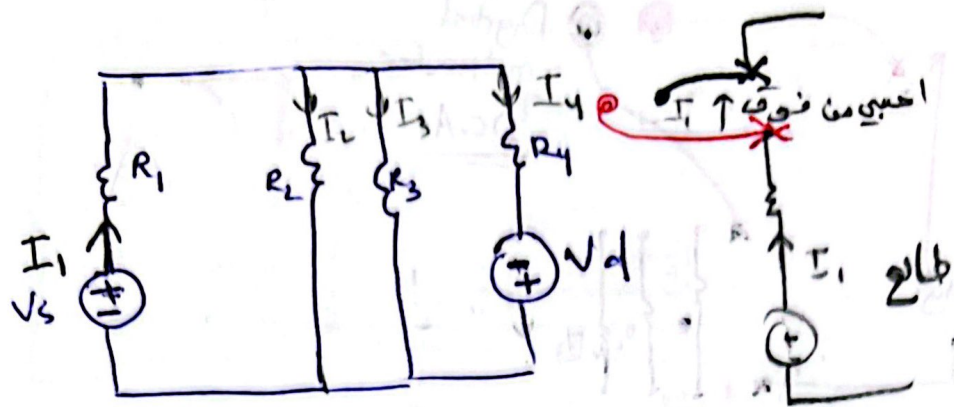

$R_2 // R_3$

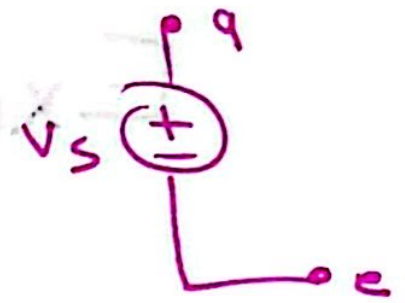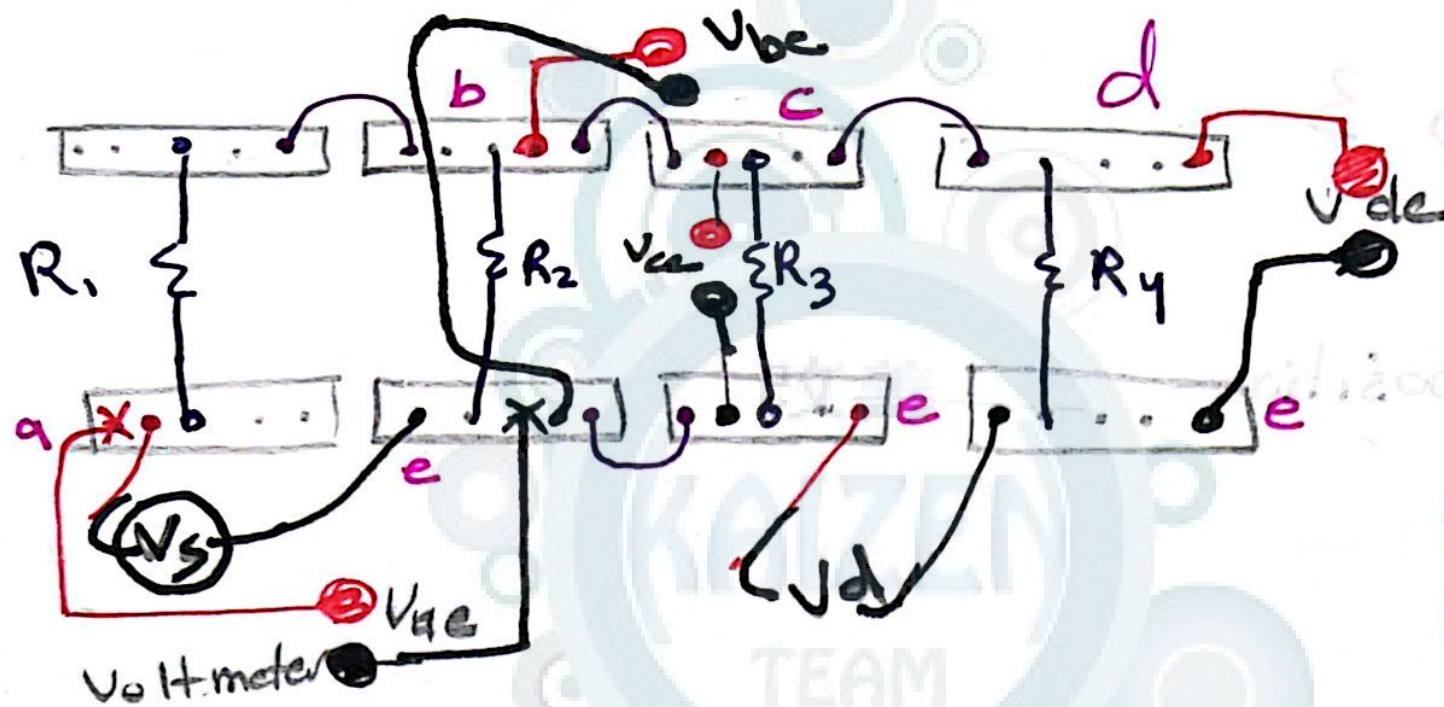


$$V_{ae} = V_s$$

First letter +
Second letter -


$$V_{be} = V_{on R_2}$$


$$\text{Deviation} = \frac{\text{Measured} - \text{Nominal}}{\text{Nominal}} \times 100\%$$

$$V_1 = V \times \frac{R_1}{R_1 + R_2}$$

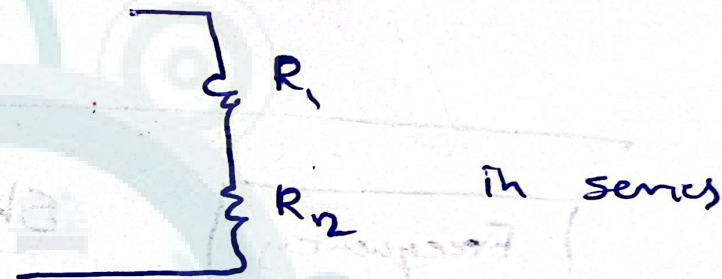

$$I_2 = I \times \frac{R_1}{R_1 + R_2}$$

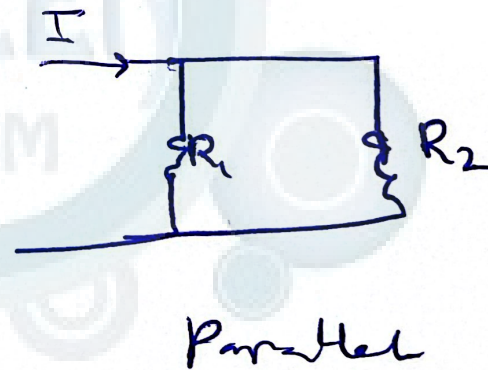

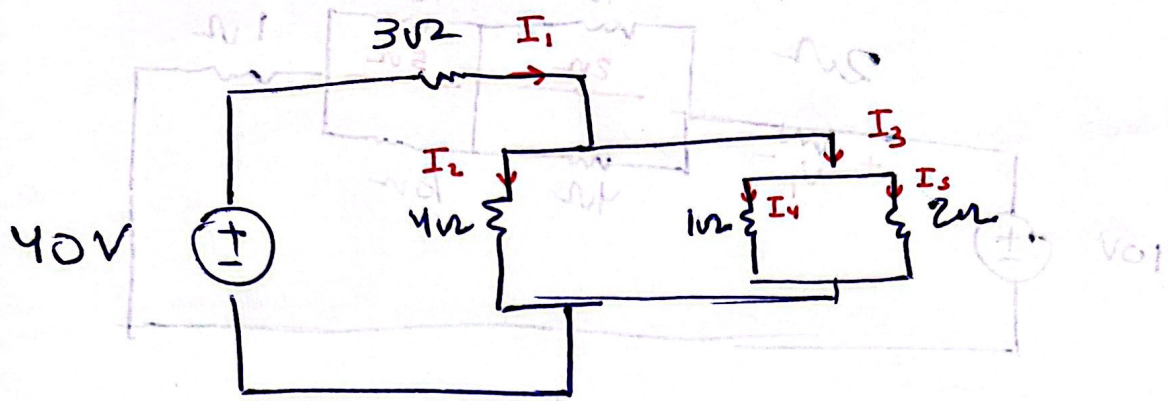

$$I_1 = \frac{40}{3.57} = 11.2 \text{ A}$$

$$I_2 = 11.2 \times \frac{2/3}{4 + (2/3)} = 1.6 \text{ A}$$


$$I_3 = I_1 - I_2 = 9.6 \text{ A}$$

$$I_3 = 11.2 \times \frac{4}{4 + \frac{2}{3}} = 9.6 \text{ A}$$

$$I_4 = 9.6 \times \frac{2}{2+1} = 6.4 \text{ A}$$

$$I_5 = I_3 - I_4 = 3.2 \text{ A}$$
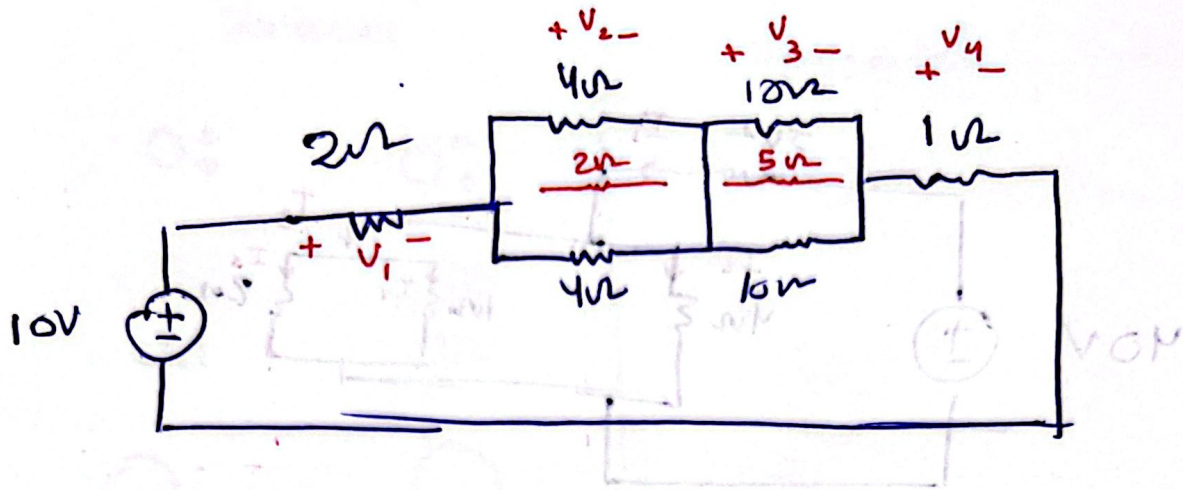
$$I_5 = 9.6 \times \frac{1}{3} = 3.2 \text{ A}$$



$$V_1 = 10 \times \frac{2}{2+8} = 2V$$

$$V_2 = 10 \times \frac{2}{10} = 2V$$


$$V_3 = 10 \times \frac{5}{10} = 5V$$

$$V_4 = 10 \times \frac{1}{10} = 1V$$


$$V_1 + V_2 + V_3 + V_4 = 10$$

$$2 + 2 + 5 + 1 = 10V \checkmark$$

① Capacitors

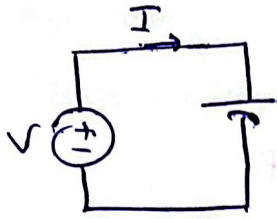

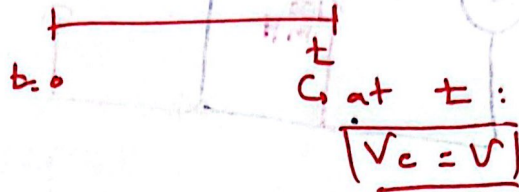
$$V(t) = \frac{Q(t)}{C}, \quad C: \text{constant}$$




$$V_c = V = \frac{Q_t}{C} \quad \text{constant}$$

V becomes constant

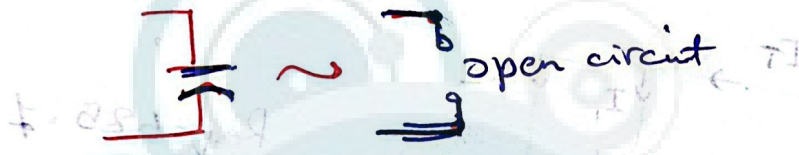$Q_t \rightarrow$ should become constant too





② Inductors


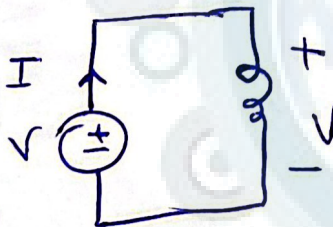


$$V_L = L \frac{di}{dt} \rightarrow V_L = V$$

constant L alternating current

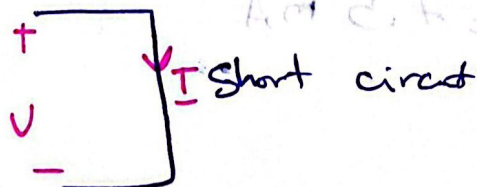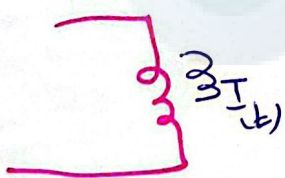When $(V_L = V)$ $I \rightarrow$ becomes constant



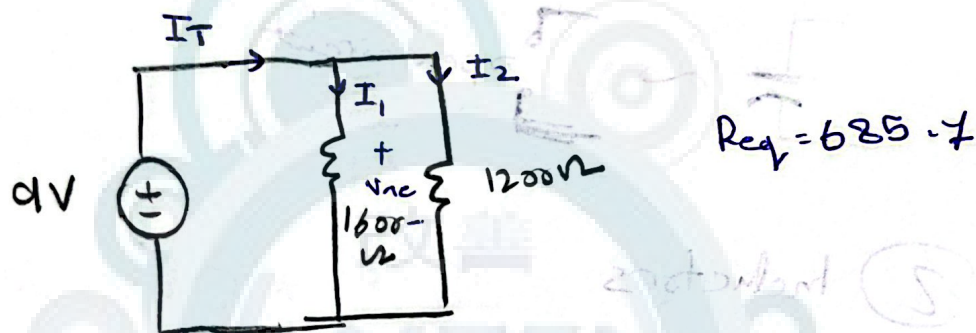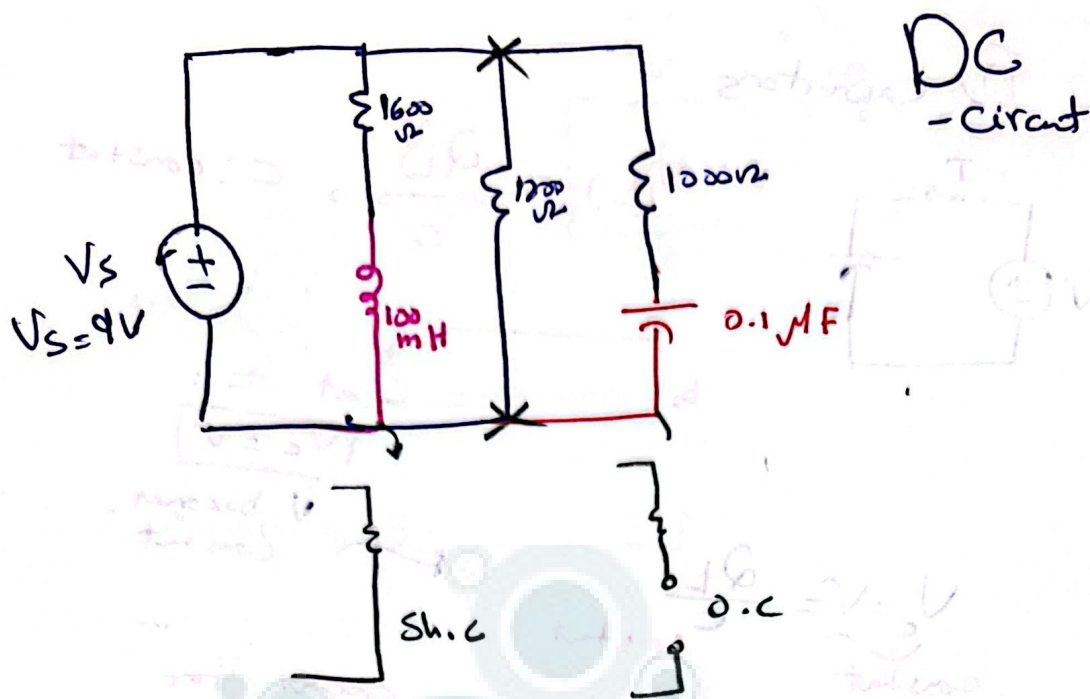

$$V_{ae} = 9V$$

$$I_T = 0.013125 A$$


$$I_1 = 5.625 \times 10^{-3} A = 5.625 mA$$

$$I_2 = 7.5 mA$$

Nodal & Mesh Analysis

to find
Node-Voltages

to find
Mesh-currents

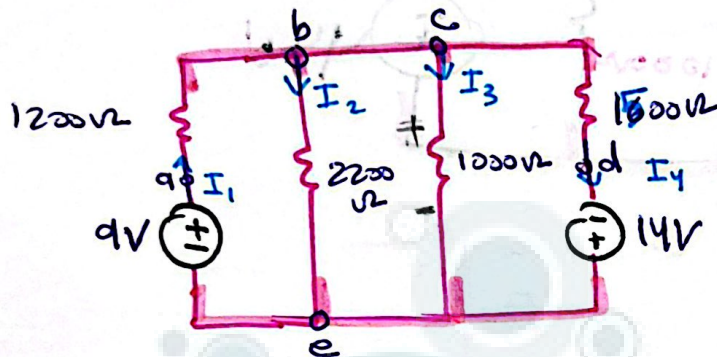

$$V_{R3} = 1000 \times I_3$$

$$-V_{R3} = -1000(I_3)$$

$$I_1 - I_2 - I_2 - I_4 = 0$$

$$-9 + 1200(I_1) + 2200(I_2) = 0$$

$$-2200 I_2 + 1000 I_3 = 0$$

$$-14 + 1000 I_3 + 1500 I_4 = 0$$


$$I_1 = 8.0171 \text{ mA}$$

$$I_2 = -2.82 \times 10^{-4} \text{ A} = -0.282 \text{ mA}$$

$$I_3 = -6.2 \times 10^{-4} \text{ A} = -0.62 \text{ mA}$$

$$I_4 = 8.92 \text{ mA}$$

Mesh
analysis

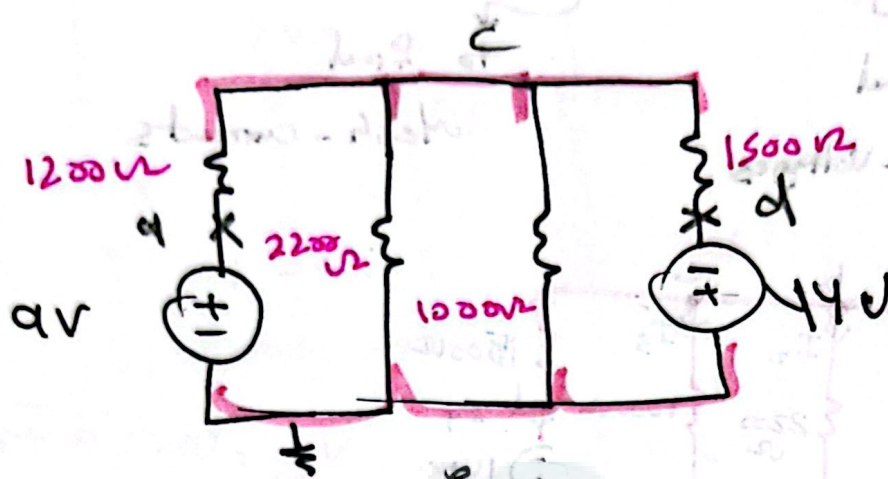

$$V_a = 9V$$

$$V_e = \text{Zero } V$$

$$V_d = -14V$$

$$\frac{-14 - V_c}{1500} + \frac{9 - V_c}{1200} + \frac{-V_c}{2200} - \frac{V_c}{1000} = 0$$


$$\frac{9 - V_c}{1200} + \frac{-V_c}{2200} + \frac{-V_c}{1000} + \frac{-14 - V_c}{1500} = 0$$

$$\frac{-V_c}{1200} - \frac{V_c}{2200} - \frac{V_c}{1000} - \frac{V_c}{1500} = \frac{14}{1500} + \frac{9}{1200}$$

$$V_c \left(\frac{-1}{1200} - \frac{1}{2200} - \frac{1}{1000} - \frac{1}{1500} \right) = \frac{14}{1500} + \frac{9}{1200}$$

$$V_c = -0.62V$$



(KVL)

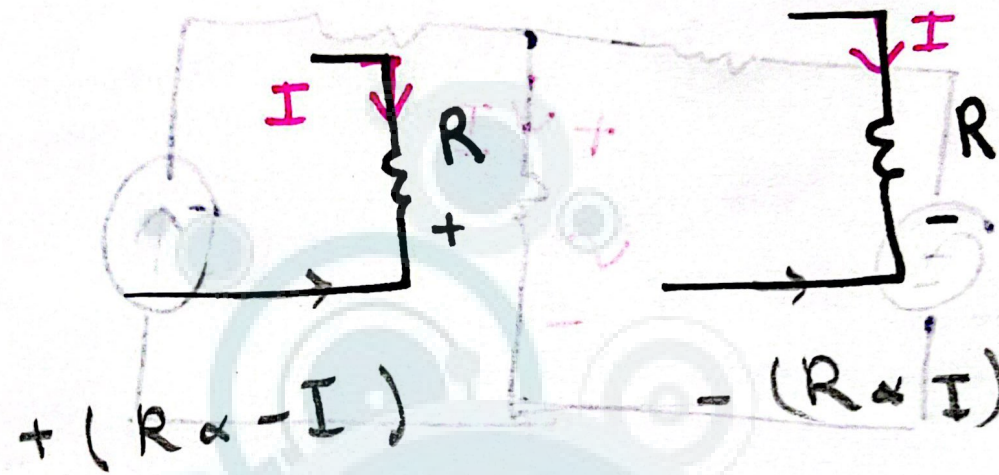

Exp 3

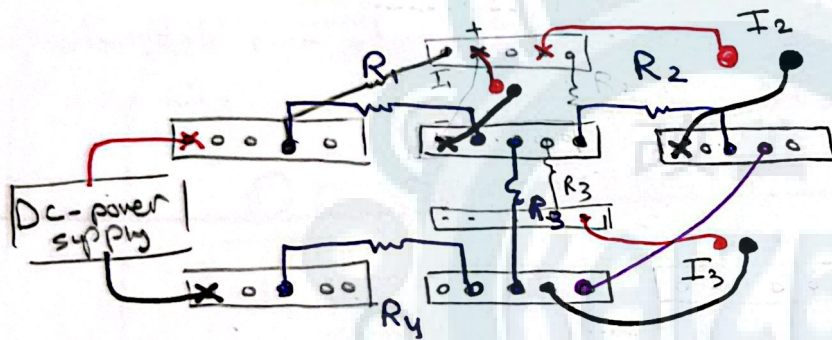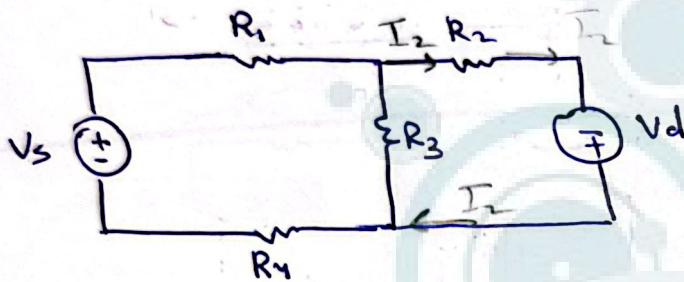
a) Super position

- 1 Kill voltage source \rightarrow short circuit (jumper)
- 2 Kill current source \rightarrow open circuit (gap)




Values
due
to (V_s)
(Kill (V_d))


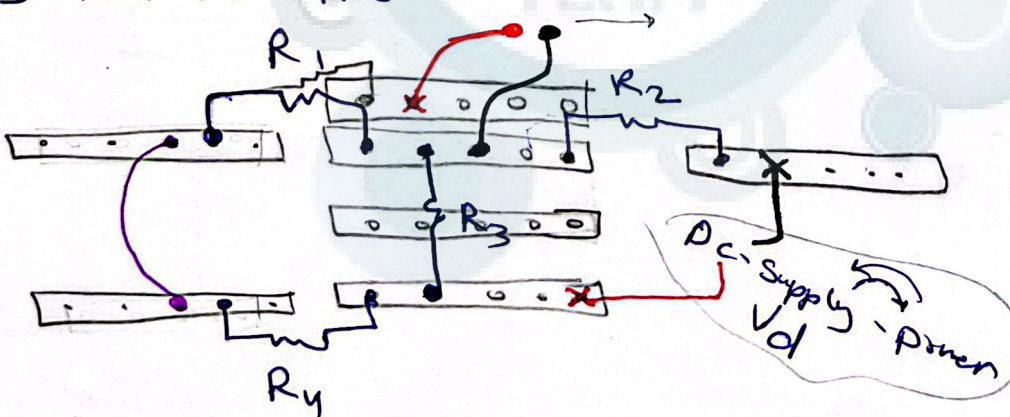
- 1 Form the circuit
- 2 turn the supply on



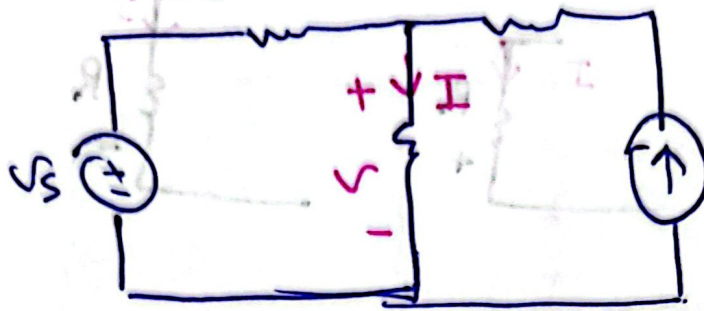
- 1 turn the DC-power-supply off
- 2 Form the circuit
- 3 turn the supply on





① $I = I' + I''$

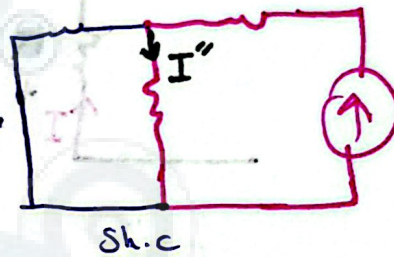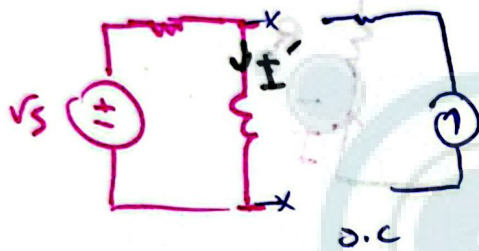


② $V = V' + V''$

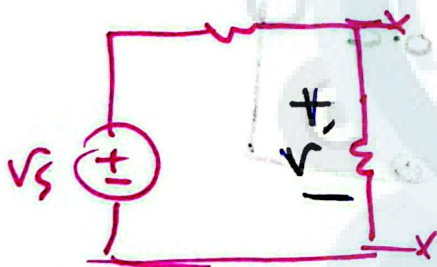

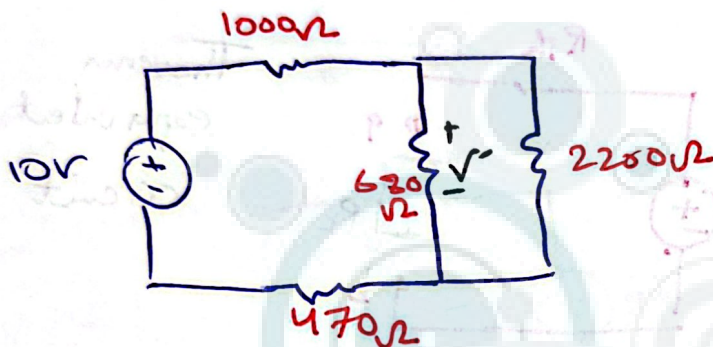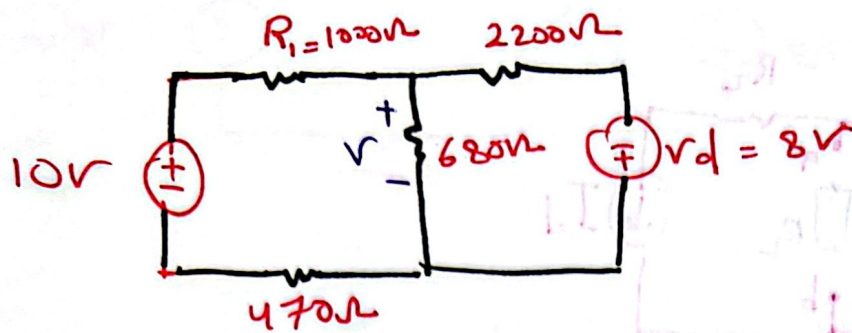



$$V' = 2.611V$$

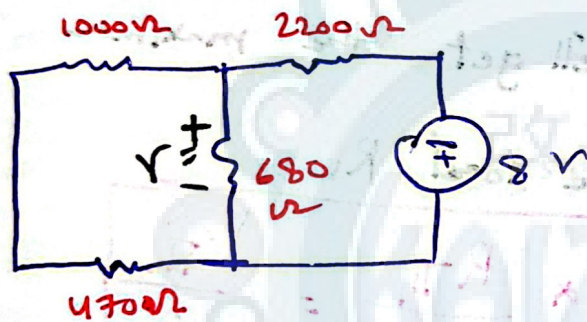

$$V'' = 1.396V$$

$$V = V' + V'' = 4.007V$$

" Thevenin & Norton Theorems "

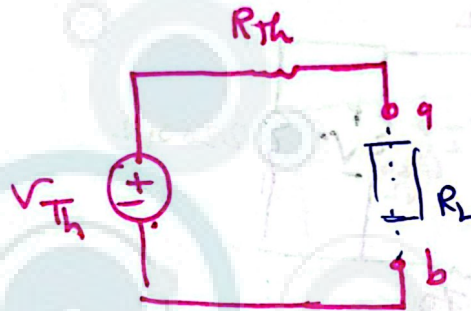
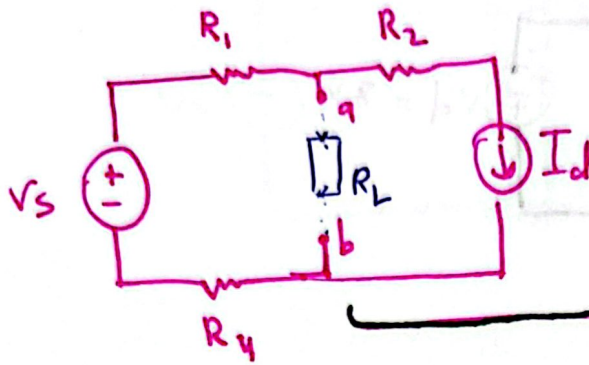


Thevenin
equivalent
circuit


∝ when $(R_L = R_{Th})$ we'll get the maximum power transferred to the load R_L

$$\boxed{R_L = R_{Th}} \Rightarrow \boxed{V_{R_L} = V_{Th} \times \frac{R_{Th}}{2R_{Th}} = \frac{V_{Th}}{2}}$$
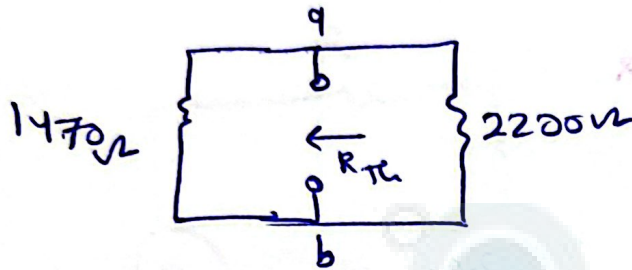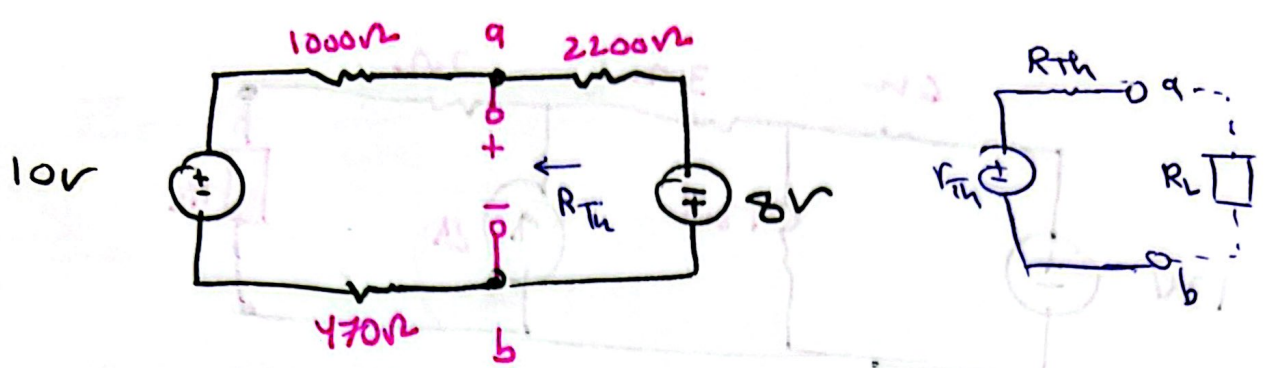
$$P_{(R_L)} = P_{max} = \frac{(V_{Th}/2)^2}{R_{Th}} = \frac{V_{Th}^2}{4R_{Th}}$$



$$R_{Th} = 881.2 \Omega$$

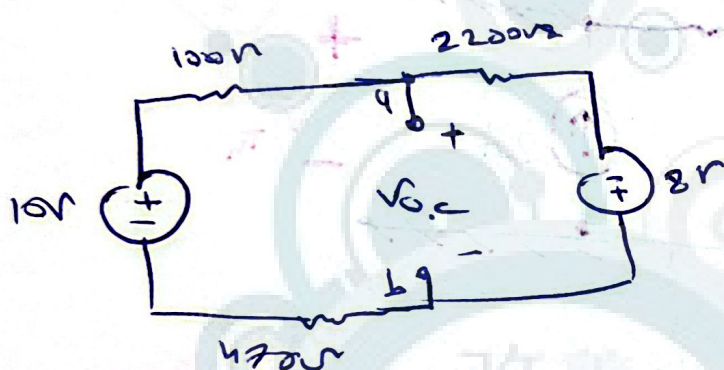

$$-10 + 1000 I + 2200 I - 8 + 470 I = 0$$


$$18 = I (3670)$$

$$I = 4.9 \text{ mA}$$


$$-10 + 1000(4.9 \times 10^{-3}) + V_{0.c} + 470(4.9 \times 10^{-3}) = 0$$

$$V_{0.c} = 2.79 \text{ V}$$

$$P_{max} = 2.2 \text{ mW}$$

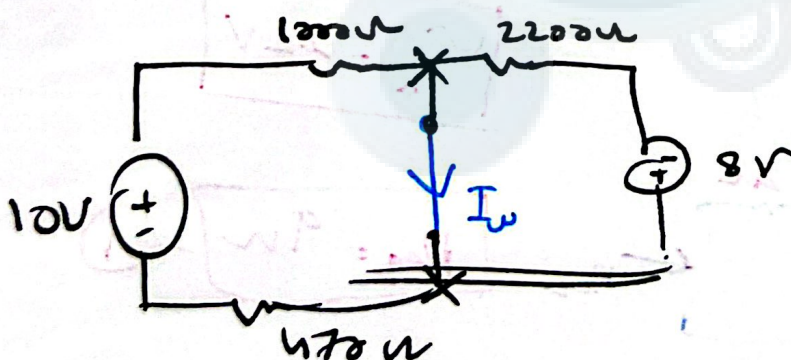


$$I_u = 3.166 \text{ mA}$$

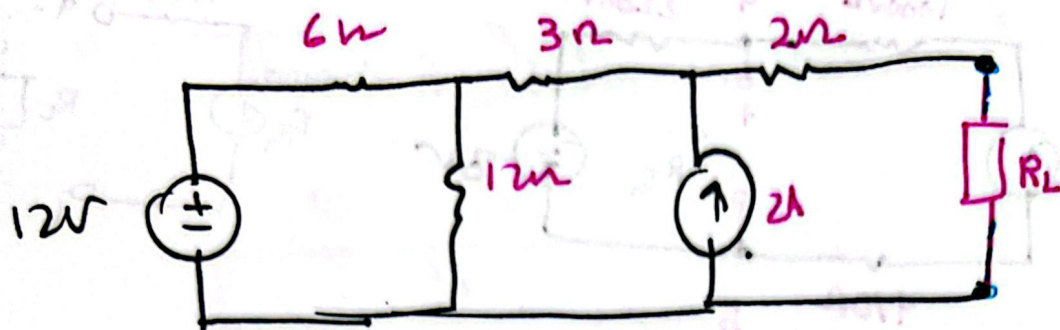

Find R_L & P_{max}

① $V_{Th} :-$

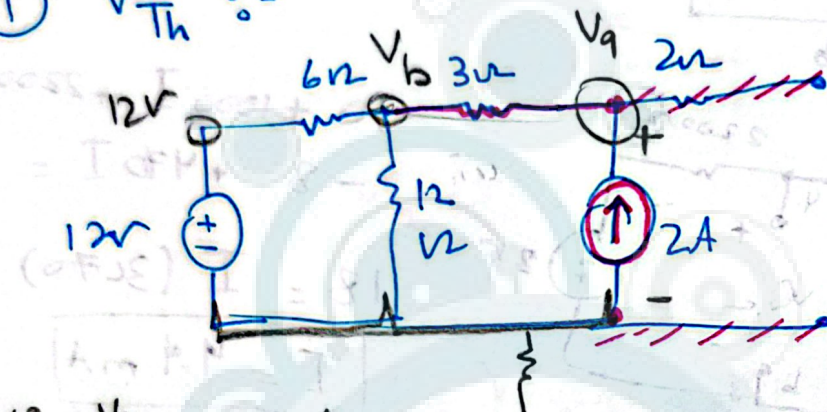

$$\frac{12 - V_b}{6} + \frac{-V_b}{12} + \frac{V_a - V_b}{3} = 0$$


$$2 + \frac{V_b - V_a}{3} = 0$$

$$-\frac{1}{3} V_a + \frac{1}{3} V_b = -2 \quad \text{--- ①}$$

$$\frac{1}{3} V_a + \frac{-7}{12} V_b = \frac{-12}{6} \quad \text{--- ②}$$

$$V_a = 22V$$




$$\boxed{V_{Th} = 22V}$$

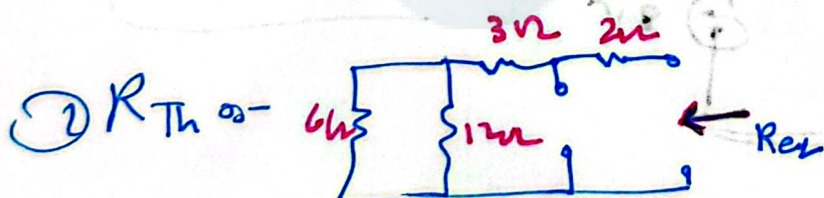

$$\boxed{R_{eq} = 9\Omega} \quad \text{--- ①}$$

$$\boxed{P_{max} = 13.44W}$$


(B) Thevenin & Norton

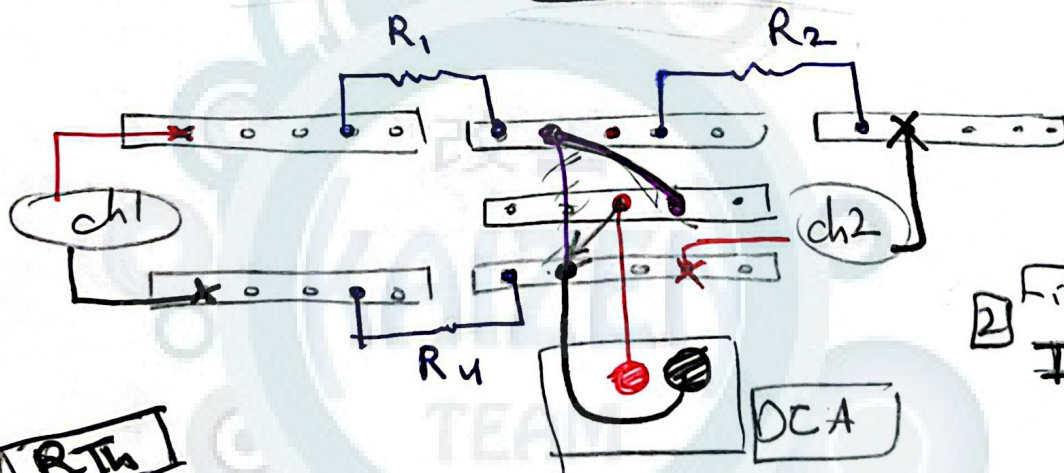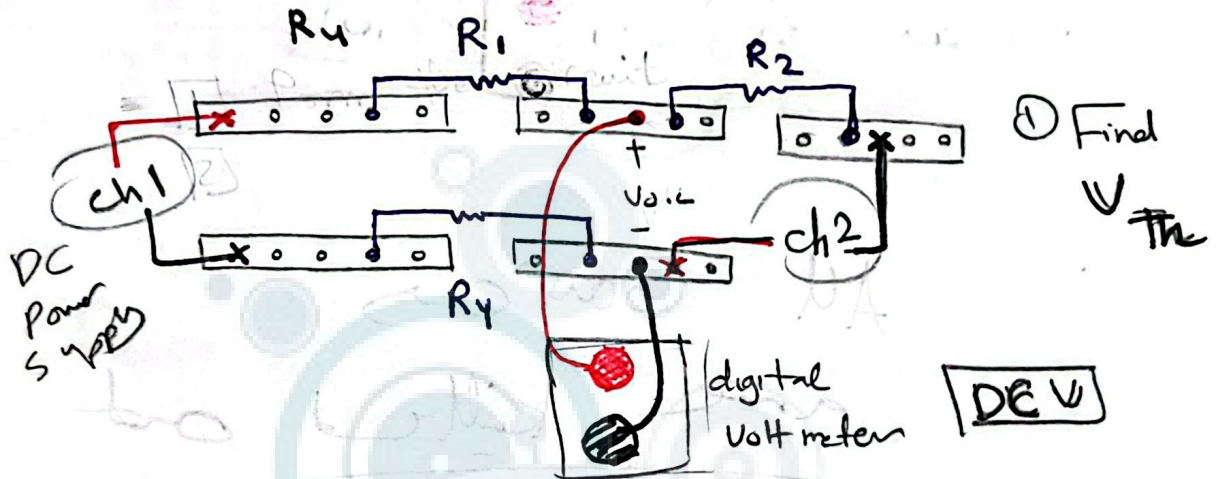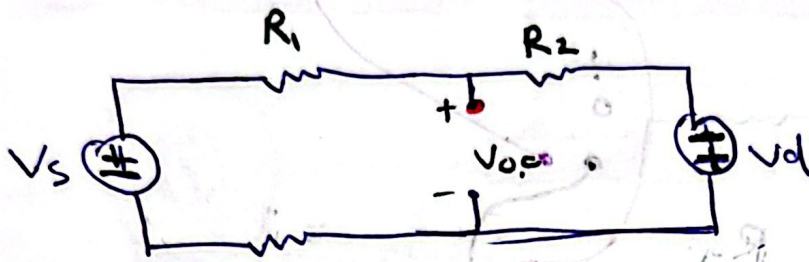

R_{Th}



- 1] turn the supplies off (DC power supply)
- 2] Remove them from the circuit
- 3] put short circuit at the voltages places
- 4] leave the place of current supplies as an open circuit

R_{th}

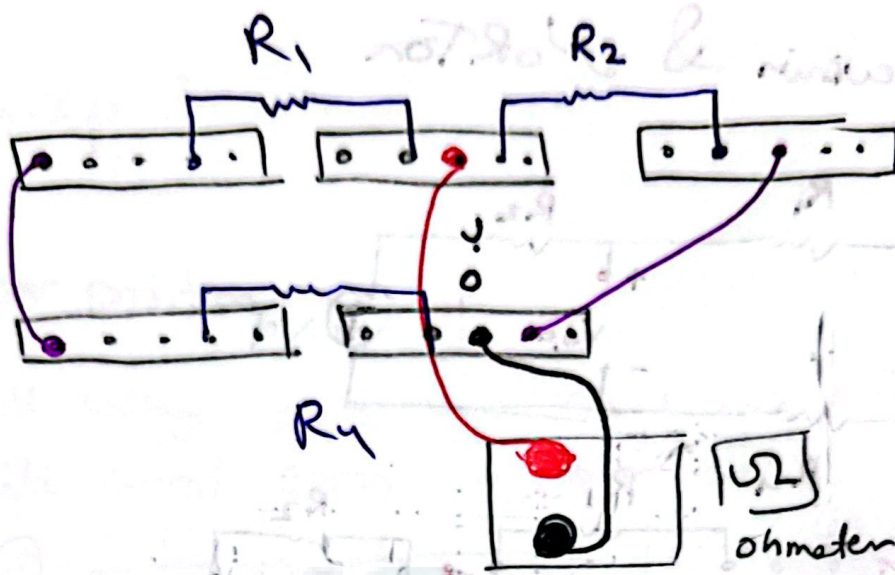



All sources
are killed out

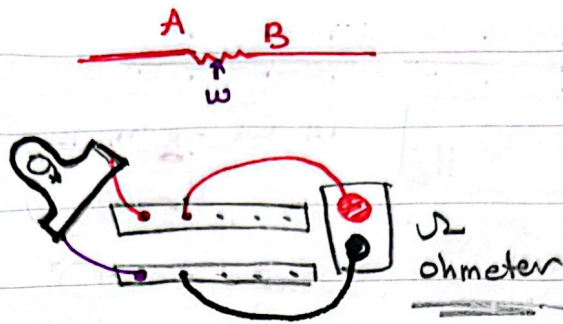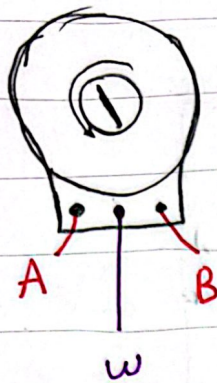[C] Maximum Power Transfer ((potentio-meter))



$$P_{max} = \frac{1}{4} \left(\frac{V_{Th}^2}{R_{Th}} \right)$$



Power Transfer

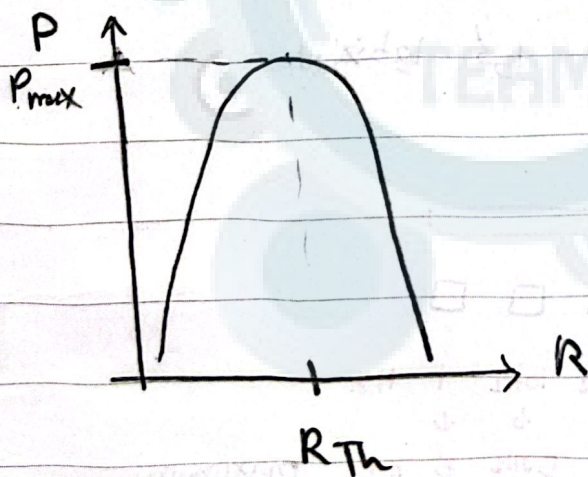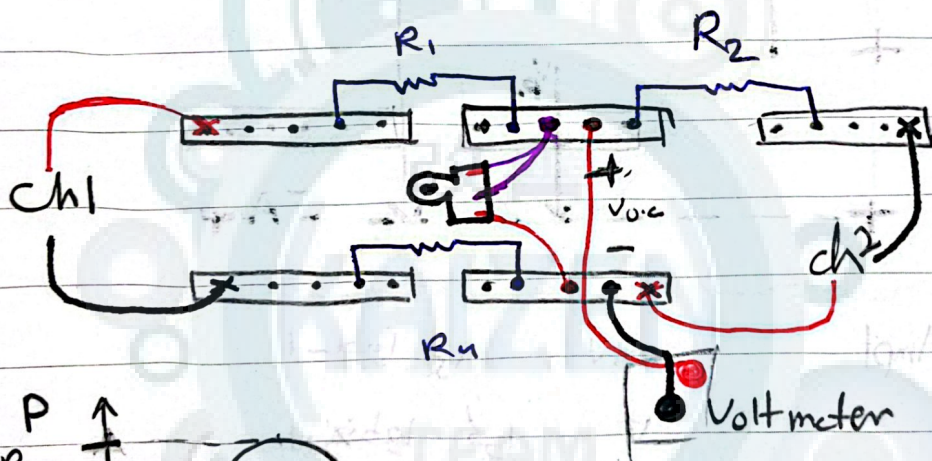


Exp 4

Shape \leftarrow Frequency \uparrow Ampl (+ oscilloscope)

Function Generator (AC - supply)

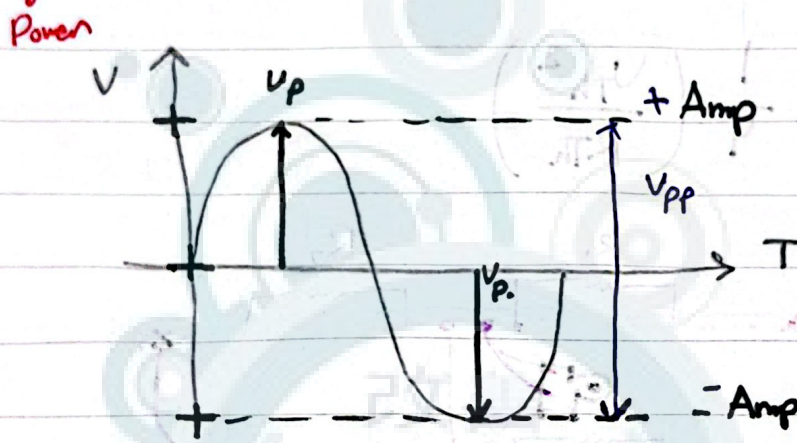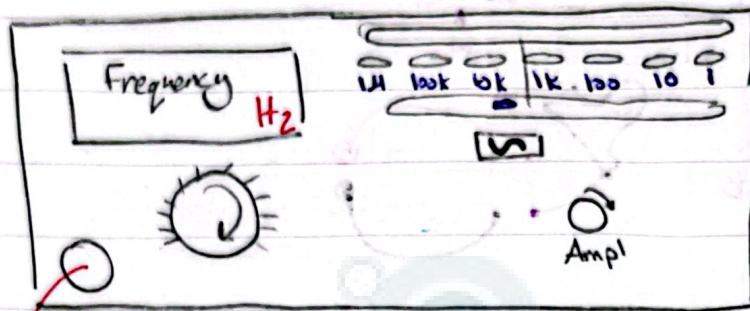

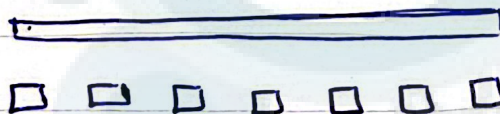Ampl \rightarrow mv \rightarrow احسبها لـ V \rightarrow احسبها لـ



1m 10k 50k 1k 100Hz 10Hz 1 Hz
 $\downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow$
 5m 500k 50k 5K 500Hz 50Hz 5 Hz maximum

① 7 Hz \rightarrow 10Hz



② 0 Hz

800Hz 0-


0.1K

② 0 Hz

{ Oscilloscope }

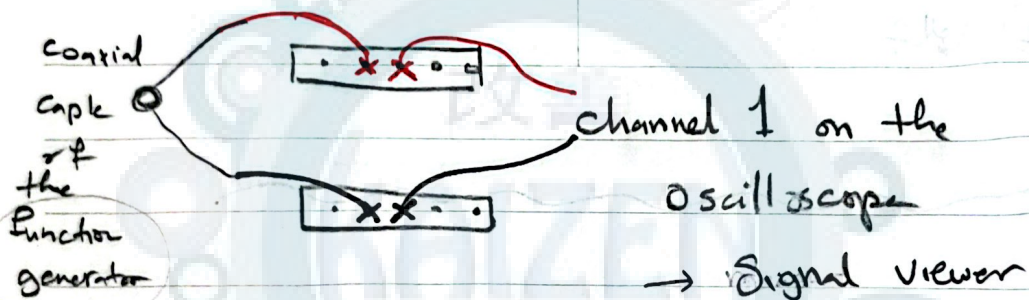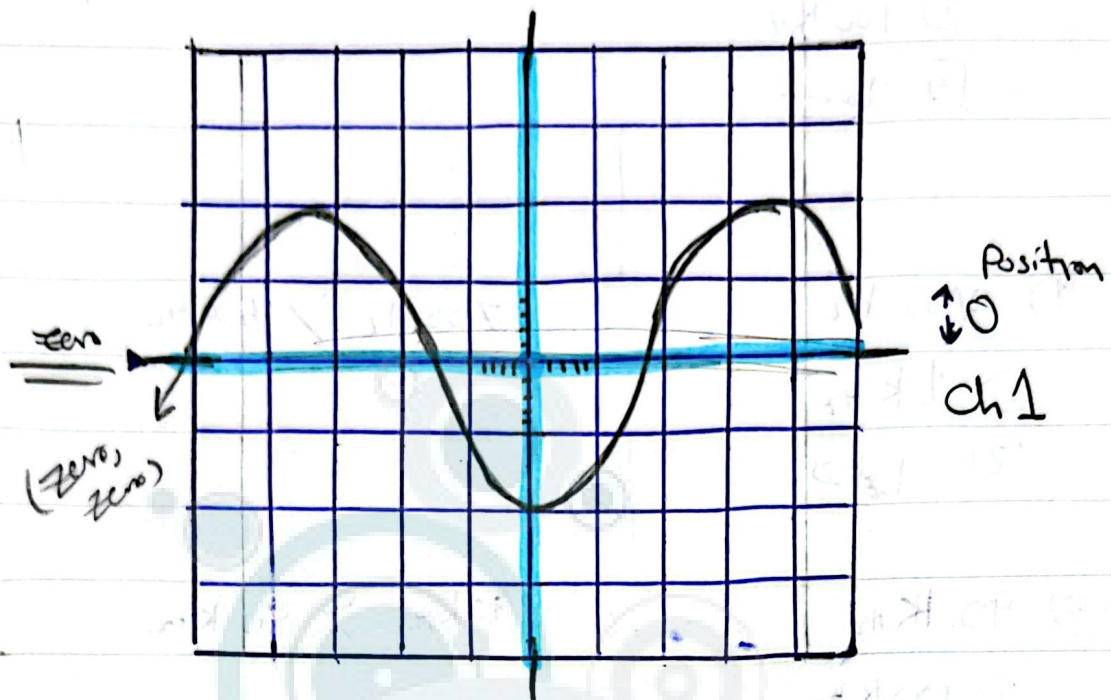

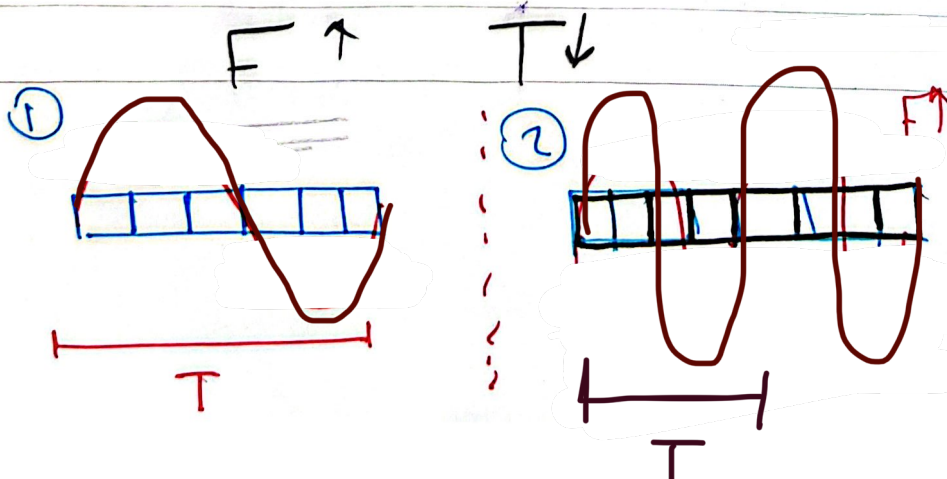- ① Frequency → ~~extension horizontally~~
- ② Shape
- ③ Amplitude → V_{pp} \updownarrow extension vertically



(A-c)
① connect the Oscilloscope parallel to the generator

② set the position at Zero

③ Volt/division

ch1 = 1V/division

1V

④ Time/division


50μs/division

50μs

$$V_{pp} = \text{Scale}_{(ch)} \times \text{no of squares vertically}$$

$$T_{(period)} = \text{Scale}_{(T)} \times \text{no of squares horizontally}$$
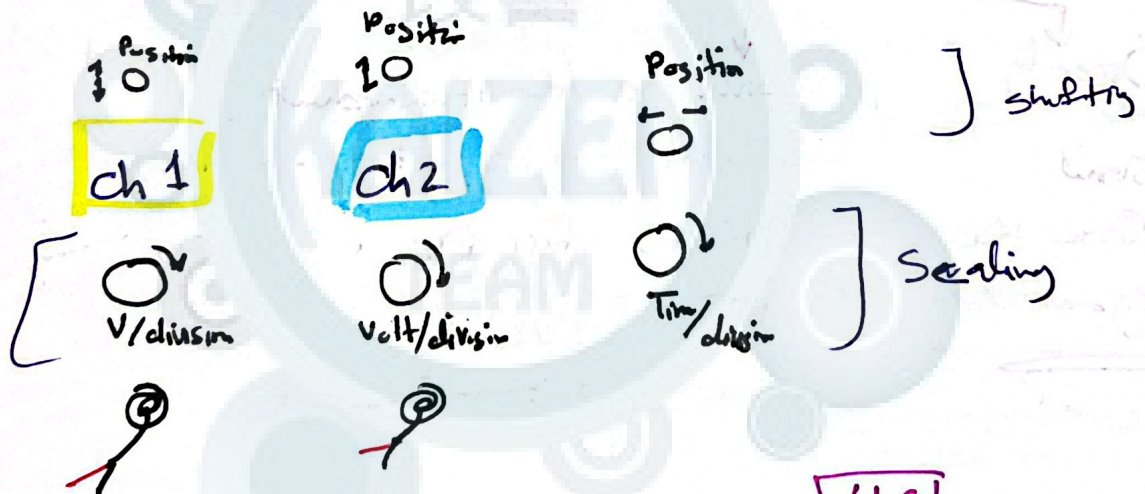
$$F = \frac{1}{T} \text{ or from the Function generator}$$



$$V_p = \frac{V_{pp}}{2}$$


$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

μs
↳ Micro-sec




V _{pp}	
1:	—
2:	—

V _{avg}	
1:	—
2:	—

measure

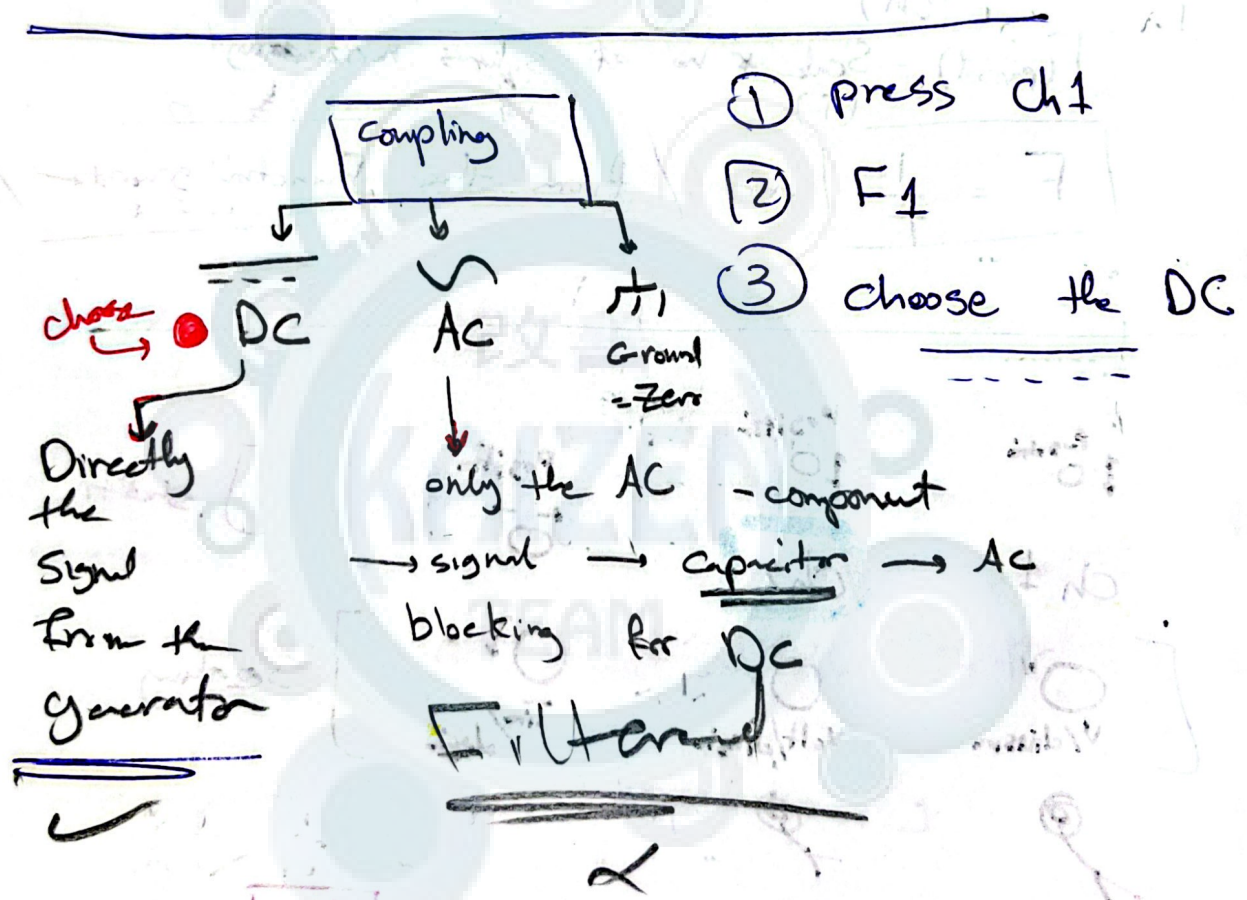


Capacitors (pF)

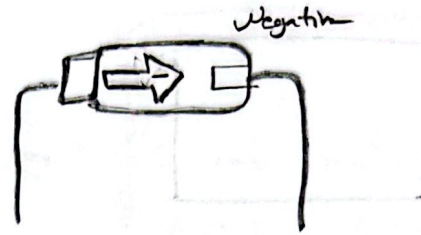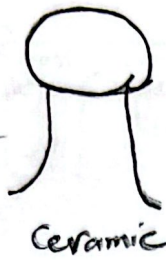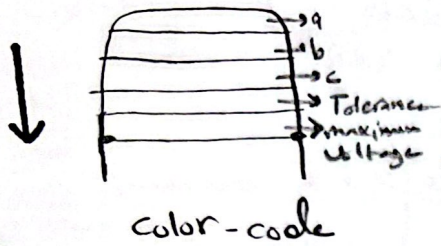


من فوق لعتة
بالألوان

$$a b \times 10^c \pm d \text{ pF}$$

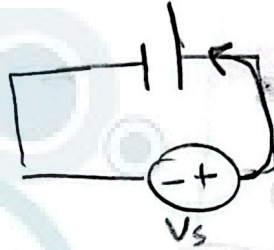

store charge 'till
the $V_{\text{capacitor}} = V_s$
than the $-||-$
will be open circuit
no current returns
the capacitor

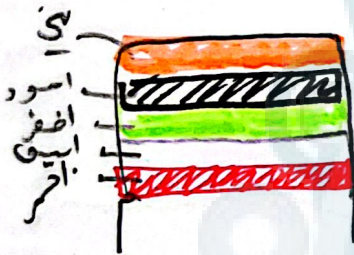

$$10 \times 10^5 \text{ pF} \%$$


$$10 \times 10^5 \times 10^{-12} \text{ F pF}$$

$$1 \times 10^{-6} \text{ F} = 1 \mu\text{F}$$


$$\text{Tolerance} = 10\%$$

$$C = \underline{1 \mu\text{F} \pm 10\%} \text{ Nominal}$$

RLC - Meter

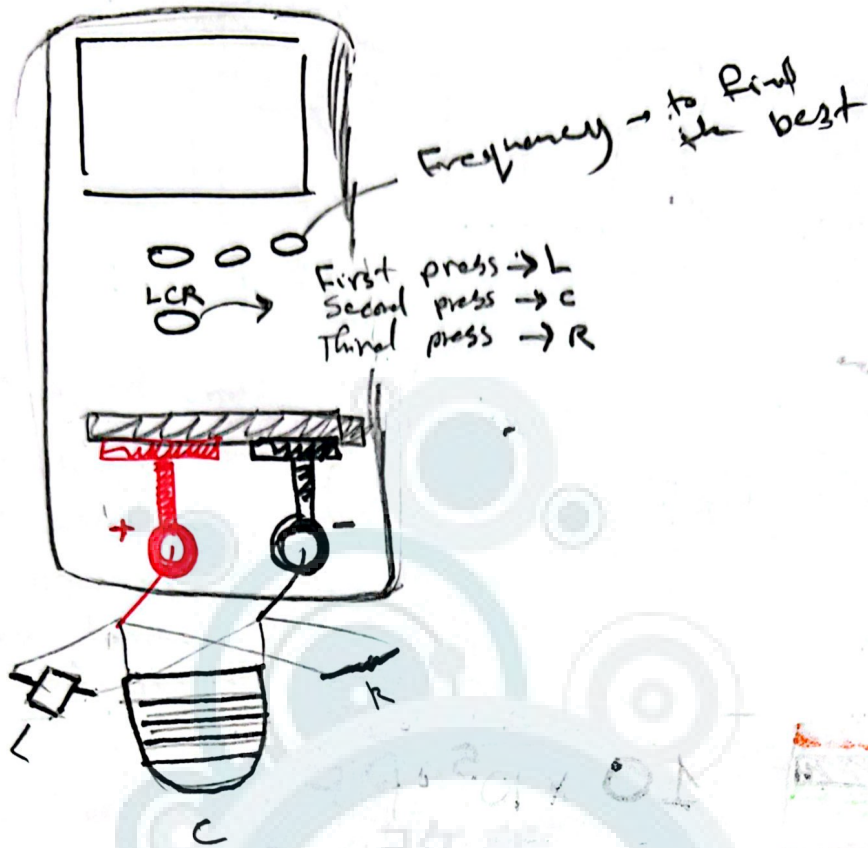

[2] Inductor :- (mH)

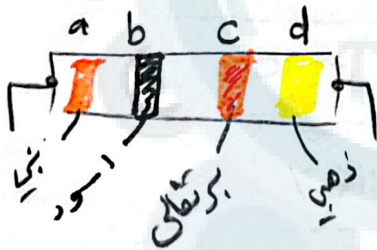

$$ab \times 10^c \pm d \text{ mH}$$


$$10 \times 10^3 \pm 5\% \text{ mH}$$

$$10^4 \times 10^{-6} \text{ H} \pm 5\%$$


$$L = 10^{-2} \text{ H} \pm 5\% \text{ H}$$

$$L = 10 \pm 5\% \text{ mH}$$

$$L = 10 \pm 0.5 \text{ mH}$$

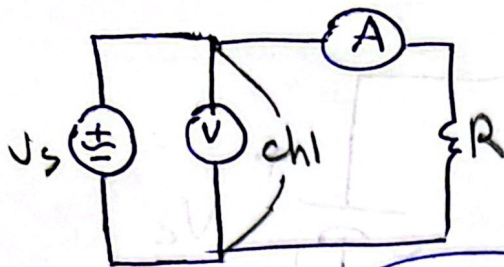

$R = 3300 \Omega$
 امر سکتا ہے

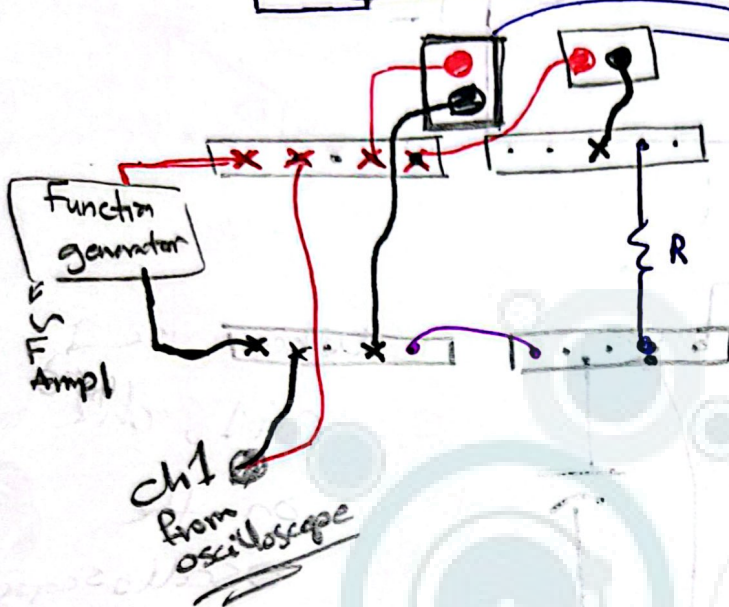

digital multimeters


ACA, ACV $\rightarrow V_{rms}$

PCA, PCU $\rightarrow V_{avg}$

$F \uparrow$ $T \downarrow$

R is constant, V_{rms} , I_{rms}
 \rightarrow constant



$C, L \rightarrow$ variation

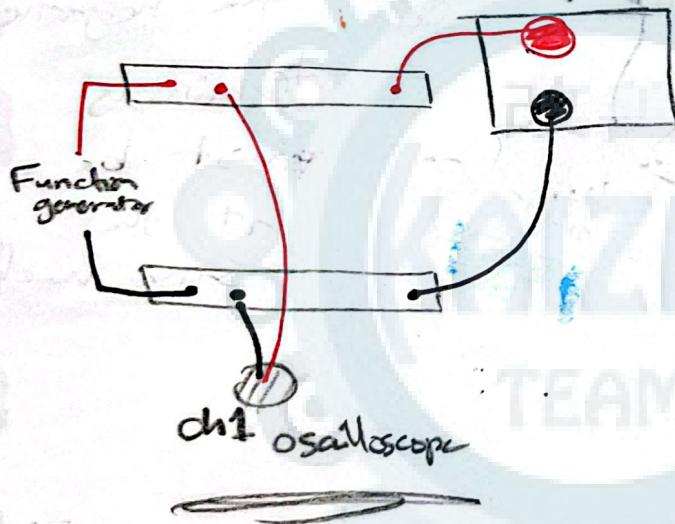


ACU
 $\rightarrow V_{rms}$

$F \uparrow$




$T \downarrow$ $\rightarrow C, L$

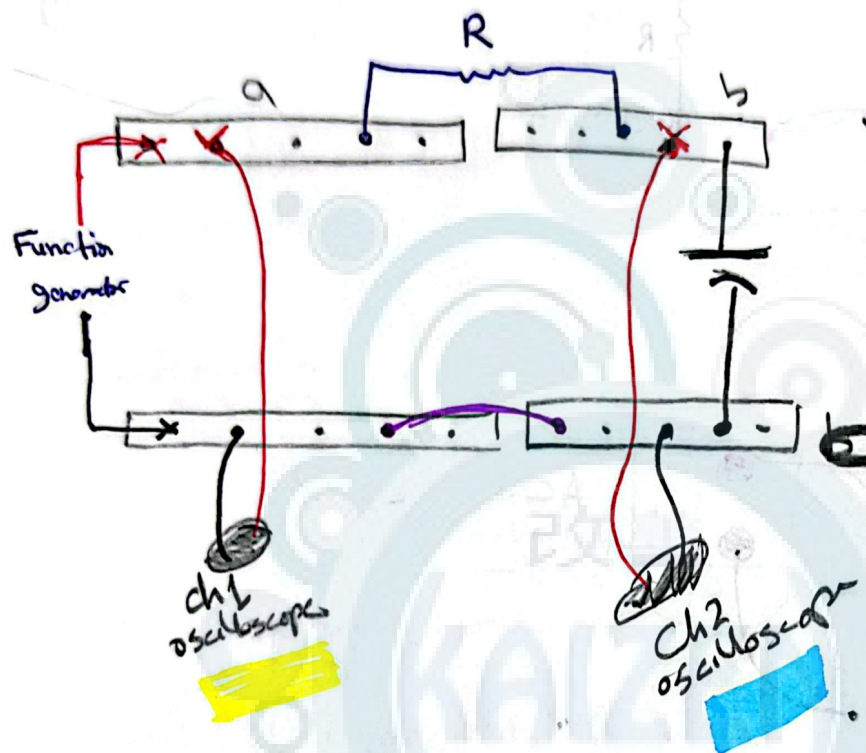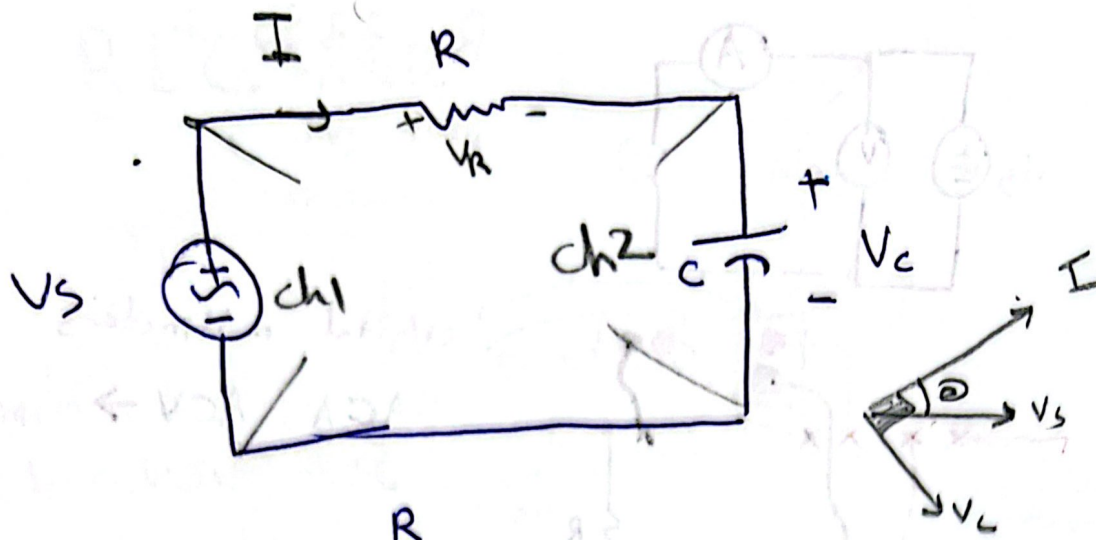

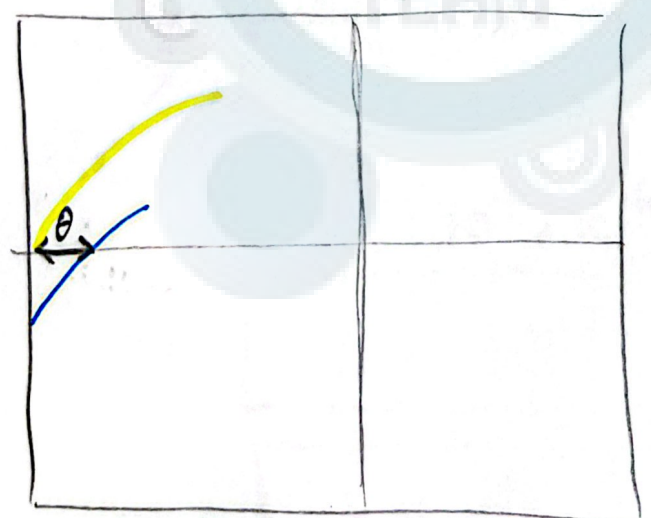When use
ch1, ch2
on the
Oscilloscope
the negative
terminals
must be
at the
same node





Capacitor
lags the supply -- by θ

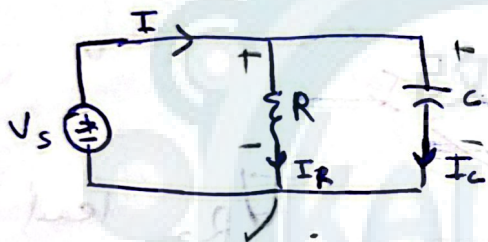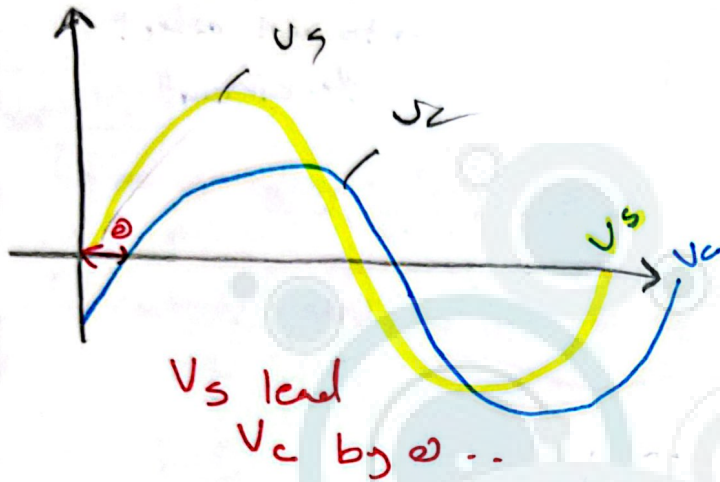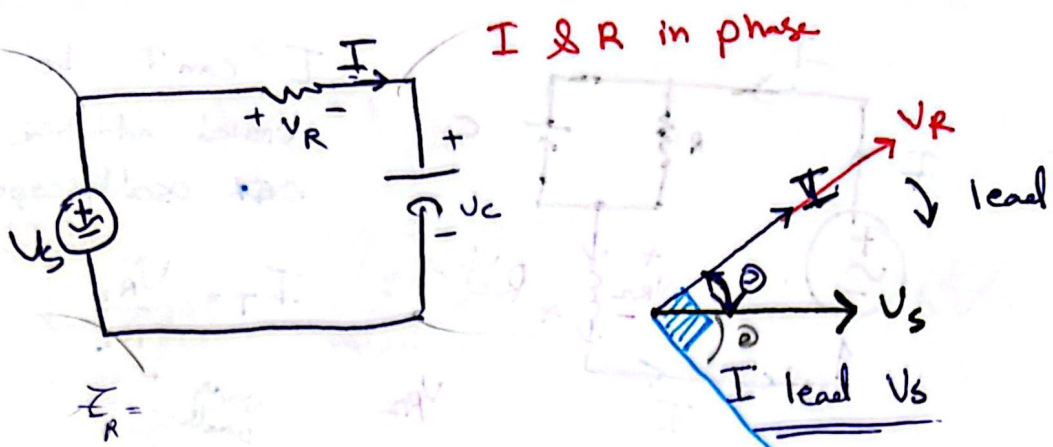


$$|V_s = V_R = V_C|$$

I_R & V_R in phase

$$I = I_R + I_C$$

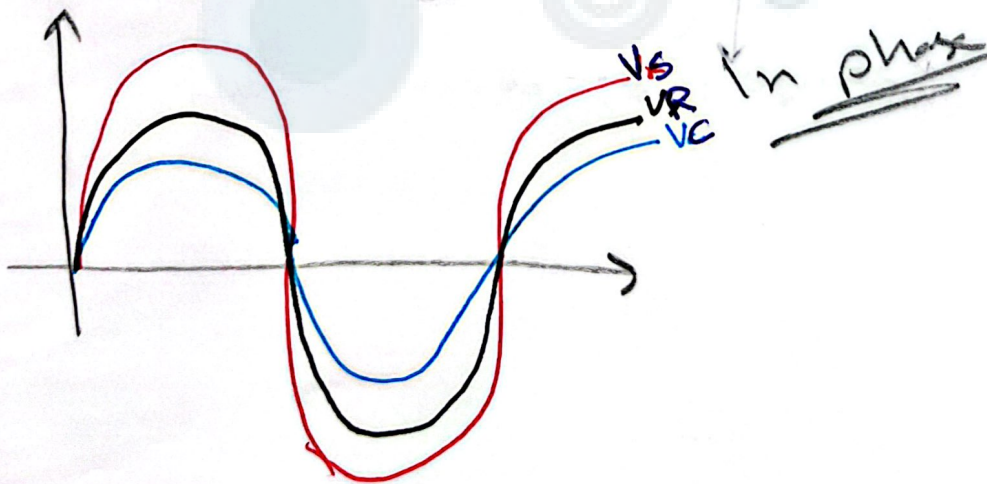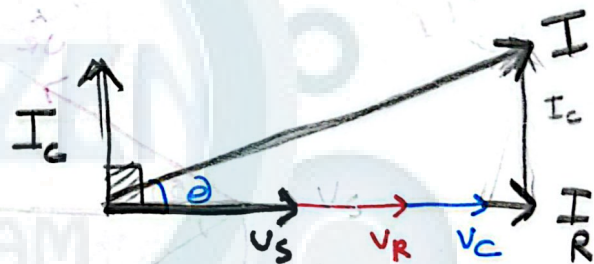

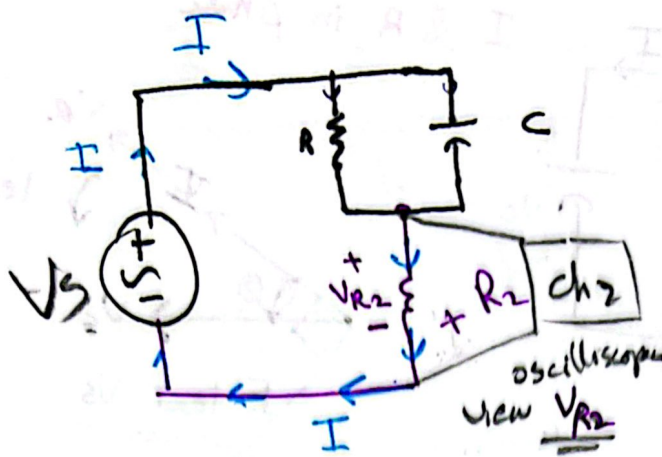

I can't be
viewed at the
oscilloscope -

$$I_T = \frac{V_{R_2}}{R_2}$$

very
small...


→ to not affect
the circuit

$$V_{R_2} = I_T R_2$$


In phase

$$\phi_R = 0$$

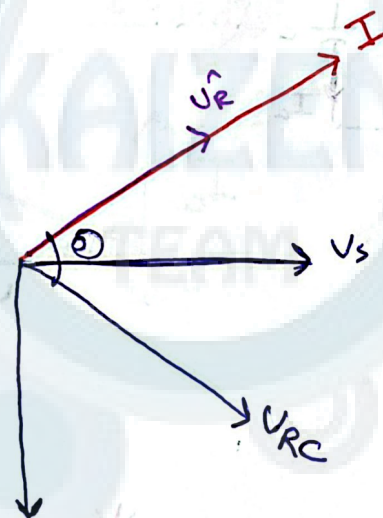ای تیار پر ر مقاومت
نہیں ہوتا In phase ہوتا
ف you can find ϕ_I by ϕ_V




V_{R_2} lead
 V_s

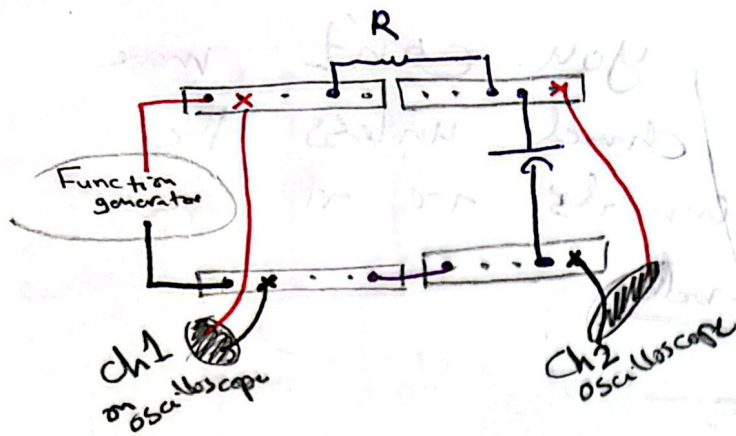


$$V_{pp} = 10V$$

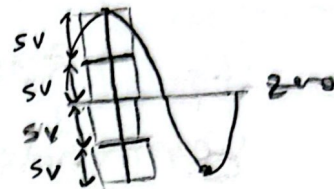↳ no of squares $\times V_{ch1} = 10V$
P-P



$$V_{pp} = 10$$

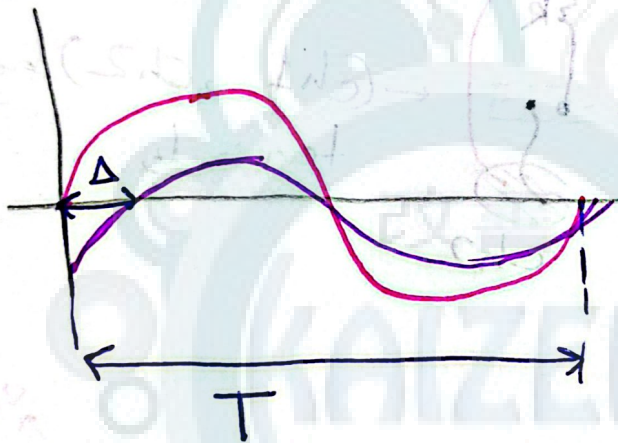↳ control it by Amp1 on the function generator



$$\phi = \frac{360^\circ \times (\Delta \text{ divisions})}{(T \text{ divisions})}$$

$$T (\text{divisions}) \rightarrow 360^\circ$$



$$\Delta (\text{in divisions}) \rightarrow \phi$$

phase shift

divisions \rightarrow no. of squares


✗ Remember you can't move
 The other channel unless the
 negative terminals are at the
same node

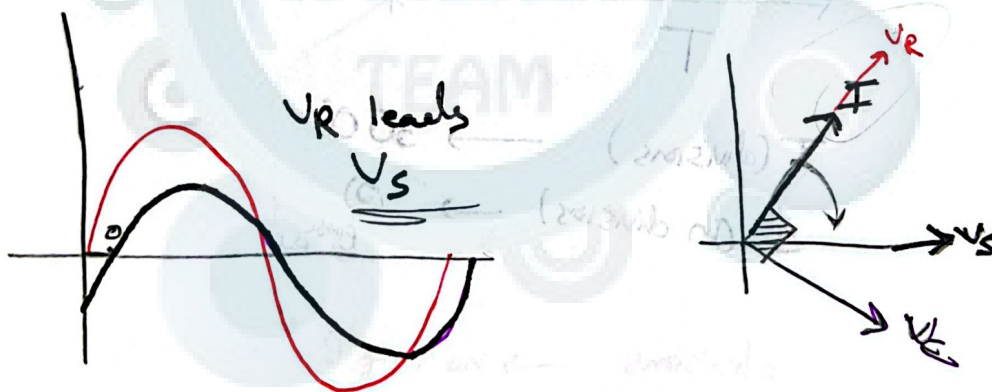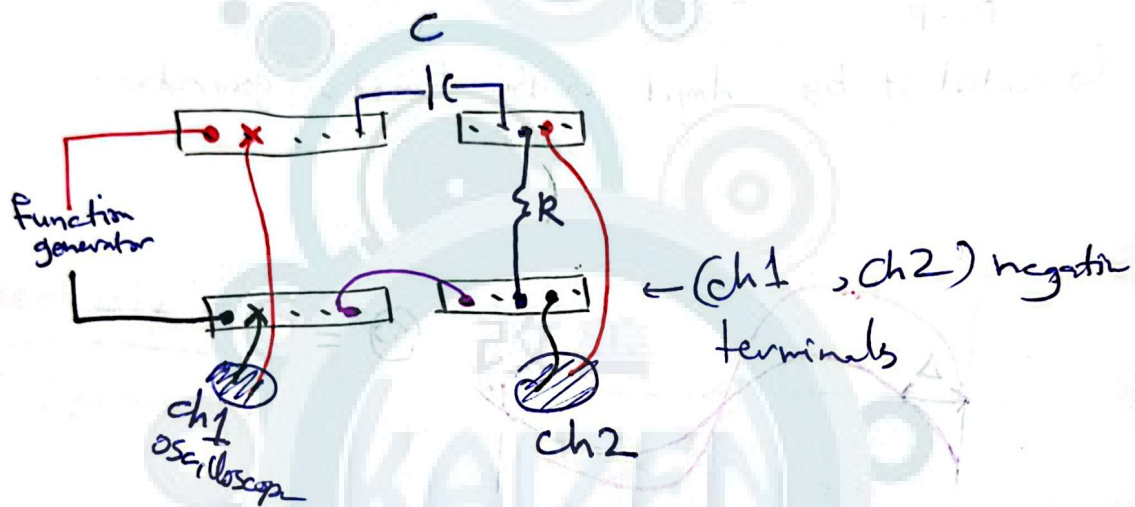→ So to find V_R move
 the Resistor not the channel
 terminals



$$\phi = \frac{360^\circ \times T_d}{\Delta t}$$

$F \downarrow$	$T \uparrow$	expansion
$F \uparrow$	$T \downarrow$	compression

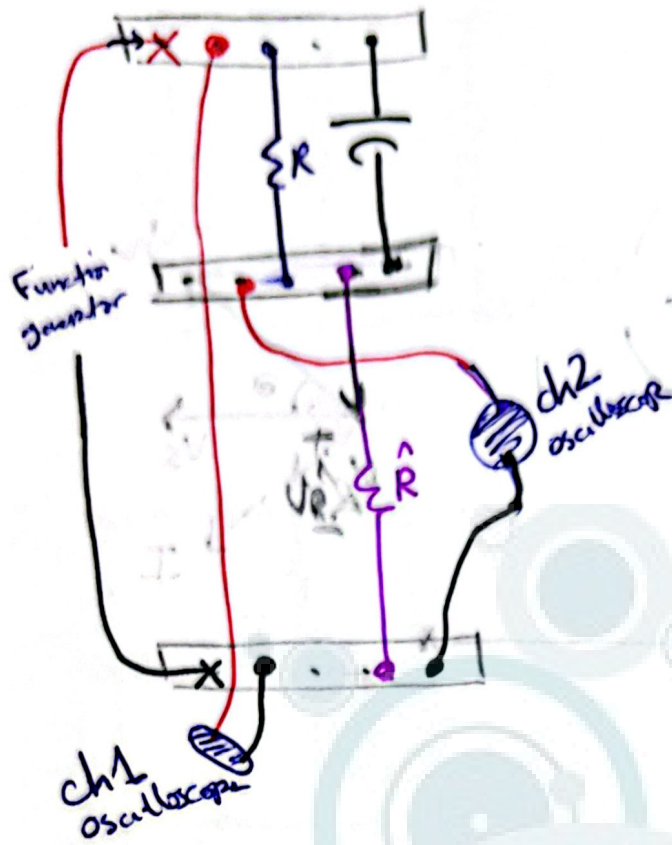

V_R in phase I

ch2 // \hat{R}
 ↳ to view \hat{V}_R
 ↳ determine ϕ_I
 ↳ $\phi_I = \phi_{V_R}$

改善


KAIZEN

TEAM

*

$$Z_c = \frac{1}{\omega c} \angle -90^\circ$$
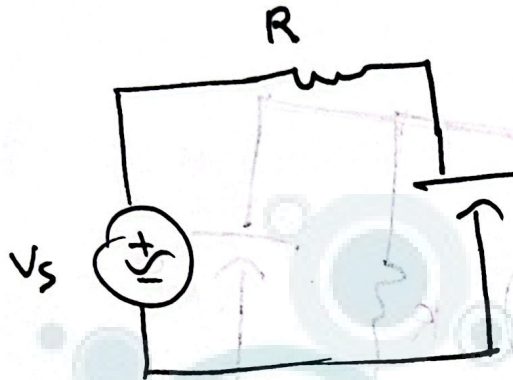
$$Z_c = -j \left(\frac{1}{\omega c} \right)$$




$$Z = Z_R + Z_c$$

$$Z = R - j \frac{1}{\omega c}$$


$$|Z| = \sqrt{R^2 + \left(\frac{1}{\omega c} \right)^2}$$

$$R = |Z| \cos \theta$$

$$|Z| \sin \theta$$

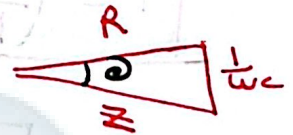

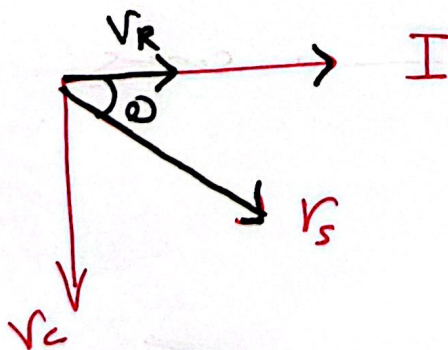
$$\theta = \tan^{-1} \left(\frac{1}{\omega c R} \right)$$



Admittance $\left(\frac{1}{Z}\right)$

$$R \rightarrow \frac{1}{R} (S)$$

$$ZC \rightarrow \omega C$$

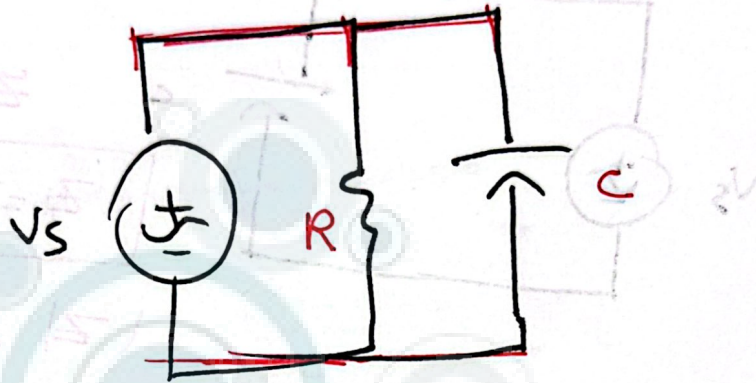


$(R \parallel C)$

$\rightarrow \left(\frac{1}{R} \text{ series with } \omega C\right)$

$$\rightarrow |Y| = \sqrt{\left(\frac{1}{R}\right)^2 + (\omega C)^2}$$

$$Y = \frac{1}{R} + j\omega C$$

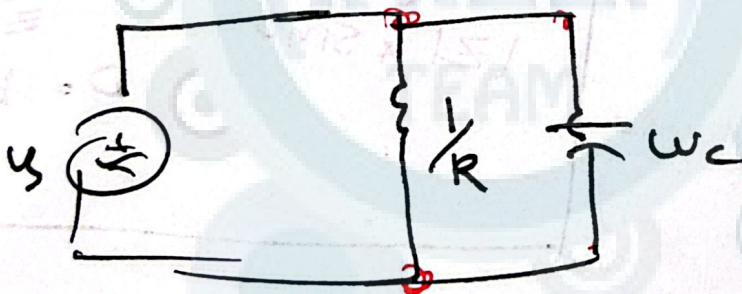

Series \rightarrow Parallel

Parallel \rightarrow Series

$$P = V * I \quad \sim \text{In DC}$$

$$P(t) = V(t) * I(t) \quad \sim \text{AC}$$

Real power :- (P_{avg})


$$P = \frac{1}{2} V_p I_p \cos(\omega_r - \omega_i)$$

$$= V_{rms} * I_{rms} * \cos(\omega_r - \omega_i) \quad (\underline{\underline{W}})$$

Reactive Power :- (Q)

$$Q = V_{rms} * I_{rms} * \sin(\omega_r - \omega_i) \quad (\underline{\underline{VAR}})$$
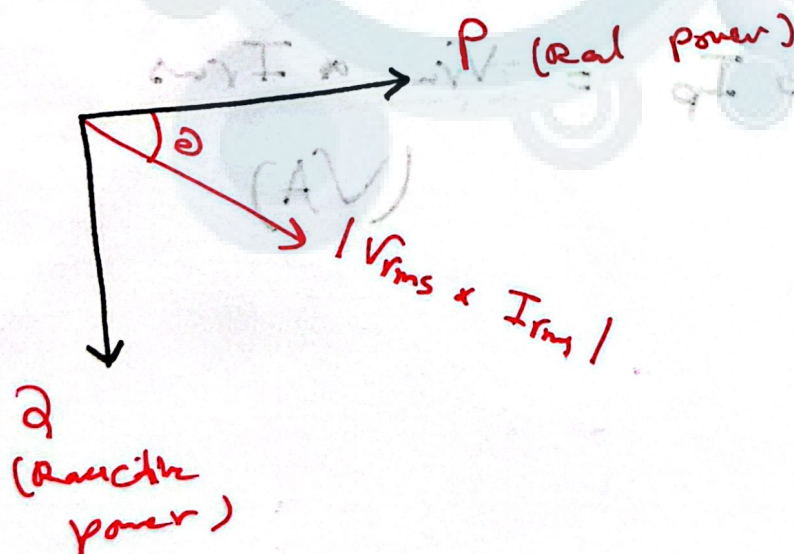
$$= \frac{1}{2} V_p I_p \sin(\omega_r - \omega_i)$$



$$\vec{S} = P + j Q \quad (\text{VA})$$

$$= V_{\text{rms}} \times I_{\text{rms}} \angle (\phi_v - \phi_i)$$

$$|\vec{S}| = S \text{ (Apparent power)}$$


$$\vec{S} = \frac{1}{2} V_p \times I_p \angle (\phi_v - \phi_i)$$

$$\text{PF} = \cos (\phi_v - \phi_i) \quad (\text{Power Factor})$$

\swarrow lagging (Inductive)
 \searrow leading (Capacitive)

$$S = \frac{1}{2} V_p I_p = V_{\text{rms}} \times I_{\text{rms}} \quad (\text{VA})$$

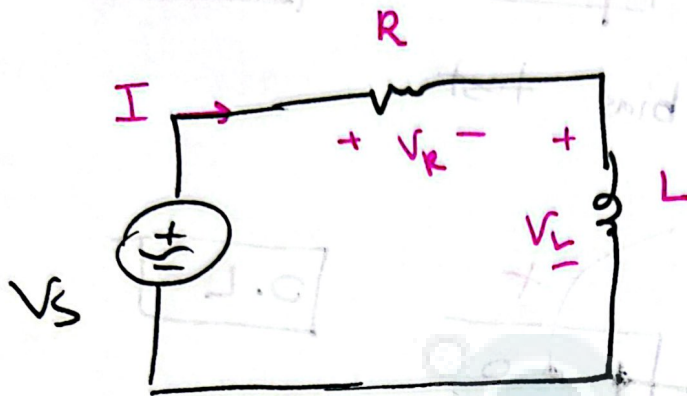
$$Z_L = \omega L \angle 90^\circ = j\omega L$$



$$Z_L = j\omega L$$


$$Z = Z_R + Z_L$$

$$= R + j(\omega L)$$


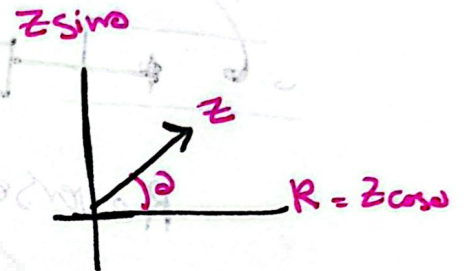



$$Z = \sqrt{(\omega L)^2 + R^2} \angle \phi$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

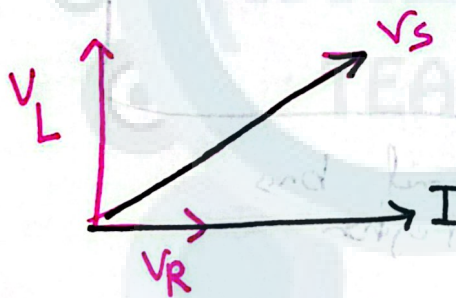

Exp 6

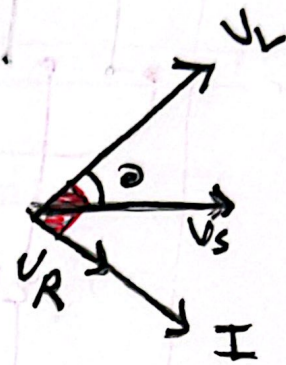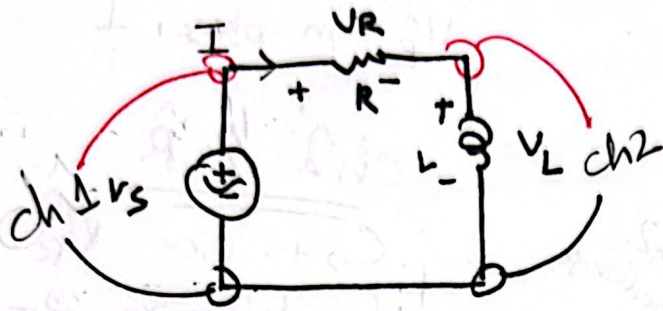


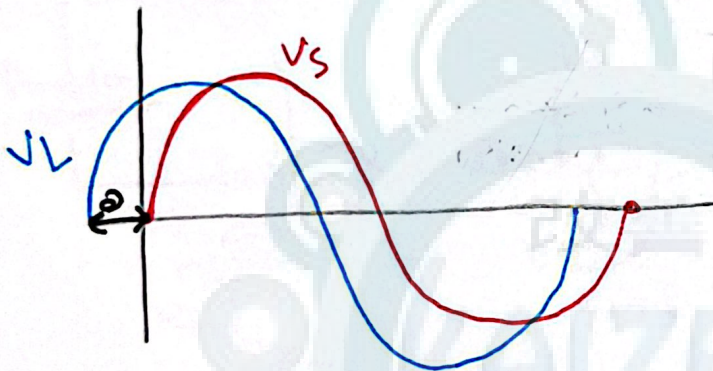

V_L lags V_S

V_S lags V_L

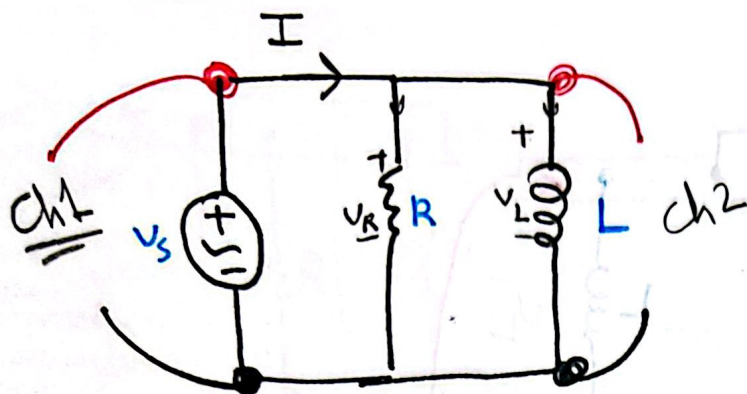
② depends on the frequency of the supply.




$$I_R + I_L = I$$

$$V_S = V_R = V_L$$

I_R in phase V_R

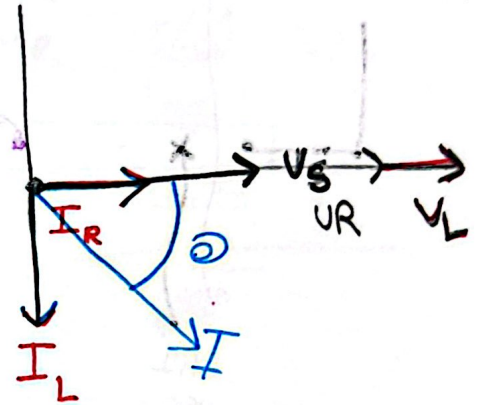


V_S lead I by θ

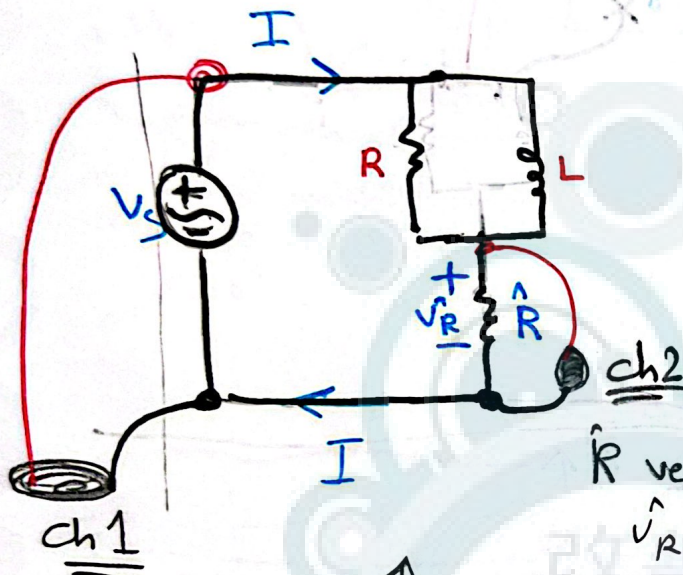


\hat{R} very small --


\hat{V}_R in phase with I

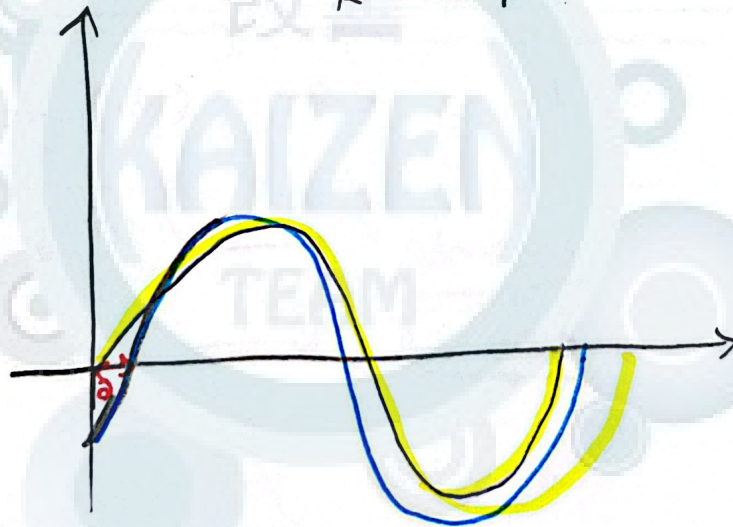

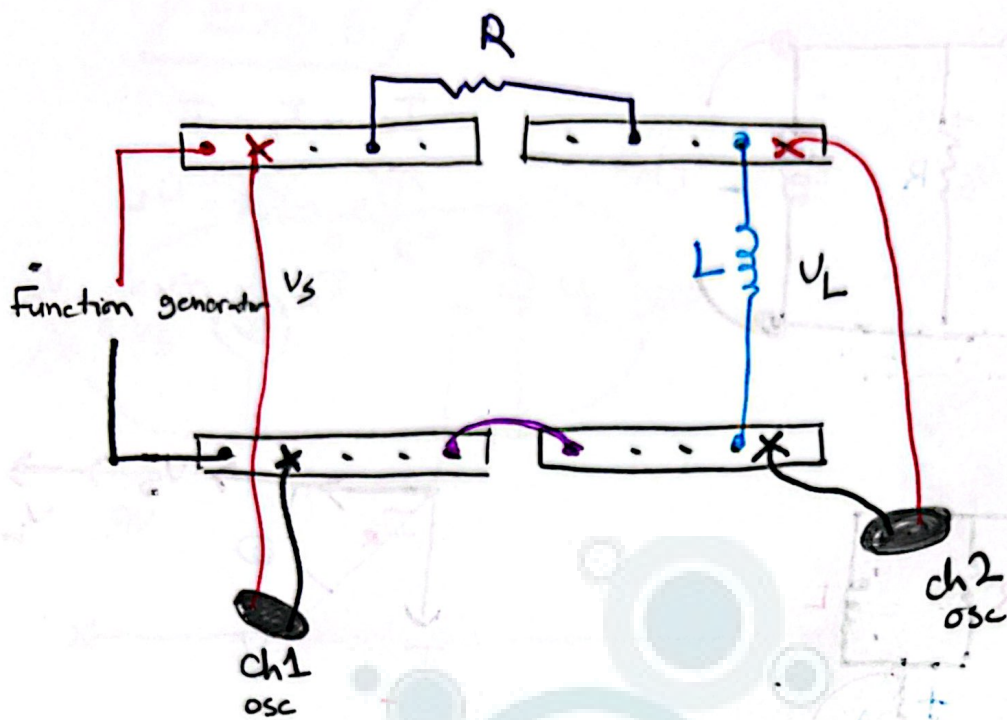$\left\{ \frac{\hat{V}_R}{I} \text{ lags } \frac{V_S}{V_S} \text{ by } \theta \dots \right\}$ Inductive load ..



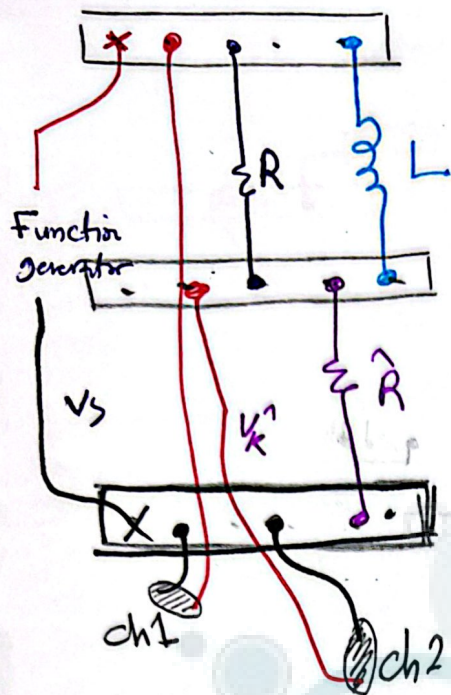$F \uparrow$ Inductance $\uparrow \uparrow$
(VPP)




I in phase V_s

I in phase V_R

V_R leads V_s

V_s leads I

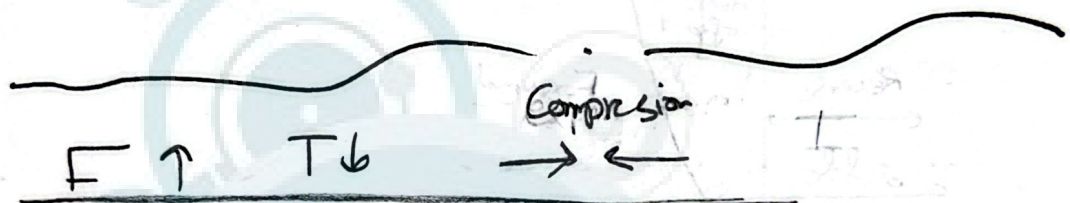

Ampl (V_s) \rightarrow ωL




Ampl (V_L) \rightarrow Varies

ωL \rightarrow Varies

with ω

with ω

Exp 8

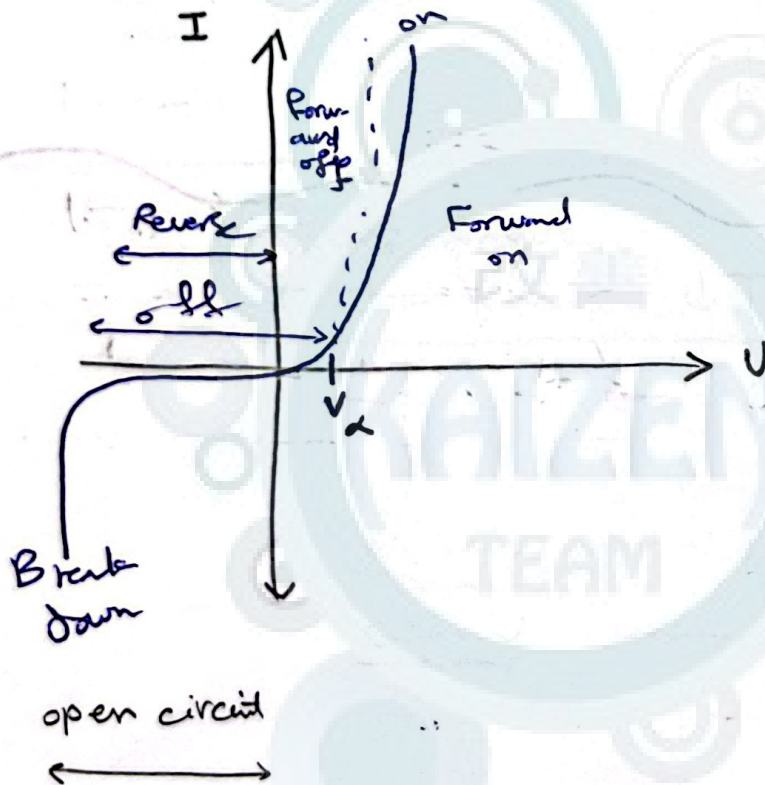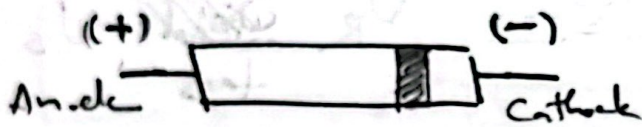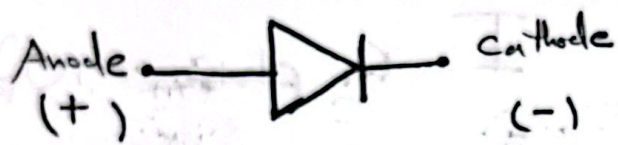

$V_d \approx 0.7 \rightarrow$ Silicon $V < V_d$ off

$V_d \approx 0.2, 0.3 \rightarrow$ germanium $V > V_d$ on



Forward bias test

V_x





Reverse bias test

O.L

I Diode test :-


To determine the Cathode, anode

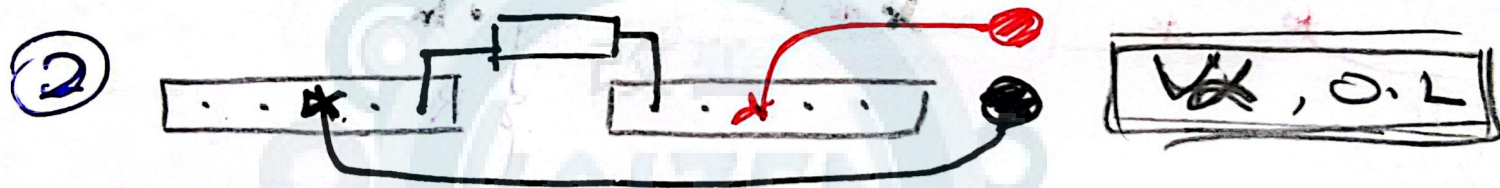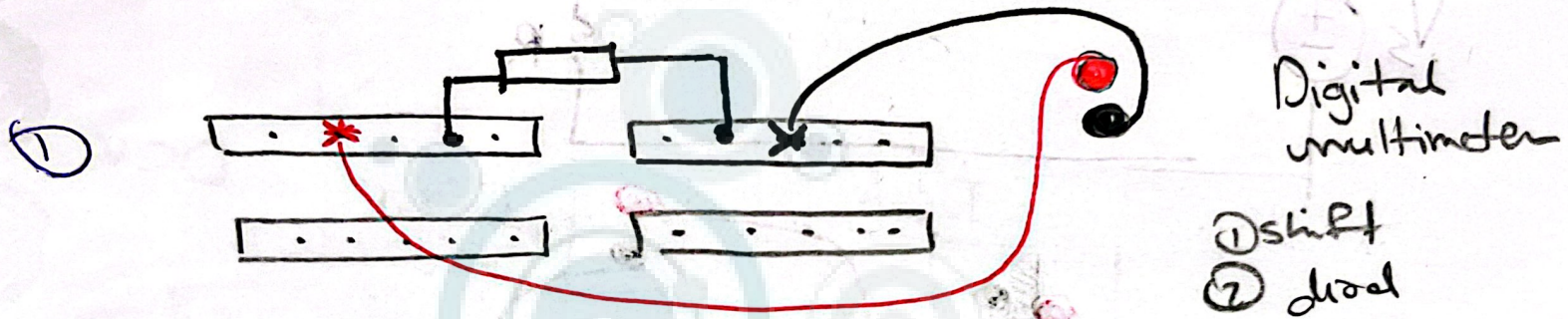



مثلاً

one of them	→	<u>0.2</u>	(reverse)
second one	→	real value	(Forward)

اذا كانو ال 2 (قراءة / 0.2) يكون خرابه

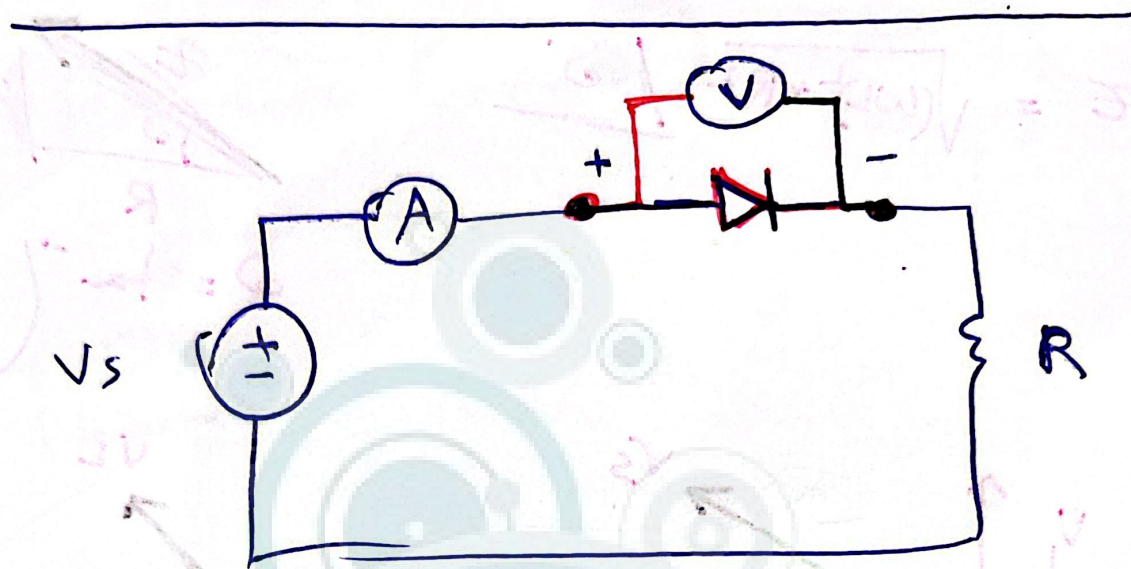


Forward bias
region

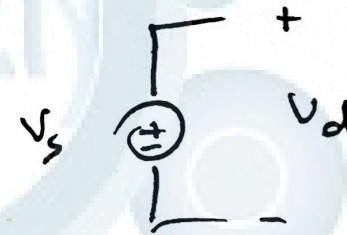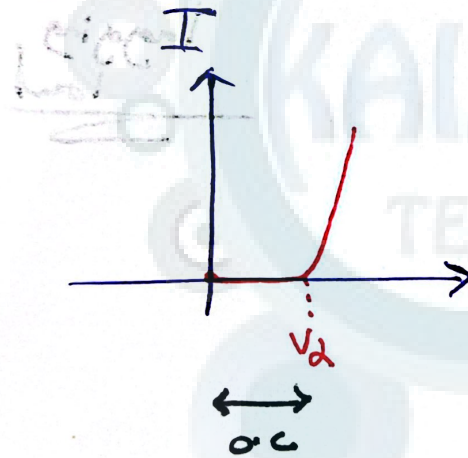


① $V_s \approx V_d$


② $V_s \geq V_d, V_d = V_s - V_R$

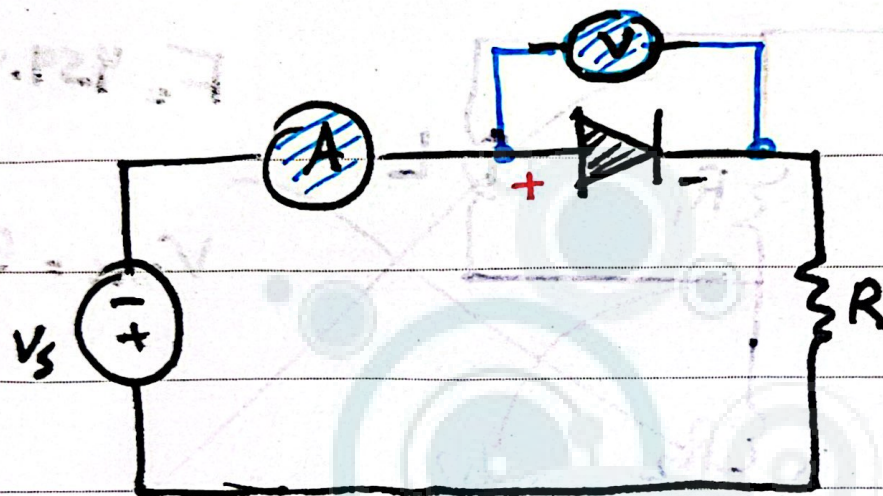

reverse bias
region

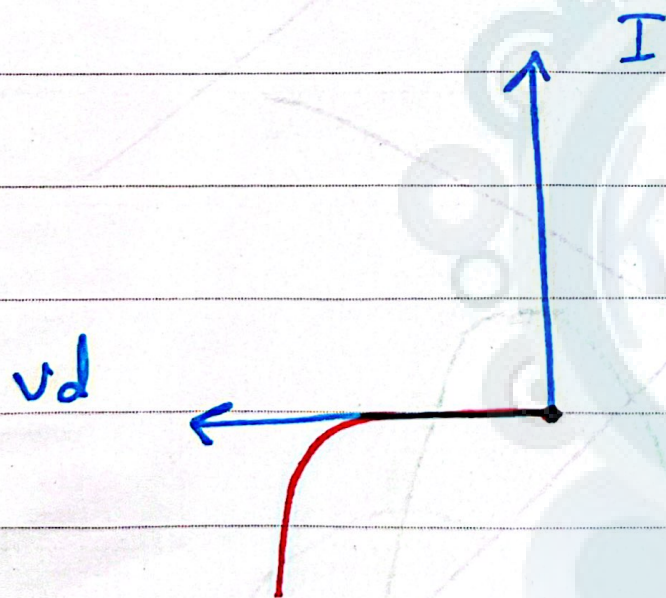


"open circuit"

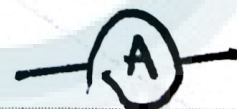


zero



negative value

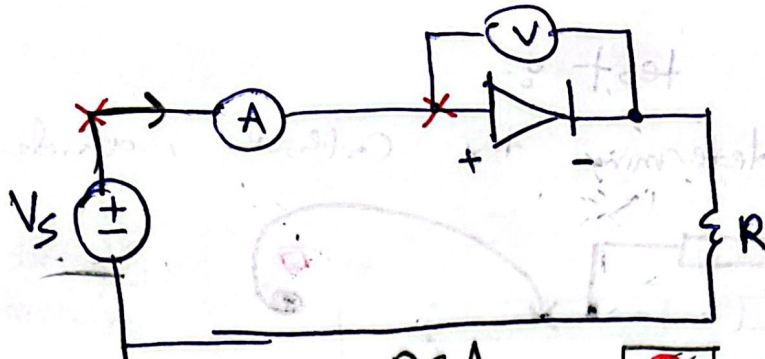



DCV

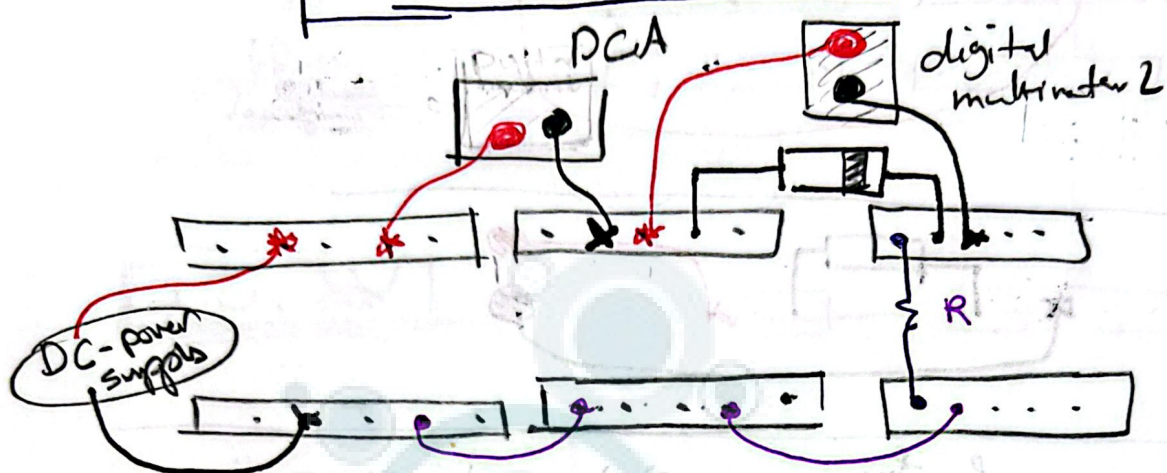



Forward


$U < U_d$	off	$\rightarrow (V_s = V_d)$
$U > U_d$	on	open circuit

2 Reversed :

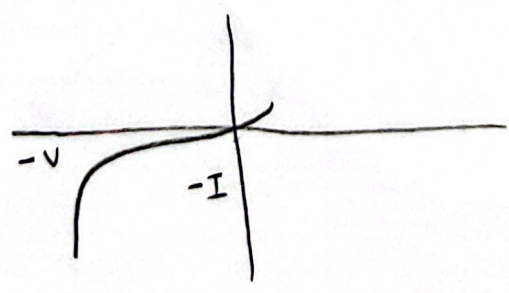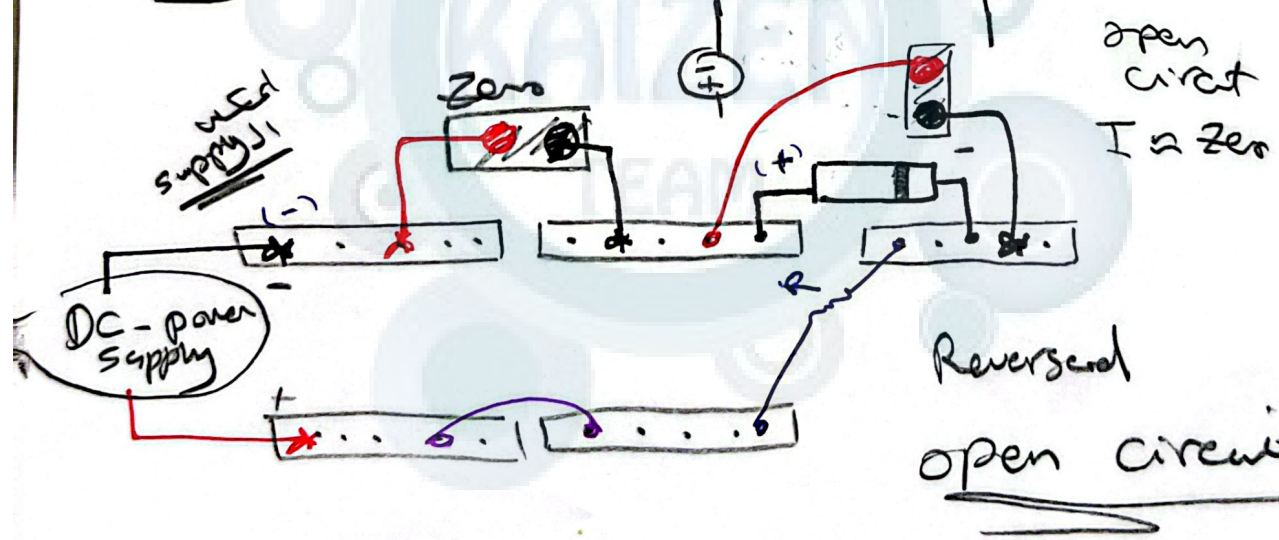


Half wave Rectifier

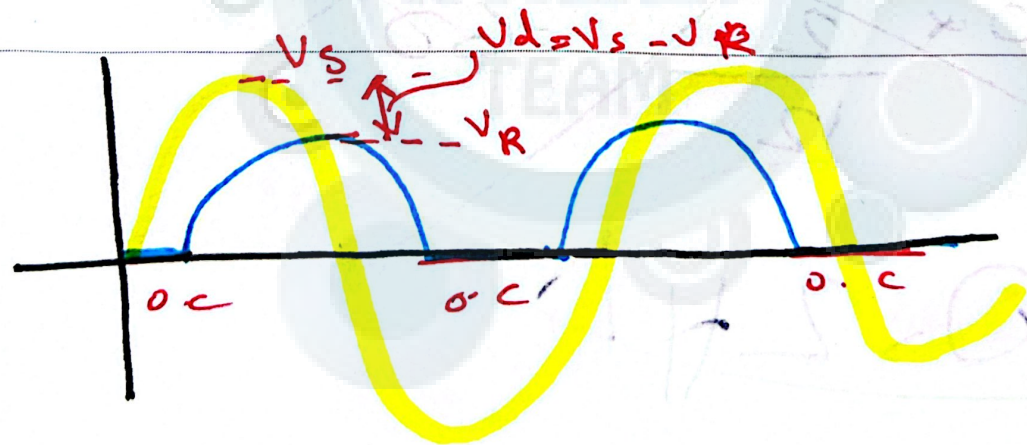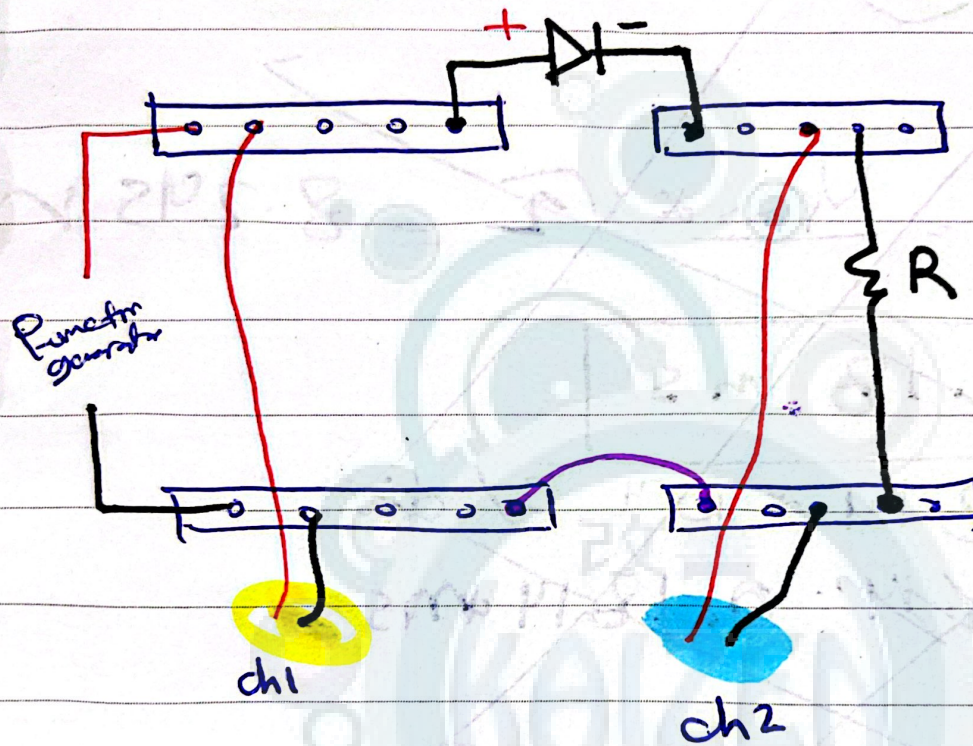

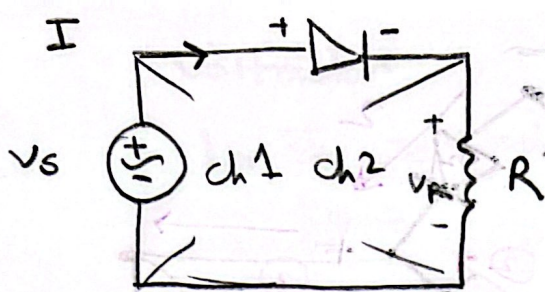


"Half Wave"
Rectifier

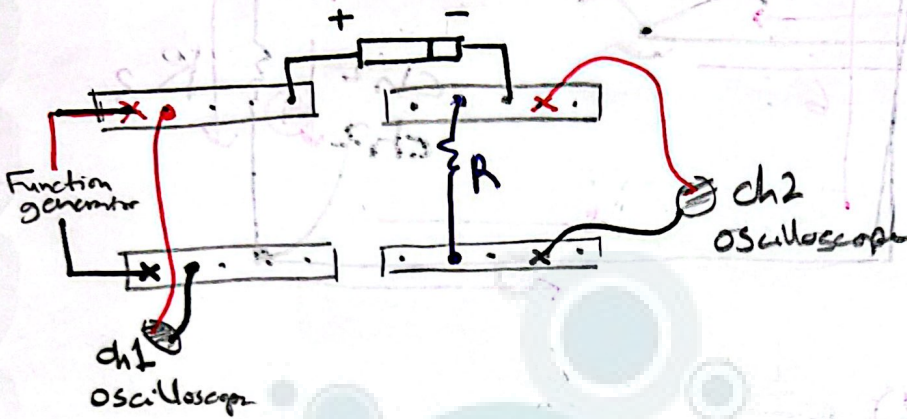





Forward

Un Filtered

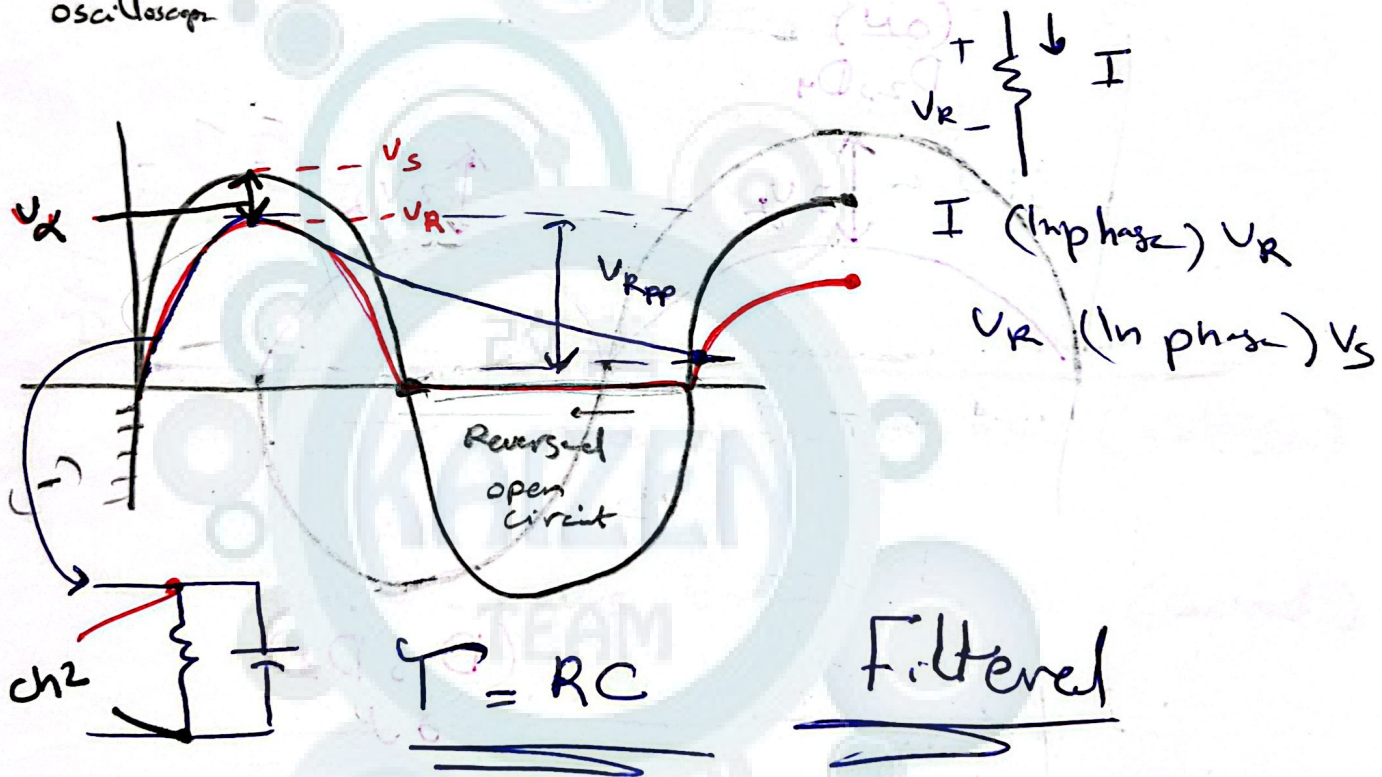

$\tau \uparrow$, $V_{RPP} \downarrow$

$L(DC) \rightarrow \frac{V_{RPP}}{2}$

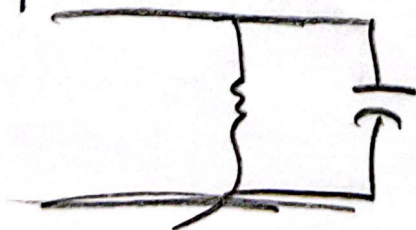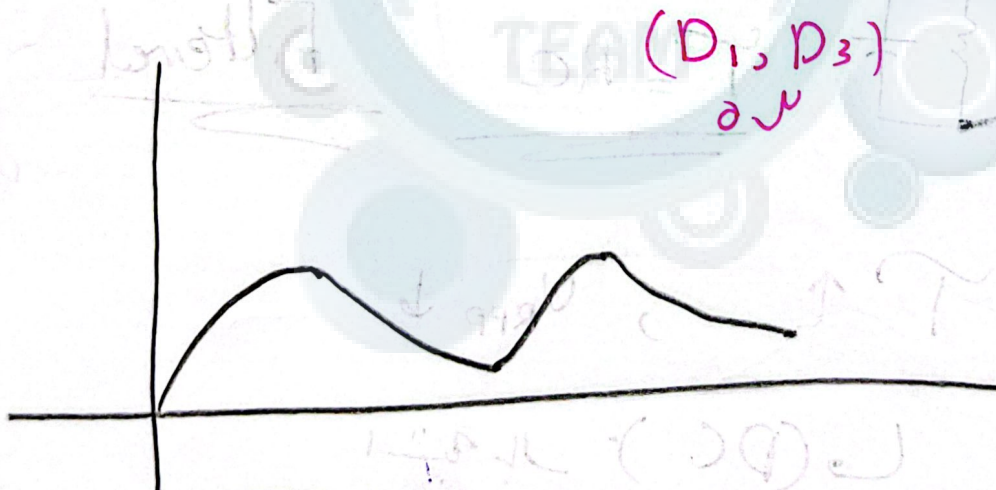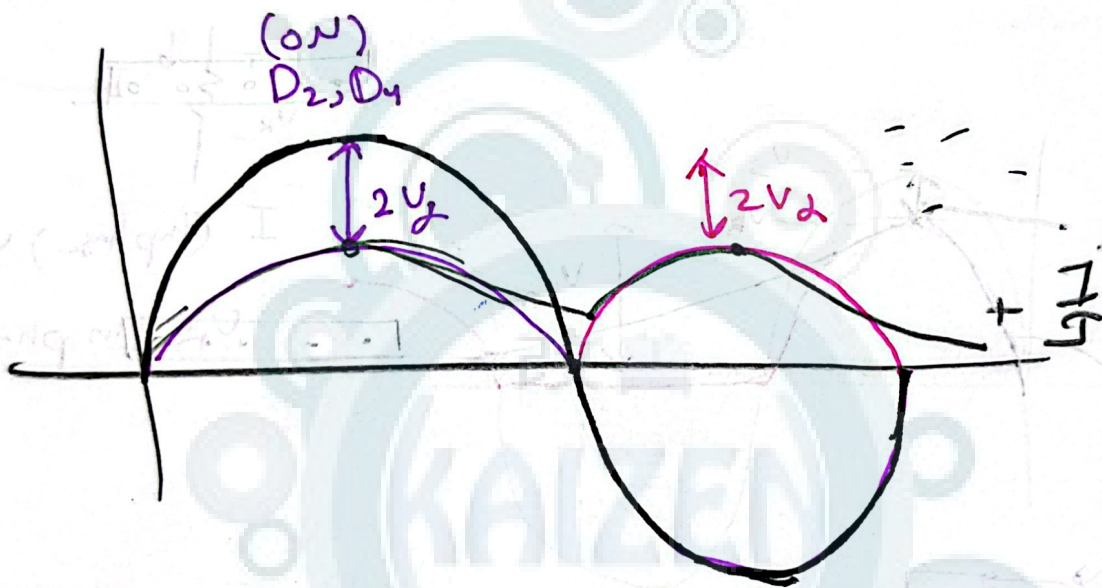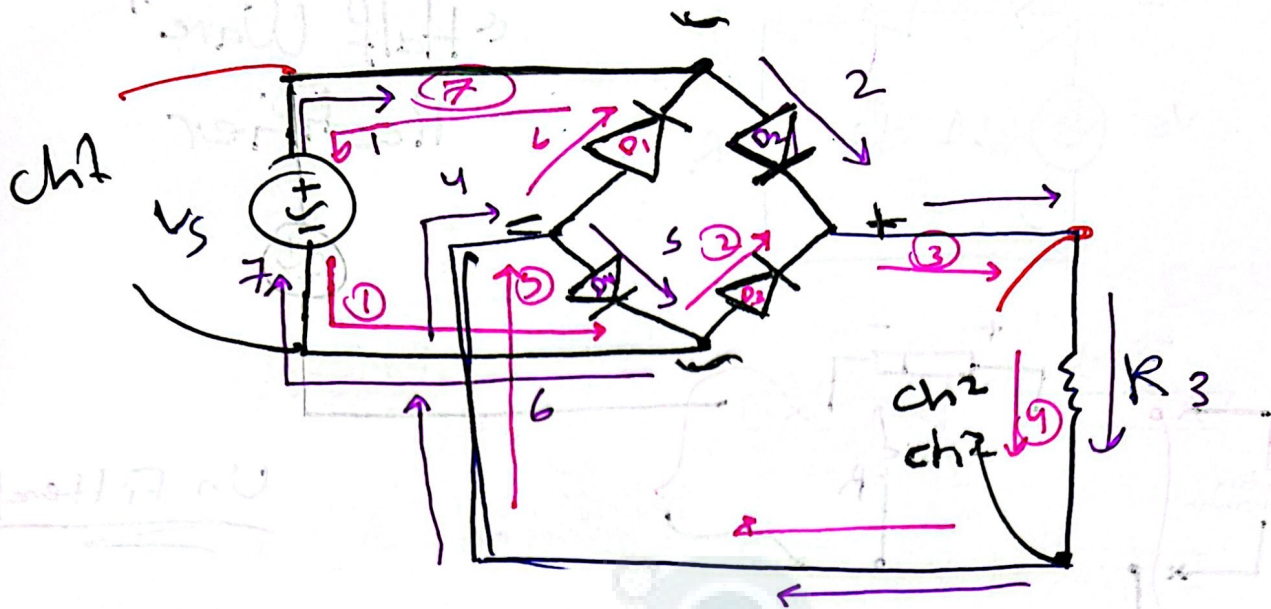

$T \uparrow$

$V_{rpp} \downarrow$

Close to DC ~