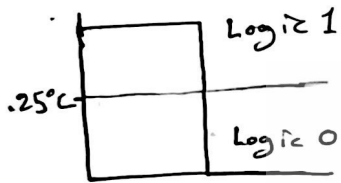




## Discrete Control

1 Switching elements (actuators) ON/OFF

2 Discrete variables, ex:



Logic control  
(independent of time)

في حال كانت الحرارة فوق 25°C تغل المروحة  
وفي حال كانت أقل من 25°C لا تغل المروحة  
لا تعتمد على زمن معين

sequencing: time-driven changes } for automation

Logic control: events-driven changes }

## Example (المثال) / slide 6

Inputs:

$$A \begin{cases} 1 = A \\ 0 = \bar{A} \end{cases}$$

$$B \begin{cases} 1 = B \\ 0 = \bar{B} \end{cases}$$

$$C \begin{cases} 1 = C \\ 0 = \bar{C} \end{cases}$$

Output:

$$D \begin{cases} 1 = D \\ 0 = \bar{D} \end{cases}$$

logic statements

connects between input and output

conditions/statements

$$1 \quad \bar{A} \cdot B$$

$$2 \quad A \cdot C$$

$$3 \quad A \cdot \bar{C} \cdot B$$

$$\Rightarrow D = \bar{A} \cdot B + A \cdot C + A \cdot \bar{C} \cdot B$$

[Boolean expression]

# Truth tables

OR

| $x_1$ | $x_2$ | F |
|-------|-------|---|
| 0     | 0     | 0 |
| 1     | 0     | 1 |
| 0     | 1     | 1 |
| 1     | 1     | 1 |



Digital/logic gates  
[multiple inputs  $\Rightarrow$  single output]


AND

| $x_1$ | $x_2$ | F |
|-------|-------|---|
| 0     | 0     | 0 |
| 0     | 1     | 0 |
| 1     | 0     | 0 |
| 1     | 1     | 1 |




Inverter


| x | F |
|---|---|
| 0 | 1 |
| 1 | 0 |

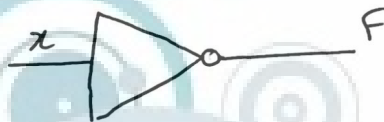

## "Combination logic gates"


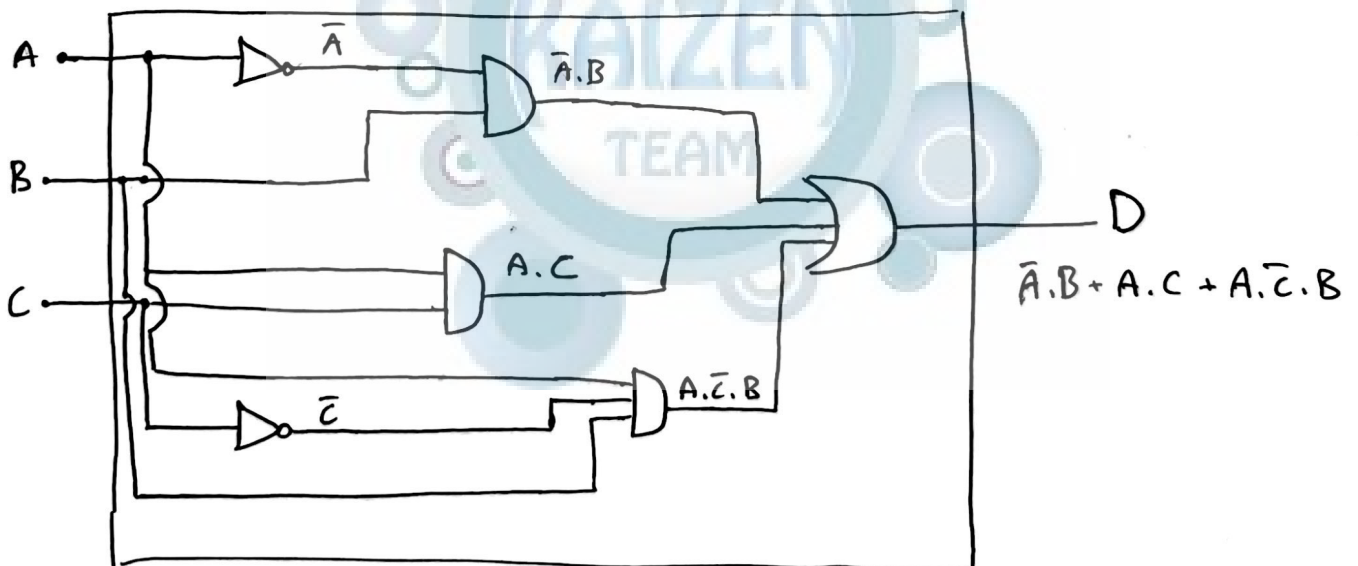


$\Rightarrow$  for the same example

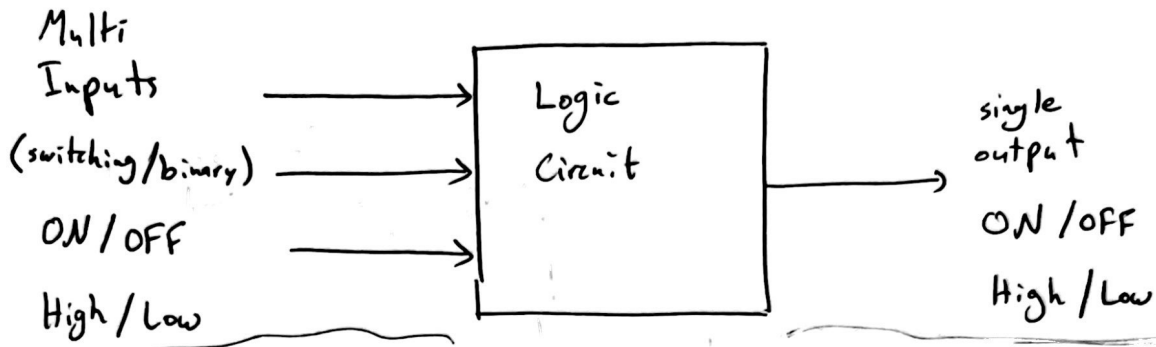


steps to build logic controllers

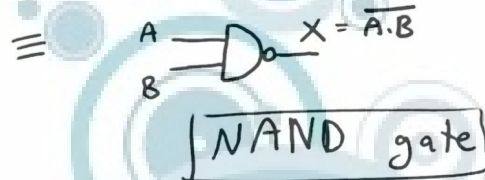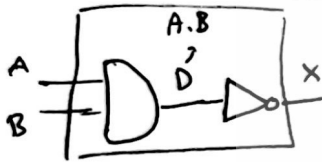- ① Logic statements (given in question)
- ② Boolean expression (built using logic gates)
- ③ simplification based on Boolean algebra rules
- ④ Implementation by using combinational logic gates




| A | B | D | X |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

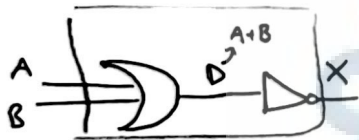


| A | B | D | X |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 |

| A | B | X |
|---|---|---|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

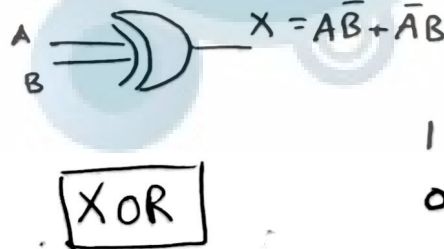


عند الاختلاف = 1  
عند التشابه = 0

| A | B | D | X |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 |

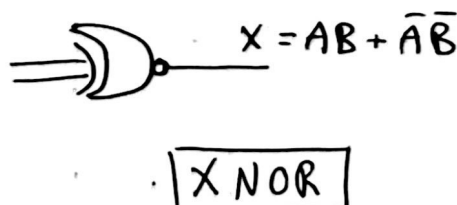

عند الاختلاف = 0  
عند التشابه = 1

## Copy machine example (slide 13)

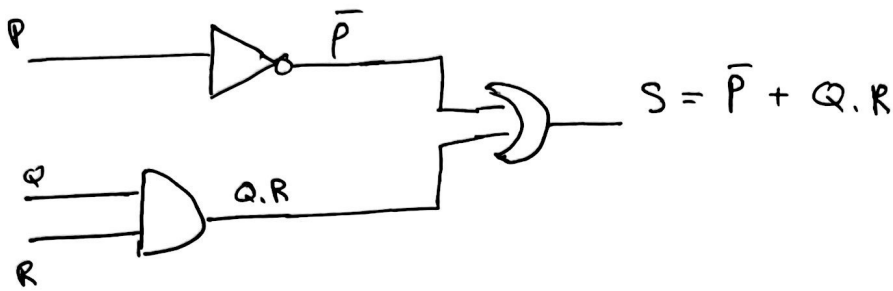

## Fundamentals of logic (some proofs)

\* Absorption law:

$$\begin{aligned}
 A(A+B) &= A.A + A.B \\
 &= A + A.B \\
 &= A(1+B) \\
 &= A(1) \\
 &= A
 \end{aligned}$$

يمكن الإثبات بهذه  
الطريقة أو من خلال  
Truth table

\* De Morgan's :  $\overline{AB} = \bar{A} + \bar{B}$

| A | $\bar{A}$ | B | $\bar{B}$ | A.B | $\overline{A.B}$ | $\bar{A} + \bar{B}$ |
|---|-----------|---|-----------|-----|------------------|---------------------|
| 0 | 1         | 0 | 1         | 0   | 1                | 1                   |
| 1 | 0         | 0 | 1         | 0   | 1                | 1                   |
| 0 | 1         | 1 | 0         | 0   | 1                | 1                   |
| 1 | 0         | 1 | 0         | 1   | 0                | 0                   |

equal ✓

### Example

A, B, C inputs

D output

\* D is high when

two of the 3 inputs

is at least high

⇒ Derive Boolean expression  
for D

① no. of states =  $2^{\text{no. of inputs}} = 2^3 = 8$

② Truth table:


| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$D = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$


Boolean expression  
for D

De Morgan's Law
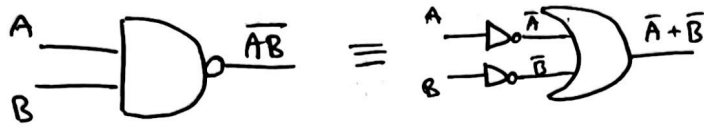
$$\textcircled{1} \overline{AB} = \bar{A} + \bar{B} \quad (\text{أثبتناها سابقاً})$$


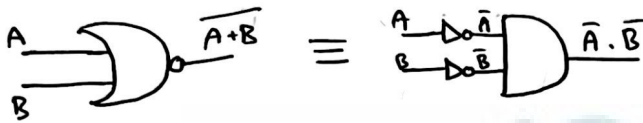
$$\textcircled{2} \overline{A+B} = \bar{A} \cdot \bar{B}$$



\* فكرة القانون:

إذا نقلنا ال inverter من

ال input لل output أو

العكس، تنقلب ال gate

AND  $\Rightarrow$  OROR  $\Rightarrow$  AND

\* Extra laws:


$$\textcircled{1} A + \bar{A}B = A + B$$

$$\textcircled{2} \bar{A} + AB = \bar{A} + B$$

| A | B | $\bar{A}$ | $\bar{A}B$ | $A + \bar{A}B$ | $A + B$ | $AB$ | $\bar{A} + AB$ | $\bar{A} + B$ |
|---|---|-----------|------------|----------------|---------|------|----------------|---------------|
| 0 | 0 | 1         | 0          | 0              | 0       | 0    | 1              | 1             |
| 1 | 0 | 0         | 0          | 1              | 1       | 0    | 0              | 1             |
| 0 | 1 | 1         | 1          | 1              | 1       | 0    | 1              | 1             |
| 1 | 1 | 0         | 0          | 1              | 1       | 1    | 1              | 1             |

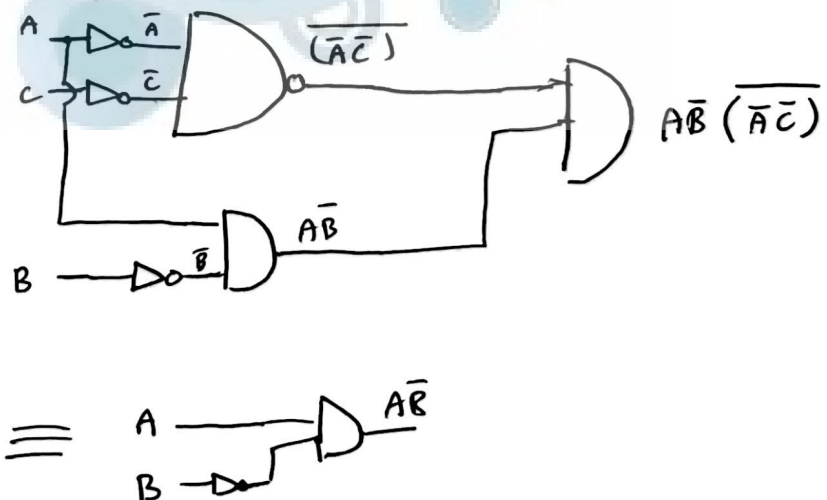Example

$$\begin{aligned} \textcircled{1} & \overline{AB}(\bar{A}\bar{C}) \\ &= \overline{AB}(\bar{A} + \bar{C}) \\ &= \overline{AB}(A + C) \\ &= \overline{AB} + \overline{AB}C \\ &= \overline{AB}(1 + C) \\ &= \overline{AB} \end{aligned}$$



# Copy machine example (using truth table)

| P | Q | R | S |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

⇒

$$\begin{aligned}
 S &= \bar{P}\bar{Q}\bar{R} + \bar{P}\bar{Q}R + \bar{P}Q\bar{R} + \bar{P}QR + P\bar{Q}\bar{R} + \underline{\bar{P}QR} \\
 &= \bar{P}\bar{Q}(\bar{R} + R) + \bar{P}Q\bar{R} + QR(\bar{P} + P) + \bar{P}QR \quad \begin{array}{l} A + A = A \\ AB + AB = AB \end{array} \\
 &= \bar{P}\bar{Q} + \bar{P}Q\bar{R} + \underline{QR} + \bar{P}QR \\
 &\quad \text{Factor out QR} \\
 &= \bar{P}\bar{Q} + \bar{P}Q(\bar{R} + R) + QR \\
 &= \bar{P}\bar{Q} + \bar{P}Q + QR \\
 &= \bar{P}(\bar{Q} + Q) + QR \\
 &= \underline{\bar{P} + QR}
 \end{aligned}$$



Examples

$$\begin{aligned}
 \textcircled{1} \quad Z &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}C \quad (\text{sum of multiplications}) \quad (\text{SOM}) \\
 &= \overline{A}\overline{B}(\overline{C} + C) + A\overline{B}C \\
 &= \overline{A}\overline{B} + A\overline{B}C \\
 &= A(\overline{B} + BC) \quad [\overline{B} + BC = \overline{B} + C] \\
 &= A(\overline{B} + C)
 \end{aligned}$$

OR

$$\begin{aligned}
 Z &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}C + A\overline{B}C \quad [A + A = A] \\
 &= \overline{A}\overline{B}(\overline{C} + C) + A\overline{B}(\overline{C} + C) \\
 &= \overline{A}\overline{B} + A\overline{B}
 \end{aligned}$$

\* إذا عندنا 3 terms ،  
ممكن نضيف حد رابع

يكون الحد الذي فيه عوامل  
مشتركة من العددين الباقيين  
(بحالتنا  $\overline{A}\overline{B}C$ )

$$\begin{aligned}
 \textcircled{2} \quad Z &= \overline{A}C(\overline{A}BD) + \overline{A}B\overline{C}\overline{D} + A\overline{B}C \\
 &= \overline{A}C(\overline{A} + B + D) + \overline{A}B\overline{C}\overline{D} + A\overline{B}C \\
 &= 0 + \overline{A}BC + \overline{A}C\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}C \\
 &= \overline{B}C(\overline{A} + A) + \overline{A}\overline{D}(\overline{C} + B\overline{C}) \\
 &= \overline{B}C + \overline{A}\overline{C}\overline{D} + \overline{A}B\overline{D}
 \end{aligned}$$

\* Hint: start with brackets

$$\textcircled{3} \quad X = (\overline{A} + B)(A + B + D)\overline{D} \quad (\text{multiplication of sum}) \quad (\text{MOS})$$

$$\begin{aligned}
 &= (\overline{A} + B)(A + B + D)\overline{D} \\
 &= (B + \overline{A}D)\overline{D} \\
 &= B\overline{D} + \overline{A}D\overline{D} \\
 &= B\overline{D}
 \end{aligned}$$

$$A + B + D$$

$$\overline{A} + B$$

$$0 + \overline{A}B + \overline{A}D + AB + B + BD$$

$$= B(\overline{A} + A) + B(\overline{D} + D) + \overline{A}D$$

$$= B + \overline{A}D$$

$$\text{Exercises: } \textcircled{1} X = \overline{A}\overline{B}C + \overline{A}BD + \overline{C}\overline{D}$$


$$\textcircled{2} X = R\overline{S}\overline{T} + \overline{R}S\overline{T} + \overline{T}$$

$$\textcircled{3} X = \overline{A}\overline{C}\overline{D} + \overline{A}CD$$


$$\textcircled{4} X = M\overline{N}\overline{P} + (M + \overline{N})P$$

$$\textcircled{5} X = AB + \overline{A}B\overline{C} + A\overline{B}\overline{C}D$$



## ladder diagram

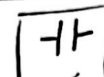A High ON  Logic 1 Active Start  
 $\bar{A}$  Low OFF  Logic 0 Inactive Stop  
 shattered switches

## logic gate

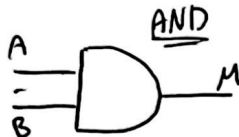


## ladder diagram

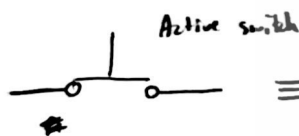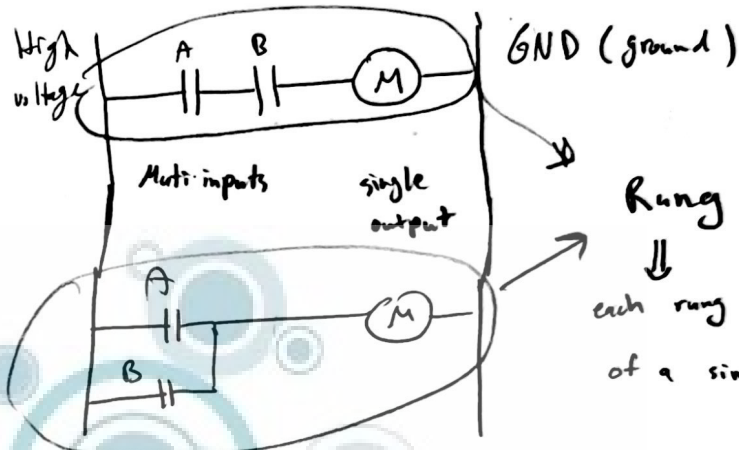

$\equiv$    $\Rightarrow$  Normally open (NO) / Starts

$\equiv$    $\Rightarrow$  Normally closed (NC) / Stops

[هاي كانه الازمة  
هو انما مش شغالة]

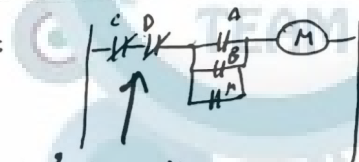\* Example 4-9  $\Rightarrow$    
 (slide 24)

التعديل

## NAND





$\equiv$



## NOR



$\equiv$

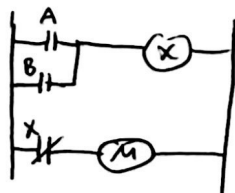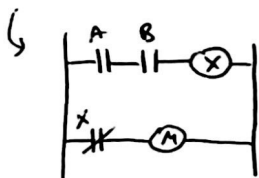

ladder diagrams

## Example

$$A = \bar{B} \cdot (\overline{C \cdot (\bar{D} + E + \bar{C})} + \bar{F} \cdot C)$$

\* Before simplification:


- 1 Draw logic combination circuit for A
- 2 Draw the ladder diagram for A

\* After simplification:


- 3 Draw logic combinational circuit for A
- 4 Draw ladder diagram for A

## Answer

\* Before: 1  
Simplification

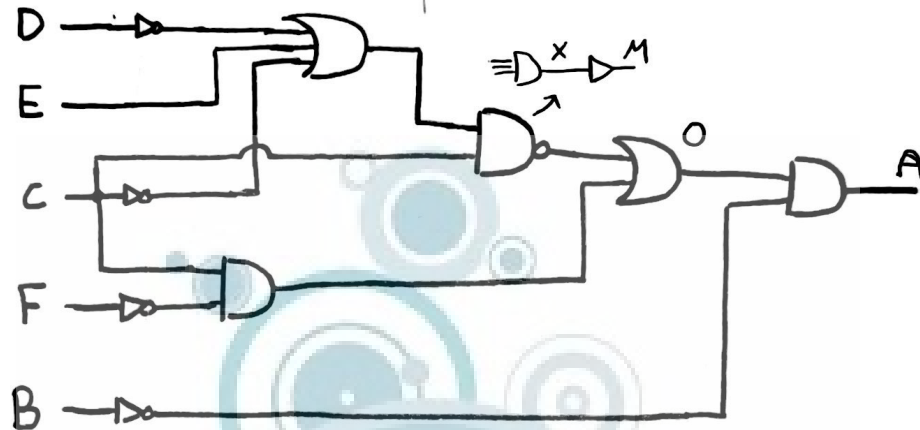

2

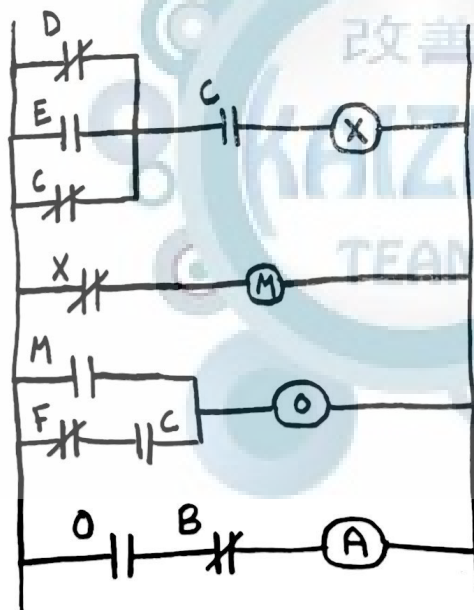

Contd. →

\* Simplification:

AND

$$A = \overline{B \cdot \left( \underbrace{C \cdot (\overline{D+E+\overline{C}})}_{\text{OR}} + \overline{F} \cdot C \right)}$$

$$\overline{C \cdot (\overline{D+E+\overline{C}})}$$

$$\overline{C} + (\overline{\overline{D+E+\overline{C}}}) \Rightarrow \text{De Morgan's}$$

$$\overline{C} + (\overline{\overline{D}} \cdot \overline{\overline{E}} \cdot \overline{\overline{C}})$$

$$\overline{C} + \overline{D} \cdot \overline{E} \cdot \overline{C} \Rightarrow \overline{A} + BA = \overline{A} + B$$



$$\boxed{\overline{C} + \overline{D} \cdot \overline{E}}$$

$$A = \overline{B} \cdot (\overline{C} + \overline{D} \cdot \overline{E} + \overline{F} \cdot C) \Rightarrow \overline{C} + \overline{F} \cdot C = \overline{C} + \overline{F}$$

$$A = \overline{B} \cdot (\overline{C} + \overline{F} + \overline{D} \cdot \overline{E})$$


$$\boxed{A = \overline{B} \cdot \overline{C} + \overline{B} \cdot \overline{F} + \overline{B} \cdot \overline{D} \cdot \overline{E}}$$

\* After 3 simplification

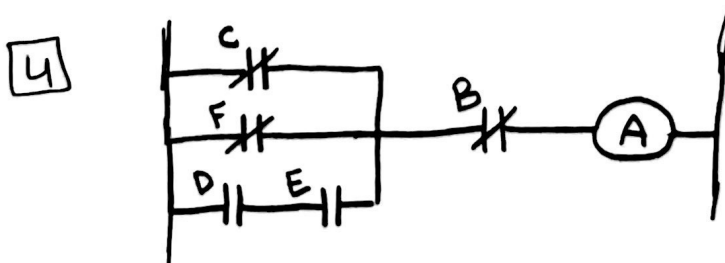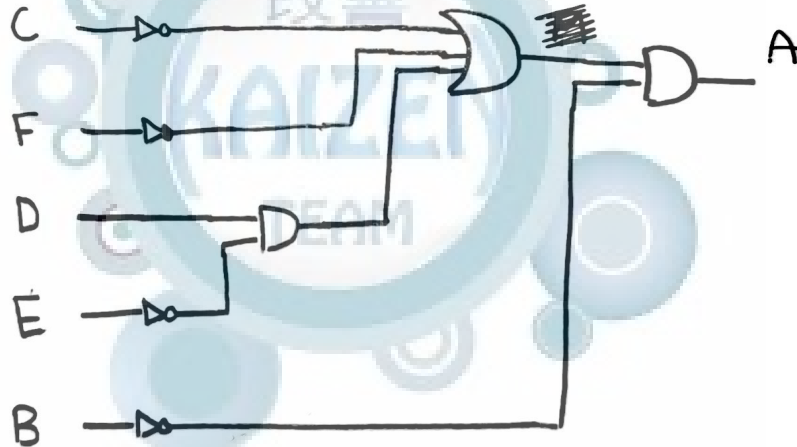


# CH.9 - lect. 6


Sequencing

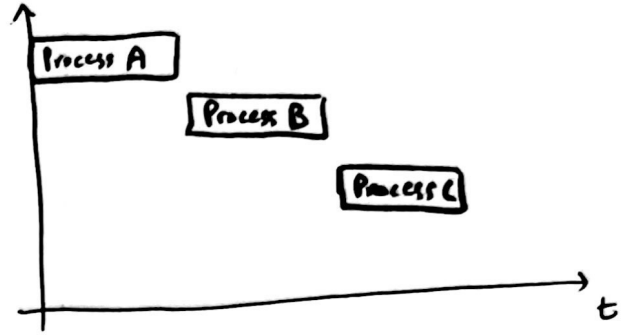

Time - dependent

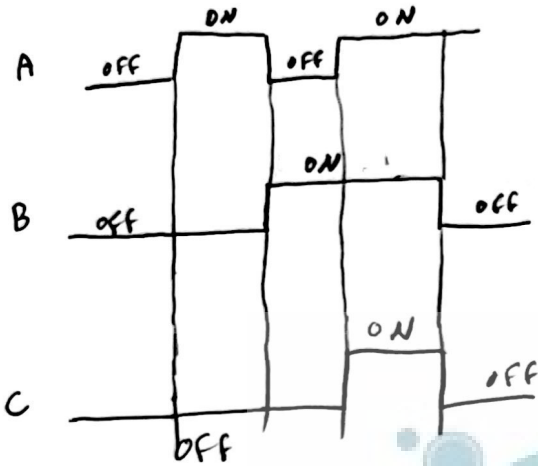

Push Button Switch / Start - Stop switch

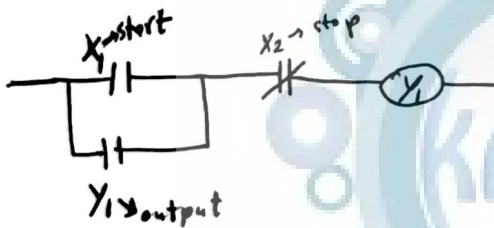

\* latching: output parallel with start switch

→ in our case, Y<sub>1</sub> is latched with start switch X<sub>1</sub>

ladder diagram (components)

\* Inputs

- switches:  
START  
STOP
- sensors

\* Outputs

- Actuators
- Indicators (lights)
- Valves
- Motors

\* [Timers/counters]


Dependencies

## Example 8


Slide 43

~~ladder diagram~~

ladder diagram

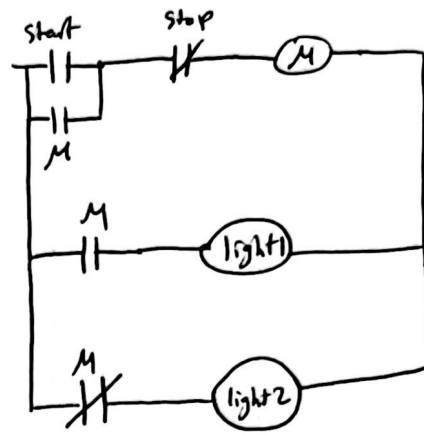
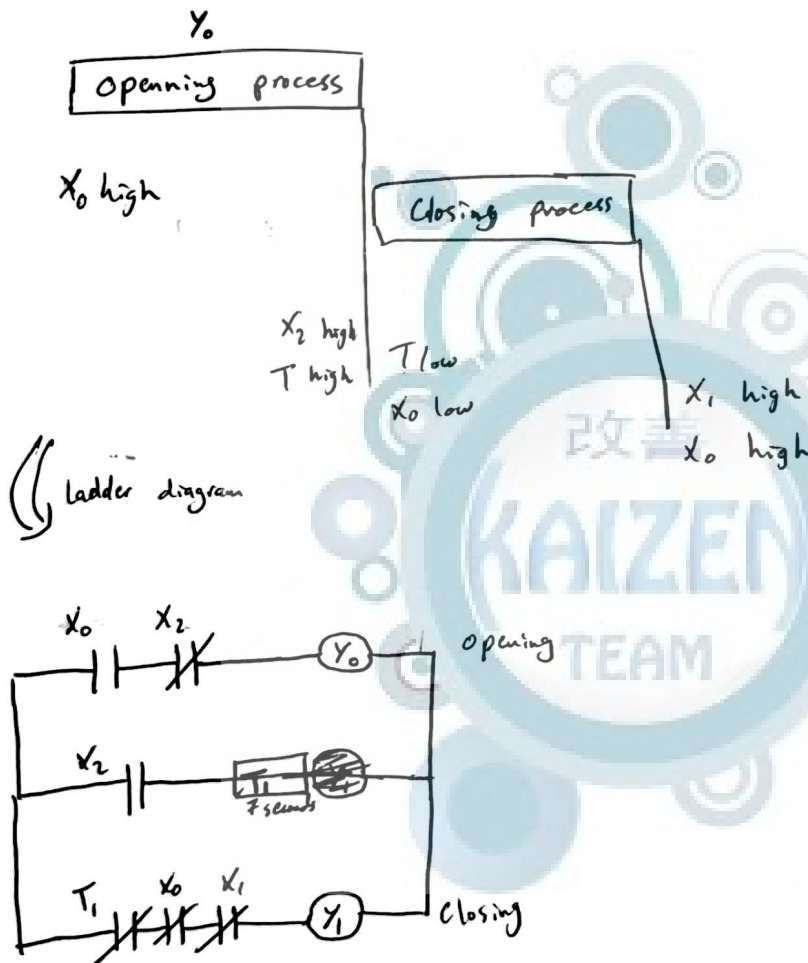
## Q2) Automatic doors example ~~PLC questions file~~ (PLC questions file)




## Q4) Infusing container system example ~~PLC questions file~~

Process 1 : inlet


Process 2 : Mixing ,  $T_0 = 60 \text{ sec.}$

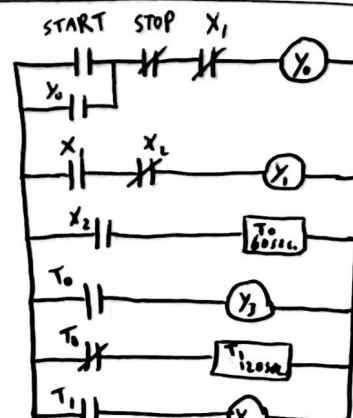Process 3 : Draining ,  $T_1 = 120 \text{ sec.}$


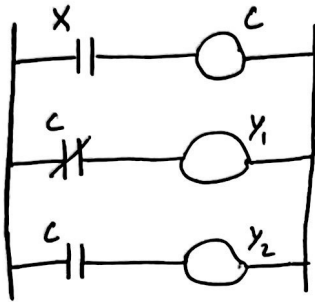
## CH. 9 - lect. 7

Control Relay: an actuator that manages multiple applicants (circuits) using one control signal




$Y_1$ : Normally Closed (NC), opens when the relay is energized

$Y_2$ : Normally Open (NO), closes when the relay is energized

## PLC questions file


Q1) Industrial Robot

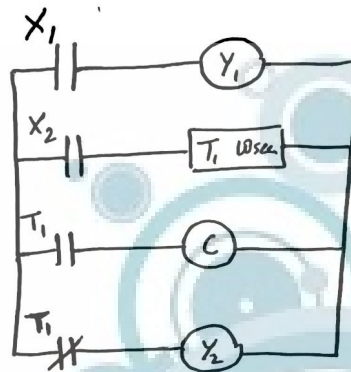

Process 1: nest → heating coil


Process 2: Heating

Process 3: heating coil → conveyor

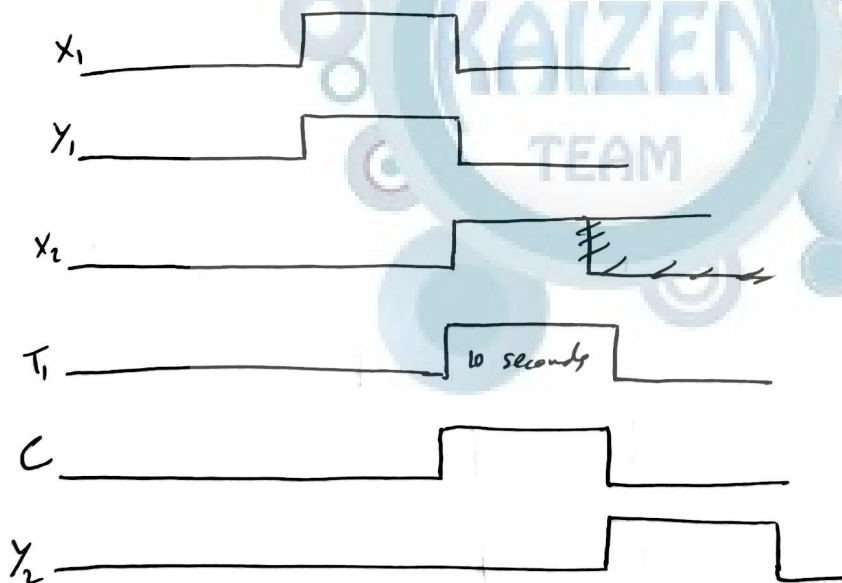

Timing diagram (signals)

# Coffee machine example (Q3)

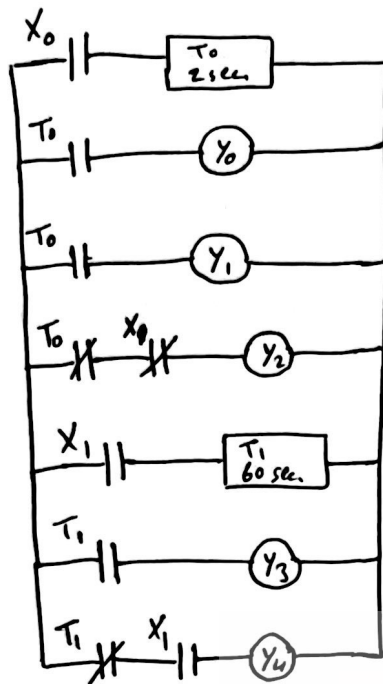

→ A coin is inserted

→ A paper cup is sent out

→ certain amount of coffee will be poured into the container

→ Hot water poured into the container

→ Agitator mixing

→ Made coffee pouring out from Y4 outlet into the paper cup

