



Automation Slides With Notes

(2nd Semester 2023/2024)
Notes are written by Nada Ababneh





Automation

Chapter Nine:

Discrete Control Using Programmable Logic Controllers

Dr. Eng. Baha'eddin Alhaj Hasan
Department of Industrial Engineering

Chapter 9: Discrete Control

Sections:

1. Discrete Process Control
2. Ladder Logic Diagrams
3. Programmable Logic Controllers

→ PLC → (discrete controllers)

2 States → 0 → ex: Low/off/.....
 → 1 → ex: High/on/.....



0 → zero volt
1 → five volt

Sec 9.1: Discrete Process Control

- **Continuous Control:** deals with controlling continuous variables or parameters in the system.
- **Discrete Control:** Control systems that operate on parameters and variables that change at discrete moments in time or at discrete events,
 - usually binary (0 or 1, off or on, open or closed, etc.)
 - Called also: switching systems.



Sensors and Actuators Used in Discrete Process Control

Sensors	Interpretation	Actuators	Interpretation
Limit switch	Contact/no contact	Motor <small>e.x: stepper motor</small>	On/off
Photo-detector	On/off	Valve	Open/closed
Timer	On/off	Clutch	Engaged/not engaged
Push-button switch	On/off	<u>Control relay</u>	Contact/no contact
<u>Control relay</u>	Contact/no contact	Light	On/off
Circuit breaker	Contact/no contact	Solenoid	Energized/not energized


 Normally Open switch (NO)

 No push button

 No switch

NO
normally open

Push button

 Normally closed switch (NC)

 NC push button switch


 NC switch

NC
normally closed

push button

Categories of Discrete Control

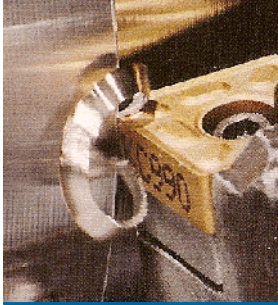
- **Logic control:** event-driven changes
- **Sequencing:** time-driven changes
- **Logic Control:** a switching system whose output at any moment is determined exclusively by the values of inputs.
 - No memory
 - No operating characteristics that depend on time
 - Also called combinational logic control




Digital Variables

2 States $\begin{cases} 0 \rightarrow \text{ex: Low/off/.....} \\ 1 \rightarrow \text{ex: High/on/.....} \end{cases}$

غالباً *
0 → zero volt
1 → five volt

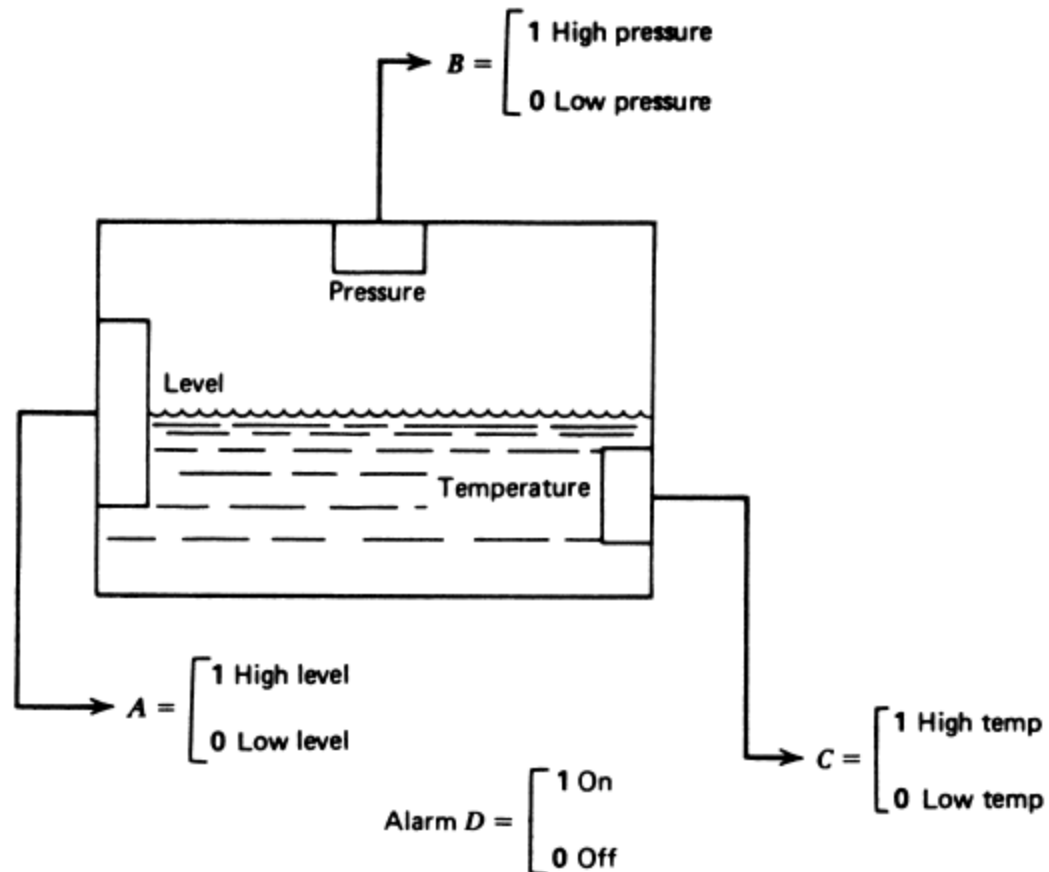

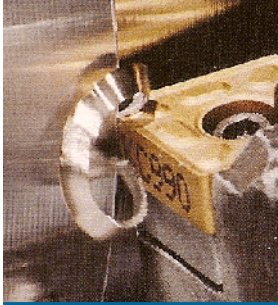

Boolean Algebra

The alarm will be triggered when the Boolean variable D goes to the logic true state. The alarm conditions are:

1. Low level with high pressure
2. High level with high temperature
3. High level with low temperature and high pressure

- A (Level)
- B (Pressure)
- C (Temperature)
- D (Alarm)

Boolean Algebra

We now define a Boolean expression with AND operations that will give a $D = 1$ for each condition:

1. $D = \overline{A} \cdot B$ will give $D = 1$ for condition 1.
2. $D = A \cdot C$ will give $D = 1$ for condition 2.
3. $D = A \cdot \overline{C} \cdot B$ will give $D = 1$ for condition 3.


The alarm conditions are:

1. Low level with high pressure
2. High level with high temperature
3. High level with low temperature and high pressure

The final logic equation results from combining all three conditions so that if any is true, the alarm will sound ($D = 1$). This is accomplished with the OR operation

$$\underline{D = \overline{A} \cdot B + A \cdot C + A \cdot \overline{C} \cdot B} \quad (2)$$

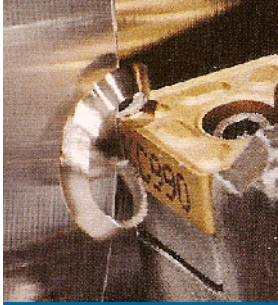This equation would now form the starting point for a design of electronic digital circuitry that would perform the indicated operations.



Boolean Algebra


Develop a digital circuit using AND/OR gates that implements Equation (2).

Solution


The problem posed in Section 2.3 (with Figure 1) has a Boolean equation solution of

$$D = \overline{A} \cdot B + A \cdot C + A \cdot \overline{C} \cdot B \quad (2)$$
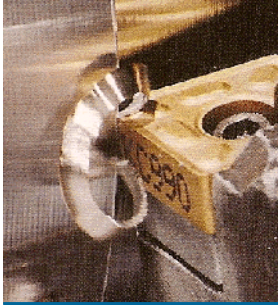
$$D = \bar{A} \cdot B + A \cdot C + A \cdot \bar{C} \cdot B$$



Boolean Algebra

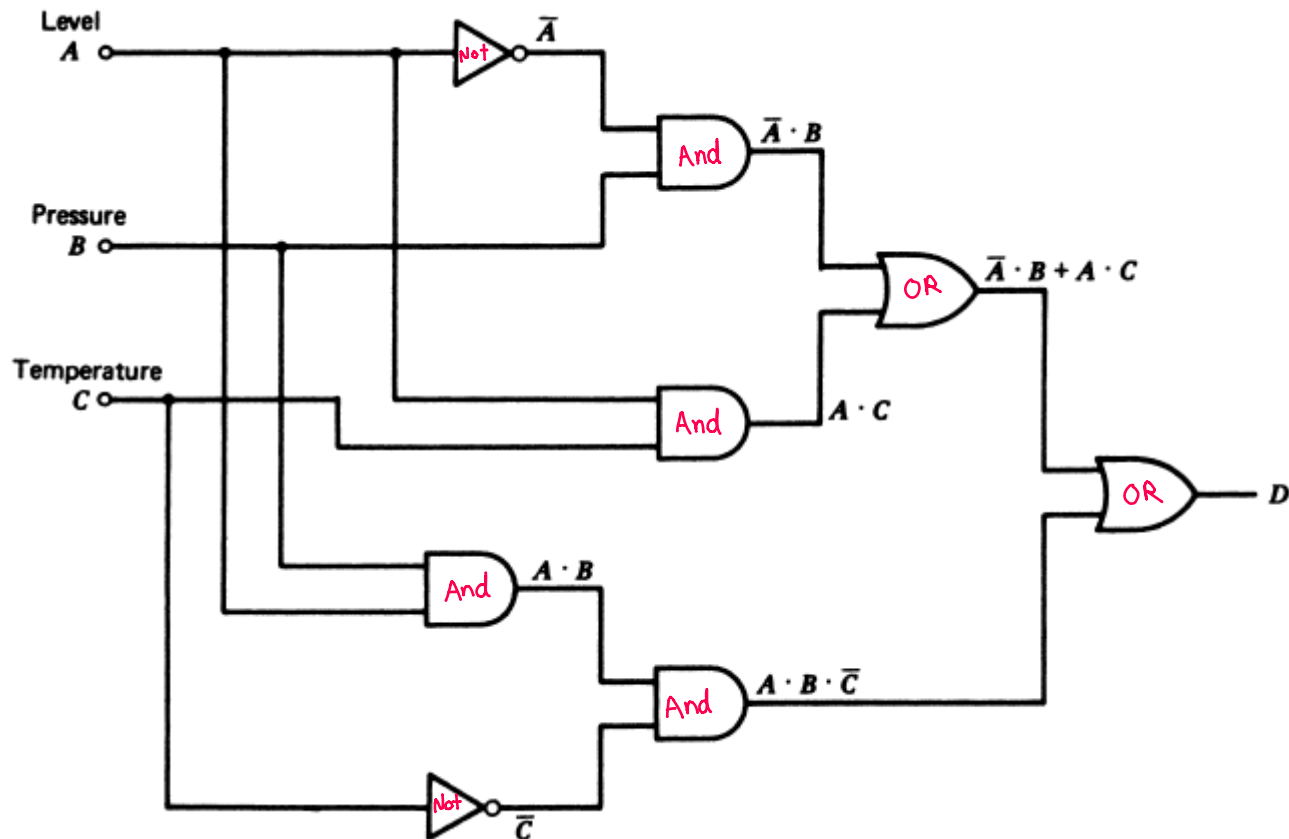


-single output < 1

-multiple input
(not ال not)



Fundamentals of Logic


Hardwired circuit

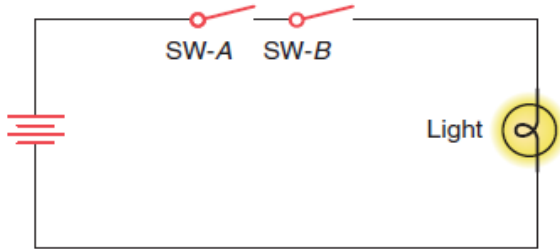

Truth table

SW-A		SW-B		Light
Open	(0)	Open	(0)	Off (0)
Open	(0)	Closed	(1)	Off (0)
Closed	(1)	Open	(0)	Off (0)
Closed	(1)	Closed	(1)	On (1)


Logic representation

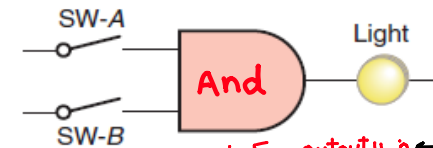

(And)

لو أي input $\leftarrow 0$ ف output سيكون $\leftarrow 0$
لو كلهم شغالين يعني جميع input $\leftarrow 1$ ف output سيكون $\leftarrow 1$


Hardwired circuit

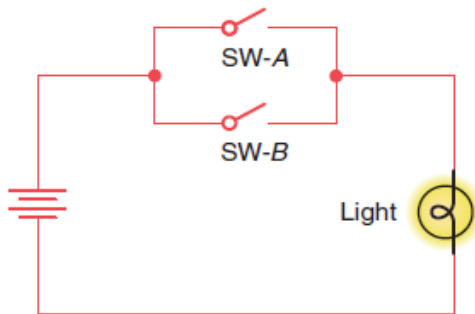

Truth table

SW-A		SW-B		Light
Open	(0)	Open	(0)	Off (0)
Open	(0)	Closed	(1)	On (1)
Closed	(1)	Open	(0)	On (1)
Closed	(1)	Closed	(1)	On (1)


Logic representation

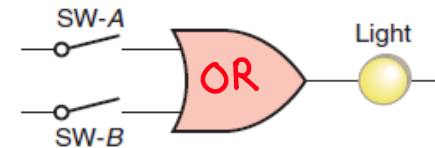

(OR)

أي input $\leftarrow 1$ ف output يعطيني $\leftarrow 1$


Hardwired circuit

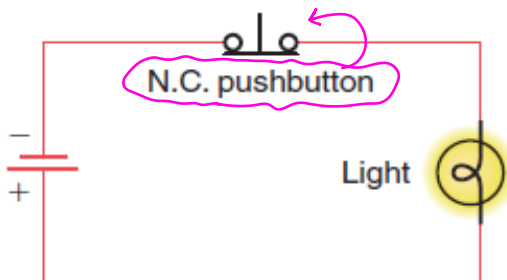

Truth table

Pushbutton		Light
Not pressed	(0)	On (1)
Pressed	(1)	Off (0)

Logic representation

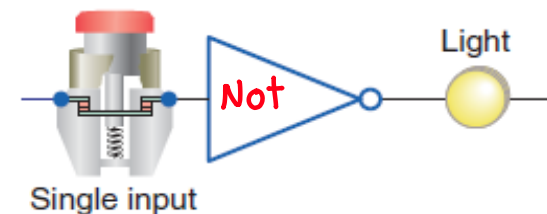

(Not)

عكس ال input

N.C. A normally closed pushbutton.

Fundamentals of Logic




(Power on)

$A = 1$

$B = 0$

(Pressure switch open)

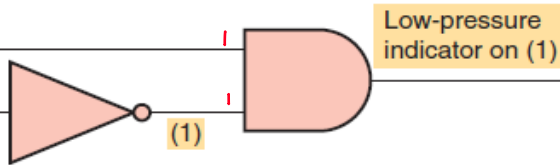

Truth table		
Pressure switch	Power	Pressure indicator
0	1	1
1	1	0

(Power on)

$A = 1$

$B = 1$

(Pressure switch closed)



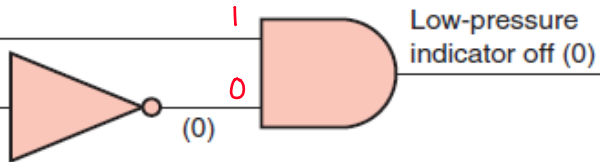


Figure 4-11 NOT function is most often used in conjunction with an AND gate.

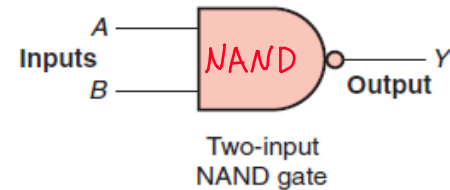

NAND truth table		
Inputs		Output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


Figure 4-12 NAND gate symbol and truth table.

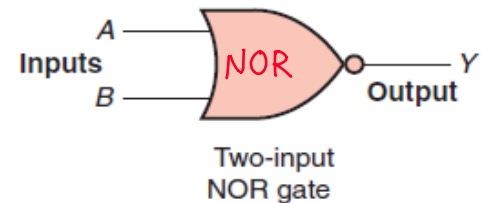

NOR truth table		
Inputs		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Figure 4-13 NOR gate symbol and truth table.

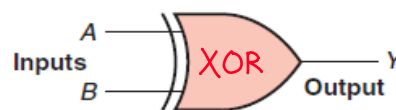(XOR)
(XNOR)
input متشابه → output zero
input مختلف → output one



Truth table		
Inputs		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Figure 4.14 The XOR gate symbol and truth table.

Table 4-1 Typical Boolean Instruction or Statement List**Boolean Instruction and Function****Graphic Symbol****Store (STR)–Load (LD)** → output

Begins a new rung or an additional branch in a rung with a normally open contact.

**Store Not (STR NOT)–Load Not (LD NOT)**


Begins a new rung or an additional branch in a rung with a normally closed contact.

**Or (OR)**

Logically ORs a normally open contact in parallel with another contact in a rung.

**Or Not (OR NOT)**

Logically ORs a normally closed contact in parallel with another contact in a rung.

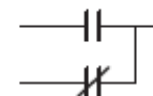**And (AND)**


Logically ANDs a normally open contact in series with another contact in a rung.

**And Not (AND NOT)**


Logically ANDs a normally closed contact in series with another contact in a rung.

**And Store (AND STR)–And Load (AND LD)**


Logically ANDs two branches of a rung in series.

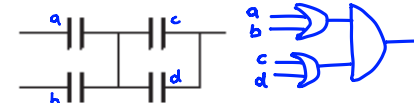**Or Store (OR STR)–Or Load (OR LOAD)**


Logically ORs two branches of a rung in parallel.

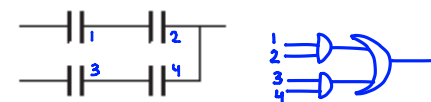**Out (OUT)**

Reflects the status of the rung (on/off) and outputs the discrete (ON/OFF) state to the specified image register point or memory location.

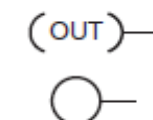
**Or Out (OR OUT)**

Reflects the status of the rung and outputs the discrete (ON/OFF) state to the image register. Multiple OR OUT instructions referencing the same discrete point can be used in the program.

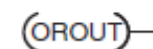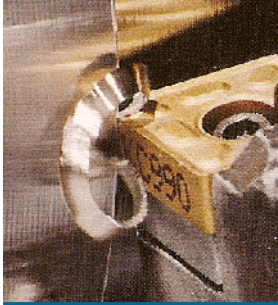**Output Not (OUT NOT)**

Reflects the status of the rung and turns the output OFF for an ON execution condition; turns the output ON for an OFF execution condition.





Fundamentals of Logic

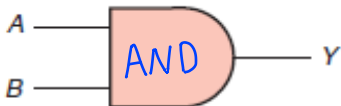
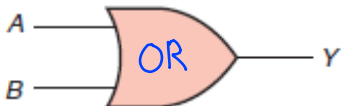
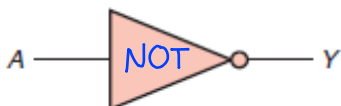
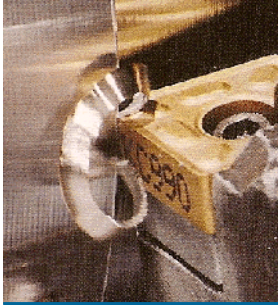
Logic symbol	Logic statement	Boolean equation	Boolean notations
	Y is 1 if A and B are 1	$Y = A \cdot B$ or $Y = AB$	Symbol Meaning • and + or − not ° invert = result in
	Y is 1 if A or B is 1	$Y = A + B$	
	Y is 1 if A is 0 Y is 0 if A is 1	$Y = \bar{A}$	

Figure 4-15 Boolean algebra as related to AND, OR, and NOT functions.



Fundamentals of Logic


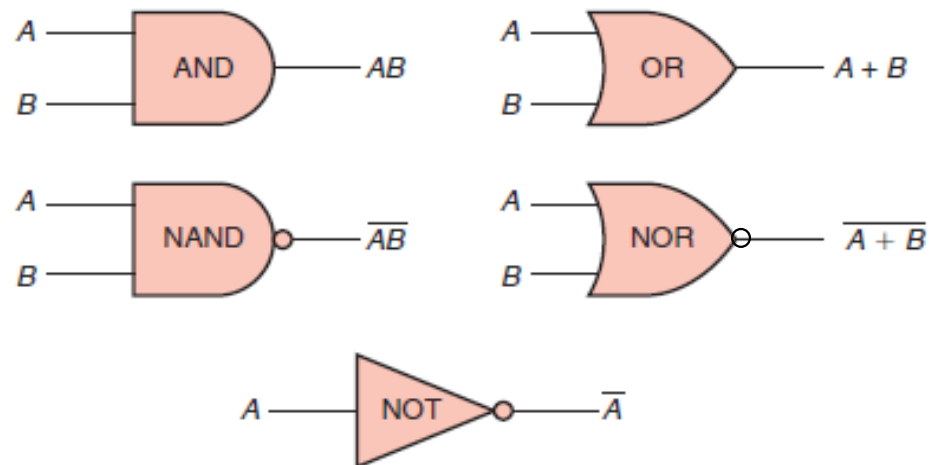


Figure 4-16 Logic operators used singly to form logical statements.

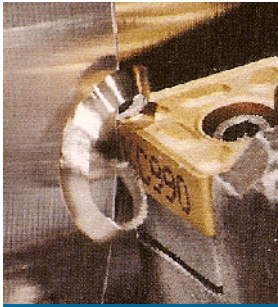

Fundamentals of Logic




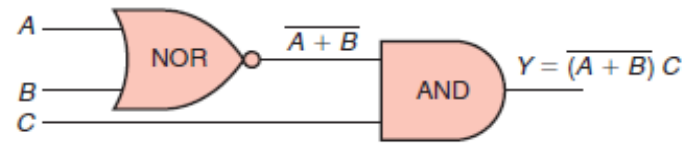
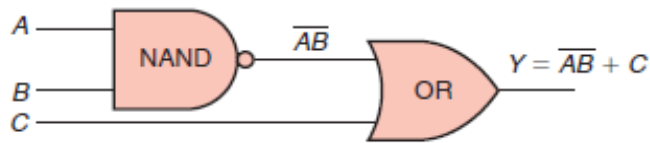
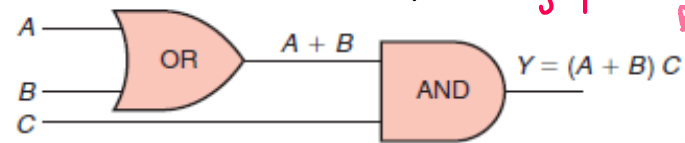
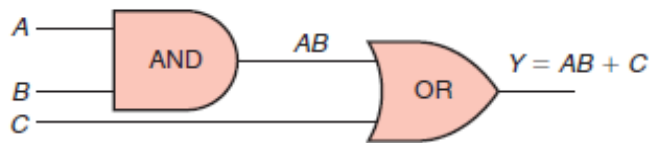
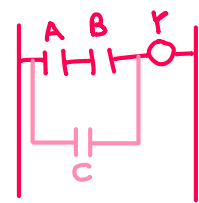
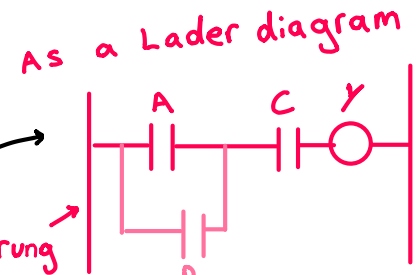
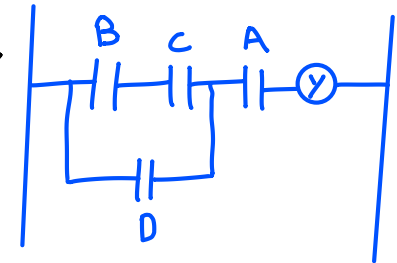


Figure 4-17 Logic operators used in combination to form Boolean equations.

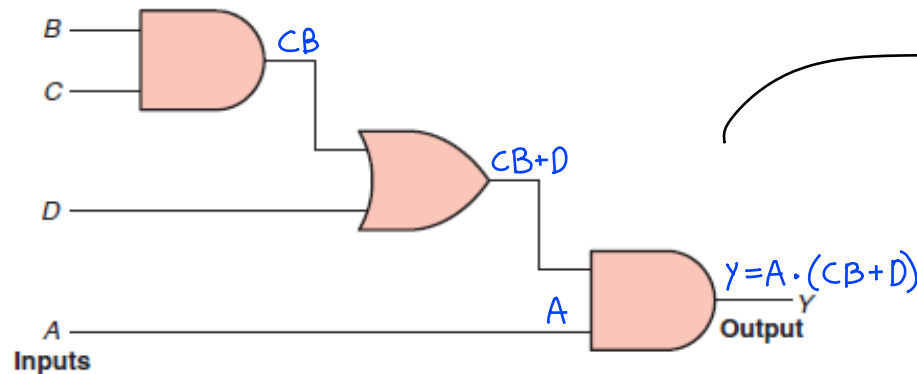

* in the next slide
!!

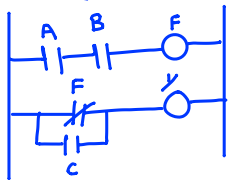

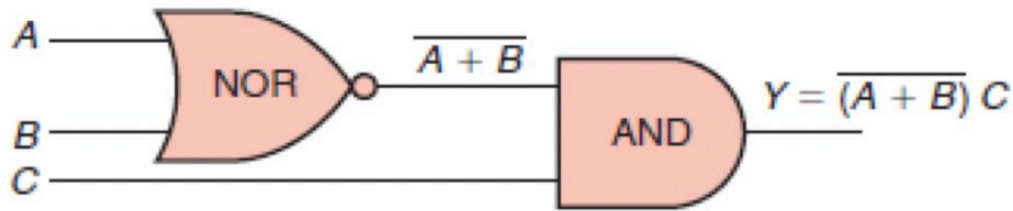


* Second Method


$$Y = \overline{(A+B)} C$$

$$A+B = D$$

$$Y = \overline{D} C$$

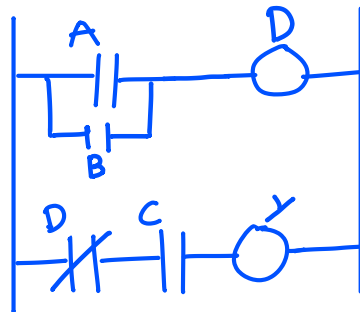

$$Y = \overline{(A+B)} C$$

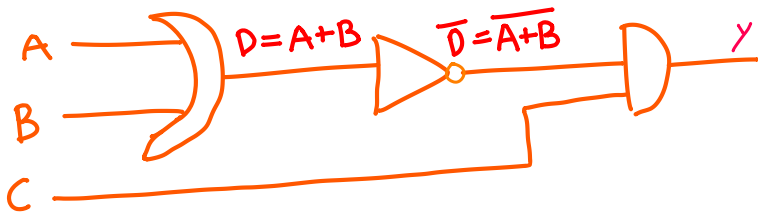


* first method



Demorgan's Theory

$$Y = \overline{(A+B)} C$$
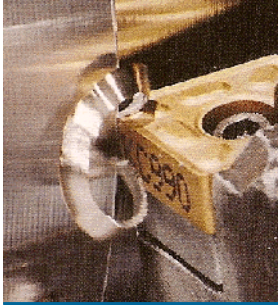
$$= \overline{A} \cdot \overline{B} \cdot C$$



Fundamentals of Logic

- **COMMUTATIVE LAW**

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

- **ASSOCIATIVE LAW**

$$(A + B) + C = A + (B + C)$$


$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

- **DISTRIBUTIVE LAW**

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$$


$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

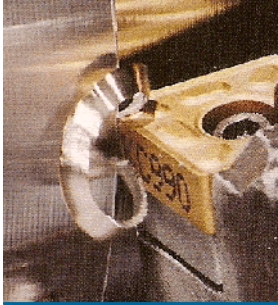This law holds true only in Boolean algebra.




Fundamentals of Logic


Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + (BC) = (A + B)(A + C)$	$A(B + C) = AB + AC$
* Absorption law	$A(A + B) = A$ *	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

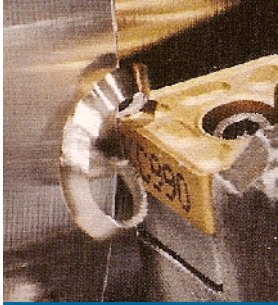

Fundamentals of Logic

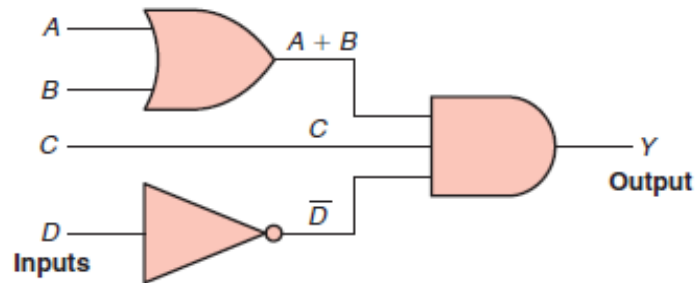


$$Y = (A + B).C.\bar{D}$$

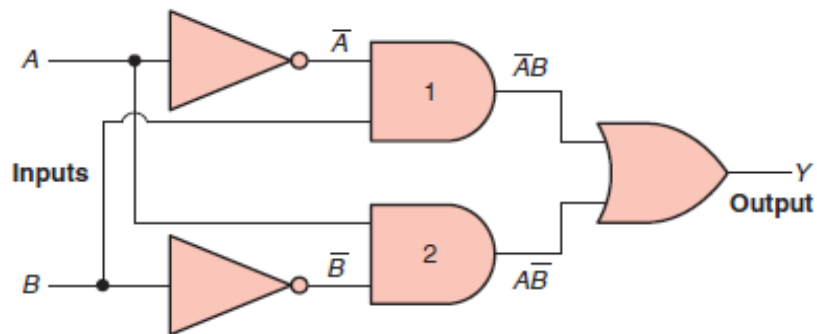


$$Y = \bar{A}B + A\bar{B}$$




Relay schematic

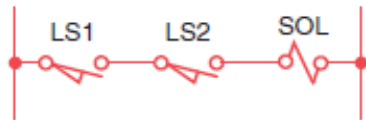

Ladder logic program

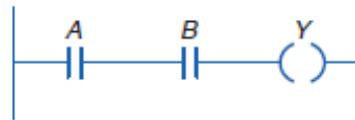


Gate logic

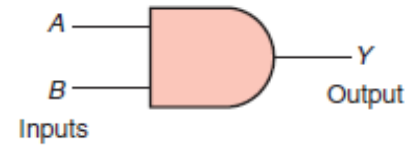


Boolean equation: $AB = Y$


Relay schematic

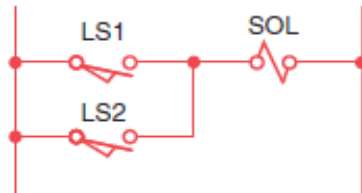

Ladder logic program

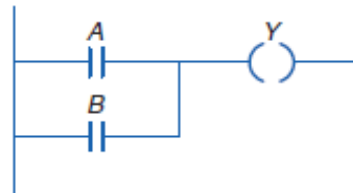


Gate logic

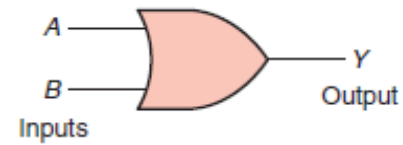


Boolean equation: $A + B = Y$


Relay schematic

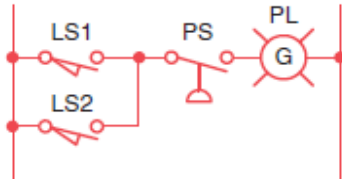

Ladder logic program

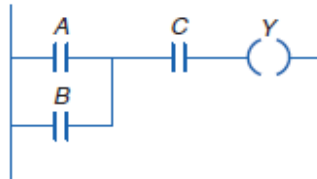


Gate logic

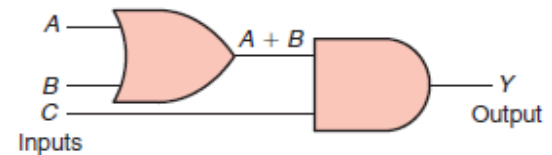


Boolean equation: $(A + B)C = Y$


Relay schematic

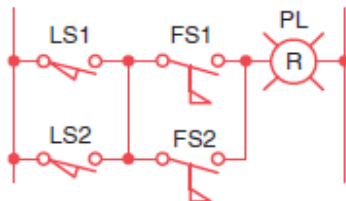





Ladder logic program

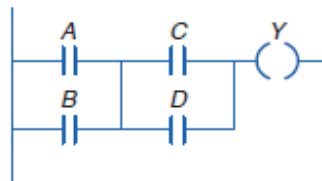

Gate logic



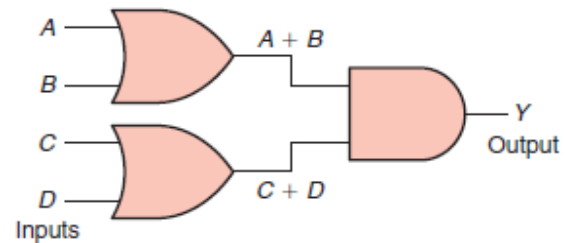


Boolean equation: $(A + B)(C + D) = Y$

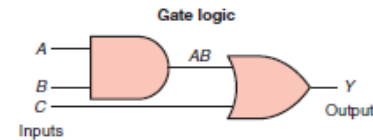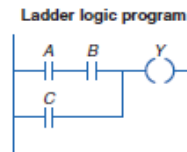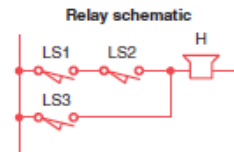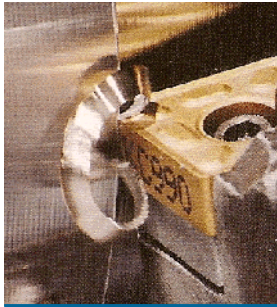




Boolean equation: $(AB) + C = Y$

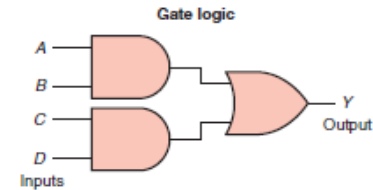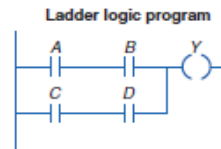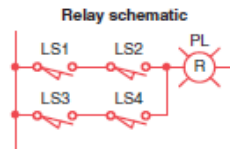Example 4-5 Two limit switches connected in series with each other and in parallel with a third limit switch, and used to control a warning horn.






Boolean equation: $(AB) + (CD) = Y$

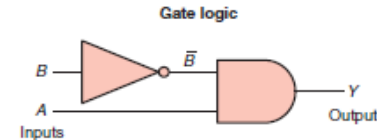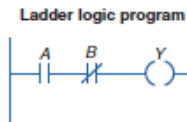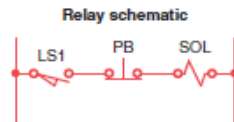Example 4-6 Two limit switches connected in series with each other and in parallel with two other limit switches (that are connected in series with each other), and used to control a pilot light.




Boolean equation: $A\bar{B} = Y$

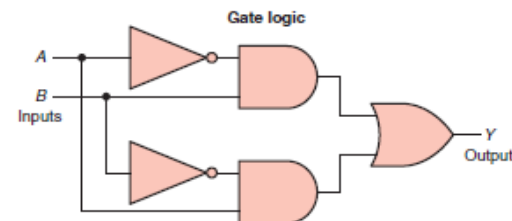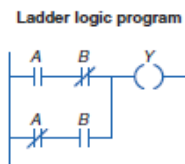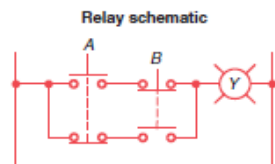Example 4-7 One limit switch connected in series with a normally closed pushbutton and used to control a solenoid valve. This circuit is programmed so that the output solenoid will be turned on when the limit switch is closed and the pushbutton is *not* pushed.




Boolean equation: $\bar{A}\bar{B} + AB = Y$
 $A \oplus B = Y$

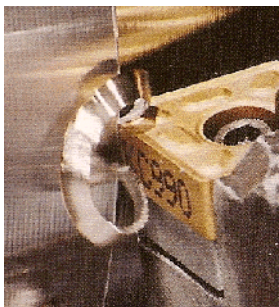Example 4-8 Exclusive-OR circuit. The output lamp of this circuit is ON only when pushbutton A or B is pressed, but not both. This circuit has been programmed using only the normally open A and B pushbutton contacts as the inputs to the program.



Fundamentals of Logic

دوائر فيها اغلاق بدنا نصلحها

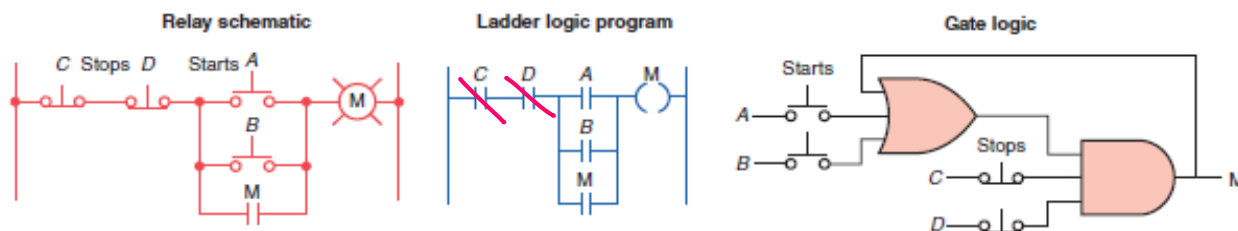

Example 4-9 A motor control circuit with two start/stop buttons. When either start button is depressed, the motor runs. By use of a seal-in contact, it continues to run when the start button is released. Either stop button stops the motor when it is depressed.

* Example :-

$$Z = \bar{A}c(\bar{A}\bar{B}\bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$= \bar{A}c(\bar{A} + \bar{B} + \bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$= \bar{A}c \cdot \bar{A} + \bar{A}\bar{B}C + \bar{A}c\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}C + \bar{A}c\bar{D} + \bar{A}B\bar{C}\bar{D}$$

$$= \bar{B}C(\underbrace{A + \bar{A}}_1) + \bar{A}\bar{D}(\underbrace{c + B\bar{C}}_{c+B})$$

$$= \bar{B}C + \bar{A}\bar{D}(c+B)$$

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{\bar{A}} = A$$

$$A \cdot \bar{A} = 0$$

$$A + A = A$$

$$A + \bar{A} = 1$$

$$\bar{A} + AB = \bar{A} + B$$

$$A + \bar{A}B = A + B$$

* Example :-

$$\bar{A}\bar{B}C + \bar{A}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$= \bar{A}\bar{B}C + (\bar{A}C\bar{D} + \bar{A}C\bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$= \bar{A}C(\bar{B} + \bar{D}) + (\bar{A}\bar{D}(\underbrace{C + B\bar{C}}_{c+B})) + A\bar{B}C$$

$$= \bar{A}C(\bar{B} + \bar{D}) + \bar{A}\bar{D}(c+B) + A\bar{B}C$$

$$= \bar{A}\bar{B}C + \bar{A}C\bar{D} + \bar{A}C\bar{D} + \bar{A}B\bar{D} + A\bar{B}C$$

$$\quad \quad \quad \underbrace{\bar{A}C\bar{D}} + \bar{B}C(\underbrace{A + \bar{A}}_1) + \bar{A}B\bar{D}$$

$$= \bar{A}C\bar{D} + \bar{B}C + \bar{A}B\bar{D}$$

$$= \bar{A}\bar{D}(c+B) + \bar{B}C$$

Boolean Simplification Algebra

$$\begin{aligned}
 & A(\bar{B} + A + \bar{B}\bar{C}(A + \bar{B}\bar{C})) \\
 &= A(\bar{B} + A + \bar{B}\bar{C}A + \bar{B}\bar{C}\bar{B}\bar{C}) \\
 &= A(\bar{B} + A + \underbrace{\bar{B}\bar{C}}_{\text{عامل مشترك}}(A + 1)) \\
 &= A(\bar{B}(\bar{C} + 1) + A) \\
 &= A(\bar{B} + A) \\
 &= \bar{A}\bar{B} + AA \\
 &= A(\bar{B} + 1) \\
 &= A
 \end{aligned}$$

$$\begin{aligned}
 & (A\bar{B}(C + BD) + \bar{A}\bar{B})C \\
 &= (\bar{A}\bar{B}C + \underbrace{\bar{A}\bar{B}BD}_{\bar{B}B=0}) + \bar{A}\bar{B}C \\
 &= \bar{A}\bar{B}C + \bar{A}\bar{B}C \\
 &= \bar{B}C(\bar{A} + \bar{A}) \\
 &= \bar{B}C
 \end{aligned}$$


$CC = C$

$$\begin{aligned}
 Z &= ABC + A\bar{B} \cdot (\bar{A} \cdot \bar{C}) \\
 &= ABC + A\bar{B} \cdot (\underbrace{\bar{A}}_A + \underbrace{\bar{C}}_C) \\
 &= \bar{A}BC + A\bar{B}A + A\bar{B}\bar{C} \\
 &= AC(\bar{B} + \bar{B}) + A\bar{B} \\
 &= A(C + \bar{B})
 \end{aligned}$$

$$\begin{aligned}
 & \bar{X}YZ + (\overline{X\bar{Y}\bar{Z}}) \\
 &= \bar{X}YZ + (\bar{X} + \bar{Y} + \bar{\bar{Z}}) \\
 &= \bar{X}YZ + (\bar{X} + \bar{Y} + Z) \\
 &= Z(\bar{X}Y + 1) + \bar{X} + \bar{Y} \\
 &= \bar{X} + \bar{Y} + Z
 \end{aligned}$$

$$\begin{aligned}
 & XY + X(Y + Z) + Y(Y + Z) \\
 &= \bar{X}Y + \bar{X}Y + XZ + \bar{Y}Y + YZ \\
 &= Y(\bar{X} + 1) + XZ + YZ \\
 &= Y(1 + Z) + XZ \\
 &= Y + XZ
 \end{aligned}$$

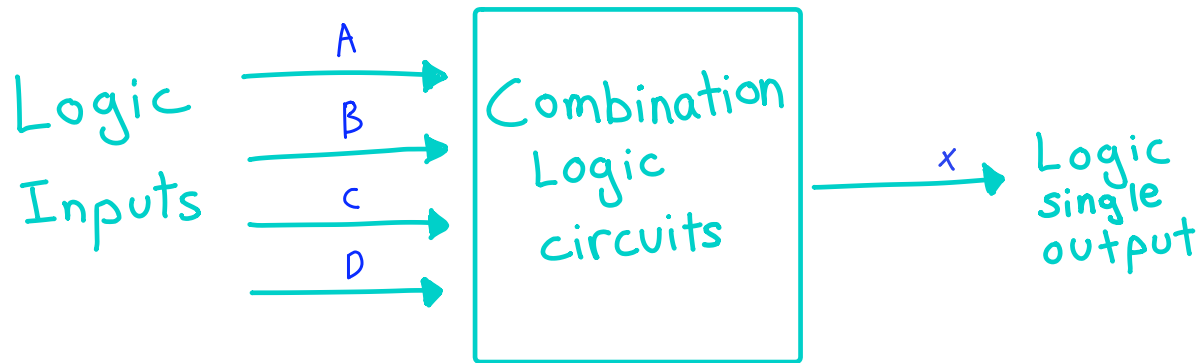
$$\begin{aligned}
 Z &= A\bar{B}\bar{C} + A\bar{B}C + ABC \\
 &= A\bar{B}\bar{C} + AC(\underbrace{\bar{B} + B}_1) \\
 &= A(\bar{B}\bar{C} + C) \\
 &= A(C + \bar{B})
 \end{aligned}$$



*based on Logic statements that converts Logic inputs into output



*example

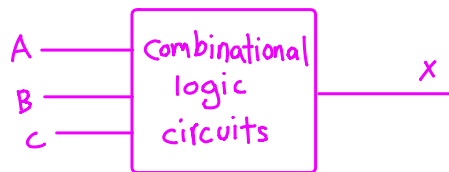

في هذا المثال ↴
Logic statment
[X is high when two or more of the inputs are high]

* Combinational Logic Circuit Design

- 1 Truth Table to connect all combinational possibilities of inputs to output
- $\rightarrow \text{No. of them} = 2^{\text{inputs}} = 2^3 = 8$

	C	B	A	X
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

في هذا الجدول
Logic statement
[X is high when two or more of the inputs are high]

- 2 Write the output as a boolean expression based on the Truth table


$$X = A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC + ABC$$


$A + A = A$
 $ABC + ABC = ABC$
 $A + \bar{A} = 1$

- 3 Simplify :-

$$\begin{aligned}
 X &= A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC + ABC + ABC + ABC \\
 &= AB(C + \bar{C}) + AC(\bar{B} + B) + BC(A + \bar{A}) \\
 &= AB + AC + BC
 \end{aligned}$$

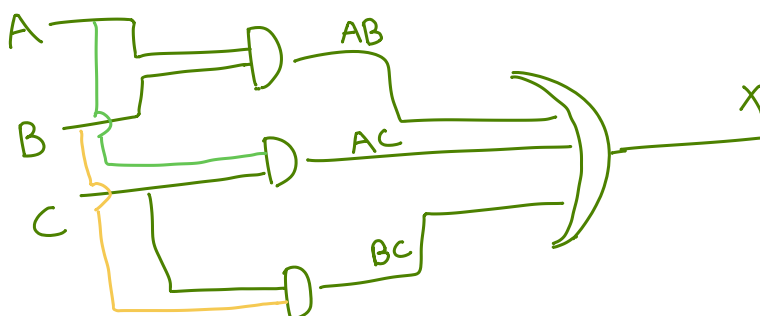- 4 Draw the Combinational Logic circuit :-



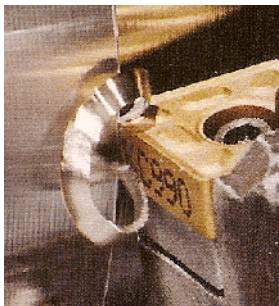

Fundamentals of Logic

Develop a logic gate circuit for each of the following Boolean expressions using AND, OR, and NOT gates:

a. $Y = ABC + D$

b. $Y = AB + CD$

c. $Y = (A + B)(\bar{C} + D)$


d. $Y = \bar{A}(B + CD)$

e. $Y = \bar{A}B + C$


f. $Y = (ABC + D)(\bar{E}\bar{F})$

* Develop a Logic Gate circuit :-


(a) $Y = ABC + D$

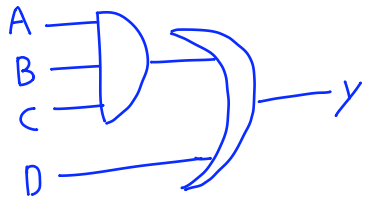


(b) $Y = AB + CD$

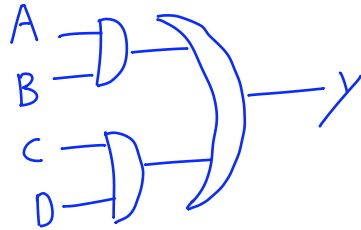


(c) $Y = (A+B)(\bar{C}+D)$

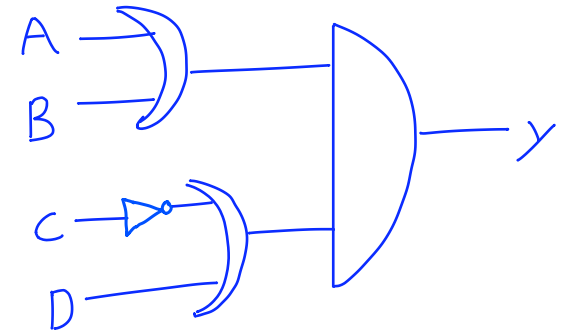


(d) $Y = \bar{A}(B+CD)$

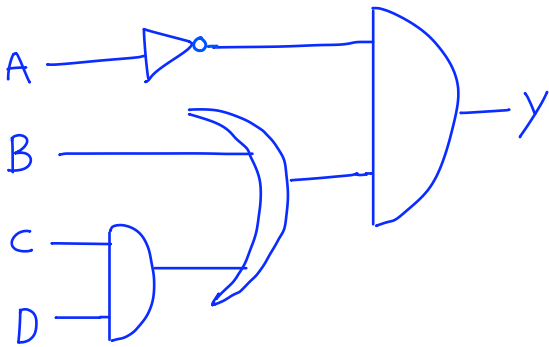

(e) $Y = \bar{A}B + C$

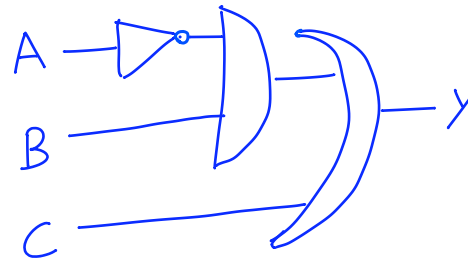


(f) $Y = (ABC+D)(E\bar{F})$

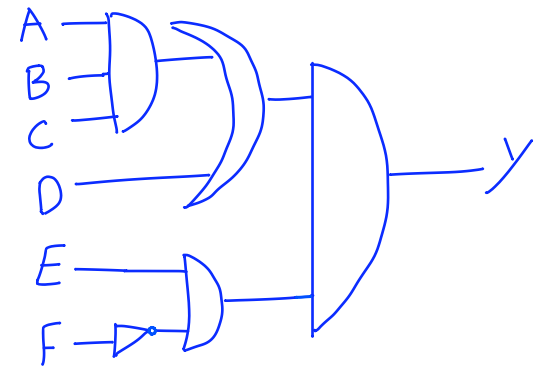

Ladder diagram :-

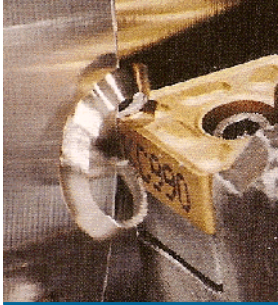- * single output
- * multiple input
- * no feedback



Fundamentals of Logic

4. Express each of the following equations as a ladder logic program:




a. $Y = (A + B)CD$

b. $Y = ABC + \bar{D} + E$

c. $Y = [(\bar{A} + \bar{B})C] + DE$

d. $Y = (\bar{A}BC) + (DEF)$

* Gates in Ladder Diagram

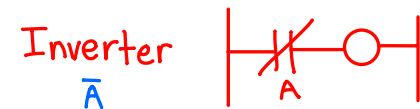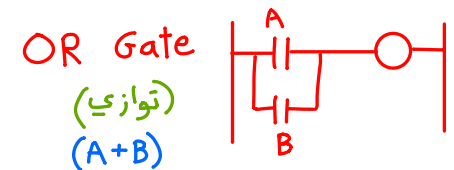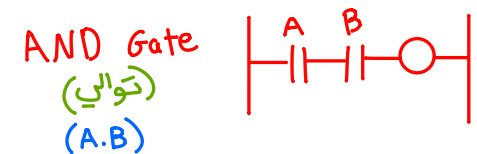

(Always start from inside the brackets)

* Express each of the following equation as a Ladder


$$Y = \overline{(\overline{A+B}) \cdot C} + DE$$

Diagram illustrating the equation $Y = \overline{(\overline{A+B}) \cdot C} + DE$ with annotations:





- The expression $(\overline{A+B}) \cdot C$ is enclosed in an orange box, labeled F .
- The entire expression $\overline{(\overline{A+B}) \cdot C} + DE$ is enclosed in a green box, labeled G .
- The expression $\overline{(\overline{A+B}) \cdot C}$ is enclosed in a pink box, labeled \overline{F} .

$$Y = \overline{(\overline{A+B}) \cdot C} + DE$$



ببداً دائماً بالجزء الداخل الأقواس

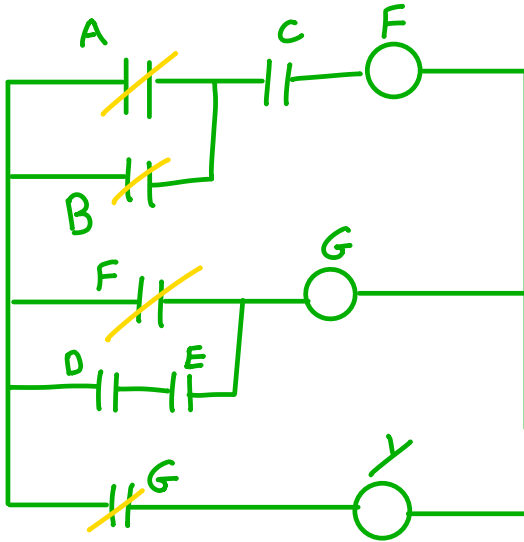

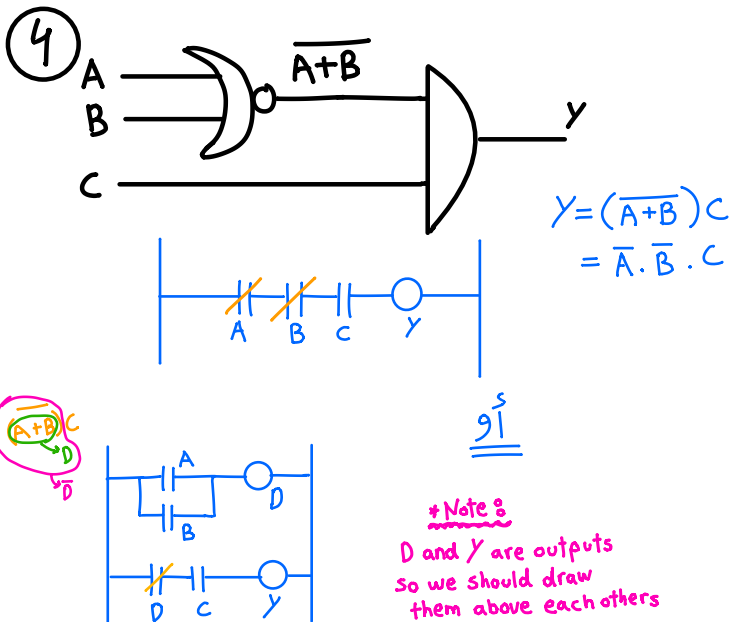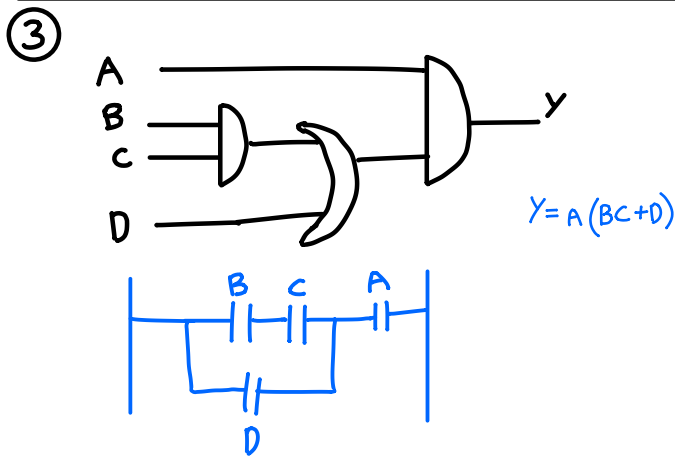
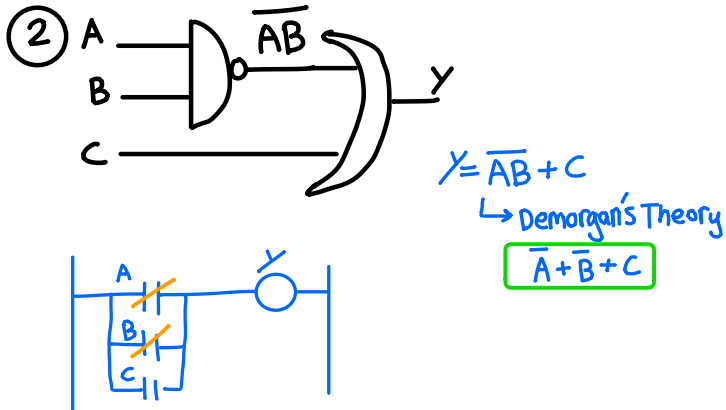
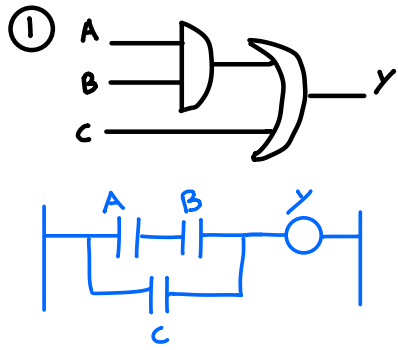
* Convert from (combinational Logic circuit) to (Ladder Diagram)




⑤ $Y = [(\overline{A+B})C] + DE$

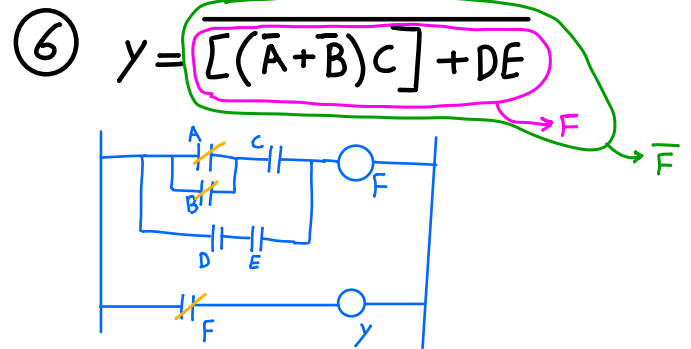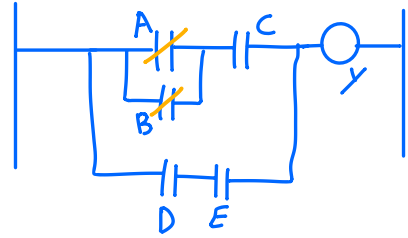

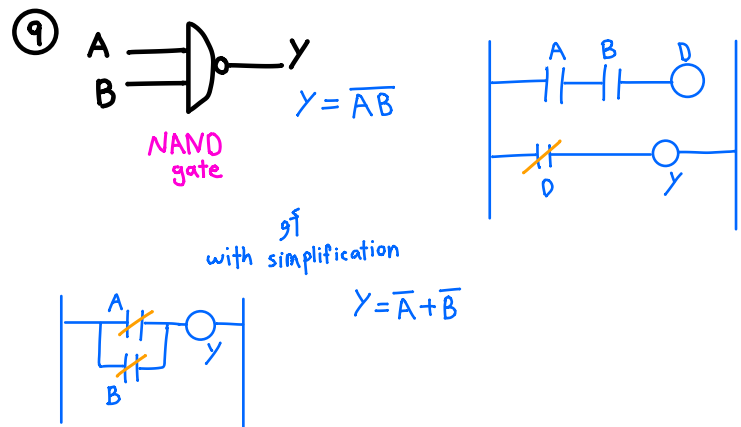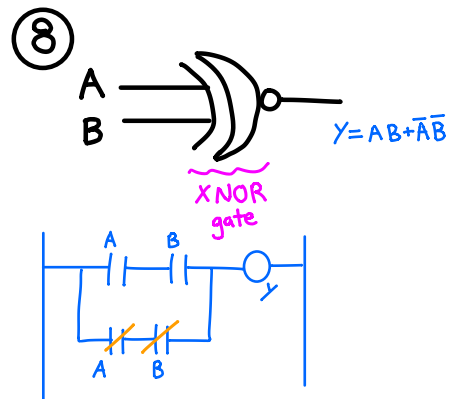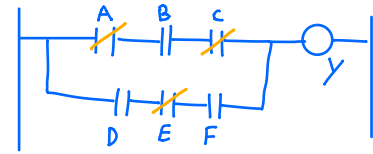⑦ $Y = (\overline{A} B \overline{C}) + (D \overline{E} F)$



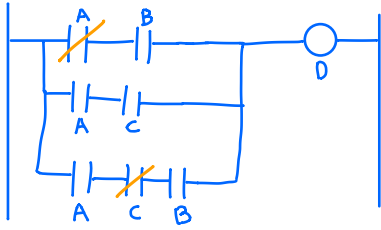⑩ $D = \bar{A} \cdot B + A \cdot C + A \cdot \bar{C} \cdot B$



أ
with simplification

$$D = \bar{A} \cdot B + \underbrace{A \cdot C + A \cdot \bar{C} \cdot B}_{\text{عامل مشترك}}$$


$$= \bar{A}B + A(C + \bar{C}B)$$

$$= \bar{A}B + A(C + B)$$

$$= \bar{A}B + AC + AB$$

$$= B(\bar{A} + A) + AC$$


$$= B + AC$$

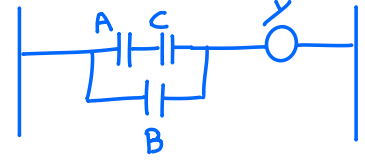

Note:-

يا برسم ال Ladder من البداية
diagram

يا بسوي Simplifications بعدين برسمه

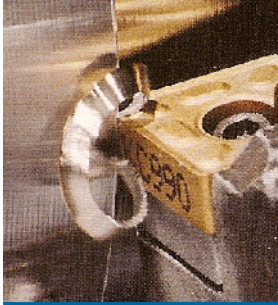


Example 1:

- On a particular piece of operator-controlled production equipment, the production process may only be performed by the operator activating two safety switches, located at some distance from each other. This is to prevent the equipment from accidentally starting whilst the operator is loading or unloading the machine. The switches have to be depressed together by the operator using both hands.

→ That means
(AND gate)

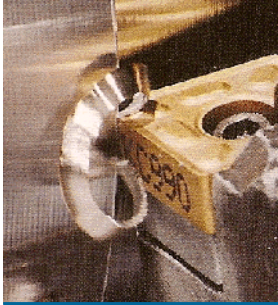- (a) What is the truth table for this operation?
- (b) What is the Boolean logic expression for this operation?
- (c) What is the **logic network diagram** for the operation?




Example 1 solution:


- (a) Where X1 is first switch, and X2 is second switch, and Y is the output of switch activation.


Inputs		Output
X1	X2	Y
0	0	0
0	1	0
1	0	0
1	1	1

- (b) $Y = X1 * X2$
- (c)

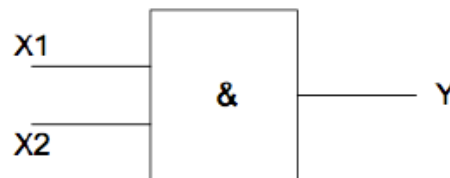

logic network diagram

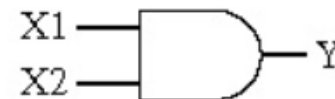

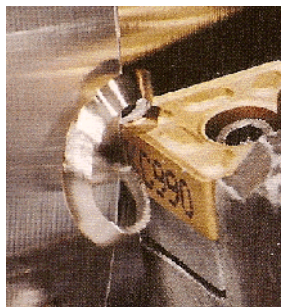

Example 2:

No push button


NC push button

Write the Boolean logic expression for the pushbutton switch system below using the following symbols:


X1 = START, X2 = STOP, Y1 = MOTOR, and Y2 = POWER-TO-MOTOR.

← X2 بتطفي
ال system
بس ما بتشغله


← X1 بتشغل
ال system
بس ما بتطفئه

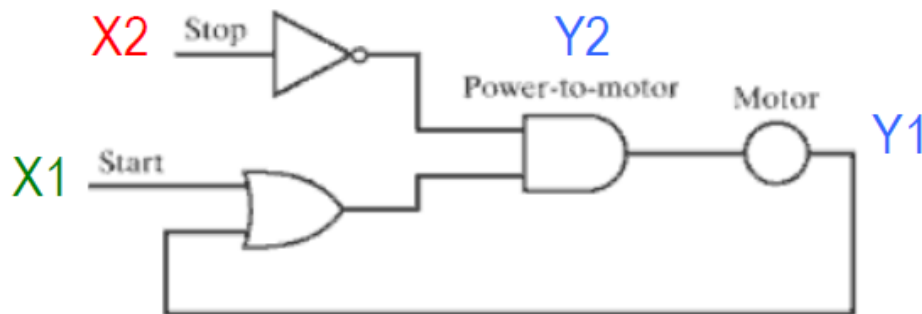

logic network diagram

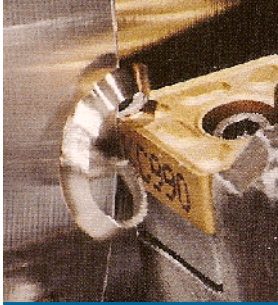

Example 2 Solution:

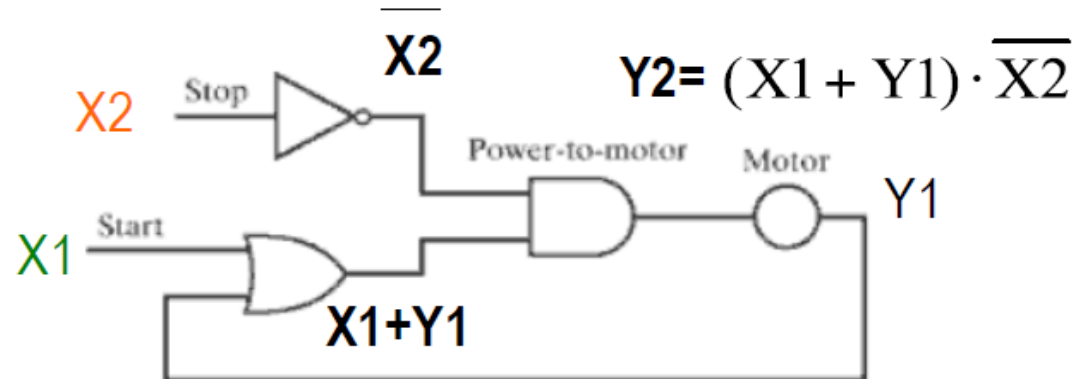

Truth Table

$$= \overline{X_2}(X_1 + Y_1)$$


Start	Stop	Motor	Power-to-Motor
0	0	0	0
0	1	0	0
1	0	0	1
X 1	1	0	0
0	0	1	1
0	1	1	0
1	0	1	1
X 1	1	1	0

This Truth table :-

→ Logically is correct

→ but in Reality it is not correct

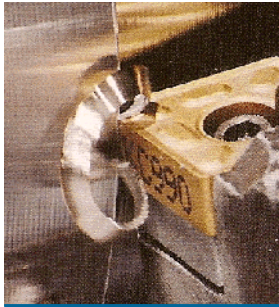
the Automation is sequencing Logic events




Sequencing

A switching system that uses internal timing devices to determine when to initiate changes in output variables

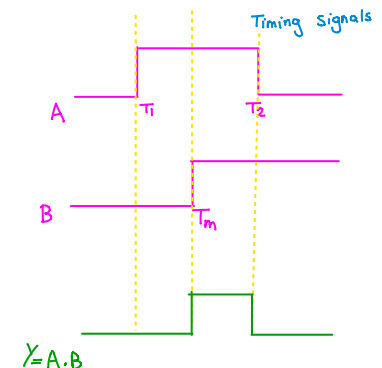
- Examples: Washing machines, dryers, dishwashers, Traffic light.



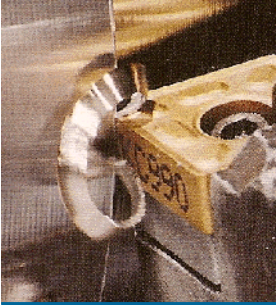


Sequencing

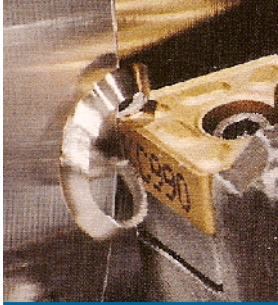
- Outputs are usually generated “open loop”
 - No feedback that control function is executed
- Sequence of output signals is usually cyclical, as in a high production work cycle
 - The signals occur in the same repeated pattern within each regular cycle
- Common sequencing devices:
 - Timer – output switches on/off at preset times
 - Counter – counts electrical pulses and stores them



Ladder Logic Diagrams

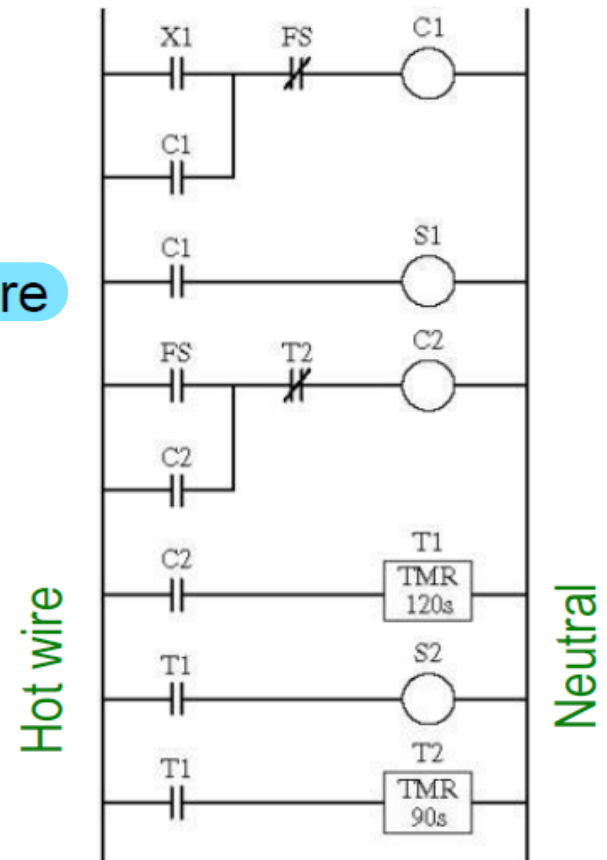- Another way for drawing Logic Network Diagrams.
- A diagram where logic elements are displayed along horizontal lines (rungs) connecting two rails.
- Combines both: logic and sequencing control.




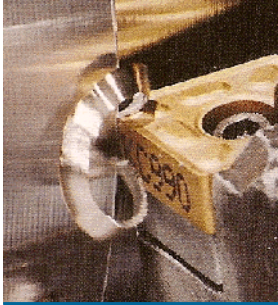


Ladder Logic Diagrams


- Components of Ladder Diagrams:

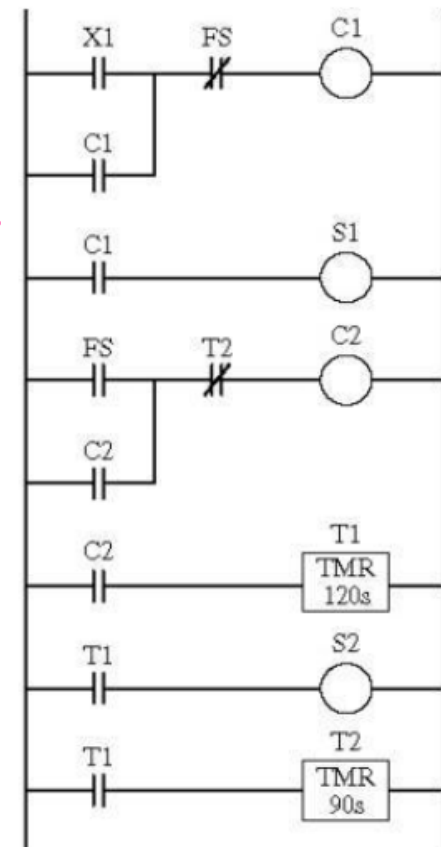1. **Contacts** - logical inputs, e.g., limit switches, photo-detector.
2. **Loads (coils)** - outputs, e.g., motors, lights, alarms, solenoids.
3. **Timers** - to specify length of delay.
4. **Counters** - to count pulses received




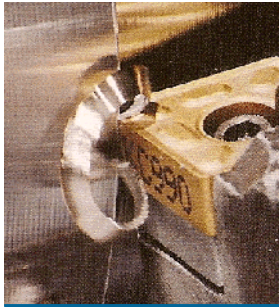

Components of Ladder Logic Diagram

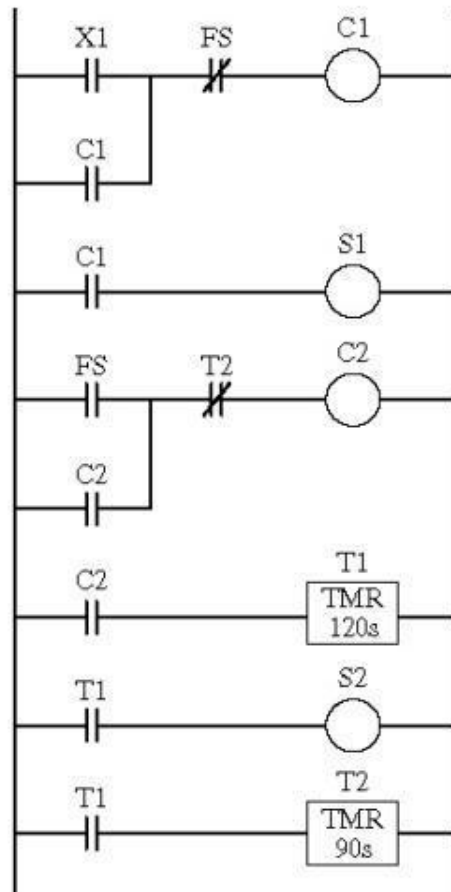



Ladder symbol	Hardware component
(a)	Normally open contacts (switch, relay, other ON/OFF devices)
(b)	Normally closed contacts (switch, relay, etc.)
(c)	Output loads (motor, lamp, solenoid, alarm, etc.)
(d)	Timer
(e)	Counter

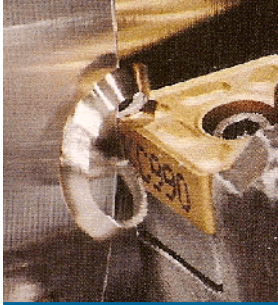


Example 1

- Construct the ladder logic diagrams for the **AND** gate.
(series)

- Solution:

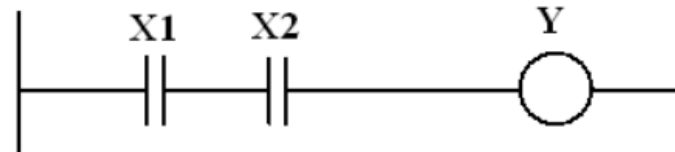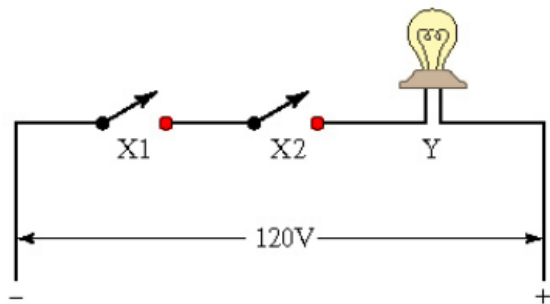


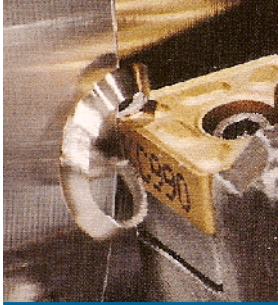



Example 2

- Construct the ladder logic diagrams for the OR gate.



(parallel)

- Solution:

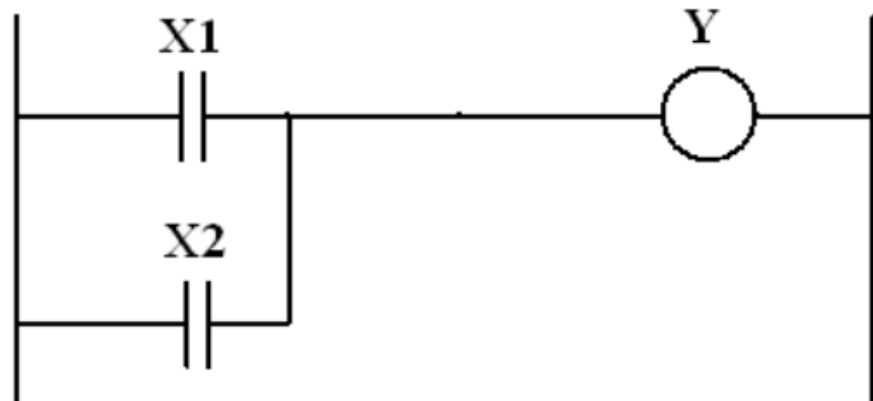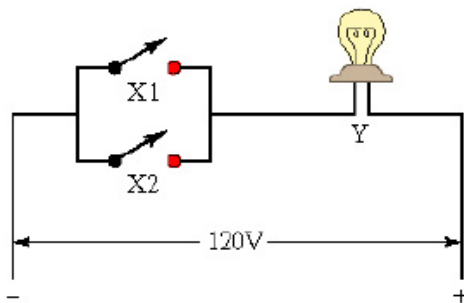


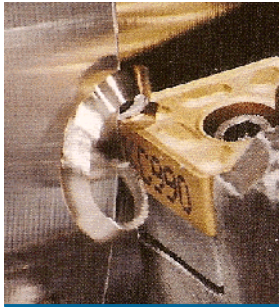


Example 3

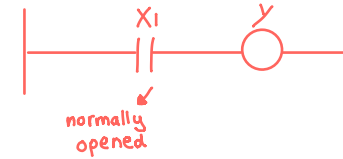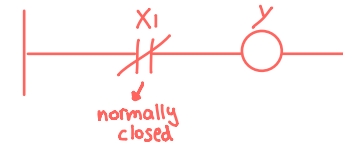

- Construct the ladder logic diagrams for the **NOT** gate.

- Solution:**

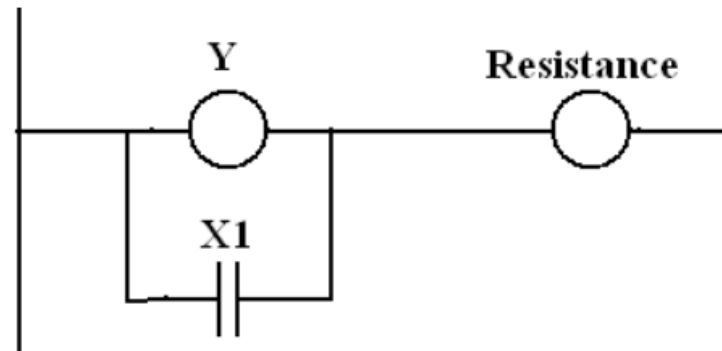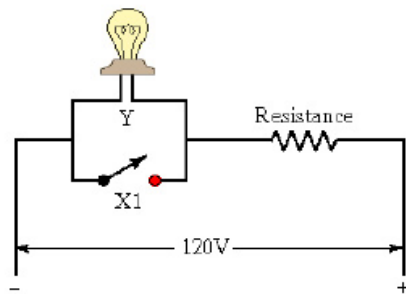

التيار سوف يمر بـ X_1 لما نسكّر switch لأنّها short circuit فـ الـ LED سوف ينطفئ

$$X_1 : 0 \rightarrow Y : 1$$

$$X_1 : 1 \rightarrow Y : 0$$



Example 4


- Construct the ladder logic diagrams for the **NAND** gate.

- Solution:**




$$Y = \overline{X_1 \cdot X_2} \rightarrow \text{we can simplify } \overline{X_1} + \overline{X_2}$$

(a) NAND		
Inputs		Output
X1	X2	$Y = \overline{X_1 \cdot X_2}$
0	0	1
0	1	1
1	0	1
1	1	0

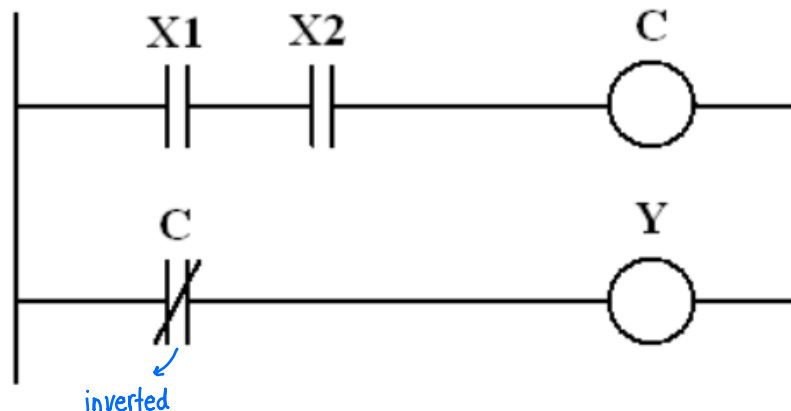


- If X1 or X2 remain open then C coil is unexcited and C contact remains closed, therefore Y is on.
- If X1 and X2 are closed then C coil is excited and C contact is opened and Y is off

Y عكس C

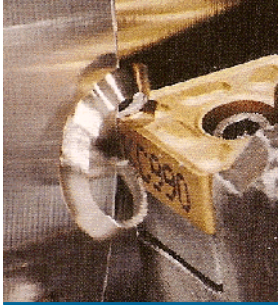


Example 5


- Construct the ladder logic diagrams for the **NOR gate.**

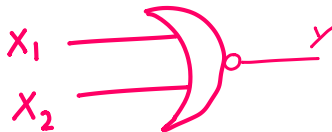- Solution:** 

(b) NOR		
Inputs		Output
X1	X2	$Y = \overline{X1 + X2}$
0	0	1
0	1	0
1	0	0
1	1	0

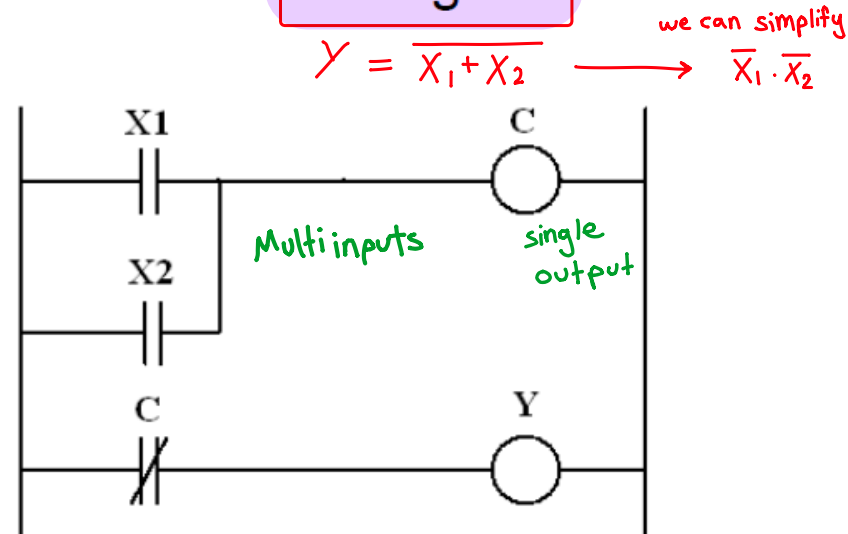



- If X1 and X2 remain open then C coil is unexcited and C contact remains closed, therefore Y is on.
- If X1 or X2 are closed then C coil is excited and C contact is opened and Y is off

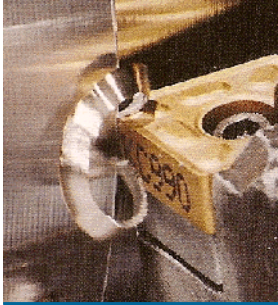


Example 6: Safety switches

- The production process may only be performed when the operator activates two spring activated safety switches. The switches have to be depressed and held closed together by the operator using both hands

→ AND

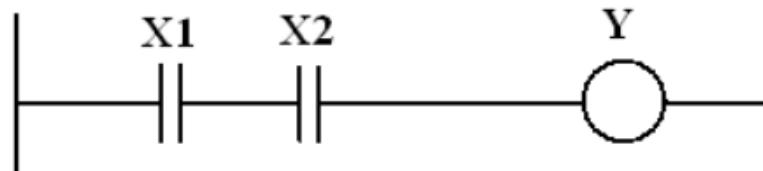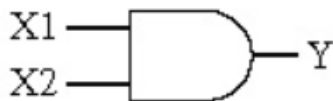


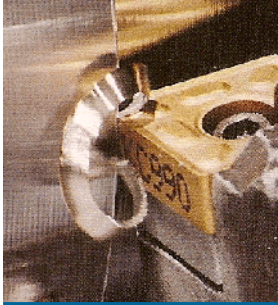

Example 7: Push Button



- Create ladder logic diagram for Push Button switch.


مهم

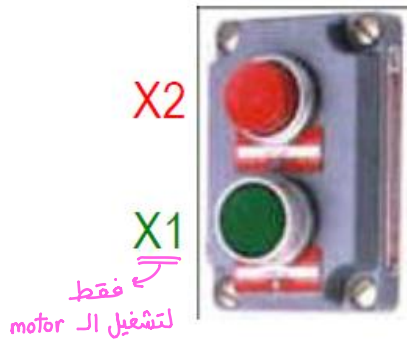

$(X1 \text{ OR } Y1) \text{ AND } (\text{NOT } X2)$

$$(X1 + Y1) \cdot \overline{X2}$$

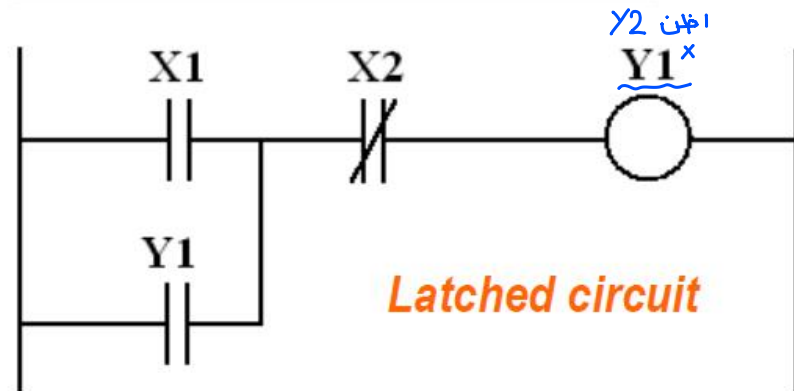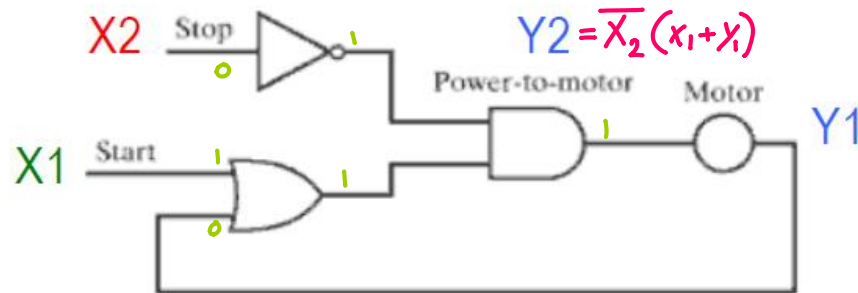

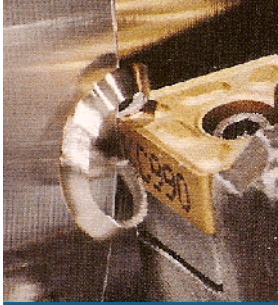

Example 8

- A motor controlled by stop and start push button switches.
- One signal light must be illuminated when the power is applied to the motor and another when it is not applied.


$X_1 \rightarrow \text{ON only}$
 $X_2 \rightarrow \text{OFF only}$

X_1 oring with Y_1

عشان بس اكبس X_1
 اكر من مرة يفشل شغال
 طبيعي و بس اكبس X_2 يسكن

Multi inputs

Single output

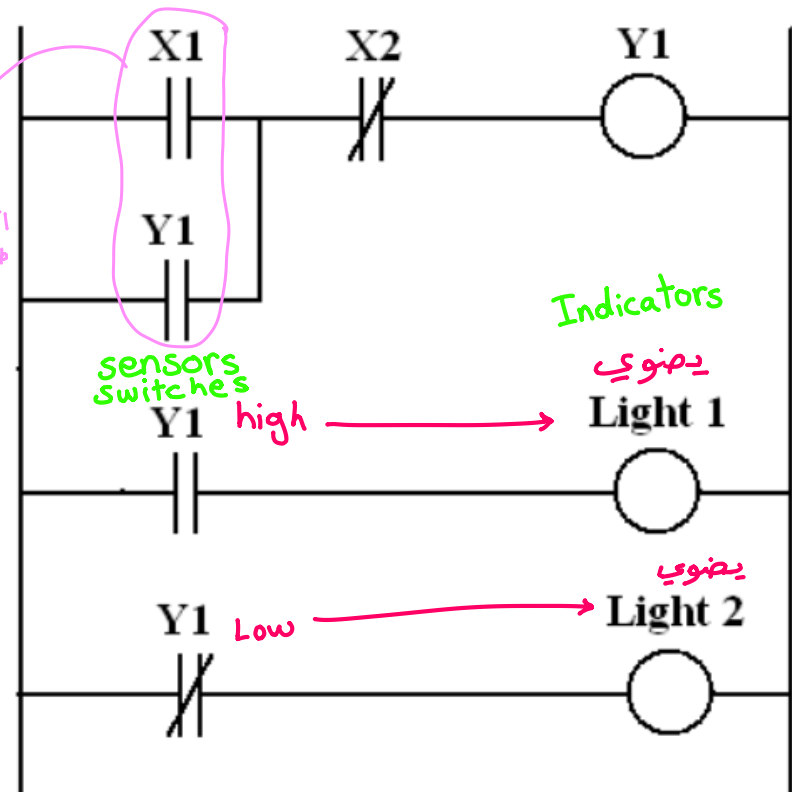

كل Rung عبارة عن
 one event


Indicators

يضوي

Light 1

يضوي

Light 2

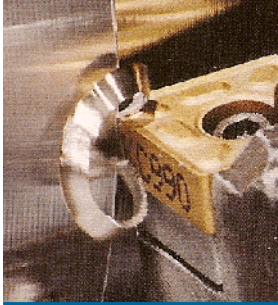


Example 9.5 Control Relay



electro magnetic device

يتحكم

- A control relay can be used to control on/off actuation of a powered device at some remote location. It can also be used to define alternative decisions in logic control. Construct the ladder logic diagram of a control relay.


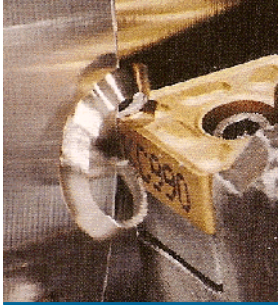


Example 9.5 Control Relay

important

- Electromagnetic relay is an electronic control device. It has a control system (also called an input loop) and a controlled system (also called an output loop). It is usually used in automatic control circuits. It actually a kind of "automatic switch" that uses a smaller current and a lower voltage to control a larger current and a higher voltage.

X_1	C_1	Y_1	Y_2
1	1	0	1
0	0	1	0

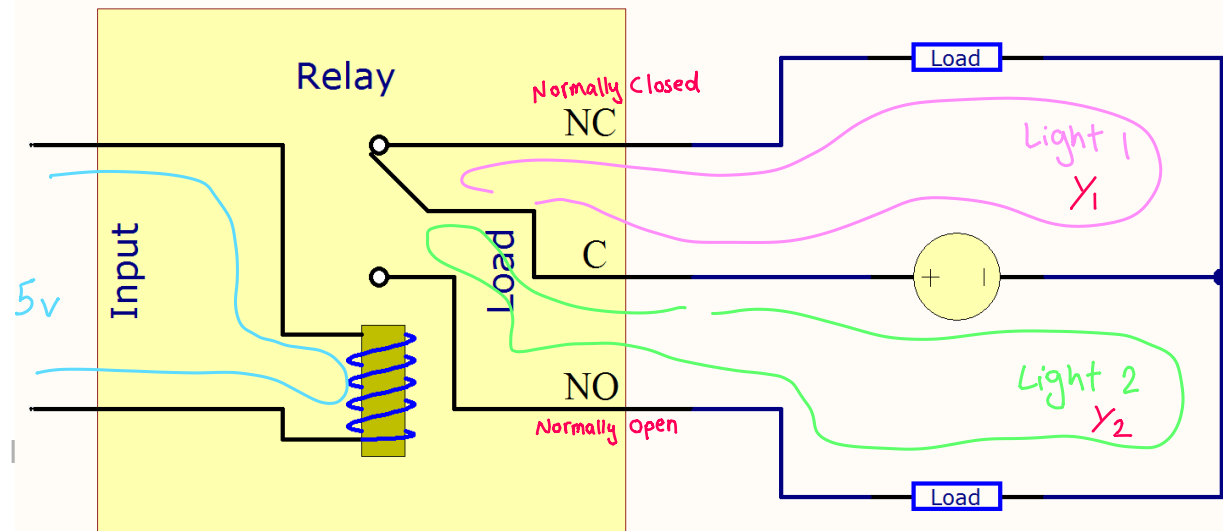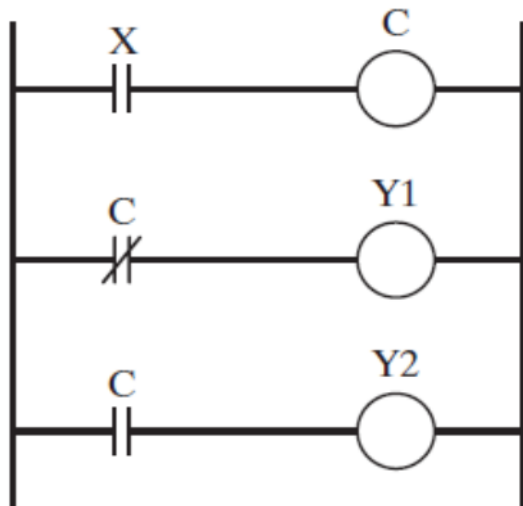



Example 9.6 Fluid Storage Tank

هدف هذا المثال
دراسة ال dependencies
between inputs and outputs

- Consider the fluid storage tank illustrated in Figure 9.10.

- When the start button X1 is depressed this closes the control relay C1, which energizes solenoid S1, which opens a valve allowing fluid to flow into the tank.

- When the tank becomes full, the float switch FS closes, which opens relay C1, causing the solenoid S1 to be de-energized, thus turning off the in-flow.

- Switch FS also activates timer T1, which provides a 120-sec delay for a certain chemical reaction to occur in the tank.



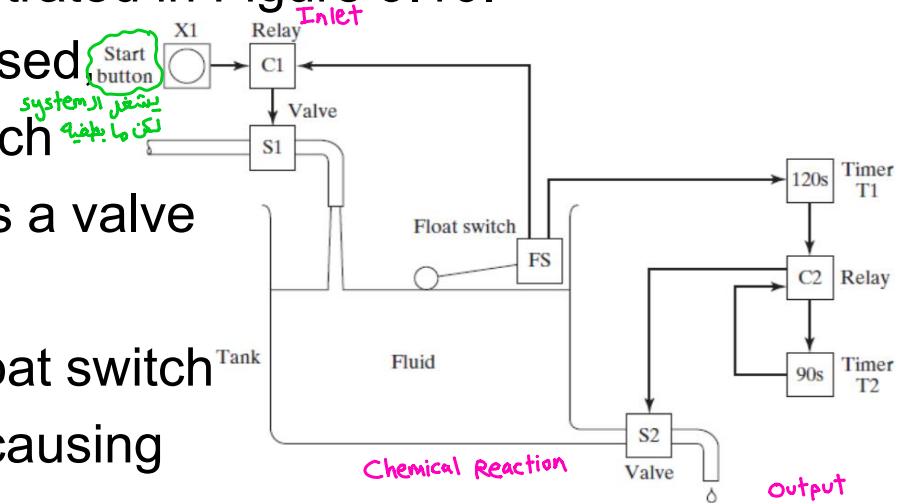



Figure 9.10 Fluid filling operation of Example 9.6.

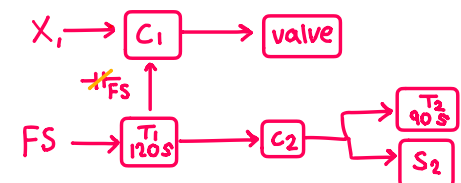

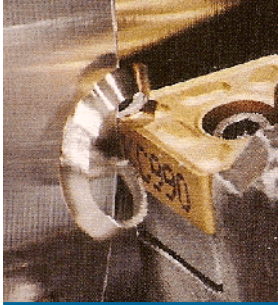

Example 9.6 Fluid Storage Tank

- At the end of the delay time, the timer energizes a second relay C2, which controls two devices: (1) It initiates timer T2, which
- waits 90 sec to allow the contents of the tank to be drained, and (2) it energizes solenoid S2, which opens a valve to allow the fluid to flow out of the tank.
- At the end of the 90 sec, the timer breaks the current and de-energizes solenoid S2, thus closing the out-flow valve.
- Depressing the start button X1 resets the timers and opens their respective contacts.

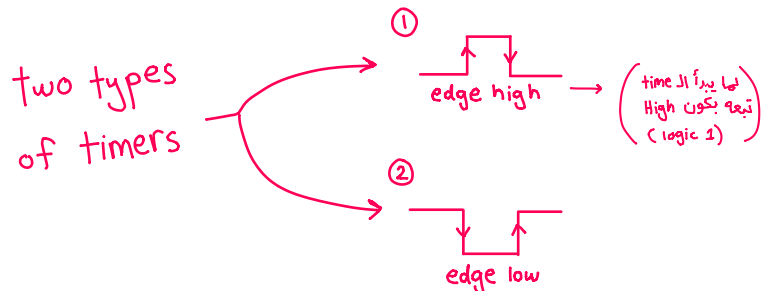



Example 9.6 Fluid Storage Tank



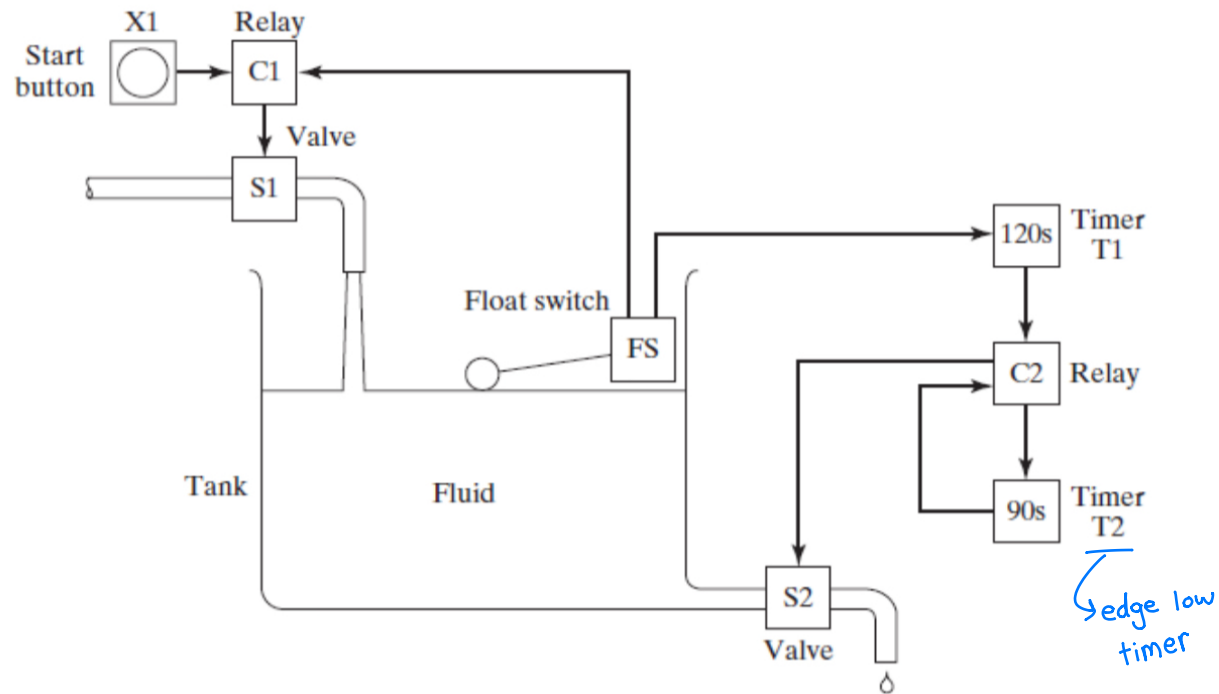
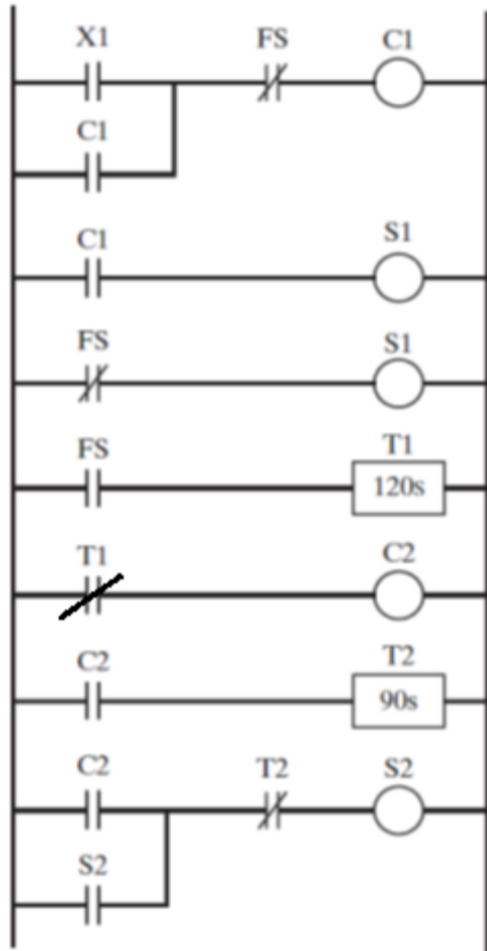


Figure 9.10 Fluid filling operation of Example 9.6.

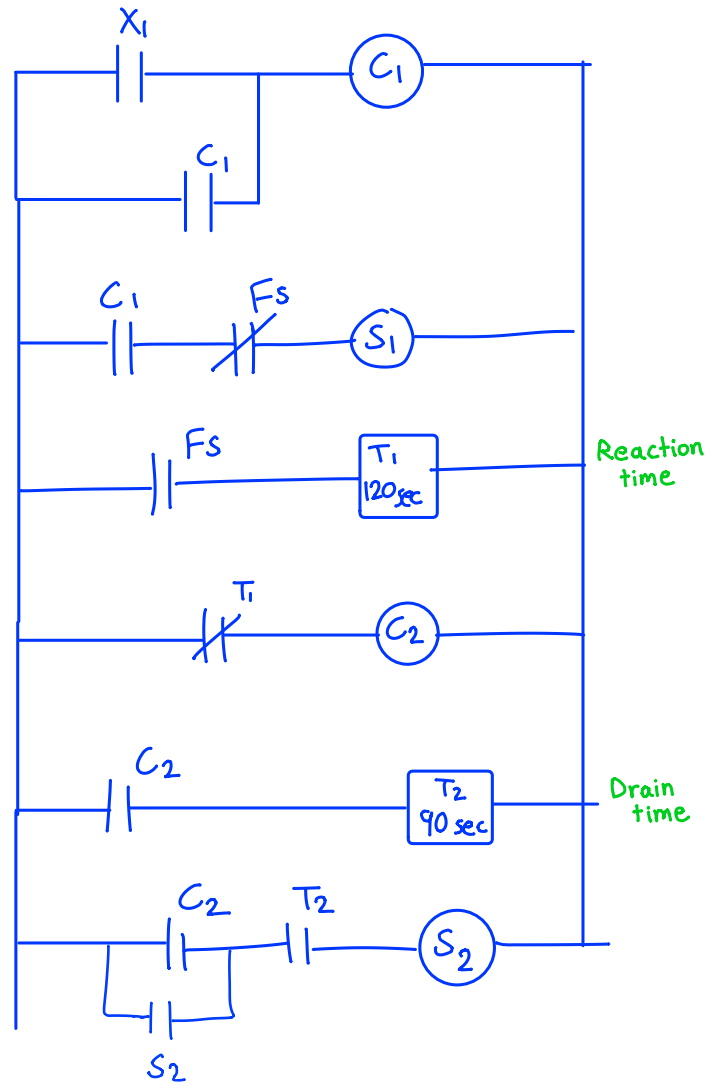
Timer will be logic 1 when it's time is expired.



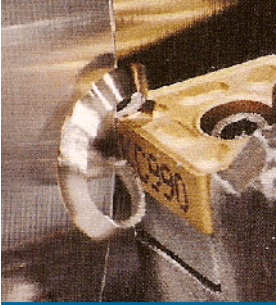

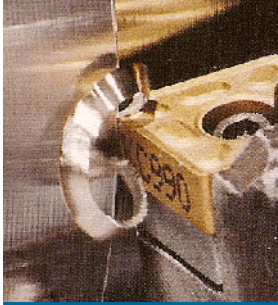
Question

- An industrial robot performs a machine loading and unloading operation. A PLC is used as the cell controller. The cell operates as follows:
 - (1) a human worker places a part into a nest,
 - (2) the robot reaches over and picks up the part and places it into an induction heating coil,
 - (3) a time of 10 sec is allowed for the heating operation, and (
 - 4) the robot reaches into the coil, retrieves the part, and places it on an outgoing conveyor.



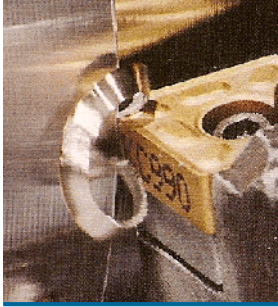
Question

- A limit switch X1 (normally open) is used to indicate that the part is in the nest in step (1). This energizes output contact Y1 to signal the robot to execute step (2) of the work cycle (this is an output contact for the PLC, but an input interlock signal for the robot controller).
- A photocell X2 is used to indicate that the part has been placed into the induction heating coil C1.
- Timer T1 is used to provide the 10-sec heating cycle in step (3), at the end of which, output contact Y2 is used to signal the robot to execute step (4).
- Construct the ladder logic diagram for the system



Answer ::

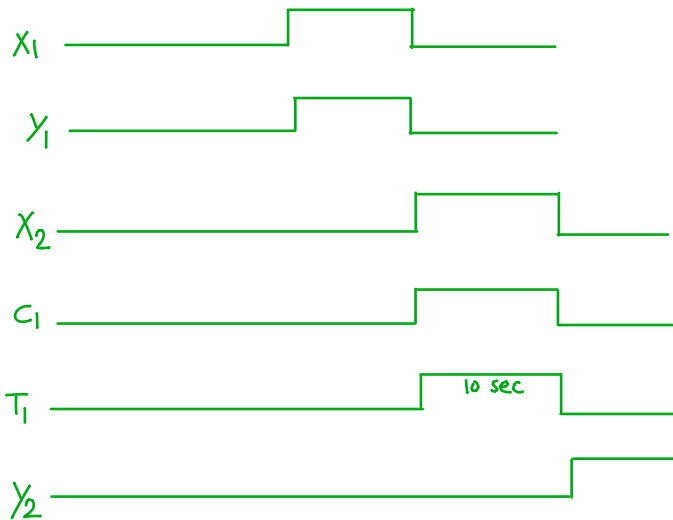→ c_1 is on if the timer is on and there is a part on heating coil





inputs $\rightarrow X_1, X_2$

Timers $\rightarrow T_1$

outputs $\rightarrow Y_1$ robot signal nest \rightarrow heating coil
 $\rightarrow C_1$ heating coil
 $\rightarrow Y_2$ robot signal


Ladder diagram

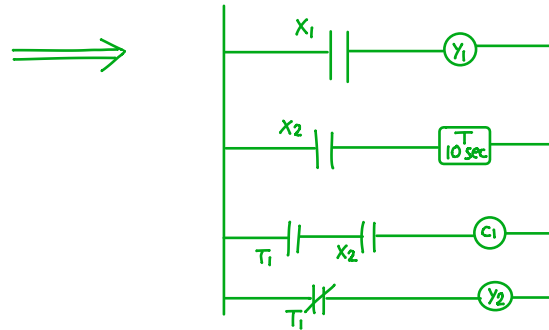

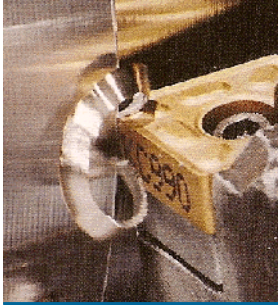


Another Question:

- An emergency stop system is to be designed for a certain automatic production machine.
- A single “start” button is used to turn on the power to the machine at the beginning of the day.
- In addition, there are two “stop” buttons located at two locations on the machine, either of which can be pressed to immediately turn off power to the machine.
- Let $X1$ = start button (normally open), $X2$ = stop button 1 (normally closed), $X3$ = stop button 2 (normally closed), and Y = power to the machine.

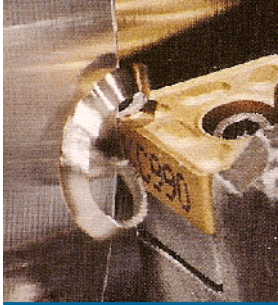


Another Question:

- (a) Construct the truth table for this system.
- (b) Write the Boolean logic expression for the system.
- (c) Construct the ladder logic diagram for the system.

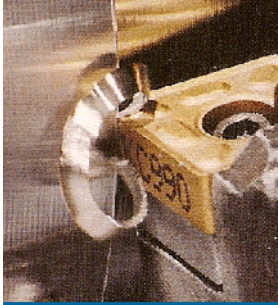


Sec 9.3: Programmable Logic Controller (PLC)


- https://www.youtube.com/watch?v=PbAGI_mv5XI
- <https://www.youtube.com/watch?v=pPUnihpL6UI>
- <https://www.youtube.com/watch?v=wICG8d2iQ5c>

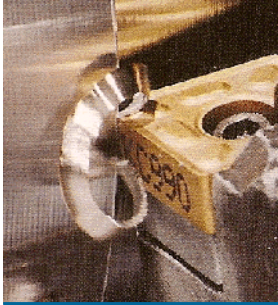

Sec 9.3: Programmable Logic Controller (PLC)

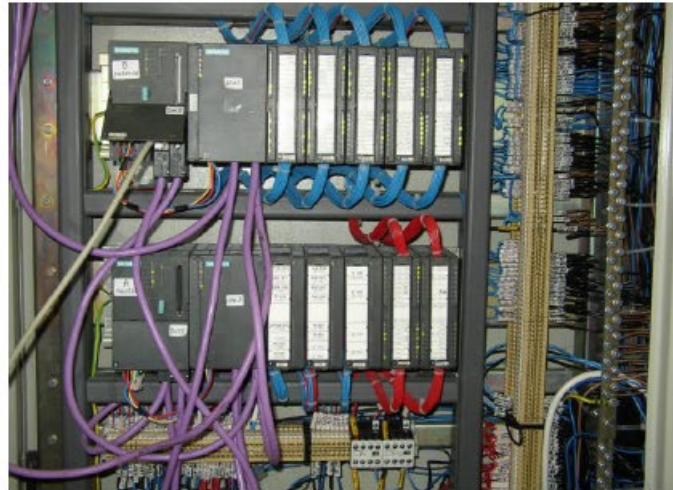- A microcomputer-based controller that uses stored instructions in programmable memory to implement logic, sequencing, timing, counting, and arithmetic functions through digital or analog modules, for controlling machines and processes.



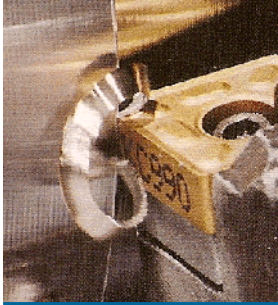

Components of a PLC



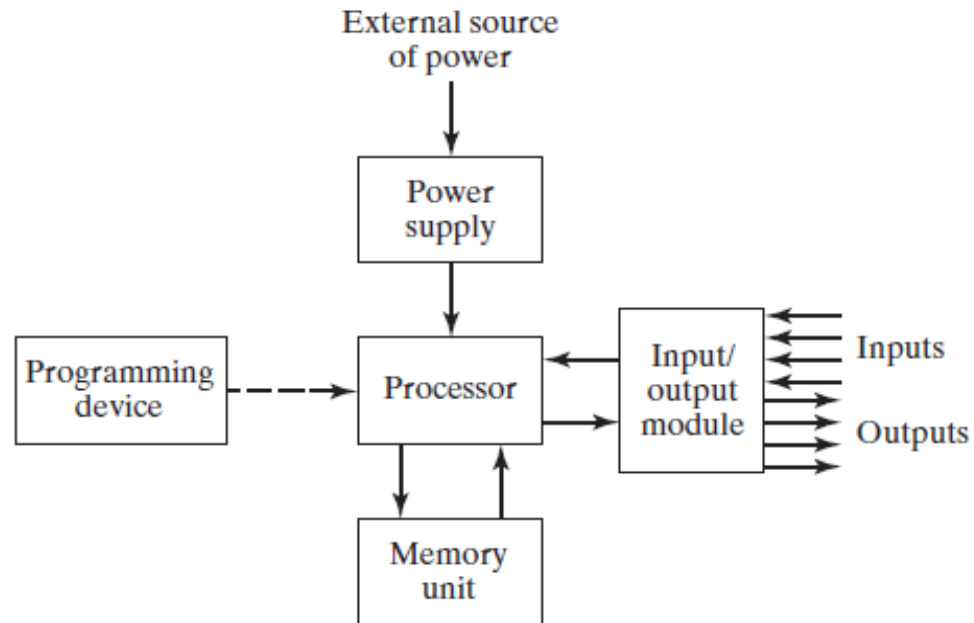


Figure 9.11 Components of a PLC.

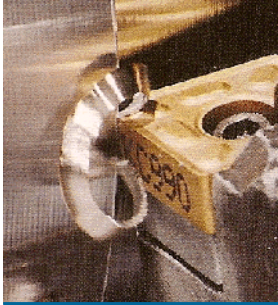


Advantages of PLCs Compared to Relay Control Panels

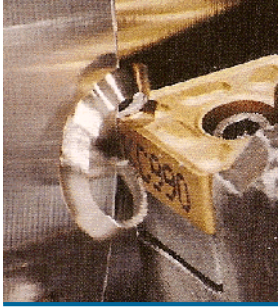- Programming a PLC is easier than wiring a relay control panel
- PLC can be reprogrammed
- PLCs take less floor space
- Greater reliability, easier maintenance
- PLC can be connected to computer systems (CIM)
- PLCs can perform a greater variety of control functions




Typical PLC Operating Cycle

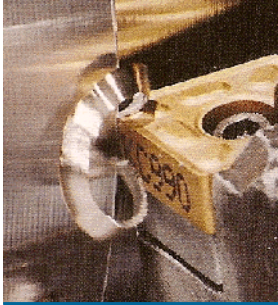1. **Input scan** – inputs are read by processor and stored in memory
2. **Program scan** – control program is executed
 - Input values stored in memory are used in the control
 - logic calculations to determine values of outputs
3. **Output scan** – output values are updated to agree with
 - calculated values
 - Time to perform the three steps (scan time) varies between 1 and 25 msec




PLC Programming

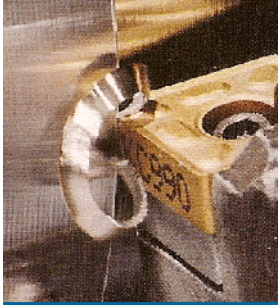- Graphical languages:
 1. Ladder logic diagrams – most widely used
 2. Function block diagrams – instructions composed of operation blocks that transform input signals
 3. Sequential function charts – series of steps and transitions from one state to the next (Europe)
- Text-based languages:
 1. Instruction list - low-level computer language
 2. Structured text – high-level computer language




PLC Programming

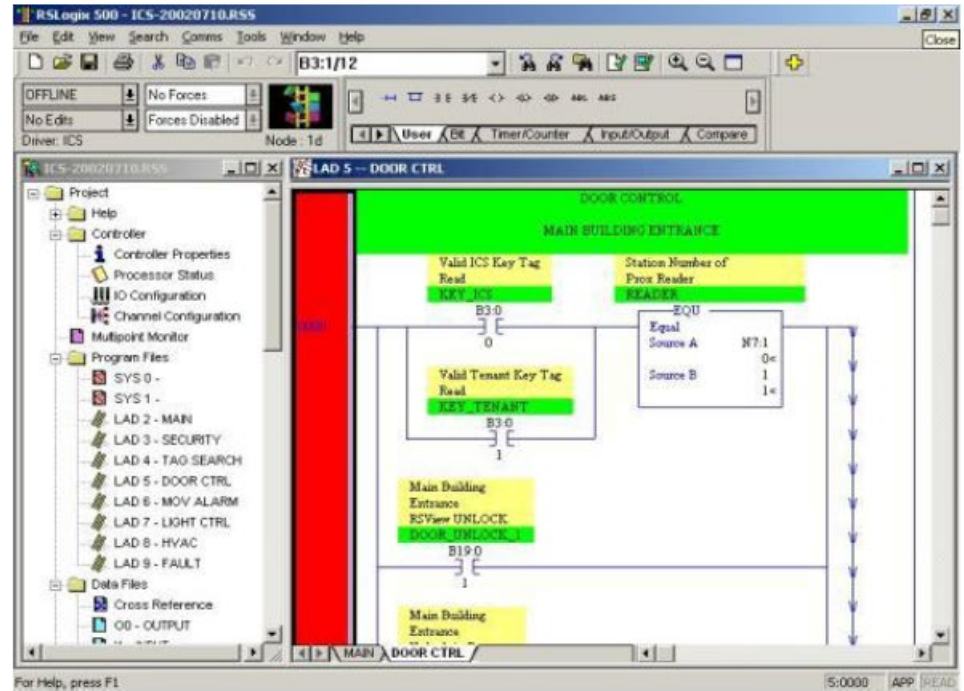

أهم اشي تحديد
 inputs
 outputs
 كيف يرتبطو مع بعض

PLC Questions

An Industrial Robot

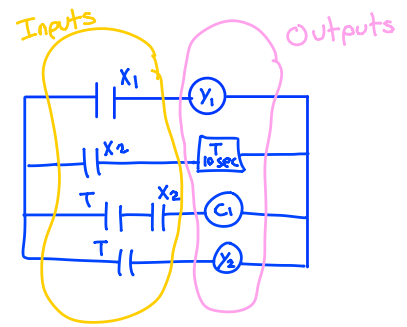

An industrial robot performs a machine loading and unloading operation. A PLC is used as the cell controller. The cell operates as follows:

- (1) a human worker places a part into a nest,
- (2) the robot reaches over and picks up the part and places it into an induction heating coil,
- (3) a time of 10 sec is allowed for the heating operation, and (
- 4) the robot reaches into the coil, retrieves the part, and places it on an outgoing conveyor.

A limit switch X1 (normally open) is used to indicate that the part is in the nest in step (1). This energizes output contact Y1 to signal the robot to execute step (2) of the work cycle (this is an output contact for the PLC, but an input interlock signal for the robot controller).

A photocell X2 is used to indicate that the part has been placed into the induction heating coil C1.

Timer T1 is used to provide the 10-sec heating cycle in step (3), at the end of which, output contact Y2 is used to signal the robot to execute step (4).

Construct the ladder logic diagram for the system

* Inputs

X₁: limit switch
part on the nest

X₂: photocell
part on heating coil

* Timer

T: 10 sec

* outputs


Y₁: Robot signal
nest → heating coil



Y₂: Robot signal
heating coil → conveyor

C₁: heating coil

لبسبب تنشيل
 X₁
 اشتغل
 Y₁

يعملون
 في نفس
 الوقت

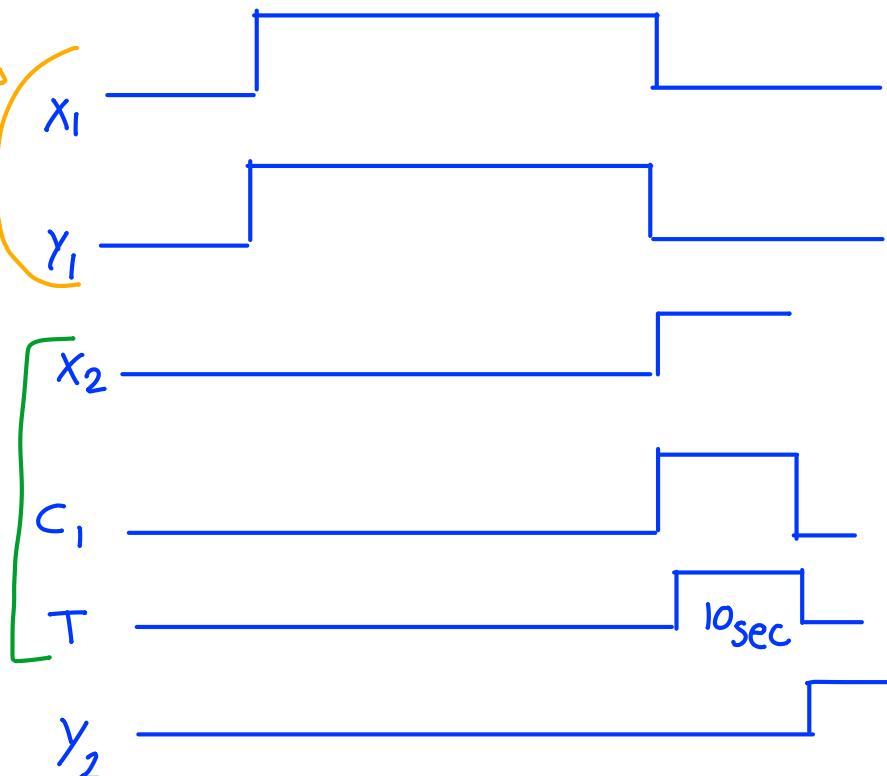

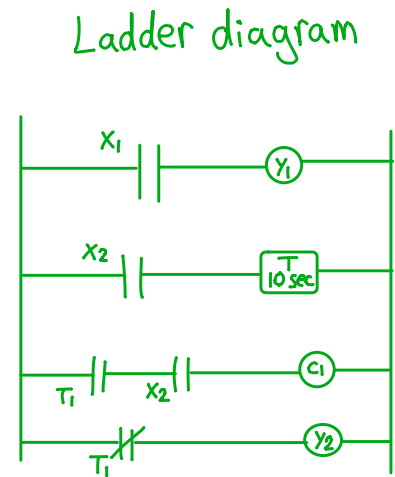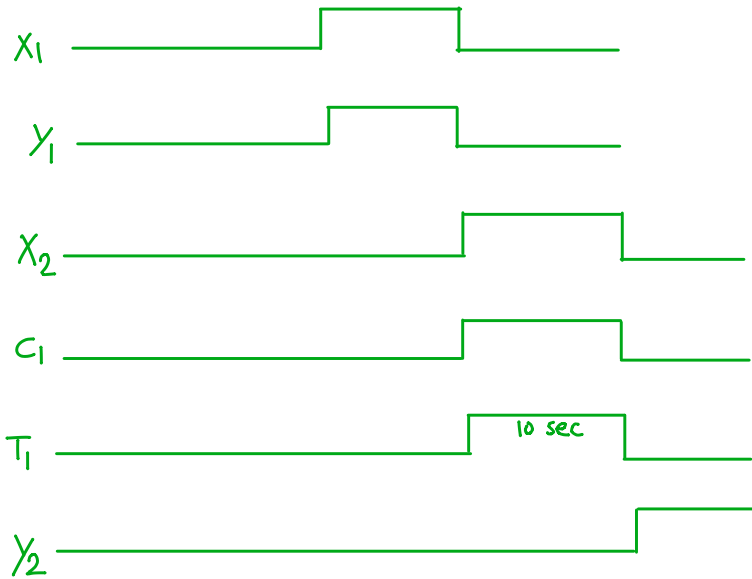

inputs $\rightarrow X_1, X_2$

Timers $\rightarrow T_1$

outputs $\rightarrow Y_1$ robot signal nest \rightarrow heating coil
 $\rightarrow C_1$ heating coil
 $\rightarrow Y_2$ robot signal

Inputs: X_0
 X_2 open limit switch
 X_1 close limit switch


Time: $T : 7 \text{ seconds}$

Outputs: Y_0 open the door
 Y_1 close the door

Automatic opening closing Door PLC Program

motor
motor
Sensor
time

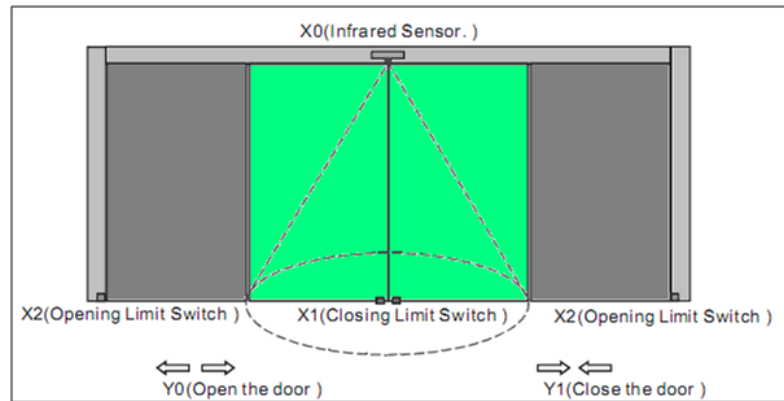يُنْتَظَرُ وَهُوَ فَاتِحٌ 7 seconds
إلا إذا حداجي



When someone enters the infrared sensing field, opening motor starts working to open the door automatically till the door touches the opening limit switch. If the door touches the opening limit switch for 7 sec and nobody

enters the sensing field, the closing motor starts working to close the door automatically till the closing limit switch touched together. Stop the closing action immediately if someone enters the sensing field during the door closing process.

Number of PLC Inputs Required

$X_0 - X_0 = \text{ON}$ when someone enters the sensing field.

X_1 – Closing limit switch. $X_1 = \text{ON}$ when 2 switches touched together.

X_2 – Opening limit switch. $X_2 = \text{ON}$ when the door touched the switches.

Number of PLC Outputs Required

Y_0 -Opening motor

Y_1 – Closing motor



Number of PLC Timers Required

$T_0 - 7 \text{ sec timer.}$

Inputs :
 X_0 open limit switch
 X_2 close limit switch
 X_1 close limit switch

Time : T : 7 seconds

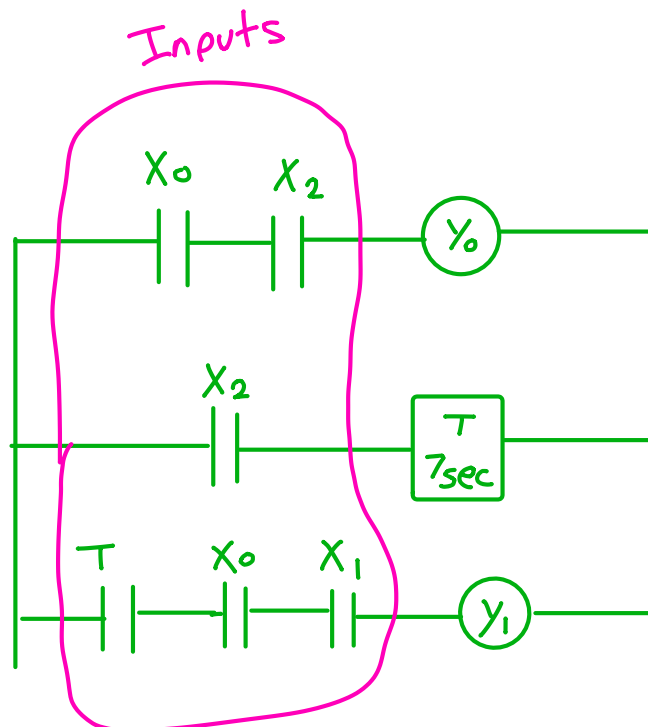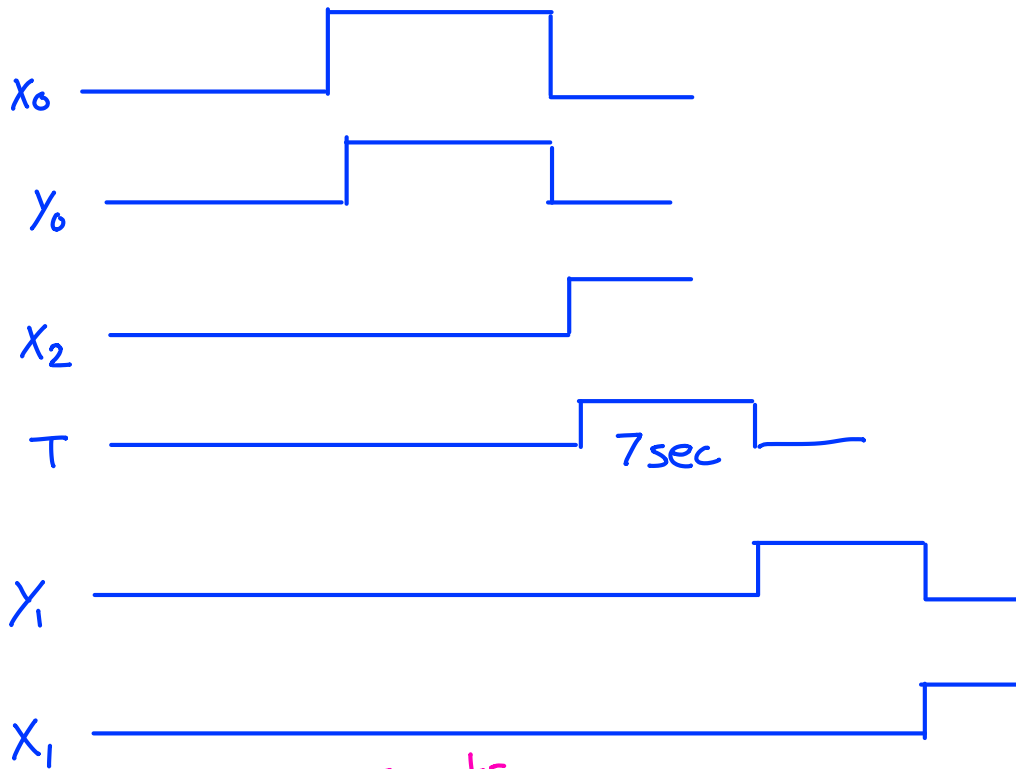outputs :
 Y_0 open the door
 Y_1 close the door



Consider the Automatic coffee maker as illustrated in Figure 1:


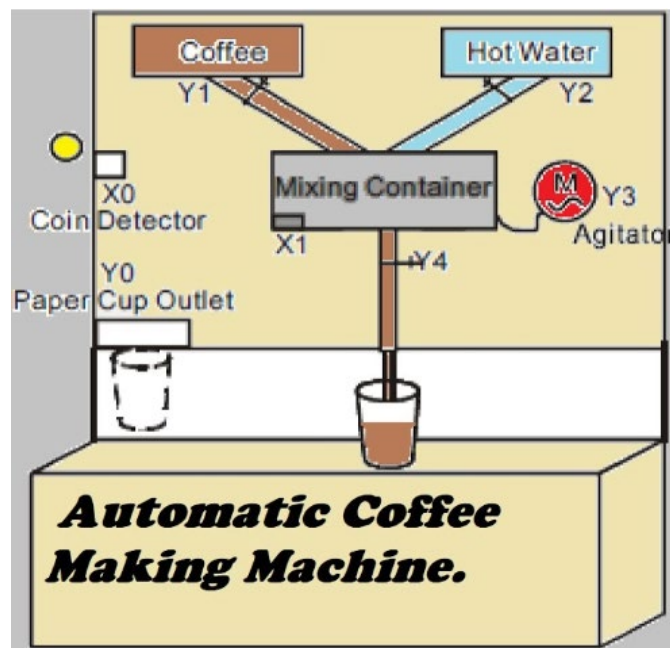


Fig.1 Automatic coffee maker

1. When a coin is inserted, ^{افزن X0} X1 is HIGH (ON) and the following outputs will be activated at the same time:
 - A timer T0 will be activated for 2 sec
 - Y0 (paper cup outlet) will be HIGH (ON) and latched (a paper cup will be sent out)
 - Y1 (coffee powder outlet) will be HIGH (ON) and latched (a certain amount of coffee will be poured into the container).
 - Y0 and Y1 will be HIGH (ON) for 2 sec, which is the set value of the timer T0.
2. After 2 sec, Y2 (hot water outlet) will be activated HIGH (ON), and the hot water will be poured in the container. At the same time, Y0 and Y1 will be closed LOW (OFF).
3. When the liquid in the container reaches a certain amount of pressure:
 - A pressure sensor X1 will be activated HIGH (ON).
 - Y2 will be reset LOW (OFF)
 - Timer T1 will be activated HIGH (ON) for 60 sec.
 - The agitator Y3 will be HIGH (ON) for 60 sec, which is the set value of Timer T1.
4. After 60 sec, the agitator Y3 will be Low (OFF) and Y4 (the ready – made coffee outlet) will be HIGH (ON) and latched and the ready –made coffee will be pouring out from the Y4 outlet.
5. When the coffee is poured into the paper cup completely, X1 will be LOW (OFF) and Y4 will be reset LOW (OFF) the ready-made coffee outlet will be closed.

Draw the PLC ladder diagram for the infusing container system above.

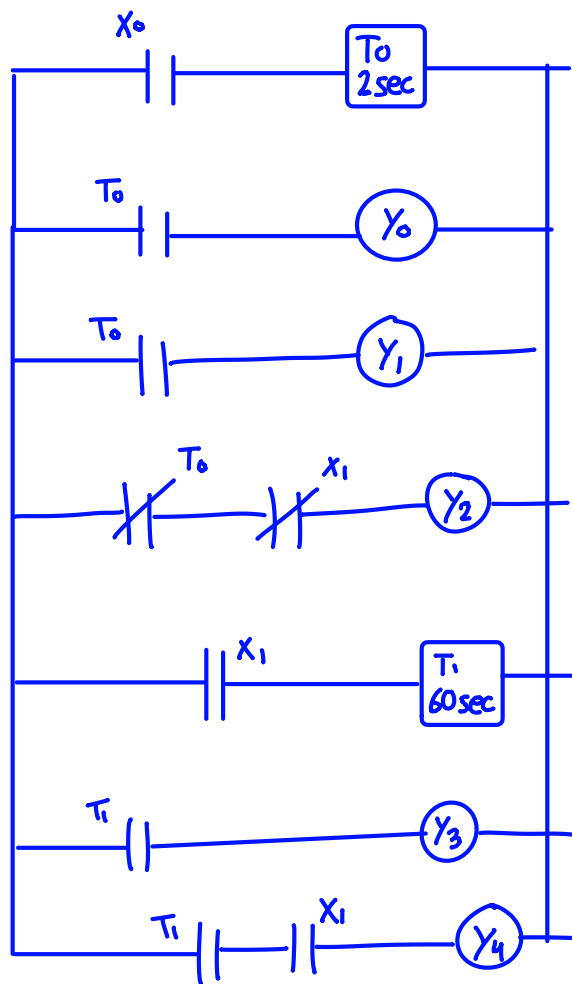

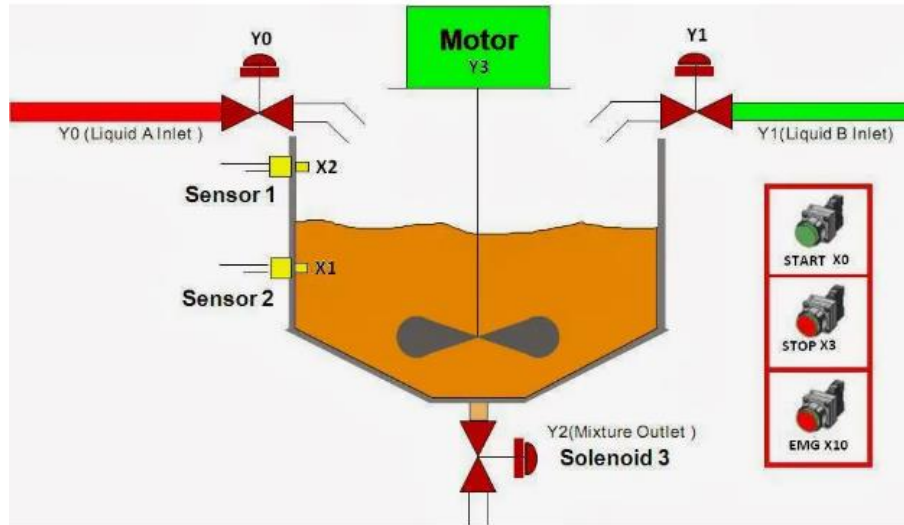


Fig.2

Consider the automatically infusing container with liquids A and B as illustrated in Figure 2:

1. When X0 (start button) will be ON when START is pressed. Y0 will be ON and latched, and the valve will be opened for infusing liquid A until the level reaches the low-level set point indicated by float sensor X1.
2. X1 will be ON when the level reaches the low-level float sensor. Y1 will be ON and latched, and the valve will be opened for infusing liquid B until the level reaches the high-level float sensor X2.
3. X2 will be ON when the level reaches the high-level float sensor. Y3 will be ON and activates the motor of the mixer. Also, timer T0 will be activated and start to count for 60 sec (mixing period).
4. After 60 sec, T0 will be OFF, and the mixer motor Y3 will stop working. Y2 will be ON, and the mixture will drain out of the container.
5. When Y2 = ON, timer T1 will be activated and start to count for 120 sec. After 120 sec, T1 will be Off and Y2 will be OFF. The draining process will be stopped.
6. When an error occurs, press EMERGENCY STOP button X10. The NC contact X10 will be ON to disable all the outputs. The system will then stop running.

Draw the PLC ladder diagram for the infusing container system above.

