

Electrical




First Semester 2024


INTRO TO ELECTRICAL ENG.


9

D


哪

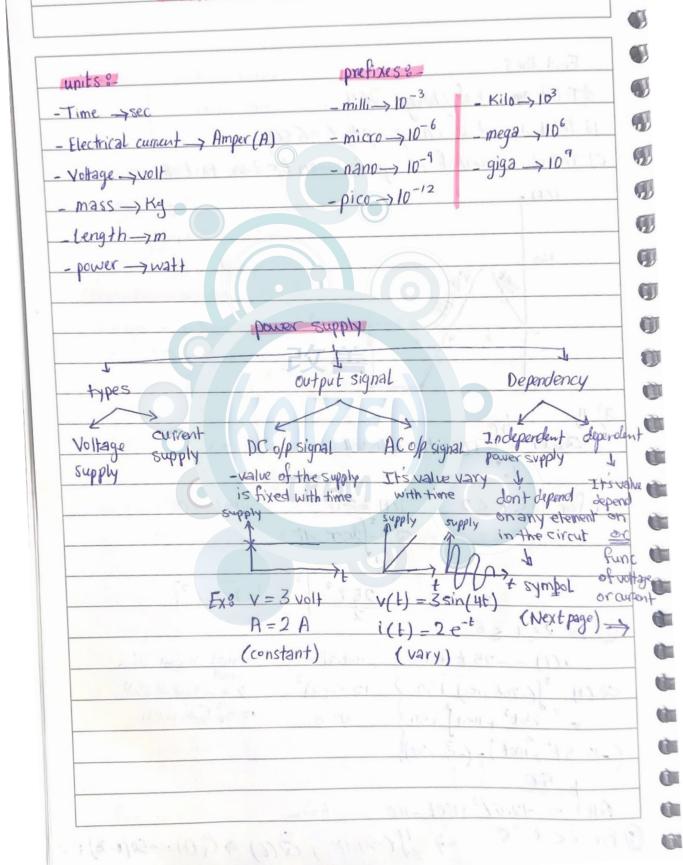


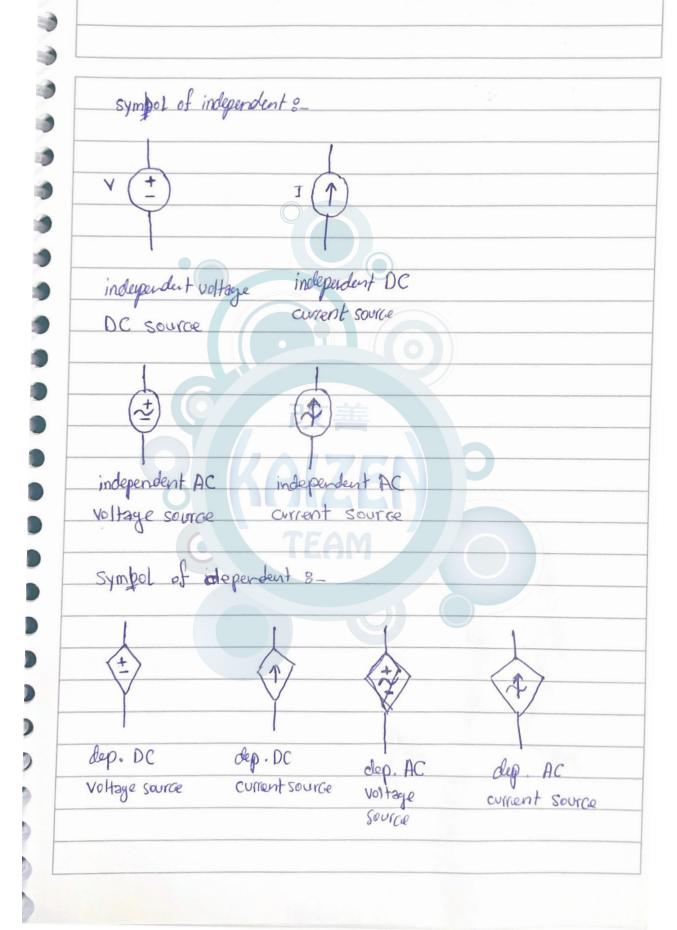

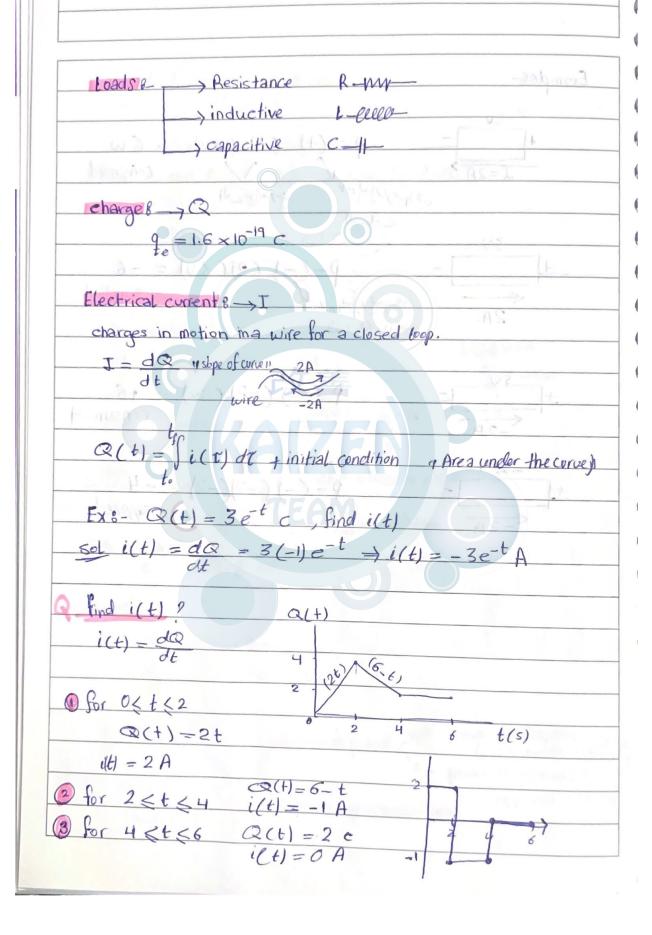

Find the 8a) Total amount of charge Q(t)
b) Total amount of charge up to t=6 sec 1 1 c) Total amount of charge between t = 2 sec to t=8 sec 1 i(+) 50 a) W 1 9 1 Ofor Osts2 i(t) =25t initial = 0 1 Q = 257 dr 2 12.5 t2 1 3 2 , initial = 2Q(t) = (-25t +100) +50 2-25t2 + 100t +50 -12.5 t2 + 100t) - (-30+200)} $Q(t) = -12.5t^{2} + 100t - 100 \qquad 6 \text{ in sin}$ $\text{3 for } 6 < t < 8 \Rightarrow t \leq (-50) de + Q(6) \Rightarrow Q(1) = -50(t-8) + 50$

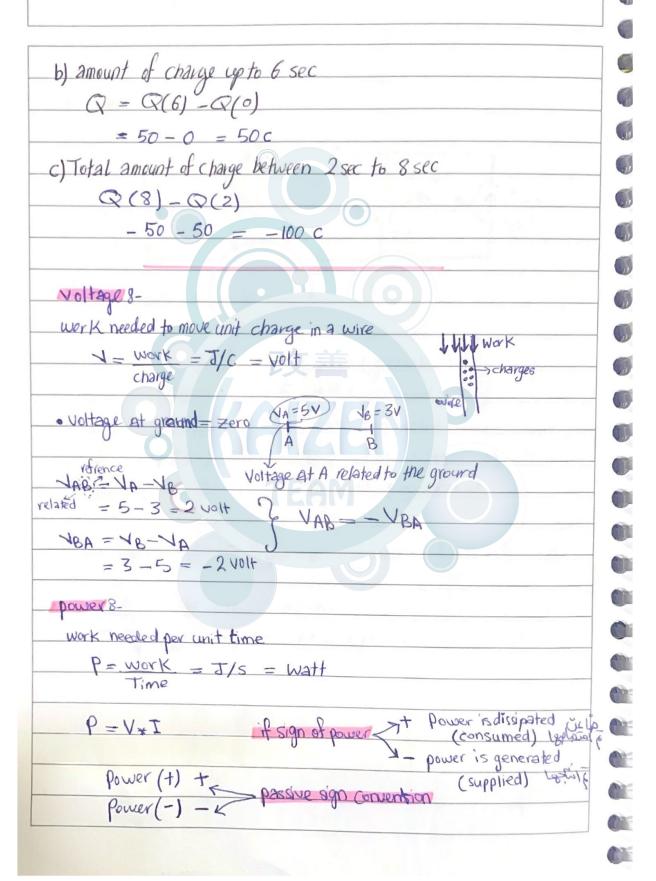

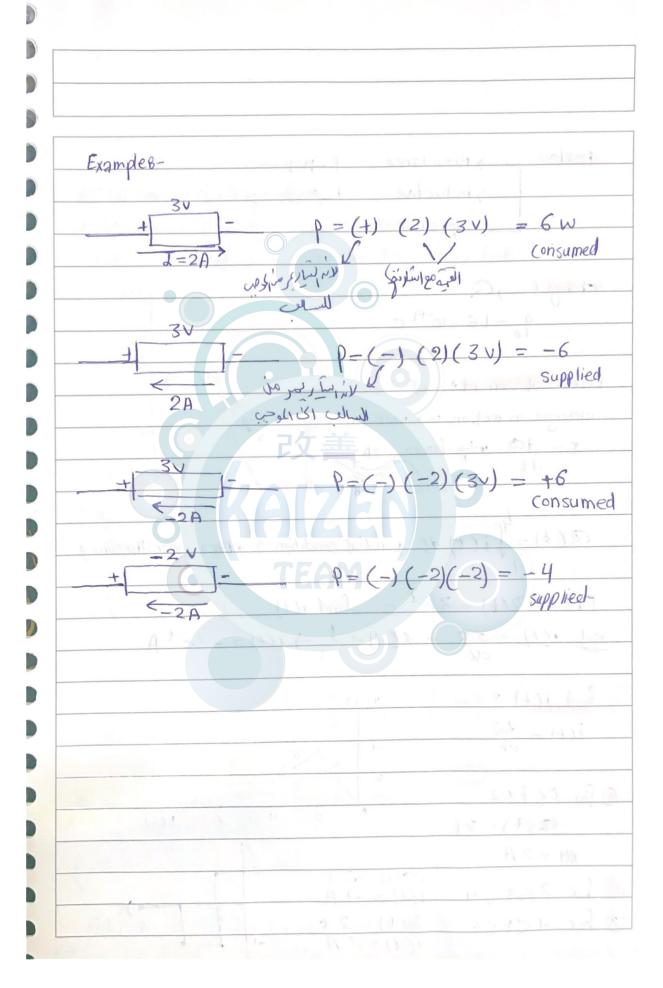

Example 8-5A - +12V+ 7 200 8A find power for each element $P_1 = (-1)(7)(8) = -56 \text{ watt (generated)}$ $P_2 = (+)(8)(2) = +16$ walt (consumed) P3 = (-) (5)(12) =-60 watt (generated) P4 = (+) (20) (8) = +160 watt (consumed) $P_{5} = (-)(2)(3) = -60 \text{ watt (generated)}$ EP consumed = & Pgenovated EPcons = 16 + 160 = 176 W E Pgenerald = 56 +60 +60 = 176 W

9

9

9

-

9

9

9

0

0

6


(1)


61


(1)

(6)


Chapter 28 Basic Laws

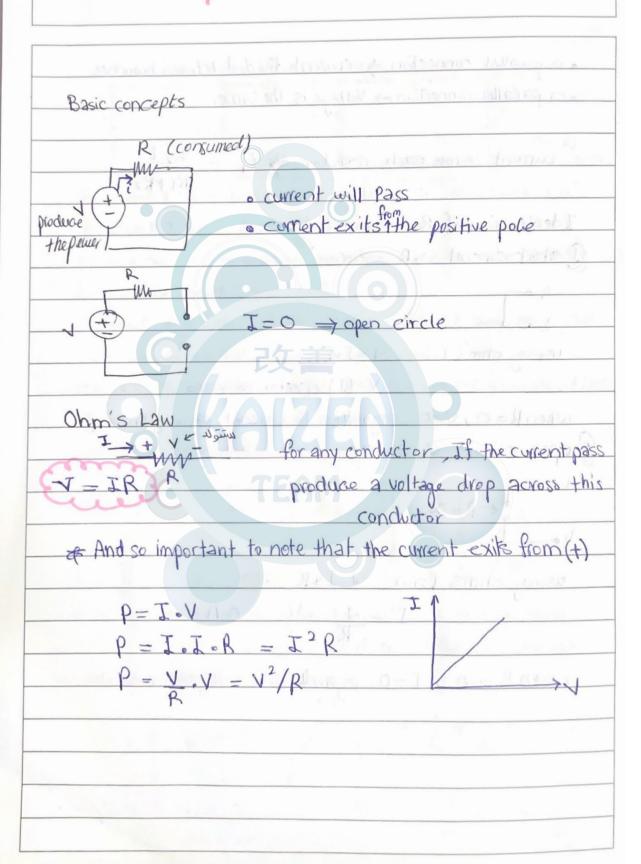


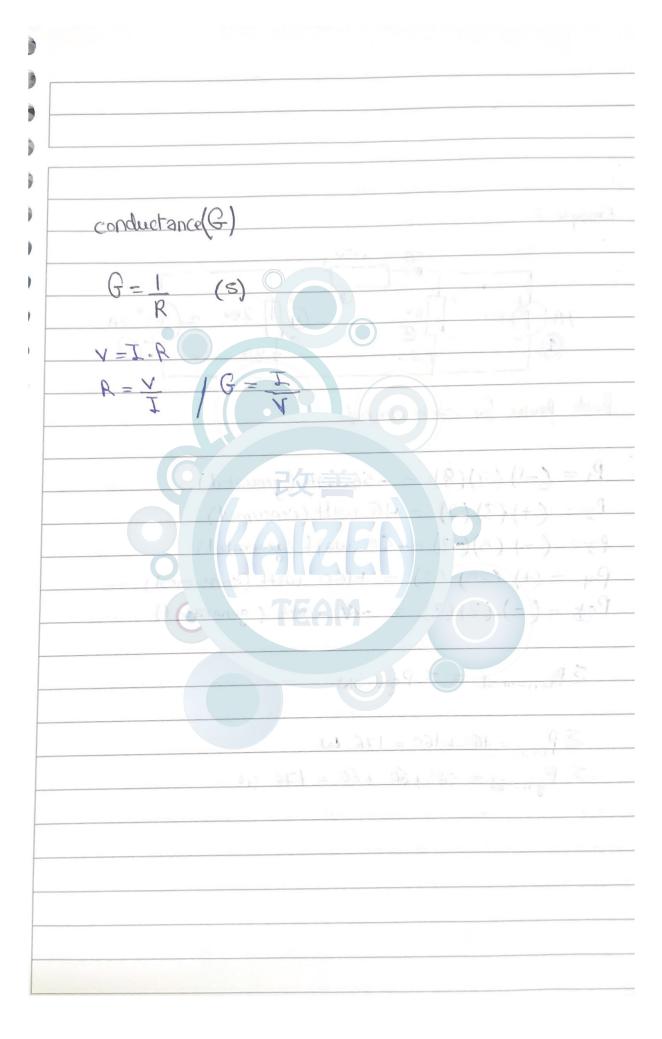


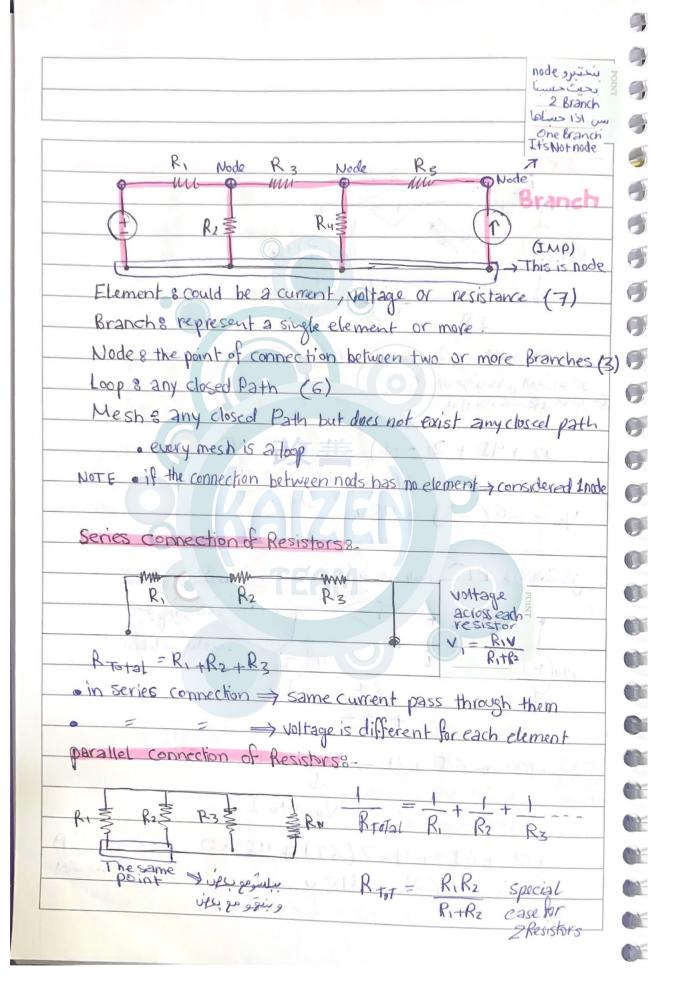



· in parallel connection > current divided between branches oin parallel connection -> Voltage is the same. Rzi current across each resistor > i, Ri+Rz Idealization of Resistance :-1) short circuit >R = Zero using ohm's Law Y=I*R V=(1) x(zero) = zero when R=0, V=0 regardless to current passing through. 2 open circuit > R-00 4 ER = 00 40 bo 40 using ohms Law 00000 when R = 0, I = 0 regardless to voltage across it

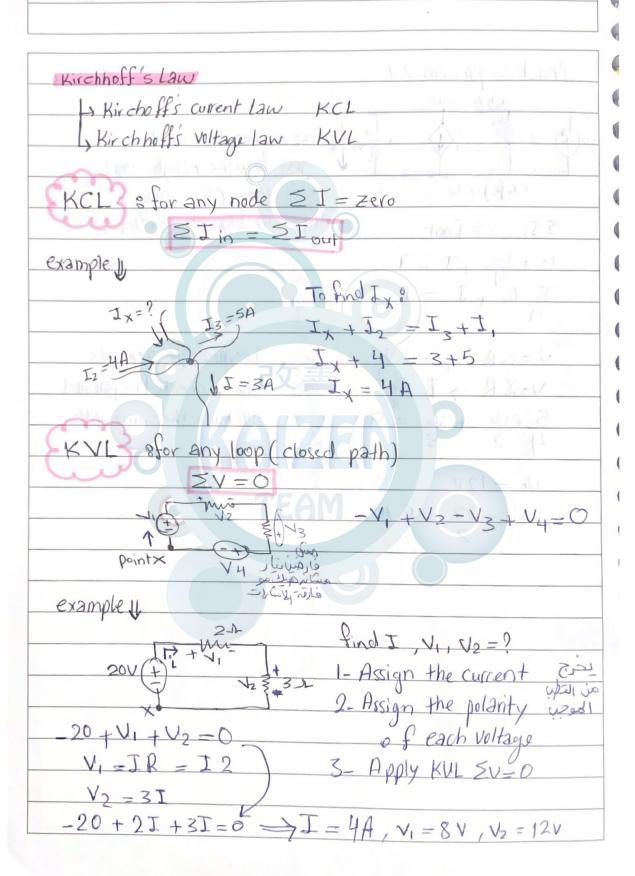

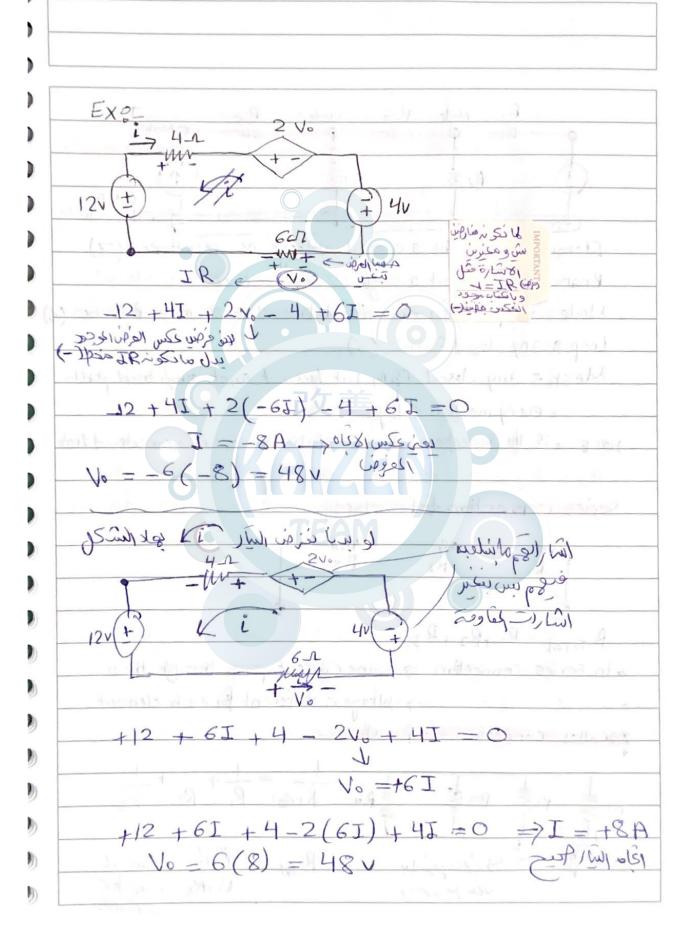

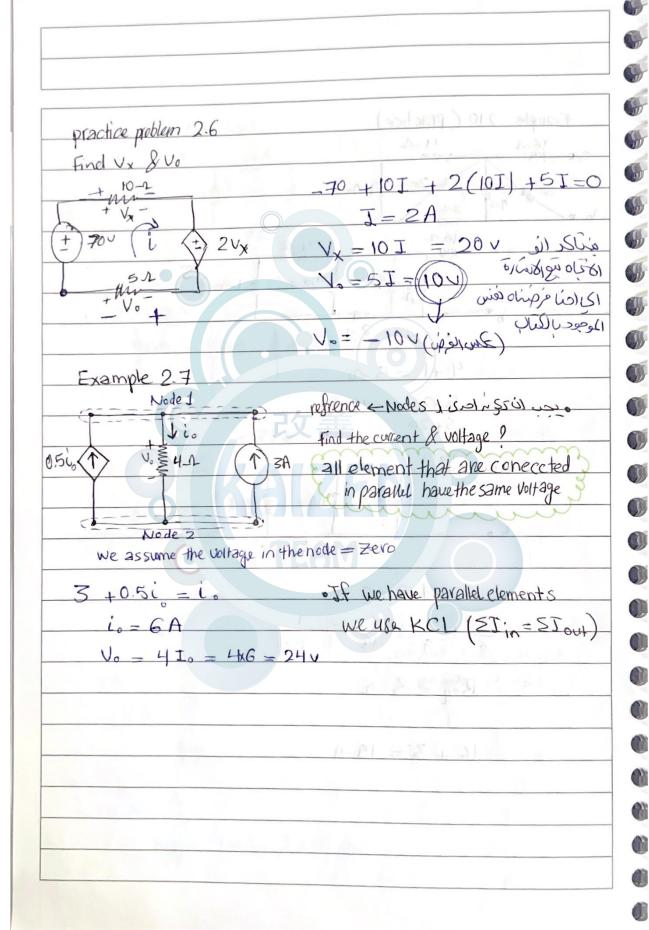

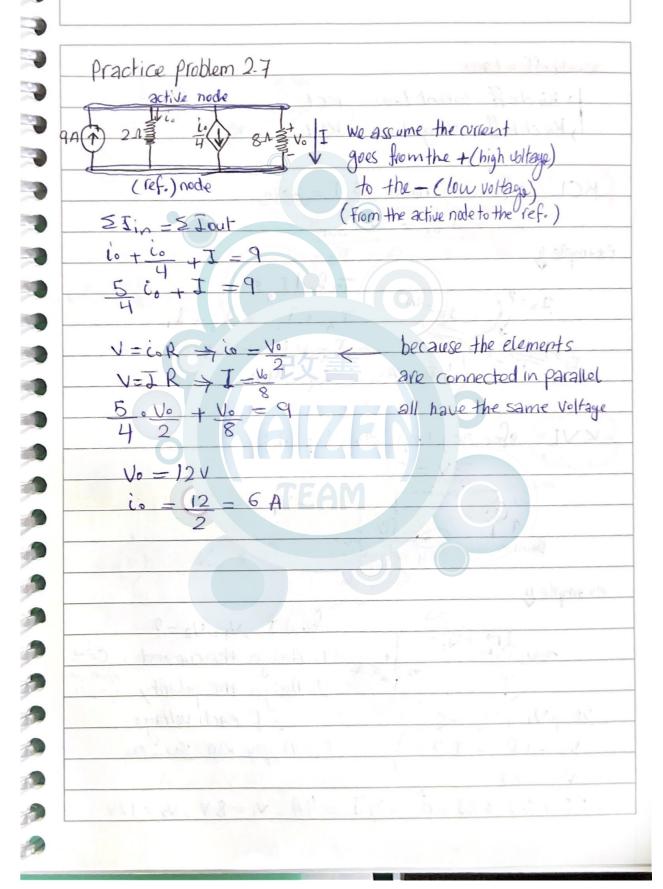


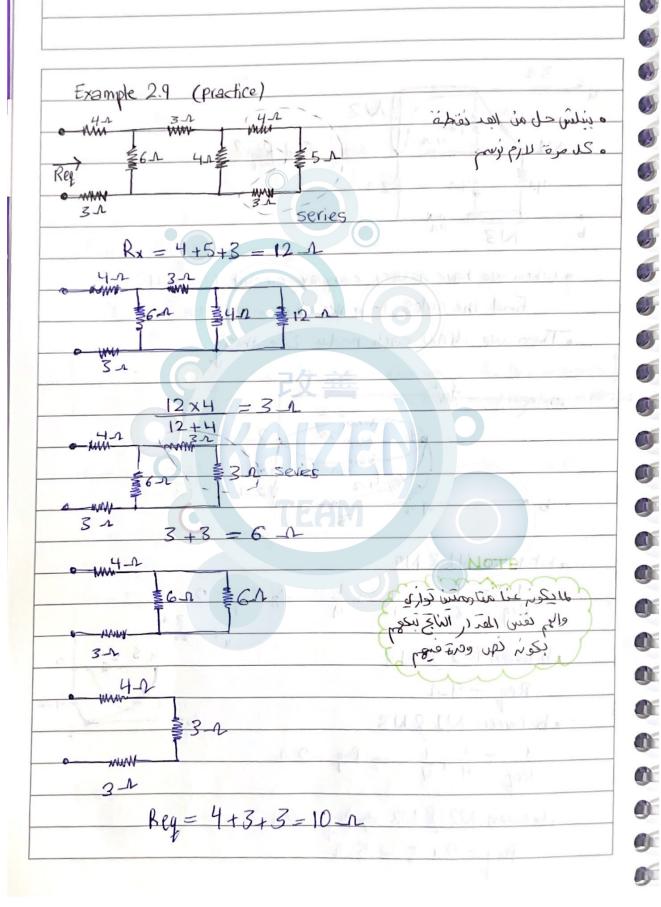



3)) Example 2.10 (practice)) Man_ 16-2 9 Mu 20-1 7 22 162 7 5 3 1 7 w 22 7 4+1=52 7 =41 5 x20 5+20 162 \$18-2 391 1 5 21 4+2=61 16+3=19-1


)


Examples 8-	
2-2	1
= 42	81 Find I,?
I	
(30)	
· Sinding Reg	O de Carlos Sen 4 1 chape
· Marie Key	27 1
Reg 4 8	g = 2. + . K
2-1	A CONTRACTOR OF THE PARTY OF TH
W///4	La Marine Date Control
V+1 2.71 (Ve	that are linked together in parall
T 77 FX	that are linked together in parall
using voltage divider	A Control of the Cont
	to the way they do was
V = 10(2.7) = 5.74 Volt 2 + 2.7	S The state of the
+ C. I. G. A. TEA	Many and the same of the same
to finding I, (using ohms	s Law)
V = I, R	1 15 Alac Jall year mi
$5.74 = I_1(8) \Rightarrow I_1 = 0$.71 A
the second discount	0101
At The Date of the world	
dissessables and	
All Mills	Talkel Vis- elik ball at
with the	
at the state of	10 (2) of 1 (4) 1 1 1 1 1 1 1 1

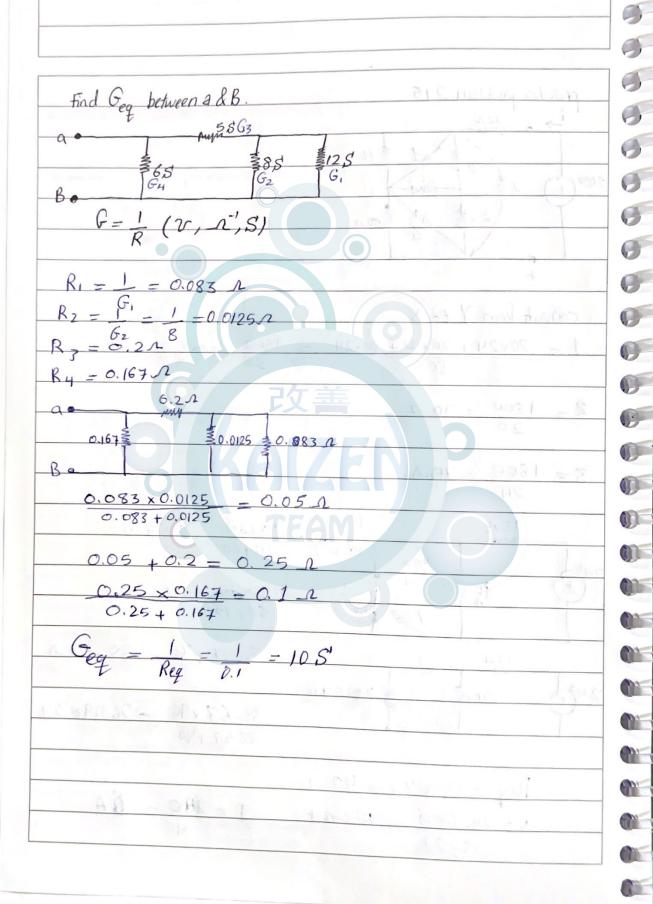


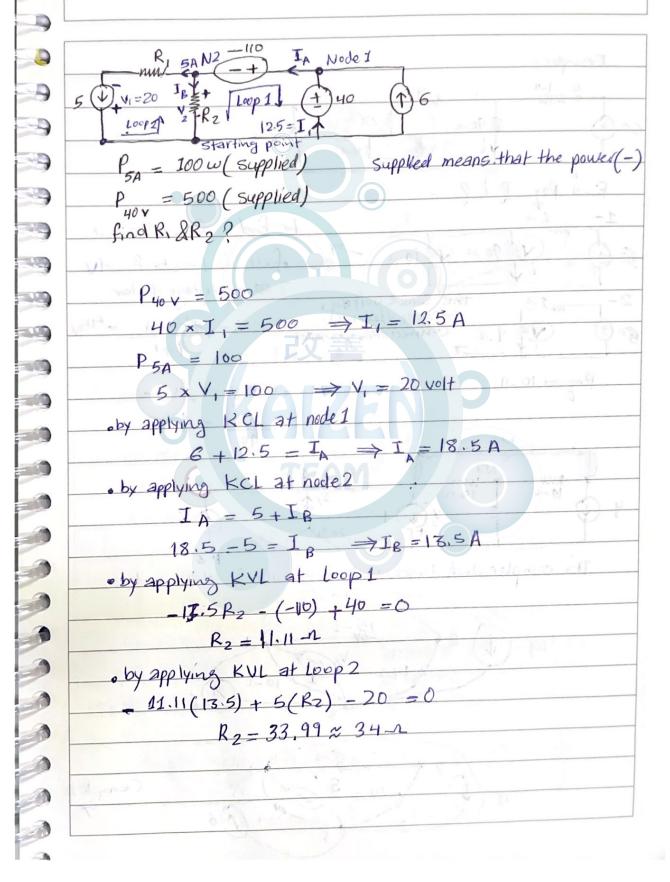

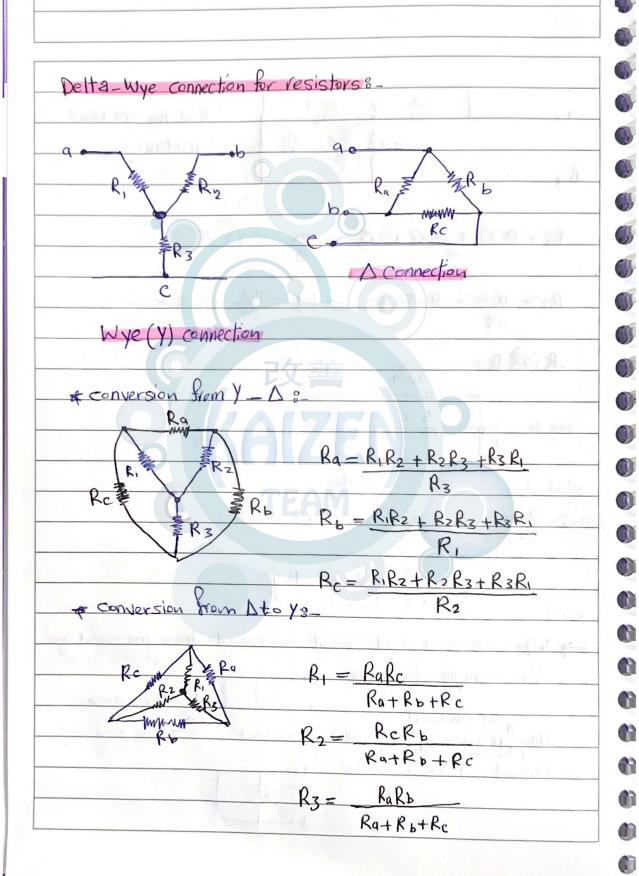


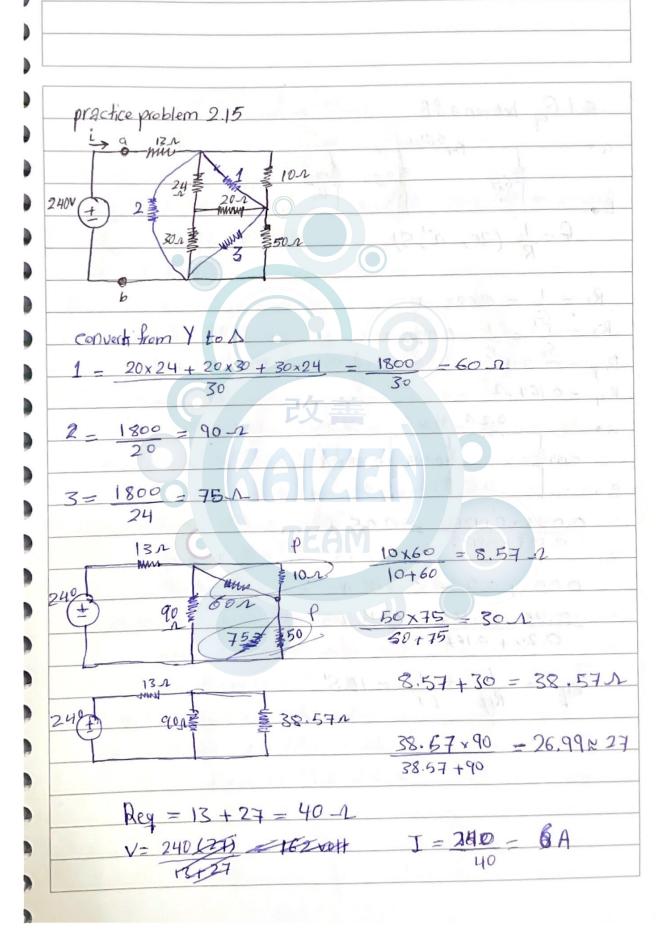

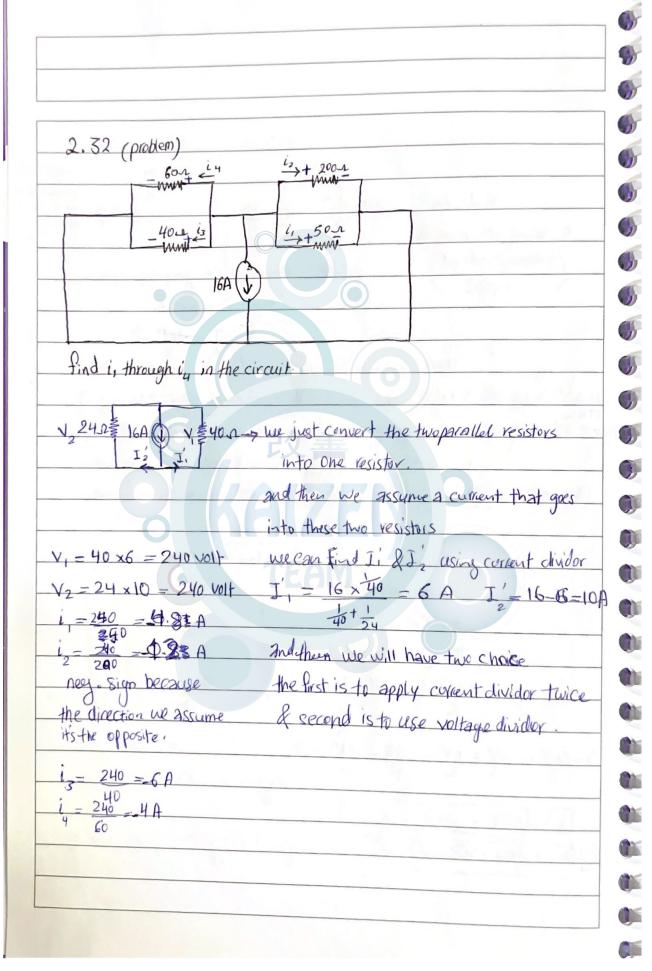


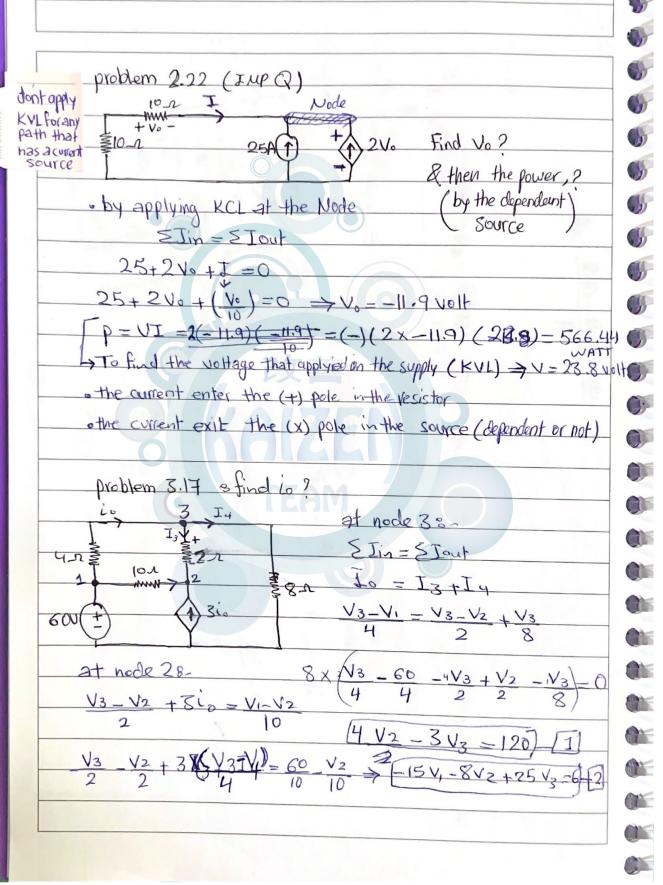



Chapter 3 & METHOOS OF ANALYSIS

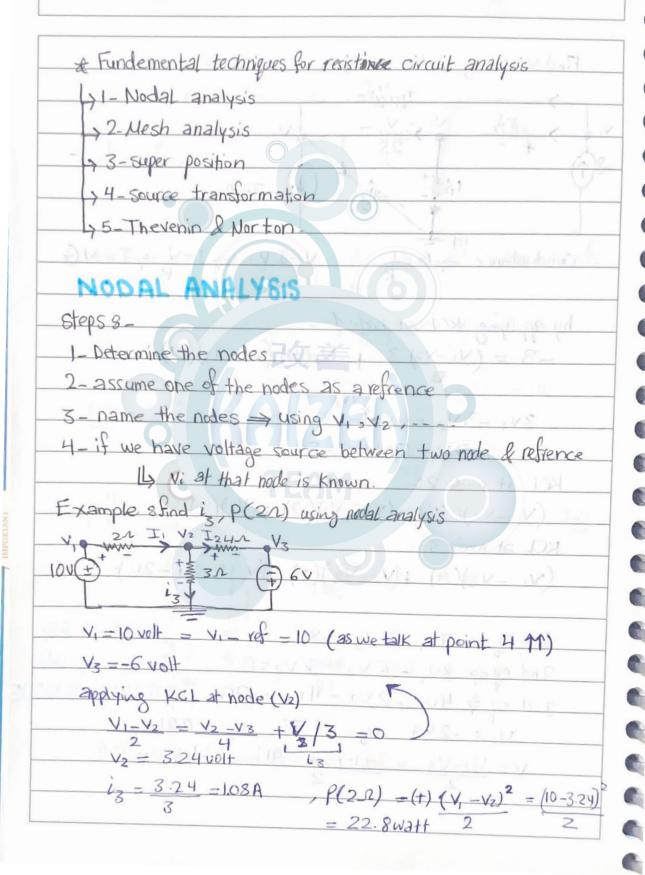



C

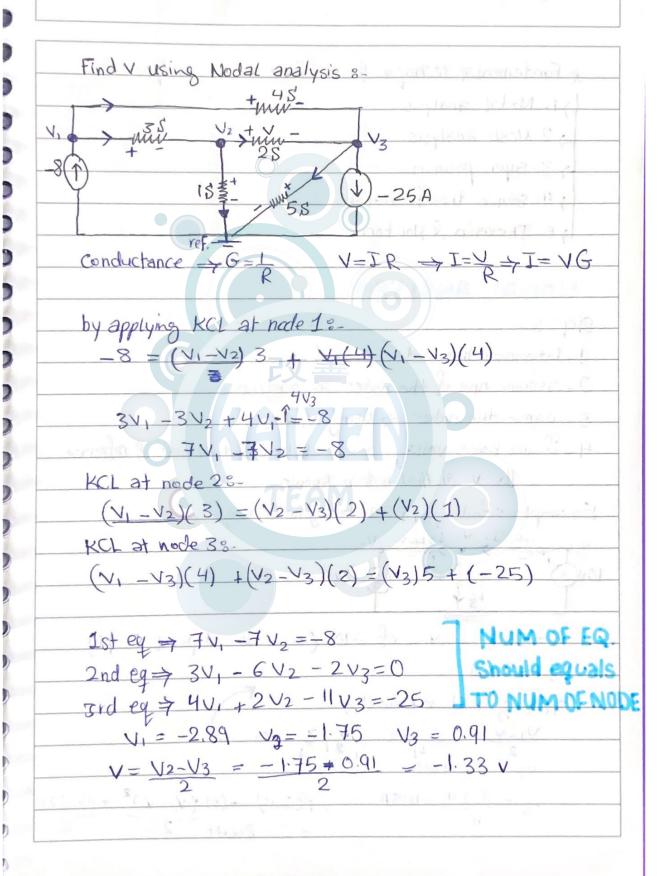


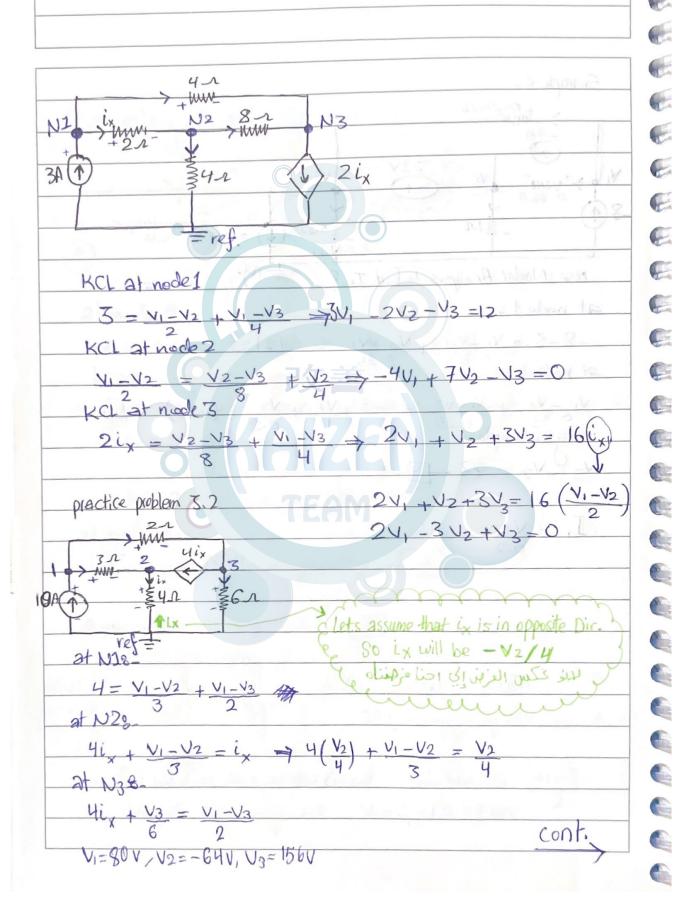

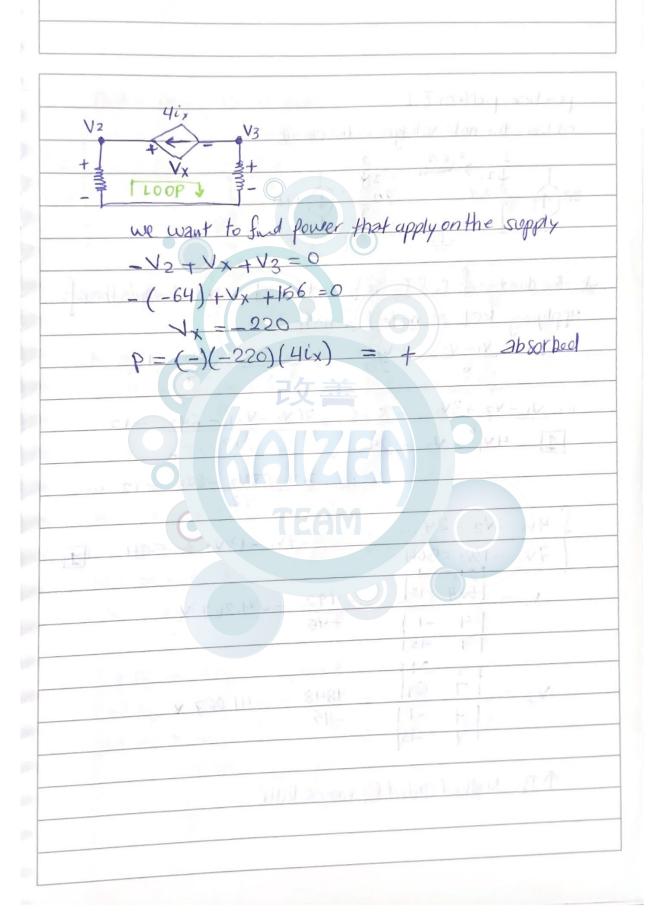

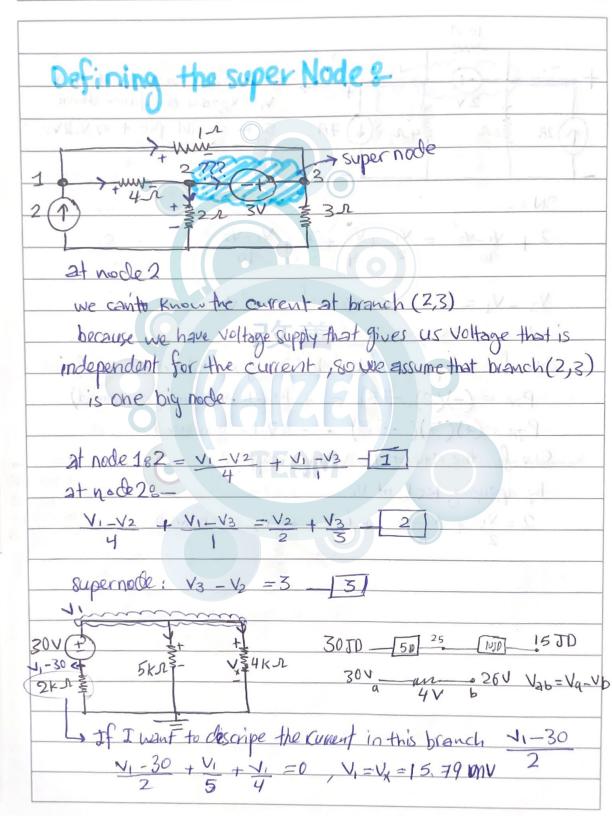

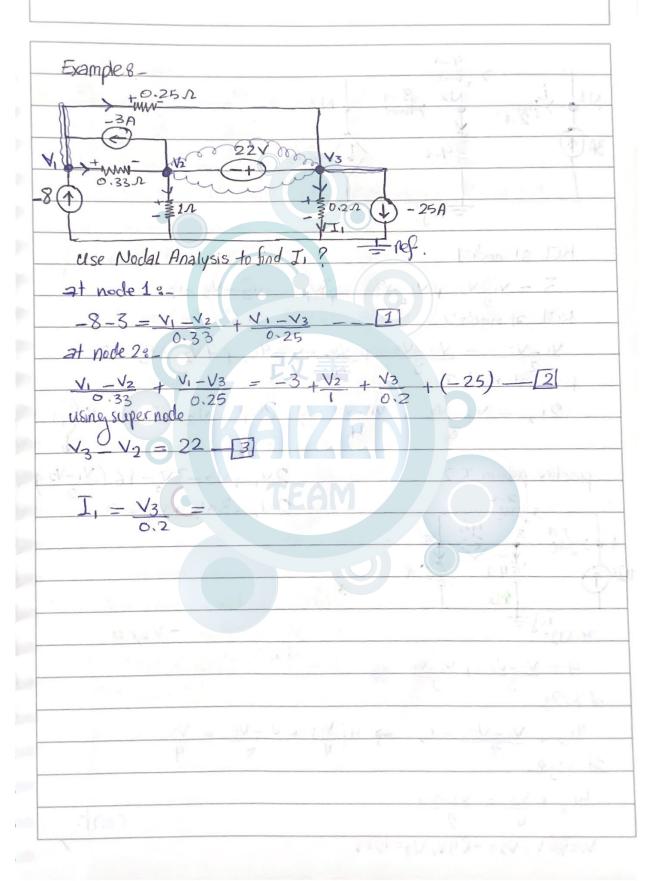

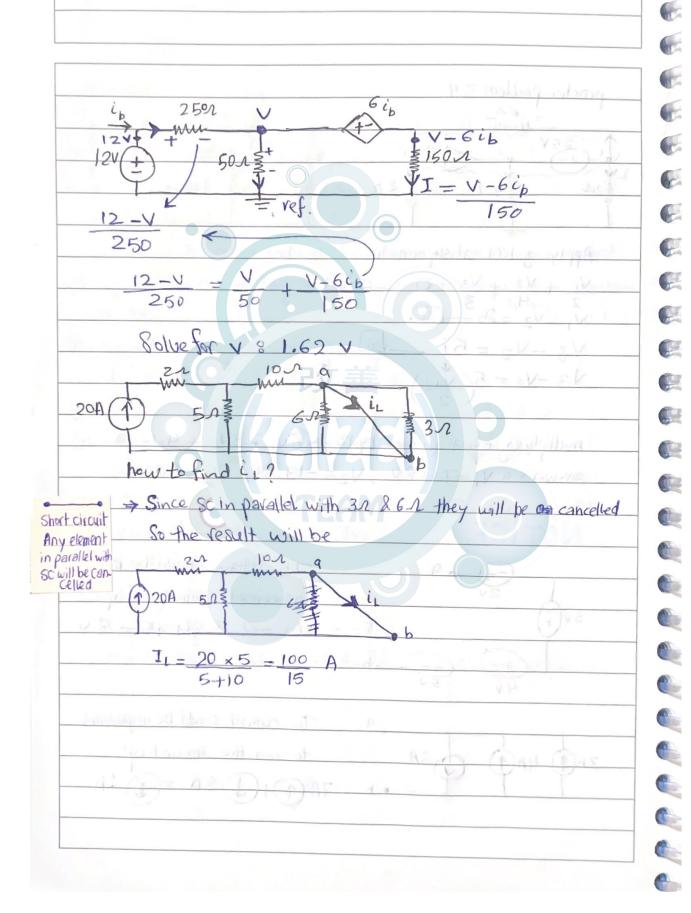

MESH ANALYSIS 1- assign # of Mesh 2 - assign a current for each mesh 3 - Apply KVL for eath mesh (5V= 7ero) 4 - solve to find i, iz, I the common resister we will keep it as it is without any polarity MESH 18. $-5 + 4I_1 + 6(I_1 - I_2) = 0$ 10I1 -6I2 = 5 -4ESH 28-10 I2 + 20 +6[2-]1) =0 -6I, +16I2 = -20 -[2] I, = -0.32 A, I2=-1.37 A If we want to find Vx? [II] =6.0 $(I_1-I_2)(6) = (-0.32 + 1.37)(6) = 6.3 V$

1

(F

Q.F

OF.

OF

0

0


0


6

6


6


6

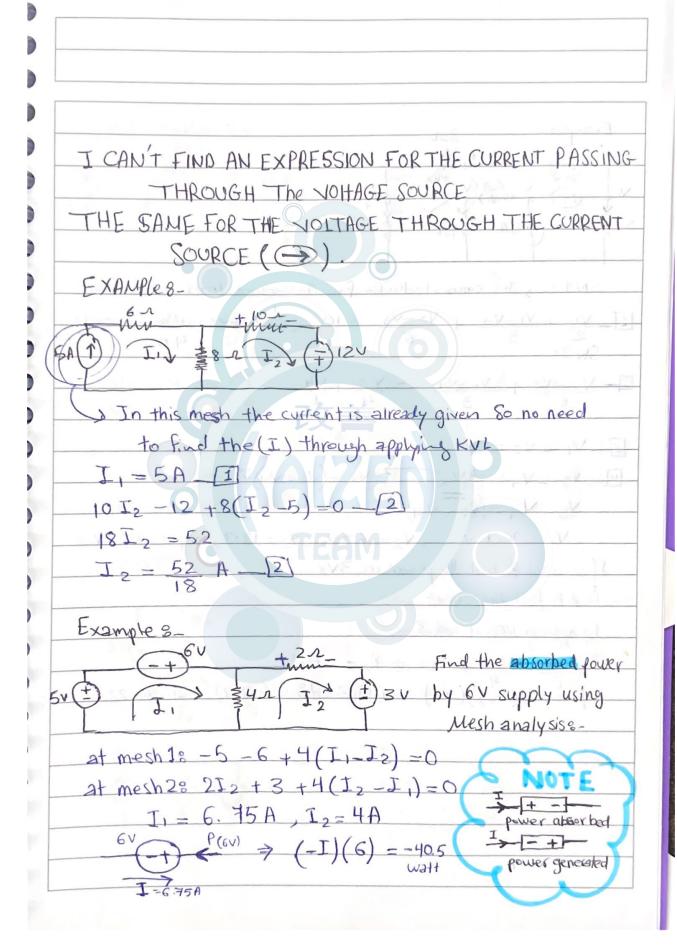


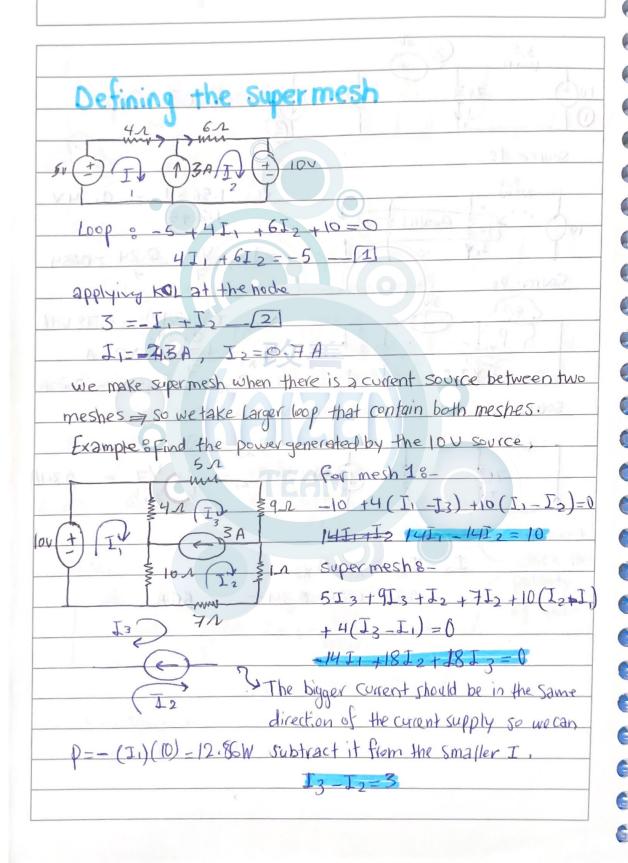



Chapter 4: Circuit THeorem

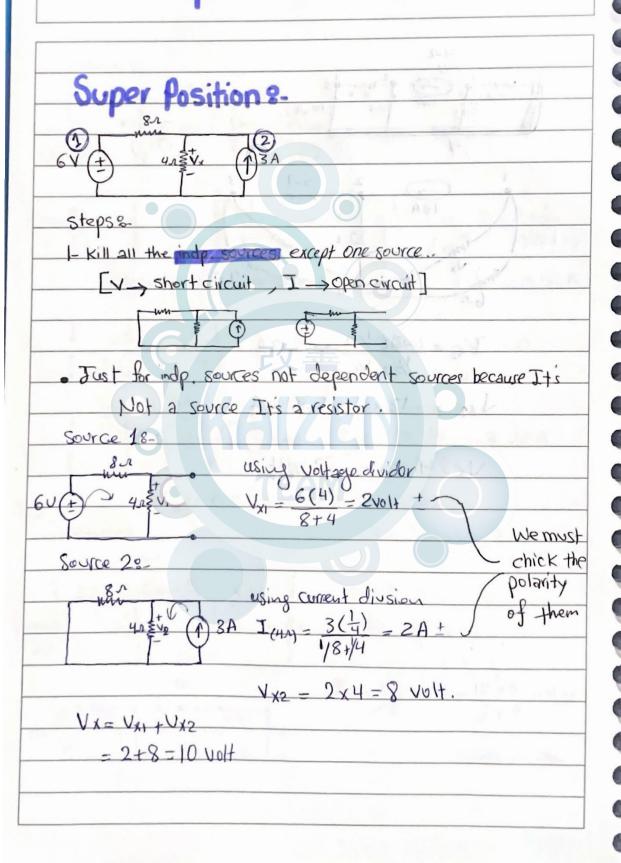


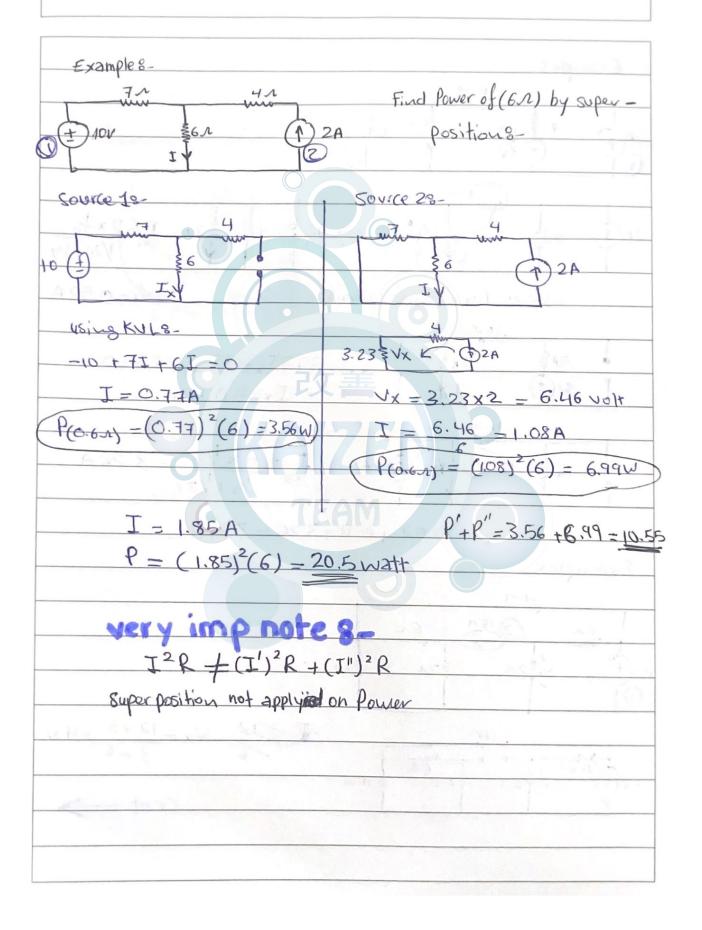


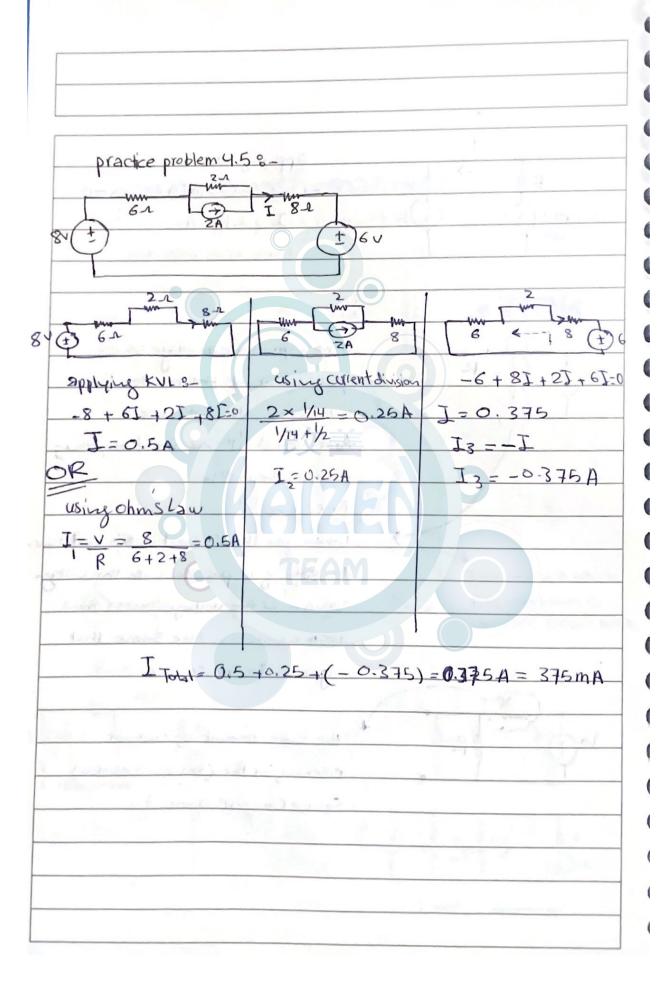


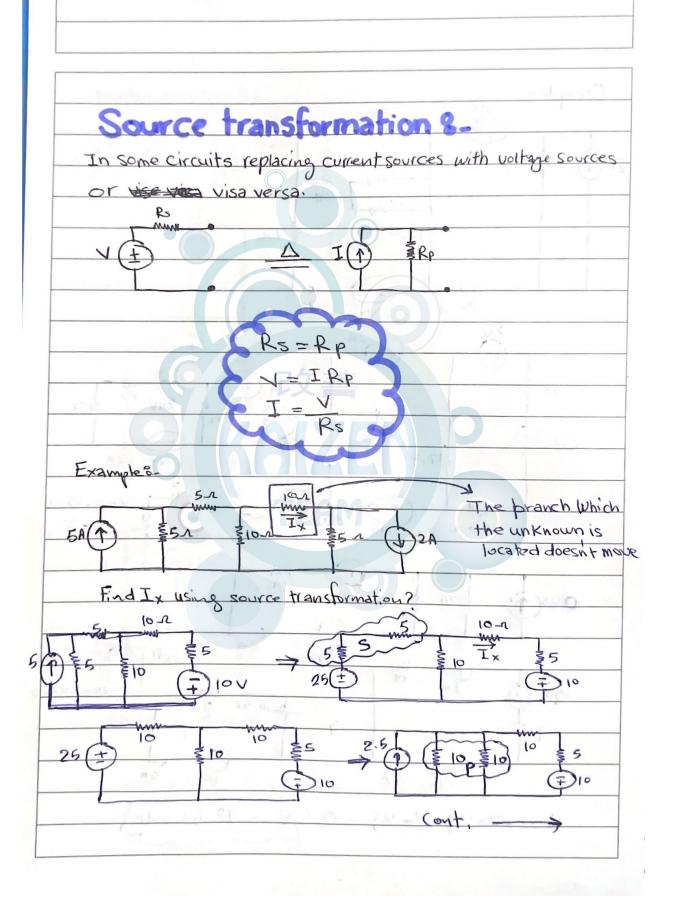


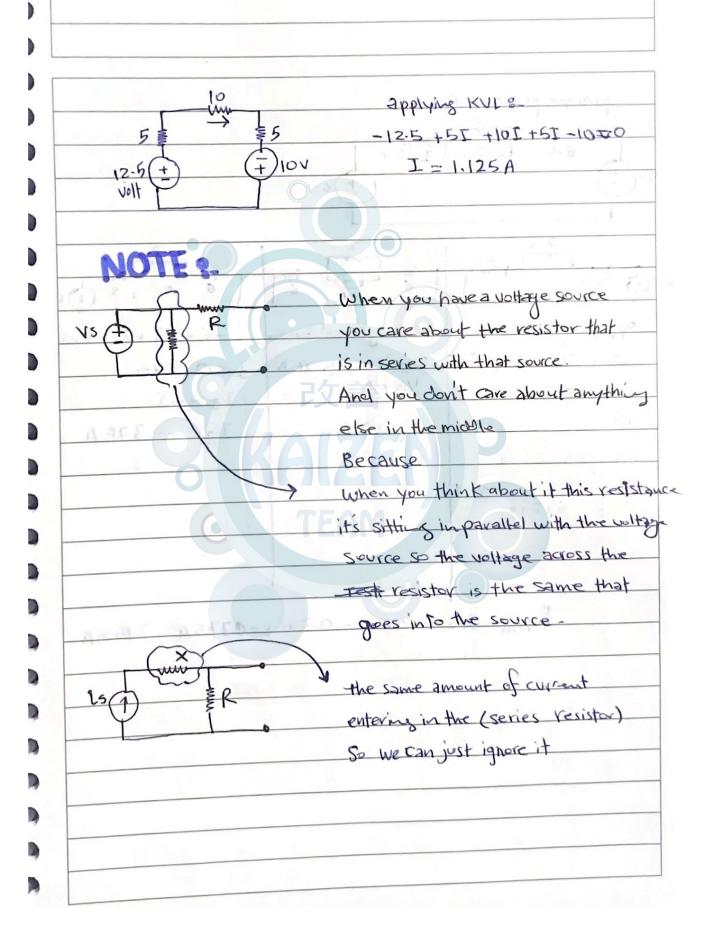


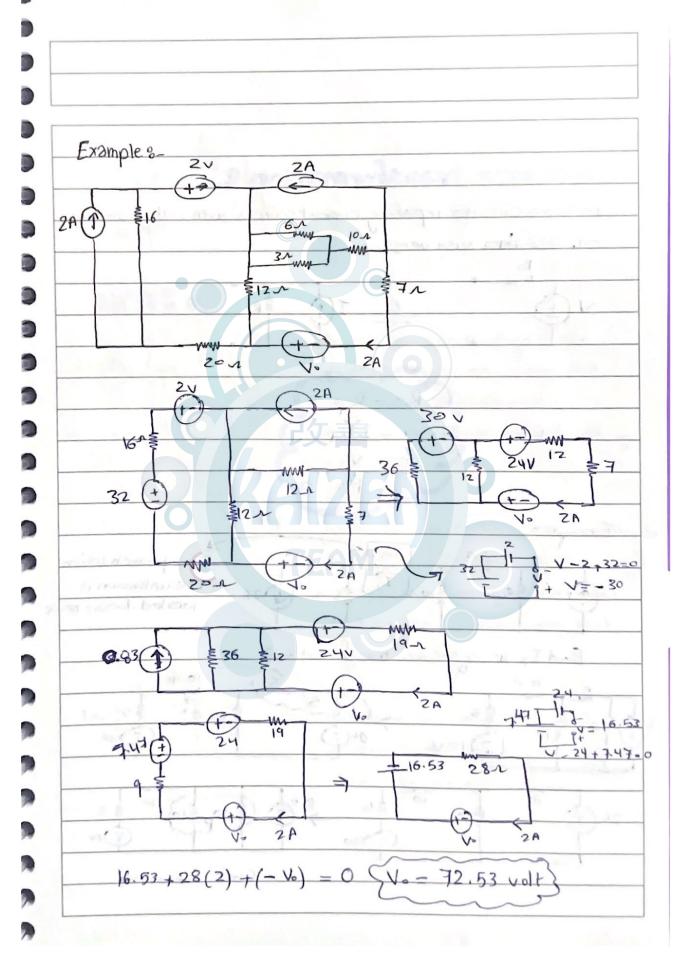

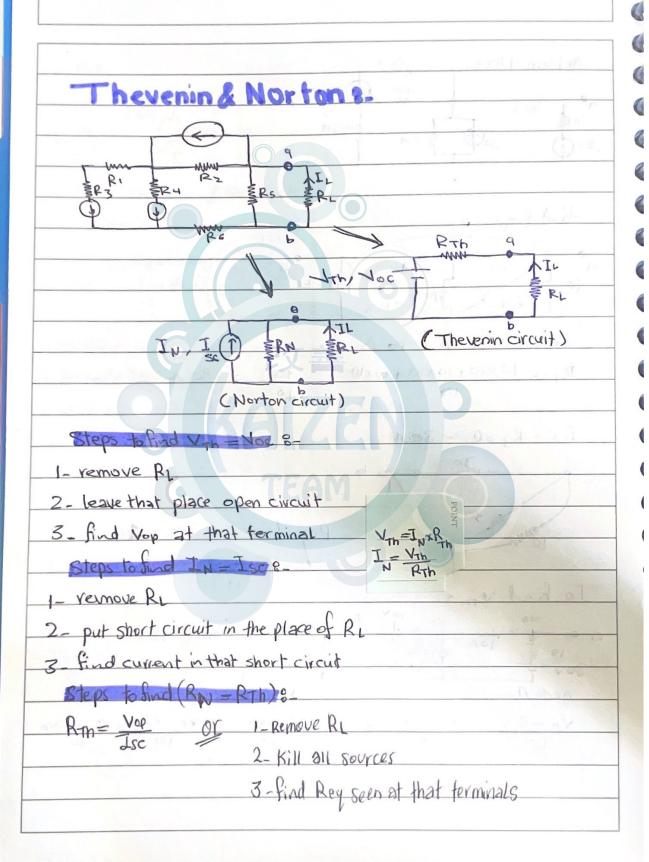

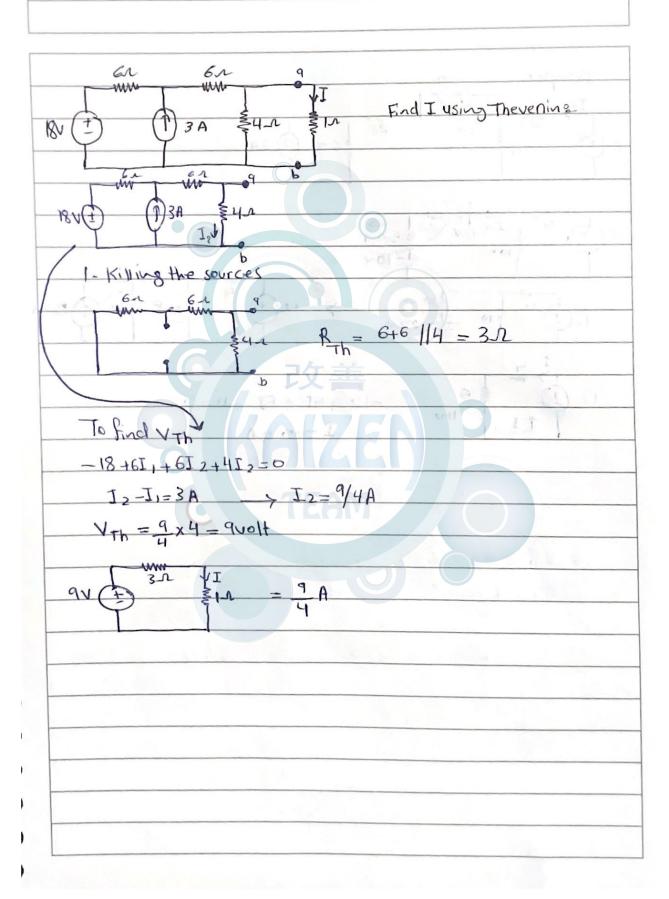


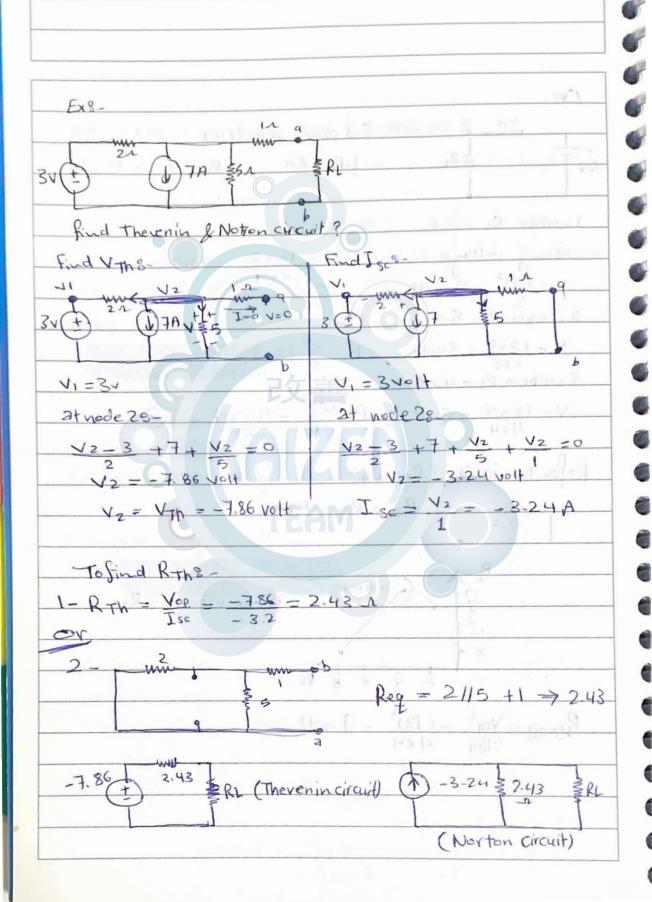


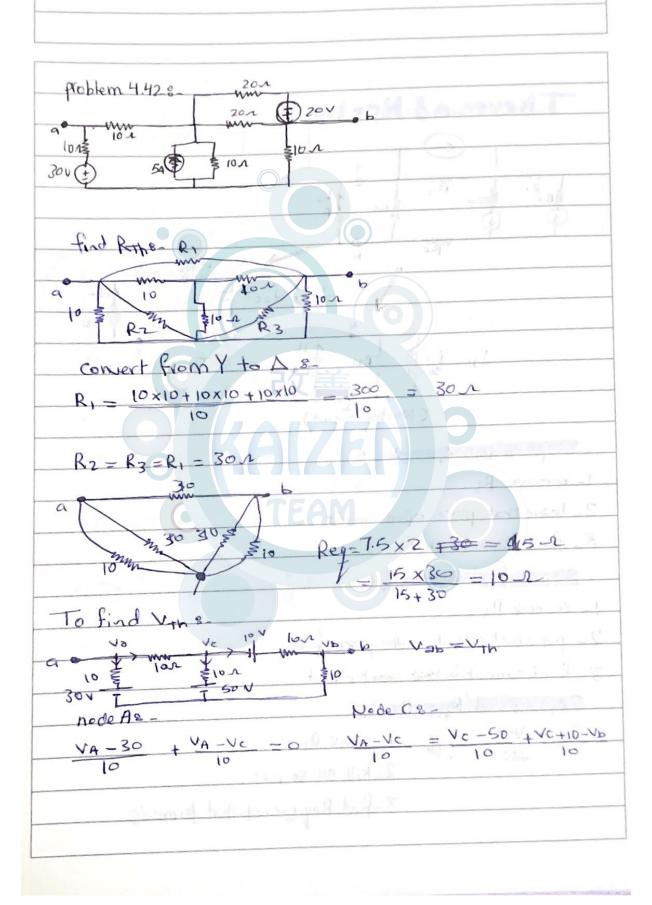

Maximum Power We concern about power consu of the Rircuit either who I RTH VINT I-what is the value of Ri to get (umption by Load after simplicates
of the Eircuit either who Party I whatis the value of Ri to get (umption by Load after simplicates
of the Rircuit either um L RTN VTh T L-whatis the value of Ri to get (FRL IN FRN FRL
1- what is the value of Ri to get (FRL IN FRL
1- what is the value of Ri to get (FRL I RN FRL
1- what is the value of Ri to get (Ole May On on or Com the source
	Aprorped) max power from the source
- Land = 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	
2- Pland = I2 R1 [] , I = 14th 3- by putting eq 2 into 1 Rth	+Ri mv giritad 1
PLOAD = (VTh) PL 3	no sty works of syen I took
4- for max power load -> s	JAN 20 With spotier perizu
4- for max power load > s	of payment words
Result RE- RTD @	
So for any circuit to get the n	naximum power at the load
TEAL TEAL	
5- by putting cq 4 in 3	2-Enfort
$P_L(max) = \frac{v_{Th}^2}{4R_{Th}} = \frac{In^2 R_L}{4R_{Th}}$	A Arm
98th 4	A out
	y Y
(the raise serve which att)	Anys - 545 T
The same of the sa	61
	2
	Alow I can calculate Rty
1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	178 I=17V
0.880	5H= - ATV - MTSI
^	The we want the power
W 5211 + 5(81	1-) = (atV) = q

T.

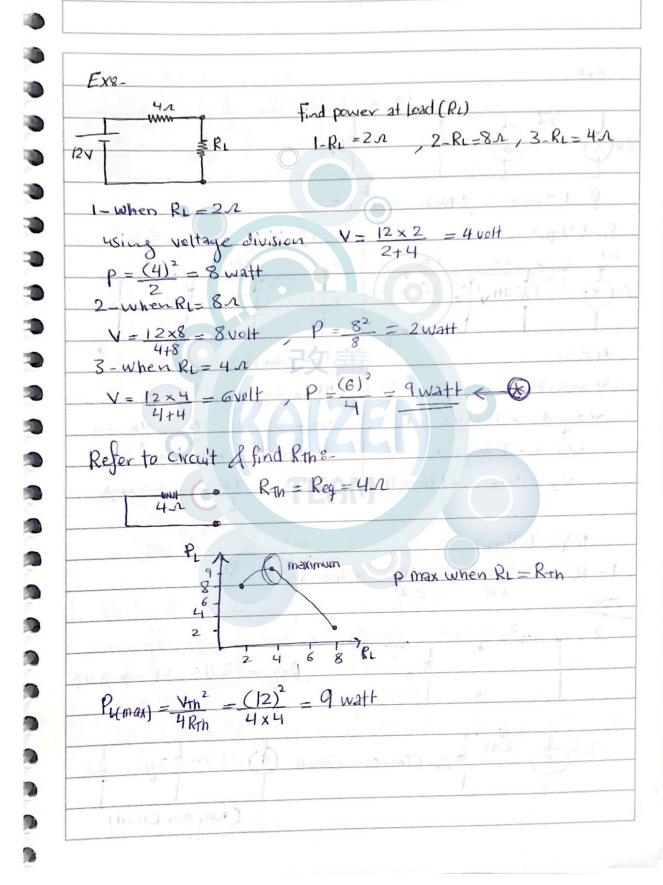

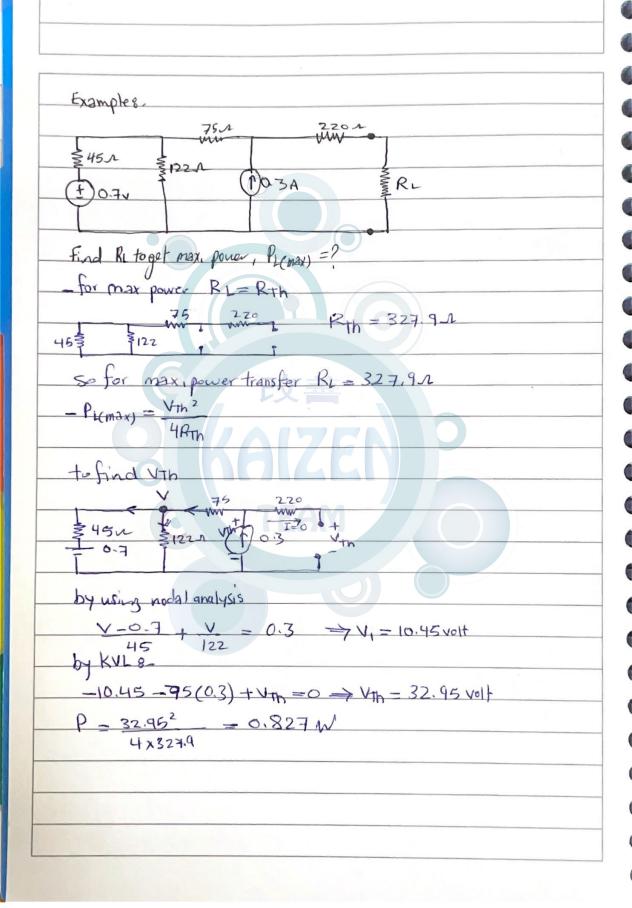



Chapter 6: Capacitor & Inductors


Explored to the control of the contr
We will talk about energy storage elements
I- Capacitor
1- device (element) that store energy
2 - consists of two parallel plates, each plate has a cross sectional (A
have distance (d) between them.
& it Riled with dielectric material.
has certain permitivity (E)
LEC-EARRISH CONSPILL SVILLE AL
3-unit of capacitance >(F)
4 - charge on plates of capacitor Q = CV (fixed voltage)
g(t) = CV(t) (Variable voltage)
$5-i=dQ \Rightarrow i_c(t)=c \frac{dv_c(t)}{dt}$
$G - V_c = \frac{1}{C} \int_{c} \dot{t}_c(T) dT + V_c(t_0)$
if Ve(t)=DC vatue = fixed
$\Rightarrow L_c(t) = zero$
means that capacitor act like open
circuit in DC-Circuit
The same of the sa
- 1 - 2 1 - 1 - 2
7- energy stored in the capacitor = 1 CV2 = 10V=10


the calc should beRAD Capacitor in parallel capacitor in series Ex3-Ve(t) = 5 sin(t) Vc(t) 1- energy stored = 25 sin (t) Joyl CV = 2x 5sin(t) = losin(t) colonub $dv_{6}(t)$ = 2 x (+5 Eos(t)) = 10 cos(+) A Note that capacitors are used to block DC, pass AC Shift phase, store energy, start motors & suppersonoise du-finite The capacitor doesn't allow the sudden change in voltage i = c dv = c Ginited dt =0 in so not possible


AT

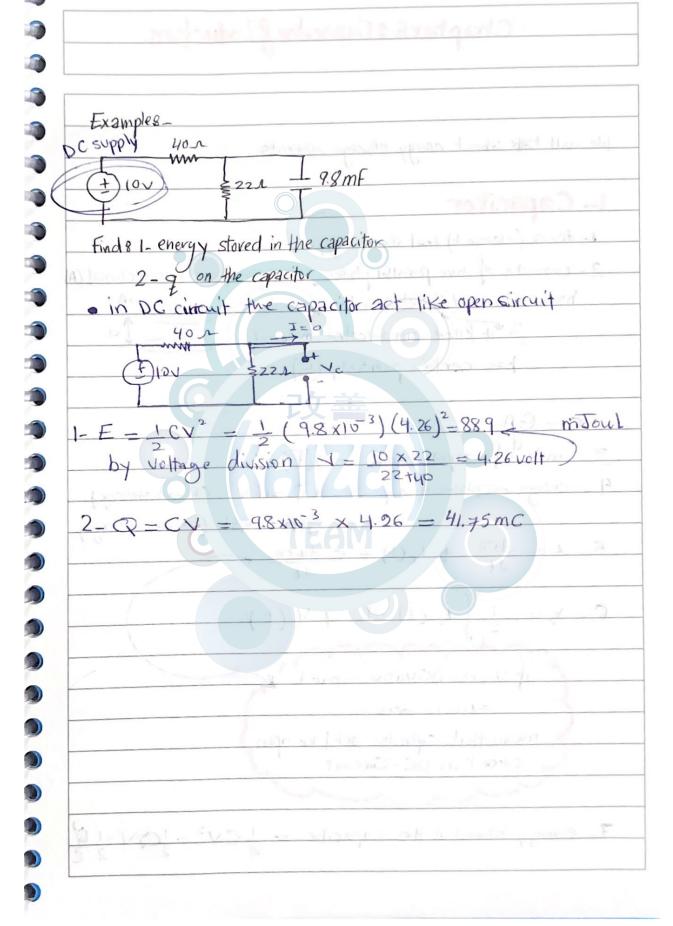


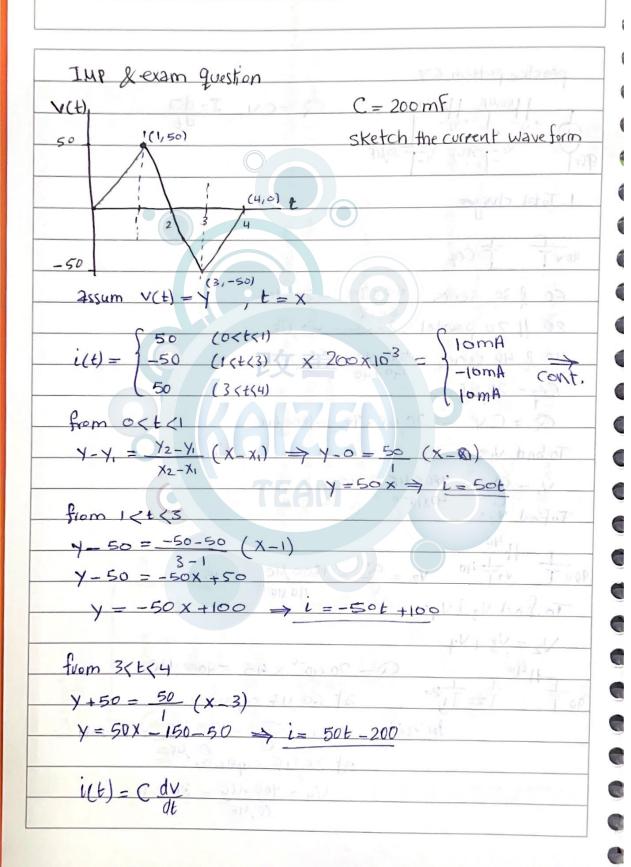


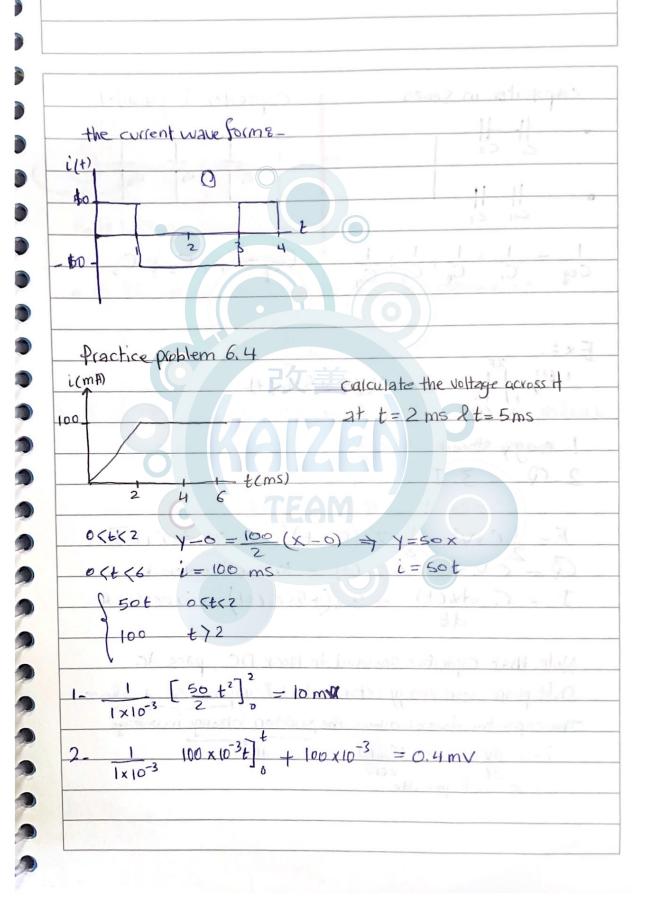


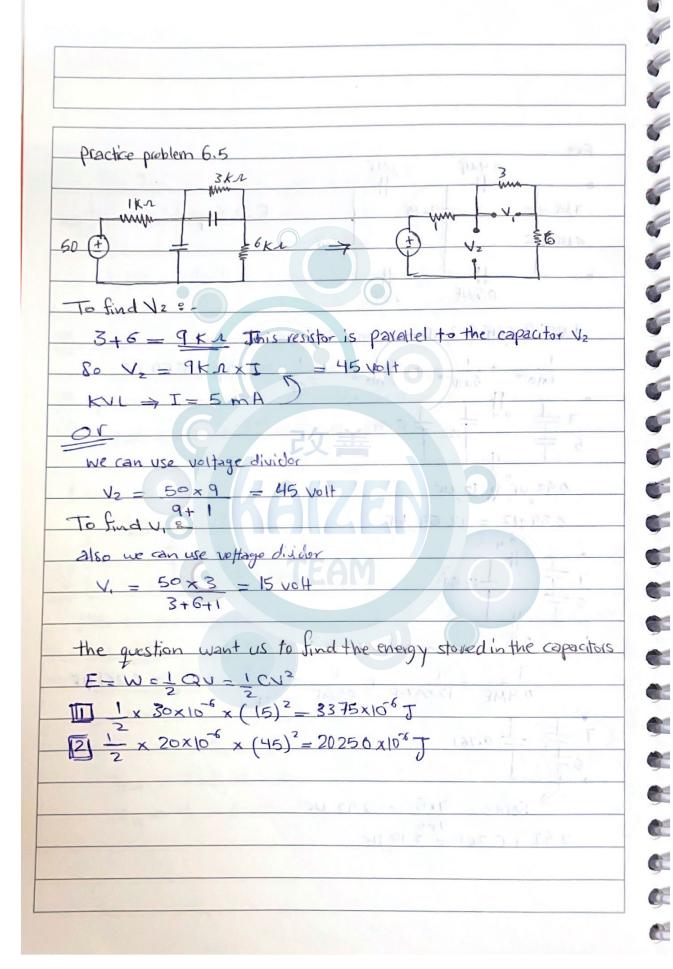


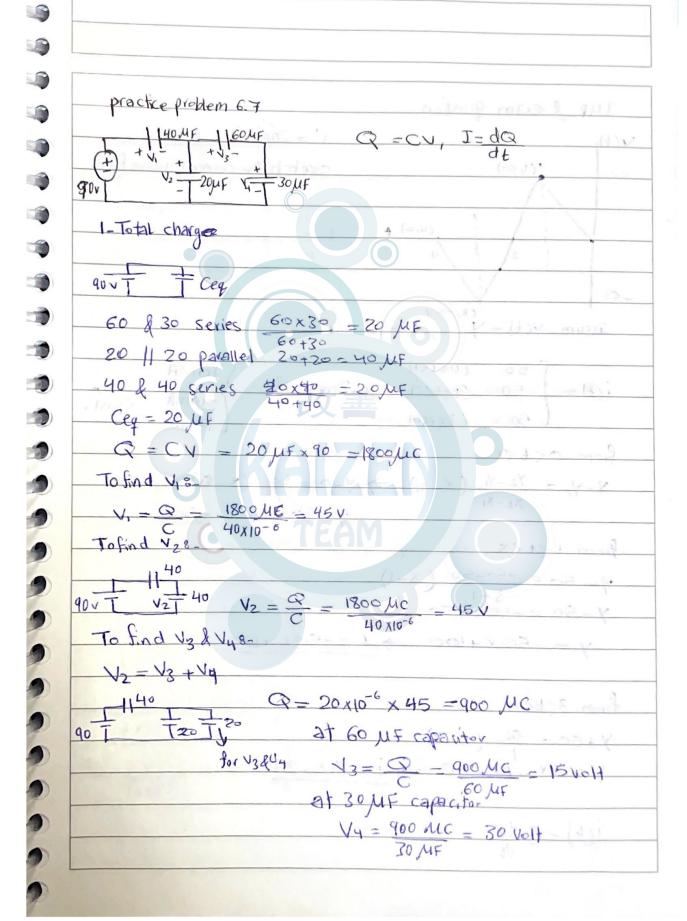


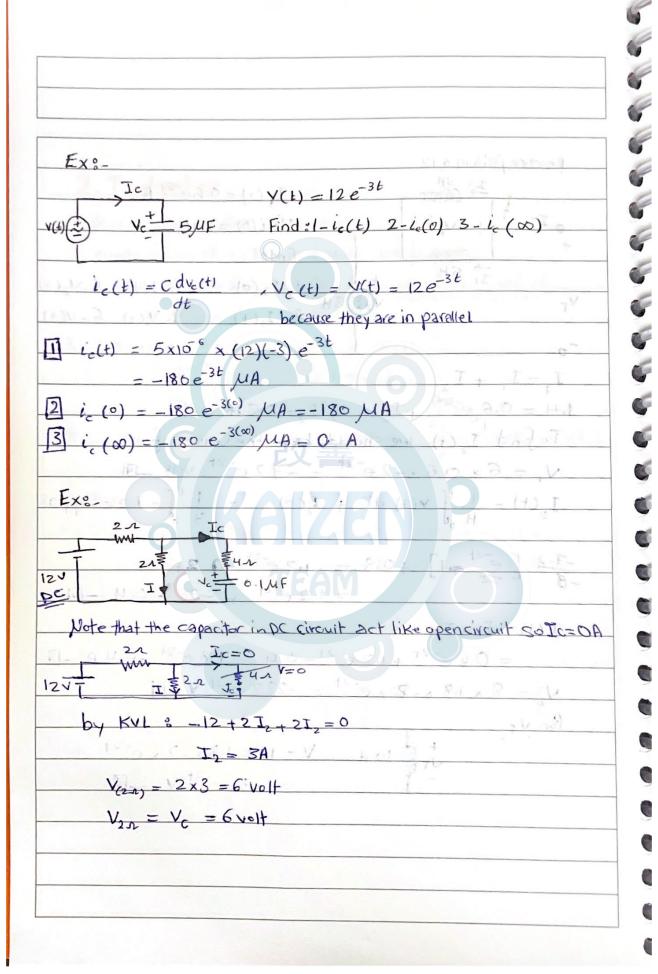


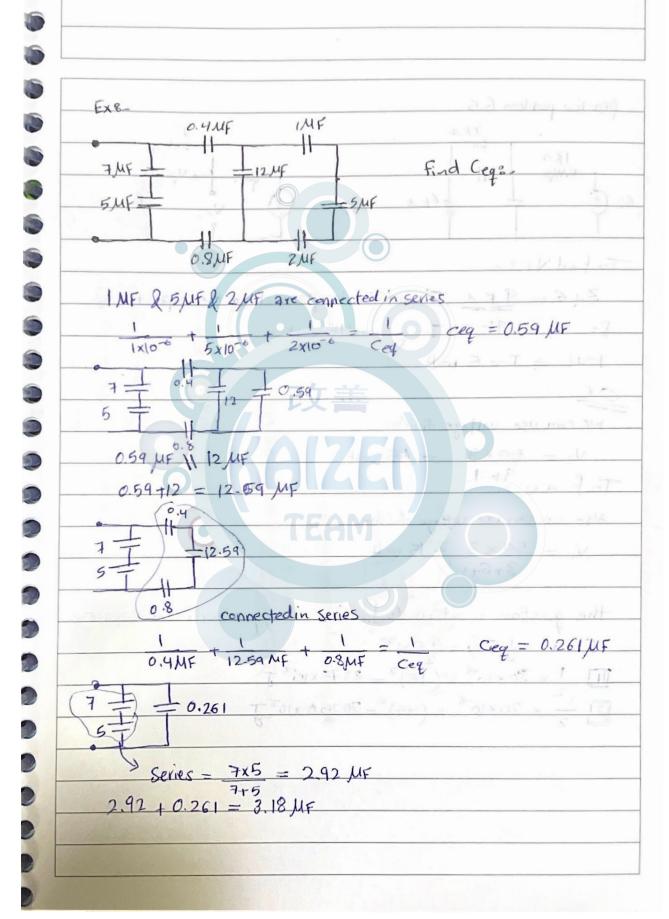

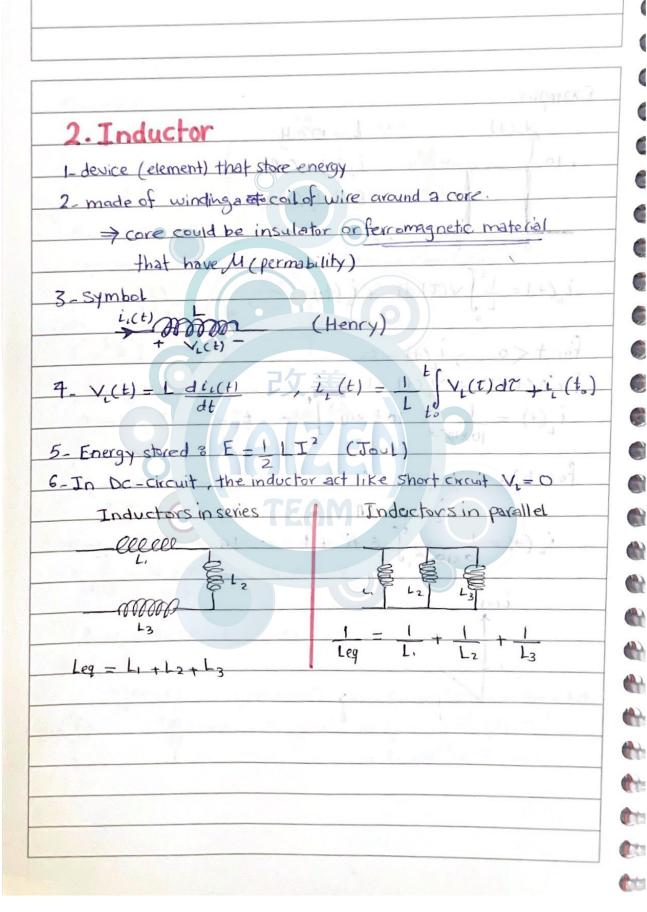

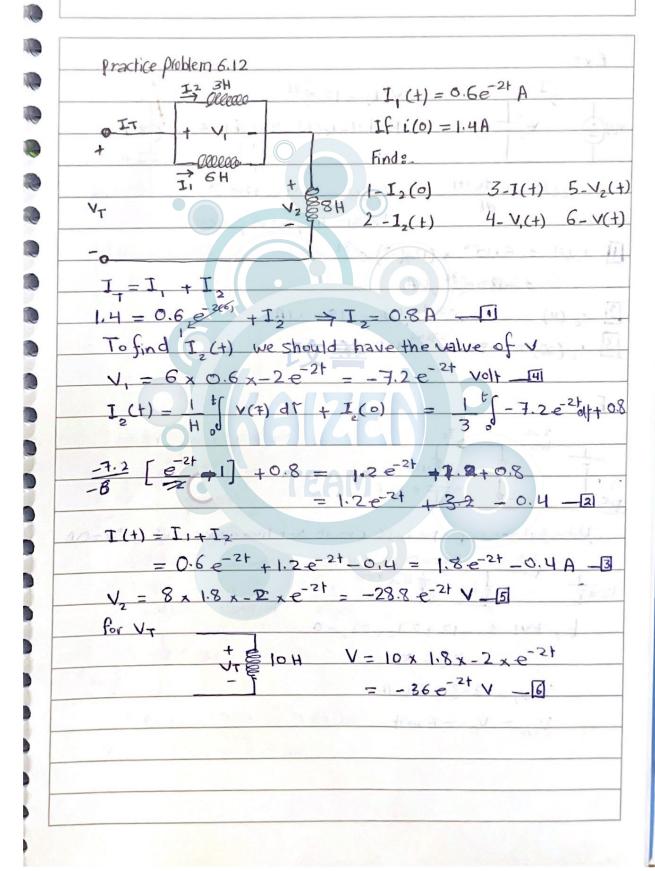

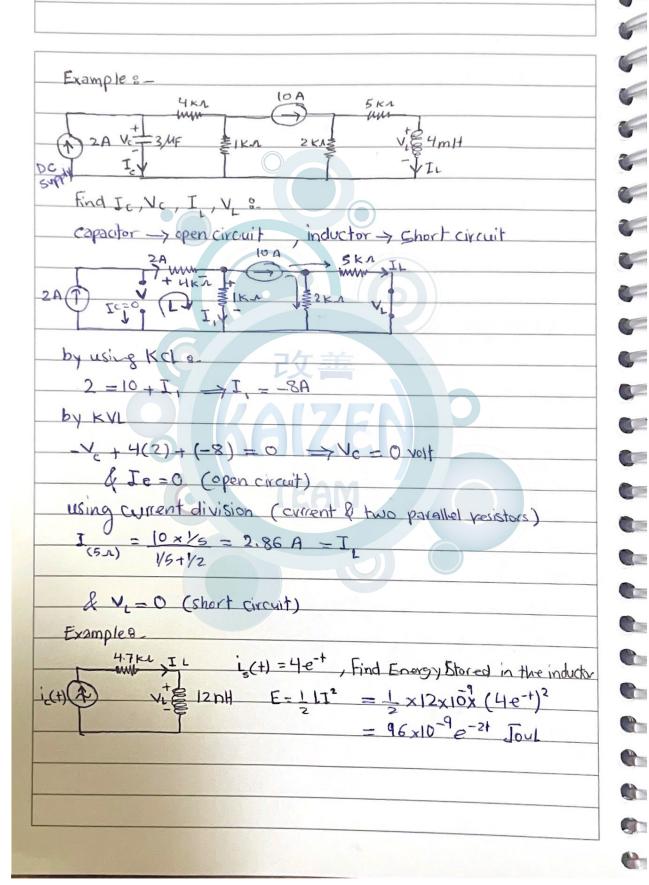

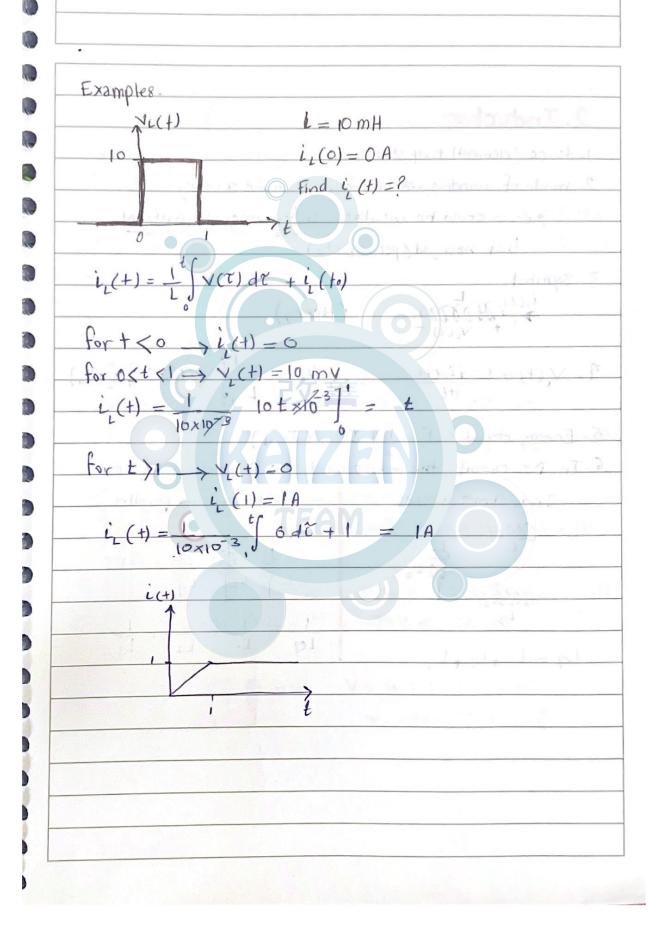

Chapter 9 8 Sinusoids & Phasors

Time Dependent signal so	VCCess_	Set New York 18	Signo)
DC - sources - fixed va			
Para Mas V V	I		
AC (224) (A)	b	t to a land	- 1.0.17
AC - Sources -> generate	Voltage	Cultert varying	5 with time
×(t)		700	1 Ve II
+ + + 50 1	n +	t	Ver Link
triangle signal santoo	h	quare vave	
		S VITTER 30	ICH) lead:
4 124 6043	40	0	
			(000 00)
Pulse-trainsignal	1276	- sign way	e signal
periodic signal & It's a sig	nal Paral		9
Percole signs) . It's a sig	ial ne pear	11 sell aller c	ne persae (1)
Since dal sino	El el		77
Divided 219U	al o-		
X(+) 1	<u> </u>		
XC+)		
year year	:/	Å	
(A)	peak	t t	
B(+ve) B(-ve)			
	101	A = = = = = = = = = = = = = = = = = = =	. 0
$X(t) = A \cos(\omega t - \omega t)$	0)		de of signal (peck)
$y(t) = B \cos(\omega t)$	1.	peak to peak :	= 2 x peak
Z(+) = C cos (w++	φ)		2×A
		Cor	+


3 We radian freq - unit rad/s 3 fornatural freq (HZ) W=2TF -(sec) -0 -A: phase shift between two signal in sec 3 -3 1 period 3 Sin (w) = cos(w+ -90) 7 Example: > moved to left i(+) = 10 cos (377 t (+) 30°) I = 10 A 2×10=20A peak to peak 8 = 30° W = 377 vad/6 2H 00 = 778 = W = 781 = 1 = 0.016 Sec = 10 cos (377 (0.1) +30°) = 7.8A i (0.1 sec) 30 1 1 3

=

2000000	H - 0' - 1 (100	dia a laggina	6.为江西州中国75次本
to Company	e the signals (lea	aing or ragjing	and Grantilad
They show	ld have the same	trequency &	same formulas
examples :-			to crangle x
V(+) = 10 C	05 [400 £ _30°]	NA	0) = X+1X
	os [600 t - 60°]		
7			= trichtantous &
V(+) - 10 c	os[800+ +60°]	irth lead	s v(+) by 10°
	os[(300t +70°]		201 =
1(1)=5(03[(3002 +70]		Jana de Middel
1.000.000	02 [100 +, - 30]		
			= 50s(x-90)
ican	transfe / All	b (+ (i(+) =	5 cos (100+ - 160)
from	sin to cos	v(t) les	ds i(+) by 130°
A = 4	17.0	i(+) (ad	s v(t) by 130°
Sina	= sin(x=180°		Xz
	= COS (X = 180°		batop
		6-3	C+ 62
ZOIG -	= cos(x-90°)		744
According to the second	(a Carrella)	c - New X	Young Not
Complete 9	CASHBY AND	= /	1 6 , Y = , X
× 49+,6	人」」と一般		MAN WATE
120	The bear law	2.0	
2 2 100	7 7 20 EY	XIXX	
	no Physical		5 44 12 1 12 1 1
7 2	12.747.10	1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	
-			
		136	

--Compare between V(t) = -10 cos (w+ +50), I(t) = 12 sin (w+10) -V(t) = 10 cos(wt-130°) I(t) = 12 cos (wt-100°) --0 ight lead 3 3 the first wavethat appears whenwe go 3 on clock wise direction V(H) It will be loads. (IH) 7 & first wave (CW) I(t) leads v(t) by 30° 3 3 1 MESTY 1 (84)8 1 5 AXS

1

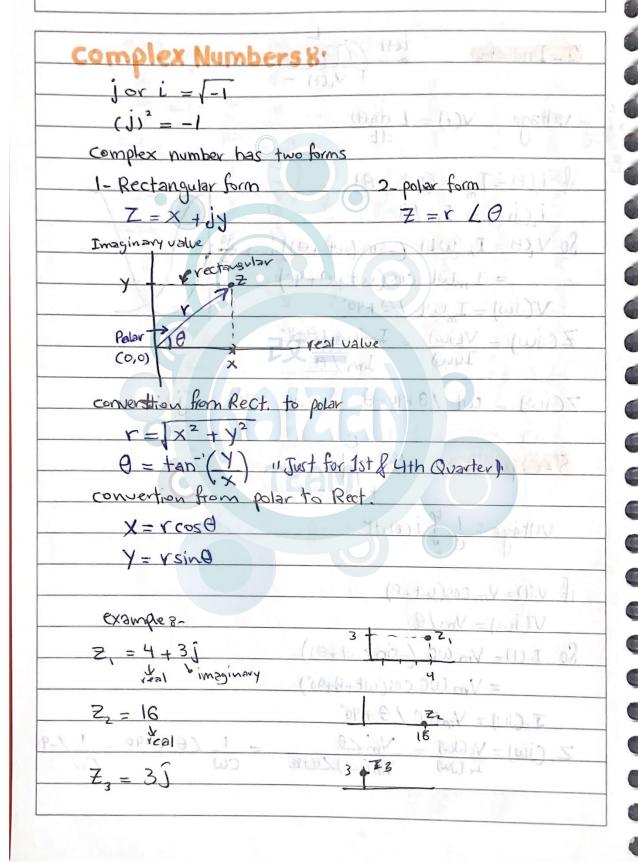

-MATHMATICAL as Addition I made a supplied to the supplied 3 for example x, = a+jb X2=C+jd X1+X2= (a+jb)+(c+jd) 105-4000 21-(4) -= (a+c)+j(b+d)3 3 & subtraction $X_{+}X_{2} = (a+jb)-(c+jd)$ -= (a-c)+i(b-d)-3 & Multiplication - $X_1 \times X_2 = (a + ib) \times (c + id)$ 3 = ac +jda +jbc -bd (ac bd) + j(da + bc) & division 1 state Come $X_1 = a+jb \times (c-jd)$ $X_2 = c+jd \times (c-jd)$ $\frac{ac+bd}{C^2+d^2}+\frac{1}{bc-ad}$ For polar $X_1 * X_2 = (r_1/\theta_1)(r_2/\theta_2)$ $X_1 = r_1 / \theta_1 + \theta_2$ $\frac{X_1 - r_1 \angle \theta_1}{X_2} = \frac{r_1}{r_2} \angle \frac{\theta_1 - \theta_2}{r_2}$ 1 $\chi_2 = r_2 / \theta^2$ XIIX2= 1, LO, tr2 LO2


-

-

Sinusoidal signals in Frequedomain
time domain $\rightarrow X(t) = A \cos(\omega t + \theta)$
Freq. domain > X(iw) = A 10 As peak value Osphase shift ref
Examples to cosine signal
V.(+) = 15 cos(377++ II)
$V_2(t) = 15\cos(3776+11)$
Find $V_s(t) = V_1(t) + V_2(t)$
V, (jw)=15/11/4 V2 (jw)=15/11/12
V8 = V, (ciw) + V2 (iv) (ctx fam 1160 sell-day)
= 25-1 + j 14.5 P > 28.98 / TT/6
V _s (+) = 28.98 cos(377++T)
- OLIAN ORD
Impedance (3) Va Sur Dave Vi Ph
-> we will describe the circuit element (R, L, C) in Ac circuit
" they will have impedance"
L- Resistor (1) MM
if v(+) = 1 cos (w++1) + v(+) -
- Viw - Vm 10 / Later 1
to find I (Ju) = V(Ju) = Vm/0 = Vm/0 shift between
$J(t) = V_m \cos(\omega t + B)$ R R Voltage govern
R
Z(jw) = V(jw) = Vm/t = R/20~> There is no phase shift
$Z_{p}(jw) = R$
IUF

2-Inductor voltage: V(+) = L dic(+) 1 if i(t)=I cos(w++0) i(Jw) = Im/0 3 80 V(t) = Im(WL) (-sin (wt +0)) = I mul cos(w+0+90) V(jw) = I w/ 10+90° ZCojus = Vcojus = Imul 10+90° Z(Jw) = w/ 10+90-0 = w/ 190° 3-capacitor Voltage : 1 \$ i(x) dt if Vo(t) = Vm cos(w+0) V(iw) = Vm/0 So Ic(+)= Vm WC (-sin (w++0)) = Vm WC cos(wt+0+90°) -IcClw) = Vm Cuc / 0+90° Z_c(jw) = Vc(Jw) = Vm (UC) / 0+90 1 1 1

3

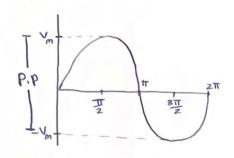

V(t) = Vm sin (wt+ p) the begining of the wave

If we want to compare two waves

$$\begin{array}{c} sin \rightarrow cos & \phi - 9^{\circ} \\ cos \rightarrow sin & \phi + 90^{\circ} \\ -sin \rightarrow sin & \phi \pm 180^{\circ} \\ -cos \rightarrow cos & \phi \pm 180^{\circ} \end{array}$$

phasor (complex number)

> real axis

$$r = \sqrt{x^2 + y^2}$$

$$\phi = \tan(\frac{y}{x})$$

$$x = r\cos\phi$$

$$y = r\sin\phi$$

Imagin any

 $Z_1 \mp Z_2$ (must be vectangular form) = $(x_1+iy_1) \mp (x_2+iy_2)$ (x_1+x_2) $\mp i(y_1+y_2)$

 $Z_1 * Z_2$ (must be in polarform) = $r_1 \angle \theta_1 + r_2 \angle \theta_2$

 $\frac{Z_1}{Z_2}$ (must be in polar form) = $\frac{r_1}{r_2} \frac{1}{1 + r_2} \frac{1}$


$$\frac{1}{Z} = \frac{1}{VL0} = \frac{2-0}{r}$$


VZ = VrlG must be in polar = [r] 18/2


Z* = X Ojy (convert the sign from t to - (vice verca))
= r/e -> v/o

$$\dot{J} = \frac{1}{-J} \quad 5 - \dot{J} = \frac{1}{J} \quad 5 \quad \frac{1}{J} = -\dot{J} \quad 5 \quad \frac{1}{-\dot{J}} = \dot{J}$$
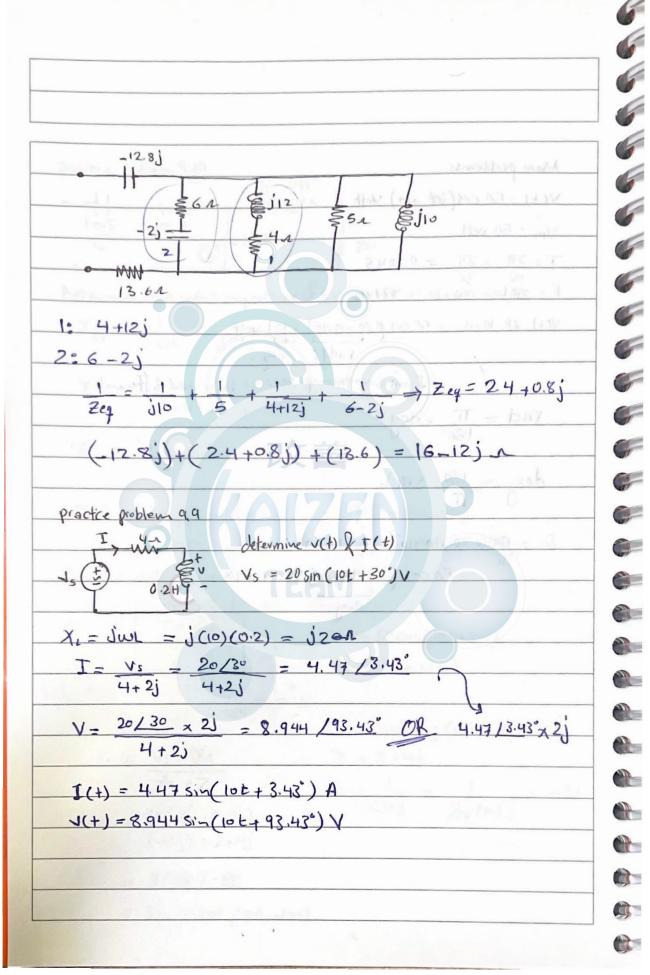
$$\int_{V} d(t) = \frac{V}{J} \quad \int_{V} dv = J\omega V$$



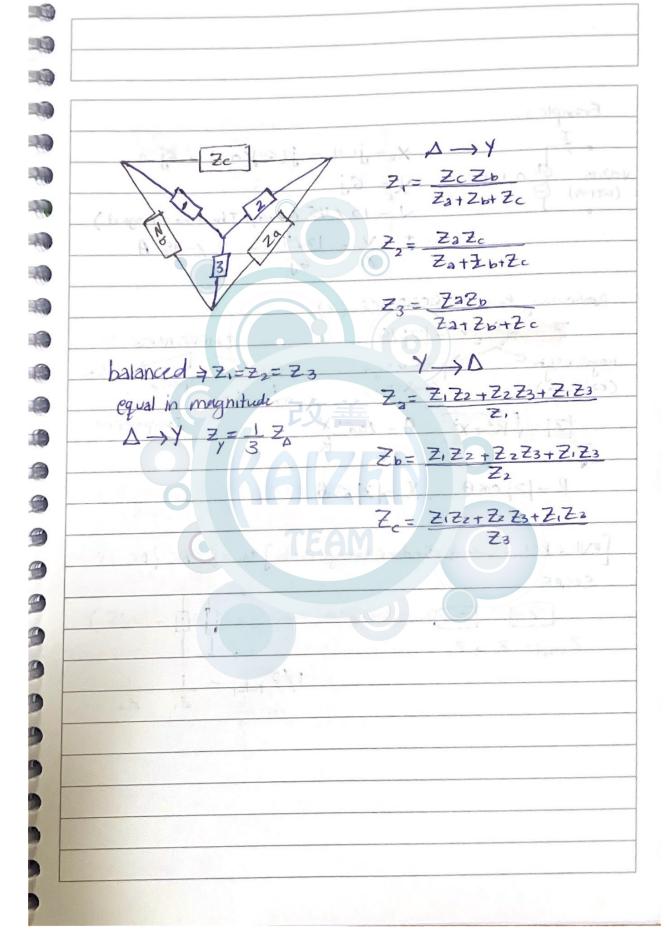

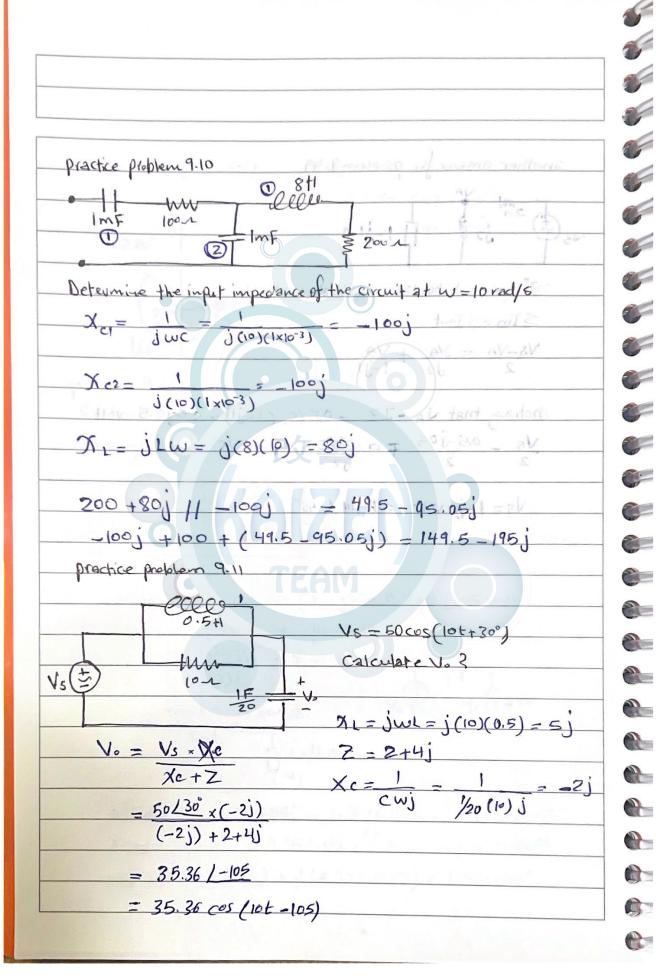

More problems. V(t) = 50 cos(30t +10) Volt Vm = 50 Volt T = 2TT = 2TT = 0.2045 F = 2TT W = 2TT x30 = 4.71 Hz V(t) at 10 ms = 50 cos (30 x10x10 ³ + 10) volt Vad/s deg. Trant Sum therrup be cause the Vad = TT x deg.	2eq 310 /
Vm = 50 volt T = 2TT = 2TT = 0.2045 F = 2TT W = 2TT x30 = 4.77 Hz V(t) at 10 ms = 50 cos (30 x10x10 ³ + 10) volt rad/s deg. Trant Sum thereop because the	ay are different
$T = 2\pi = 2\pi = 0.2045$ $F = 2\pi \omega = 2\pi \times 30 = 4.71 Hz$ $V(t)$ at 10 ms = 50 cos (30 x 10 x 10 ³ + 10) volt rad/s deg. - I can't Sum them up be cause the	ay are different
F = 211 W = 211x30 = 4.77 Hz V(t) at 10 ms = 50 cos (30 x10x103 + 10) volt rad/s deg. - I can't Sum therap be cause the	ay are different
V(t) at 10 ms = 50 cos (30 x10x103 + 10) volt rad/s day. I can't sum themup be cause the	ay are different
- I can't Sum themup be cause the	ey are different
- I can't sum themup be cause the	ey are different
	2eq 310 /
rad = TT x deg:	2 4010 405
	0 14/12 01/1
dey - 180 xvad.	100
TT TOTAL	
	- 6 leg s draw
80 = 80 x 30 x 10 x 10 3 = 17.19	The state of
50 cos (17.9 +10) = 44.19	volt
deg	
Aux 1, - 1000	pal - July - X
ED. 87 FH 19 (2) 05/	O. W. T
	18+12
- 8 444 /13.43 PR 44431845 21	in novem
THE STATE OF THE S	V- 20/30 x 21
A (51. 8 4 30)	JONE HILLS (1) }
V (*5 = 5 P + 10)	JULY = ROLLY SING

