

# Chapter 2: Basic Laws

## Lecture#1

### Reference:

Fundamentals of  
**Electric Circuits**

Charles K. Alexander | Matthew N. O. Sadiku




- This chapter will introduce Ohm's law: a central concept in electric circuits.**
- Resistors will be discussed in more detail.**
- Circuit topology and the voltage and current laws will be introduced.**
- Finally, meters for measuring voltage, current, and resistivity will be presented.**

# Ohm's Law

## □ Resistance:

- ✓ **Def:** *a material property to resist the flow of the electric current.*
- ✓ **Symbol:**  $R$
- ✓ **Unit:** Ohm,  $\Omega$
- ✓ In mathematical form (as measured in the Lab):


$$R = \rho \frac{\ell}{A}$$

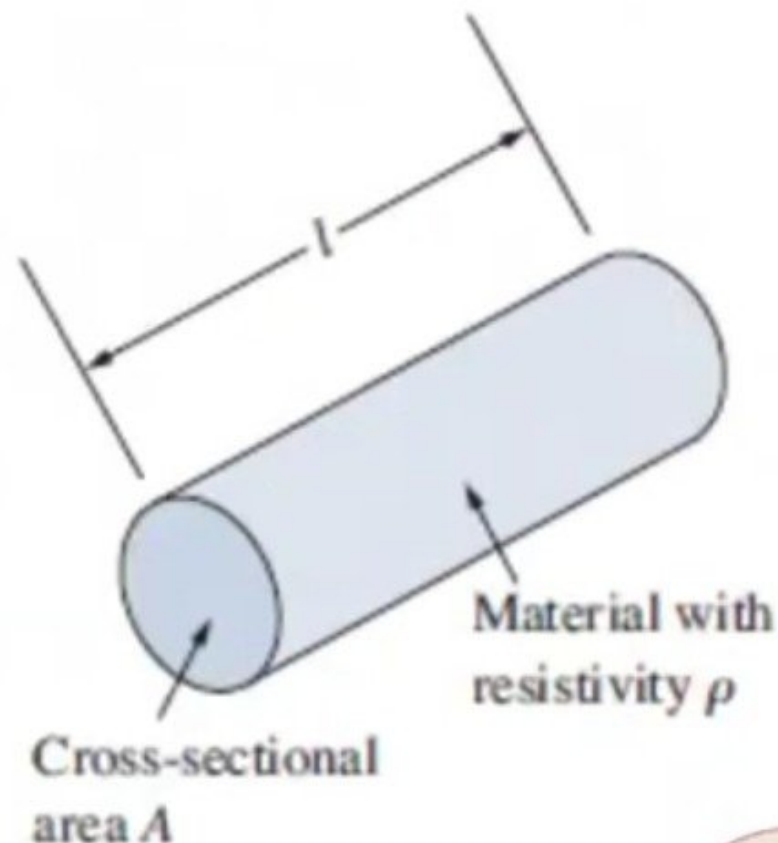


# Ohm's Law
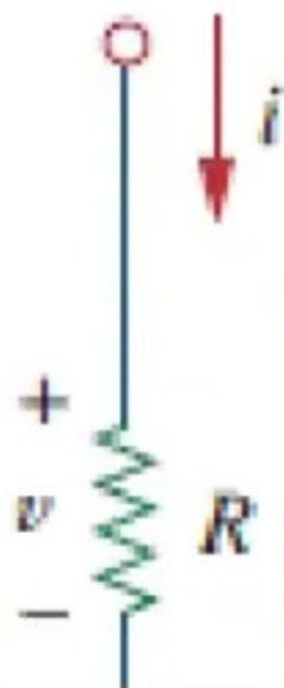
## □ The Resistor:


- ✓ **Def:** *The circuit element used to model the current-resisting behavior of a material.*
- ✓ The resistor has a resistance  $R$ .
- ✓ It is the basic passive element in a CKT.
- ✓ Use passive sign convention.



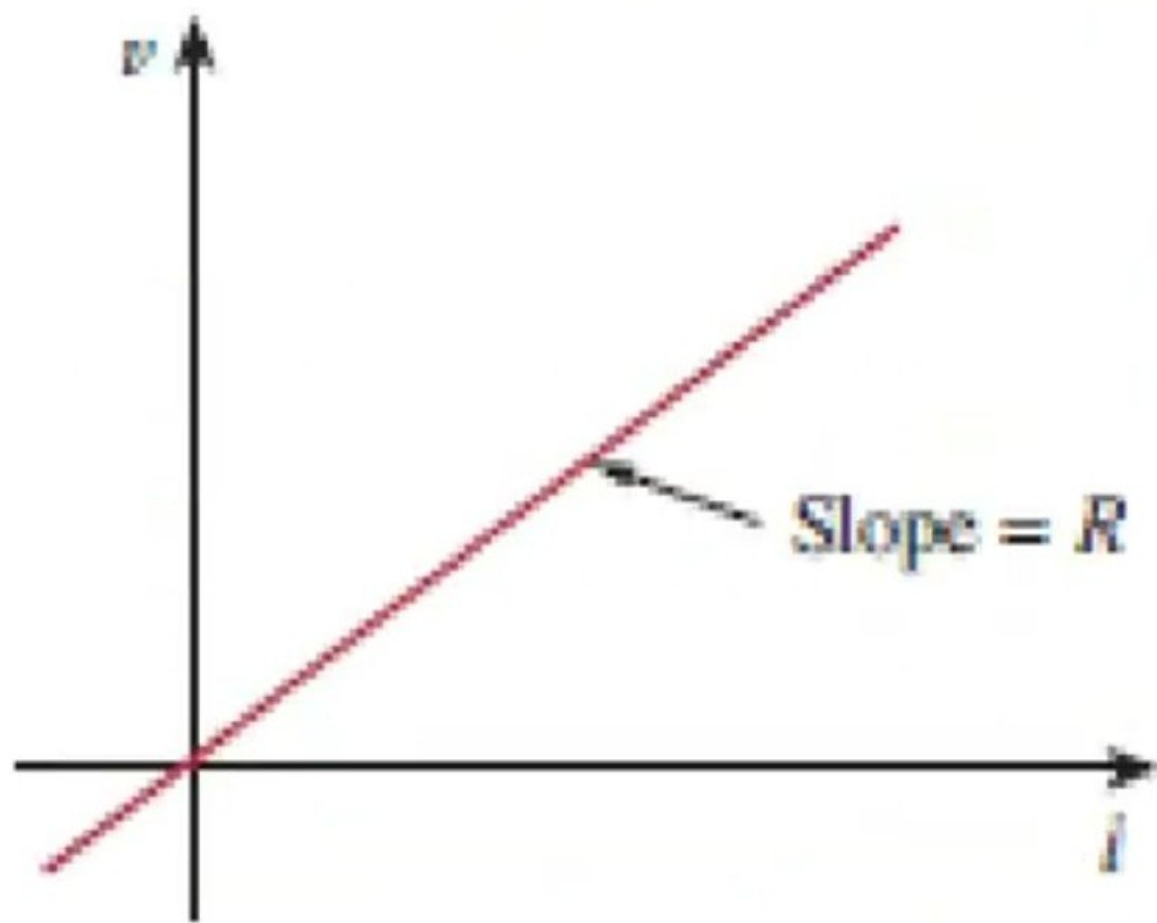
Resistors that obey Ohm's law are linear.



$$v = Ri$$

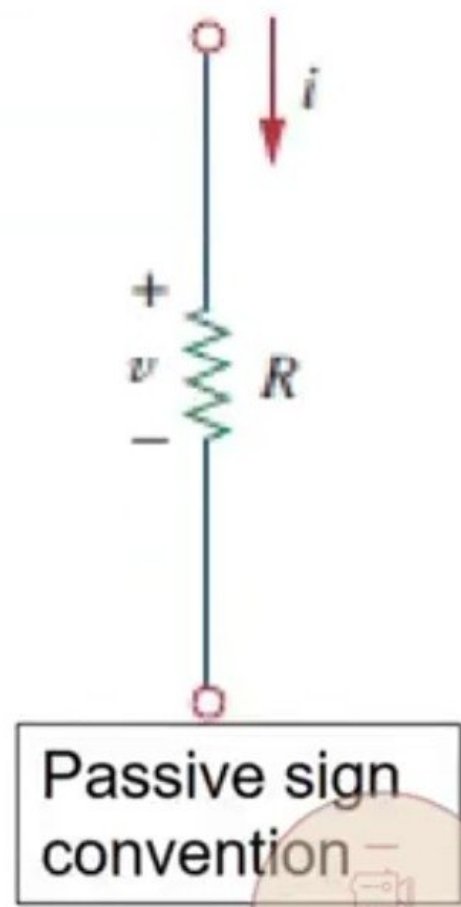


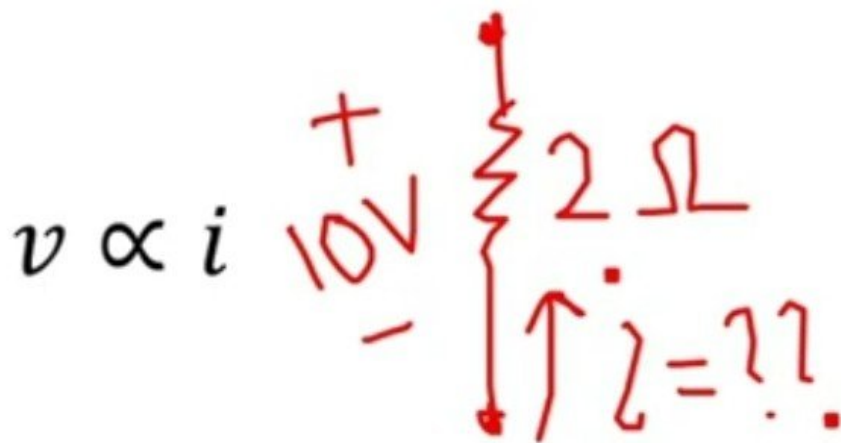- ✓ **Def:** the voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through the resistor.



- ✓ Ohm defined the constant of proportionality for a resistor to be the resistance,  $R$ , which is a material property.
- ✓ Mathematical form:

$$v = Ri$$

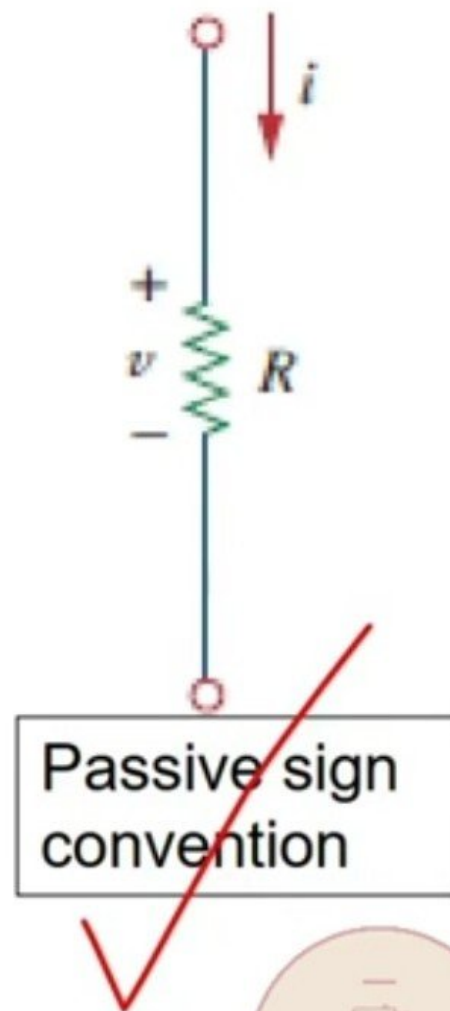

## □ Ohm's Law:

- **Note:** Ohm's law implies that:

$$R = \frac{v}{i}$$


and

$$i = \frac{v}{R}$$

and

$$1 \Omega = 1 \text{ V/A}$$

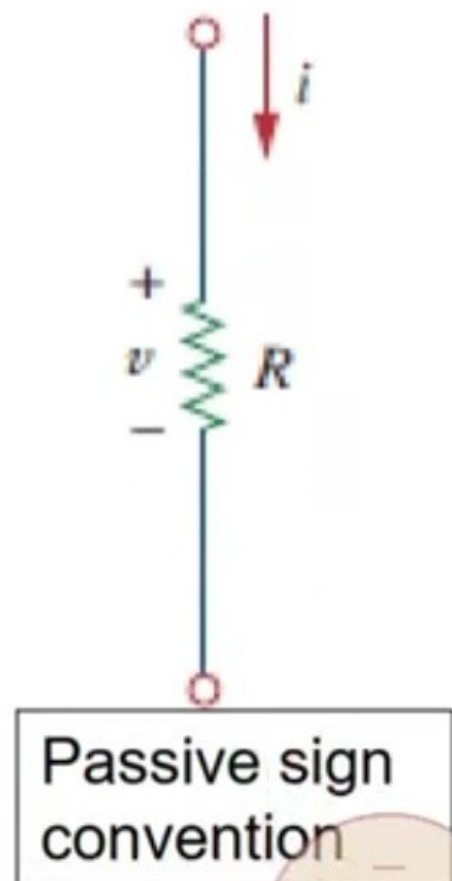- **Note:** To apply Ohm's law, the direction of current  $i$  and the polarity of voltage  $v$  must conform with the passive sign convention.



# Ohm's Law

## □ Short Circuit (S.C.):


- S.C. is a circuit element with resistance approaching zero.
- This implies that:

$$v = Ri = (0)i = 0$$

but the current could be anything.

- **Note:** in practice, a short circuit is usually a connecting wire assumed to be a perfect conductor.

WIRES  
NUMBERS

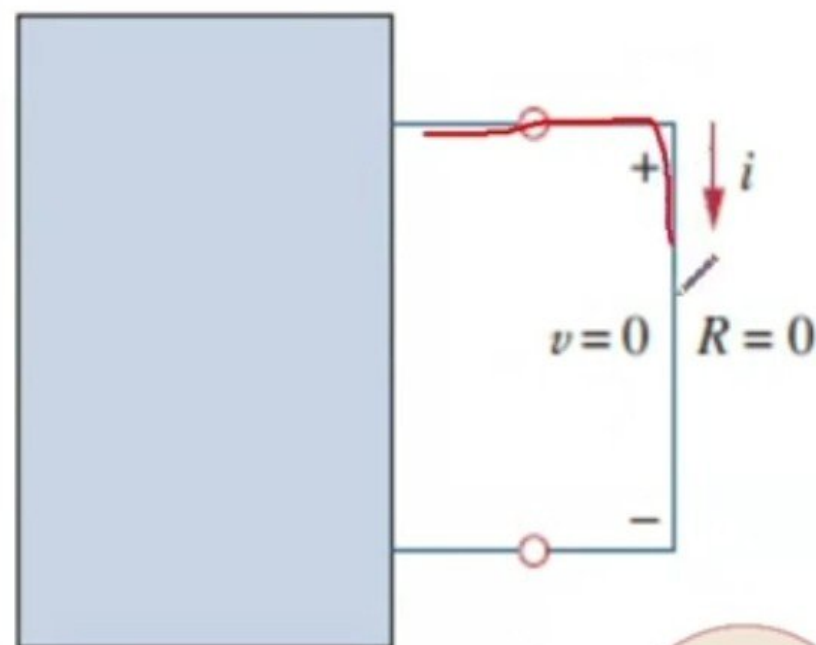


# Ohm's Law

## □ Open Circuit (O.C):

- O.C: is a circuit element with resistance approaching  $\infty$ .
- This implies that:

$$i = \lim_{R \rightarrow \infty} \frac{v}{R} = 0$$

but the voltage could be anything.

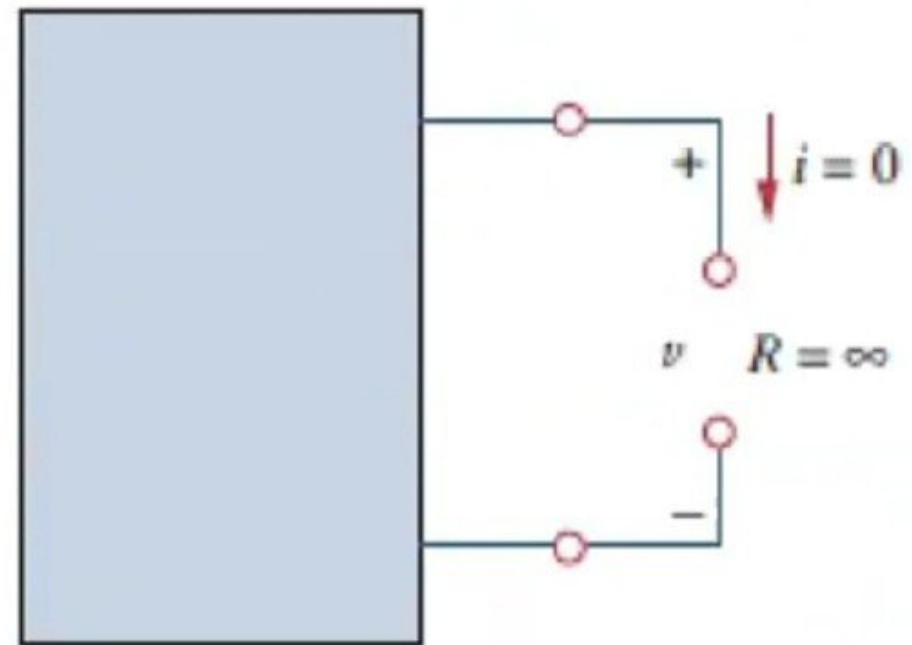

# Ohm's Law

## □ The Conductance $G$ :

- It is the reciprocal of resistance  $R$ .
- It is the ability of an element to conduct electric current.
- it is measured in mhos  $\mathcal{U}$  or siemens ( $S$ ).

$$G = \frac{1}{R} = \frac{i}{v}$$

$$1 S = 1 \mathcal{U} = 1 A/V$$




# Ohm's Law

## □ Power Dissipated by a Resistor:

$$p = vi = i^2R = \frac{v^2}{R}$$

$$p = vi = v^2G = \frac{i^2}{G}$$

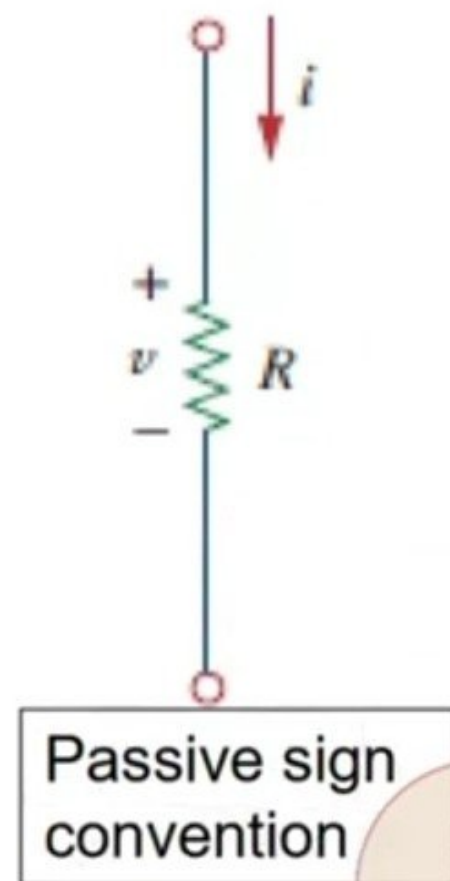

# Ohm's Law

## ❑ Power Dissipated by a Resistor:

### ❖ Note:

1. The power dissipated in a resistor is a nonlinear function of either current or voltage.
2. Since  $R$  and  $G$  are positive quantities, the power dissipated in a resistor is always positive. Thus, a resistor always absorbs power from the circuit. This confirms the idea that a resistor is a passive element, incapable of generating energy.



48. For each of the circuits in Fig. 2.38, find the current  $I$  and compute the power absorbed by the resistor.

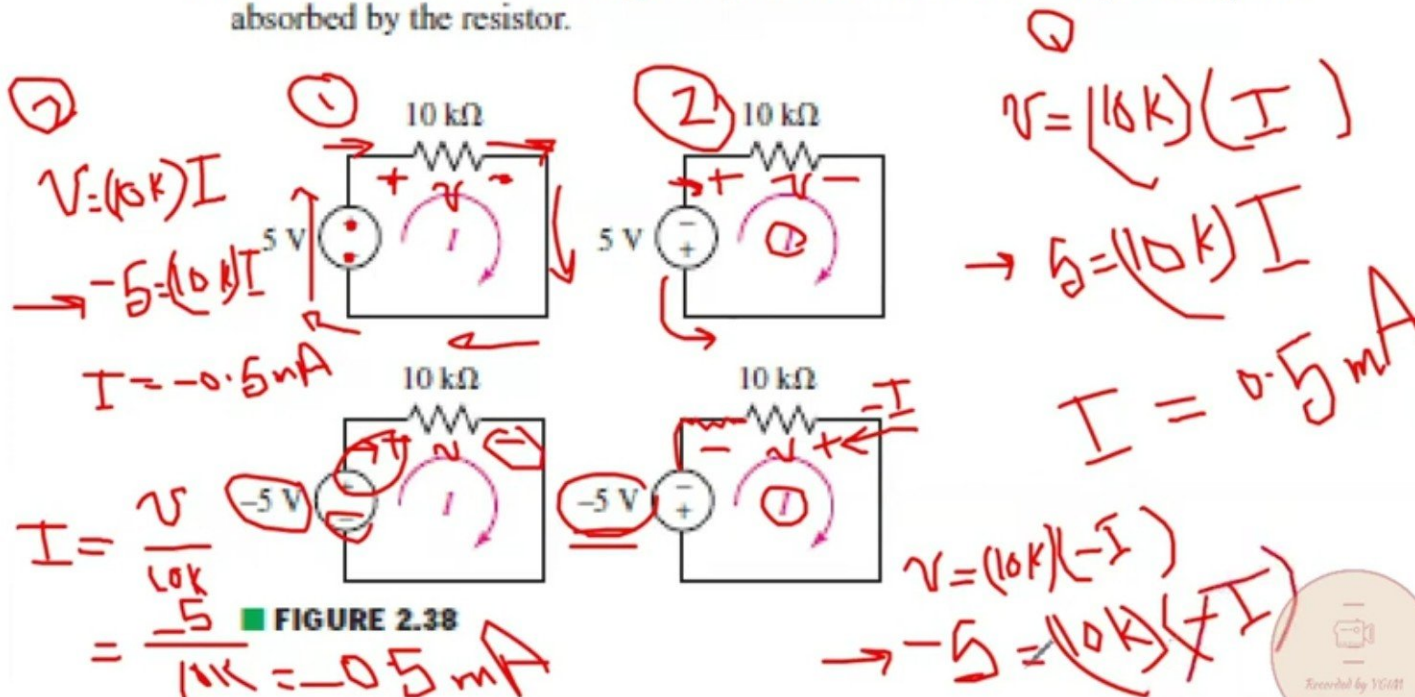



FIGURE 2.38

Ref: Hart, William Hart, Jack Ellsworth Kemmerly, and Steven M.

# Ohm's Law
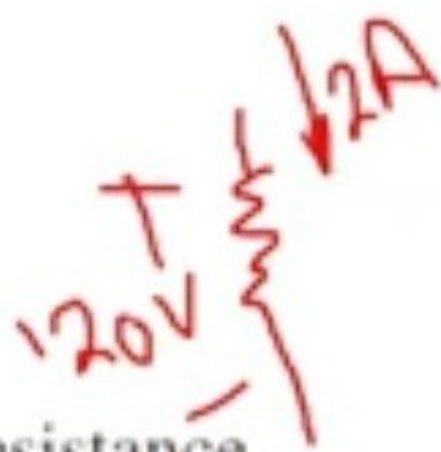
## Example 2.1

An electric iron draws 2 A at 120 V. Find its resistance.



### Solution:

From Ohm's law,


$$R = \frac{V}{i} = \frac{120}{2} = 60 \Omega$$



## Practice Problem 2.2

For the circuit shown in Fig. 2.9, calculate the voltage  $v$ , the conductance  $G$ , and the power  $p$ .

**Answer:** 30 V,  $100\ \mu\text{S}$ , 90 mW.

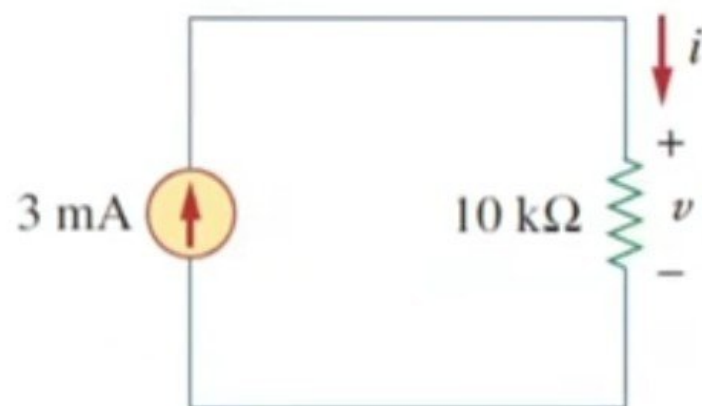


**Figure 2.9**

For Practice Prob. 2.2



# Ohm's Law

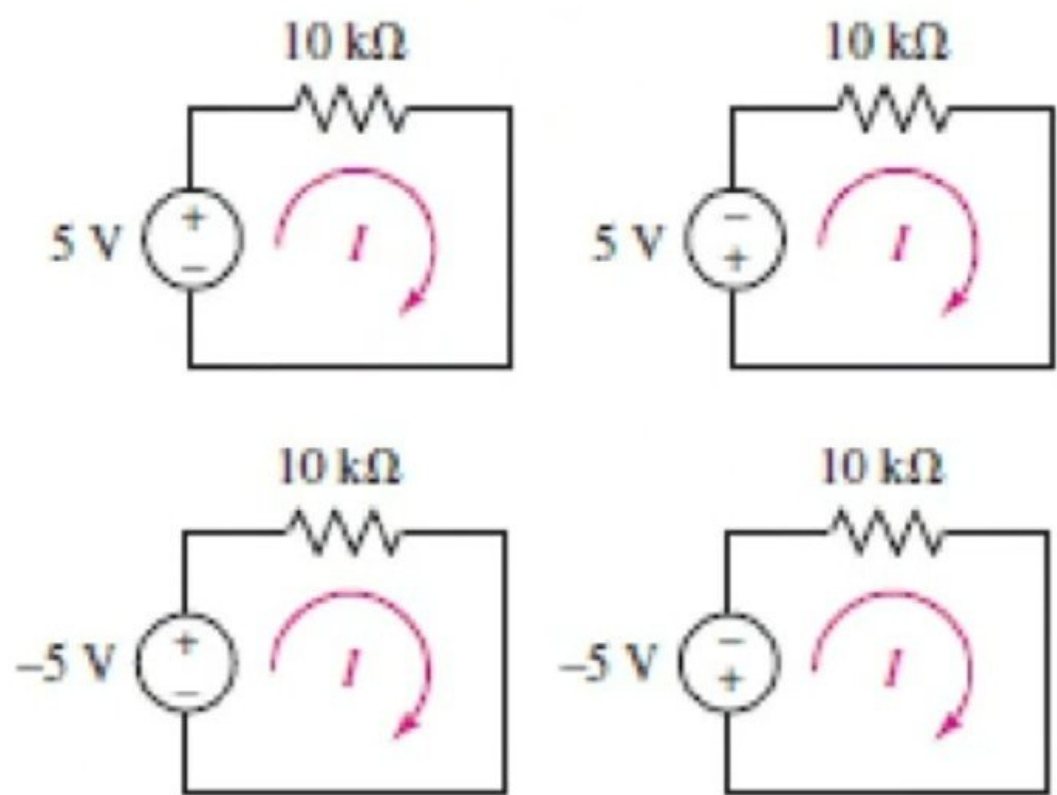48. For each of the circuits in Fig. 2.38, find the current  $I$  and compute the power absorbed by the resistor.




■ FIGURE 2.38


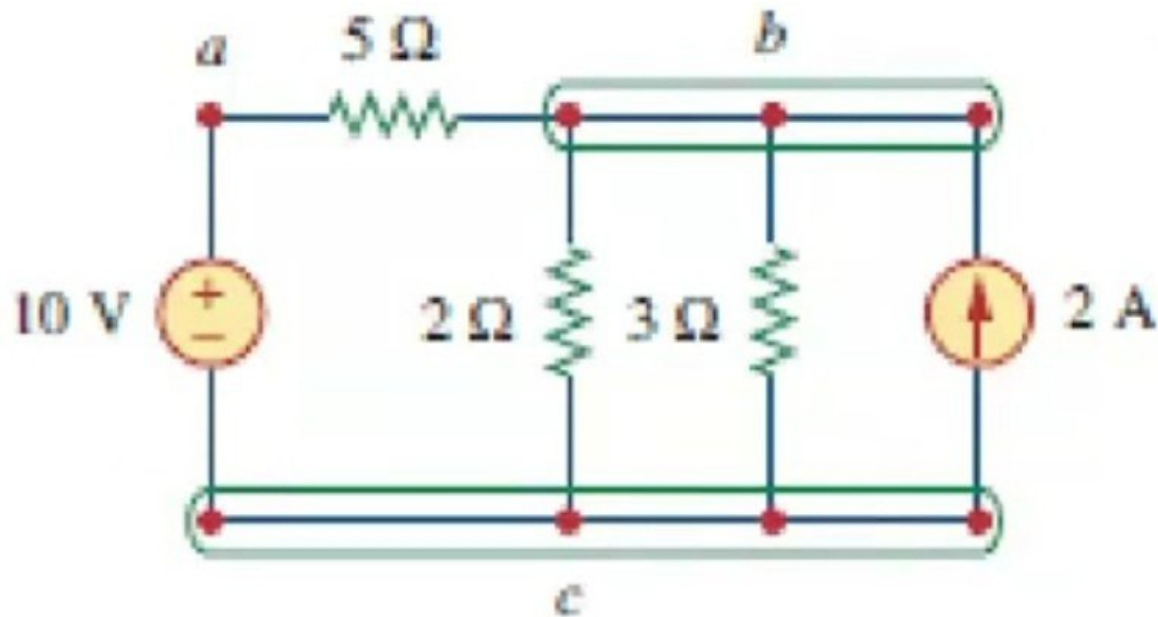
# Network Topology


□ **Branch:** *represents a single element such as a voltage source or a resistor (two-terminal element.)*

Note: a branch can represent elements in series.



❑ **Node**: the point of connection between two or more branches.

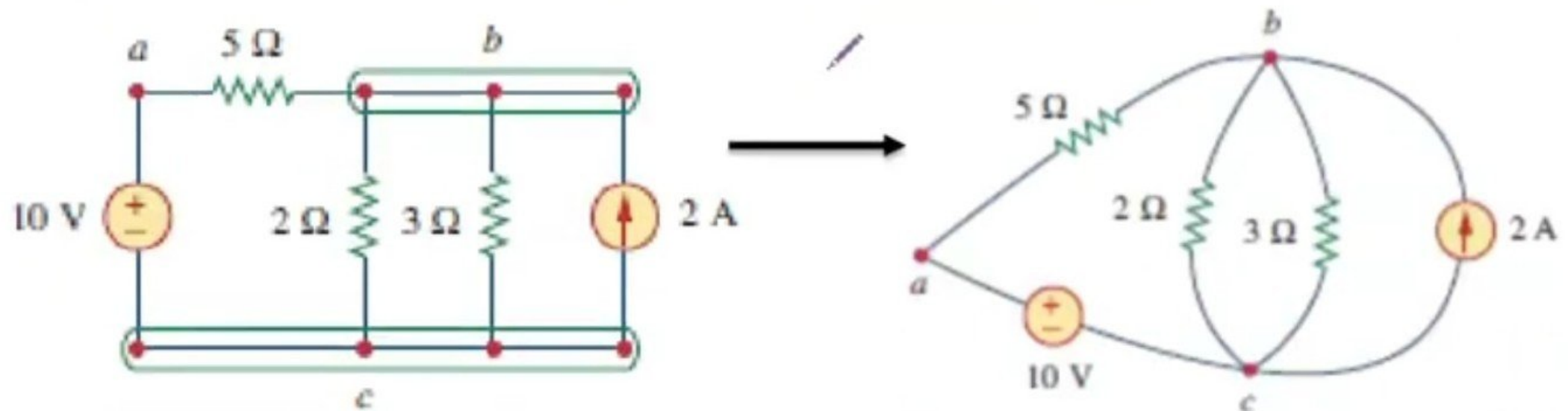❑ Note: usually indicated by a dot in a CKT.




▪ **The CKT has 3 nodes.**



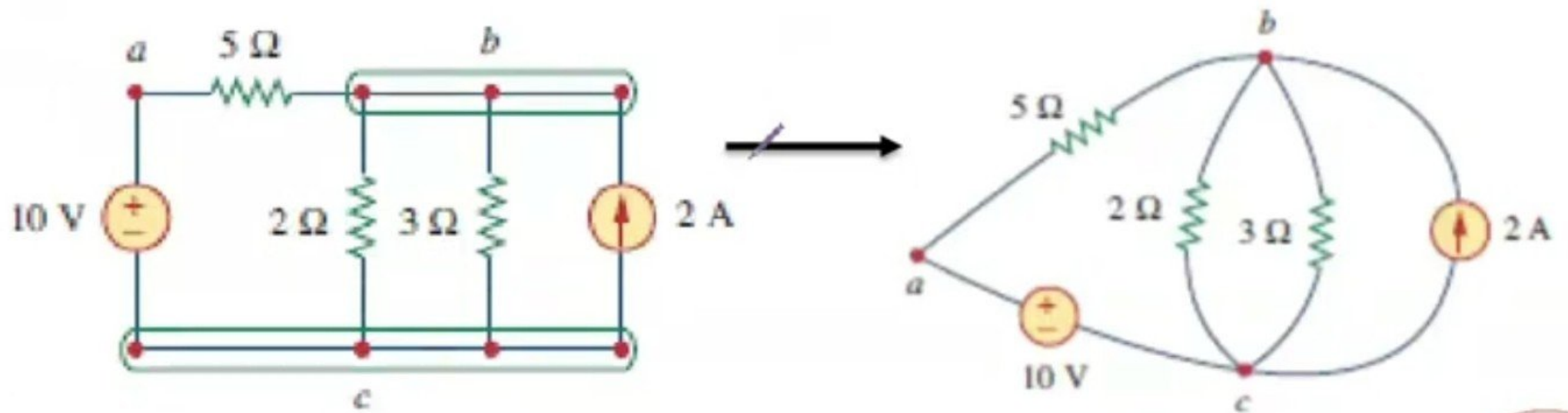
# Network Topology

□ **Path:** *a set of nodes and element passed.*


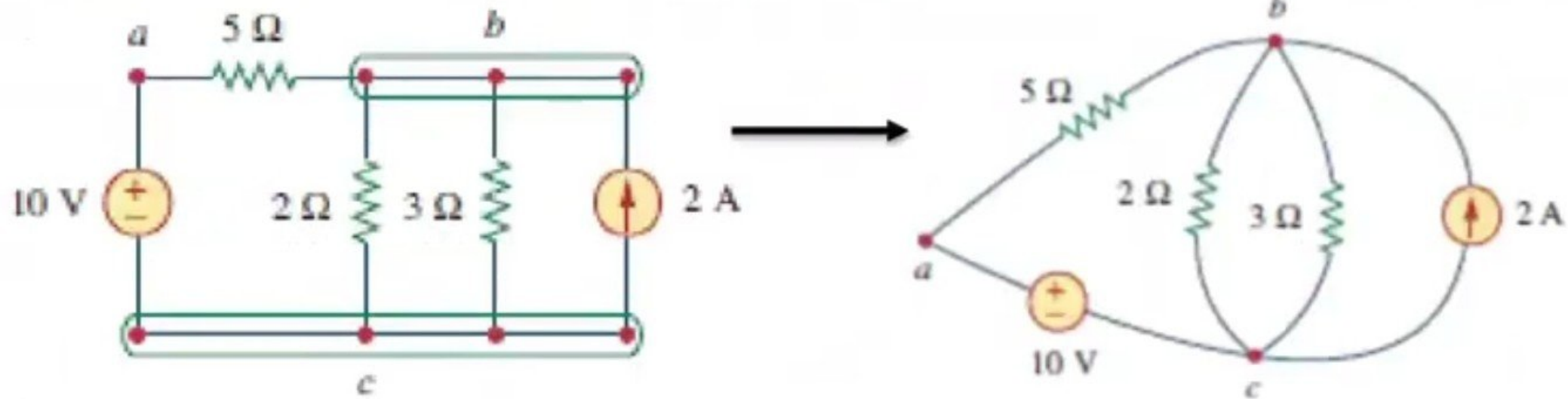
# Network Topology

□ **Loop:** is any closed path in a CKT (path from a node and back to the same node).



□ **The CKT has 6 loops.**



# Network Topology

- **Elements in Series**: *exclusively share a single node and consequently carry the same current.*
  
- **Elements in Parallel**: *are connected to the same two nodes and consequently have the same voltage across them.*




- Ref: Hayt, William Hart, Jack Ellsworth Kemmerly, and Steven M. Durbin. *Engineering circuit analysis*. New York: McGraw-Hill, 2002.

Dr. Yazid Khattabi. Electrical Circuits (I). The University of Jordan

18

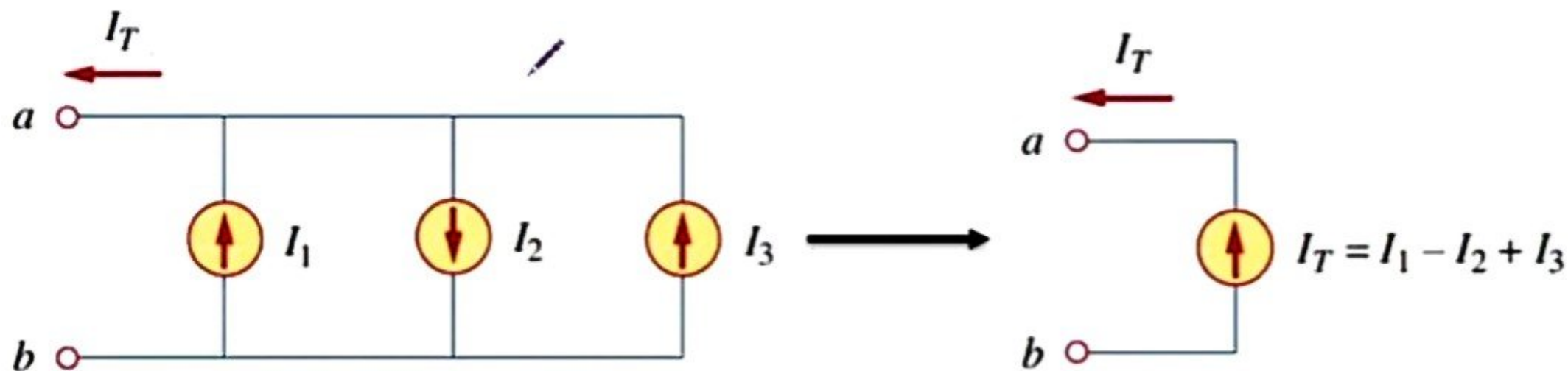
## Kirchhoff's current law (KCL).

- **Application of KCL**: combining current sources in parallel.



## PRACTICE

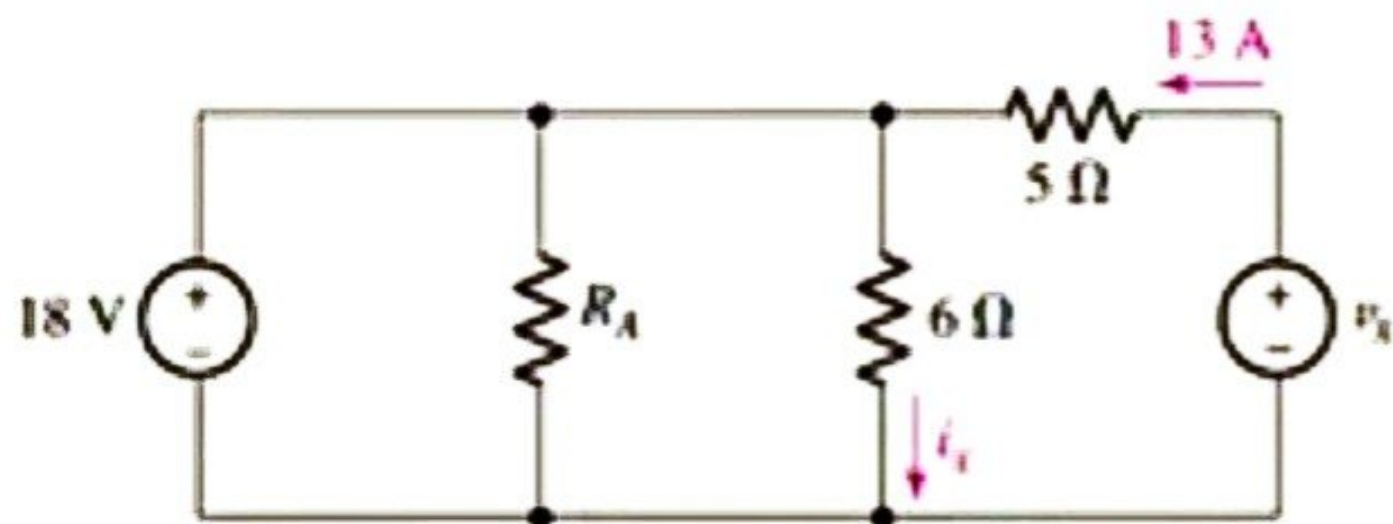3.1 Count the number of branches and nodes in the circuit in Fig. 3.4. If  $i_x = 3$  A and the 18 V source delivers 8 A of current, what is the value of  $R_A$ ? (Hint: You need Ohm's law as well as KCL.)



■ FIGURE 3.4


---

Ans: 5 branches, 3 nodes, 1 Ω.

# Kirchhoff's current law (KCL).

## Example 2.7

Find current  $i_o$  and voltage  $v_o$  in the circuit shown in Fig. 2.25.

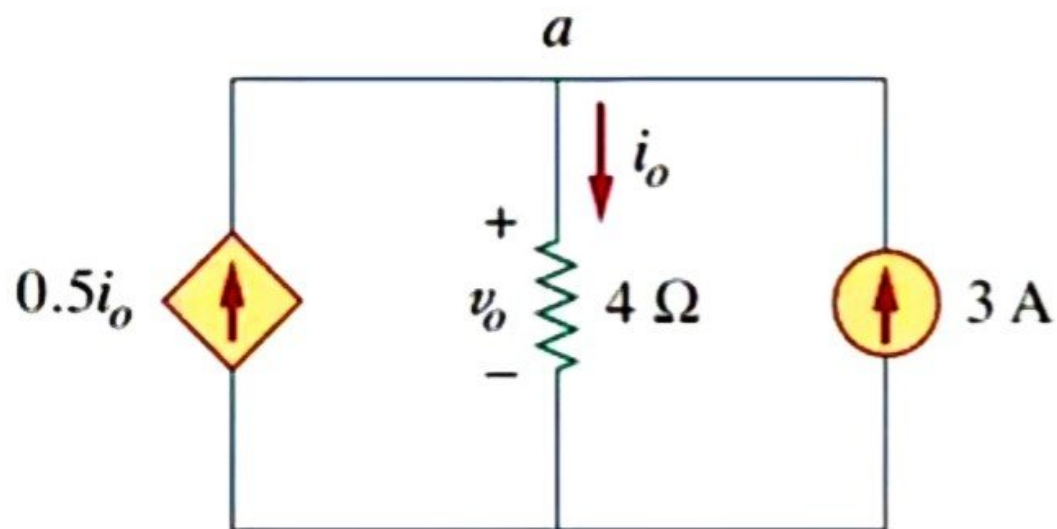


**Figure 2.25**

For Example 2.7.

## Example 2.7

Find current  $i_o$  and voltage  $v_o$  in the circuit shown in Fig. 2.25.

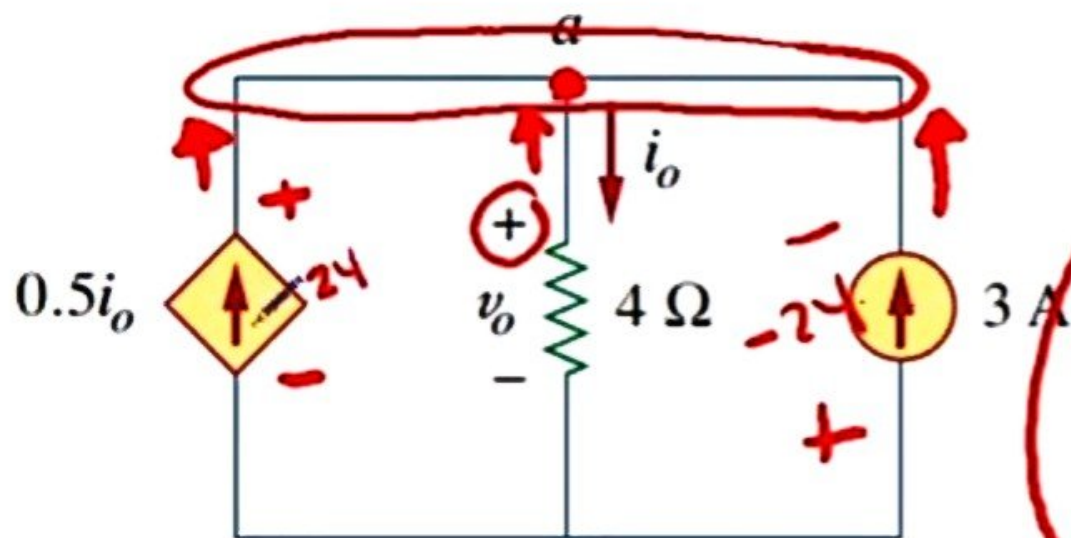

**Figure 2.25**

For Example 2.7.

$$v_o = 4i_o \quad \text{--- (1)}$$

$$0.5i_o - i_o + 3 = 0$$


$$\Rightarrow i_o = 6 \text{ A} \quad \checkmark$$

$$v_o = (4)(6) = 24 \text{ V} \quad \checkmark \checkmark$$

Find  $v_o$  and  $i_o$  in the circuit of Fig. 2.26.

**Answer:** 12 V, 6 A.

**HW:** also find the power absorbed by each element.

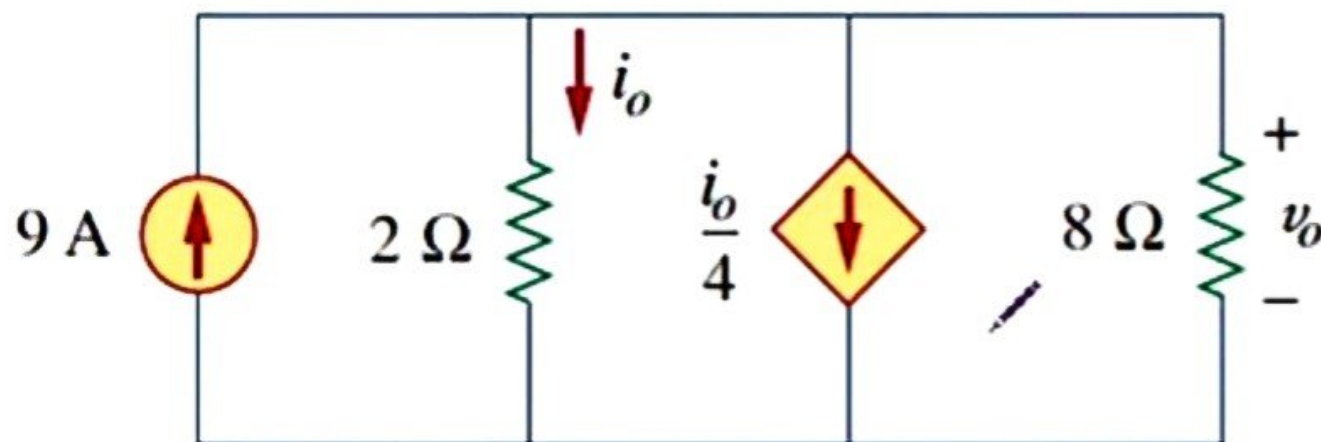

**Figure 2.26**


For Practice Prob. 2.7.

Find  $v_o$  and  $i_o$  in the circuit of Fig. 2.26.

**Answer:** 12 V, 6 A.

*single-node KCL*

**HW:** also find the power absorbed by each element.

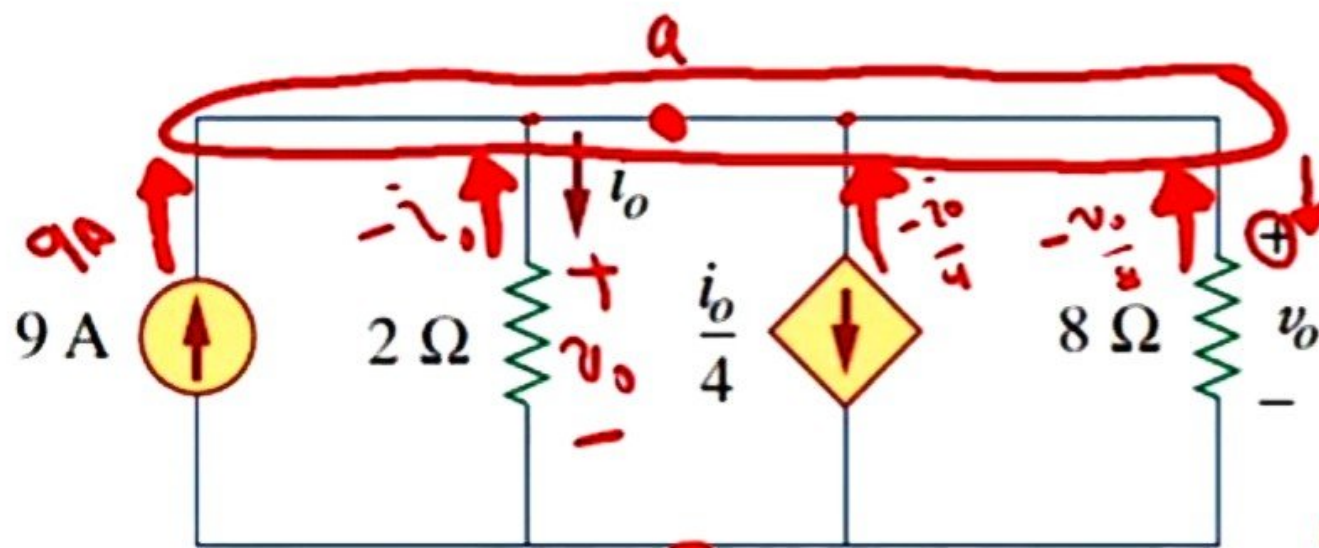

**Figure 2.26**

For Practice Prob. 2.7.

$9 - i_o - \frac{i_o}{4} - \frac{v_o}{8} = 0$

$v_o = 2i_o$

$-1.25i_o - \frac{2i_o}{8} = -9$

## Kirchhoff's current law (KCL).

- **Note**: In the last two examples are CKTs are called **single-node CKT**, in which all elements are in parallel and connected between two nodes.
- For such CKTs it is better to apply KCL.

- ❖ Ohm's law by itself is not sufficient to analyze circuits. However, when it is coupled with Kirchhoff's two laws, we have a sufficient, powerful set of tools for analyzing a large variety of electric circuits.
  
- ❖ Kirchhoff's laws were first introduced in 1847 by the German physicist Gustav Robert Kirchhoff (1824–1887).
  
- ❖ These laws are formally known as:
  - ✓ **Kirchhoff's current law (KCL).**
  - ✓ **Kirchhoff's voltage law (KVL)**

# Kirchhoff's voltage law (KVL).

□ **KVL:** the algebraic sum of all voltages around a closed path (or loop) is zero.


Mathematically:

$$\sum_{m=1}^M v_m = 0$$

where  $M$  is the number of voltages in the loop (or the number of branches in the loop) and  $v_m$  is the  $m$ th voltage.

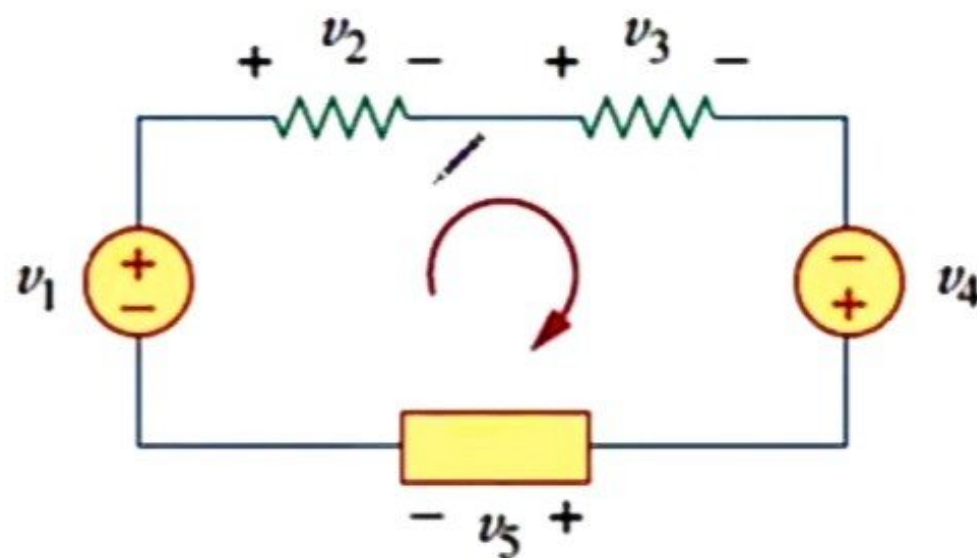
# Kirchhoff's voltage law (KVL).

□ **KVL:** the algebraic sum of all voltages around a closed path (or loop) is zero.



$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

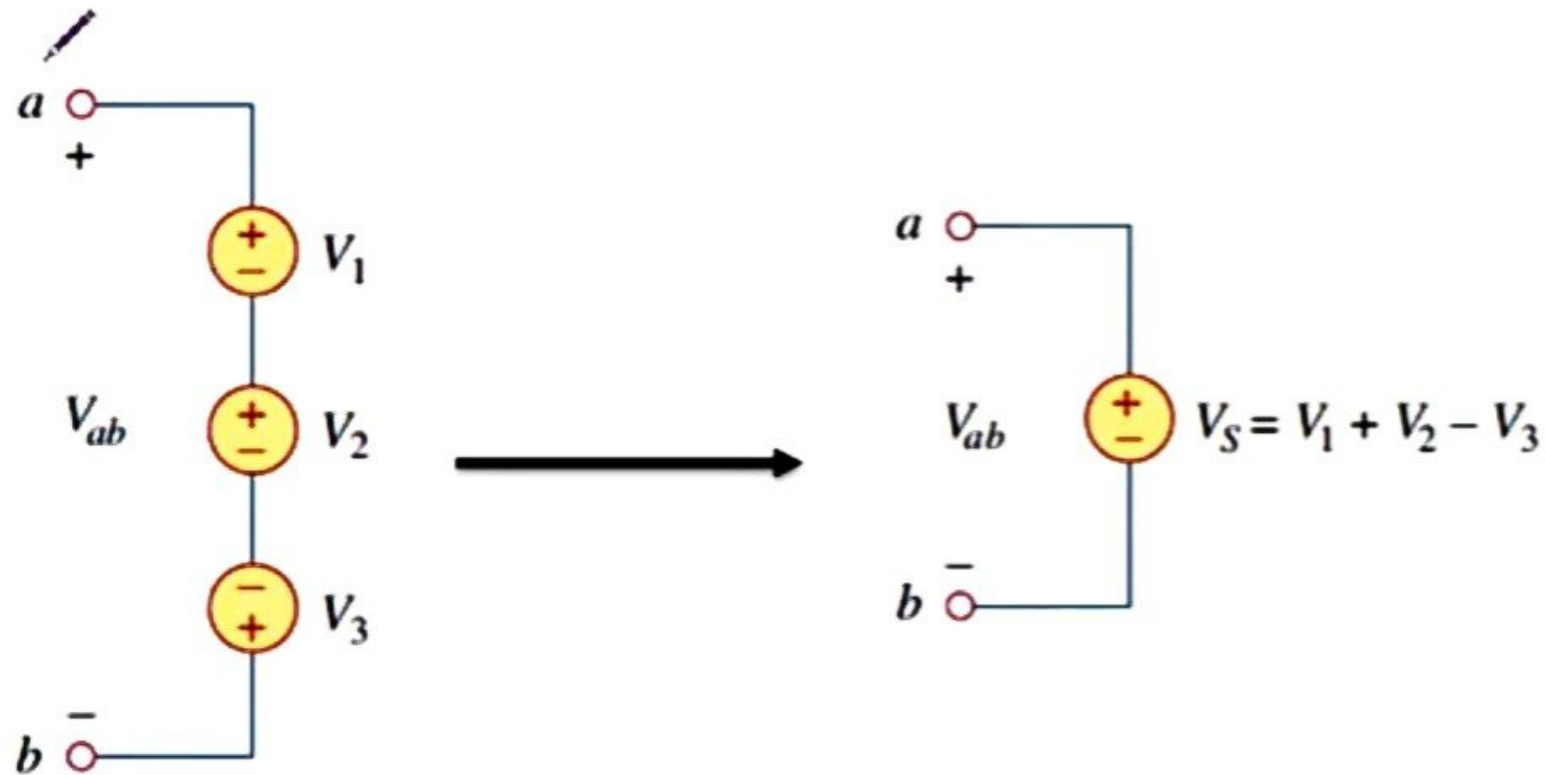
## Application on KVL: combining in series voltage sources.



Note: voltage sources in parallel should have same value.
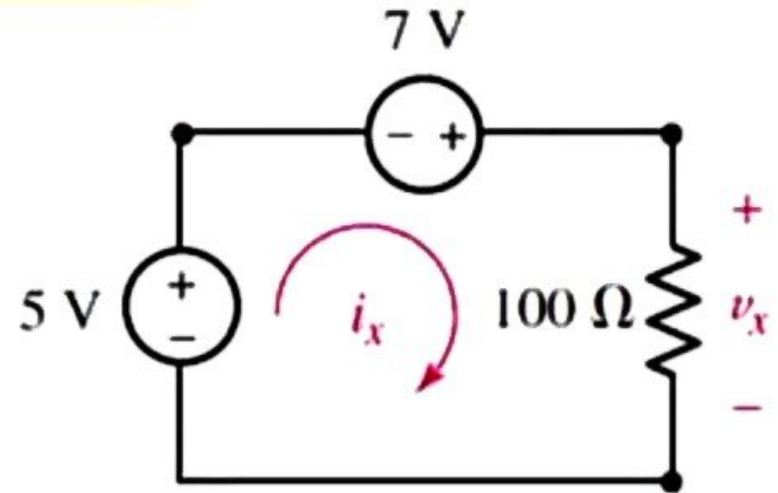
# Kirchhoff's voltage law (KVL).

In the circuit of Fig. 3.6, find  $v_x$  and  $i_x$ .




■ **FIGURE 3.6** A simple circuit with two voltage sources and a single resistor.

$$-12 + 4i + 2v_o - 4 + 6i = 0$$

$$v_o = -6i$$

$$i = -8 \text{ A}$$

$$v_o = 48 \text{ V.}$$

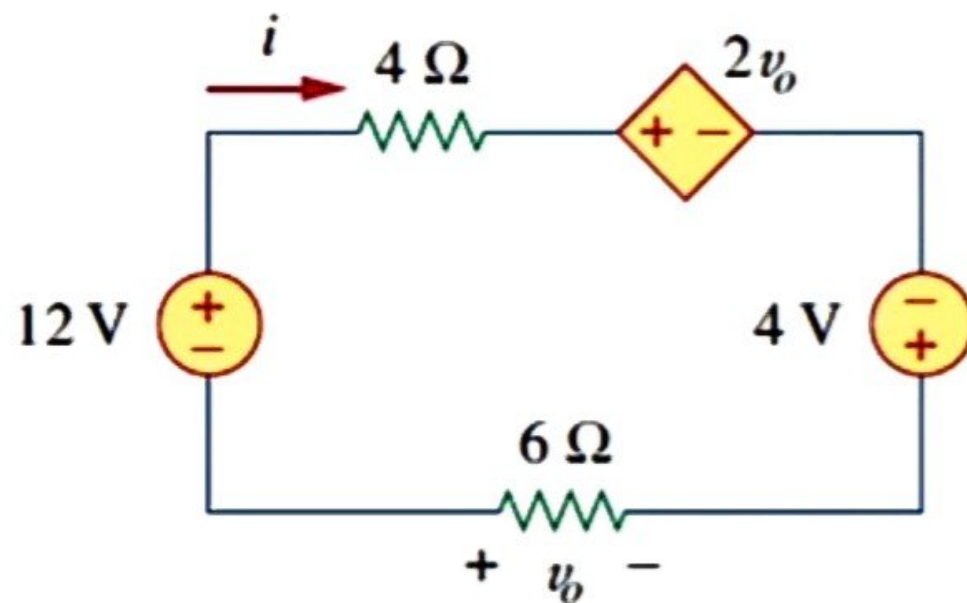

## **Kirchhoff's current law (KCL).**

- **Note: In the last two examples the CKTs are called single-Loop CKT, in which all elements are in series and carry same current.**
- **For such CKTs it is better to apply KVL.**


## Example 2.8

Find currents and voltages in the circuit shown

$$i_1 - i_2 - i_3 = 0$$


$$-30 + 8i_1 + 3i_2 = 0$$
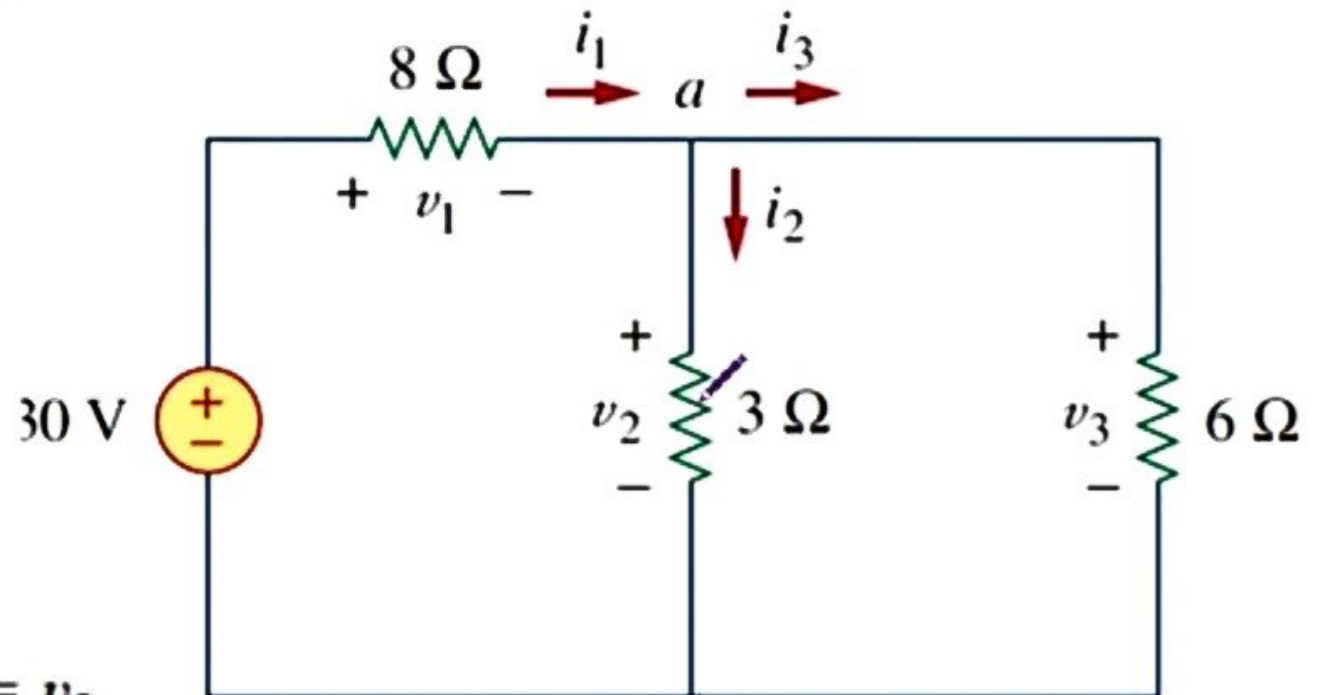
$$\begin{aligned} -v_2 + v_3 = 0 &\Rightarrow v_3 = v_2 \\ 6i_3 = 3i_2 & \end{aligned}$$



$$i_1 = 3 \text{ A}, \quad i_3 = 1 \text{ A}, \quad v_1 = 24 \text{ V}, \quad v_2 = 6 \text{ V}, \quad v_3 = 6 \text{ V}$$

In the circuit of Fig. 3.8 there are eight circuit elements. Find  $v_{R_2}$  (the voltage across  $R_2$ ) and the voltage labeled  $v_x$ .

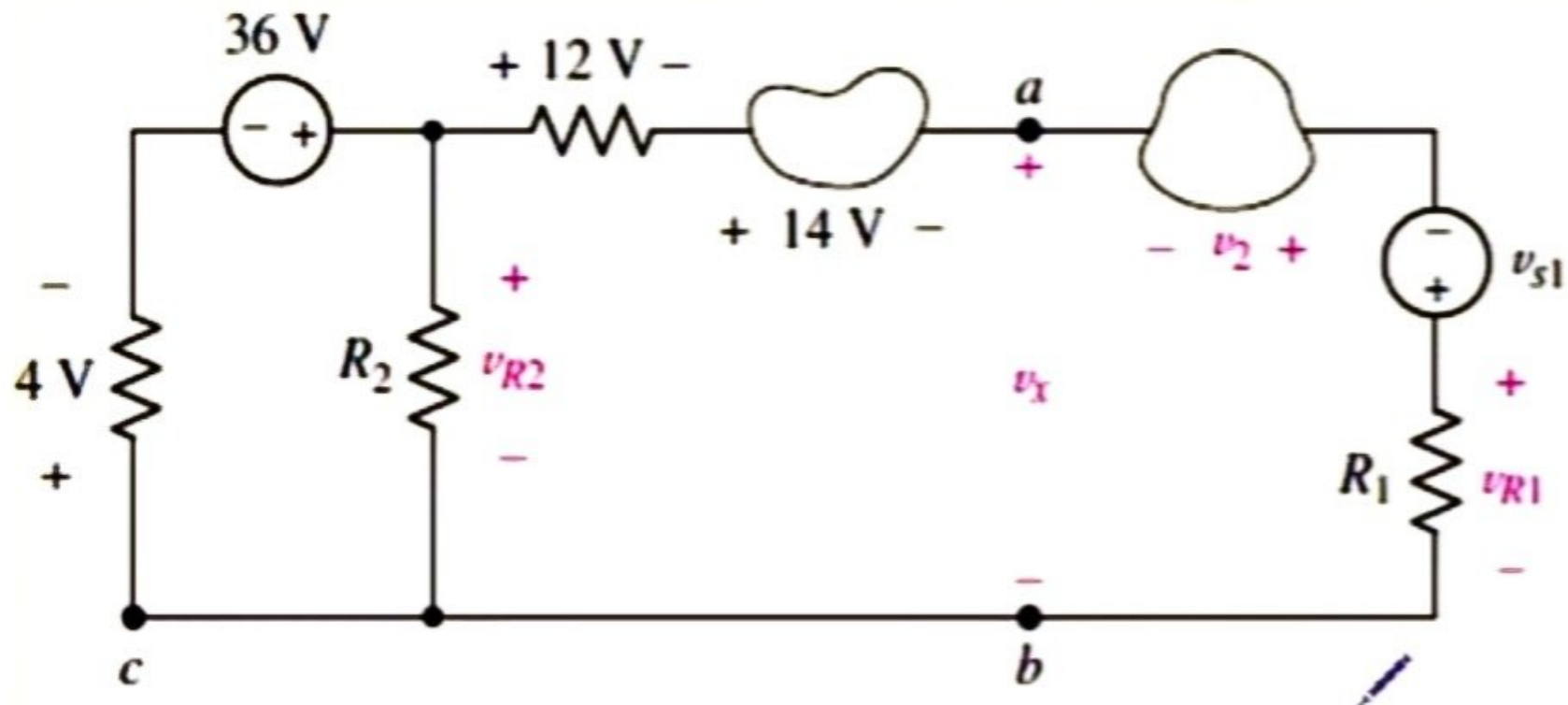


**FIGURE 3.8** A circuit with eight elements for which we desire  $v_{R_2}$  and  $v_x$ .

$$4 - 36 + v_{R_2} = 0 \quad v_{R_2} = 32 \text{ V.}$$

$$+4 - 36 + 12 + 14 + v_x = 0 \quad v_x = 6 \text{ V}$$

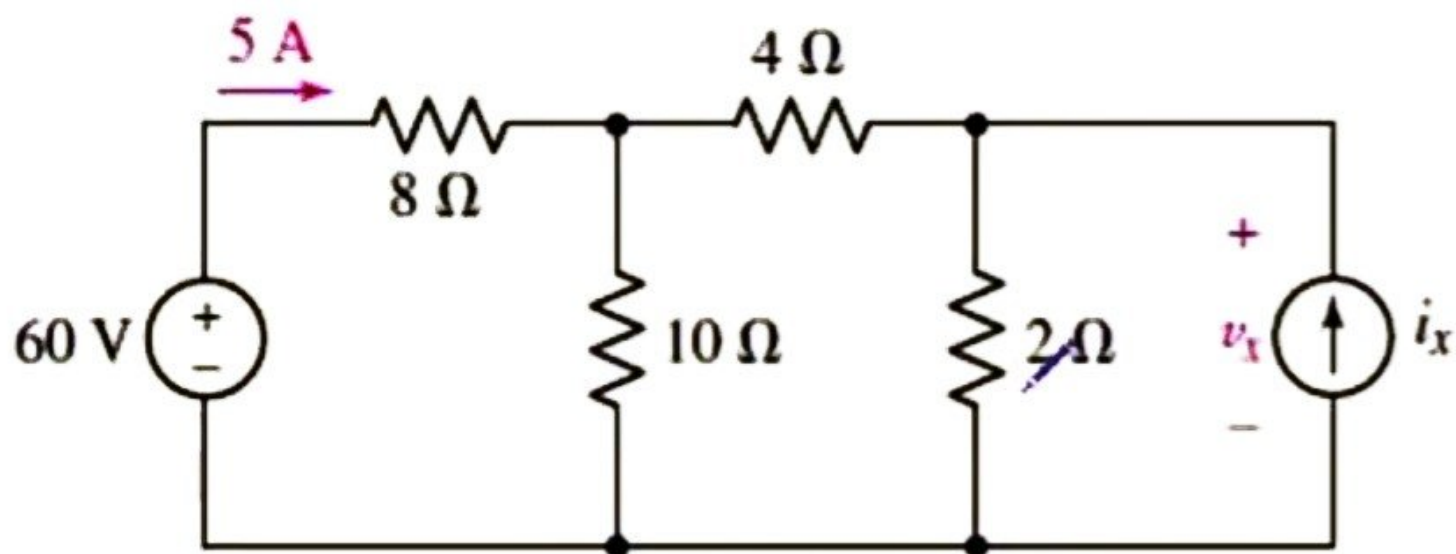**EXAMPLE 3.4**

Determine  $v_x$  in the circuit of Fig. 3.10a.



(a)

# Series Resistors & Voltage Division

$$v_1 = iR_1, \quad v_2 = iR_2$$

**KVL:**



$$-v + v_1 + v_2 = 0$$


$$v = v_1 + v_2 = i(R_1 + R_2)$$

$$i = \frac{v}{R_1 + R_2}$$

$$v = iR_{\text{eq}}$$

$$R_{\text{eq}} = R_1 + R_2$$

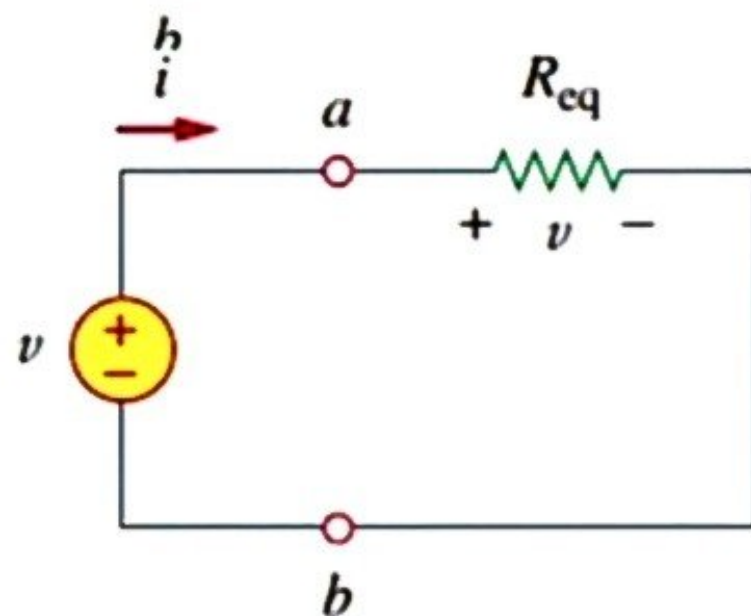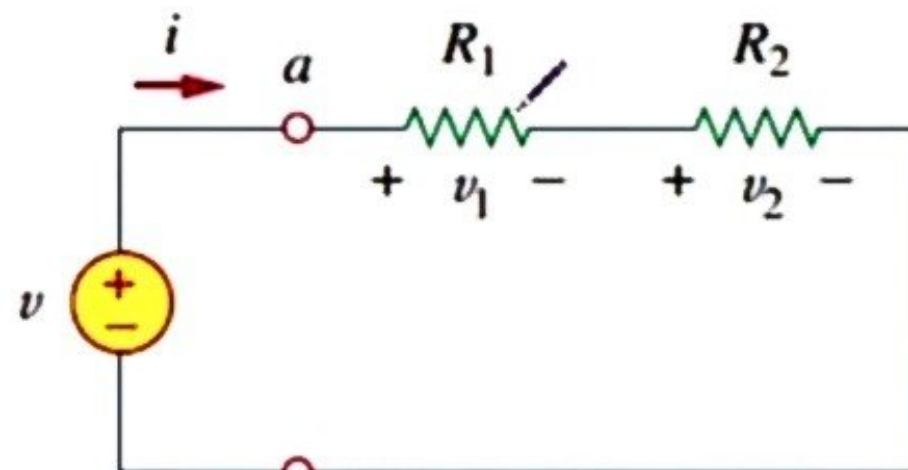

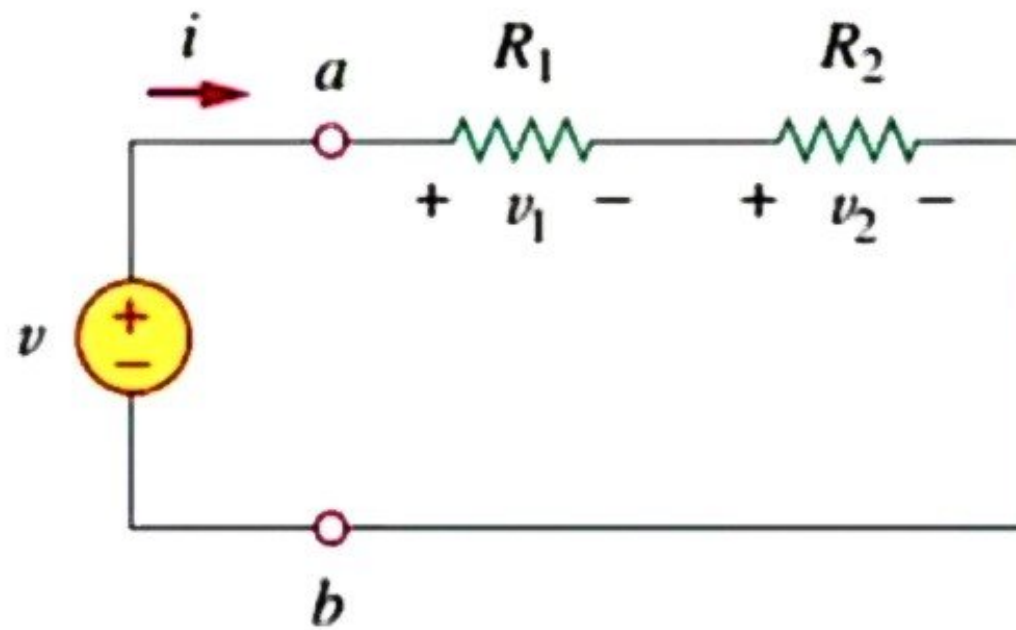

$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

## Rule:

The **equivalent resistance** of any number of resistors connected in series is the sum of the individual resistances.

For  $N$  resistors in series then,

$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

the  $n$ th resistor ( $R_n$ ) will have a voltage drop of

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

## & Current Division

□ Series resistors in terms of conductance:

$$\frac{1}{G_{\text{eq}}} = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3} + \dots + \frac{1}{G_N}$$

where  $G_{\text{eq}} = 1/R_{\text{eq}}$ ,  $G_1 = 1/R_1$ ,  $G_2 = 1/R_2$ ,  $G_3 = 1/R_3$ , ...,  $G_N = 1/R_N$ .

# Parallel Resistors & Current Division

Ohm's law,

$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$


KCL  $i = i_1 + i_2$

$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{\text{eq}}}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$


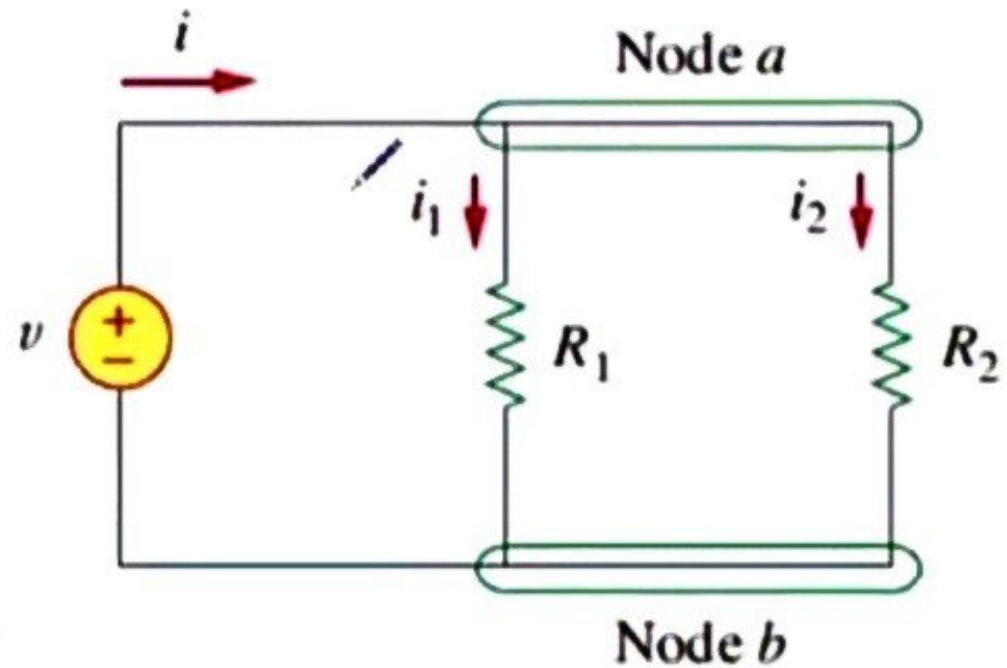
$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$



# & Current Division

The **equivalent resistance** of two parallel resistors is equal to the product of their resistances divided by their sum.

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

Note that  $R_{\text{eq}}$  is always smaller than the resistance of the smallest resistor in the parallel combination. If  $R_1 = R_2 = \dots = R_N = R$ , then

$$R_{\text{eq}} = \frac{R}{N}$$

# Parallel Resistors & Current Division

□ Parallel resistors in terms of conductance:


$$G_{\text{eq}} = G_1 + G_2 + G_3 + \dots + G_N$$

where  $G_{\text{eq}} = 1/R_{\text{eq}}$ ,  $G_1 = 1/R_1$ ,  $G_2 = 1/R_2$ ,  $G_3 = 1/R_3$ , ...,  $G_N = 1/R_N$ .


□ Current through the nth resistor:

$$G_n$$

- **Note:**

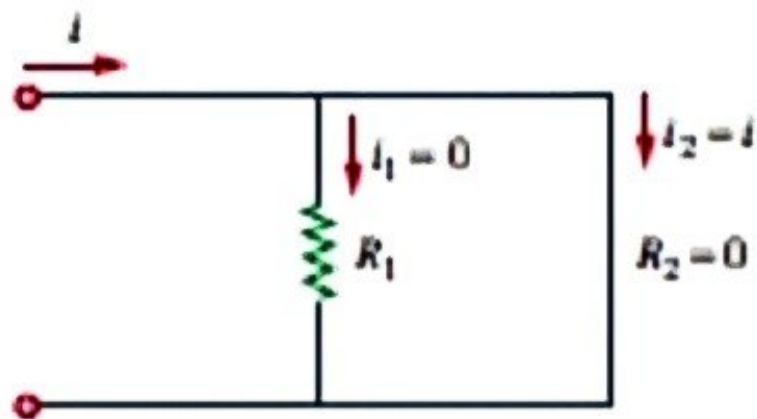

(a)

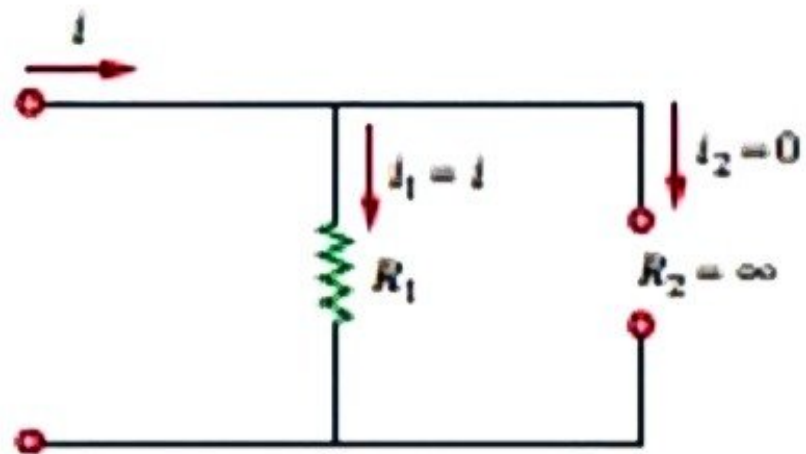

### Example 2.9

Find  $R_{\text{eq}}$  for the circuit shown in Fig. 2.34.


$$6\ \Omega \parallel 3\ \Omega = \frac{6 \times 3}{6 + 3} = 2\ \Omega$$

$$1\ \Omega + 5\ \Omega = 6\ \Omega$$

$$2\ \Omega + 2\ \Omega = 4\ \Omega$$

$$4\ \Omega \parallel 6\ \Omega = \frac{4 \times 6}{4 + 6} = 2.4\ \Omega$$

$$R_{\text{eq}} = 4\ \Omega + 2.4\ \Omega + 8\ \Omega = 14.4\ \Omega$$

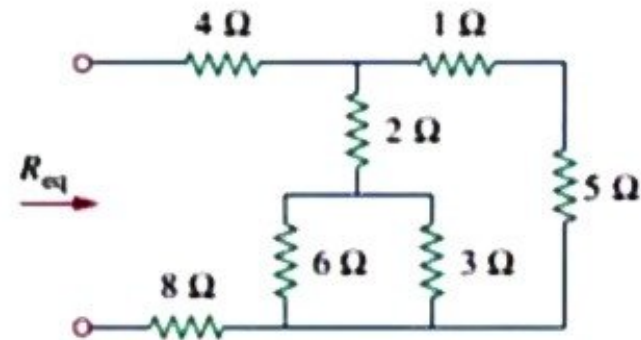

**Figure 2.34**  
For Example 2.9.

### Example 2.10

Calculate the equivalent resistance  $R_{ab}$  in the circuit


$$3\ \Omega \parallel 6\ \Omega = \frac{3 \times 6}{3 + 6} = 2\ \Omega$$

$$12\ \Omega \parallel 4\ \Omega = \frac{12 \times 4}{12 + 4} = 3\ \Omega$$

$$1\ \Omega + 5\ \Omega = 6\ \Omega$$

$$2\ \Omega \parallel 3\ \Omega = \frac{2 \times 3}{2 + 3} = 1.2\ \Omega$$

$$R_{ab} = 10 + 1.2 = 11.2\ \Omega$$

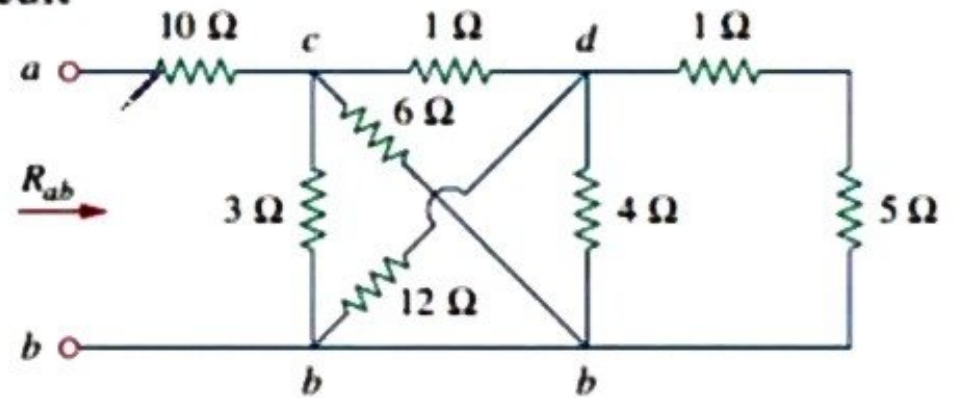


### Example 2.11

Find the equivalent conductance  $G_{eq}$

$$8\text{ S} + 12\text{ S} = 20\text{ S}$$


$$\frac{20 \times 5}{20 + 5} = 4\text{ S}$$

$$G_{eq} = 6 + 4 = 10\text{ S}$$

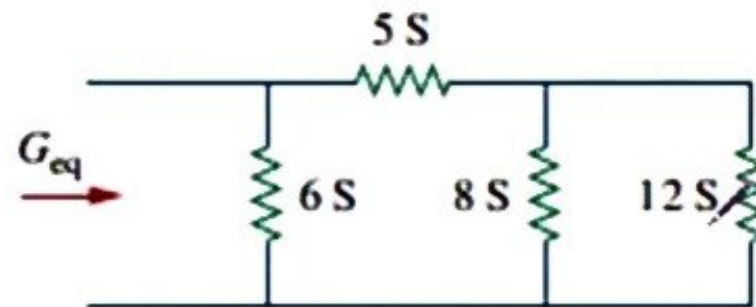
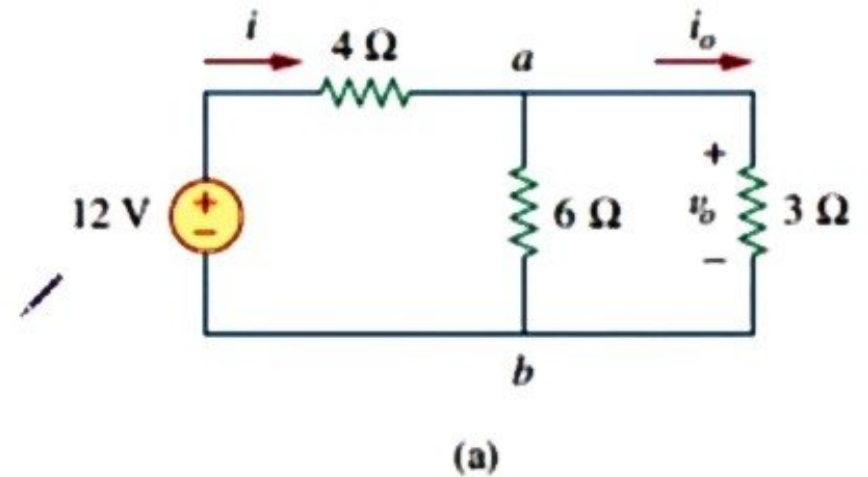
### Example 2.12

Find  $i_o$  and  $v_o$  in the circuit shown in Fig. 2.42(a). Calculate the power dissipated in the 3- $\Omega$  resistor.




$$v_o = 4 \text{ V}$$

$$i_o = \frac{4}{3} \text{ A}$$

$$p_o = 5.333 \text{ W}$$


Practice Problem 2.12

Find  $v_1$  and  $v_2$  in the circuit shown in Fig. 2.43. Also calculate  $i_1$  and  $i_2$  and the power dissipated in the 12- $\Omega$  and 40- $\Omega$  resistors.

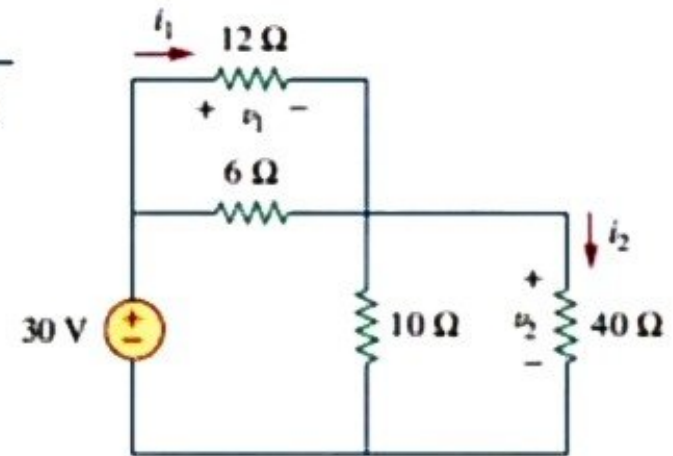

**Figure 2.43**  
For Practice Prob. 2.12.

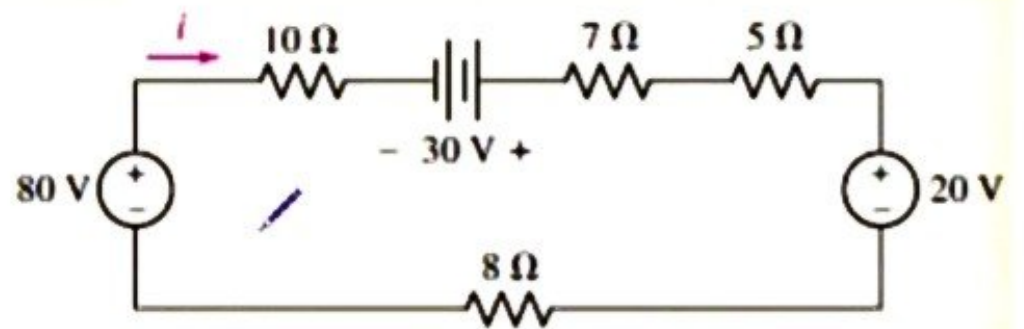
Use resistance and source combinations to determine the current  $i$



# Series & Parallel Resistors. Voltage & Current Divisions

Calculate the power and voltage of the dependent source

Single-Node  
CKT

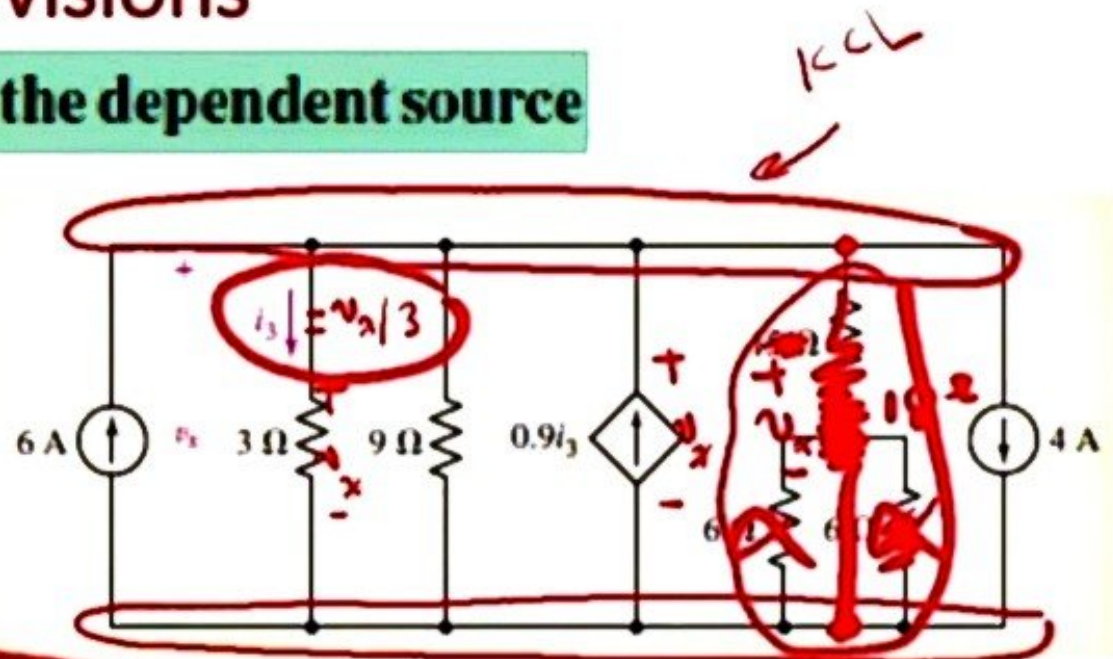


KCL:

$$-0.9i_3 - 2 + i_3 + \frac{10}{6} = 0$$

$$v = 3i_3$$

$$i_3 = \frac{10}{3} \text{ A}$$

$$v = 3i_3 = 10 \text{ V}$$

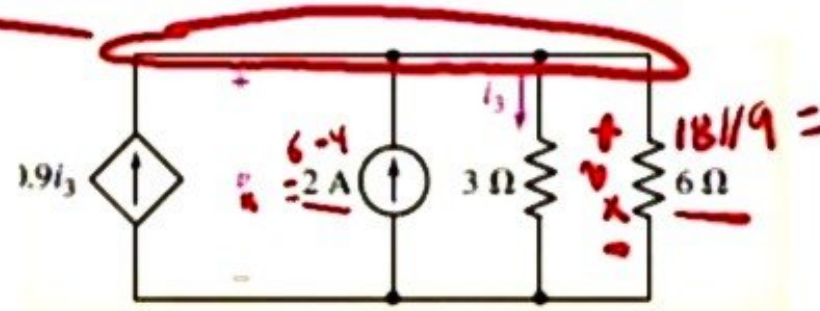

The Y and  $\Delta$  networks are said to be *balanced* when


$$R_1 = R_2 = R_3 = R_Y, \quad R_a = R_b = R_c = R_\Delta$$

Under these conditions, conversion formulas become

$$R_Y = \frac{R_\Delta}{3} \quad \text{or} \quad R_\Delta = 3R_Y$$

### Example 2.14

Convert the  $\Delta$  network in Fig. 2.50(a) to an equivalent Y network.

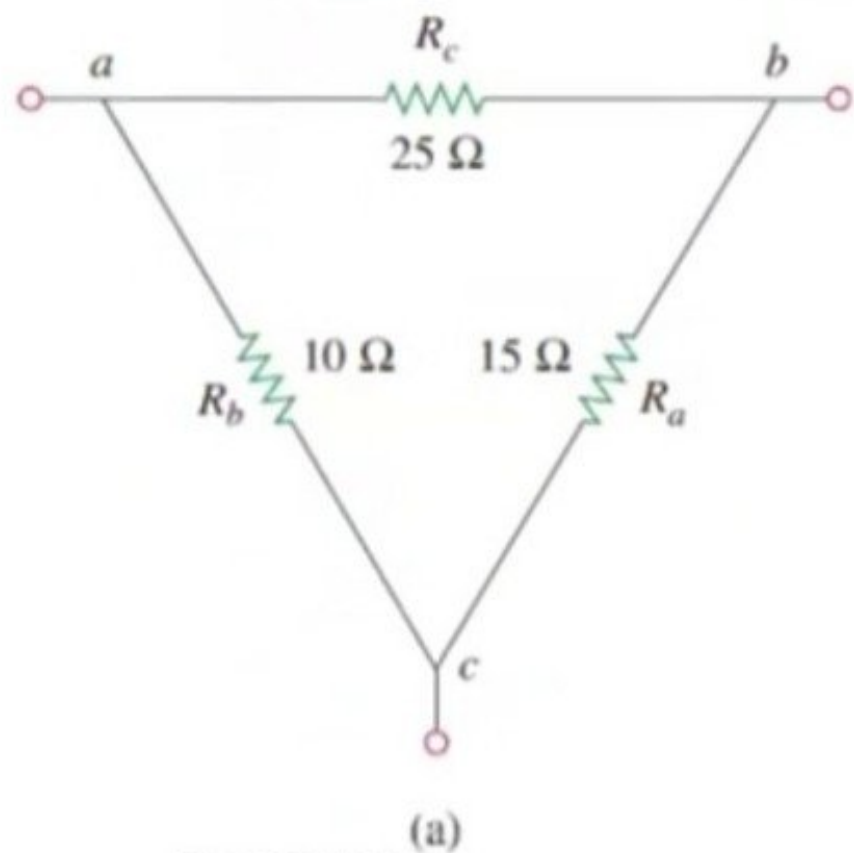

Summer 2019

Dr. Yazid Khattabi. Electric Circuits (1). The University of Jordan.


**Solution:**

Using Eqs. (2.49) to (2.51), we obtain

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{10 \times 25}{15 + 10 + 25} = \frac{250}{50} = 5 \Omega$$


$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{25 \times 15}{50} = 7.5 \Omega$$
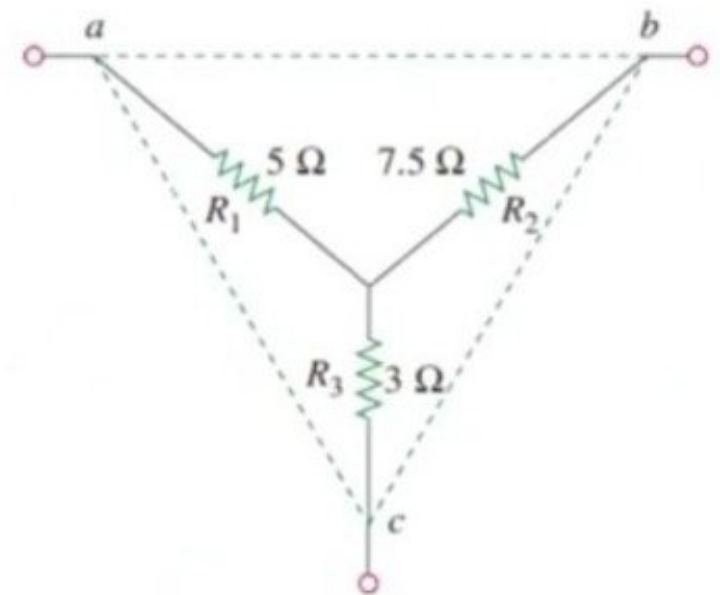
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{15 \times 10}{50} = 3 \Omega$$


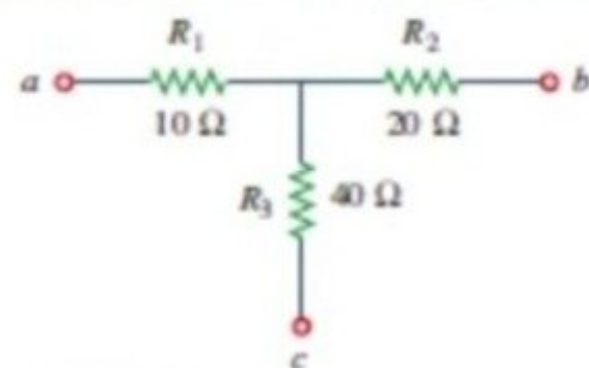
### Practice Problem 2.14

Transform the wye network in Fig. 2.51 to a delta network.




**Answer:**  $R_a = 140\ \Omega$ ,  $R_b = 70\ \Omega$ ,  $R_c = 35\ \Omega$ .

**Figure 2.51**

For Practice Prob. 2.14.



### Example 2.15

Obtain the equivalent resistance  $R_{ab}$  for the circuit in Fig. 2.52 and use it to find current  $i$ .

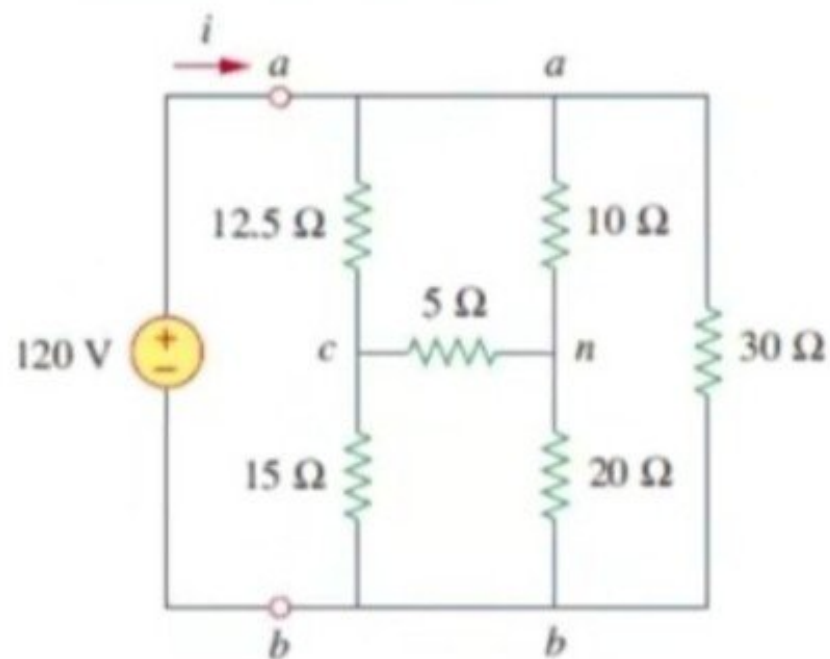

**Figure 2.52**  
For Example 2.15.

• Solution:

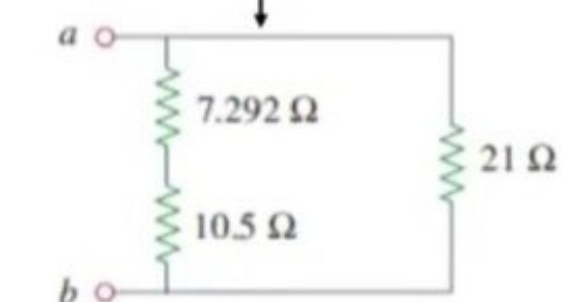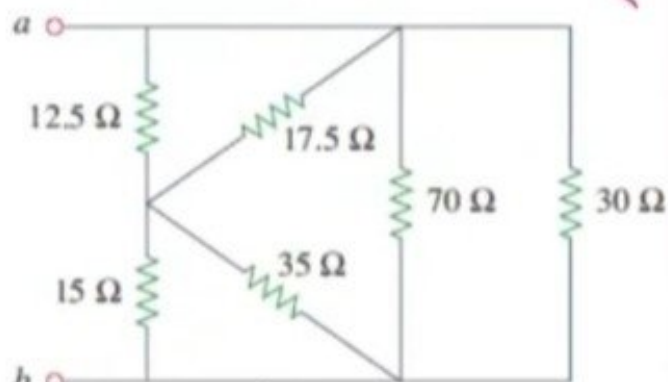

$$R_1 = 10 \Omega, \quad R_2 = 20 \Omega, \quad R_3 = 5 \Omega$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10}$$

$$= \frac{350}{10} = 35 \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{350}{20} = 17.5 \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{350}{5} = 70 \Omega$$

$$70 \parallel 30 = \frac{70 \times 30}{70 + 30} = 21 \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 \times 17.5}{12.5 + 17.5} = 7.292 \Omega$$

$$15 \parallel 35 = \frac{15 \times 35}{15 + 35} = 10.5 \Omega$$

$$R_{ab} = (7.292 + 10.5) \parallel 21 = \frac{17.792 \times 21}{17.792 + 21} = 9.632 \Omega$$

$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = 12.458 \text{ A}$$