

Chapter 6: Capacitors and Inductors

Lecture#1

Reference:



Fundamentals of
Electric Circuits



Charles K. Alexander | Matthew N. O. Sadiku

- ❑ Two new linear (passive) circuit elements will be introduced:
 - ✓ The capacitor.
 - ✓ The inductor.
- ❑ They do not dissipate energy, but instead, they store energy.
- ❑ Called storage elements.
- ❑ Practical circuit applications are composed of resistors, capacitors and inductors.

Capacitors

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

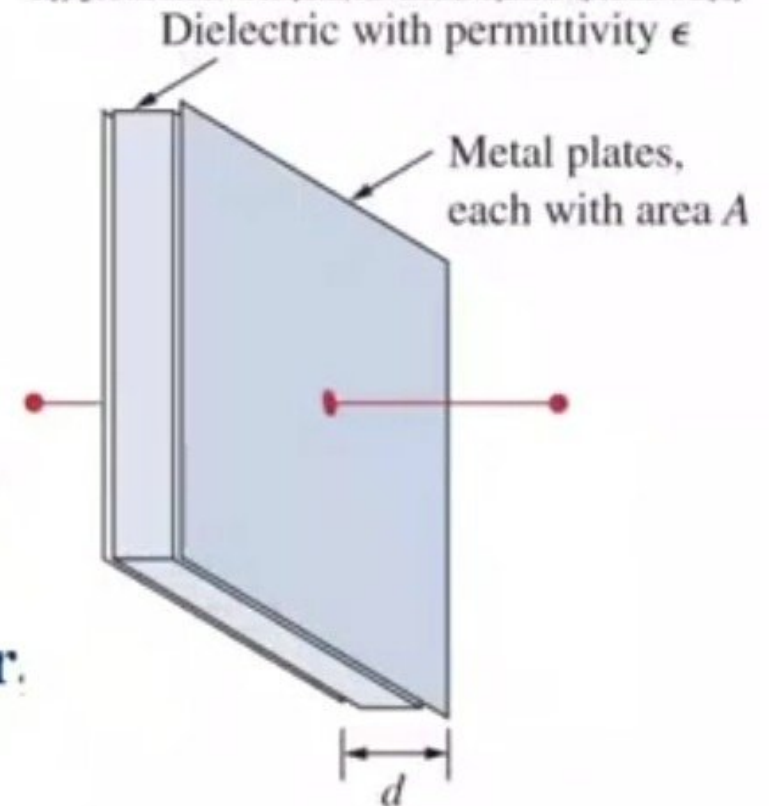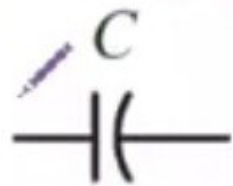- ❑ It is a passive element.
- ❑ It stores energy in its electric field.
- ❑ It consists of two conducting plates separated by an insulator (or dielectric).
- ❑ The plates are typically aluminum foil.
- ❑ The dielectric is often air, ceramic, paper, plastic, or mica.
- ❑ Each capacitor has a capacitance C measured in Farads (F).
- ❑ The symbol:




Capacitors

- ❑ **1 F = 1 Coulomb/Volt.**
- ❑ **Most capacitors are rated in pF and μF .**
- ❑ **Capacitance is determined by the *geometry* of the capacitor:**
 - ✓ **Proportional to the area of the plates (A).**
 - ✓ **Inversely proportional to the space between them (d).**

$$C = \frac{\epsilon A}{d}$$

where ϵ is the permittivity of the dielectric.

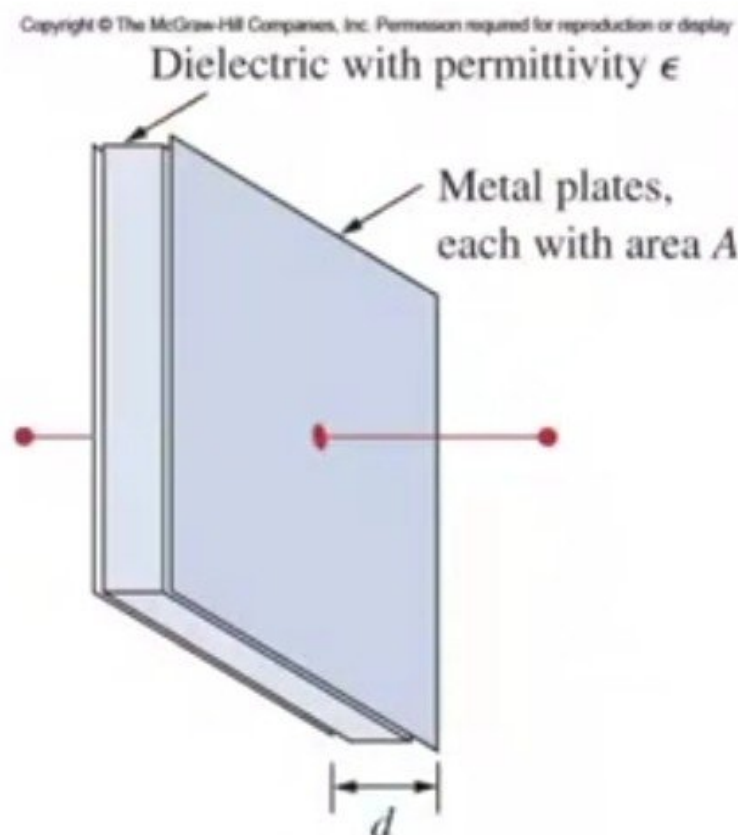- **Note**: more details will be covered in EM courses.




Capacitors

□ A capacitor stores charges (energy) on its plates! How??

- When a voltage source v is connected to the capacitor, the source deposits a positive charge q on one plate and a negative charge $-q$ on the other (these charges will be equal in magnitude).
- The amount of stored charge is proportional to the voltage:

$$q = Cv$$

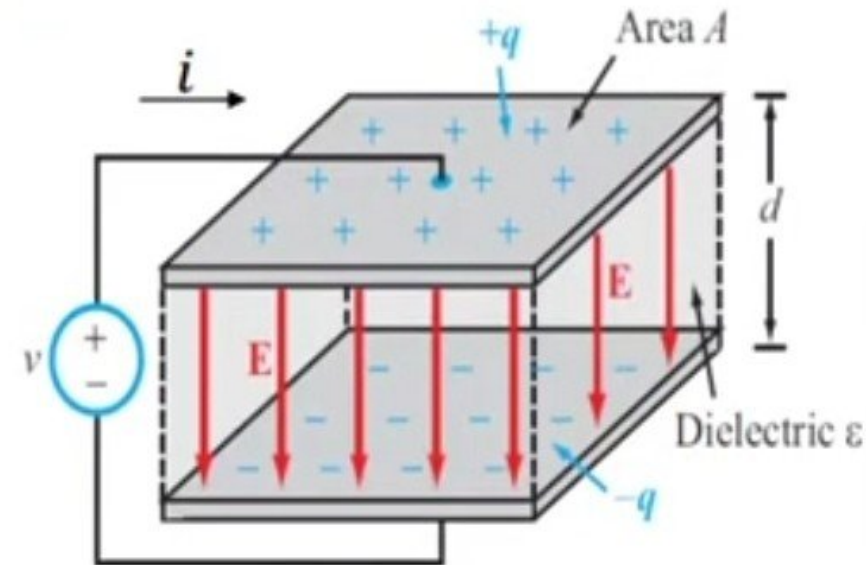

▪ In general $q = q(t)$ and $v = v(t)$, and $i = i(t)$.

▪ **Note:** if $v = V$ (DC), then $q = Q$ and $i = 0$, i.e., the capacitor = O.C (see later!)

Note: The value of C does not depend on v or q .

Capacitors

❑ For capacitor Types, shapes, and applications see the textbook!



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)



(b)

Courtesy of TechAmerica



(c)

Capacitor Current-Voltage Relationship



- By taking the first derivative of

$$q(t) = Cv(t)$$

with respect to time t , we can have:



$$i = C \frac{dv}{dt}$$

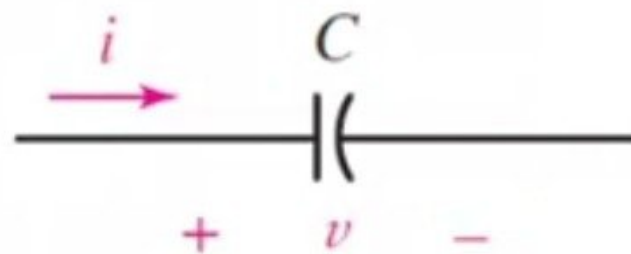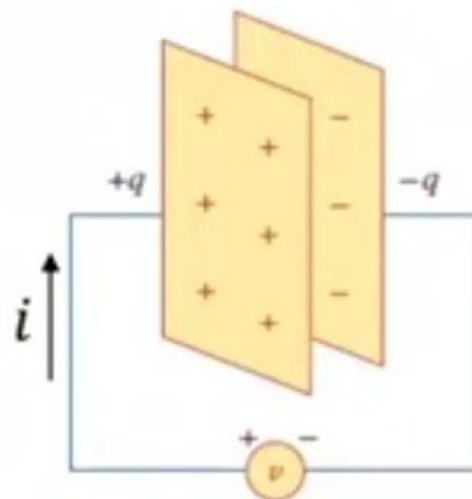- Note:** this assumes the passive sign convention.



Note: if $vi > 0$ → the capacitor is charging.
if $vi < 0$ → the capacitor is discharging

- If $v = V$ (DC), then $i = C \frac{dv}{dt} = 0$.
- Also $q = Q$ (constant stored charge).
- This means that with DC voltage applied to the terminals no current will flow, i.e., the capacitor is open circuit (o.c).
- However, the voltage on the capacitor's plates can't change instantaneously.
- The capacitor's voltage is continuous function of t
- An abrupt (sudden) change in voltage would require an infinite current (see the equation)!

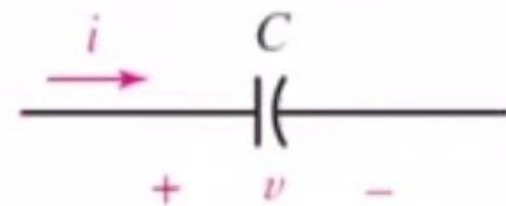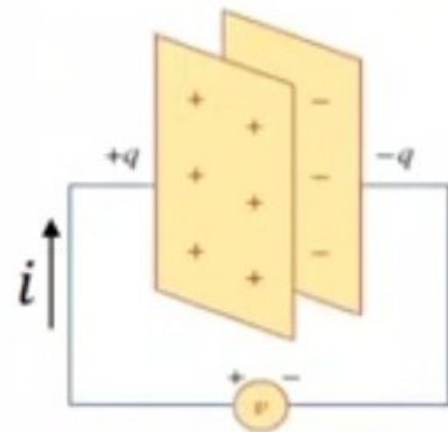

Capacitor Current-Voltage Relationship

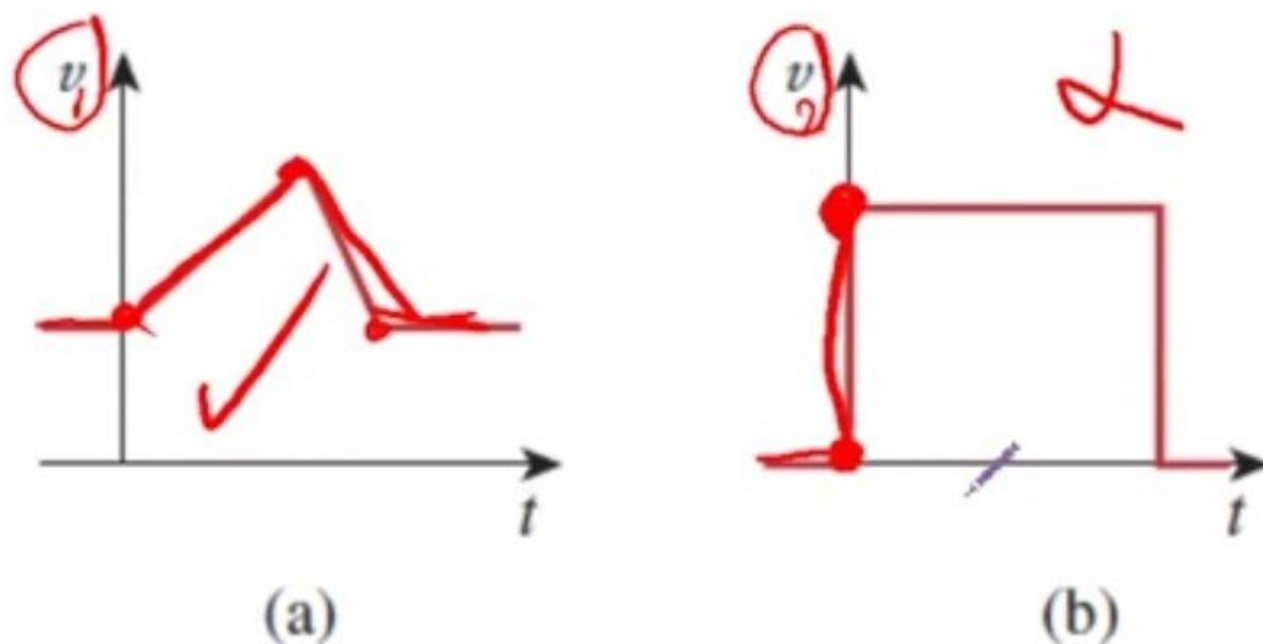


Figure 6.7

Voltage across a capacitor: (a) allowed, (b) not allowable; an abrupt change is not possible.

Capacitor Current-Voltage Relationship

- The cap's voltage can be obtained from the current by:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

where $v(t_0)$ is the cap's voltage at the initial time t_0 . It can be obtained from the initial stored charge by $v(t_0) = \frac{q(t_0)}{C}$.

- **Proof:**

$$dv = \frac{1}{C} i(t) dt$$

and then integrate² between the times t_0 and t and between the corresponding voltages $v(t_0)$ and $v(t)$:

- **Note:** this shows the capacitor has a memory, which is often exploited in circuits.

Energy Stored in the Capacitor

- The energy stored in the capacitor is computed by:

$$w = \frac{1}{2} C v^2 \quad \xrightarrow{\text{Or}} \quad w = \frac{q^2}{2C}$$

- Proof:**


The instantaneous power delivered to the capacitor is

$$p = v i = C v \frac{dv}{dt}$$

The energy stored in the capacitor is therefore

$$w = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v \frac{dv}{d\tau} d\tau = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}$$

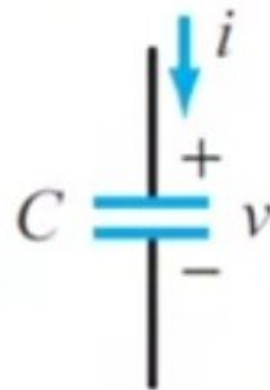We note that $v(-\infty) = 0$, because the capacitor was uncharged at $t = -\infty$. Thus,



Capacitors

Example 6.1



- (a) Calculate the charge stored on a 3-pF capacitor with 20 V across it.
- (b) Find the energy stored in the capacitor.

Solution:

- (a) Since $q = Cv$,

$$q = 3 \times 10^{-12} \times 20 = 60 \text{ pC}$$

- (b) The energy stored is

$$w = \frac{1}{2}Cv^2 = \frac{1}{2} \times 3 \times 10^{-12} \times 400 = 600 \text{ pJ}$$

What is the

Capacitors

Example 6.2

The voltage across a $5\text{-}\mu\text{F}$ capacitor is

$$v(t) = 10 \cos 6000t \text{ V}$$

Calculate the current through it.

Solution:


By definition, the current is

$$\begin{aligned} i(t) &= C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt}(10 \cos 6000t) \\ &= -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t = -0.3 \sin 6000t \text{ A} \end{aligned}$$

Capacitors

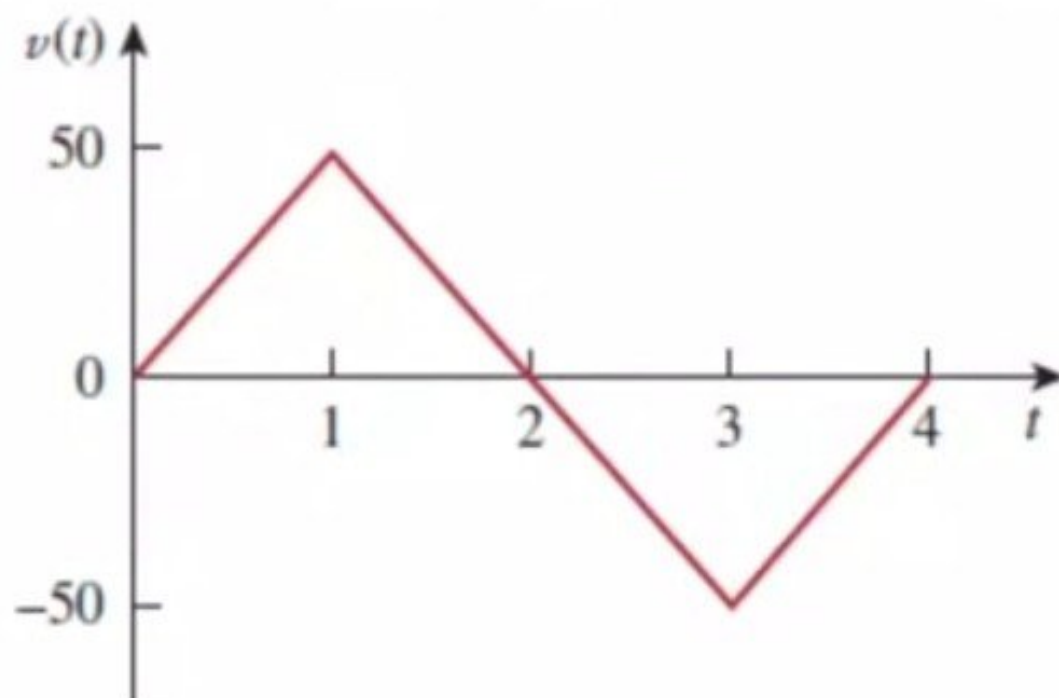Example 6.4

Determine the current through a $200\text{-}\mu\text{F}$ capacitor whose voltage is




Capacitors

Example 6.4

Solution:

$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} \quad C = 200 \mu\text{F}$$

$$i = C \frac{dv}{dt} = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} = \begin{cases} 10 \text{ mA} & 0 < t < 1 \\ -10 \text{ mA} & 1 < t < 3 \\ 10 \text{ mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

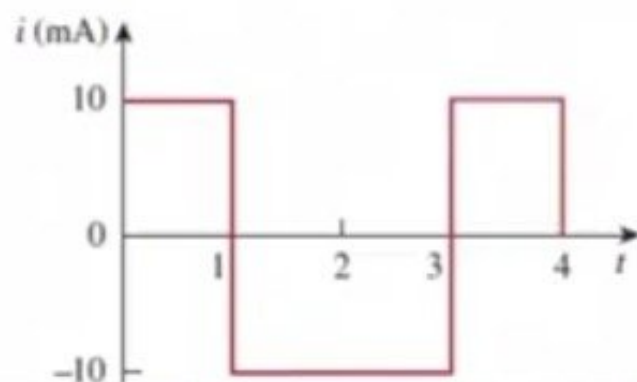

Example 6.3

Determine the voltage across a $2\text{-}\mu\text{F}$ capacitor if the current through it is

$$i(t) = 6e^{-3000t} \text{ mA}$$

Assume that the initial capacitor voltage is zero.

Solution:

Since $v = \frac{1}{C} \int_0^t i dt + v(0)$ and $v(0) = 0$,

$$\begin{aligned} v &= \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000t} dt \cdot 10^{-3} \\ &= \frac{3 \times 10^3}{-3000} e^{-3000t} \Big|_0^t = (1 - e^{-3000t}) \text{ V} \end{aligned}$$

Capacitors

Practice Problem 6.4


An initially uncharged 1-mF capacitor has the current shown

Find $v(t)$, $v(2\text{ms})$, $v(5\text{ms})$

Solution:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$
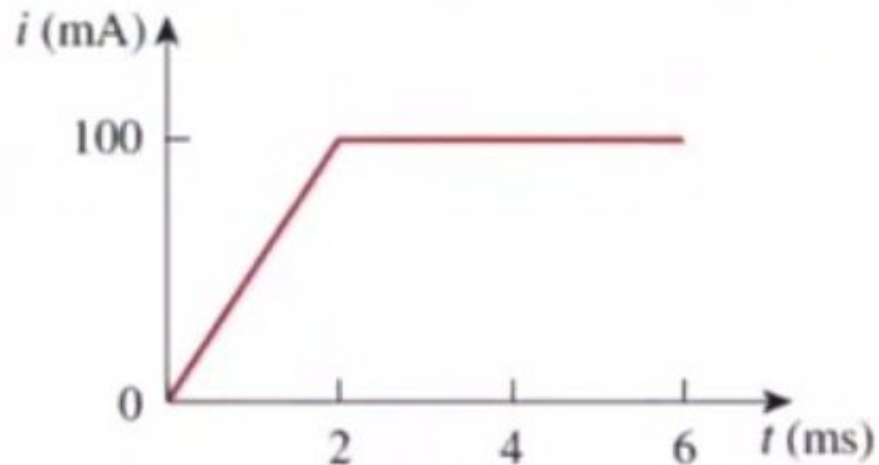
$$i(\tau) = \begin{cases} 5\tau, & 0 < \tau < 2 \text{ ms} \\ 100 \text{ mA}, & \tau > 2 \text{ ms} \end{cases}$$



Case: $0 < t < 2 \text{ ms}$:

$$v(t) = 1000 \int_0^{t \text{ (ms)}} 50\tau d\tau + v(0) = 25000t^2 \text{ V}; \quad (t \text{ in ms})$$


Case: $2 \text{ ms} < t$:

$$v(t) = 1000 \int_{2 \text{ ms}}^{t \text{ (ms)}} 100 \text{ mA} d\tau + v(2 \text{ ms}) = 100(t - 0.002) + 0.1 \text{ V}, \quad (t \text{ in ms})$$

Capacitors

HW:

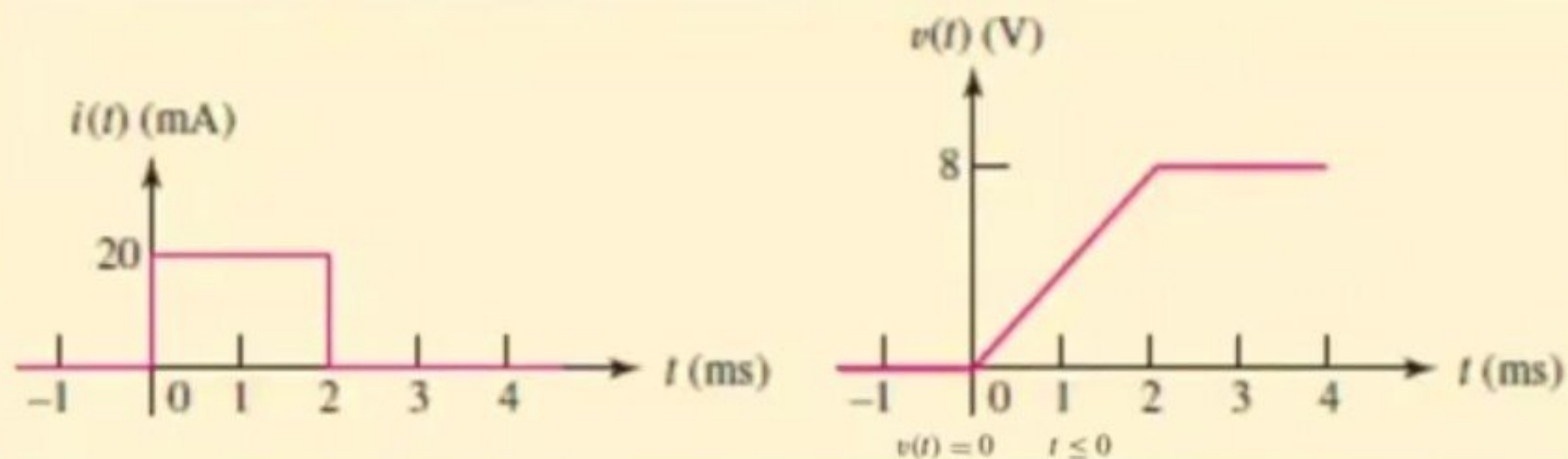Find the capacitor voltage that is associated with the current shown graphically in Fig. 7.5a. The value of the capacitance is $5 \mu\text{F}$.




$$v(t) = 4000t \quad 0 \leq t \leq 2 \text{ ms}$$

$$v(t) = 8 \quad t \geq 2 \text{ ms}$$

Capacitors

Example 6.5 Obtain the energy stored in each capacitor

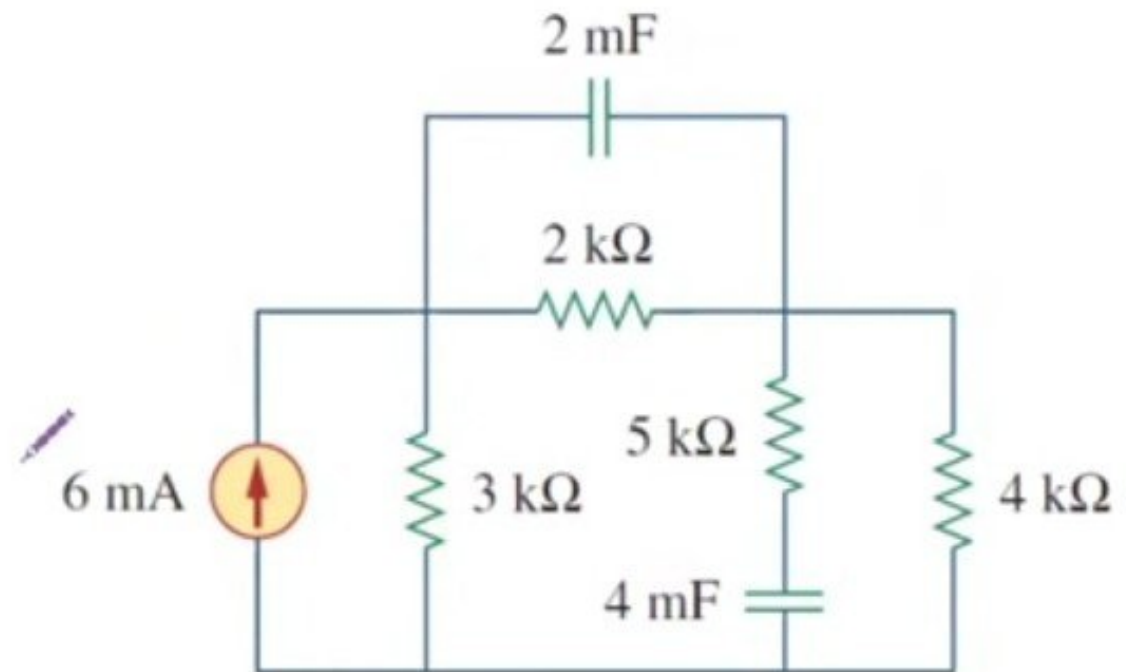

Example 6.5 Solution:


Under dc conditions, we replace each capacitor with an open circuit,

$$i = \frac{3}{3 + 2 + 4}(6 \text{ mA}) = 2 \text{ mA}$$

$$v_1 = 2000i = 4 \text{ V} \quad v_2 = 4000i = 8 \text{ V}$$



$$w_1 = \frac{1}{2}C_1v_1^2 = \frac{1}{2}(2 \times 10^{-3})(4)^2 = 16 \text{ mJ}$$
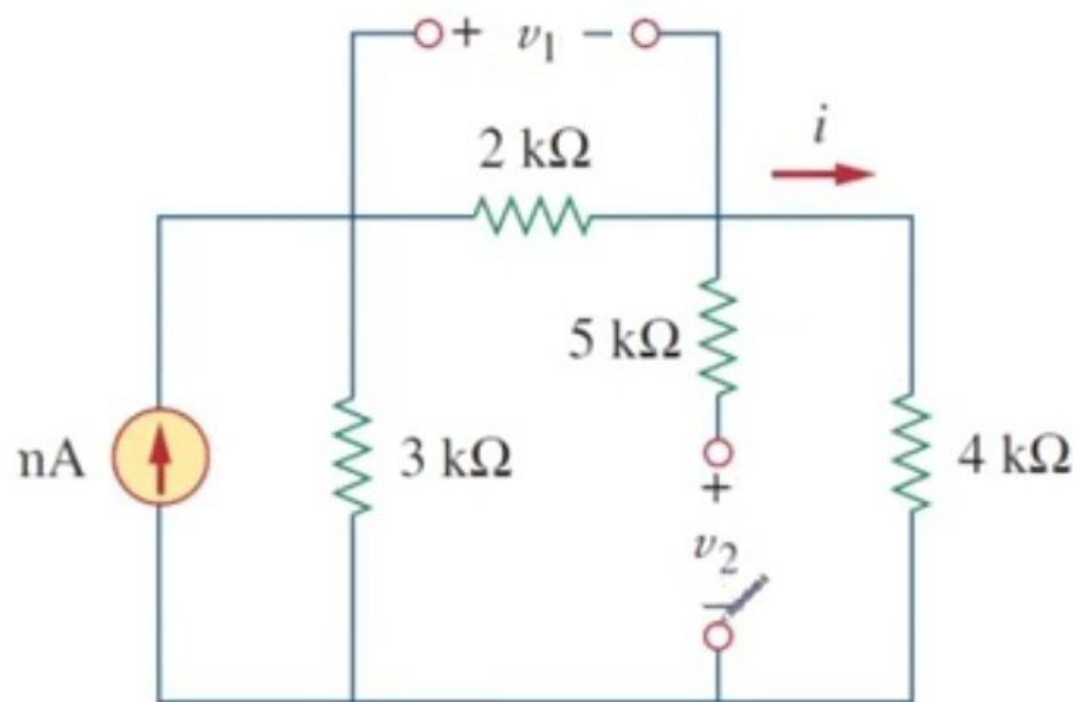
$$w_2 = \frac{1}{2}C_2v_2^2 = \frac{1}{2}(4 \times 10^{-3})(8)^2 = 128 \text{ mJ}$$





Capacitor Response: Given $v(t)$, determine $i(t)$, $p(t)$, and $w(t)$

$C = 0.6\text{-}\mu\text{F}$
 v (V)

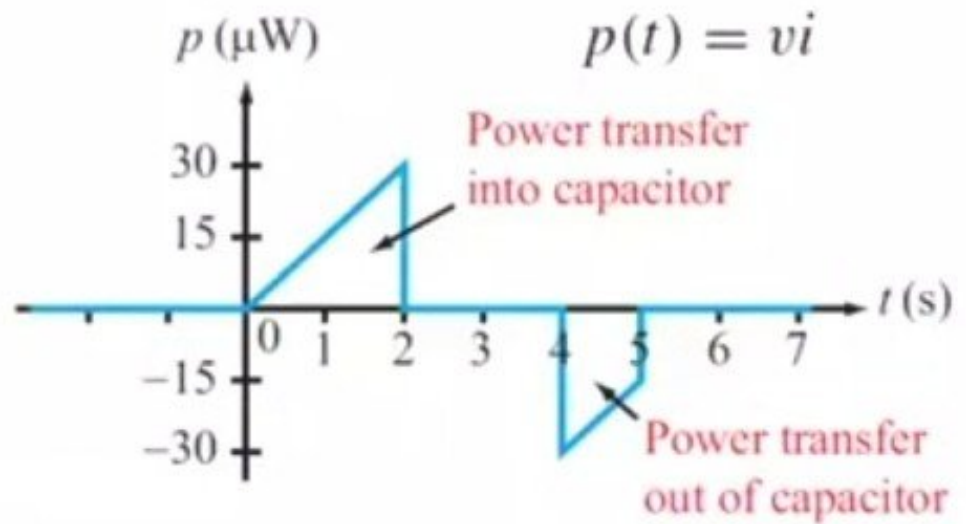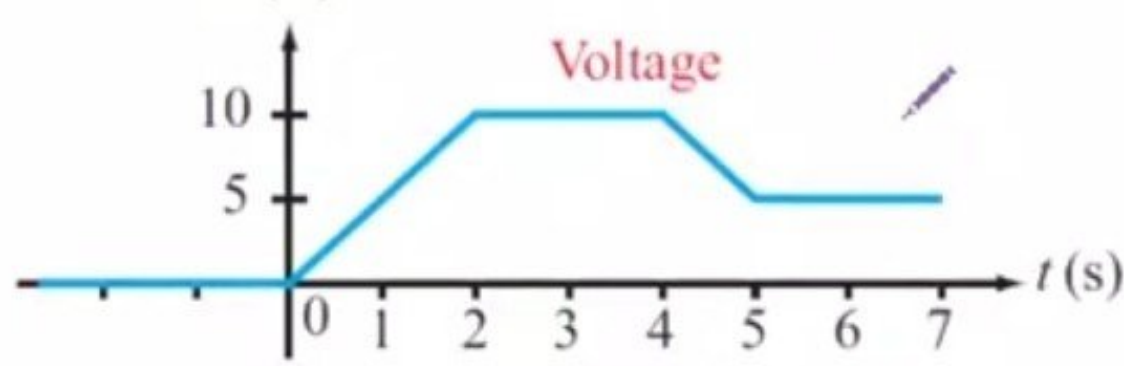

i (μA)
 $i(t) = C \frac{dv}{dt}$

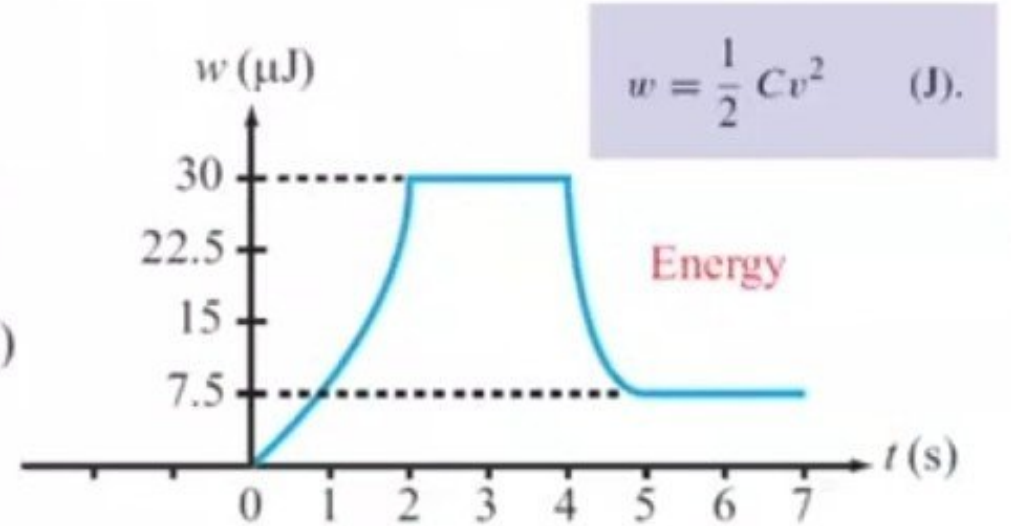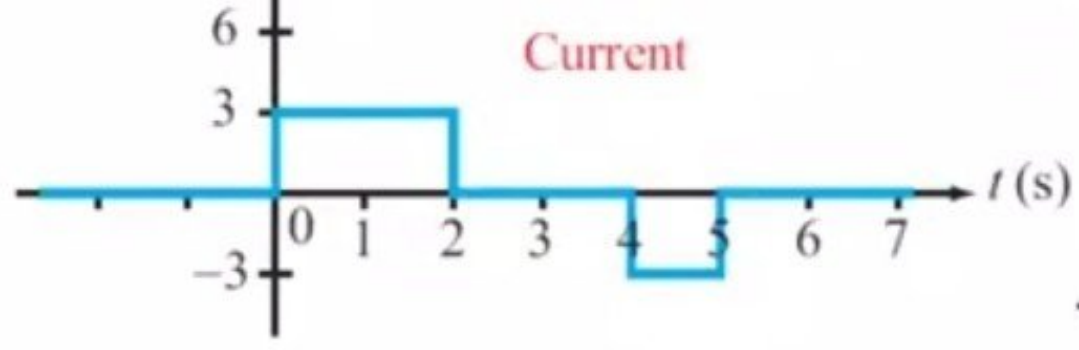

Capacitors



□ Capacitors in parallel:

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

Proof:

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

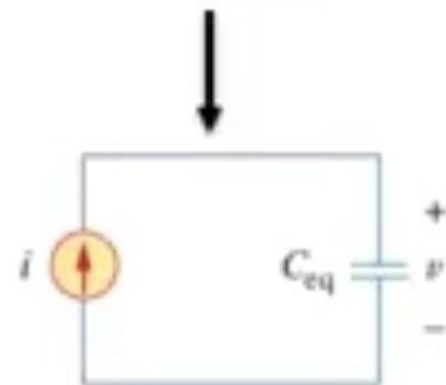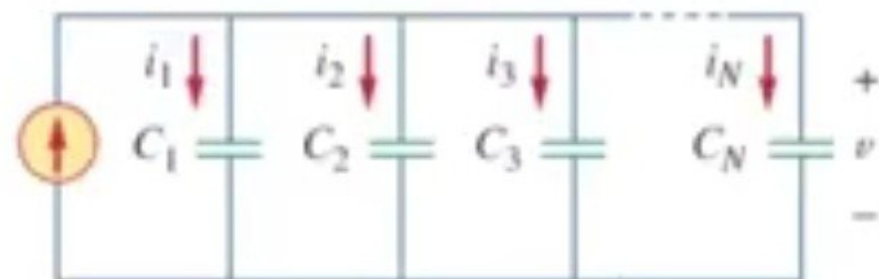
$$\begin{aligned} \rightarrow i &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt} \\ &= \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt} \end{aligned}$$



Capacitors


□ Capacitors in series:
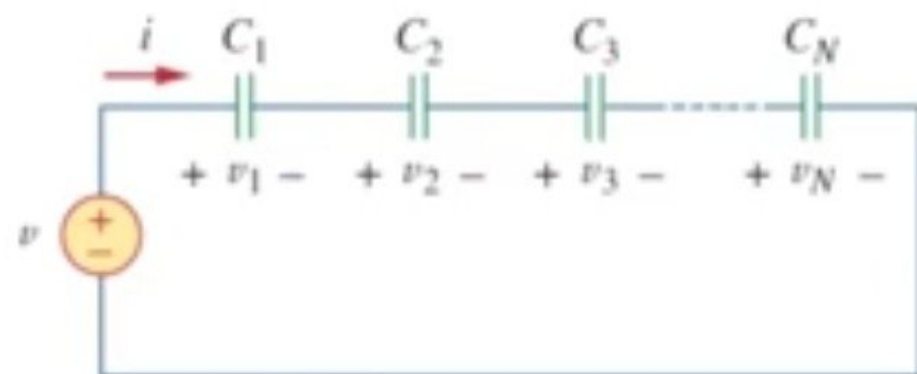
$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$



For two caps in parallel
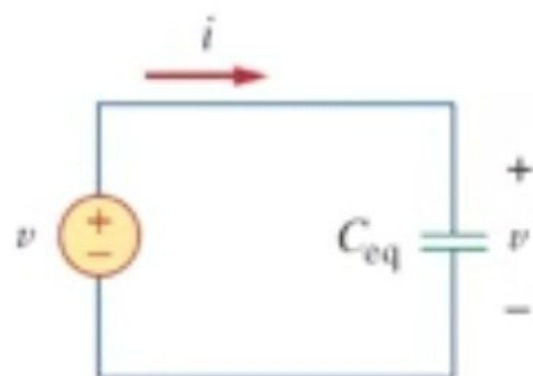
$$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$$




Capacitors

□ Capacitors in series:

Proof:

$$v = v_1 + v_2 + v_3 + \dots + v_N$$

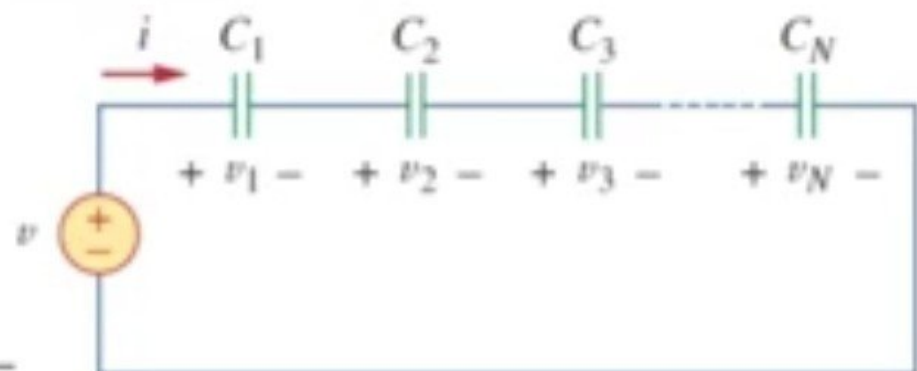

→

$$\begin{aligned} v &= \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0) \\ &\quad + \dots + \frac{1}{C_N} \int_{t_0}^t i(\tau) d\tau + v_N(t_0) \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + v_2(t_0) \\ &\quad + \dots + v_N(t_0) \\ &= \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v(t_0) \end{aligned}$$

$$v(t_0) = v_1(t_0) + v_2(t_0) + \dots + v_N(t_0)$$

Series and Parallel Caps

- Another way to think about the combinations of capacitors is this:
- Combining capacitors in parallel is equivalent to increasing the surface area of the capacitors:
- This would lead to an increased overall capacitance (as is observed)
- A series combination can be seen as increasing the total plate separation
- This would result in a decrease in capacitance (as is observed)


Capacitors

Example 6.6 Find the equivalent capacitance seen between terminals a and b

$$\frac{20 \times 5}{20 + 5} = 4 \mu\text{F}$$

$$4 + 6 + 20 = 30 \mu\text{F}$$

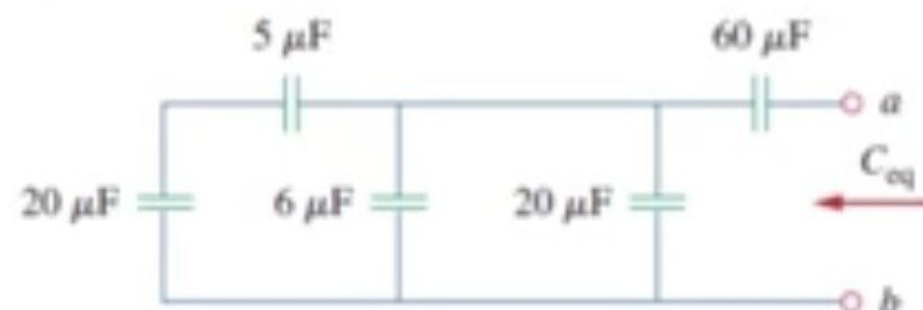
$$C_{\text{eq}} = \frac{30 \times 60}{30 + 60} = 20 \mu\text{F}$$



Capacitors

6.18 Find C_{eq} in the circuit of Fig. 6.52 if all capacitors are $4 \mu\text{F}$.


$$C_{eq} = 2.1818 \mu\text{F}$$

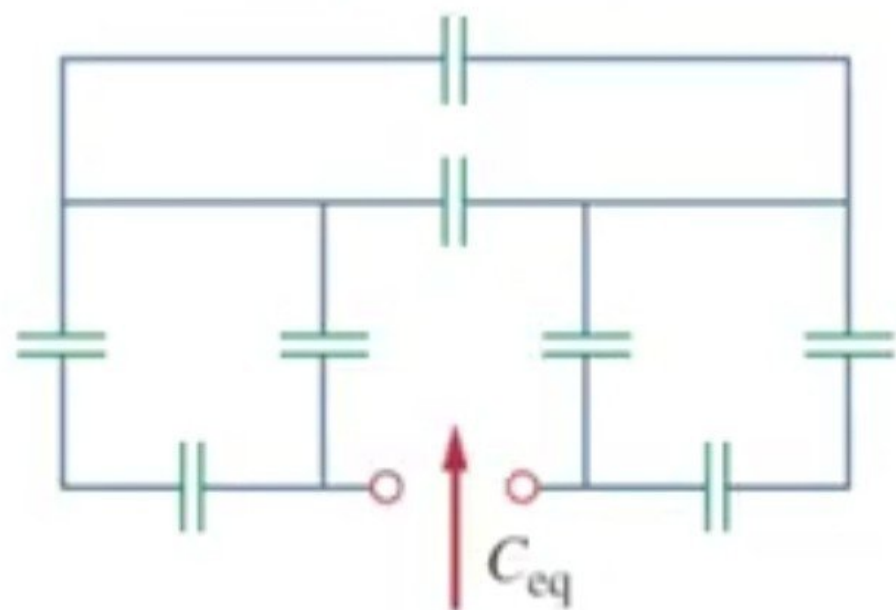

Capacitors

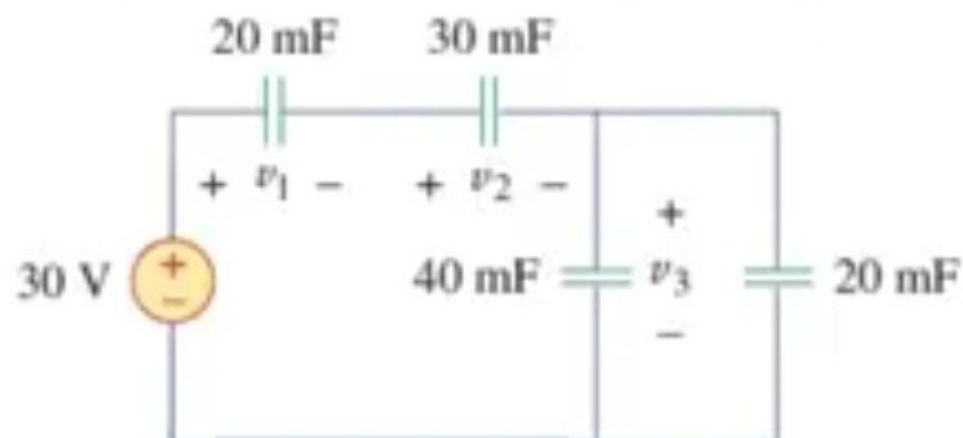Example 6.7

For the circuit in Fig. 6.18, find the voltage across each capacitor.




Capacitors

Example 6.7

For the circuit in Fig. 6.18, find the voltage across each capacitor.

$$C_{eq} = \frac{1}{\frac{1}{60} + \frac{1}{30} + \frac{1}{20}} \text{ mF} = 10 \text{ mF}$$
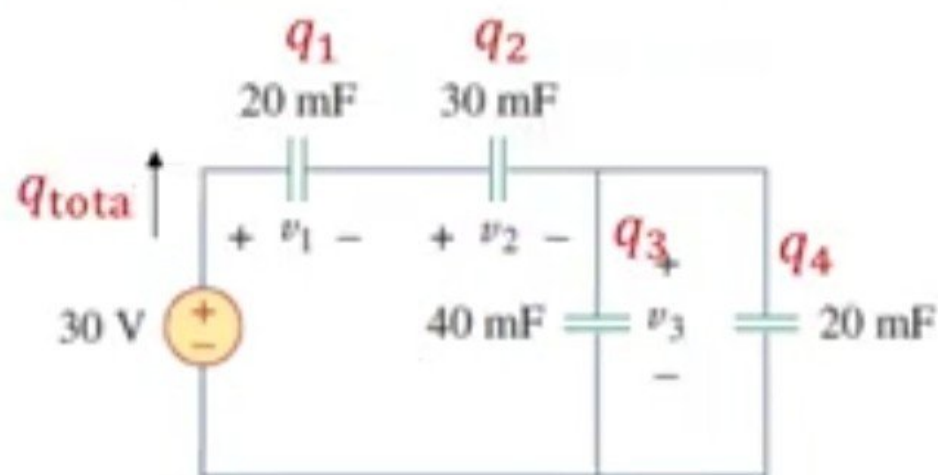
$$q_{total} = C_{eq}(30) = 0.3 \text{ C}$$



charge acts like current, so:

$$q_1 = q_2 = q_{total}$$

$$\text{and then: } v_1 = \frac{q_1}{C_1} = 15 \text{ V}$$

$$\text{and } v_2 = \frac{q_2}{C_2} = 10 \text{ V}$$

$$v_3 = 30 - v_1 - v_2 = 5 \text{ V}$$


OR:

$$q_3 = \frac{C_3}{C_3 + C_4} q_{total} = 0.2 \text{ C}$$

$$q_4 = \frac{C_4}{C_3 + C_4} q_{total} = 0.1 \text{ C}$$

Inductors

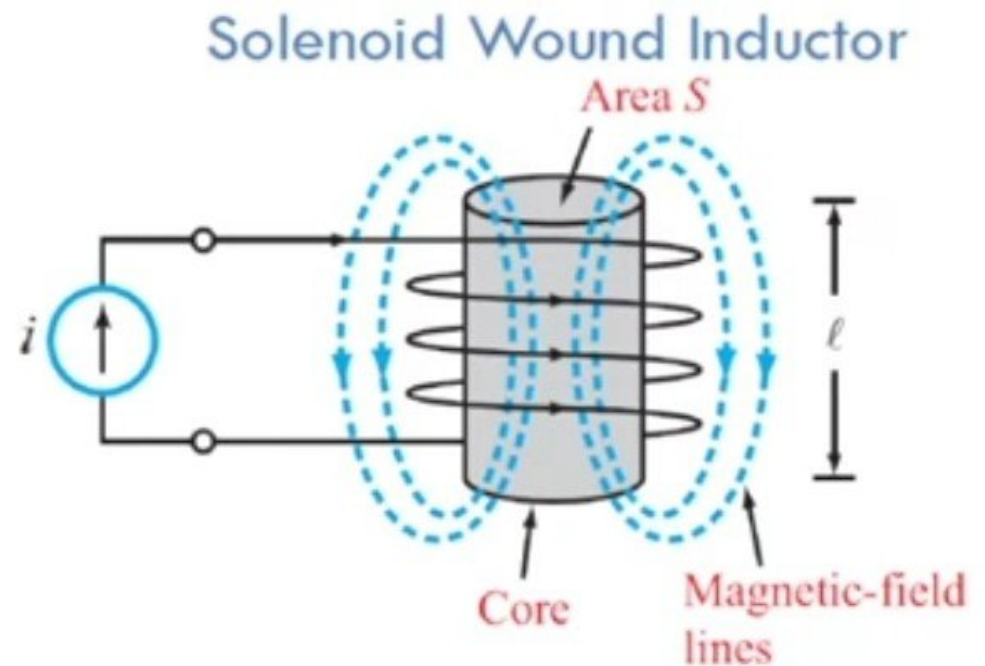
- ❑ An inductor is a passive element that stores energy in its magnetic field
- ❑ They have applications in power supplies, transformers, radios, TVs, radars, and electric motors.
- ❑ Any conductor has inductance L , but the effect is typically enhanced by coiling the wire up.




□ Several Types



High current inductor

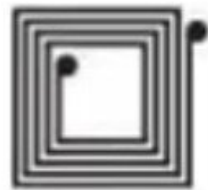

Planar inductor

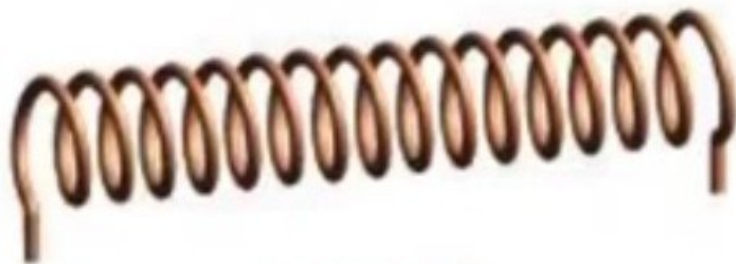

Solenoid

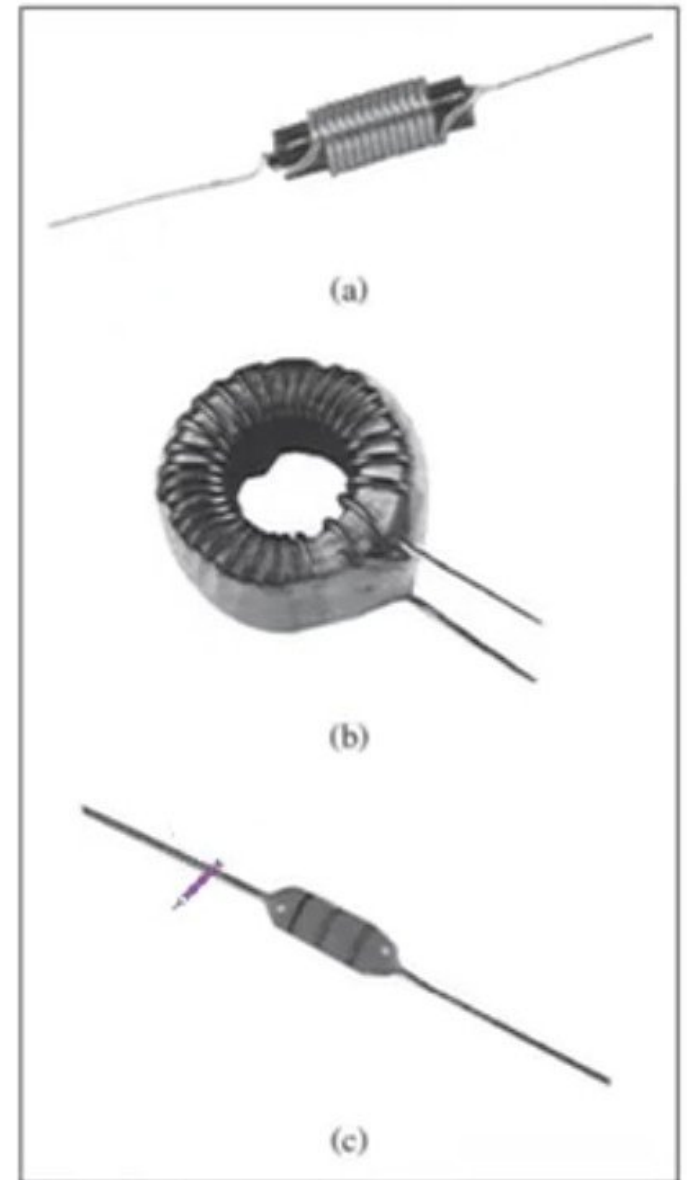


Figure 6.22

Various types of inductors: (a) solenoidal wound inductor, (b) toroidal inductor, (c) chip inductor.


Courtesy of Tech America.

Inductors

- ❑ *An inductor consists of a coil of conducting wire.*
- ❑ Calculating the inductance depends on the geometry:
 - For example, for a solenoid the inductance is:

$$L = \frac{N^2 \mu A}{l}$$

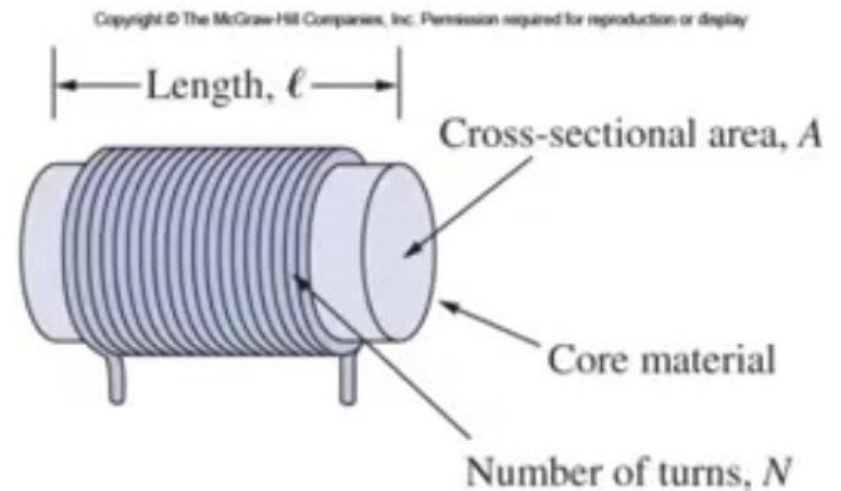- ✓ Where N is the number of turns of the wire around the core of cross sectional area A and length l .
- ✓ The material used for the core has a magnetic property called the permeability, μ .




- ❑ Inductance, measured in Henries, H.
- ❑ 1 Henry = 1 volt-second per ampere.

Inductors current-voltage relationship


- *The inductor opposes the change of current flowing through it.*
- If a current is passed through an inductor, the voltage across it is directly proportional to the time rate of change in current:

$$v = L \frac{di}{dt}$$

with passive sign convention.

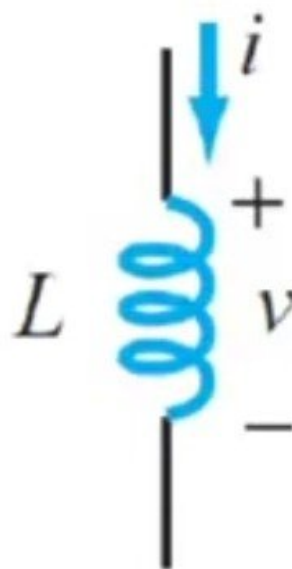


Inductors

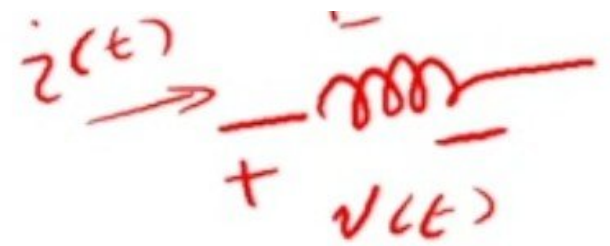

Example 6.8

The current through a 0.1-H inductor is $i(t) = 10te^{-5t}$ A. Find the voltage across the inductor and the energy stored in it.

$$v(t) = L \frac{di(t)}{dt}$$

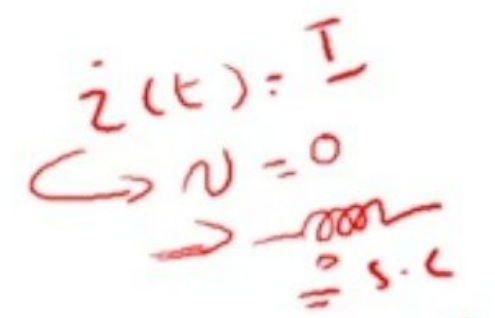

$$w = \frac{1}{2} Li^2$$

$$v = L di/dt$$

$$L = 0.1 \text{ H,}$$

$$v = 0.1 \frac{d}{dt}(10te^{-5t}) = e^{-5t} + t(-5)e^{-5t} = e^{-5t}(1 - 5t) \text{ V}$$

The energy stored is


$$w = \frac{1}{2} Li^2 = \frac{1}{2} (0.1) 100t^2 e^{-10t} = 5t^2 e^{-10t} \text{ J}$$

$$p(t) = v(t)i(t)$$

$$w(t) = \int p(t) dt = \int v(t)i(t) dt$$

Inductors

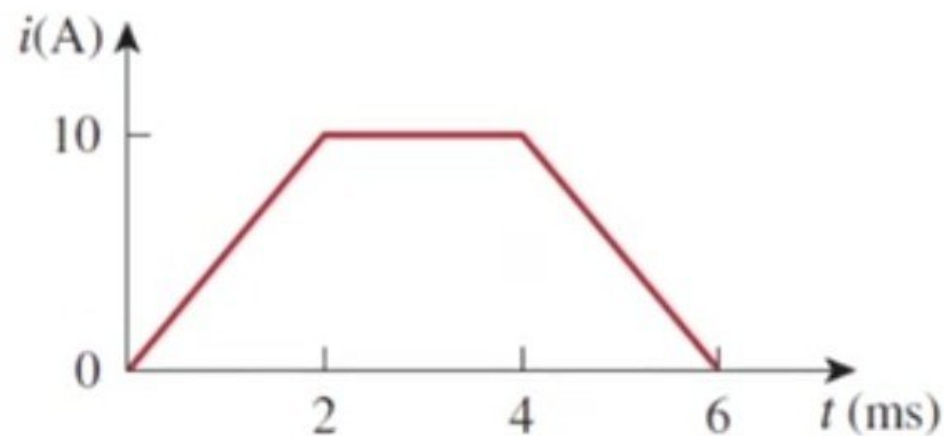- 6.40 The current through a 5-mH inductor is shown in Fig. 6.66. Determine the voltage across the inductor at $t = 1, 3,$ and 5 ms.



Inductors

Example 6.9

Find the current through a 5-H inductor if the voltage across it is

$$v(t) = \begin{cases} 30t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$

Also, find the energy stored at $t = 5$ s. Assume $i(v) > 0$.


Since $i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$ and $L = 5$ H,

$$i = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A}$$

$$w|_0^5 = \frac{1}{2}Li^2(5) - \frac{1}{2}Li^2(0) = \frac{1}{2}(5)(2 \times 5^3)^2 - 0 = 156.25 \text{ kJ}$$

Inductors

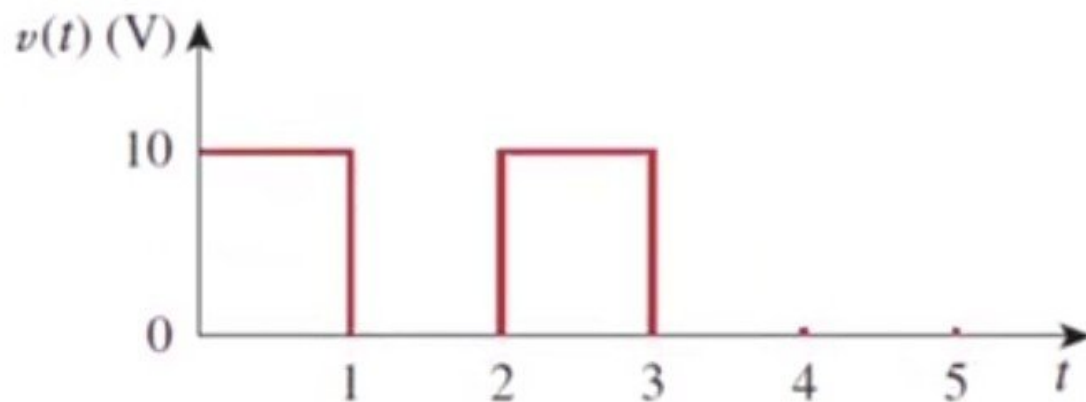
- 6.42** If the voltage waveform in Fig. 6.67 is applied across the terminals of a 5-H inductor, calculate the current through the inductor. Assume $i(0) = -1$ A.



Inductors

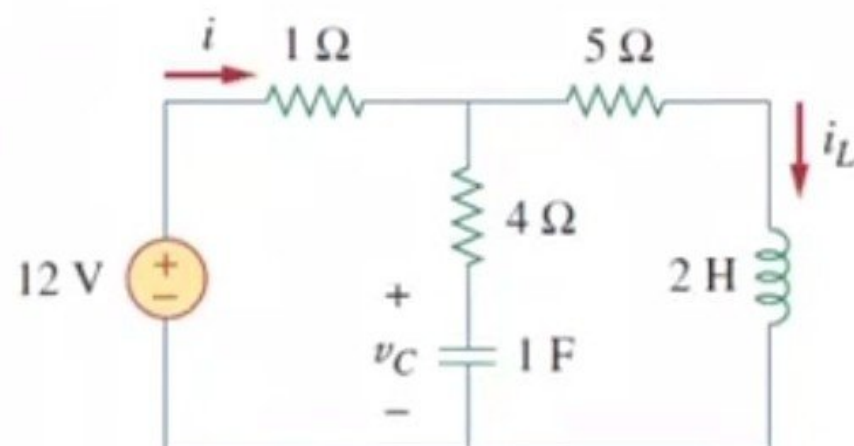Example 6.10

Under dc conditions, find: (a) i , v_C , and i_L , (b) the energy stored in the capacitor and inductor.



Inductors


Solution:

$$i = i_L = \frac{12}{1 + 5} = 2 \text{ A}$$



$$v_C = 5i = 10 \text{ V}$$

$$w_C = \frac{1}{2}Cv_C^2 = \frac{1}{2}(1)(10^2) = 50 \text{ J}$$
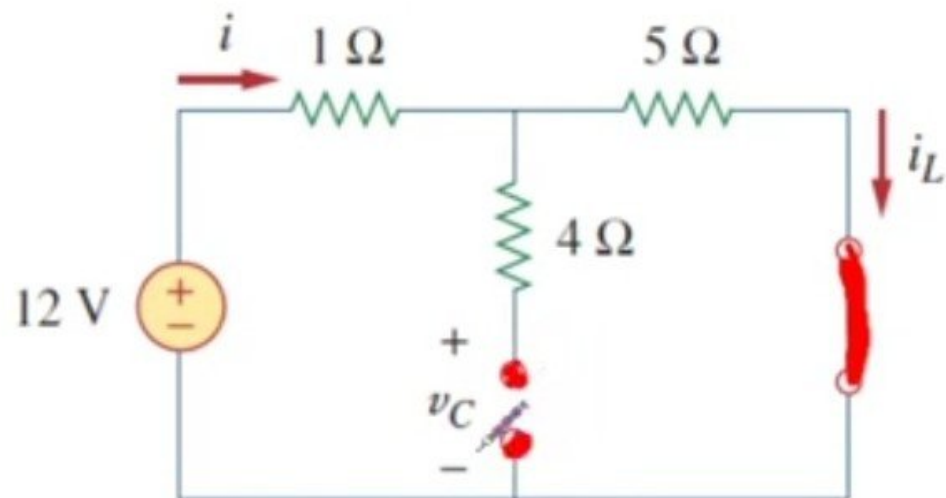
$$w_L = \frac{1}{2}Li_L^2 = \frac{1}{2}(2)(2^2) = 4 \text{ J}$$



Series Inductors

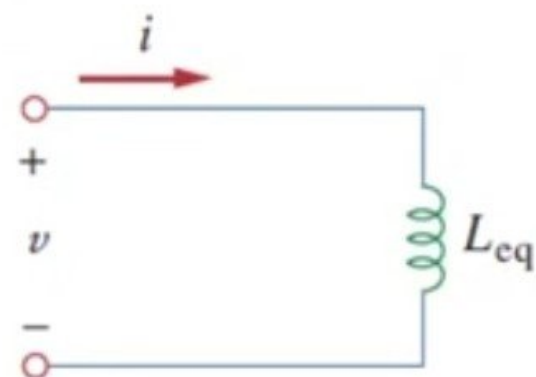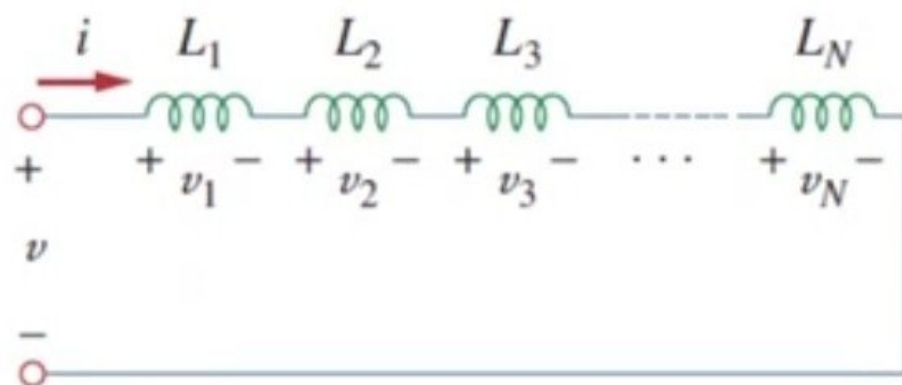

$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$

Proof:


$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt}$$

$$= \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

Parallel Inductors

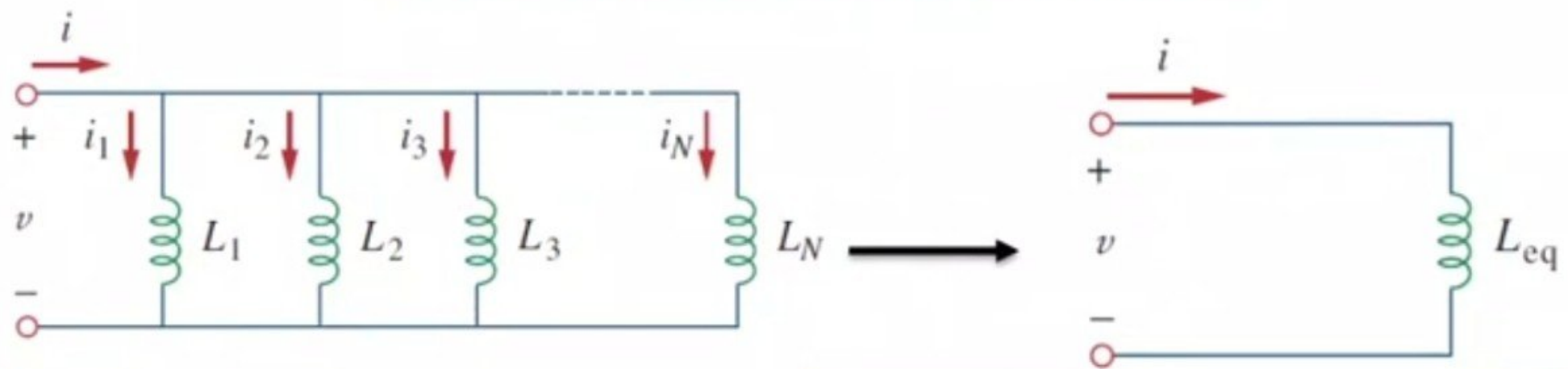

Proof:

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0)$$

$$+ \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$

$$= \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_{t_0}^t v dt + i_1(t_0) + i_2(t_0) + \dots + i_N(t_0)$$

$$= \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$

$$i(t_0) = i_1(t_0) + i_2(t_0) + \dots + i_N(t_0)$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$

For two inductors in parallel

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

TABLE 6.1Important characteristics of the basic elements.[†]

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
v - i :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
i - v :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{\text{eq}} = R_1 + R_2$	$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{\text{eq}} = L_1 + L_2$
Parallel:	$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{\text{eq}} = C_1 + C_2$	$L_{\text{eq}} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

Inductors

Example 6.12

For the circuit in Fig. 6.33, $i(t) = 4(2 - e^{-10t})$ mA. If $i_2(0) = -1$ mA, find: (a) $i_1(0)$; (b) $v(t)$, $v_1(t)$, and $v_2(t)$; (c) $i_1(t)$ and $i_2(t)$.

