


③ AC circuits Analysis

CU9
CU10

④ Complex Numbers

• $\vec{x} = a + jb$
• $a = \text{Re}\{\vec{x}\}$
• $b = \text{Im}\{\vec{x}\}$

rectangular form

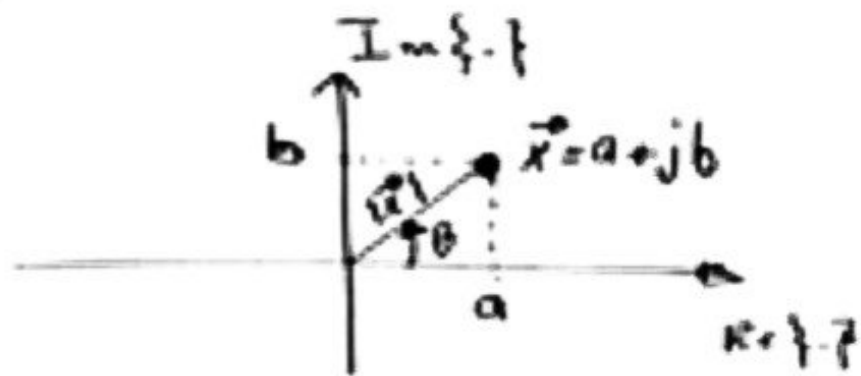

• $\vec{x} = |\vec{x}| \angle \theta$


polar form

• Convert from rectangular form to polar form

$$\vec{x} = a + jb \quad , \quad |\vec{x}| = \sqrt{a^2 + b^2}$$

$$A = 1 \angle 0^\circ$$

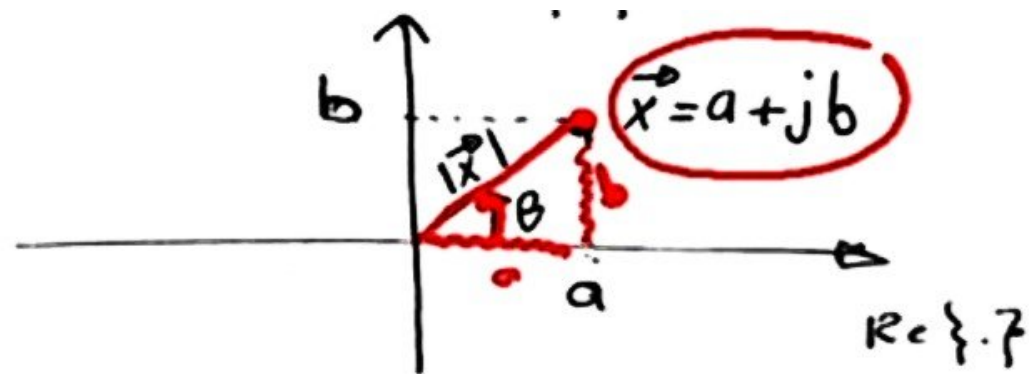rectangular form \rightarrow $a + jb$
 $a = \text{Re}\{\vec{x}\}$
 $b = \text{Im}\{\vec{x}\}$



polar form \rightarrow $\vec{x} = |\vec{x}| \angle \theta$

$$|\vec{x}| = \sqrt{a^2 + b^2}$$
$$\theta = \tan^{-1}(b/a)$$

- Convert from rectangular form to polar form:

$$\vec{x} = a + jb \quad , \quad |\vec{x}| = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1}(b/a)$$



- Convert from polar form to rectangular form:

$$\theta = \tan^{-1}(b/a).$$

- Convert from polar form to rectangular form:


$$\vec{x} = |\vec{x}| \angle \theta \quad \Rightarrow \quad a = |\vec{x}| \cos \theta$$
$$b = |\vec{x}| \sin \theta$$

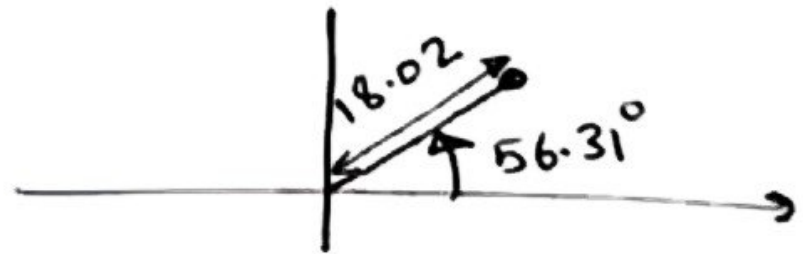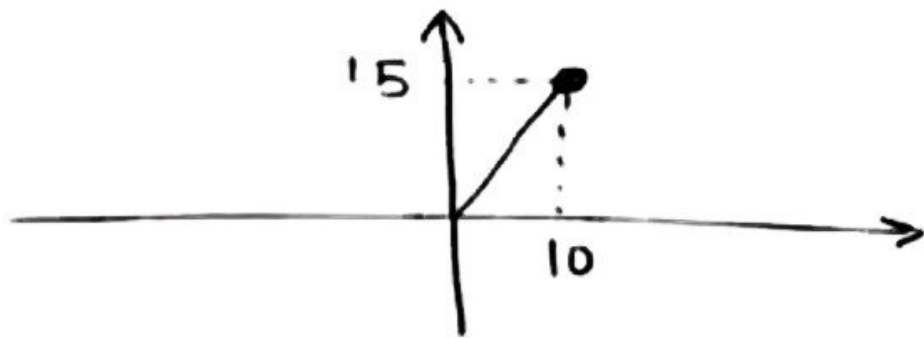• Ex^o $\vec{x} = 10 + j15 \triangleq \sqrt{10^2 + 15^2} \angle \tan^{-1}(15/10) = 18.02 \angle 56.31^\circ$



(1)


• Ex:

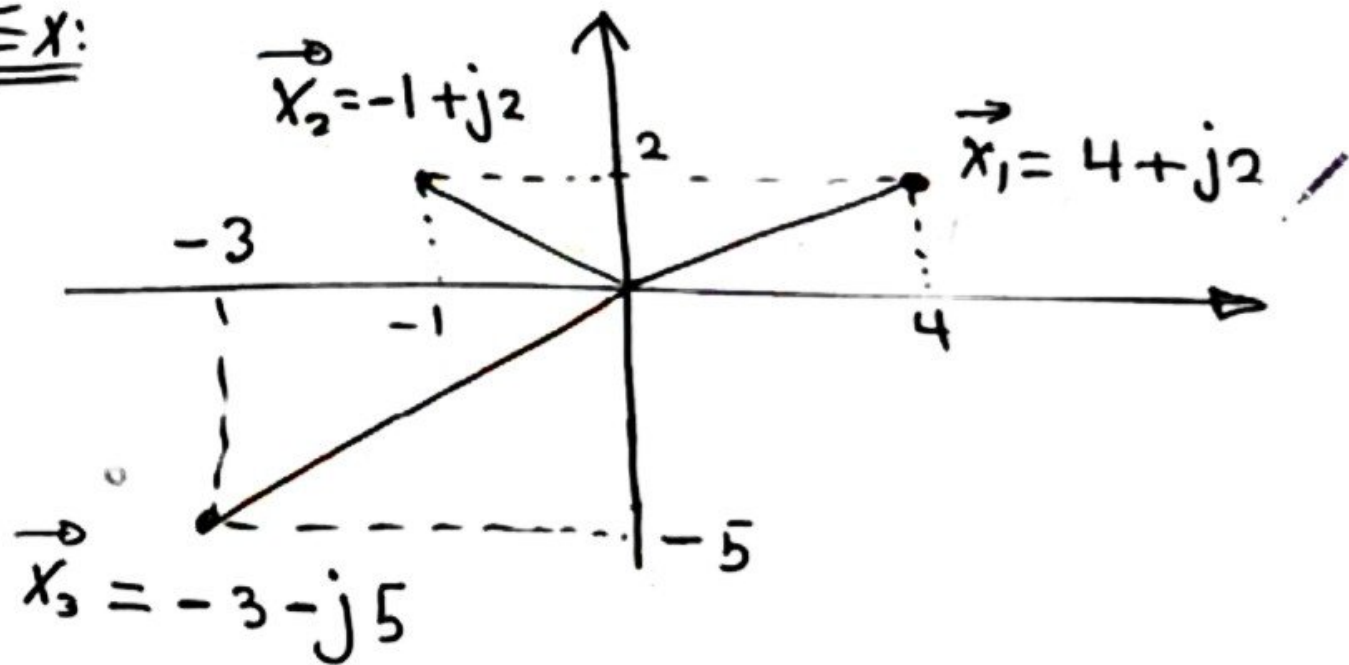

Find the polar form for each of these complex numbers.

• Ex: $\vec{y} = 110 \angle 93^\circ \Rightarrow \vec{y} = \underbrace{110 \cos(93^\circ)}_{=a} + j \underbrace{110 \sin(93^\circ)}_{=b}$
 $= -5.76 + j109.849$

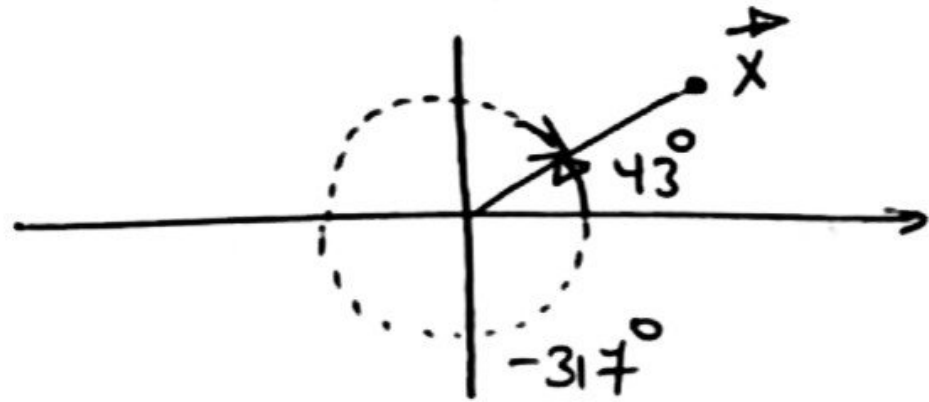
• EX: $\vec{x} = 12 \angle 43^\circ \equiv 12 \angle 43^\circ \pm 360^\circ = 12 \angle 403^\circ = 12 \angle -317^\circ$



• EX $\vec{x}_1 = 5 \angle 63^\circ \Rightarrow \vec{x}_2 = -\vec{x}_1 = 5 \angle 63^\circ \pm 180^\circ$

$$= 5 \angle 243^\circ$$

$$= 5 \angle -117^\circ$$

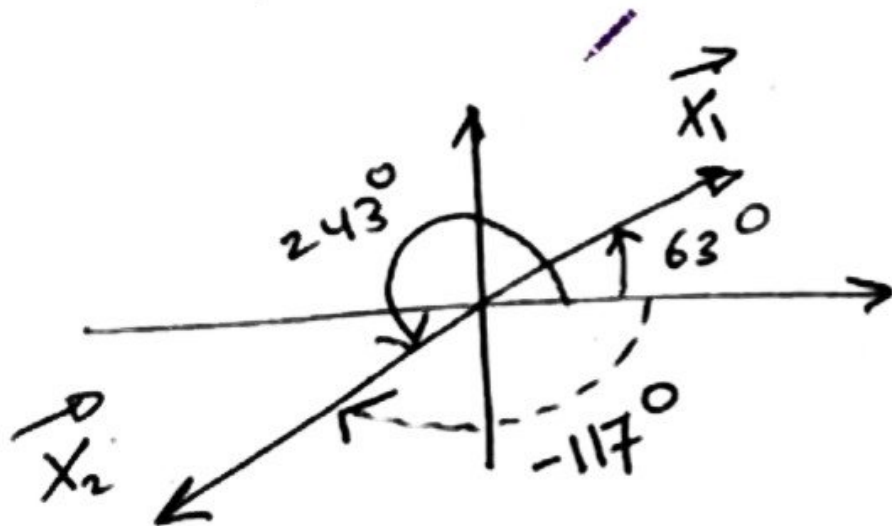

- sum & subtraction of two complex numbers
(preferred in the rectangular form)

Ex: $\vec{x}_1 = 3 + j4$, $\vec{x}_2 = -9 + j2$

$$\vec{x}_1 + \vec{x}_2 = (3 + (-9)) + j(4 + 2) = -6 + j6 .$$

$$\vec{x}_1 - \vec{x}_2 = (3 - (-9)) + j(4 - 2) = 12 + j2 .$$

- multiplication & division:
(preferred in polar form)

Ex: $\vec{x}_1 = 120 \angle -89^\circ$, $\vec{x}_2 = 60 \angle 112^\circ$

$$\vec{x}_1 \vec{x}_2 = (120)(60) \angle (-89^\circ) + (112^\circ)$$

$-j - 12 + j2$ ✓



• multiplication & division:
(preferred in polar form)

EX: $\vec{x}_1 = 120 \angle -89^\circ$, $\vec{x}_2 = 60 \angle 112^\circ$


$$\vec{x}_1 \vec{x}_2 = (120)(60) \angle (-89^\circ) + (112^\circ)$$
$$= 7200 \angle 23^\circ$$

$$\frac{\vec{x}_1}{\vec{x}_2} = \frac{120 \angle -89^\circ}{60 \angle 112^\circ} = \frac{120}{60} \angle -89^\circ - (112^\circ) = 2 \angle -201^\circ$$



Phasor Diagram

$x_1 = x_0$
 $x_2 = x_0$
 $x_3 = x_0$
 $x_4 = x_0$
 $x_5 = x_0$
 $x_6 = x_0$
 $x_7 = x_0$
 $x_8 = x_0$
 $x_9 = x_0$
 $x_{10} = x_0$
 $x_{11} = x_0$
 $x_{12} = x_0$
 $x_{100} = x_0$

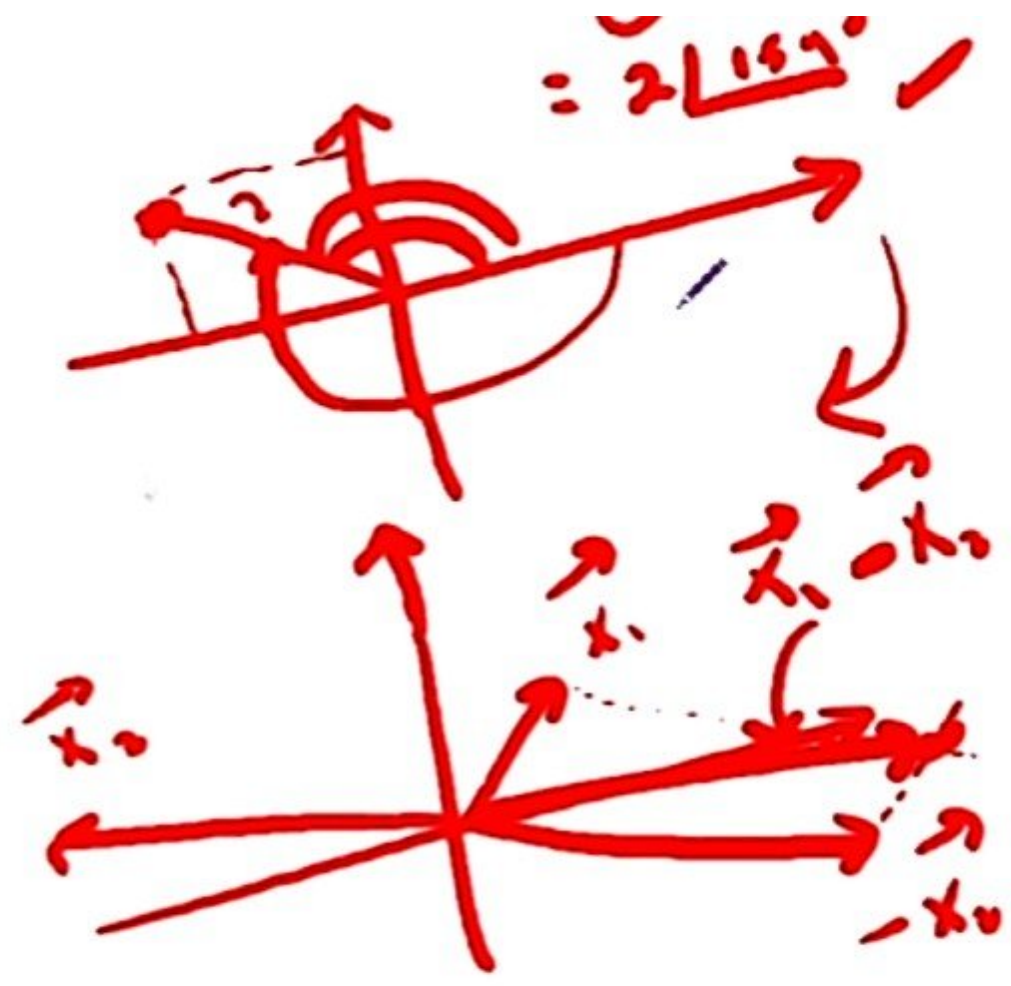

(3)

sin () OR cos ()

③ sinusoids characteristics:


• $v(t) = V_m \sin(\omega t)$


$V_m \doteq$ peak value (amplitude)

$\omega t \doteq$ argument $[\text{rad}]$

$\omega \doteq$ radian frequency $[\text{rad/sec}]$

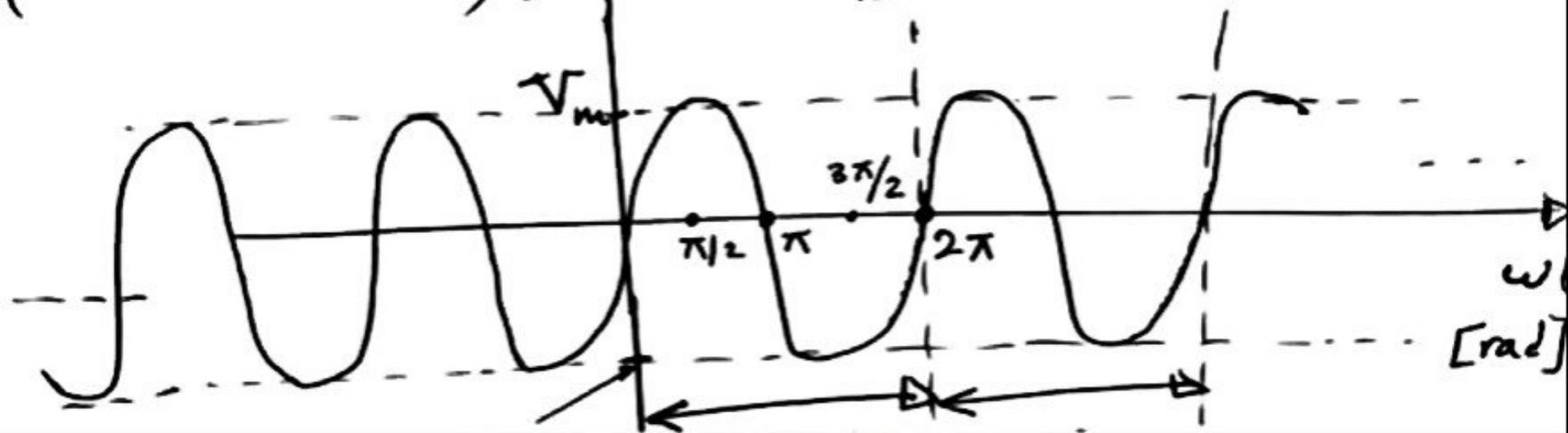(Plot $v(t)$ Vs ωt) $v(t) = V_m \sin(\omega t)$



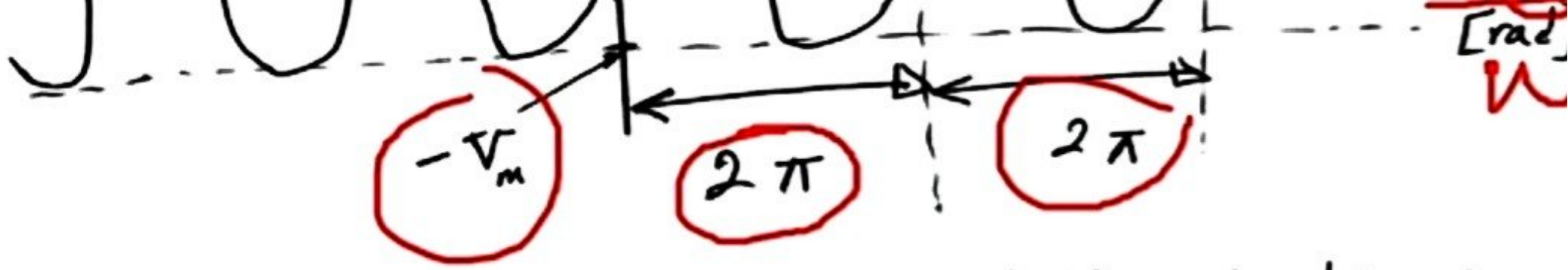

(plot v_{CE} Vs t) : divide the (ωt) -axis by ω



"period" $\rightarrow T$ [sec] "frequency"

$$\Rightarrow T = \frac{2\pi}{\omega} \Rightarrow \boxed{\omega = \frac{2\pi}{T} = 2\pi f}$$

(1)

EX: $v(t) = 20 \sin(1000t)$, find f & T . [V]

SOL: $\omega = 1000 \Rightarrow f = \frac{\omega}{2\pi} = \frac{1000}{2\pi} = 159.15 \text{ Hz}$
[rad]

$$\Rightarrow T = \frac{1}{f} = 6.283 \text{ msec.}$$

EX: $i(t) = 10 \cos(100\pi t)$ [A].

$$\omega = 100\pi \Rightarrow f = \frac{100\pi}{2\pi} = 50 \text{ Hz}$$

$$\Rightarrow T = \frac{1}{f} = 20 \text{ msec.}$$

- More general case:

$$v(t) = V_m \sin(\omega t + \theta)$$

$V_m \triangleq$ peak value or amplitude.

$\omega t + \theta \triangleq$ argument [rad]
or [degree]

$\omega \triangleq$ radian frequency [rad/sec]

$\theta \triangleq$ phase [rad] or [degree]


\nearrow
represents the signal shift
to the right or to the
left.

plot $v(t) = V_m \sin(\omega t + \theta)$ for

① $\theta = 0 \Rightarrow v_1(t)$

② $\theta < 0 \Rightarrow v_2(t)$ shift to right

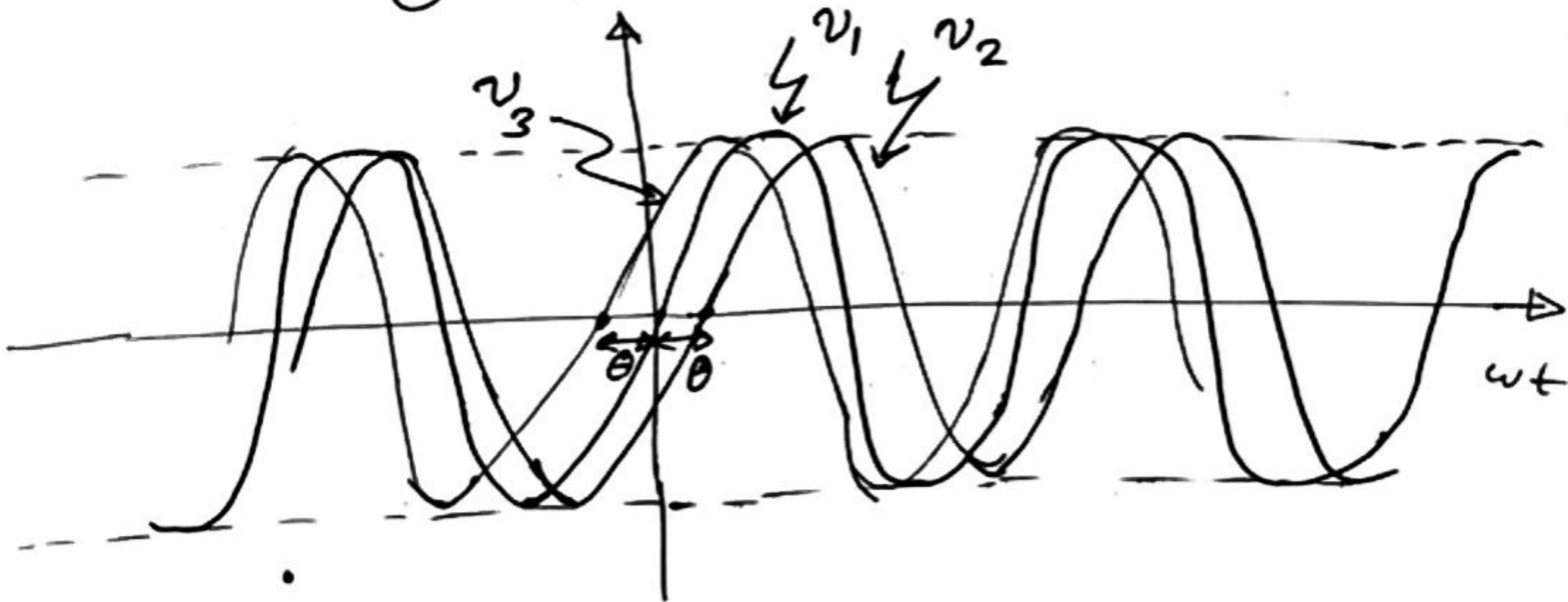③ $\theta > 0 \Rightarrow v_3(t)$ " " left



Lagging & Leading

$v_1(t)$ leads $v_2(t)$ by θ .

OR $v_2(t)$ lags $v_1(t)$ by θ .

OR $v_1(t)$ lags $v_2(t)$ by $-\theta \stackrel{\Delta}{=} 360^\circ - \theta$.

OR $v_2(t)$ leads $v_1(t)$ by $-\theta \stackrel{\Delta}{=} 360^\circ - \theta$.

what about $v_3(t)$ and $v_2(t)$?

Two compare two sinusoids:

- ① Both must have same ω .
- ② Both must be "cosine" or "sine".
- ③ Both must have +ve amplitude.

The conversion between them is:

$$\begin{aligned} - \sin(\omega t) &= \sin(\omega t \pm 180^\circ) \\ - \cos(\omega t) &= \cos(\omega t \pm 180^\circ) \\ \pm \cos(\omega t) &= \sin(\omega t \pm 90^\circ) \\ \pm \sin(\omega t) &= \cos(\omega t \mp 90^\circ) \end{aligned}$$


Ex: $v_1(t) = 10 \cos(1000\pi t - 10^\circ)$

Ex: $v_1(t) = 10 \cos(1000\pi t - 10^\circ)$

$v_2(t) = 2 \cos(1000\pi t + 40^\circ)$

which leads?, which lags?

Sol.

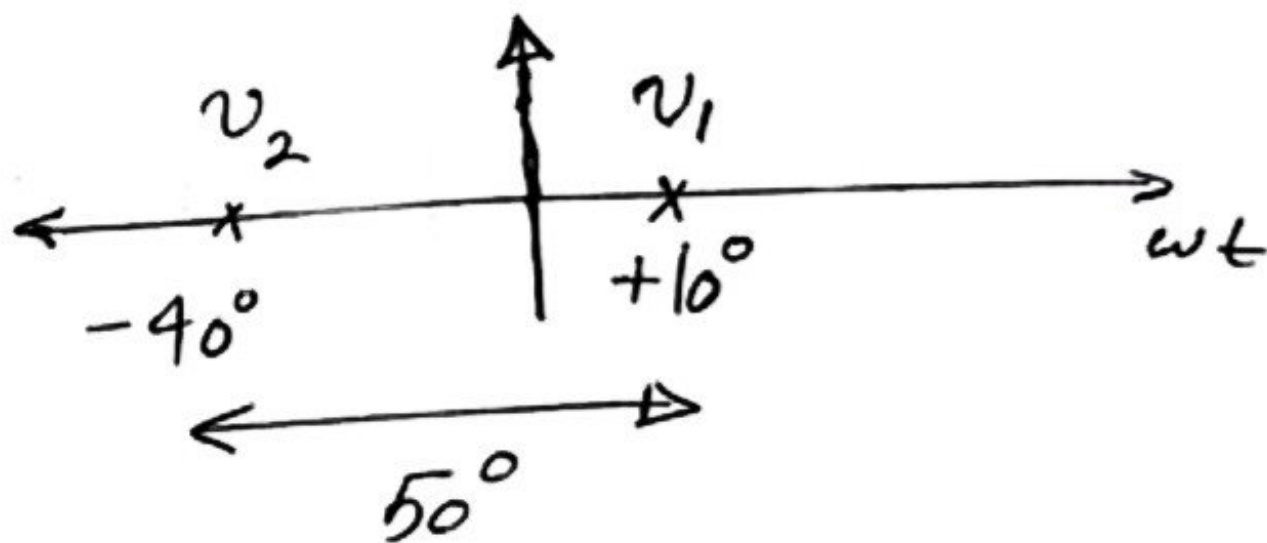


v_1 lags v_2 by 50°

v_2 leads v_1 by 50°

or v_1 leads v_2 by $-50^\circ = 310^\circ$

EX: $i(t) = -2 \cos(100\pi t + 20^\circ)$ [A]
 $v(t) = 12 \sin(100\pi t - 40^\circ)$ [V]

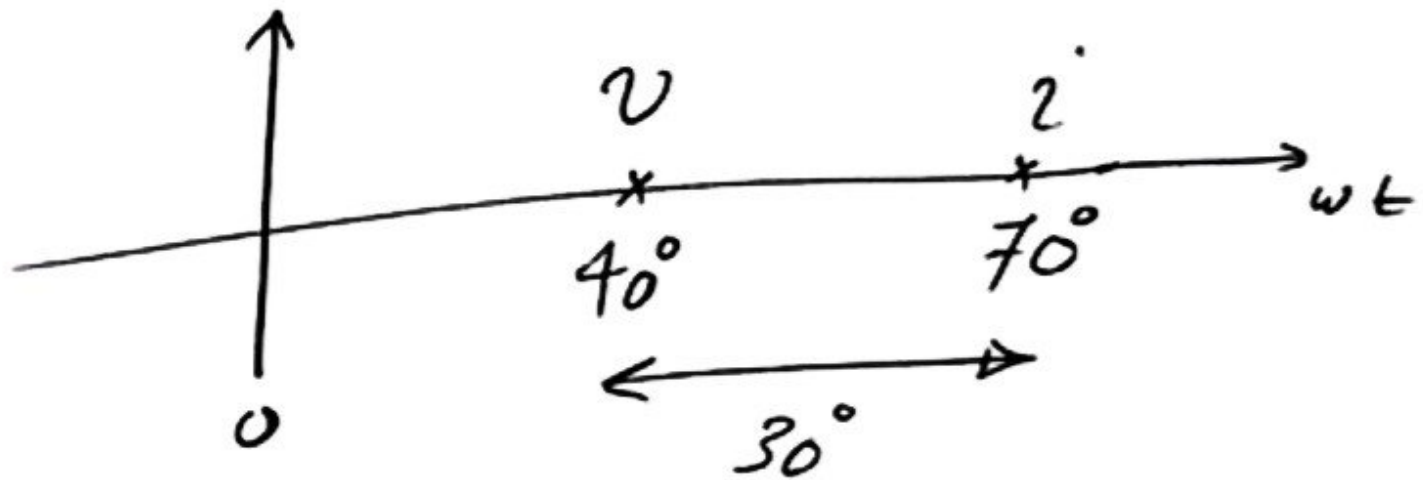SOL: $i(t) = 2 \sin(100\pi t + 20^\circ - 90^\circ)$
 $= 2 \sin(100\pi t - 70^\circ)$



v leads i by 30°
or i lags v by 30° .

EX: $v(t) = 2 \cos(200\pi t + 30^\circ)$
Find $v(0.01)$?

SOL: $v(0.01) = 2 \cos(2\pi + 30^\circ)$



Your calculator $\xrightarrow{\text{D}}$ $2 \cos(2\pi + 30^\circ \frac{\pi}{180^\circ}) = \sqrt{3}$
on [rad] \uparrow OR

Your calculator $\xrightarrow{\text{D}}$ $2 \cos(360^\circ + 30^\circ) = \sqrt{3}$
on [degree] \uparrow

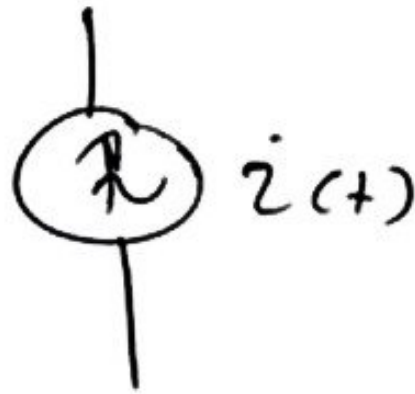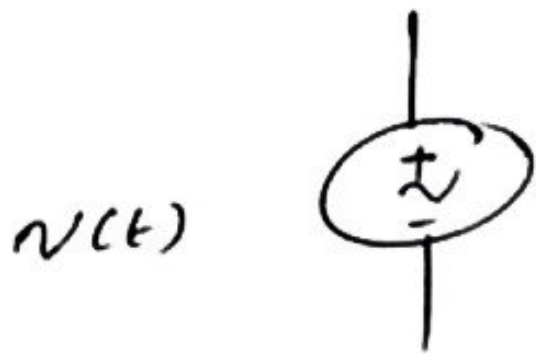(5)

② AC circuits:

Electric circuits that are driven by AC (sinusoidal) sources.



③ Why AC?

- Electric power delivered to homes and industry is AC.
- In the late 1800's, AC won out ~~his~~ little with DC due to its efficiency.

② Why AC?

DC


AC

• Electric power delivered to homes and industry is AC.

• In the late 1800's, AC won out his battle with DC due to its efficiency for long distance transmission.

② Steady-state Analysis of AC (sinusoidal)

Circuits:

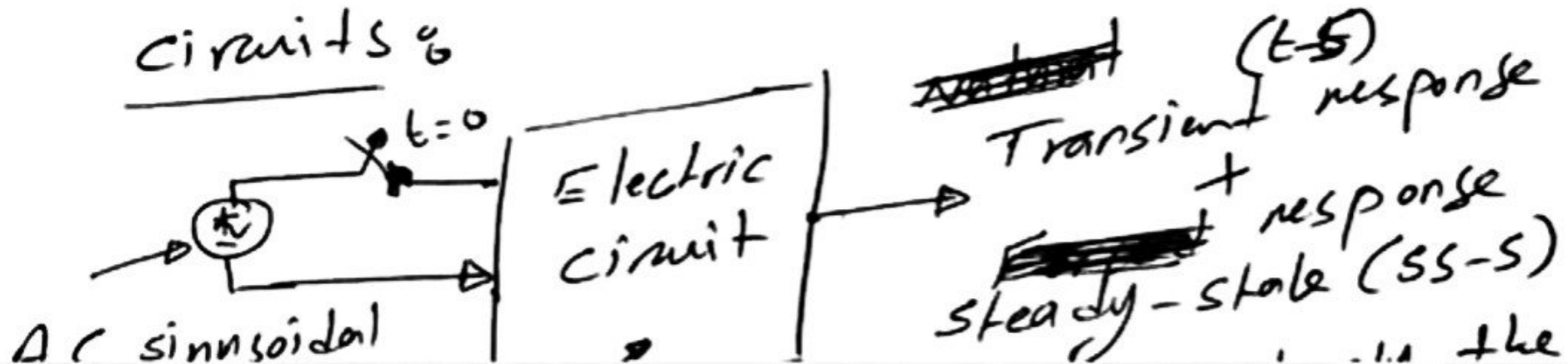


AC

In the late 1800's, AC won battle with DC due to its efficiency for long distance transmission.

② Steady-state Analysis of AC (sinusoidal)

Circuits

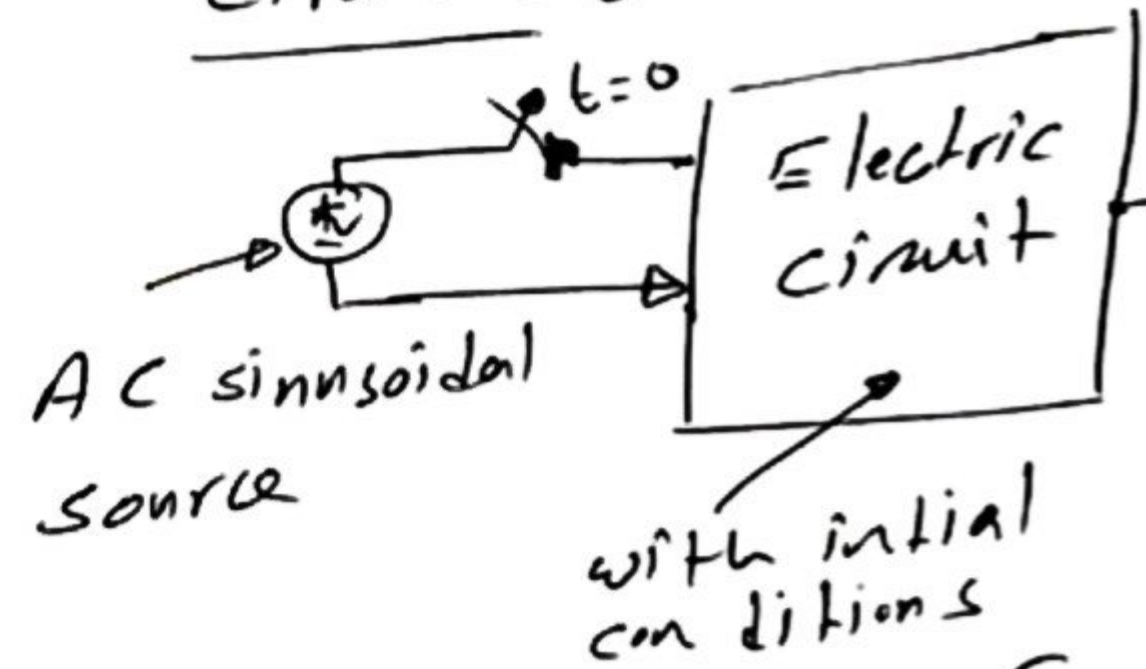

~~Transient~~ (t-s) response
 + response
~~Steady-state~~ (ss-s) response


- we need only the ss-s because the t-s is temporary and will die out.

⑥

⇒ So, we assume that AC circuits are under the steady-state and then analyze them.

To simplify analysing the steady-state AC circuits, we convert them from time-domain to complex-domain (phasor domain). So, instead of dealing with integro-differential equations we deal with algebraic equations but with complex-numbers.

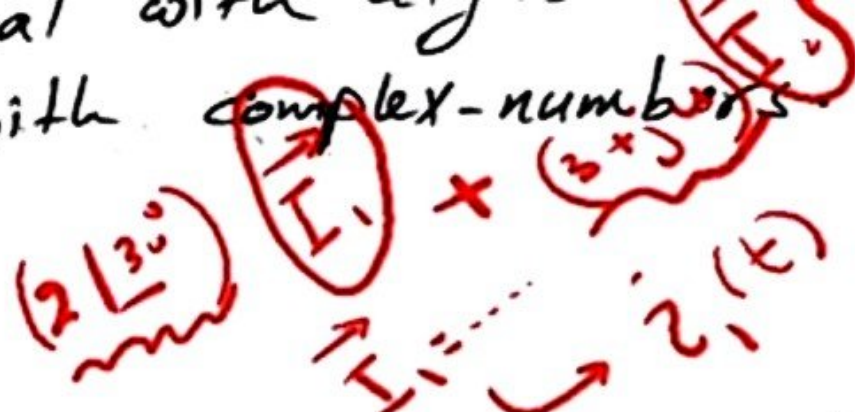equations we deal with
 equations but with complex-numbers



② Phasors:

Def: a phasor is a complex number that represents the amplitude and phase of a sinusoid. (the sinusoid has to be written as cosine with the amplitude)

$$\text{Let } v(t) = V_m \cos(\omega t + \theta_v)$$

$$= \text{Re} \{ V_m \angle \omega t + \theta_v \}$$

$$= \text{Re} \{ \underbrace{(V_m \angle \theta_v)}_{\text{phasor}} \underbrace{(1 \angle \omega t)}_{\text{operator}} \}$$

this is the phasor $\vec{V} = V_m \angle \theta_v$

(7)

the ckt
 operate at
 some ω ,
 so need
 to carry
 this.

$$v(t) = \sqrt{V_m} \cos(\omega t + \theta_v) \iff \vec{V} = V_m \angle \theta_v$$


the same for currents:

$$i(t) = \sqrt{I_m} \cos(\omega t + \theta_i) \iff \vec{I} = I_m \angle \theta_i$$

EX: $i_1(t) = 6 \cos(50t - 40^\circ) \text{ A}$

$$\Rightarrow \vec{I}_1 = 6 \angle -40^\circ \text{ A}$$


$$\equiv 6 \angle 32^\circ \text{ A}$$

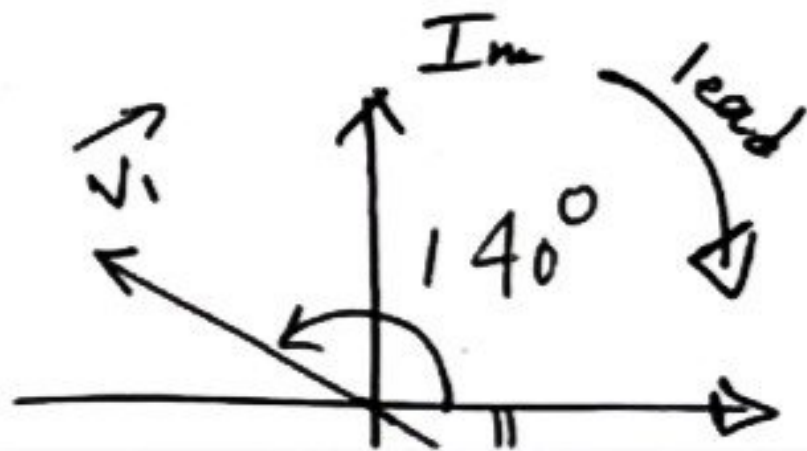

EX: $i_1(t) = 6 \cos(50t - 40^\circ) \text{ A}$

$$\Rightarrow \vec{I}_1 = 6 \angle -40^\circ \text{ A}$$

$$\equiv 6 \angle 320^\circ \text{ A}$$

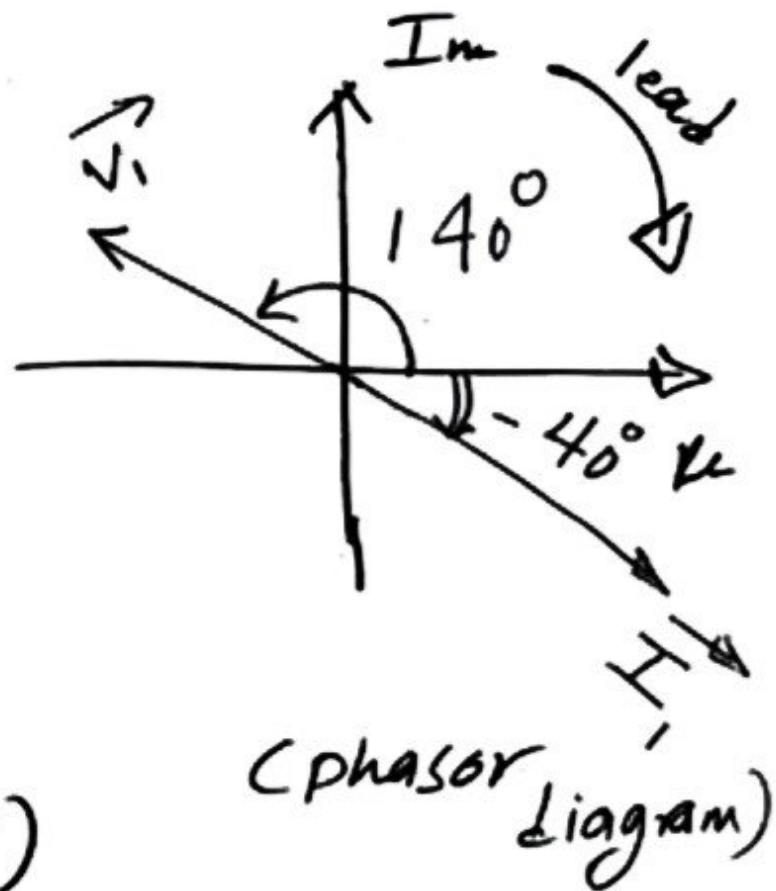

$v_1(t) = -4 \sin(30t + 50^\circ)$


~~$\Rightarrow -4 \angle 50^\circ \text{ V}$~~

$$v_1(t) = -4 \sin(30t + 50^\circ)$$

$$= 4 \cos(30t + 50^\circ + 90^\circ)$$

$$= 4 \cos(30t + 140^\circ)$$
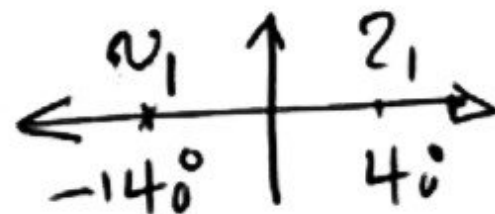
$$\Rightarrow \vec{V}_1 = 4 \angle 140^\circ \text{ V}$$



EX: $\vec{I} = 30 \angle -20^\circ$ mA Phase


$\Rightarrow i(t) = 30 \cos(\omega t - 20^\circ)$ mA.

EX: $\vec{V} = -3 + j4$ V, Find $v(t)$.

sol: $\vec{V} = \sqrt{9+16} \angle \tan^{-1}\left(\frac{4}{-3}\right) = 5 \angle 126.87^\circ$

$\Rightarrow v(t) = 5 \cos(\omega t + 126.87^\circ)$

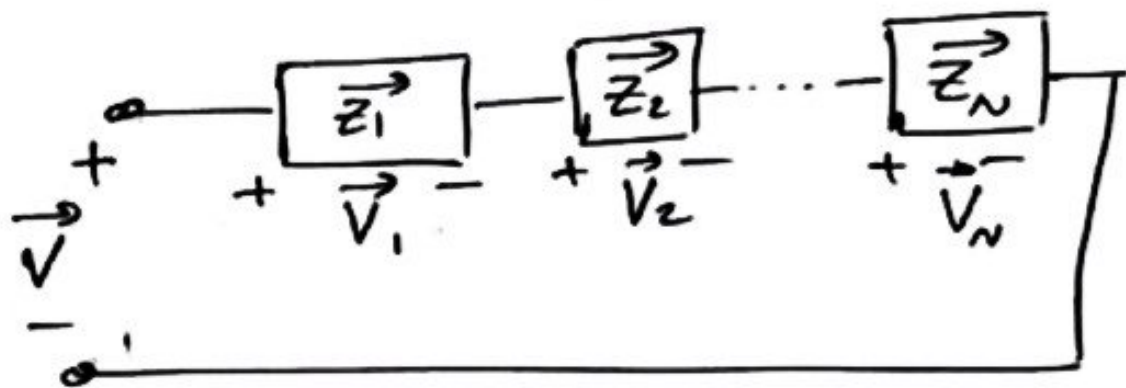
• Impedances in series & voltage division:



$$\vec{Z}_g = \vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_N$$

$$\vec{V}_n = \frac{\vec{Z}_n}{\vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_N} \quad (\text{voltage division})$$

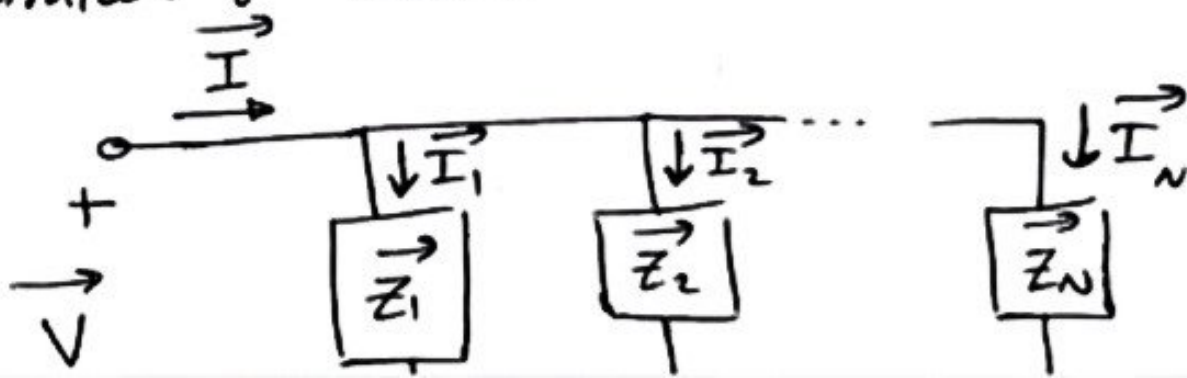• Impedances in parallel & current division:



$$\vec{Z}_{eq} = \frac{1}{\frac{1}{\vec{Z}_1} + \frac{1}{\vec{Z}_2} + \dots + \frac{1}{\vec{Z}_N}}$$

sol: $i(t) = i_1(t) + i_2(t)$

$$i_1(t) = 4 \cos(\omega t + 30^\circ) \Rightarrow \vec{I}_1 = 4 \angle 30^\circ$$

$$\begin{aligned} i_2(t) &= 5 \sin(\omega t - 20^\circ) \\ &= 5 \cos(\omega t - 110^\circ) \Rightarrow \vec{I}_2 = 5 \angle -110^\circ \end{aligned}$$

$$\begin{aligned} \Rightarrow i(t) &\Rightarrow \vec{I} = \vec{I}_1 + \vec{I}_2 \\ &= 4 \angle 30^\circ + 5 \angle -110^\circ \\ &\triangleq 3.218 \angle -56.97^\circ \end{aligned}$$

$$\Rightarrow i(t) = 3.218 \cos(\omega t - 56.97^\circ)$$

Lect #3

① In complex-domain, CKT elements converted to impedances.

what is "Impedance"?

② Impedance : can be delt as complex resistance

$$\vec{Z} = R + jX = |\vec{Z}| \angle \theta_Z \quad [\Omega]$$

resistance
(dissipate)
energy
originally


reactance
(stores energy)
originally ~~or~~ or ~~or~~

(stored energy)
originally
m

(stored energy)
originally ~~m~~ or ~~k~~

Ohm's Law is directly applied

$$\vec{V} = \vec{Z} \vec{I}$$

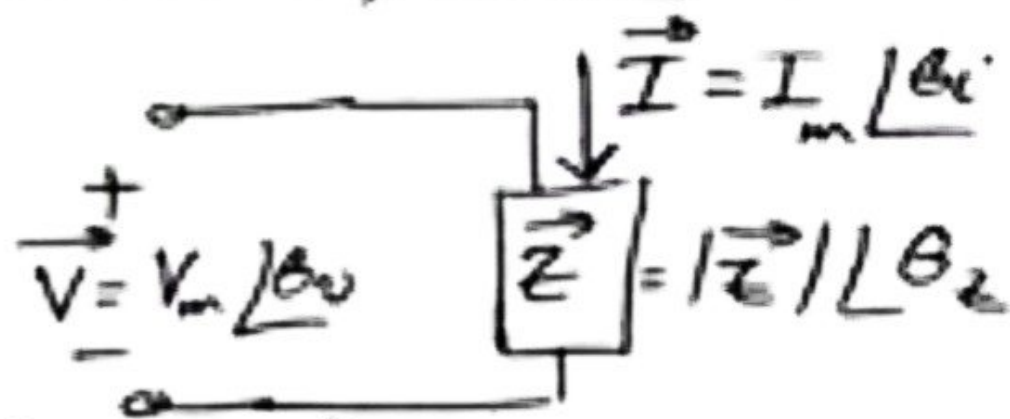


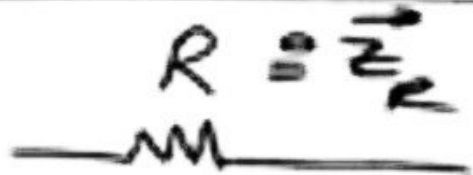
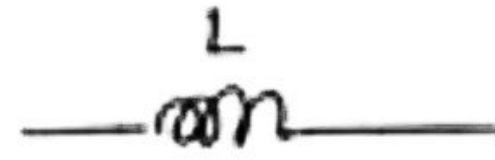
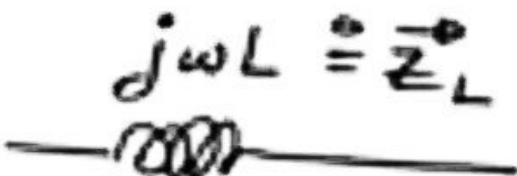
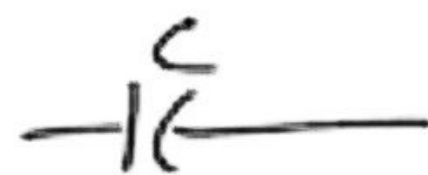
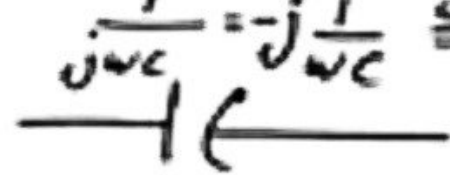
$$\Rightarrow V_m \angle \theta_v = (|\vec{Z}| \angle \theta_z) (I_m \angle \theta_i)$$

$$V_m = |\vec{Z}| I_m$$

$$\theta_v = \theta_i + \theta_z$$

①

② Convert CKT elements ^{find the impedance} for \sin, \cos, \dots

	<u>time-domain</u>		<u>complex domain</u>
[1]		\Rightarrow	$R \equiv \vec{Z}_R$ 
[2]		\Rightarrow	$j\omega L \equiv \vec{Z}_L$ 
[3]		\Rightarrow	$\frac{1}{j\omega C} = -j\frac{1}{\omega C} \equiv \vec{Z}_C$ 

Note: \vec{Z} refers to the impedance
(will be defined later).

proof: Let $v(t) = V_m \cos(\omega t + \theta_v) \Rightarrow \vec{V} = V_m \angle \theta_v$.

$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow \vec{I} = I_m \angle \theta_i$




in n

Note: \vec{Z} refers to the impedance
(will be defined later).

proof: Let $v(t) = V_m \cos(\omega t + \theta_v) \Rightarrow \vec{V} = V_m \angle \theta_v$.
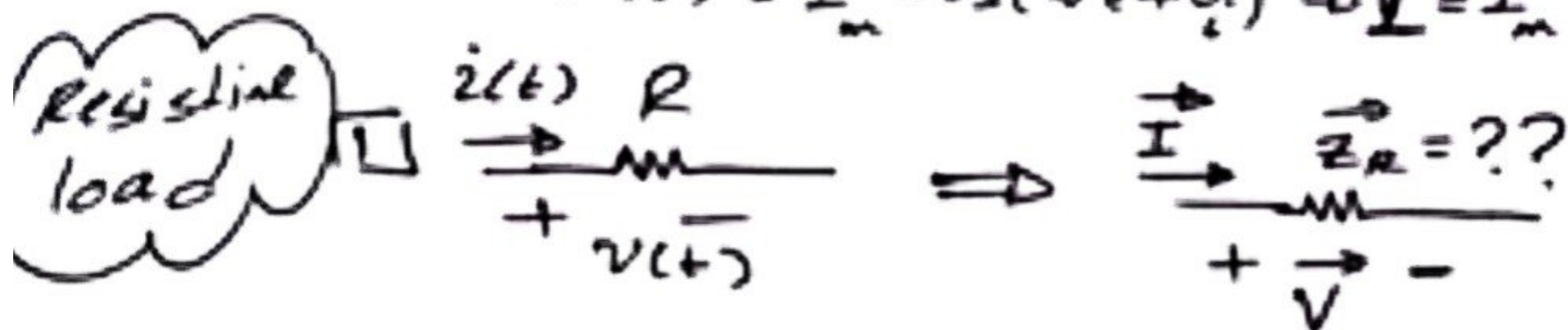
$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow \vec{I} = I_m \angle \theta_i$$




$$\bullet v(t) = R i(t)$$

$$V_m \cos(\omega t + \theta_v) = R I_m \cos(\omega t + \theta_i)$$

\Downarrow

$$V_m \angle \theta_v = R I_m \angle \theta_i$$
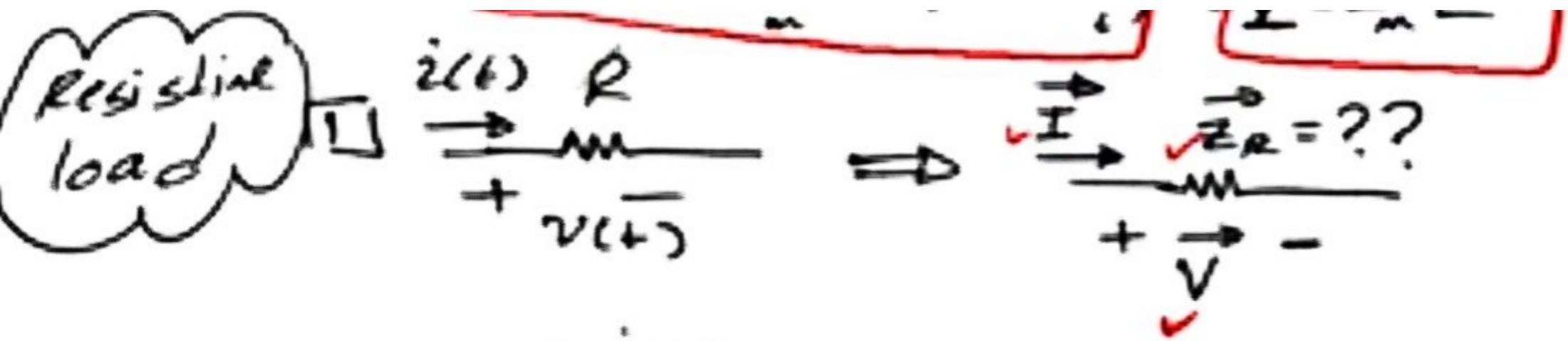
$$\Rightarrow \vec{V} = (R) \vec{I} \quad \text{note that } \theta_v = \theta_i$$



• $v(t) = R i(t)$


$V_m \cos(\omega t + \theta_v) = R I_m \cos(\omega t + \theta_i)$



$V_m \angle \theta_v = R I_m \angle \theta_i$


$\Rightarrow \vec{V} = R \vec{I}$

$\theta_v = 0$

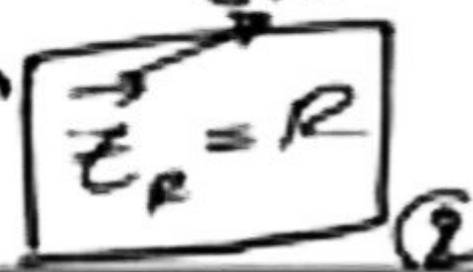

Note that $\theta_v = \theta_i$
 For resistive load
 \vec{I} & \vec{V} are in phase

pure inductive
load

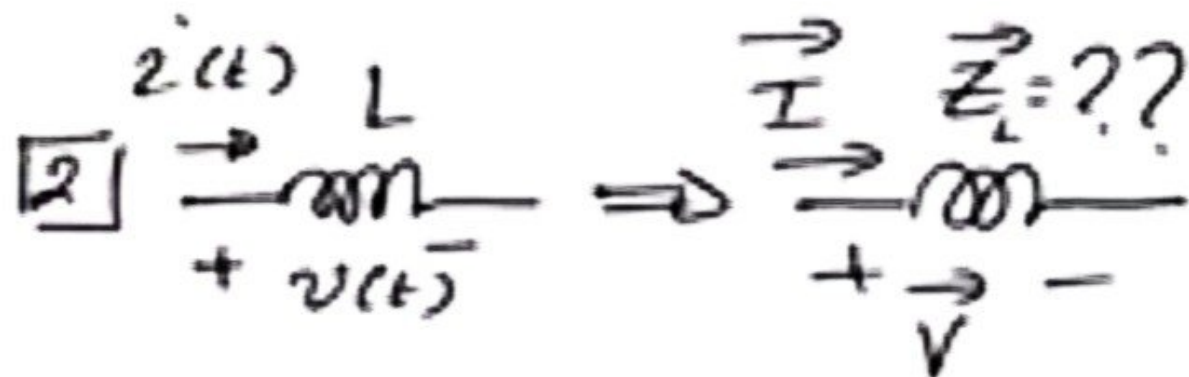

$$\bullet \quad v(t) = L \frac{di(t)}{dt}$$

$$\rightarrow V_m \cos(\omega t + \theta_v) = -L I_m \omega \sin(\omega t + \theta_i)$$

$$\rightarrow V_m \cos(\omega t + \theta_v) = \omega L I_m \cos(\omega t + \theta_i + 90^\circ)$$



$$V_m \angle \theta_v = \omega L I_m \angle \theta_i + 90^\circ$$

$$\rightarrow V_m \angle \theta_v = (\omega L \angle 90^\circ) (I_m \angle \theta_i)$$

$$V_m \angle \theta_v = \underline{\omega L I_m \angle \theta_i + 90^\circ}$$

$$\Rightarrow V_m \angle \theta_v = (\omega L \angle 90^\circ) (I_m \angle \theta_i)$$

$$\Rightarrow \vec{V} = \vec{Z}_L \vec{I}$$

$$\Rightarrow \boxed{\vec{Z}_L = \omega L \angle 90^\circ = j\omega L}$$

$$\theta_z = 90^\circ$$

Also note $\theta_v = \theta_i + 90^\circ$

$\Rightarrow \theta_i = \theta_v - 90^\circ$ (shifted to the left by 90°)


$\Rightarrow \vec{I}$ lags \vec{V} by 90°

is lagging element

always for pure

I_m

pure capacitive load

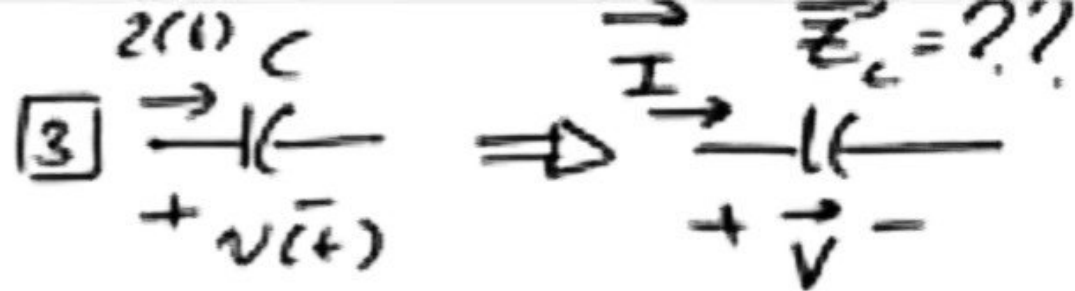

$$i(t) = C \frac{dv}{dt}$$

$$\Rightarrow I_m \cos(\omega t + \theta_i) = -C \omega V_m \sin(\omega t + \theta_v)$$

$$\Rightarrow I_m \cos(\omega t + \theta_i) = \omega C V_m \cos(\omega t + \theta_v + 90^\circ)$$

\Downarrow

$$I_m \angle \theta_i = \omega C V_m \angle \theta_v + 90^\circ$$

$$I_m \angle \theta_i = (\omega C \angle 90^\circ) V_m \angle \theta_v$$

$$\Rightarrow V_m \angle \theta_v = \left(\frac{1}{\omega C \angle 90^\circ} \right) (I_m \angle \theta_i)$$

$$\Rightarrow V_m \angle \theta_v = \left(\frac{1}{\omega C} \angle -90^\circ \right) (I_m \angle \theta_i)$$

$$\Rightarrow V_m \angle \theta_v = \left(\frac{1}{\omega C} \right) \angle 90^\circ (I_m \angle \theta_i)$$

$$\Rightarrow V_m \angle \theta_v = \left(\frac{1}{\omega C} \right) \angle -90^\circ (I_m \angle \theta_i)$$

$$\Rightarrow \vec{V} = \vec{Z}_c \vec{I} \Rightarrow \vec{Z}_c = \frac{1}{\omega C} \angle -90^\circ = -j \frac{1}{\omega C}$$

$$\theta_z = -90^\circ$$

Also note: $\theta_i = \theta_v + 90^\circ$

(i shifted to the right)


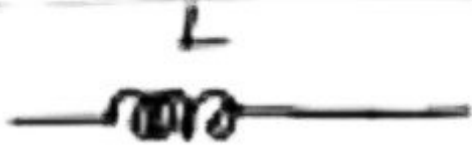
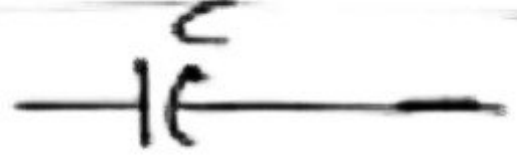
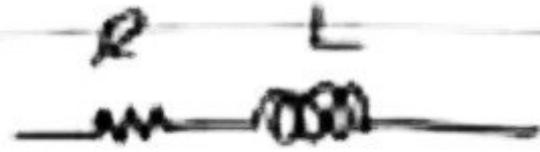
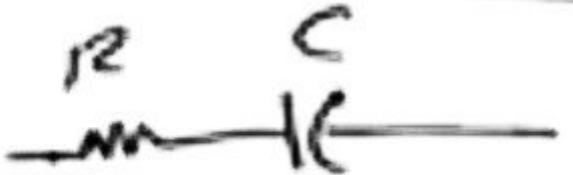
\vec{I} leads \vec{V} by 90°

It is leading element


always for pure capacitive load




(4)

Time	\vec{Z}	LOAD TYPE	θ_Z	\vec{I} & \vec{V}
	R	pure resistive	0	In phase
	$j\omega L = jX_L$	pure inductive	90°	\vec{I} lags \vec{V} by 90°
	$-j\frac{1}{\omega C} = -jX_C$	pure capacitive	-90°	\vec{I} leads \vec{V} by 90°
	$R + jX_L$	inductive (not purely)	+ve	\vec{I} lags \vec{V} by θ_Z
	$R - jX_C$	capacitive (not purely)	-ve	\vec{I} leads \vec{V} by θ_Z


Ex: If $\omega = 10$ rad/sec, specify the equivalent load for each of the following impedances

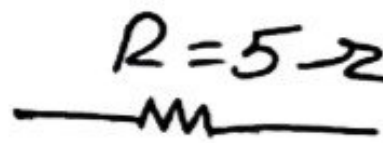① $\vec{Z} = 5 \Omega \Rightarrow$  $R = 5 \Omega$
 (pure resistive)

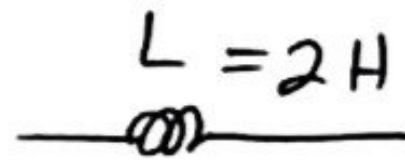② $\vec{Z} = j20 \Omega \Rightarrow$  $L = 2 \text{ H}$

pure inductive $j20 = j\omega L \Rightarrow L = \frac{20}{\omega} = 2 \text{ H}$

③ $\vec{Z} = \frac{1}{j20} \Omega$

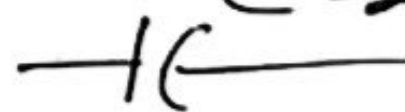$\vec{Z} = -j \frac{1}{20} \Rightarrow$ pure capacitance $C = 2 \text{ F}$


$-j \frac{1}{20} = -j \frac{1}{\omega C}$

$$-j \frac{1}{20} = -j \frac{1}{\omega C}$$

$$\Rightarrow 20 = \omega C$$

$$\Rightarrow C = 2 \text{ F}$$



④ $\vec{Z} = 4 + j3 \Rightarrow$ inductive load

$\omega L = 3$ $R = 4$ $L = 3/10 \text{ H}$

A circuit diagram showing a resistor symbol (zigzag line) labeled R=4 in series with an inductor symbol (coil) labeled L=3/10 H.

⑤ $\vec{Z} = 2 - j2 \Rightarrow$ capacitive load


$R = 2$ $C = 1/20 \text{ F}$

A circuit diagram showing a resistor symbol (zigzag line) labeled R=2 in series with a capacitor symbol (two parallel lines) labeled C=1/20 F.

$$-j2 = -j \frac{1}{\omega C}$$

$$2 = \frac{1}{\omega C} \Rightarrow C = \frac{1}{20} \text{ (8)}$$

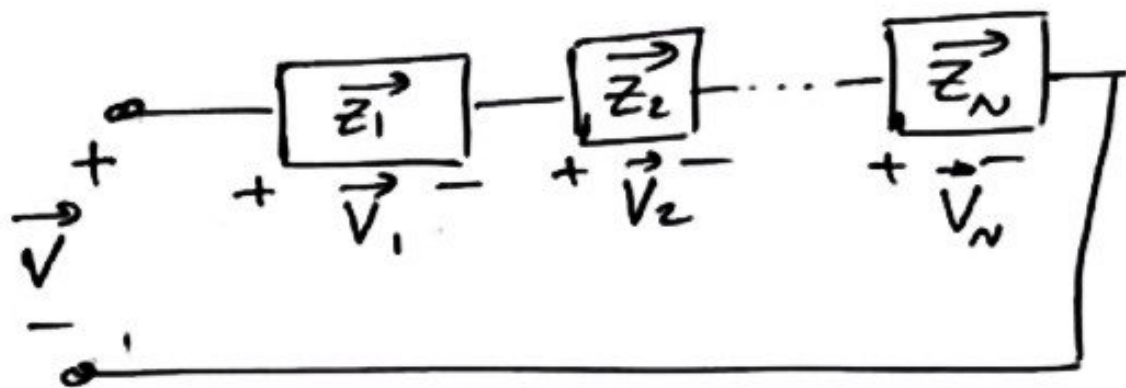
• Impedances in series & voltage division:



$$\vec{Z}_g = \vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_N$$

$$\vec{V}_n = \frac{\vec{Z}_n}{\vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_N} \quad (\text{voltage division})$$

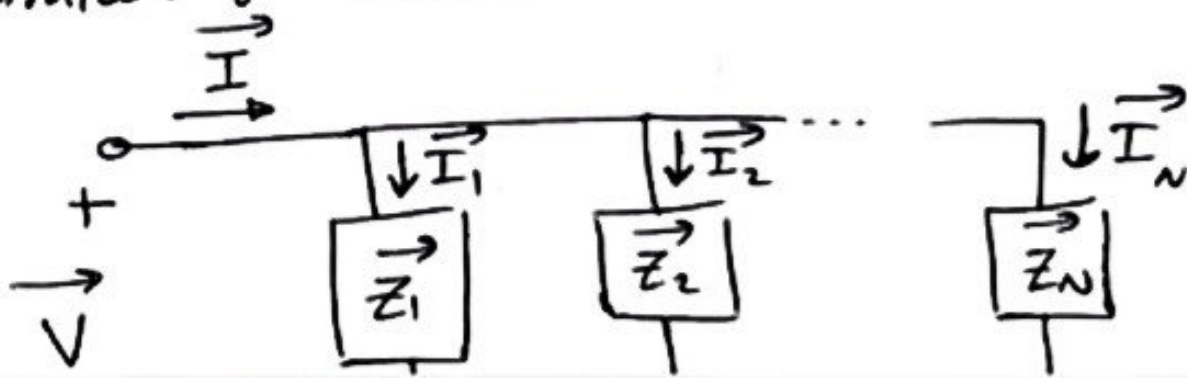• Impedances in parallel & current division:




$$\vec{Z}_{eq} = \frac{1}{\frac{1}{\vec{Z}_1} + \frac{1}{\vec{Z}_2} + \dots + \frac{1}{\vec{Z}_N}}$$


$$\vec{V}_n = \frac{\vec{Z}_n}{\vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_n} \quad (\text{voltage division})$$

• Impedances in parallel & current division:

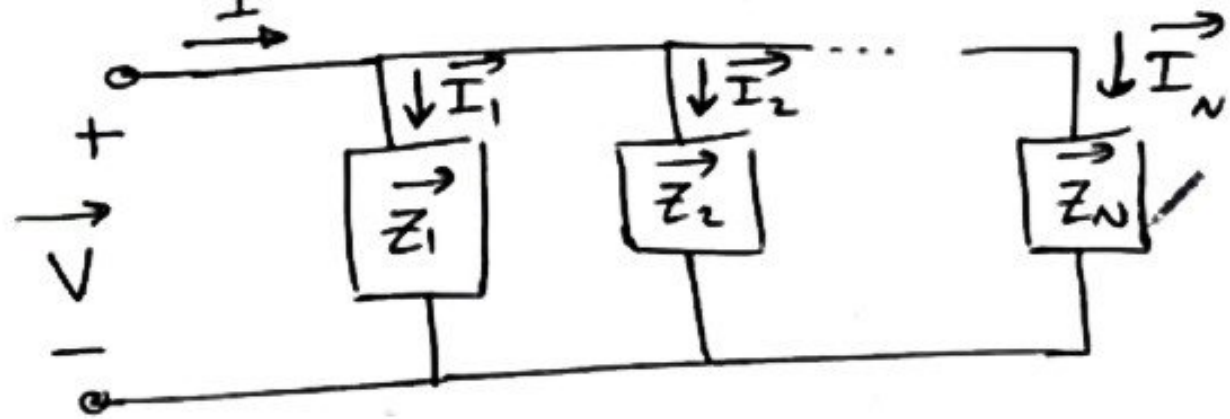
$$\vec{Z}_q = \frac{1}{\frac{1}{\vec{Z}_1} + \frac{1}{\vec{Z}_2} + \dots + \frac{1}{\vec{Z}_n}}$$


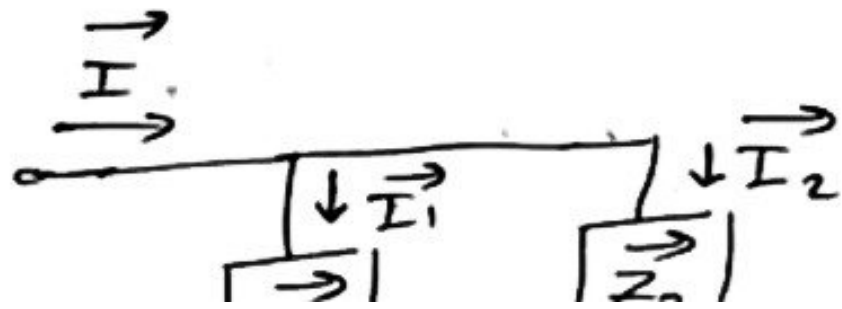
$$\vec{I}_n = \frac{\frac{1}{\vec{Z}_n}}{\frac{1}{\vec{Z}_q}} I \quad (\text{current division})$$



24

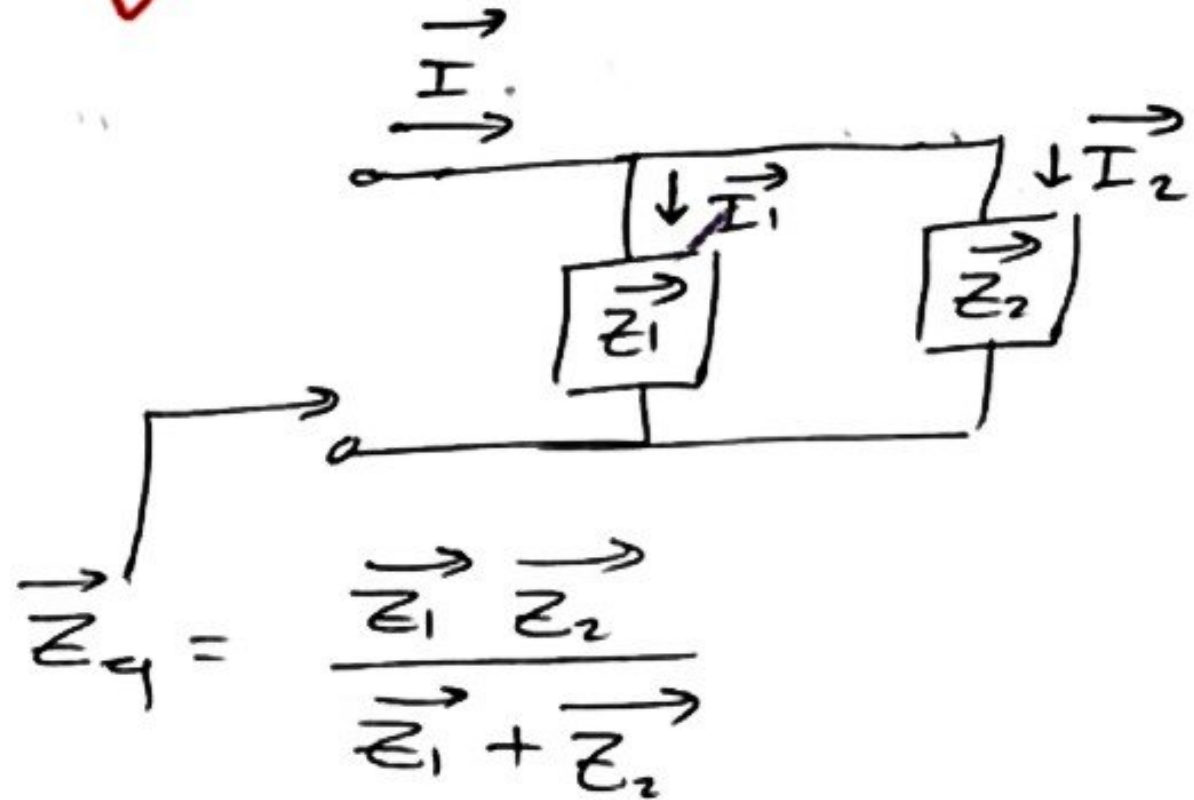


$$\vec{Z}_q = \frac{\vec{Z}_1 \vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2}$$

$$\vec{I}_1 = \frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} \vec{I}$$

$$\vec{I}_2 = \frac{\vec{Z}_1}{\vec{Z}_1 + \vec{Z}_2} \vec{I}$$

Dr. Yazid Khatkhatbi

Ex: Find the equivalent impedance.

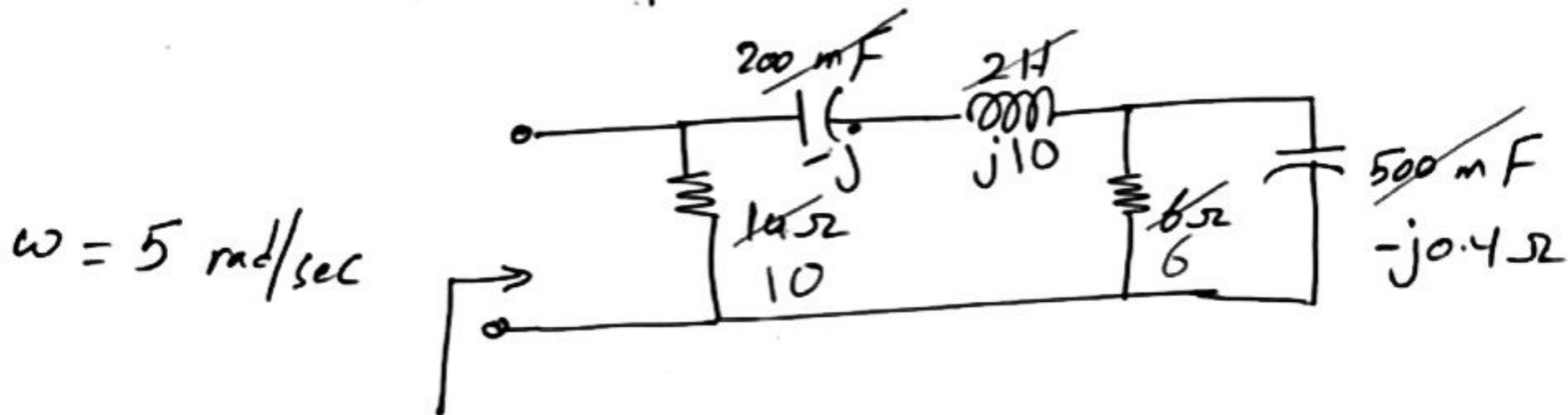

$$\vec{Z}_q = ??$$

Convert the elements to impedances:

$$R \longrightarrow R$$

$$L \longrightarrow j\omega L$$

$$C \longrightarrow -j \frac{1}{\omega C}$$

∴ ∴ ∴ (b) $(-j0.4) \triangleq 0.3991 \angle -86.18^\circ$

$$\cdot \underline{6} \parallel -j0.4 = \frac{(6)(-j0.4)}{6 - j0.4} \triangleq \boxed{0.3991 \angle -86.18^\circ}$$

$$\cdot \underline{0.3991 \angle -86.18^\circ} + \underline{j10} - \underline{j} \triangleq 8.602 \angle 89.823^\circ$$

$$\cdot (8.602 \angle 89.823^\circ) \parallel 10 \triangleq 6.511 \angle 49.19^\circ$$

$$\triangleq 4.255 + j4.93 \quad \Omega$$

equivalent to




"lagging impedance"

Ex: Find $i(t)$

Ⓐ using time-domain.

Ⓑ using complex-domain.

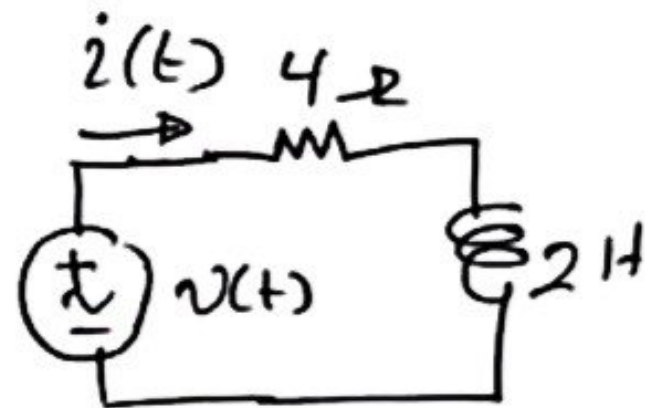

$$v(t) = 10 \cos(50t + 20^\circ)$$

sol: Ⓐ using time-domain.

KVL: $-v(t) + 4i(t) + 2 \frac{di}{dt} = 0$

$$\Rightarrow 2 \frac{di}{dt} + 4i(t) = 10 \cos(50t + 20^\circ)$$

\nearrow
we need to solve 1st order diff-equation !!

\Rightarrow proposed solution:

$$i(t) = T \cos(50t + \phi)$$

⇒ proposed solution.

$$i(t) = I_m \cos(50t + \phi)$$

$$\Rightarrow \underbrace{-100 I_m}_{=B} \sin(50t + \phi) + \underbrace{4 I_m}_{=A} \cos(50t + \phi) = 10 \cos(50t + 20^\circ)$$

using: $A \cos(\alpha) + B \sin(\alpha) = \sqrt{A^2 + B^2} \cos(\alpha - \tan^{-1}(B/A))$

$$\Rightarrow \sqrt{16 I_m^2 + 10^4 I_m^2} \cos\left(50t + \phi - \tan^{-1}\left(\frac{-100 I_m}{4 I_m}\right)\right) = 10 \cos(50t + 20^\circ)$$

$$\Rightarrow \sqrt{10^4 + 16} I_m \cos(50t + \phi + 87.7^\circ) = 10 \cos(50t + 20^\circ)$$


$$\Rightarrow I_m = \frac{10}{\sqrt{10^4 + 16}} = 0.1, \quad \phi = 20^\circ - 87.7^\circ = 67.7^\circ$$

② using complex domain:

$$R = 4 \Omega \longrightarrow \vec{Z}_R = 4 \Omega$$

$$L = 2 \text{ H} \longrightarrow \vec{Z}_L = j\omega L = j100 \Omega$$

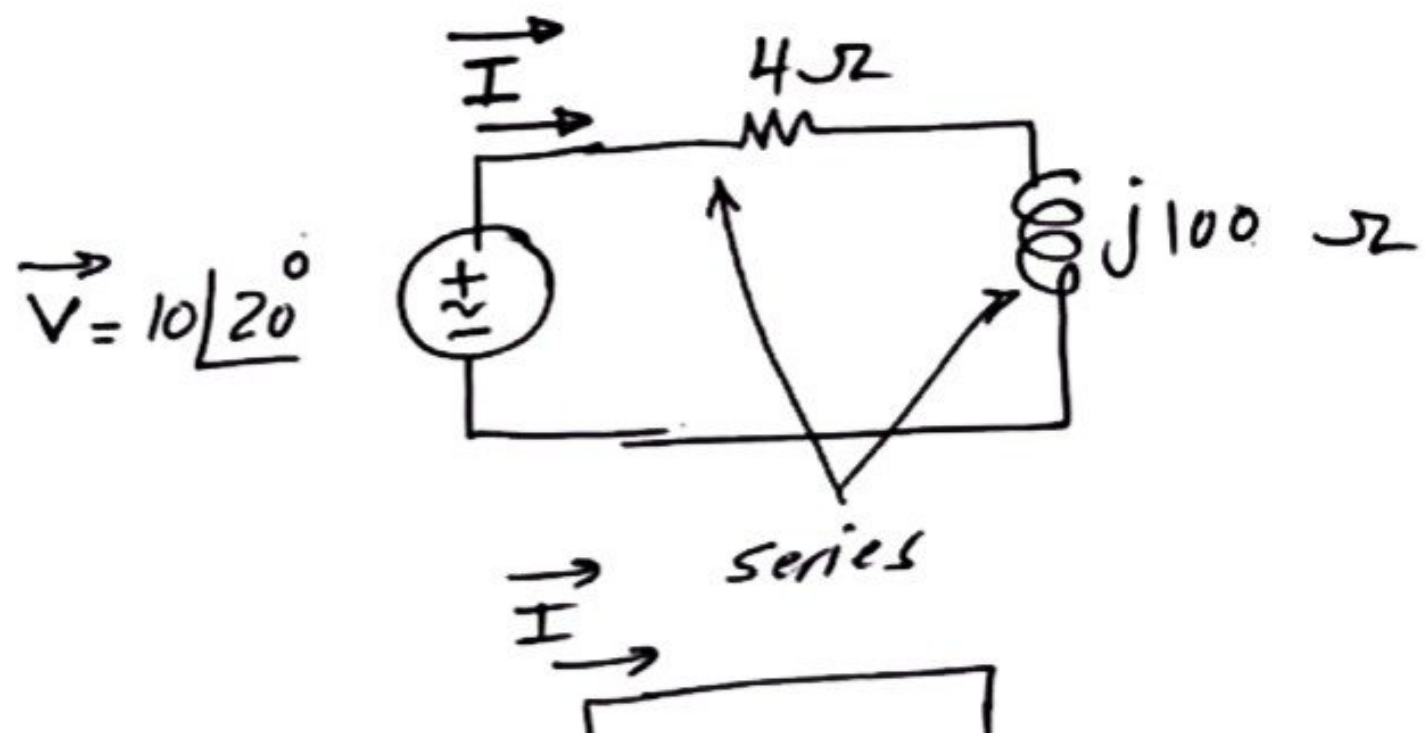
$$v(t) = 10 \cos(50t + 20^\circ) \longrightarrow \vec{V} = 10 \angle 20^\circ \text{ V}$$



$\omega = 50$


$$\vec{I} = \frac{10 \angle 20^\circ \text{ V}}{4 + j100 \ \Omega}$$

$$= 0.1 \angle -67.7^\circ \text{ A}$$

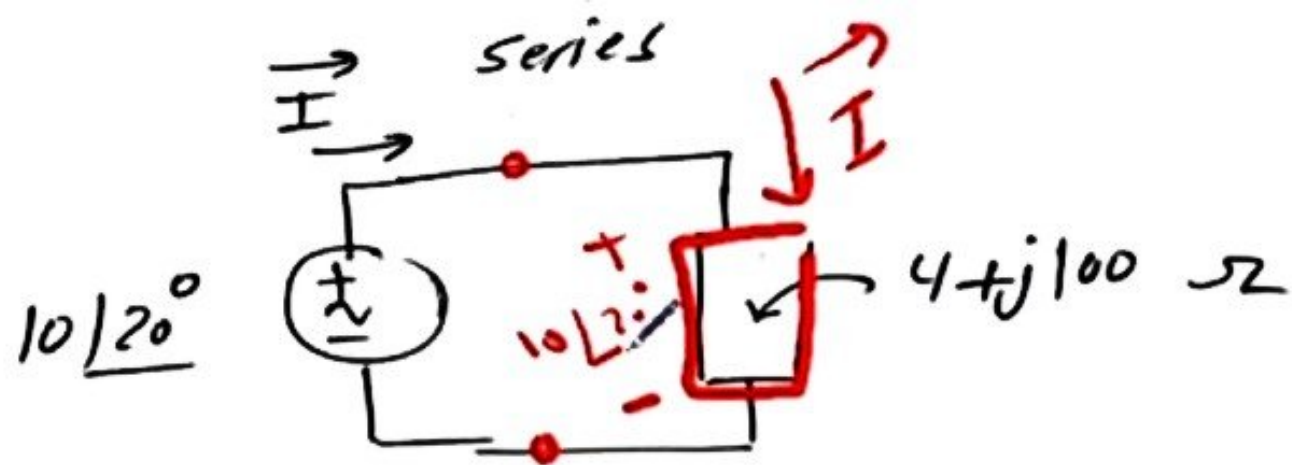


$$\Rightarrow \underline{i(t)} = 0.1 \cos(50t - 67.7^\circ) \text{ A} \checkmark$$

i lags v by 67.7°

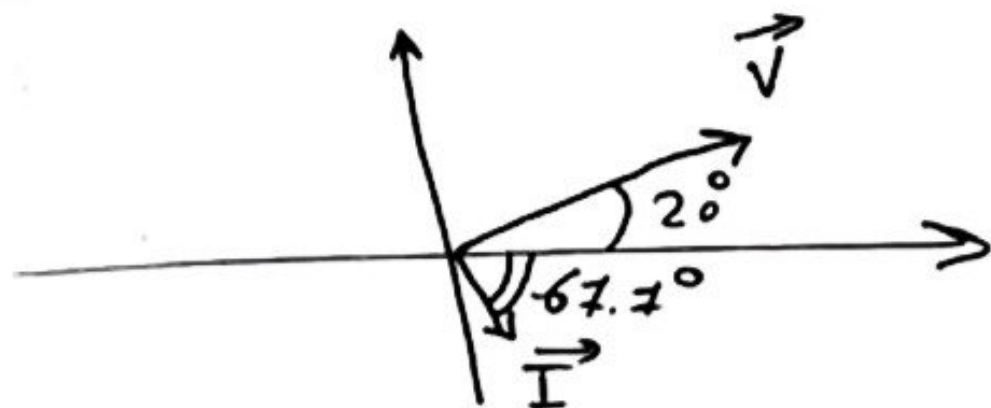


"Phasor Diagram"

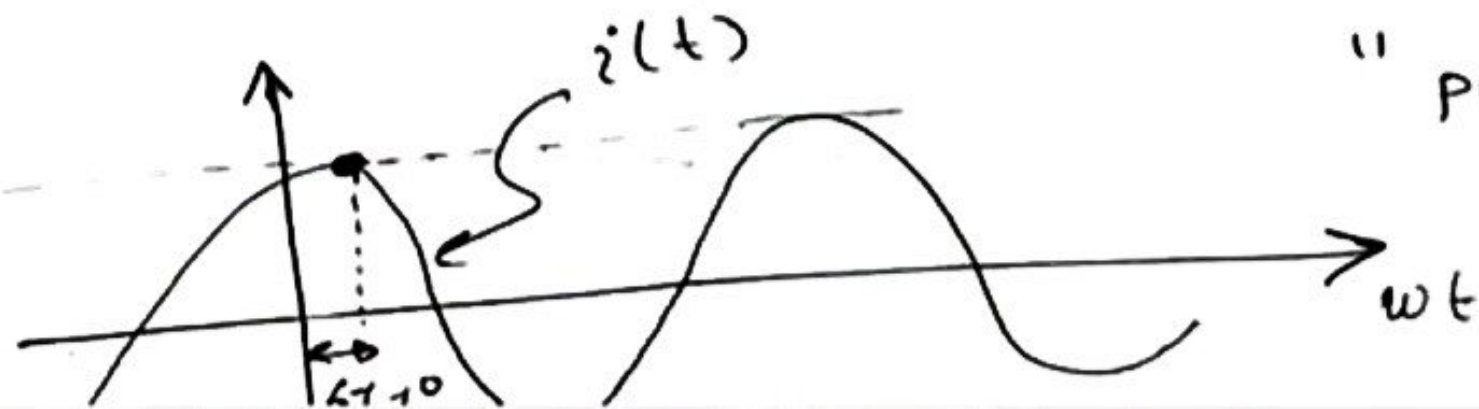

Note: In complex domain, we can apply all circuit analysis techniques we have learnt in CH#1 \rightarrow CH#5 but we deal with complex quantities.

Ex:

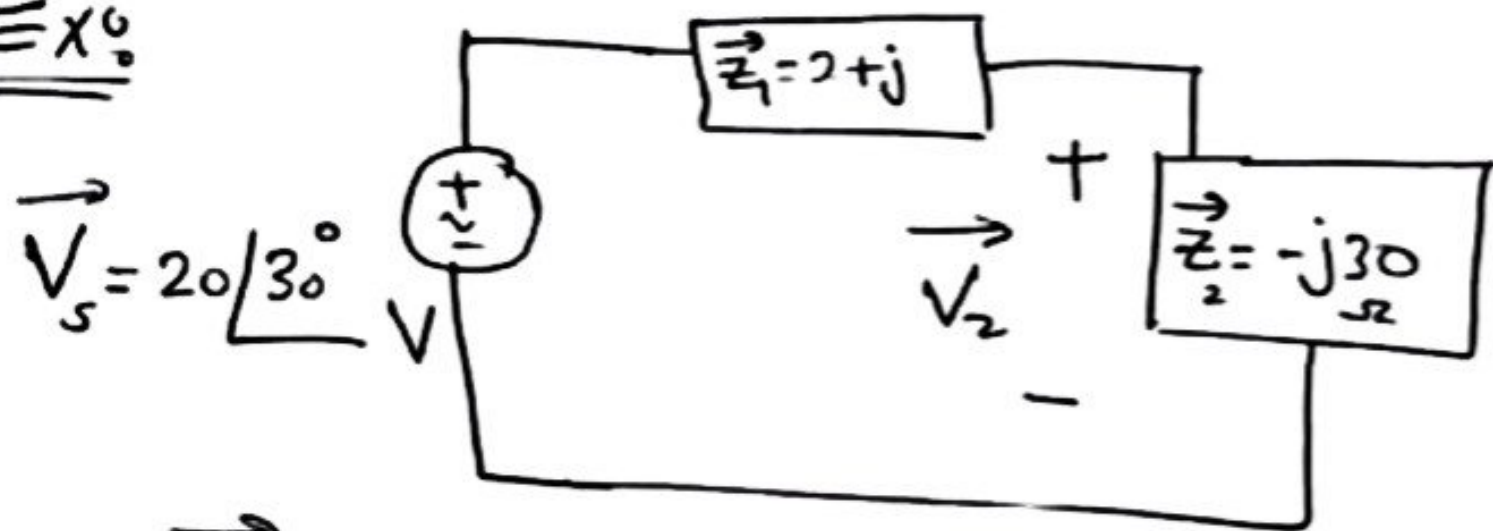


Find \vec{V}_2 ??

sol: By voltage division:

EX0
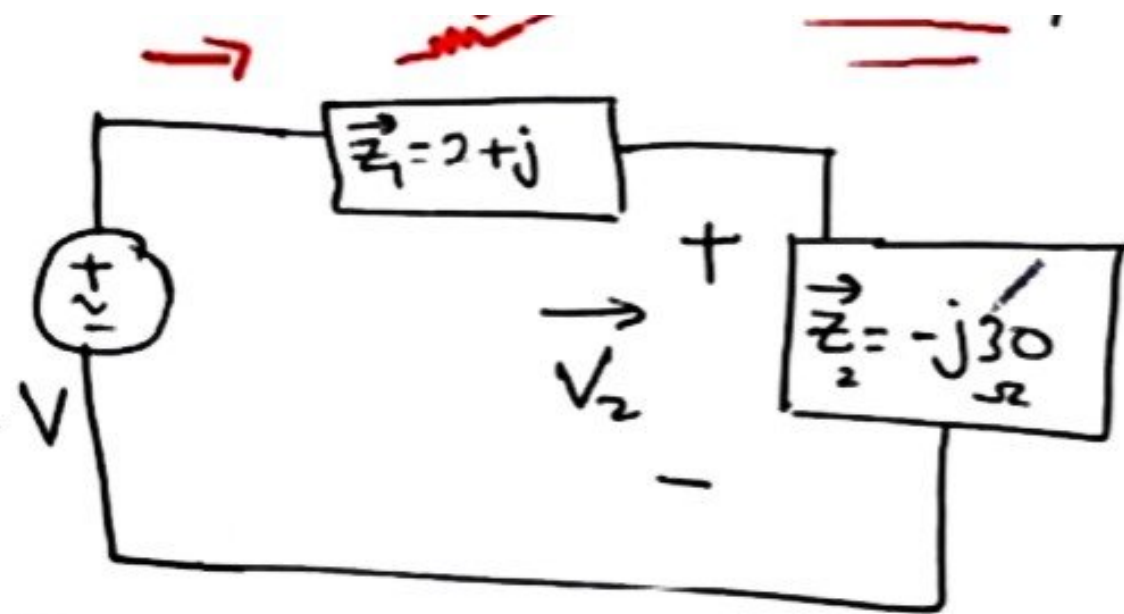
$$\vec{V}_s = 20 \angle 30^\circ \text{ V}$$



Find \vec{V}_2 ??

soln By voltage [✓] divisions

$$\vec{V}_2 = \frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} \vec{V}_s = \frac{-j30}{(2+j) + (-j30)} 20 \angle 30^\circ$$

$$\stackrel{D}{=} 19.224 + j9.34$$

$$\stackrel{D}{=} 21.374 \angle 25.91^\circ$$

$\vec{I}_s(t)$
→ $10 \angle 2$

Ex 0


EX 6

$v_s(t) = 20 \cos(100t + 10^\circ)$


" ω "
sol 6

$\vec{V}_s = 20 \angle 10^\circ$

(10)

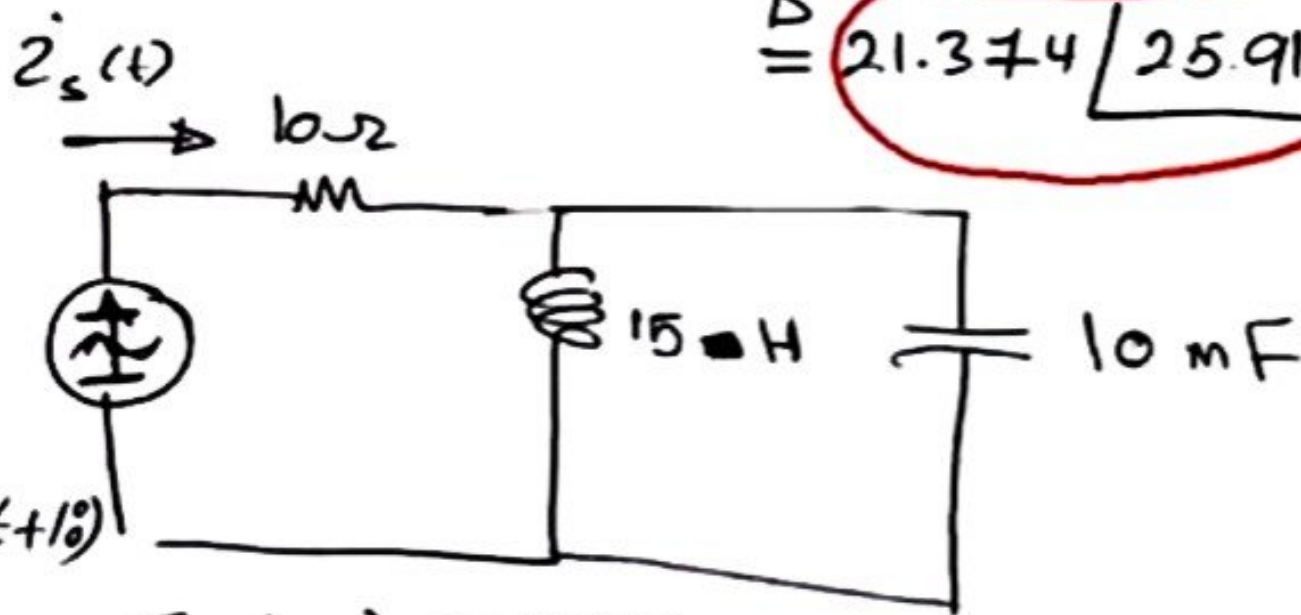

Find $i_s(t)$??

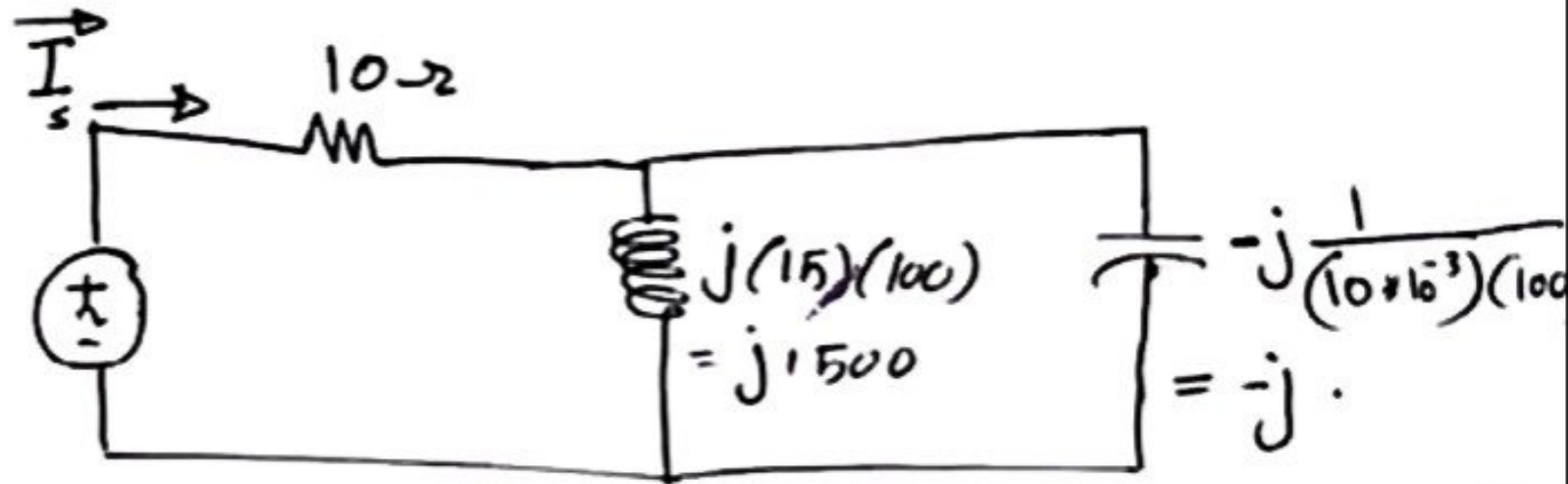

$= 21.374 \angle 25.91^\circ$



$$\vec{I}_s = \frac{\vec{V}_s}{\vec{Z}_{eq}} \quad , \quad \vec{Z}_{eq} = \underline{(-j // j1500)} + (10)$$

$$= \frac{(-j)(j1500)}{-j + j1500} + 10$$

$$\underline{= 10 - j1} \triangleq 10.05 \angle -5.71^\circ$$


Handwritten notes in red:
 \vec{I}_s
 $20 \angle 10^\circ$
 $10.05 \angle -5.71^\circ$
 $2.2 \angle 15.71^\circ$

~~$$i_s(t) = 10.05 \cos(\omega t - 5.71^\circ)$$~~

$$\Rightarrow i_s(t) = \underline{10.05 \cos(\omega t - 5.71^\circ)}$$

Exo Nodal analysis

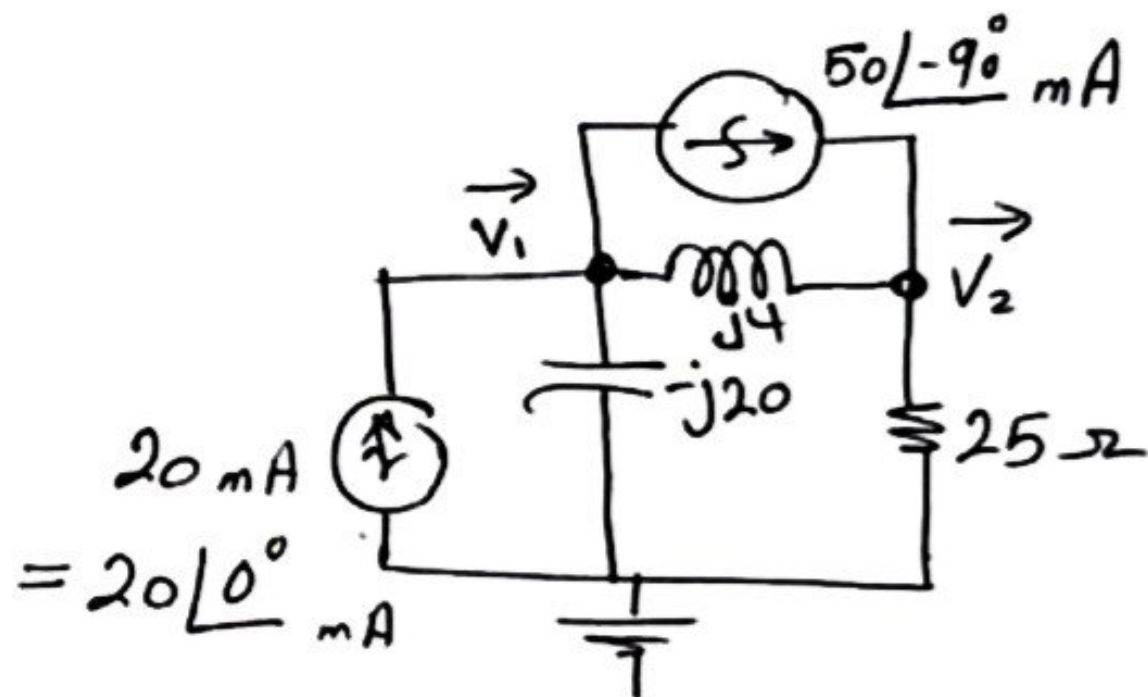Find \vec{V}_1 & \vec{V}_2
using Nodal analysis.



sol: Node ①:


$$20 \text{ mA} = \frac{\vec{V}_1 - 0}{-j20} + \frac{\vec{V}_1 - \vec{V}_2}{j4} + 50 \angle -90^\circ \text{ mA}$$

$$\Rightarrow \left(\frac{1}{-j20} + \frac{1}{j4} \right) \vec{V}_1 - \frac{1}{j4} \vec{V}_2 = 20 \text{ mA} - 50 \angle -90^\circ \text{ mA}$$

$$\boxed{-j\frac{1}{5} \vec{V}_1 - \frac{1}{j4} \vec{V}_2 = 53.85 \angle 68.19^\circ} \quad \text{--- ①}$$

Node #2: $50 \angle -90^\circ \text{ mA} = \frac{\vec{V}_2 - \vec{V}_1}{25} + \frac{\vec{V}_2 - 0}{25}$

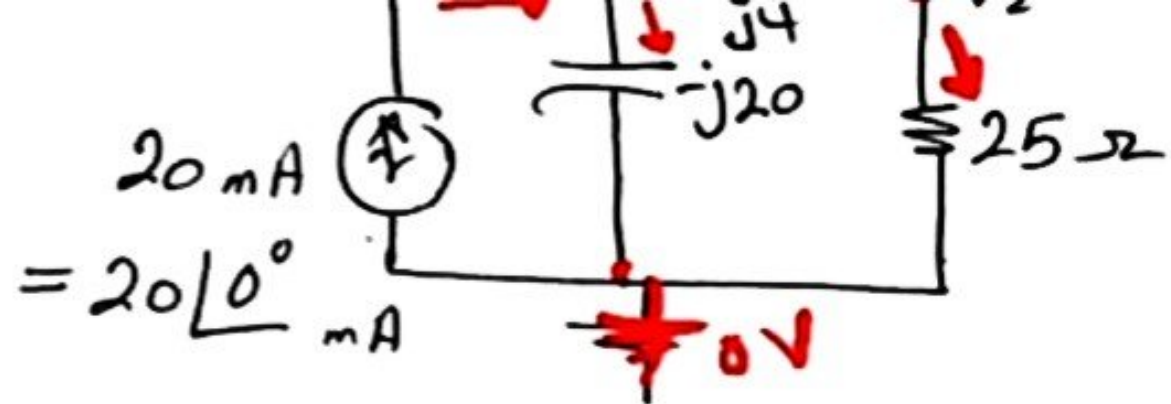Find \vec{V}_1 & \vec{V}_2
using nodal analysis.



sol: Node ①:

$$20 \text{ mA} = \frac{\vec{V}_1 - 0}{-j20} + \frac{\vec{V}_1 - \vec{V}_2}{j4} + 50\angle -90^\circ \text{ mA}$$

$$\Rightarrow \left(\frac{1}{-j20} + \frac{1}{j4} \right) \vec{V}_1 - \frac{1}{j4} \vec{V}_2 = 20 \text{ mA} - 50\angle -90^\circ \text{ mA}$$

$$\boxed{-j\frac{1}{5} \vec{V}_1 - \frac{1}{j4} \vec{V}_2 = 53.85\angle 68.19^\circ} \quad \text{①}$$

Node #2:

$$50\angle -90^\circ \text{ mA} = \frac{\vec{V}_2 - \vec{V}_1}{j4} + \frac{\vec{V}_2 - 0}{25}$$

$$\Rightarrow \boxed{j0.25\vec{V}_1 + 0.253\angle -80.91^\circ \vec{V}_2 = -50\angle -90^\circ \text{ mA}} \quad \text{②}$$

Determine current I_o in the circuit of Fig. 10.7 using mesh analysis.

Example 10.3

Applying KVL to mesh 1, we obtain

$$(8 + j10 - j2)\mathbf{I}_1 - (-j2)\mathbf{I}_2 - j10\mathbf{I}_3 = 0$$

For mesh 2,

$$(4 - j2 - j2)\mathbf{I}_2 - (-j2)\mathbf{I}_1 - (-j2)\mathbf{I}_3 + 20\angle 90^\circ = 0$$


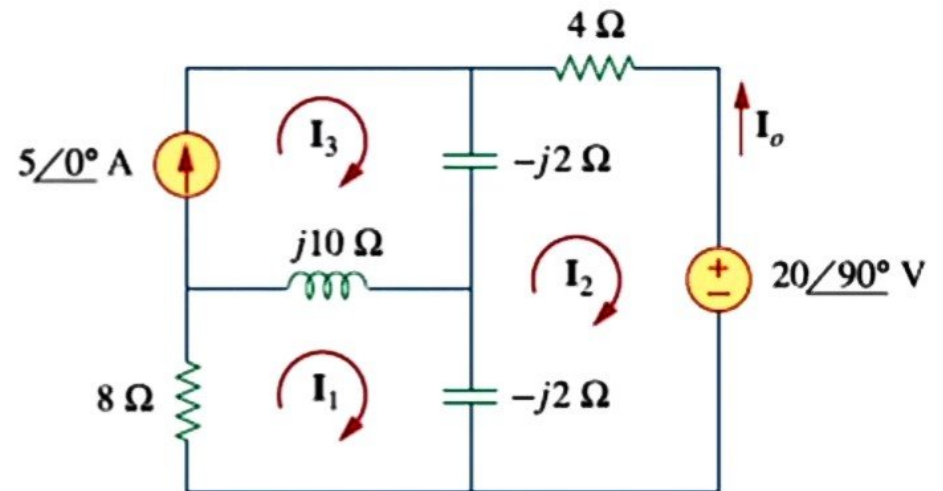



Figure 10.7
For Example 10.3.

Source Transformation
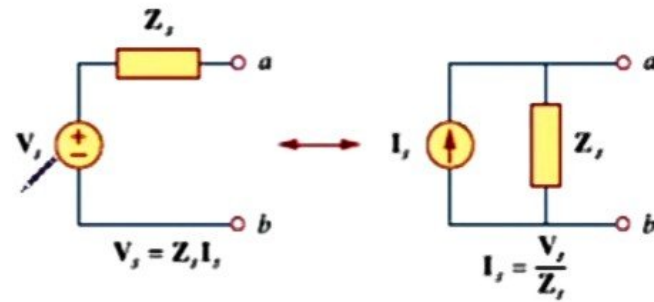
$$V_s = Z_s I_s \quad \Leftrightarrow \quad I_s = \frac{V_s}{Z_s}$$




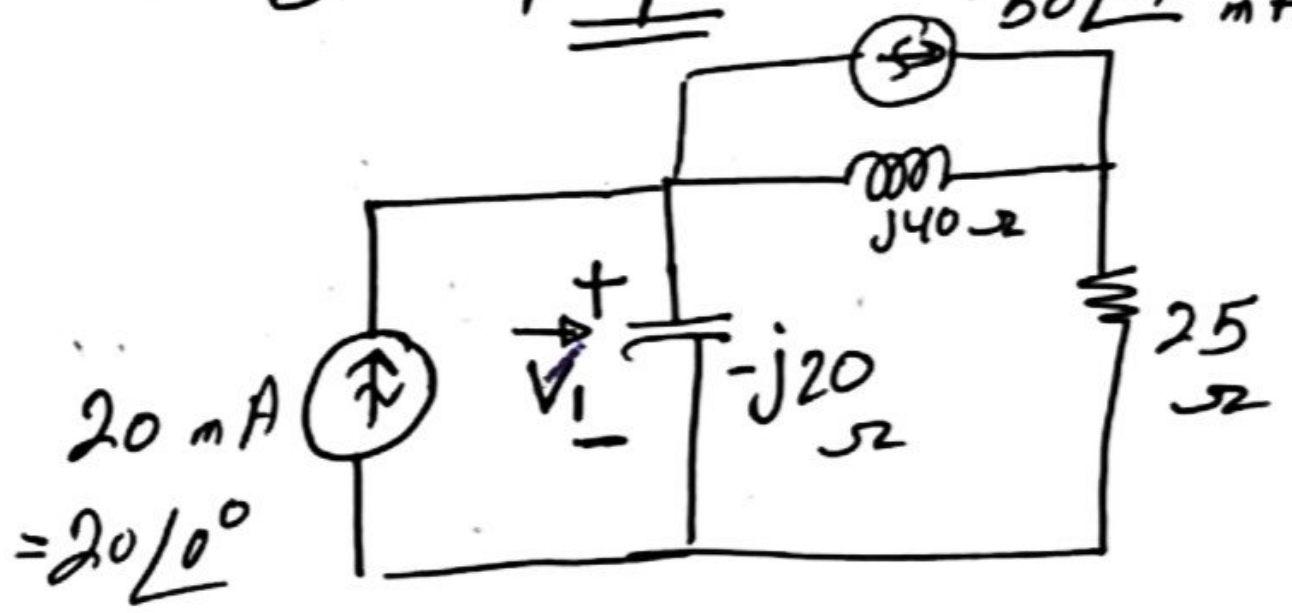
Ex: Find V_1 using superposition: $50 \angle -90^\circ \text{ mA}$



sol: $\vec{V}_1 = \vec{V}_1' + \vec{V}_1''$


\vec{V}_1' ??

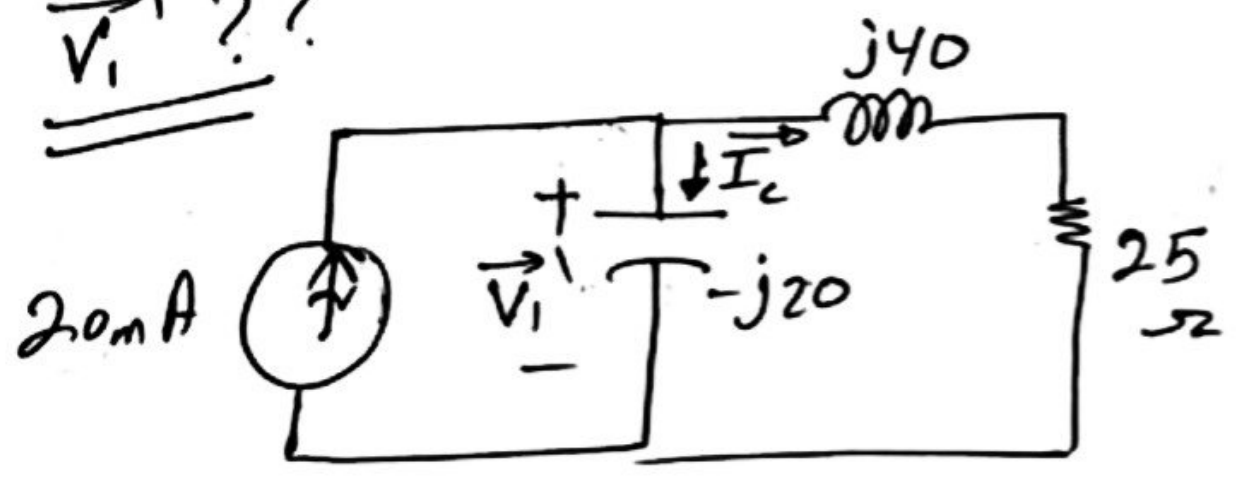

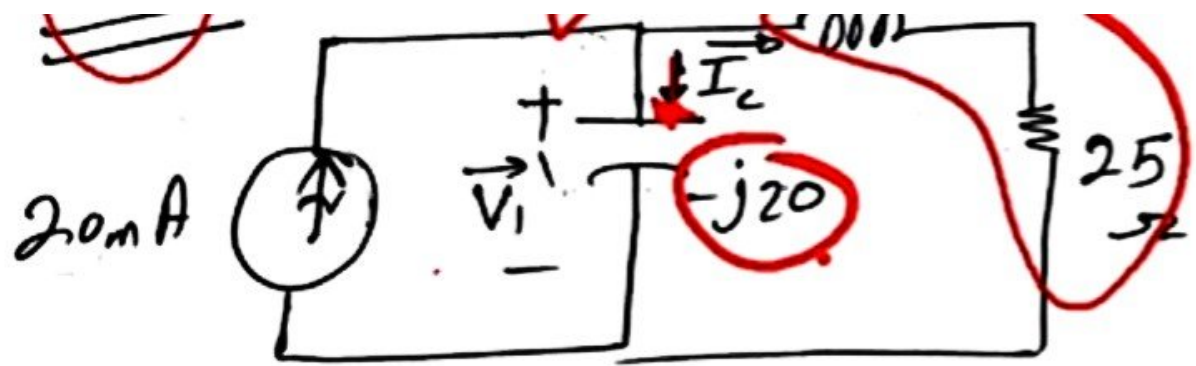

$$\vec{I}_c = \frac{(25 + j40)}{(25 + j40) - j20} 20 \text{ mA}$$

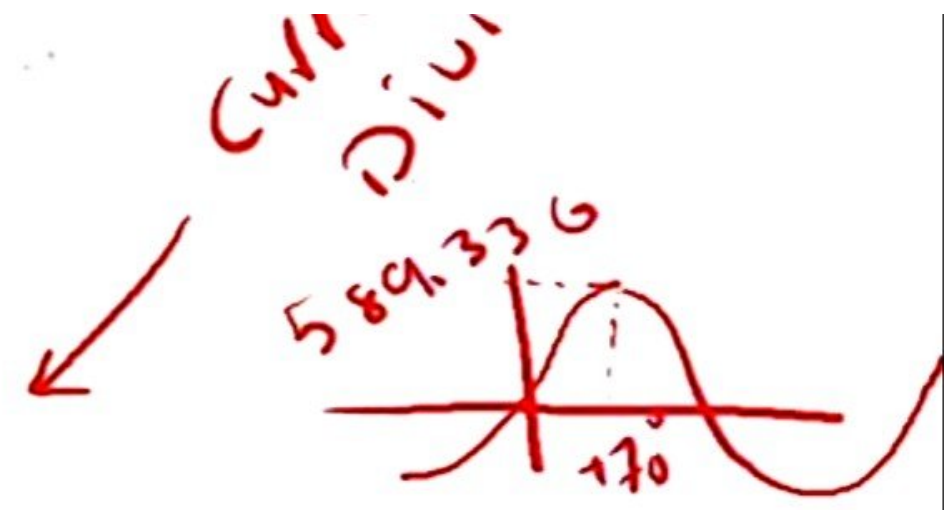
$$= 29.467 \angle 19.334^\circ \text{ mA}$$



$$\Rightarrow \vec{V}_1 = (-j20) \vec{I}_c$$

$$= 589.336 \angle -70.66^\circ \text{ mA}$$

\vec{V}_x ??

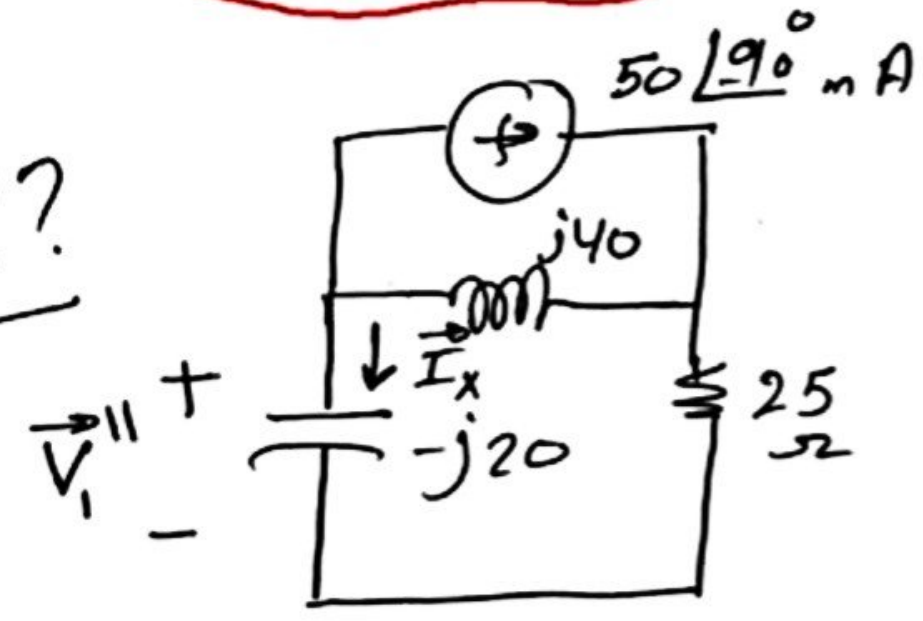


$$\vec{I}_x = \frac{(j40)(50 \angle -90^\circ) \text{ mA}}{j40 + (25 - j20)}$$

$$= \dots$$

→

Ex: For the ckt shown find the Thevenin equivalent seen to the left of a and b.

~~Then find \vec{I}_x for max power~~

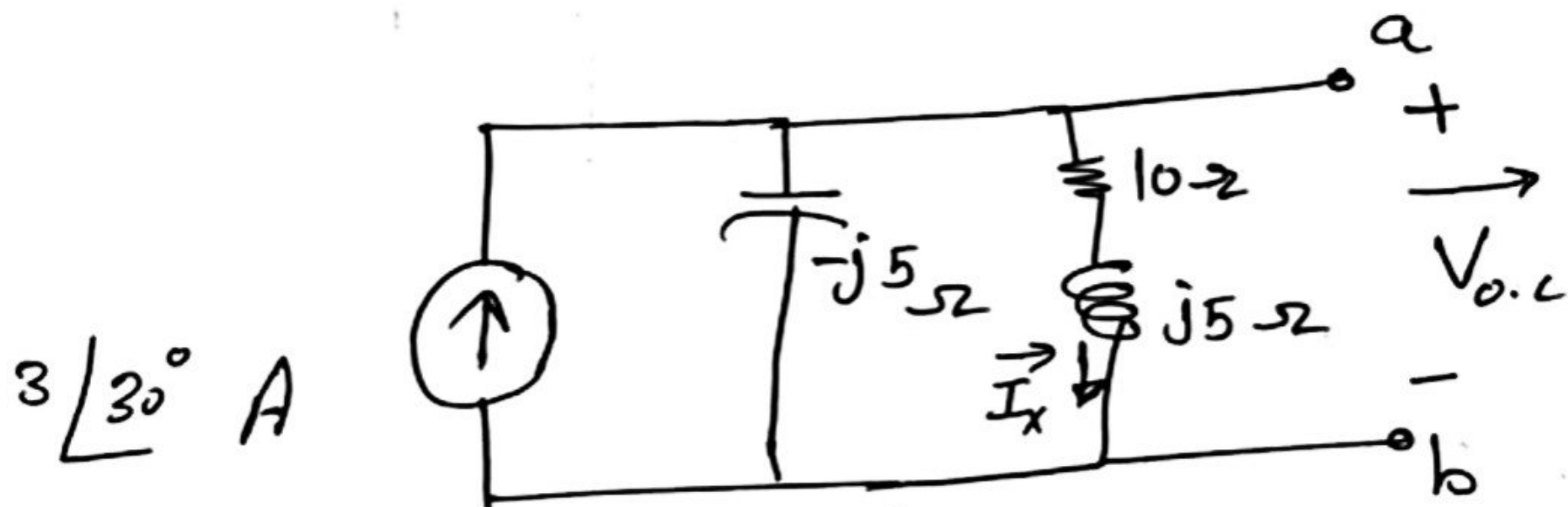


$$\vec{Z}_{th} = (-j5) \parallel (10 + j5) = \frac{(-j5)(10 + j5)}{-j5 + 10 + j5} = 2.5 - j5 \Omega$$

" Kill the current source

→

$$3 \angle 30^\circ \text{ A}$$

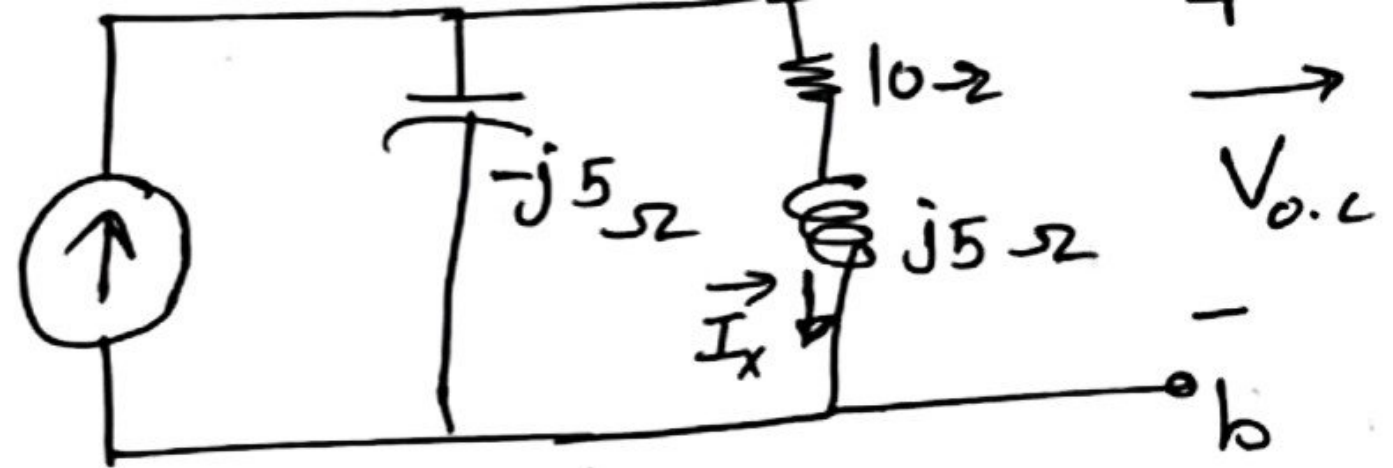

$$\vec{Z}_{th} = (-j5) \parallel (10 + j5) = \frac{(-j5)(10 + j5)}{-j5 + 10 + j5} = 2.5 - j5 \Omega$$

"kill the current source first"

$$\vec{V}_{th} = \vec{V}_{o.c} = (10 + j5) \left[\frac{-j5}{-j5 + 10 + j5} 3 \angle 30^\circ \right]$$

