

# Instantaneous and Average Power


- The instantaneous power,  $p(t)$ ,

$$\begin{aligned} p(t) &= v(t) i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i) \\ &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) \end{aligned}$$

Constant power

Sinusoidal power at  $2\omega$

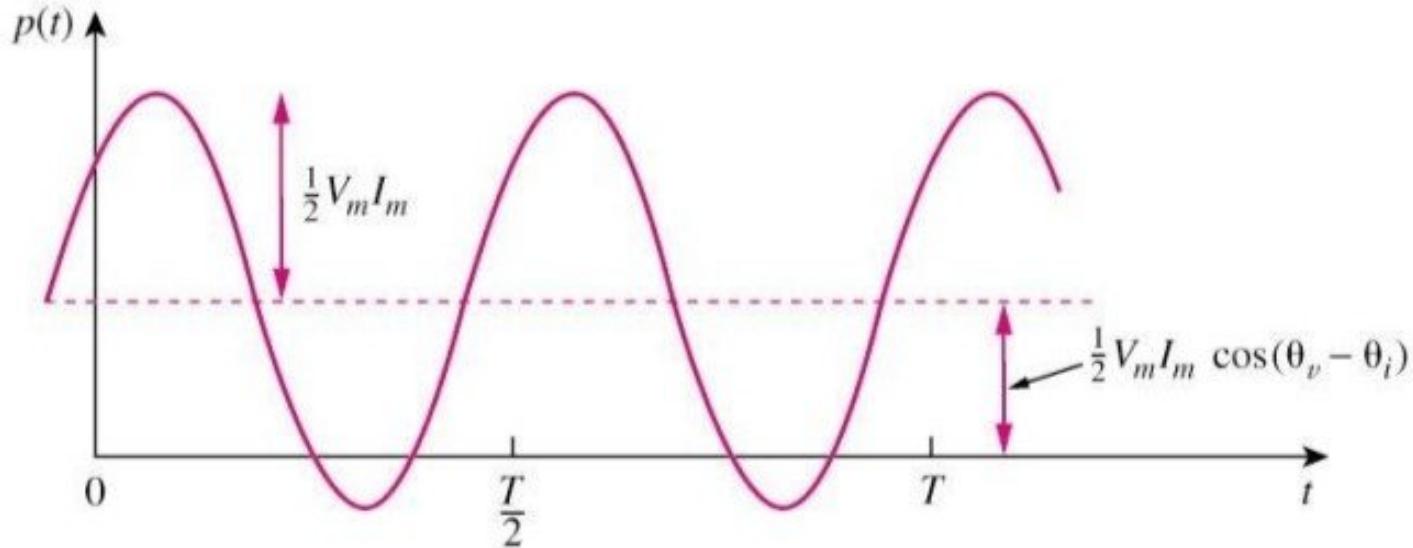The instantaneous power  $p(t)$  is composed of a constant part (DC) and a time dependent part having frequency  $2\omega$ .




$p(t) > 0$ : power is absorbed by the circuit;  $p(t) < 0$ : power is absorbed by the source.
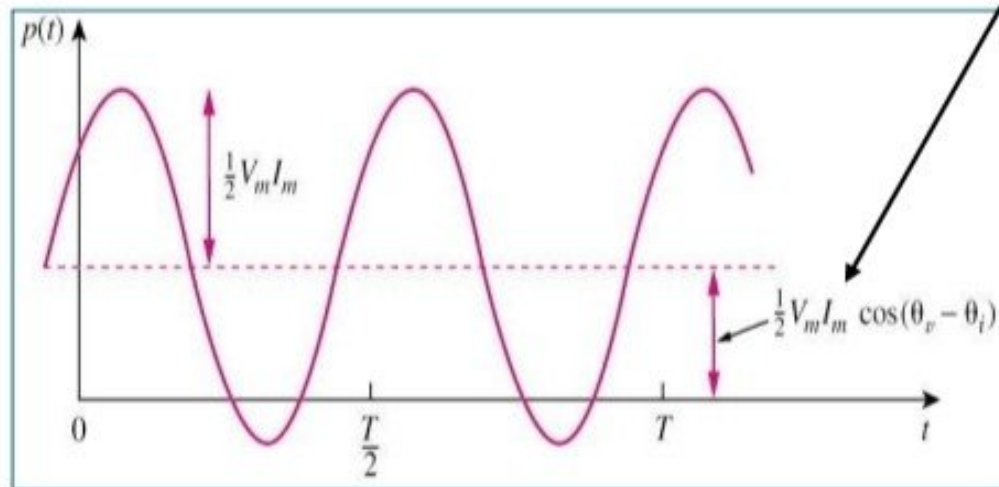
# Instantaneous and Average Power

The average power,  $P$ , is the average of the instantaneous power over one period.


$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



1.  $P$  is not time dependent.
2. When  $\theta_v = \theta_i$ , it is a purely resistive load case.
3. When  $\theta_v - \theta_i = \pm 90^\circ$ , it is a purely reactive load case.
4.  $P = 0$  means that the circuit absorbs no average power.
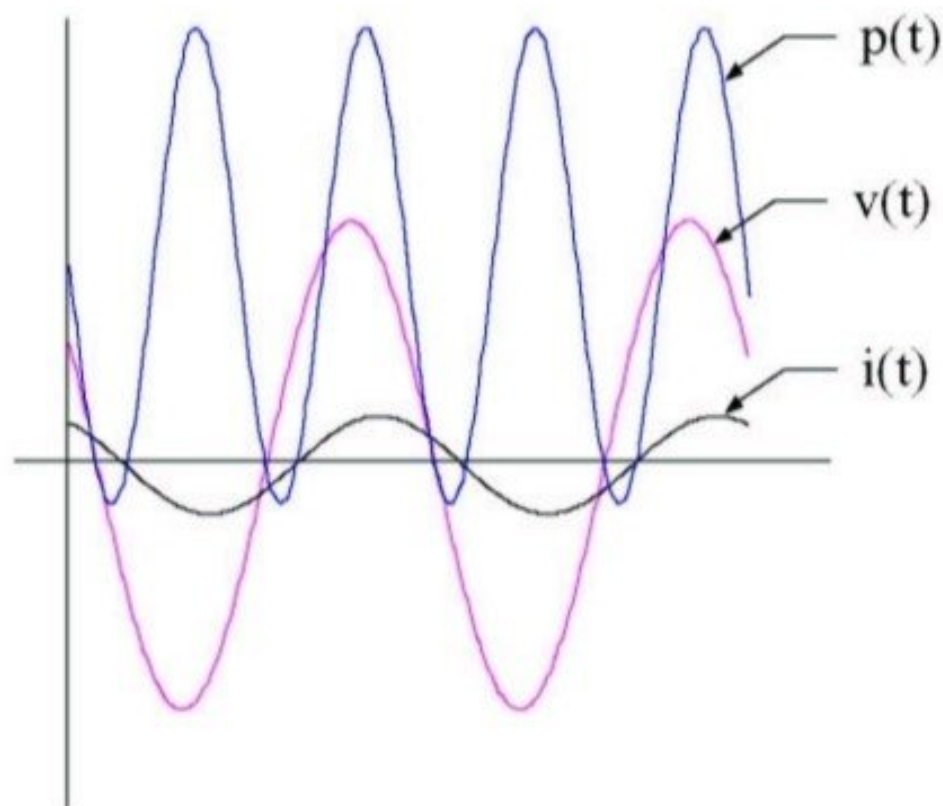
# Instantaneous Power

$$p(t) = v(t)i(t) = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2}V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$




$$v(t) = 120\sqrt{2} \cos(377t + 60^\circ)$$

$$i(t) = 24\sqrt{2} \cos(377t + 30^\circ)$$
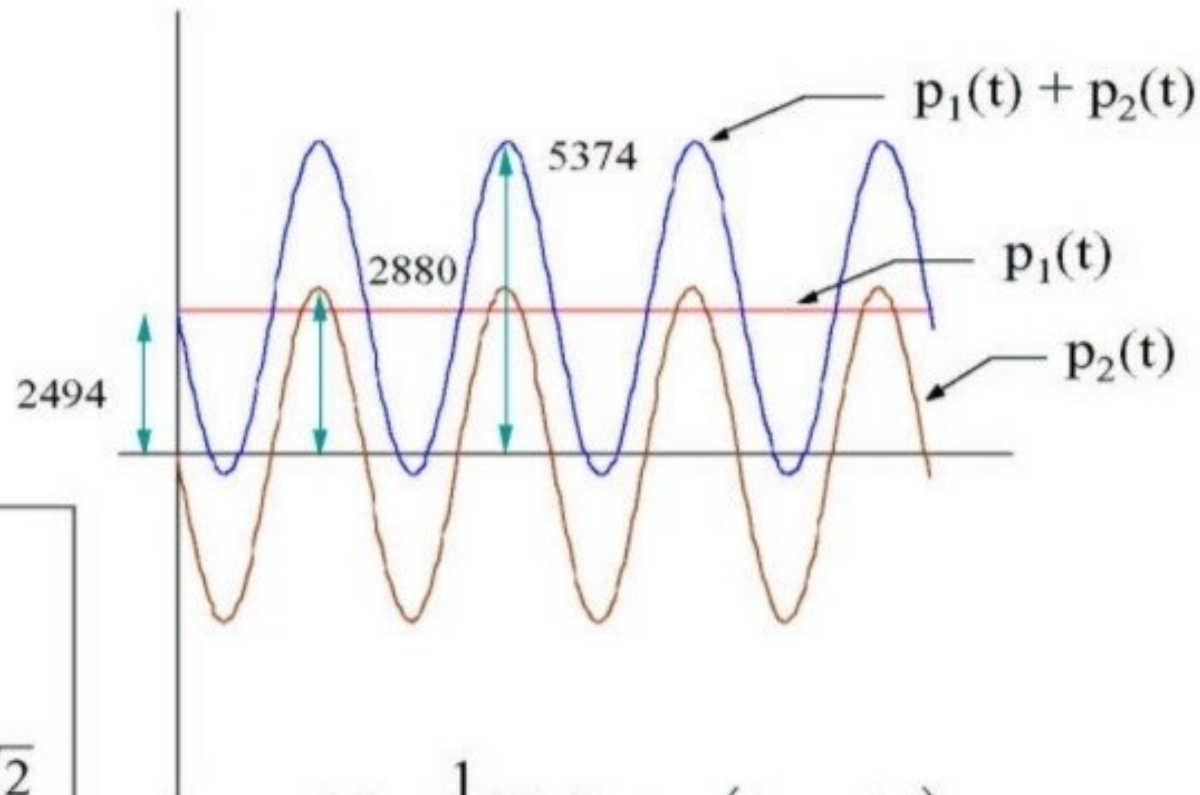
# Instantaneous Power

$$p(t) = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2}V_m I_m \cos(2\omega t + \theta_v + \theta_i) = p_1(t) + p_2(t)$$



$$\phi_V = 60^\circ$$

$$\phi_I = 30^\circ$$


$$V_m = 120\sqrt{2}$$

$$I_m = 24\sqrt{2}$$


$$p_1(t) = \frac{1}{2}V_m I_m \cos(\phi_V - \phi_I)$$

$$p_2(t) = \frac{1}{2}V_m I_m \cos(2\omega t + \phi_V + \phi_I)$$


## Resistive Circuit and Real Power

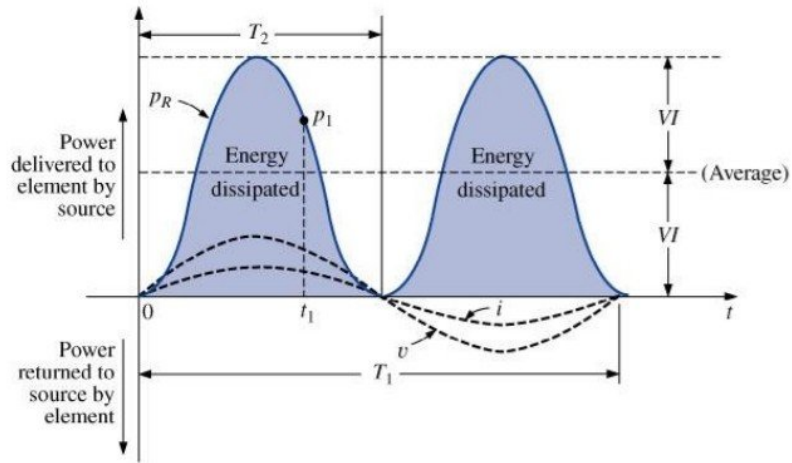

## Inductive Circuit and Reactive Power

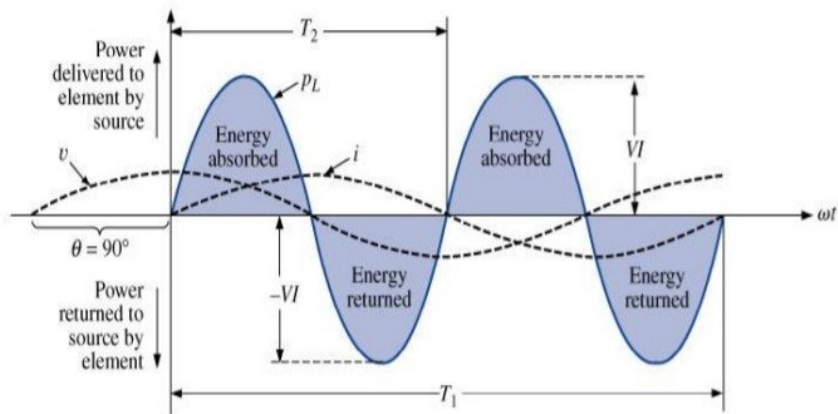

## Capacitive Circuit and Reactive Power

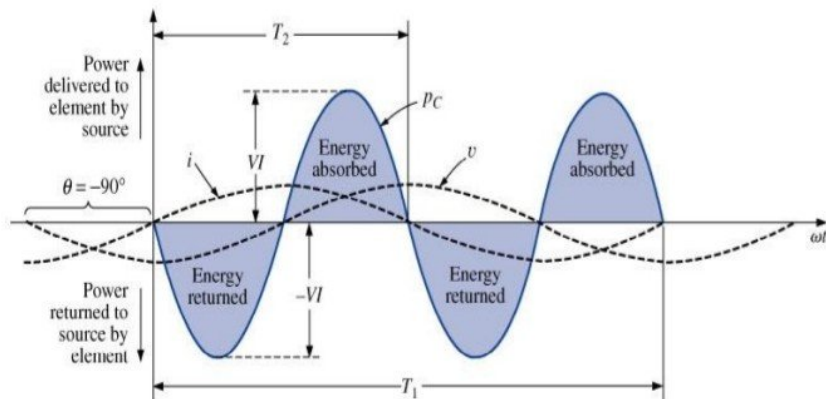

# Instantaneous and Average Power

## Example:

Calculate the instantaneous power and average power absorbed by a passive linear network if:

$$v(t) = 80 \cos (10 t + 20^\circ)$$

$$i(t) = 15 \sin (10 t + 60^\circ)$$

Answer:  $385.7 + 600 \cos(20t - 10^\circ) \text{W}, 387.5 \text{W}$

# Average Power

➤ The average power  $P$  is the average of the instantaneous power over one period .

$$p(t) = v(t)i(t) \quad \text{Instantaneous Power}$$

$$P = \frac{1}{T} \int_0^T p(t) dt \quad \text{Average Power}$$

$$v(t) = V_m \cos(\omega t + \theta_v) \quad i(t) = I_m \cos(\omega t + \theta_i)$$

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt + \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt + \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + 0 \quad (\text{Integral of a Sinusoidal}=0)$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} \text{Re}[\mathbf{VI}^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

# Average Power

## Example:

A current  $\mathbf{I} = 10 \angle 30^\circ$  flows through an impedance.


Find the average power delivered to the impedance.

$$\mathbf{Z} = 20 \angle -22^\circ \Omega$$

Answer: 927.2W

# Average Power

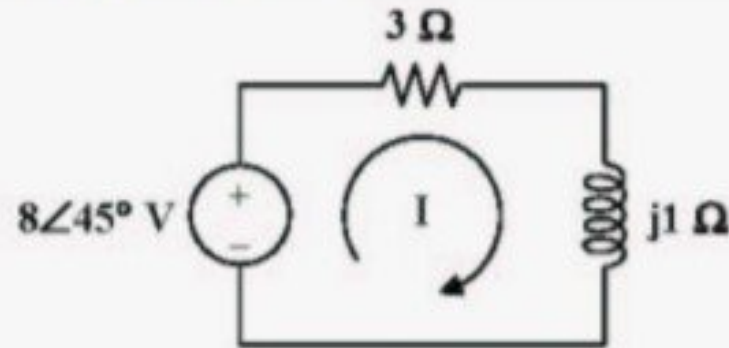**Example:** Find the average power absorbed by resistor and inductor. Find the average power supplied by the source



$$I = \frac{8\angle 45^\circ}{3+j} = 2.53\angle 26.57^\circ$$

For the resistor,  $I_R = I = 2.53\angle 26.57^\circ$      $V_R = 3I = 7.59\angle 26.57^\circ$

$$P_R = \frac{1}{2} V_m I_m = \frac{1}{2} (2.53)(7.59) = \underline{9.6 \text{ W}}$$

For the inductor,  $I_L = 2.53\angle 26.57^\circ$ ,  $V_L = jI_L = 2.53\angle (26.57^\circ + 90^\circ) = 2.53\angle 116.57^\circ$


$$P_L = \frac{1}{2} (2.53)^2 \cos(90^\circ) = \underline{0 \text{ W}}$$

The average power supplied is

$$P = \frac{1}{2} (8)(2.53) \cos(45^\circ - 26.57^\circ) = \underline{9.6 \text{ W}}$$

# Average Power

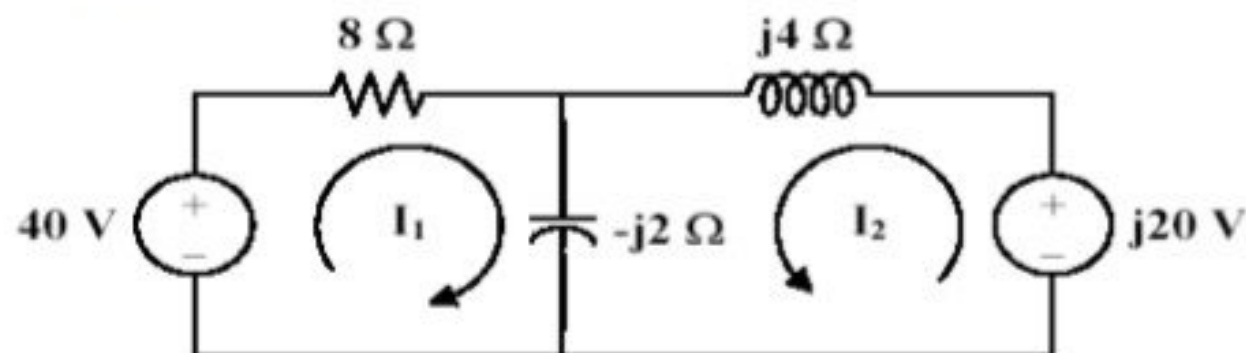Example: Calculate the average power absorbed by each of the five elements in the circuit given.



For mesh 1,

$$\begin{aligned} -40 + (8 - j2) \mathbf{I}_1 + (-j2) \mathbf{I}_2 &= 0 \\ (4 - j) \mathbf{I}_1 - j \mathbf{I}_2 &= 20 \end{aligned} \tag{1}$$

For mesh 2,

$$\begin{aligned} -j20 + (j4 - j2) \mathbf{I}_2 + (-j2) \mathbf{I}_1 &= 0 \\ -j \mathbf{I}_1 + j \mathbf{I}_2 &= j10 \end{aligned} \tag{2}$$

In matrix form,

$$\begin{bmatrix} 4 - j & -j \\ -j & j \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 20 \\ j10 \end{bmatrix}$$

$$\Delta = 2 + j4, \quad \Delta_1 = -10 + j20, \quad \Delta_2 = 10 + j60$$

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta} = 5 \angle 53.14^\circ \quad \text{and} \quad \mathbf{I}_2 = \frac{\Delta_2}{\Delta} = 13.6 \angle 17.11^\circ$$

For the 40-V voltage source,

$$\mathbf{V}_s = 40 \angle 0^\circ \quad \mathbf{I}_1 = 5 \angle 53.14^\circ$$

$$P_s = \frac{-1}{2} (40)(5) \cos(-53.14^\circ) = \underline{\underline{-60 \text{ W}}}$$

For the j20-V voltage source,

$$\mathbf{V}_s = 20 \angle 90^\circ \quad \mathbf{I}_2 = 13.6 \angle 17.11^\circ$$

$$P_s = \frac{-1}{2} (20)(13.6) \cos(90^\circ - 17.11^\circ) = \underline{\underline{-40 \text{ W}}}$$


For the resistor,

$$I = |\mathbf{I}_1| = 5 \quad V = 8|\mathbf{I}_1| = 40$$

$$P = \frac{1}{2} (40)(5) = \underline{\underline{100 \text{ W}}}$$

The average power absorbed by the inductor and capacitor is zero watts.


# Effective or RMS Value

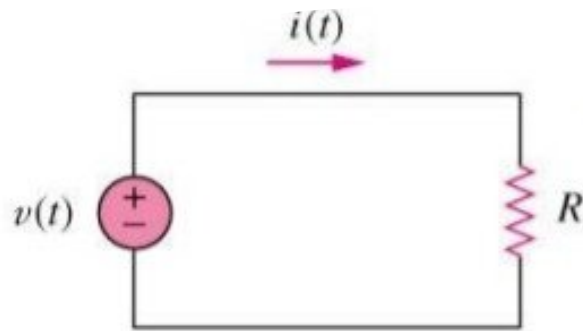

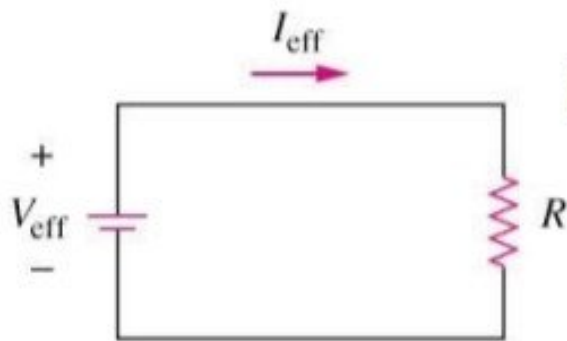a) AC circuit

The total power dissipated by  $R$  is given by:

$$P = \frac{1}{T} \int_0^T i^2 R dt = \frac{R}{T} \int_0^T i^2 dt = I_{rms}^2 R$$



b) DC circuit


Hence,  $I_{eff}$  is equal to:

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$


The rms value is a constant itself which depending on the shape of the function  $i(t)$ .

➤ The **EFFECTIVE** Value or the **Root Mean Square (RMS)** value of a periodic current is the **DC** value that delivers the same average power to a resistor as the periodic current.

# Effective or RMS Value

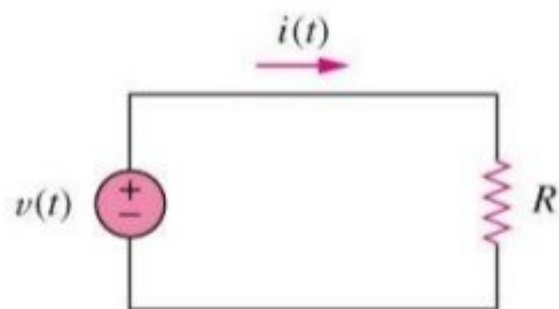

a) AC circuit

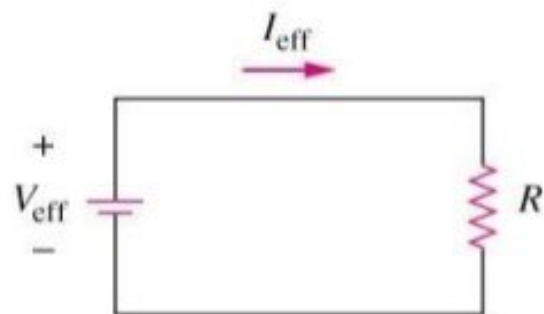

b) DC circuit

The rms value of a sinusoid  $i(t) = I_m \cos(\omega t)$  is given by:

$$I_{Rms} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2 \omega t dt} = \sqrt{\frac{I_m^2}{T} \int_0^T \frac{1}{2} (1 + \cos 2\omega t) dt} = \frac{I_m}{\sqrt{2}}$$

The average power can be written in terms of the rms values:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$


➤ The average power for resistive loads using the (RMS) value is:

$$P_R = I_{Rms}^2 R = \frac{V_{Rms}^2}{R}$$
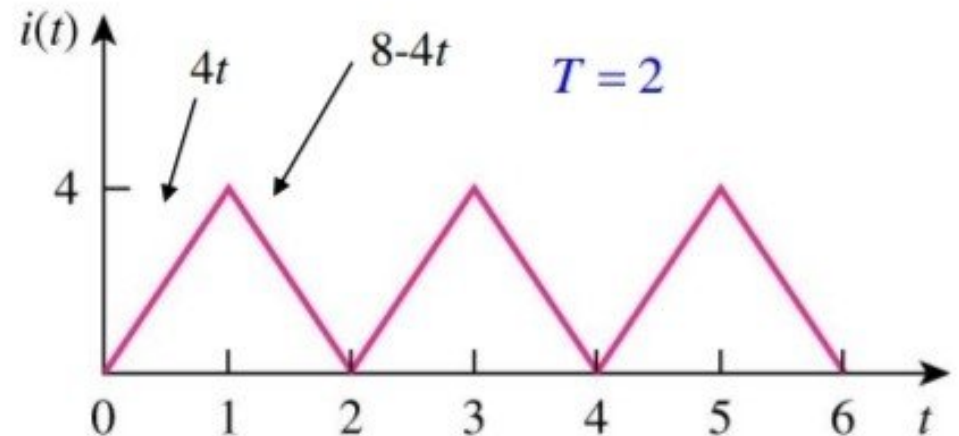
# RMS Value

Calculate the average power if the current is applied to a  $9 \Omega$  resistor.

$$i(t) = \begin{cases} 4t & 0 < t < 1 \\ 8-4t & 1 < t < 2 \end{cases}$$




$$I_{rms}^2 = \frac{1}{T} \int_0^T i^2 dt = \frac{1}{2} \left[ \int_0^1 (4t)^2 dt + \int_1^2 (8-4t)^2 dt \right]$$

$$I_{rms}^2 = \frac{16}{2} \left[ \int_0^1 t^2 dt + \int_1^2 (4-4t+t^2) dt \right] \quad I_{rms}^2 = 8 \left[ \frac{1}{3} + \left( 4t - 2t^2 + \frac{t^3}{3} \right) \Big|_1^2 \right] = \frac{16}{3}$$

$$I_{rms} = \sqrt{\frac{16}{3}} = 2.309 \text{ A}$$

$$P = I_{rms}^2 R = \left( \frac{16}{3} \right) (9) = 48 \text{ W}$$

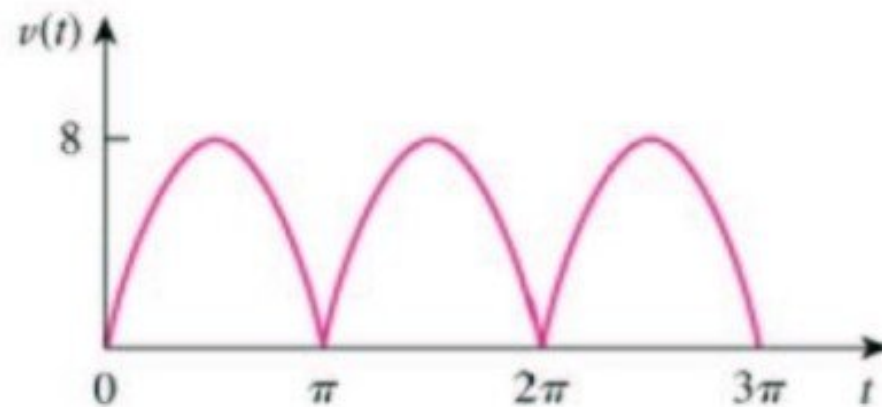**Example:** Find the RMS value of the full-wave rectified sine wave. Calculate the average power dissipated in a  $6 \Omega$  resistor.



$$T = \pi, \quad v(t) = 8 \sin(t), \quad 0 < t < \pi$$

$$V_{\text{emf}}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{\pi} \int_0^\pi (8 \sin(t))^2 dt \quad V_{\text{emf}}^2 = \frac{64}{\pi} \int_0^\pi \frac{1}{2} [1 - \cos(2t)] dt = 32$$

$$V_{\text{emf}} = \underline{\underline{5.657 \text{ V}}} \quad P = \frac{V_{\text{emf}}^2}{R} = \frac{32}{6} = \underline{\underline{5.333 \text{ W}}}$$

# Apparent Power and Power Factor

- Apparent Power,  $S$ , is the product of the r.m.s. values of voltage and current.
- It is measured in volt-amperes or VA to distinguish it from the average or real power which is measured in watts.

$$P = V_{\text{rms}} I_{\text{rms}} \cos (\theta_v - \theta_i) = S \cos (\theta_v - \theta_i)$$

**Apparent Power,  $S$**

**Power Factor, pf**

- Power factor is the cosine of the phase difference between the voltage and current. It is also the cosine of the angle of the load impedance.

# Apparent Power and Power Factor

Purely resistive load (R)	$\theta_v - \theta_i = 0, \text{ Pf} = 1$	$P/S = 1$ , all power are consumed
Purely reactive load (L or C)	$\theta_v - \theta_i = \pm 90^\circ,$ $\text{pf} = 0$	$P = 0$ , no real power consumption
Resistive and reactive load (R and L/C)	$\theta_v - \theta_i > 0$ $\theta_v - \theta_i < 0$	<ul style="list-style-type: none"> <li>• <u>Lagging</u> - inductive load</li> <li>• <u>Leading</u> - capacitive load</li> </ul>


$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{Rms} I_{Rms} \cos(\theta_v - \theta_i)$$

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

$$S = \frac{1}{2} V_m I_m = V_{Rms} I_{Rms}$$

# Power Factor

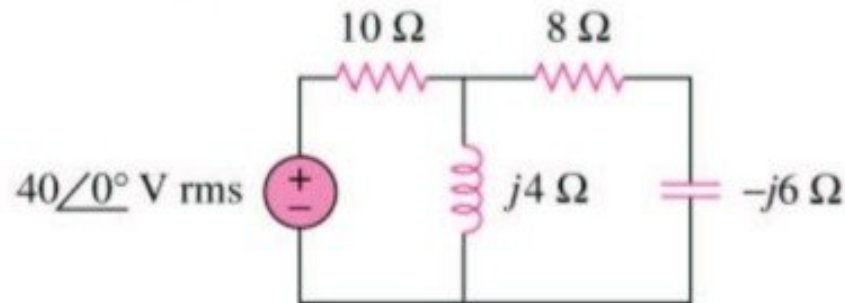**Example:** Calculate the power factor seen by the source and the average power supplied by the source



The total impedance as seen by the source is

$$\mathbf{Z} = 10 + j4 \parallel (8 - j6) = 10 + \frac{(j4)(8 - j6)}{8 - j2} \quad \mathbf{Z} = 12.69 \angle 20.62^\circ$$

The power factor is

$$\text{pf} = \cos(20.62^\circ) = \underline{\underline{\mathbf{0.936 \text{ (lagging)}}}}$$

$$\mathbf{I}_{\text{rms}} = \frac{\mathbf{V}_{\text{rms}}}{\mathbf{Z}} = \frac{40\angle 0^\circ}{12.69\angle 20.62^\circ} = 3.152 \angle -20.62^\circ$$


The average power supplied by the source is equal to the power absorbed by the load.

$$P = I_{\text{rms}}^2 R = (3.152)^2 (11.88) = 118 \text{ W}$$

$$\text{or} \quad P = V_{\text{rms}} I_{\text{rms}} \text{pf} = (40)(3.152)(0.936) = \underline{\underline{\mathbf{118 \text{ W}}}}$$
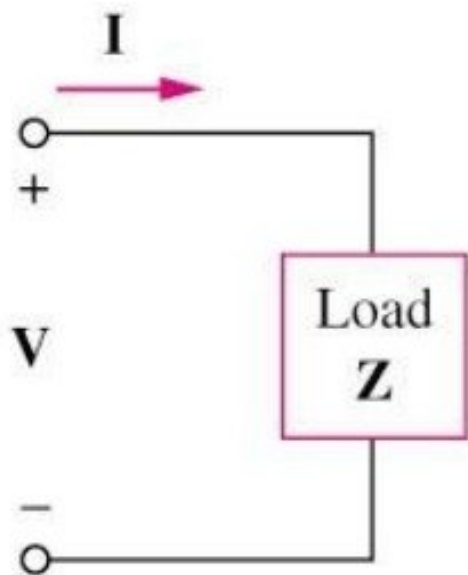
# Complex Power

- The **COMPLEX** Power **S** contains all the information pertaining to the power absorbed by a given load.
- Complex power **S** is the product of the voltage and the complex conjugate of the current:




$$\mathbf{V} = V_m \angle \theta_v$$

$$\mathbf{I} = I_m \angle \theta_i$$

$$\frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

# Complex Power

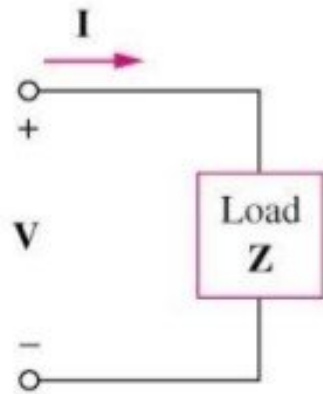

$$S = \frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$


$$\Rightarrow S = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$
$$S = \mathbf{P} + j \mathbf{Q}$$

**P:** is the average power in watts delivered to a load and it is the only useful power.

**Q:** is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR.

- $Q = 0$  for *resistive loads* (unity pf).
- $Q < 0$  for *capacitive loads* (leading pf).
- $Q > 0$  for *inductive loads* (lagging pf).

# Complex Power

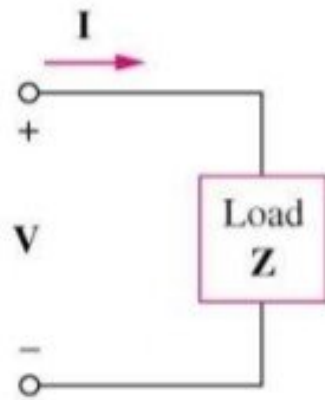

$$\Rightarrow S = \underbrace{V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)}_{\mathbf{P}} + j \underbrace{V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)}_{\mathbf{Q}}$$
$$\mathbf{S} = \mathbf{P} + j \mathbf{Q}$$

Apparent Power,  $S = |\mathbf{S}| = V_{\text{rms}} I_{\text{rms}} = \sqrt{P^2 + Q^2}$

Real power,  $P = \text{Re}(\mathbf{S}) = S \cos(\theta_v - \theta_i)$


Reactive Power,  $Q = \text{Im}(\mathbf{S}) = S \sin(\theta_v - \theta_i)$

Power factor,  $\text{pf} = P/S = \cos(\theta_v - \theta_i)$

- Real Power is the actual power dissipated by the load.
- Reactive Power is a measure of the energy exchange between source and reactive part of the load.
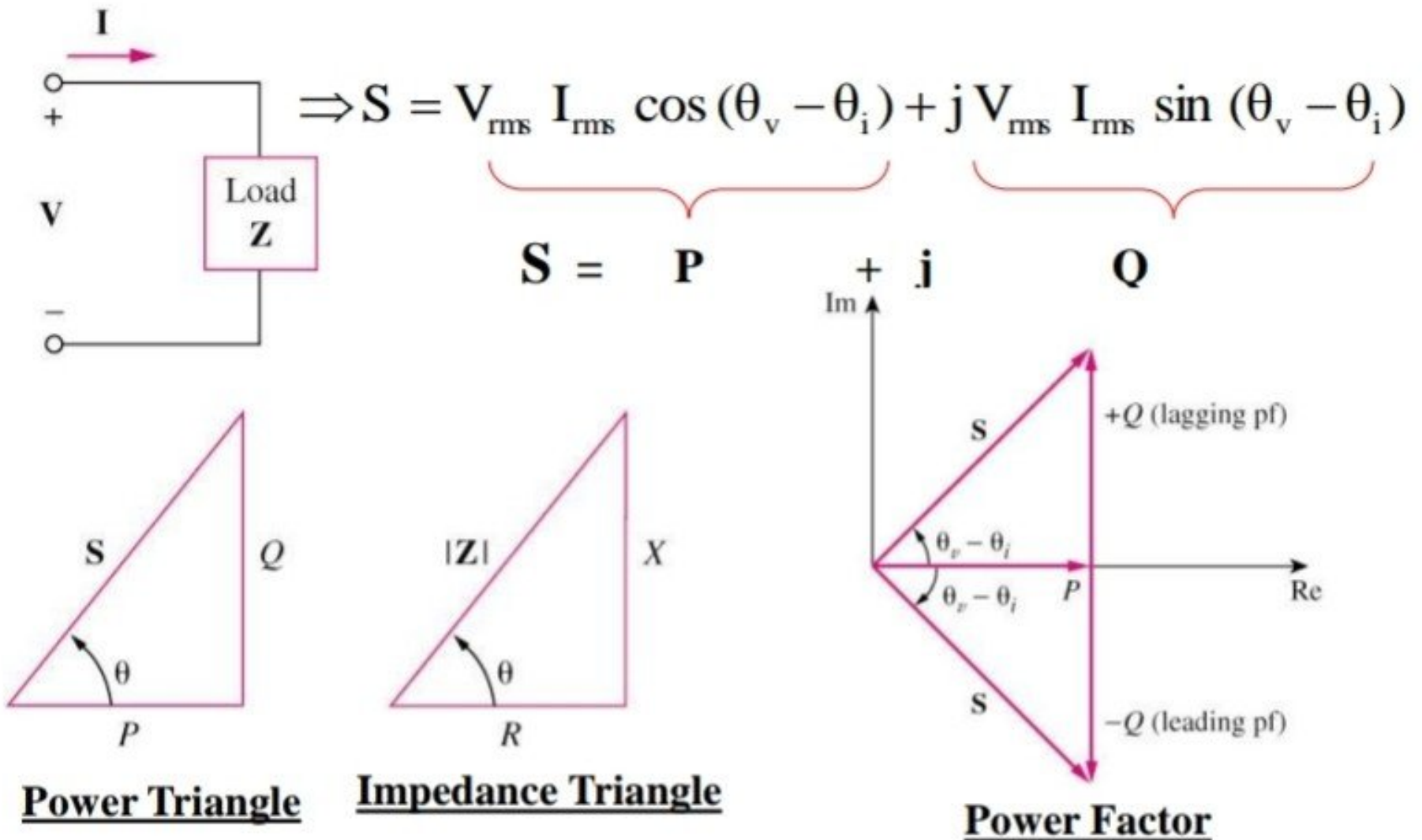
# Complex Power

➤ The COMPLEX Power is represented by the POWER TRIANGLE similar to IMPEDANCE TRIANGLE. Power triangle has four items: P, Q, S and  $\theta$ .



# Real and Reactive Powers

- The REAL Power is the only useful power delivered to the load.
- The REACTIVE Power represents the energy exchange between the source and reactive part of the load. It is being transferred back and forth between the load and the source
- The unit of Q is volt-ampere reactive (VAR)

$$\mathbf{S} = P + jQ = \text{Re}\{\mathbf{S}\} + j \text{Im}\{\mathbf{S}\}$$

=Real Power+Reactive Power

$$\mathbf{S} = I_{Rms}^2 \mathbf{Z} = I_{Rms}^2 (R + jX) = P + jQ$$

$$P = V_{Rms} I_{Rms} \cos(\theta_v - \theta_i) = \text{Re}\{\mathbf{S}\} = I_{Rms}^2 R$$

$$Q = V_{Rms} I_{Rms} \sin(\theta_v - \theta_i) = \text{Im}\{\mathbf{S}\} = I_{Rms}^2 X$$

## Complex Power

Example: Two loads are connected in parallel. Load 1 has 2 kW, pf=0.75 leading and Load 2 has 4 kW, pf=0.95 lagging. Calculate the pf of two loads and the complex power supplied by the source.

For load 1,

$$P_1 = 2000, \quad \text{pf} = 0.75 = \cos\theta_1 \longrightarrow \theta_1 = -41.41^\circ$$

$$P_1 = S_1 \cos\theta_1 \longrightarrow S_1 = \frac{P_1}{\cos\theta_1} = 2666.67$$

$$Q_1 = S_1 \sin\theta_1 = -176.85$$

$$S_1 = P_1 + jQ_1 = 2000 - j176.85 \quad (\text{leading})$$

For load 2,

$$P_2 = 4000, \quad \text{pf} = 0.95 = \cos\theta_2 \longrightarrow \theta_2 = 18.19^\circ$$

$$S_2 = \frac{P_2}{\cos\theta_2} = 4210.53$$

$$Q_2 = S_2 \sin\theta_2 = 1314.4$$

$$S_2 = P_2 + jQ_2 = 4000 + j1314.4 \quad (\text{lagging})$$



The total complex power is

$$S = S_1 + S_2 = \underline{\underline{6 - j0.4495 \text{ kVA}}}$$

$$\text{pf} = \frac{P}{|S|} = \frac{6000}{6016.18} = \underline{\underline{0.9972 \quad (\text{leading})}}$$

# Complex Power

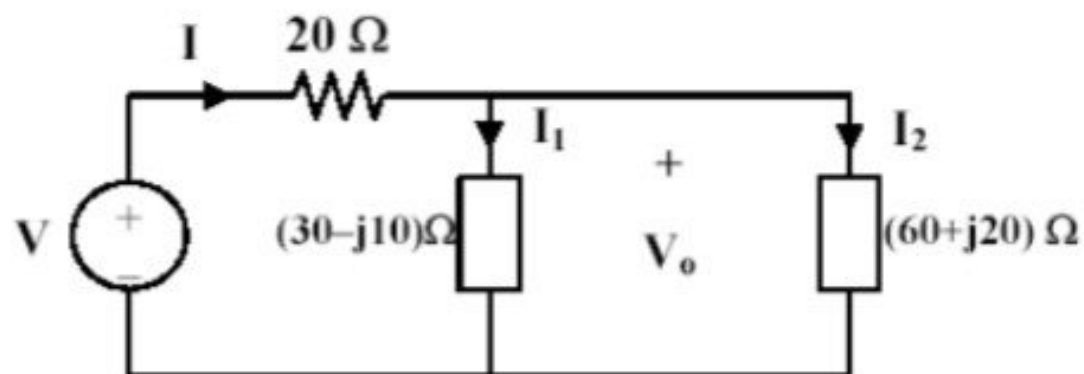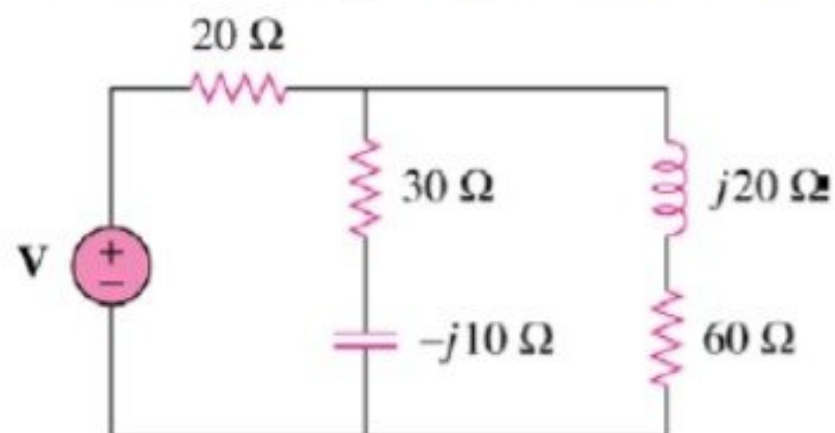**Example:** The  $60\ \Omega$  resistor absorbs 240 Watt of average power. Calculate  $V$  and the complex power of each branch. What is the total complex power?



$$P = I_2^2 R \longrightarrow I_2^2 = \frac{P}{R} = \frac{240}{60} = 4 \quad I_2 = 2 \text{ (rms)}$$

$$V_o = I_2 (60 + j20) = 120 + j40$$

$$I_1 = \frac{V_o}{30 - j10} = 3.2 + j2.4 \quad I = I_1 + I_2 = 5.2 + j2.4$$

$$V = 20I + V_o = (104 + j48) + (120 + j40)$$

$$V = 224 + j88 = \underline{\underline{240.67 \angle 21.45^\circ \text{ (rms)}}} \quad V = 224 + j88 = \underline{\underline{240.67 \angle 21.45^\circ \text{ (rms)}}}$$

## Complex Power

For the 20- $\Omega$  resistor,

$$\mathbf{V} = 20\mathbf{I} = 204 + j48 = 114.54\angle 24.8^\circ$$

$$\mathbf{I} = 5.2 + j2.4 = 5.727\angle 24.8^\circ$$

$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = (114.54\angle 24.8^\circ)(5.727\angle -24.8^\circ) \quad \mathbf{S} = \underline{\underline{656 \text{ VA}}}$$

For the (30 - j10)- $\Omega$  impedance,

$$\mathbf{V}_o = 120 + j40 = 126.5\angle 18.43^\circ$$

$$\mathbf{I}_1 = 3.2 + j2.4 = 4\angle 36.87^\circ$$

$$\mathbf{S}_1 = \mathbf{V}_o\mathbf{I}_1^* = (126.5\angle 18.43^\circ)(4\angle -36.87^\circ) \quad \mathbf{S}_1 = 506\angle -18.44^\circ = \underline{\underline{480 - j160 \text{ VA}}}$$

For the (60 + j20)- $\Omega$  impedance,  $\mathbf{I}_2 = 2\angle 0^\circ$

$$\mathbf{S}_2 = \mathbf{V}_o\mathbf{I}_2^* = (126.5\angle 18.43^\circ)(2\angle -0^\circ) \quad \mathbf{S}_2 = 253\angle 18.43^\circ = \underline{\underline{240 + j80 \text{ VA}}}$$

The overall complex power supplied by the source is


$$\mathbf{S}_T = \mathbf{V}\mathbf{I}^* = (240.67\angle 21.45^\circ)(5.727\angle -24.8^\circ)$$

$$\mathbf{S}_T = 1378.3\angle -3.35^\circ = \underline{\underline{1376 - j80 \text{ VA}}}$$

# Complex Power

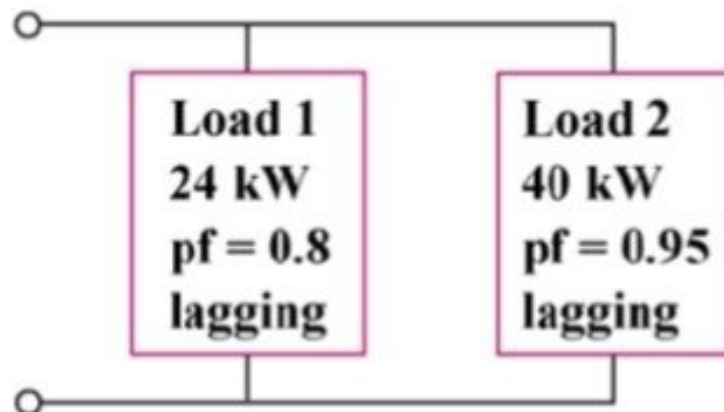**Example:** A  $120\text{-V}_{\text{rms}}$  60-Hz source supplies two loads connected in parallel, as shown below.

- Find the power factor of the parallel combination.
- Calculate the value of the capacitance connected in parallel that will raise the power factor to unity.



**Solution:**

Chapter 11, Solution 74.

$$(a) \quad \theta_1 = \cos^{-1}(0.8) = 36.87^\circ \quad S_1 = \frac{P_1}{\cos\theta_1} = \frac{24}{0.8} = 30 \text{ kVA}$$

$$Q_1 = S_1 \sin\theta_1 = (30)(0.6) = 18 \text{ kVAR} \quad S_1 = 24 + j18 \text{ kVA}$$

$$\theta_2 = \cos^{-1}(0.95) = 18.19^\circ \quad S_2 = \frac{P_2}{\cos\theta_2} = \frac{40}{0.95} = 42.105 \text{ kVA}$$

$$Q_2 = S_2 \sin\theta_2 = 13.144 \text{ kVAR} \quad S_2 = 40 + j13.144 \text{ kVA}$$

## Complex Power

$$(a) \quad \theta_1 = \cos^{-1}(0.8) = 36.87^\circ \quad S_1 = \frac{P_1}{\cos\theta_1} = \frac{24}{0.8} = 30 \text{ kVA}$$

$$Q_1 = S_1 \sin\theta_1 = (30)(0.6) = 18 \text{ kVAR} \quad \mathbf{S_1 = 24 + j18 \text{ kVA}}$$

$$\theta_2 = \cos^{-1}(0.95) = 18.19^\circ \quad S_2 = \frac{P_2}{\cos\theta_2} = \frac{40}{0.95} = 42.105 \text{ kVA}$$

$$Q_2 = S_2 \sin\theta_2 = 13.144 \text{ kVAR} \quad \mathbf{S_2 = 40 + j13.144 \text{ kVA}}$$

$$\mathbf{S = S_1 + S_2 = 64 + j31.144 \text{ kVA}}$$


$$\theta = \tan^{-1}\left(\frac{31.144}{64}\right) = 25.95^\circ \quad \text{pf} = \cos\theta = \mathbf{\underline{0.8992 \text{ (lagging)}}$$

$$(b) \quad \theta_2 = 25.95^\circ, \quad \theta_1 = 0^\circ$$


$$Q_c = P[\tan\theta_2 - \tan\theta_1] = 64[\tan(25.95^\circ) - 0] = 31.144 \text{ kVAR}$$

$$C = \frac{Q_c}{\omega V_{\text{rms}}^2} = \frac{31,144}{(2\pi)(60)(120)^2} = \mathbf{\underline{5.74 \text{ mF}}}$$

# Use of Power Triangles

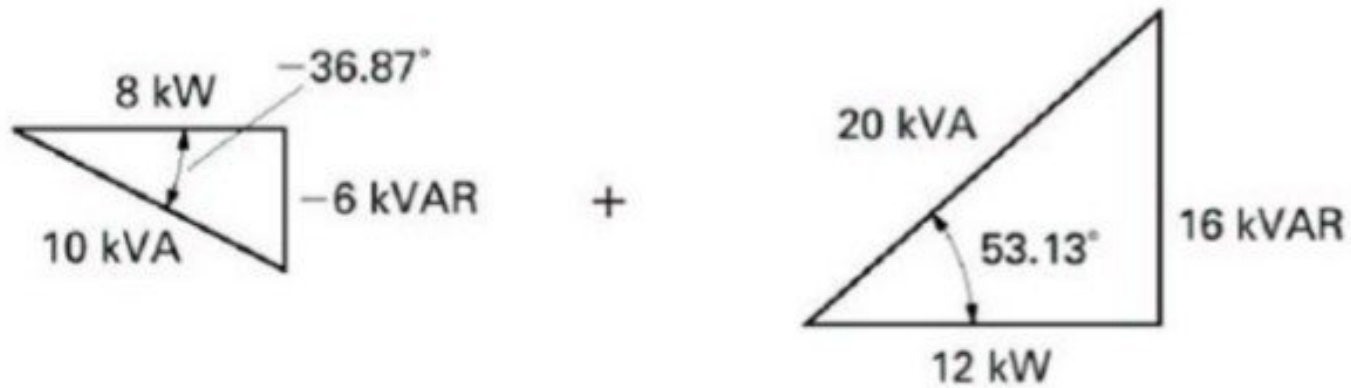

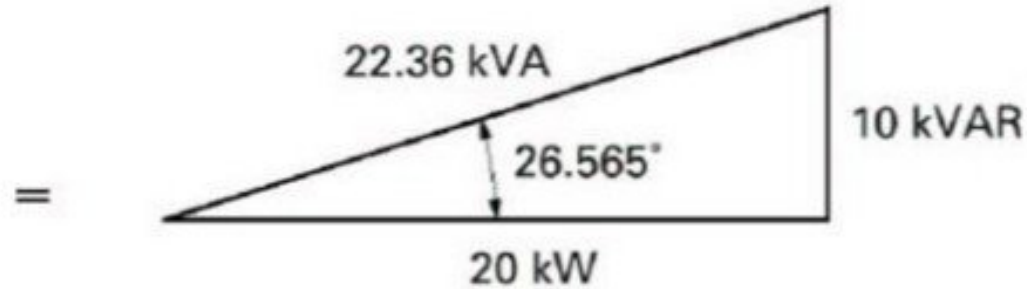
$$S = P + jQ = S_1 + S_2 = (P_1 + P_2) + j(Q_1 + Q_2)$$



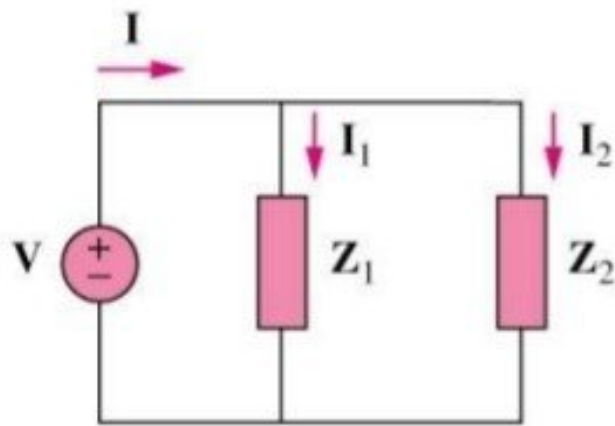
# Conservation of AC Power

➤ The complex real, and reactive powers of the sources equal the respective sums of the complex, real, and reactive powers of the individual loads.



(a)


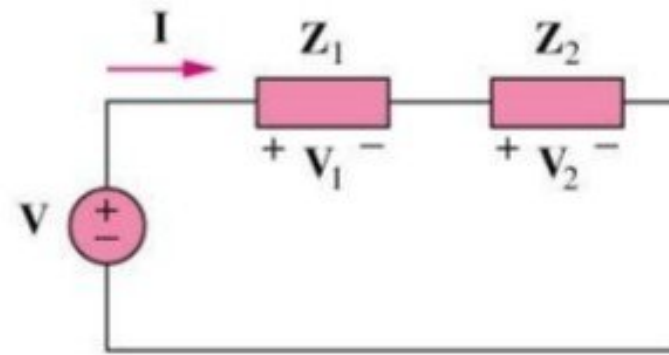


(b)

For parallel or series connection:

$$\mathbf{S} = \mathbf{V}_1 \mathbf{I}_1^* + \mathbf{V}_2 \mathbf{I}_2^* + \cdots + \mathbf{V}_N \mathbf{I}_N^*$$
$$\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 + \cdots + \mathbf{S}_N$$

## Example of Complex Power Balance

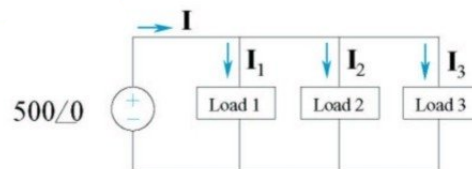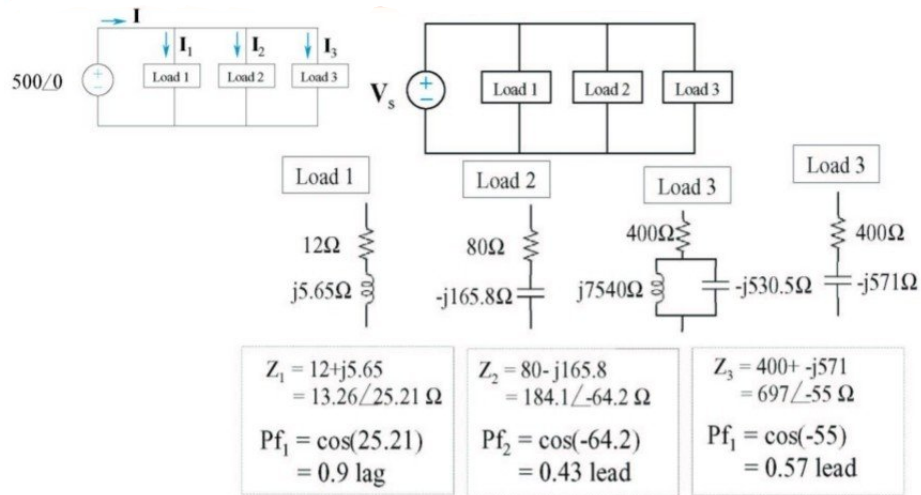


$$\mathbf{I}_1 = \frac{500 \angle 0^\circ}{13.26 \angle 25.21^\circ} = 37.7 \angle -25.21^\circ = 34.11 - j16.06$$

$$\mathbf{I}_2 = \frac{500 \angle 0^\circ}{184.1 \angle -64.2^\circ} = 2.72 \angle 64.2^\circ = 1.18 + j2.45$$

$$\mathbf{I}_3 = \frac{500 \angle 0^\circ}{697 \angle -55^\circ} = 0.72 \angle 55^\circ = 0.41 + j0.59$$

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = 35.7 - j13.02 = 38 \angle -20^\circ \text{ A}$$
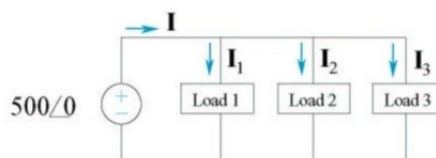
$$\text{Combined Pf} = \cos(20) = 0.94 \text{ lag}$$



$$\mathbf{S}_1 = \hat{V}_1 \hat{I}_1^* = 500 \cdot 37.7 \angle 25.21^\circ = 18850 \angle 25.21^\circ = 17055 + j8029 \text{ VA}$$

$$\mathbf{S}_2 = \hat{V}_2 \hat{I}_2^* = 500 \cdot 2.72 \angle -64.2^\circ = 1360 \angle -64.2^\circ = 592 - j1224 \text{ VA}$$

$$\mathbf{S}_3 = \hat{V}_3 \hat{I}_3^* = 500 \cdot 0.72 \angle -55^\circ = 360 \angle -55^\circ = 207 - j295 \text{ VA}$$


$$\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 + \mathbf{S}_3 = 17854 - j6510 = 19000 \angle -20^\circ \text{ VA}$$

$$\text{Check: } \mathbf{S} = \hat{V} \hat{I}^* = 500 \cdot 38 \angle -20^\circ = 19000 \angle -20^\circ \text{ VA}$$

**Complex power is Conserved**


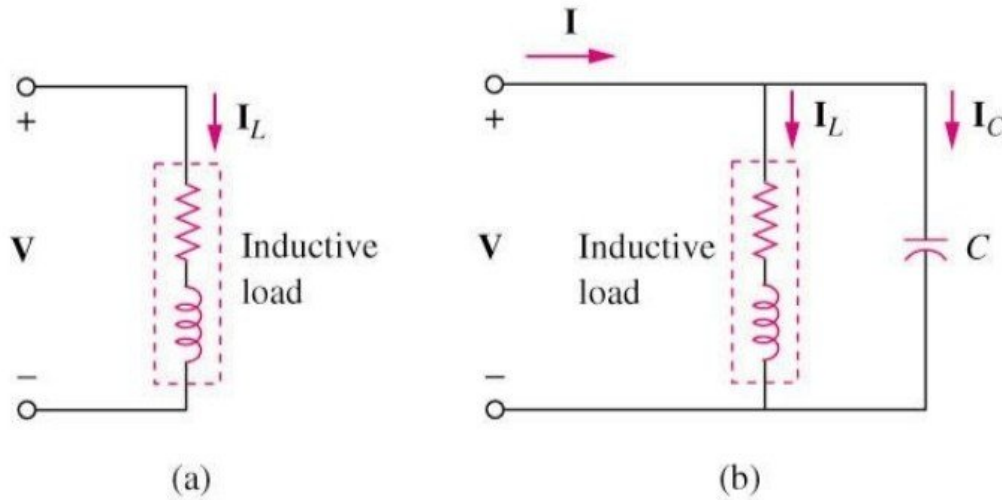
# Power Factor Correction

**Power factor correction** is the process of increasing the **power factor** without altering the voltage or current to the original load.



**Power factor correction** is necessary for economic reason.

# Power Factor Correction

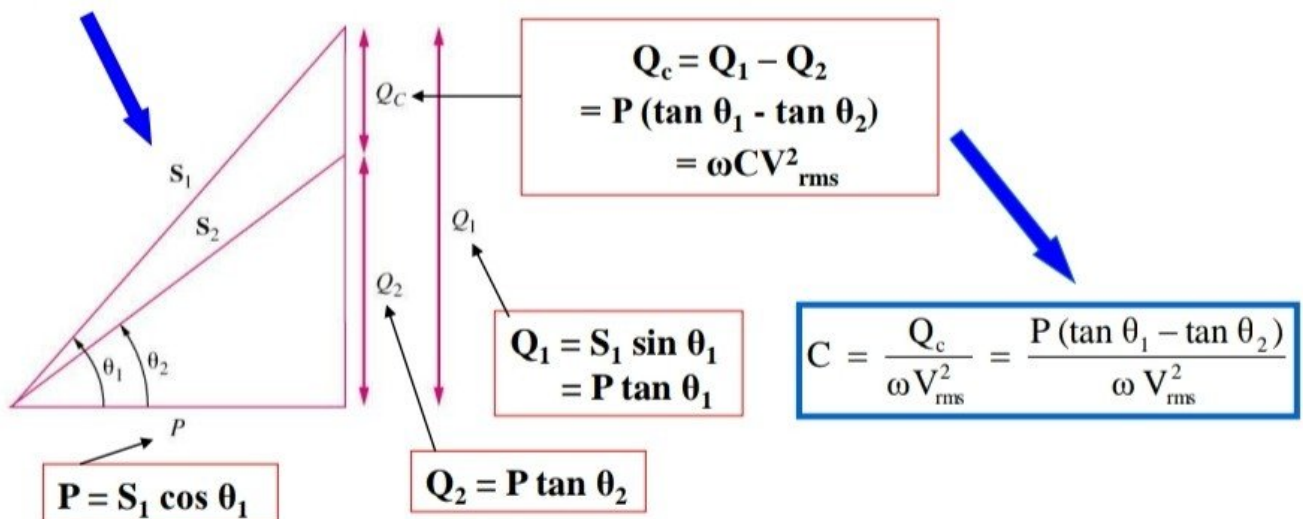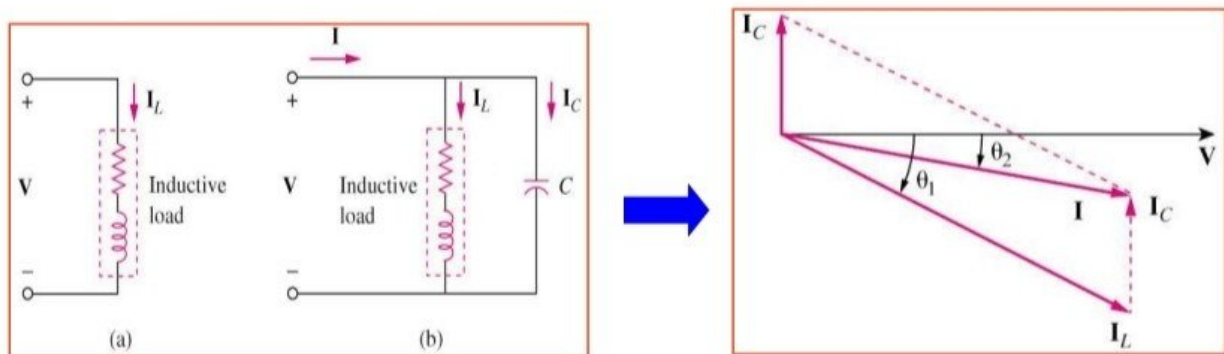

# Power Factor Correction

➤ The process of increasing the power factor without altering the voltage or current to the original load is called power factor correction.

$$P_1 = P_2 = P \quad \text{Real power stays same}$$

$$P = S_1 \cos \theta_1 \quad Q_1 = S_1 \sin \theta_1 = P \tan \theta_1 \quad Q_2 = P \tan \theta_2$$

$$Q_C = Q_1 - Q_2 = P(\tan \theta_1 - \tan \theta_2)$$

$$C = \frac{Q_C}{\omega V_{rms}^2} = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$

- The capacitance value needed to change the pf angle from  $\theta_1$  to  $\theta_2$ .
- Similarly the inductance value needed to change the pf angle from  $\theta_1$  to  $\theta_2$  for a capacitive load.

$$L = \frac{V_{rms}^2}{\omega Q_L}$$

## Power Factor Correction

**Example:** Find the value of the capacitance needed to correct a load of 140 kVAR at 0.85 lagging pf to unity pf. The load is supplied by a 110 Volt (rms), 60 Hz line.

$$\text{pf} = 0.85 = \cos\theta \longrightarrow \theta = 31.79^\circ$$

$$Q = S \sin\theta \longrightarrow S = \frac{Q}{\sin\theta} = \frac{140}{\sin(31.79^\circ)} = 265.8 \text{ kVA}$$

$$P = S \cos\theta = 225.93 \text{ kW}$$

$$\text{For } \text{pf} = 1 = \cos\theta_1 \longrightarrow \theta_1 = 0^\circ$$

Since  $P$  remains the same,

$$P = P_1 = S_1 \cos\theta_1 \longrightarrow S_1 = \frac{P_1}{\cos\theta_1} = 225.93$$

$$Q_1 = S_1 \sin\theta_1 = 0$$

The difference between the new  $Q_1$  and the old  $Q$  is  $Q_c$ .

$$Q_c = 140 \text{ kVAR} = \omega C V_{\text{rms}}^2 \quad C = \frac{140 \times 10^3}{(2\pi)(60)(110)^2} = \underline{\underline{30.69 \text{ mF}}}$$