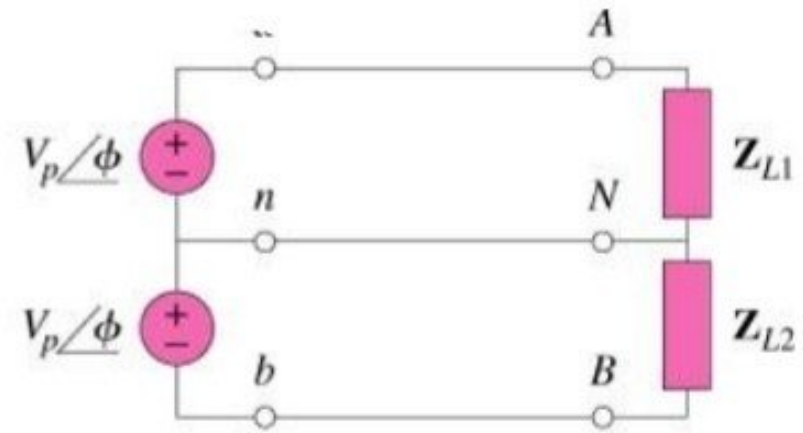


Single-Phase, Two-Phase, Three phase Circuits




(a)

a) Single phase systems two-wire type



(b)

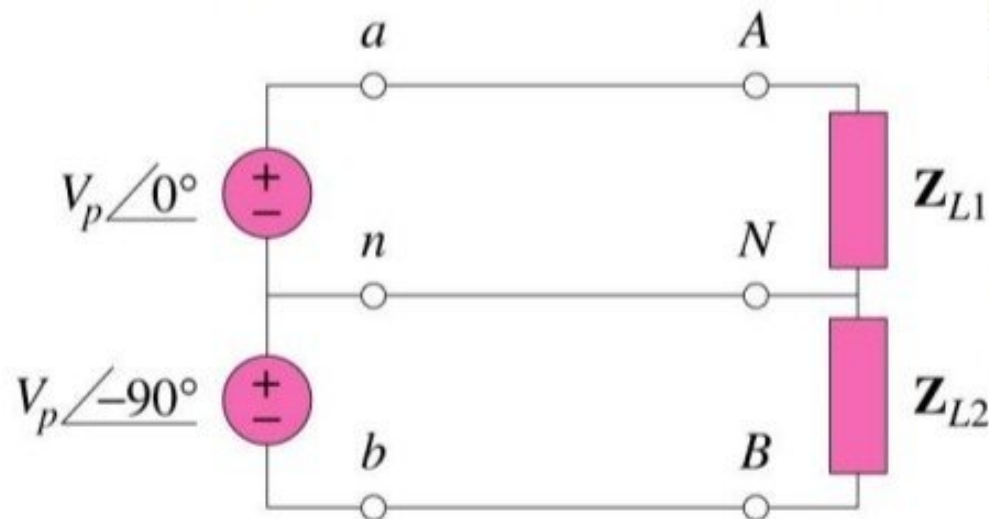b) Single phase systems three-wire type.
Allows connection to both 120 V and 240 V.




Two-phase three-wire system.

The AC sources operate at different phases.


Balanced Three-phase Voltages

Three-phase four-wire system

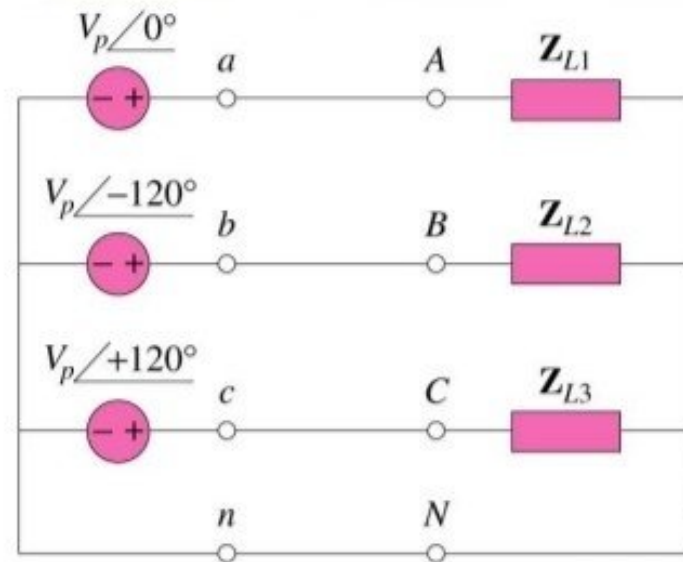


Neutral Wire


A Three-phase Generator

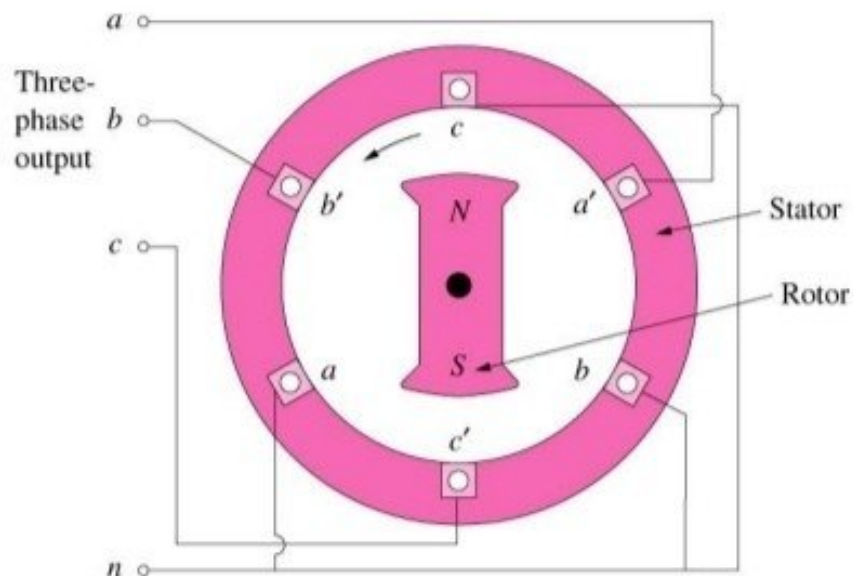


Voltages having 120° phase difference

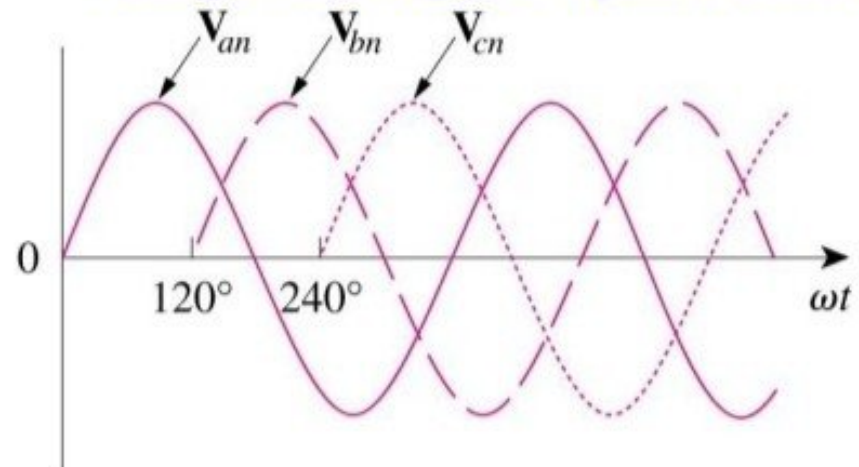


Balanced Three phase Voltages

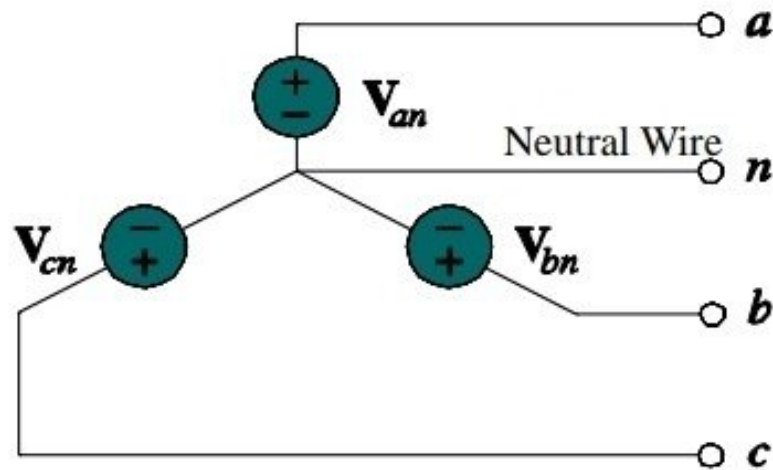


a) Wye Connected Source

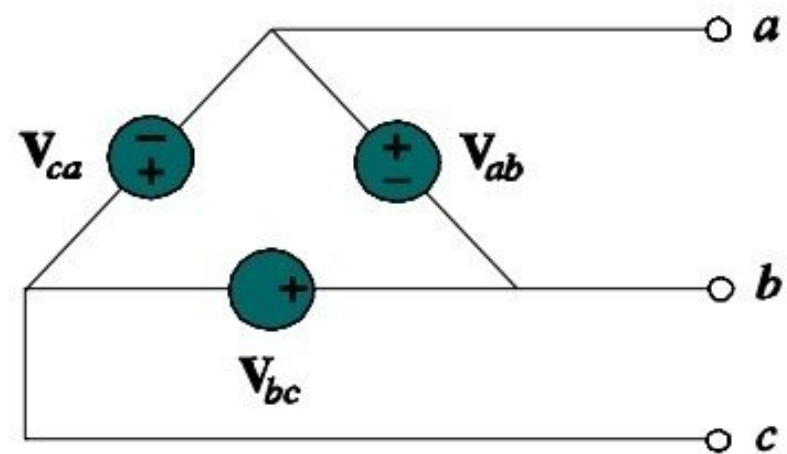

b) Delta Connected Source

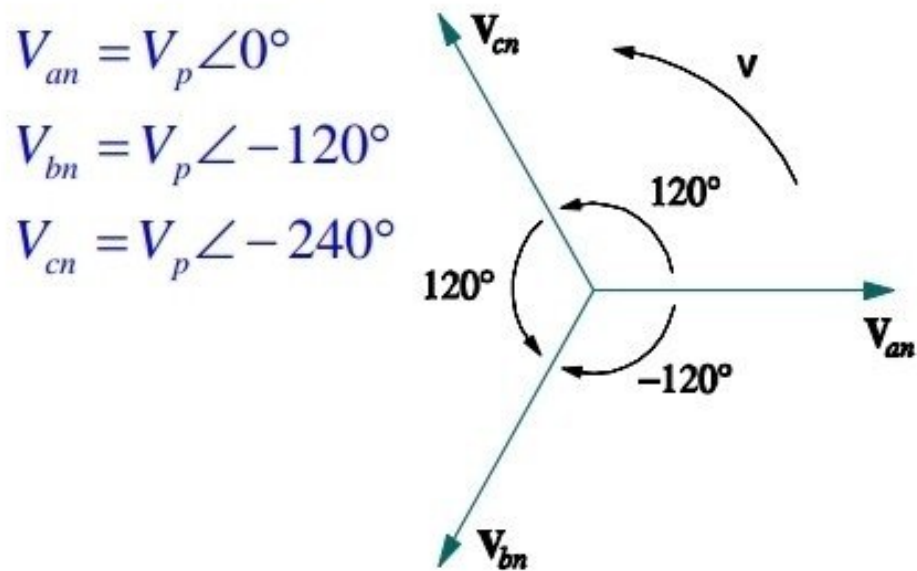


a) abc or positive sequence

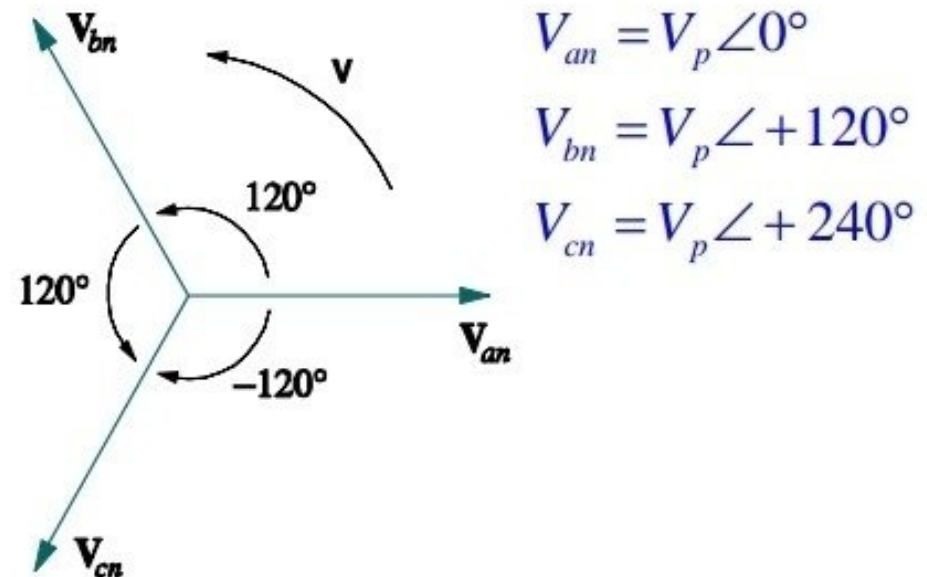

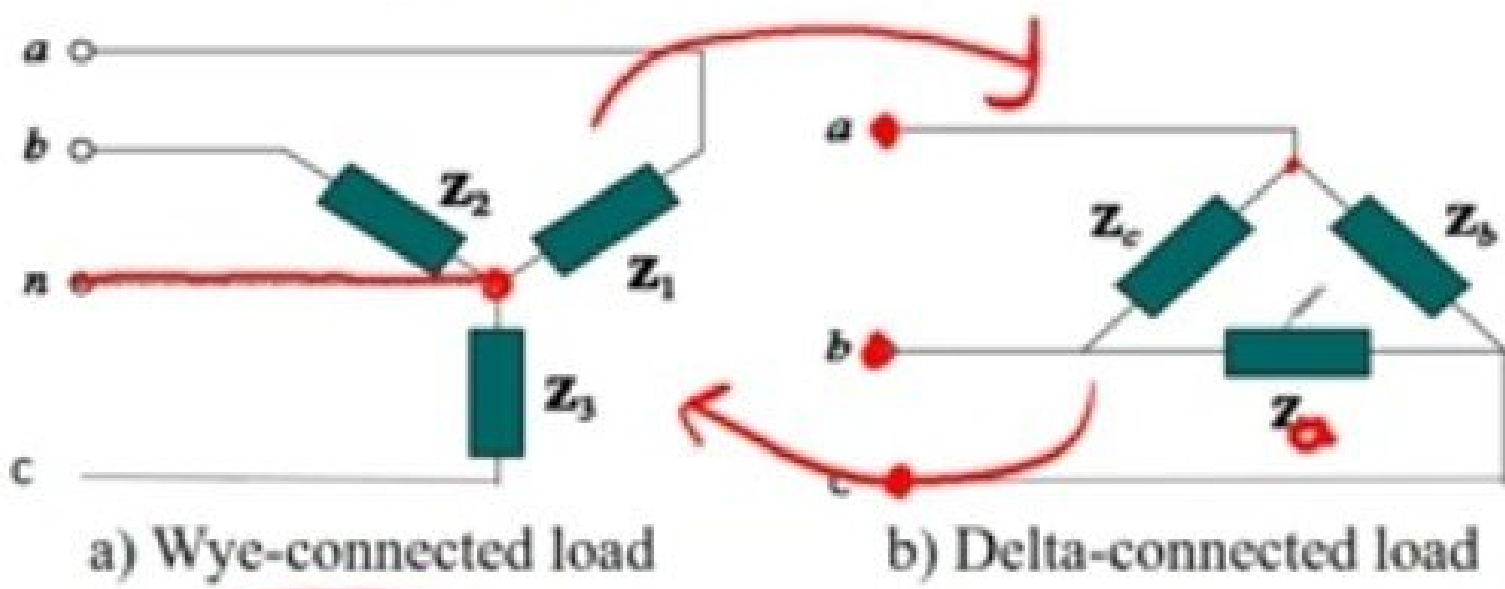b) acb or negative sequence

Handwritten notes in red ink: "D.Y.C" and a circled "D.Y.C" with a triangle next to it.



Balanced Impedance Conversion:


Conversion of Delta circuit to Wye or Wye to Delta.


$$Z_Y = Z_1 = Z_2 = Z_3$$

$$Z_\Delta = Z_a = Z_b = Z_c$$

$$Z_\Delta = 3Z_Y \quad Z_Y = \frac{1}{3}Z_\Delta$$

BALANCED Y-Y CONNECTION

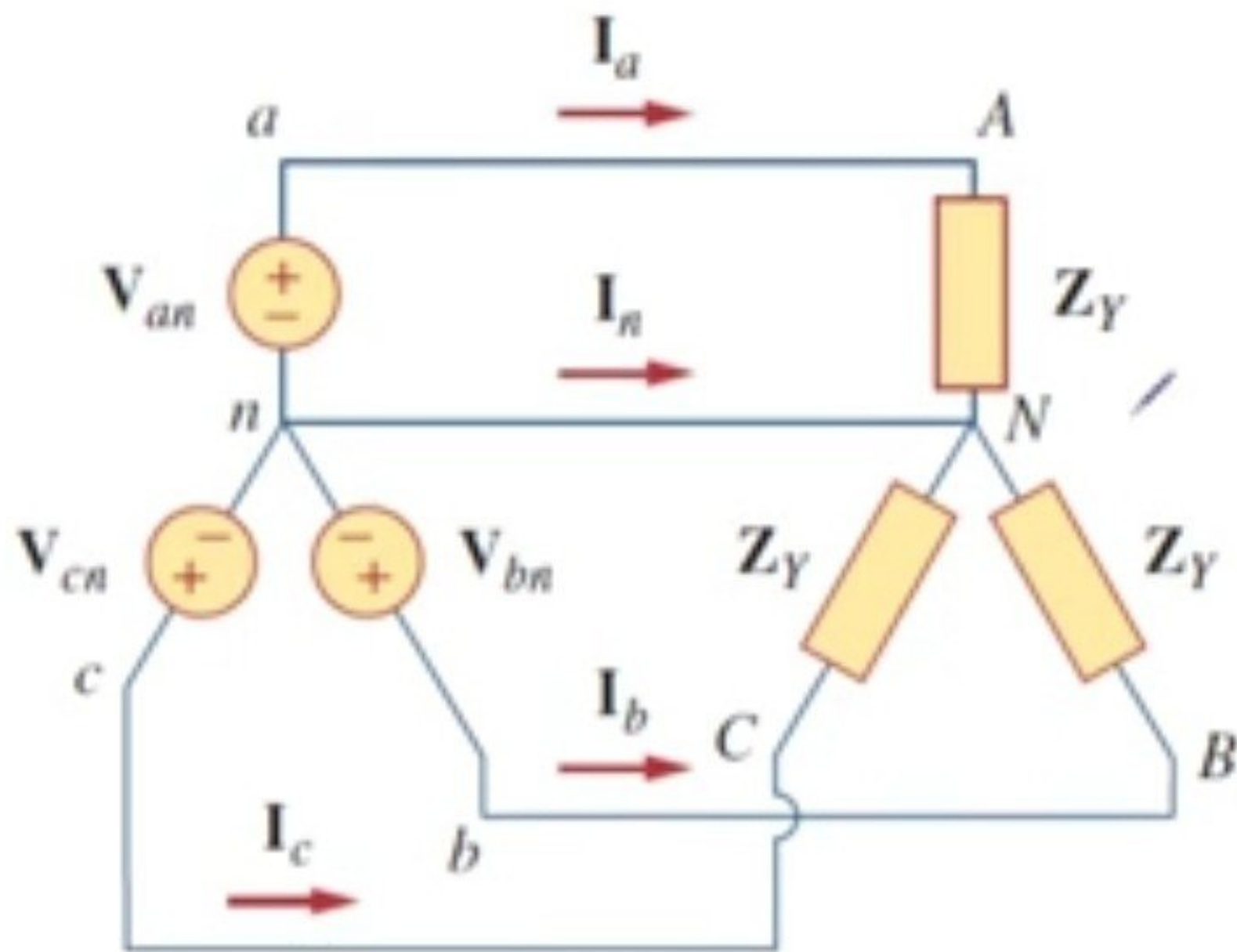


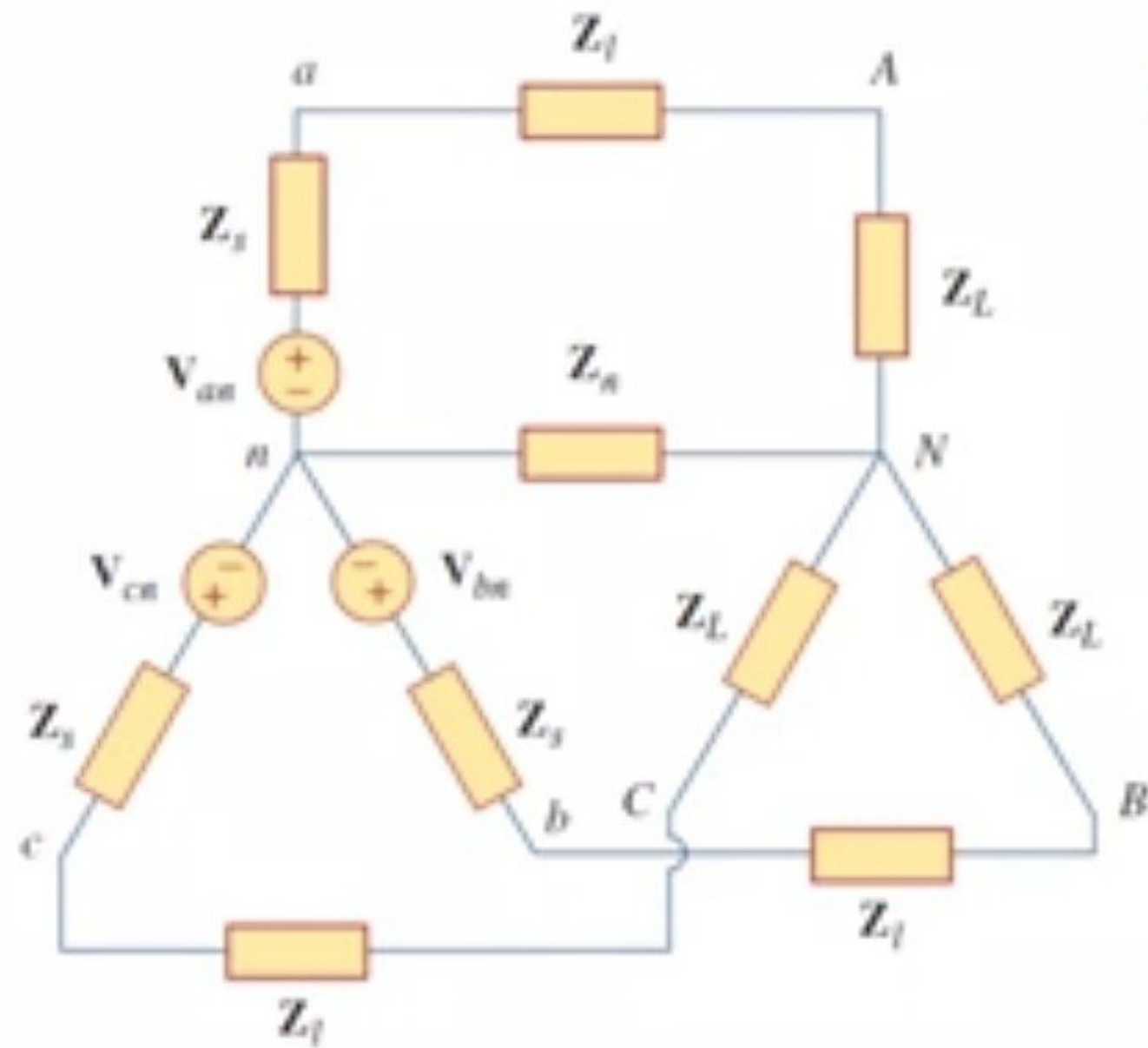

$$Z_Y = Z_s + Z_\ell + Z_L$$

Example: For an abc sequence, balanced Y-Y three phase circuit $V_{ab} = 208 \angle -30^\circ$

Determine the phase voltages.

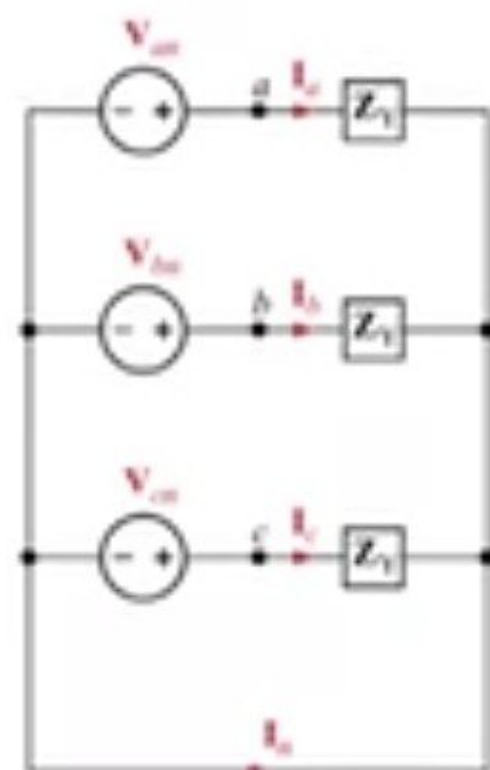

Balanced Y - Y

The phasor diagram could be rotated by any angle

$$V_{ab} = 208 \angle -30^\circ$$

$$\therefore V_{an} = \frac{|V_{ab}|}{\sqrt{3}} \angle (-30^\circ - 30^\circ)$$


$$V_{an} = 120 \angle -60^\circ$$

$$V_{bn} = 120 \angle -180^\circ$$

$$V_{cn} = 120 \angle 60^\circ$$

source $|V_{phase}| = 120(V)_{rms}$, $Z_{line} = 1 + j1\Omega$, $Z_{phase} = 20 + j10\Omega$

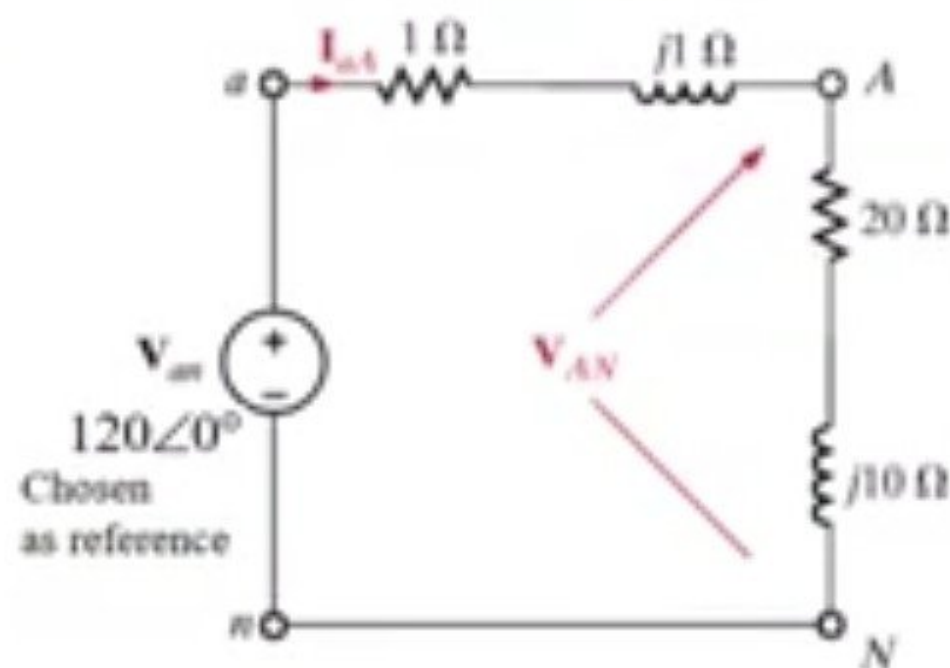Determine line currents and load voltages.



$$V_{an} = 120\angle 0^\circ$$

$$V_{bn} = 120\angle -120^\circ$$

$$V_{cn} = 120\angle 120^\circ$$

Abc sequence

$$I_{aA} = \frac{V_{an}}{Z_{line} + Z_{phase}} = \frac{120\angle 0^\circ}{21 + j11} = 23.71\angle -27.65^\circ$$

$$= 5.06\angle -27.65^\circ (A)_{rms}$$

Because circuit is balanced data on any one phase are sufficient

$$I_{bB} = 5.06\angle -120 - 27.65^\circ (A)_{rms}$$

$$I_{cC} = 5.06\angle 120 - 27.65^\circ (A)_{rms}$$

$$V_{AN} = I_{aA} \times (20 + j10) = I_{aA} \times 22.36\angle 26.57^\circ$$

$$V_{AN} = 113.15\angle -1.08^\circ (V)_{rms}$$

$$V_{BN} = 113.15\angle -121.08^\circ (V)_{rms}$$

$$V_{CN} = 113.15\angle 118.92^\circ (V)_{rms}$$

Example: For an abc sequence, balanced Y - Y three phase circuit

$V_{an} = 120\angle 90^\circ (V)_{rms}$. Find the line voltages

V_{ab} leads V_{an} by 30°

$$V_{ab} = \sqrt{3} \times 120 \angle 120^\circ (V)_{rms}$$


$$V_{bc} = \sqrt{3} \times 120 \angle 0^\circ (V)_{rms}$$

$$V_{ca} = \sqrt{3} \times 120 \angle 240^\circ (V)_{rms}$$

Example: For an abc sequence, balanced Y - Y three phase circuit

load, $|V_{phase}| = 104.02 \angle 26.6^\circ (V)_{rms}$, $Z_{line} = 1 + j1 \Omega$, $Z_{phase} = 8 + j3 \Omega$

Determine source phase voltages

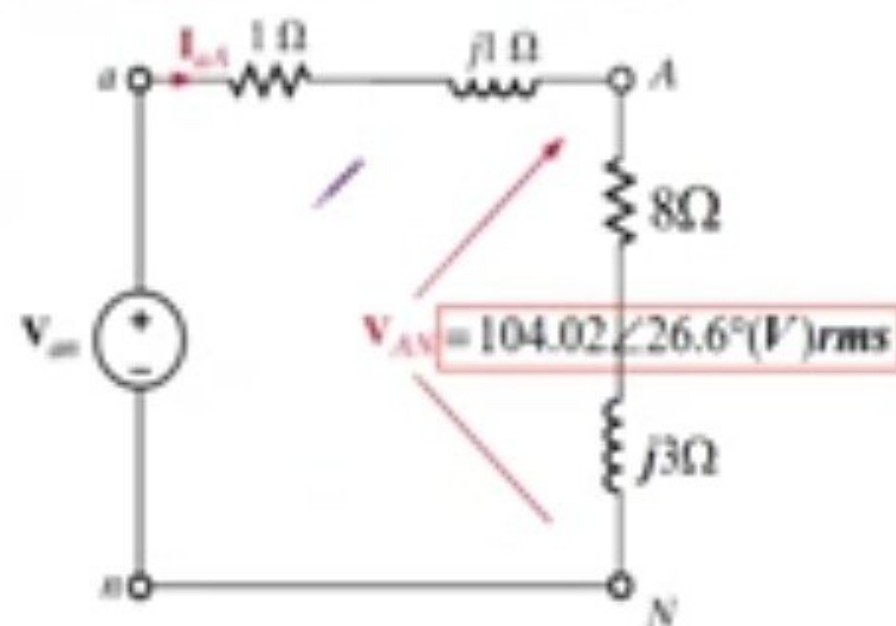

Currents are not required. Use inverse voltage divider


$$V_{an} = \frac{(8 + j3) + (1 + j1)}{8 + j3} V_{AN}$$

$$\frac{9 + j4}{8 + j3} \times \frac{8 - j3}{8 - j3} = \frac{84 + j5}{73} = 1.15 \angle 3.41^\circ$$

$$V_{an} = 120 \angle 30^\circ$$

$$V_{bn} = 120 \angle -90^\circ$$

$$V_{cn} = 120 \angle 150^\circ$$

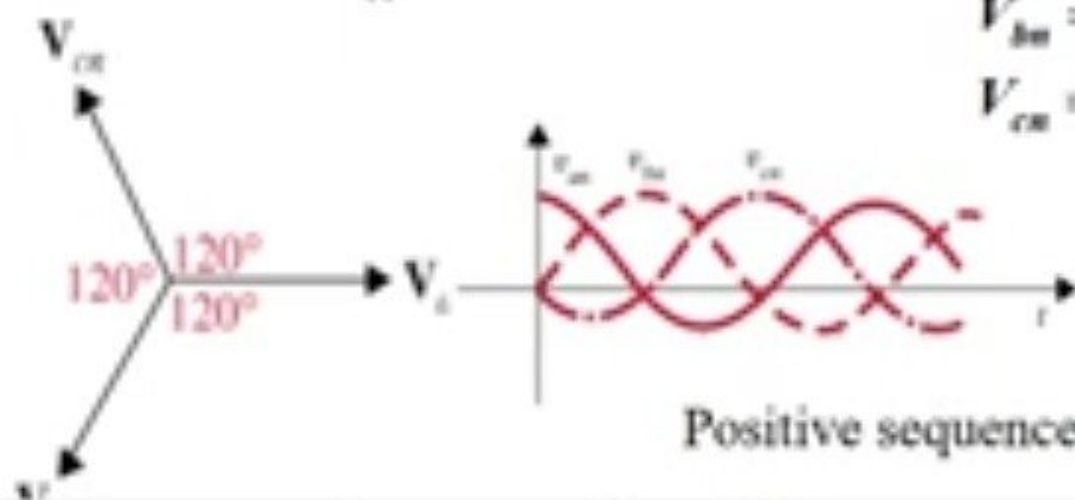


Positive sequence a-b-c

Example: For an abc sequence, balanced Y - Y three phase circuit

$$\text{source } |V_{\text{phase}}| = 120(\text{V})_{\text{rms}}, Z_{\text{line}} = 1 + j1\Omega, Z_{\text{phase}} = 20 + j10\Omega$$

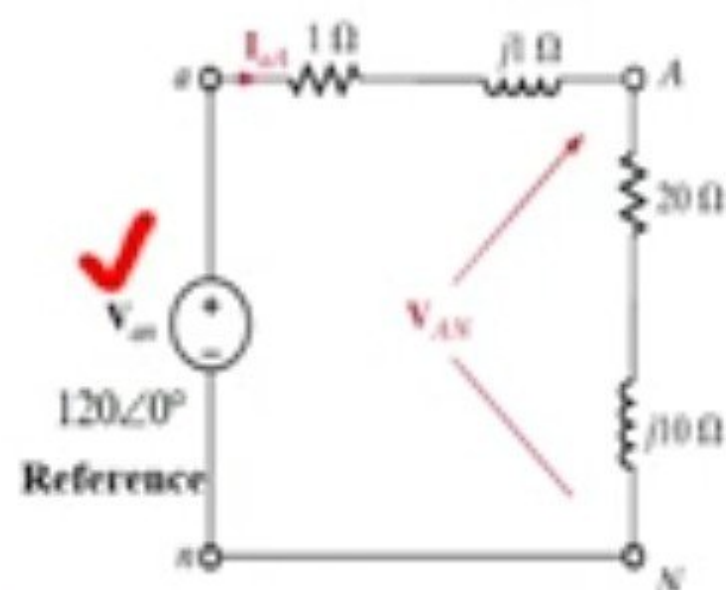Determine real and reactive power per phase at the load and total real, reactive and complex power at the source



$$V_{AN} = I_{aA} \times (20 + j10) = I_{aA} \times 22.36 \angle 26.57^\circ$$

$$V_{AN} = 113.15 \angle -1.08^\circ (\text{V})_{\text{rms}}$$

$$S_{\text{phase}} = V_{AN} I_{aA}^* = 113.15 \angle -1.08^\circ \times 5.06 \angle 27.65^\circ$$

$$S_{\text{phase}} = 572.54 \angle 26.57^\circ = 512 + j256.09 (\text{VA})_{\text{rms}}$$

$$S_{\text{source phase}} = V_{an} \times I_{aA}^* = 120 \angle 0^\circ \times 5.06 \angle 27.65^\circ$$

$$S_{\text{source phase}} = 607.2 \angle 27.65^\circ$$

$$= 537.86 + j281.78 \text{VA}$$

$$V_{an} = 120 \angle 0^\circ$$

$$V_{bn} = 120 \angle -120^\circ$$

Because circuit is balanced data on any one phase are sufficient

$$V_{cn} = 120 \angle 120^\circ$$

Abc sequence

$$I_{aA} = \frac{V_{an}}{21 + j11} = \frac{120 \angle 0^\circ}{23.71 \angle 27.65^\circ}$$

$$= 5.06 \angle -27.65^\circ (\text{A})_{\text{rms}}$$

$$P_{\text{total source}} = 3 \times 537.86 (\text{W})$$


$$Q_{\text{total source}} = 3 \times 281.78 (\text{VA})$$

$$S_{\text{total source}} = P_{\text{total source}} + jQ_{\text{total source}}$$

$$= 1613.6 + j845.2 (\text{VA})$$


$$|S_{\text{total source}}| = 1821.6 (\text{VA})$$

DELTA CONNECTED SOURCES

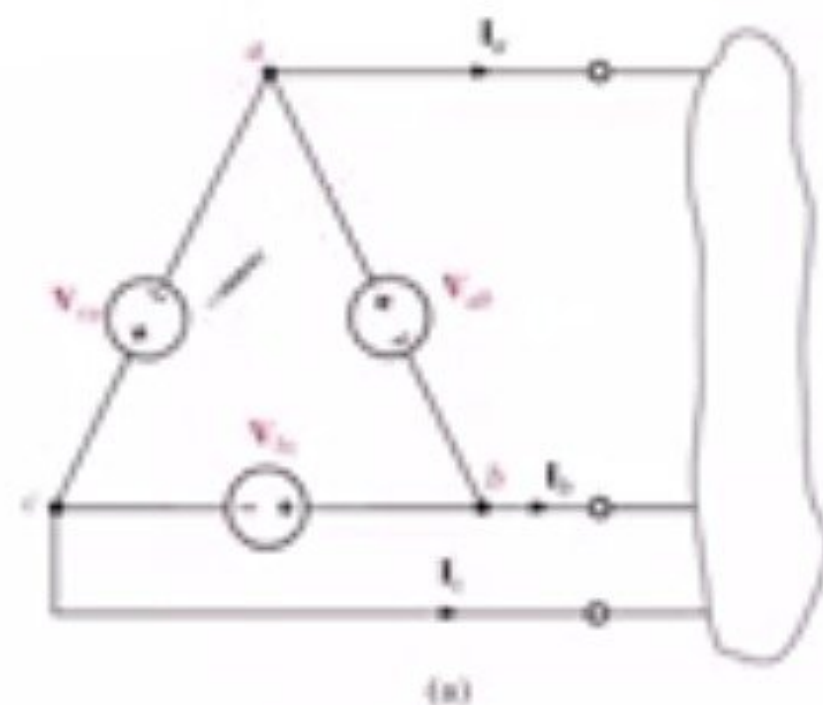

Line voltages = phase voltages
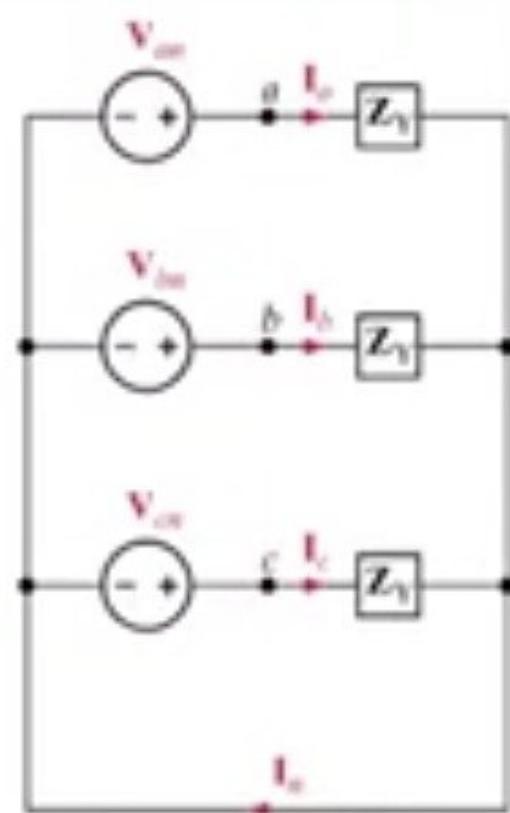
$$\left. \begin{aligned} V_{ab} &= V_L \angle 0^\circ \\ V_{bc} &= V_L \angle -120^\circ \\ V_{ca} &= V_L \angle 120^\circ \end{aligned} \right\} \Rightarrow$$



Balanced Y - Y

The phasor diagram could be rotated by any angle

$$V_{ab} = 208 \angle -30^\circ$$


$$\therefore V_{an} = \frac{|V_{ab}|}{\sqrt{3}} \angle (-30^\circ - 30^\circ)$$

$$V_{an} = 120 \angle -60^\circ$$

$$V_{bn} = 120 \angle -180^\circ$$

$$V_{cn} = 120 \angle 60^\circ$$

Balanced DELTA-to-DELTA CONNECTION

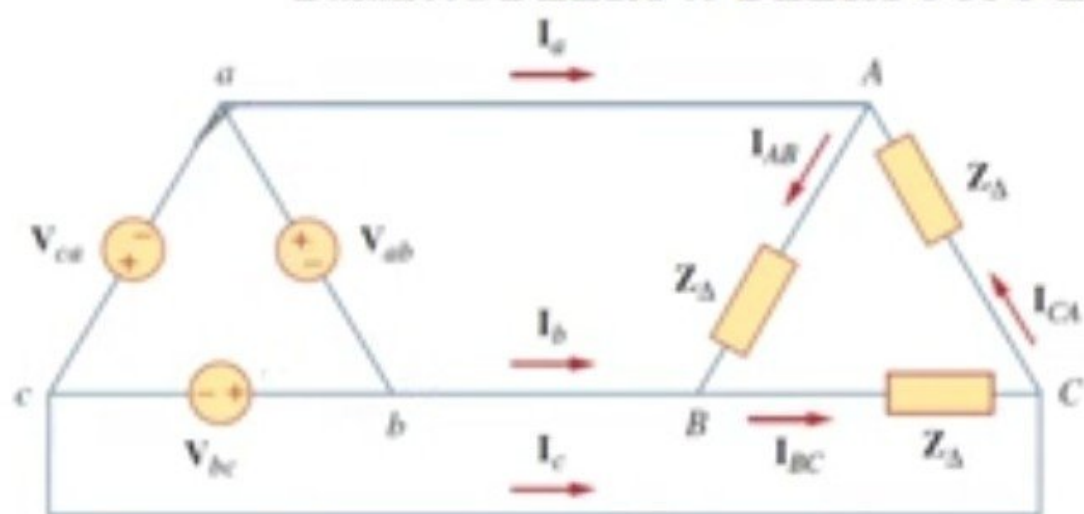

Line voltages = phase voltages

$$\left. \begin{aligned} V_{ab} &= V_L \angle 0^\circ \\ V_{bc} &= V_L \angle -120^\circ \\ V_{ca} &= V_L \angle 120^\circ \end{aligned} \right\} \Rightarrow$$

assuming there is no line impedances,

$$V_{ab} = V_{AB} \quad V_{bc} = V_{BC} \quad V_{ca} = V_{CA}$$

Hence, the phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_\Delta} = \frac{V_{ab}}{Z_\Delta}$$

The line currents are

$$I_a = I_{AB} - I_{CA} = I_{AB} \sqrt{3} \angle -30^\circ$$

$$I_b = I_{BC} - I_{AB} = I_a \angle -120^\circ$$

$$I_c = I_{CA} - I_{BC} = I_a \angle +120^\circ$$

assuming there is no line impedances,

$$V_{ab} = V_{AB} \quad V_{bc} = V_{BC} \quad V_{ca} = V_{CA}$$

Hence, the phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}} \quad \checkmark$$

$$I_{BC} = \frac{V_{BC}}{Z_{\Delta}} = \frac{V_{bc}}{Z_{\Delta}} = \underline{I_{AB} / -120^{\circ}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{\Delta}} = \frac{V_{ca}}{Z_{\Delta}} = \underline{I_{AB} / +120^{\circ}}$$

The line currents are

$$I_a = I_{AB} - I_{CA} = I_{AB} \sqrt{3} / -30^{\circ}$$

$$I_b = I_{BC} - I_{AB} = I_a / -120^{\circ}$$

$$I_c = I_{CA} - I_{BC} = I_a / +120^{\circ}$$

Balanced DELTA-to-DELTA CONNECTION

Example 12.4

A balanced Δ -connected load having an impedance $20 - j15 \Omega$ is connected to a Δ -connected, positive-sequence generator having $V_{ab} = 330/0^\circ$ V. Calculate the phase currents of the load and the line currents.

Solution:

The load impedance per phase is

$$Z_{\Delta} = 20 - j15 = 25 \angle -36.87^\circ \Omega$$

Since $V_{AB} = V_{ab}$, the phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{330/0^\circ}{25 \angle -36.87^\circ} = 13.2 \angle 36.87^\circ \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 13.2 \angle -83.13^\circ \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^\circ = 13.2 \angle 156.87^\circ \text{ A}$$

For a delta load, the line current always lags the corresponding phase current by 30° and has a magnitude $\sqrt{3}$ times that of the phase current. Hence, the line currents are

$$I_a = I_{AB} \sqrt{3} \angle -30^\circ = (13.2 \angle 36.87^\circ)(\sqrt{3} \angle -30^\circ) = 22.86 \angle 6.87^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.13^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 22.86 \angle 106.87^\circ \text{ A}$$

Since $V_{AB} = V_{ab}$, the phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{330 \angle 0^\circ}{25 \angle -36.87^\circ} = 13.2 \angle 36.87^\circ \text{ A}$$
$$I_{BC} = I_{AB} \angle -120^\circ = 13.2 \angle -83.13^\circ \text{ A}$$
$$I_{CA} = I_{AB} \angle +120^\circ = 13.2 \angle 156.87^\circ \text{ A}$$

phase or
Load currents


For a delta load, the line current always lags the corresponding phase current by 30° and has a magnitude $\sqrt{3}$ times that of the phase current. Hence, the line currents are

$$I_a = I_{AB} \angle -30^\circ = (13.2 \angle 36.87^\circ)(\sqrt{3} \angle -30^\circ)$$
$$= 22.86 \angle 6.87^\circ \text{ A}$$


$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.13^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 22.86 \angle 126.87^\circ \text{ A}$$

Balanced Wye-Delta Connection

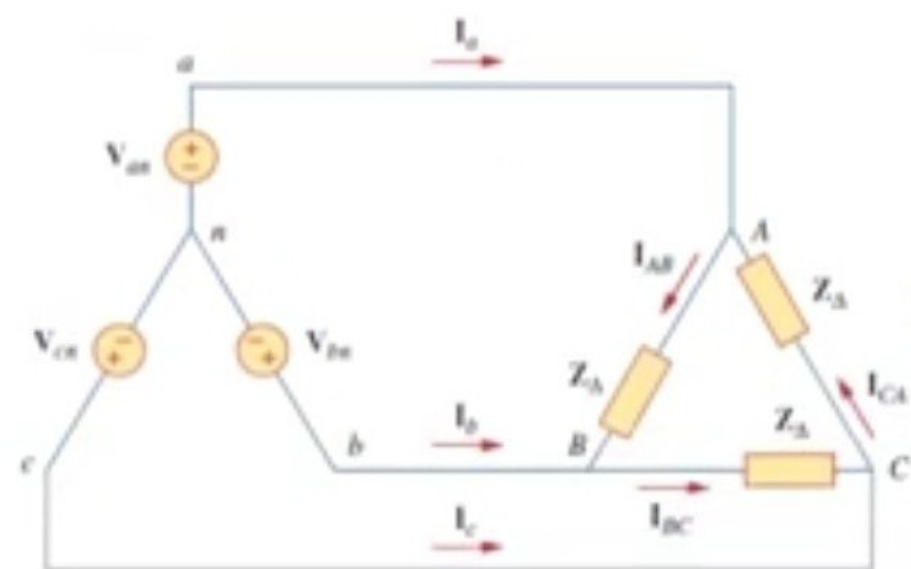

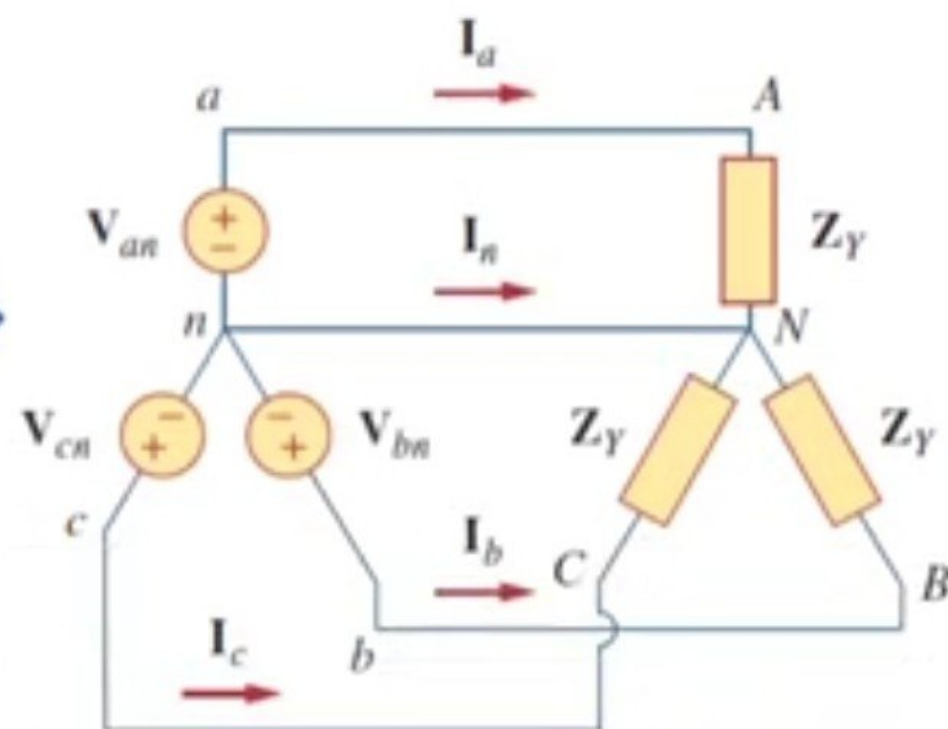An alternative way of analyzing the Y- Δ circuit is to transform the Δ -connected load to an equivalent Y-connected load. Using the Δ -Y transformation formula in Eq. (12.8),



Balanced Delta-Wye Connection

