



Weekly Notebook


ELECTRICAL

first semester
2021-2022

(1) Power supply (مصدر الطاقة)

(2) load (حمل الطاقة)


(3) connections

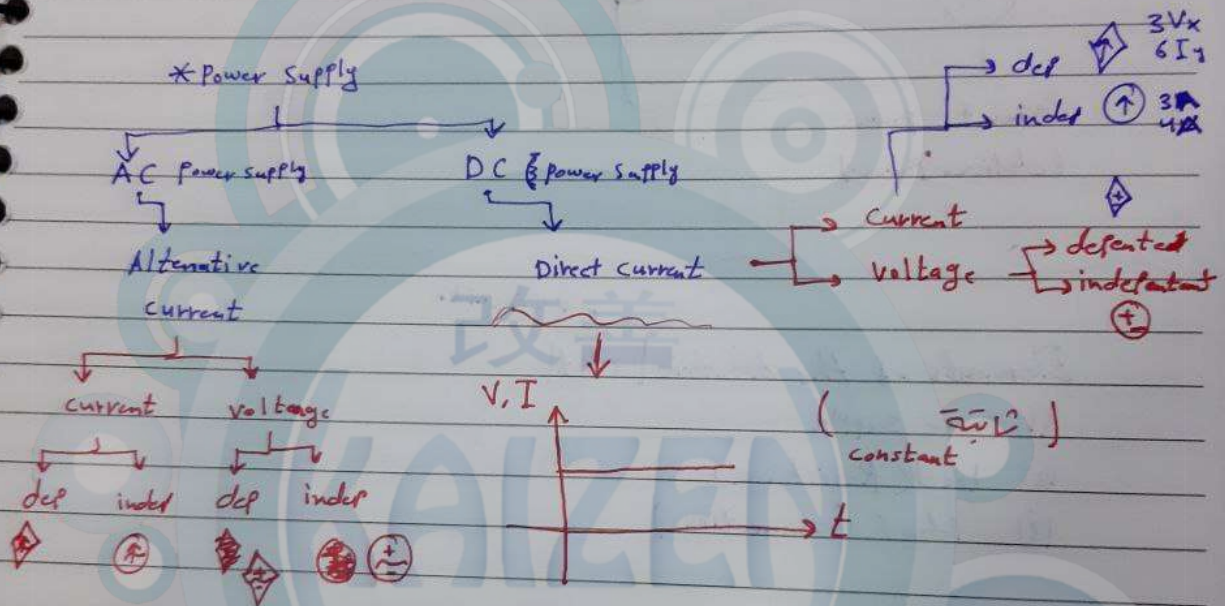

DC - Power

The Value of

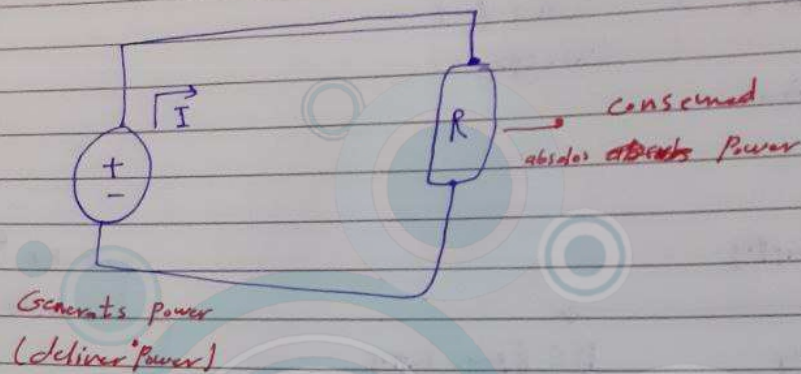(ملاحظاً ← هو المصدر الذي يبقى ثابتاً مع الزمن)



Elements of the Electric ^{Circuit} [CKT]

- (1) Power Supply
- (2) Load (Resistance)
- (3) Ideal (connections)

[*] independent ○ , Voltage $\pm$, DC (nothing)

[*] dependent ◇ , current $\uparrow$, AC ($\sim$)

→ DC → لا تتغير مع الوقت (constant)

~~Ex:-~~

EX:- Find power??, $t=3\text{ms}$, $i=5\cos 60\pi t$
 $v=3i$


$$\begin{aligned}\text{Sol:- } P &= i \times V \\ &= 5\cos 60\pi t \times 3(5\cos 60\pi t) \\ &= 75 \cos^2 60\pi t , \\ &= 75 \cos^2(60\pi \times 0.003) \\ &= 53.467 \text{ watt.}\end{aligned}$$

* $P = \ominus$ (negative)
↳ produced, generated, deliver

* $P = \oplus$ (positive)
↳ consumed

Rad $\rightarrow$ راديان
Deg $\rightarrow$ درجة
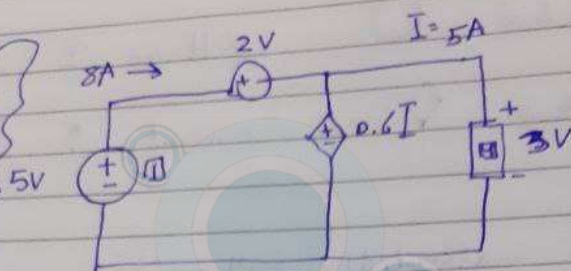
$$\begin{aligned}
 P &= \frac{dw}{dt} \quad i = \frac{dq}{dt} \\
 P &= IV \\
 P &= I^2 R \\
 P &= \frac{V^2}{R} \\
 W &= VQ \\
 V &= \frac{dw}{dq}
 \end{aligned}$$



~~$P_3 = ??$~~ $P_3 = ??$, $I_3 = ??$, $V_3 = ??$

$$P_1 = -8 \times 5 = -40 \text{ watt produced}$$

$$P_2 = 2 \times 8 = 16 \text{ watt consumed}$$


$$P_4 = 5 \times 3 = 15 \text{ watt consumed}$$

$$P_3 = (15 + 16 - 40) \times -1$$


$$P_3 = 9 \text{ watt consumed}$$

$$V_3 = \frac{9}{0.6 \times 5} = 3 \text{ A}$$
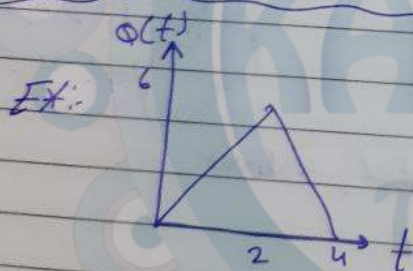
$$I_3 = \frac{9}{3} = 3 \text{ A} = V_3 = 3 \text{ volt}$$



find $i(t)$

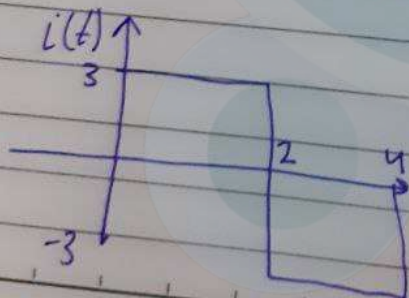

$$\text{slope } (0-2)$$

$$= \frac{6-0}{2-0} = 3 \text{ A}$$

$$\text{slope } (2-4)$$


$$= \frac{0-6}{4-2} = -3 \text{ A}$$

(*) دائماً عندما يدخل السياره يكون $(+ \text{ to } -)$ $(+ \text{ to } -)$

(*) عندما يخرج السياره في المقاومة يكون $(- \text{ to } +)$


(*) الفنا صر المتوازية تكون $V_1 = V_2$

For Any close loop $V = 0$

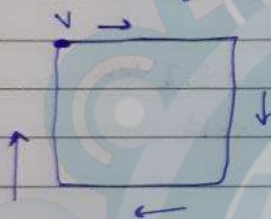


(*) اذا جرج على نفس النقطة يكون $V = 0$

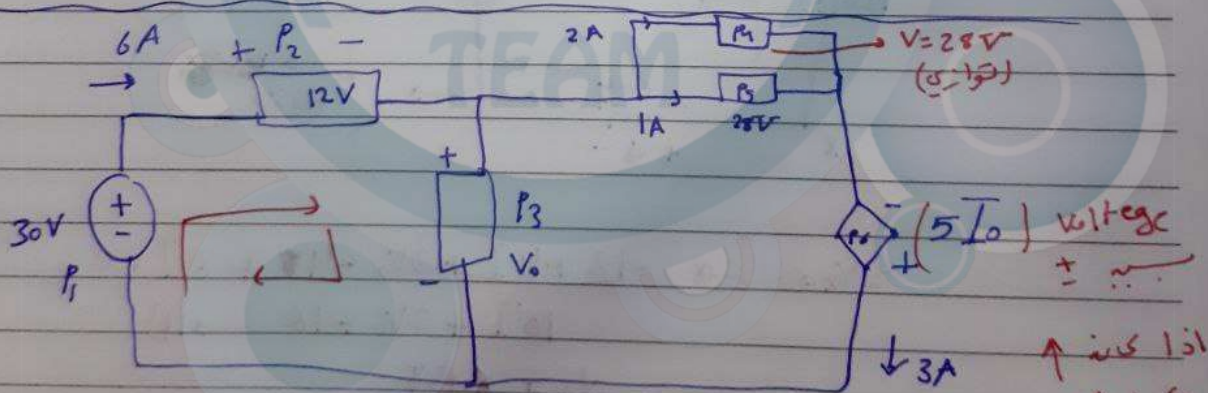(*) اذا بقول من الكوسين موجب واذا دخلنا من السالب



$$V_0 \Rightarrow \sum V = 0 \rightarrow -30 + 12 + V_0 = 0$$

$$V_0 = 18V$$

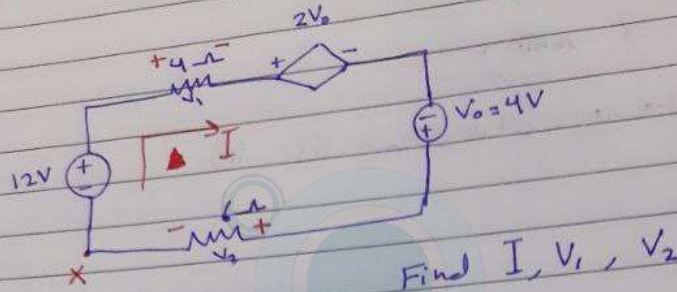

$$\sum V_x = 0$$


$$\Rightarrow -12 + 4I + 2 \times (4) - 4 + 6I = 0$$

$$10I = 8$$

$$I = 0.8 \text{ A}$$

$$V_1 = 0.8 \times 4 = \frac{16}{5} = 3.2 \text{ volt}$$
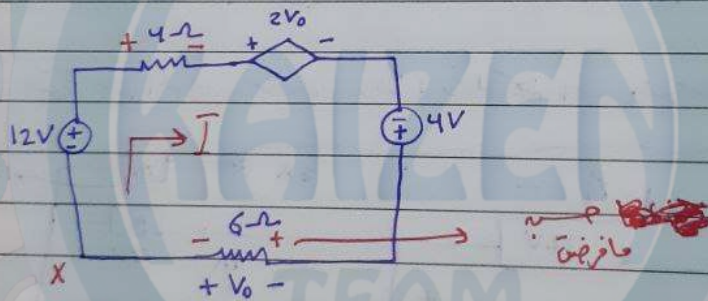
$$V_2 = 0.8 \times 6 = 4.8 \text{ volt}$$



$$\sum V_x = 0 \rightarrow -12 + 4I + 2V_0 - 4 + 6I = 0$$

$$10I + 2V_0 = 16 \rightarrow \text{II}$$

$$V_0 = 4RI$$


$$V_0 = 6 \times I \text{ (لأنه من 6Ω سلكه من قبله)}$$

$$10I + -12I = 16$$

$$-2I = 16$$

$$I = -8 \text{ A}$$

$$V_0 = 48 \text{ volt}$$

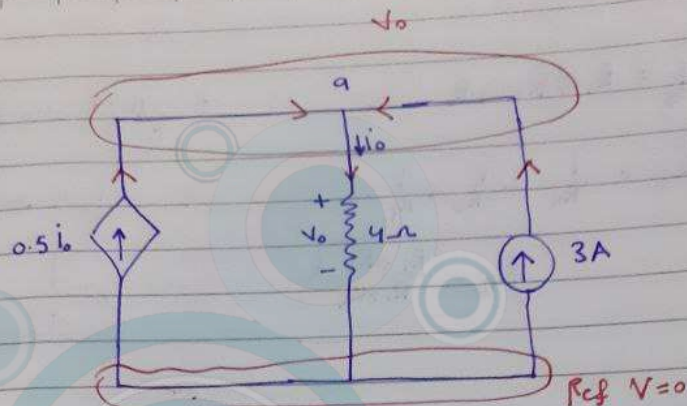

Find current i_o and V_o ??


$$\sum I_{in} = \sum I_{out}$$

$$0.5i_o + 3 = i_o$$

$$i_o = 6A$$

$$V_o = i_o \times R$$

$$= 6 \times 4 = 24 \text{ Volt}$$

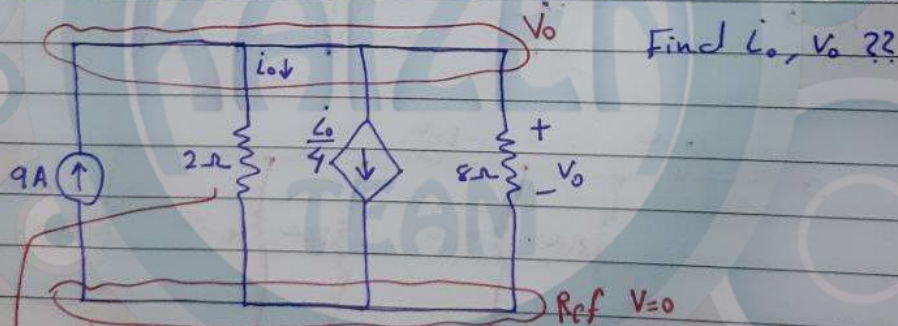

Find i_o , V_o ??

$$\sum I_{in} = \sum I_{out}$$

$$9 = i_o + \frac{i_o}{4} + \frac{V_o}{8}$$

$$V_o = 2i_o$$

فرضیه ها را در نظر بگیرید
از هر دو یکی

$$9 = i_o + \frac{i_o}{4} + \frac{1}{4}$$

$$i_o = 6A$$

$$V_o = 12V$$

في حالة التوالي :



$$\sum R = R_1 + R_2 + R_3 \dots$$

في حالة التوازي :

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2}$$

إذا
كانت مقاومتين

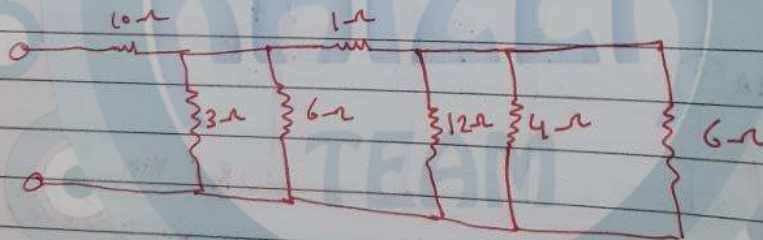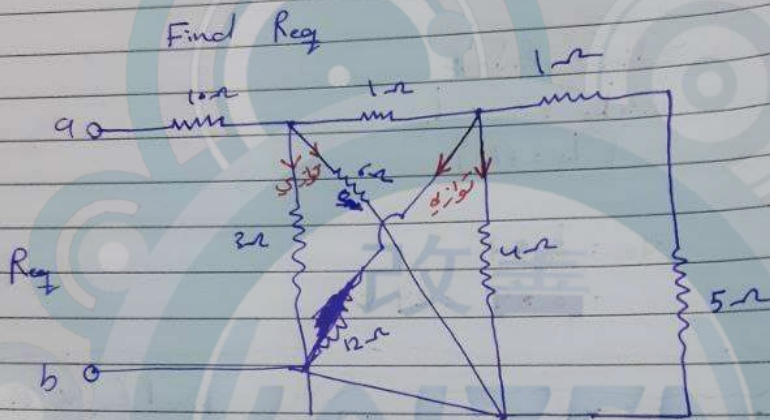


$$\frac{3 \times 6}{3+6} = 2$$

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{4} + \frac{1}{12}$$


$$= \frac{2}{12} + \frac{3}{12} + \frac{1}{12} = \frac{6}{12} = \frac{1}{2} \Rightarrow R_{eq} = 2$$

$$R = \frac{3 \times 2}{3+2} = \frac{6}{5}$$

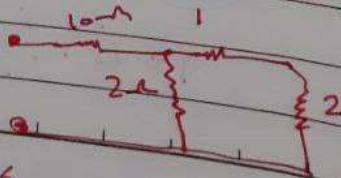
$$R_{eq} = \frac{6}{5} + \frac{50}{5} = \frac{56}{5}$$



$$V_1 = \frac{V R_1}{R_1 + R_2}$$

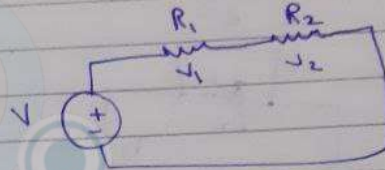

Ex:-

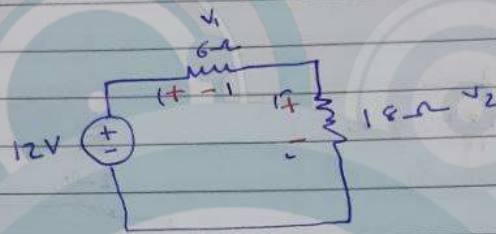

$$V_2 = \frac{18 \times 12}{18 + 6} = 9 \text{ Volt}$$


$$I_1 = \frac{I_T R_2}{R_1 + R_2}$$


$$I_2 = \frac{I_T R_1}{R_1 + R_2}$$



Ex:- $6 \parallel 9 \Rightarrow R = \frac{9 \times 6}{15} = \frac{54}{15}$

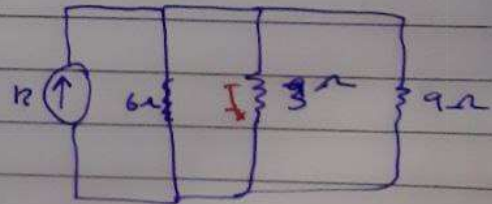
$$I_x = \frac{12 \times \frac{54}{15}}{\frac{54}{15} + 3} \text{ A}$$



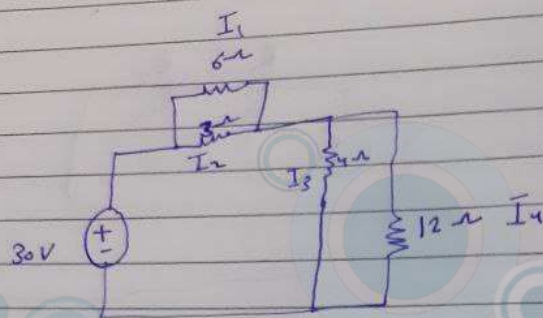

$$6 // 3 = 2 \Omega$$
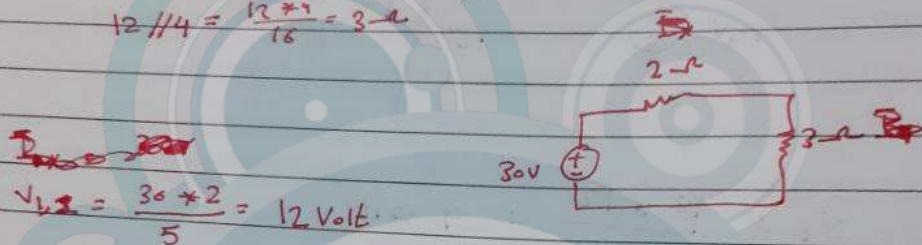
$$2 // 4 = \frac{2 \times 4}{2 + 4} = \frac{8}{6} = \frac{4}{3} \Omega$$



$$V_2 = \frac{30 \times 2}{2 + 4} = 10 \text{ Volt}$$


$$V_4 = \frac{30 \times 4}{2 + 4} = 20 \text{ Volt}$$

$$I_1 = \frac{12}{6} = 2 \text{ A}$$

$$I_2 = \frac{12}{3} = 4 \text{ A}$$

$$I_3 = \frac{16}{4} \text{ A}$$

$$I_4 = \frac{16}{12} \text{ A}$$

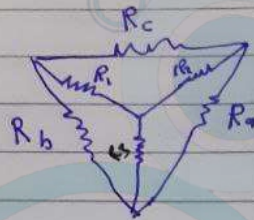

$\Delta \xrightarrow{to} Y$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_a = R_b = R_c = R_\Delta$$

$$R_Y = \frac{R_\Delta}{3}$$

$Y \xrightarrow{to} \Delta$


$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$$R_1 = R_2 = R_3 = R_Y$$

$$R_\Delta = 3 R_Y$$

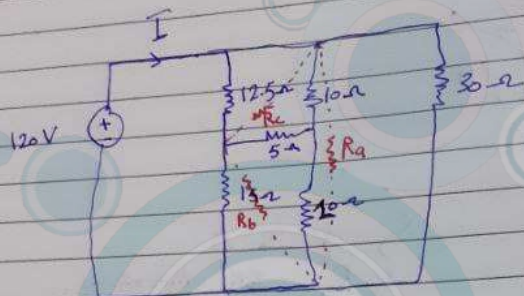

$$R_a = \frac{20 \times 10 + 10 \times 5 + 20 \times 5}{5} = \frac{350}{5} = 70 \, \Omega$$


$$R_b = \frac{350}{10} = 35 \, \Omega$$

$$R_c = \frac{350}{20} = 17.5 \, \Omega$$

$$[R_c // 12.5 + R_b // 15]$$

$$= \frac{17.5 \times 12.5}{30} + \frac{35 \times 15}{50}$$

$$= 17.79 \, \Omega$$

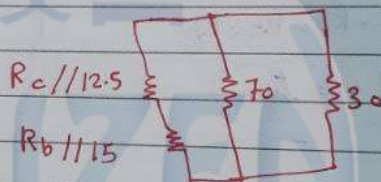


$$30 // 70 \Rightarrow \frac{30 \times 70}{100} = 21 \, \Omega$$

$$21 \, \Omega // 17.79 \, \Omega \Rightarrow R_{eq} = 9.631 \, \Omega$$

$$I = \frac{120}{9.631}$$

$$I = 12.46 \, A$$

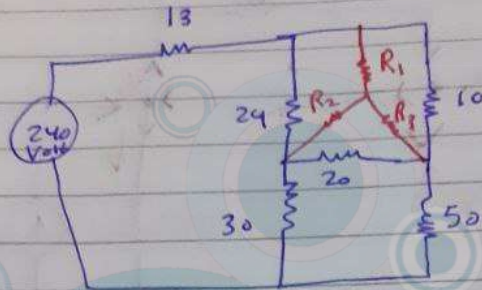

$$R_1 = \frac{10 \times 24}{10 + 20 + 24} = \frac{240}{54} = 4.44 \Omega$$

$$R_2 = \frac{20 \times 24}{54} = 8.88 \Omega$$

$$R_3 = \frac{10 \times 20}{54} = 3.7 \Omega$$

$$53.7 \parallel 38.88$$


$$\Rightarrow 22.552 \Omega$$

22

$$R_{eq} = 22.552 + 4.44 + 13$$

$$R_{eq} = 40 \Omega$$

$$I = \frac{240}{40} = 6A$$

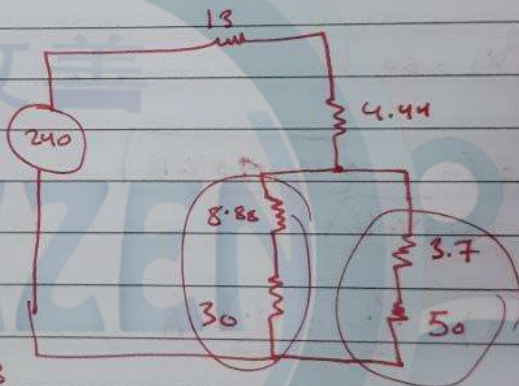

(VR = 81.4 V in (2.5))
(2.5 = 10 - 1.5)

(Node) 2

1.5 A
10 A

$$5 = \frac{V_1 - V_2}{4} + \frac{V_1}{2} \rightarrow 10$$

$$10 + \frac{V_1 - V_2}{4} = 5 + \frac{V_2}{6}$$

$$20 = V_1 - V_2 + 2V_1$$

$$3V_1 - V_2 = 20$$

$$40 + V_1 - V_2 = 20 + \frac{2}{3}V_2$$

$$V_1 - \frac{5}{3}V_2 = -20 \quad \times -3$$

$$3V_1 + 5V_2 = 60$$

$$4V_2 = 80 \rightarrow V_2 = 20 \text{ V}$$

$$V_1 = 13.3 \text{ V}$$


$$I(2\Omega) = \frac{V_1}{2} = \frac{13.3}{2} \text{ A}$$

$$I(4\Omega) = \frac{V_1 - V_2}{4} = \frac{13.3 - 20}{4} \text{ A}$$

$$V(10\text{A}) = V_2 = 20 \text{ V}$$

$$V(5\text{A}) = \frac{V_1 - V_2}{4} = \frac{13.3 - 20}{4} \text{ A}$$
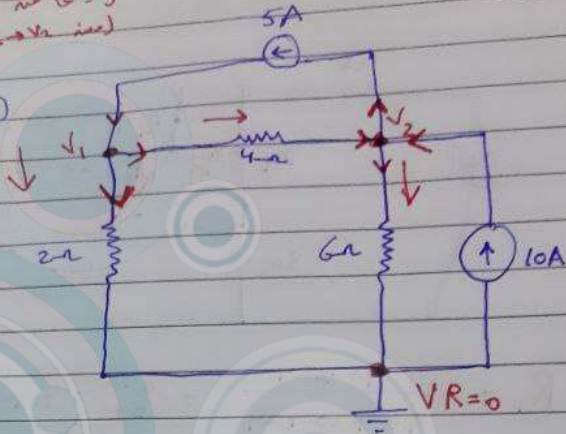
$$I(6\Omega) = \frac{V_2}{6} = \frac{20}{6} \text{ A}$$



$$6 \times 3 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 \times \frac{V_1 - V_2}{6} = 12 + \frac{V_2}{7}$$

$$V_1 - V_2 + 3V_1 = 18$$

$$V_1 - V_2 - \frac{6V_2}{7} = 72$$

$$4V_1 - V_2 = 18$$

$$V_1 - \frac{13}{7}V_2 = 72 \quad \times -4$$

$$4V_1 - V_2 = 18$$

$$-4V_1 + \frac{52}{7}V_2 = -288$$



$$\frac{45}{7}V_2 = -270$$

$$V_2 = -42 \text{ V}$$


$$V_1 = -6 \text{ Volt}$$

$$P(12A) = V_2 \times A$$

$$= -42 \times 12 = -504 \text{ watt}$$

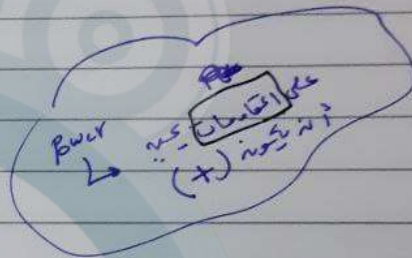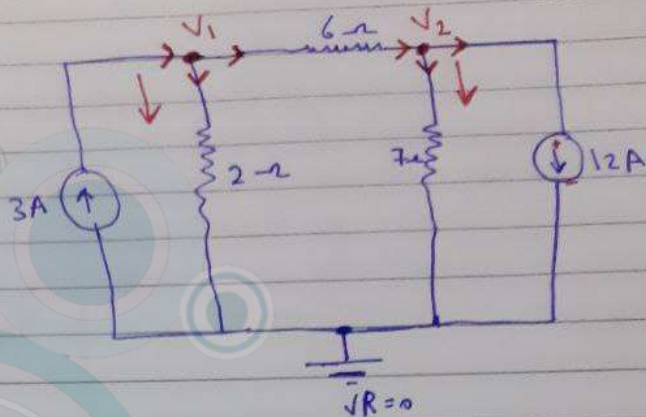

mesh analysis :-

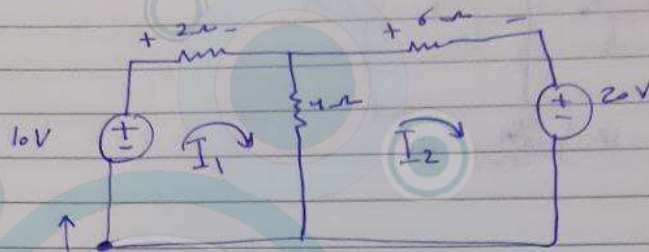

التيار I عند طريقة $\leftarrow$ polarity $\rightarrow$ الاتجاه على المقاومة (+) والآن سأل
دائماً فائدة

$$M_1 \rightarrow -10 + 2I_1 + 4(I_1 - I_2) = 0$$

$$2I_1 + 4I_1 - 4I_2 = 10$$

$$6I_1 - 4I_2 = 10$$

$$M_2 \rightarrow 6I_2 + 20 + 4(I_2 - I_1) = 0$$


دائماً +

$$-4I_1 + 10I_2 = -20$$

$$I_1 = 0.45, I_2 = -1.8$$

الآن سأل
الآن سأل
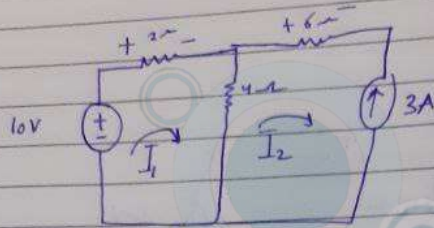
$$V_{4\Omega} = (I_1 - I_2) \times 4 = 2.25 \times 4 = 9V$$




$I_2 = -3A$ ← Super mesh لأن
التيار

$$M_1 = -10 + 2I_1 + 4(I_1 - I_2) = 0$$

$$6I_1 - 4I_2 = 10$$

$$I_2 = -3 \text{ A} \quad 6I_1 - 4(-3) = 10 \rightarrow I_1 = -\frac{1}{3} \text{ A}$$

Answer

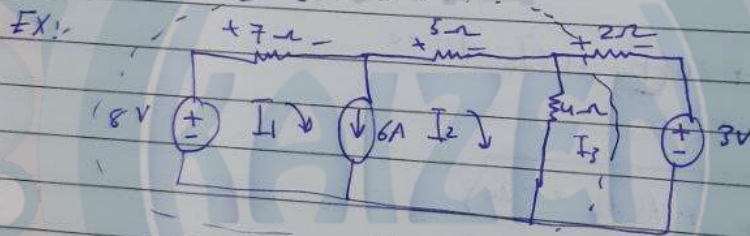

$$M_2 \Rightarrow 2I_3 + 3 + 4(I_2 - I_3) = 0$$

← Super mesh → $-8 + 7I_1 + 5I_2 + 4(I_2 - I_3) = 0$

current
من I_1, I_2, I_3

$$\Rightarrow I_1 - I_2 = 6$$

التيار في I_1 و I_2 في نفس الاتجاه
لذلك $I_1 - I_2 = 6$